

# Unipolar-to-Bipolar Level Translator Circuit, 0-V to 5-V Unipolar to $\pm 12$ -V Bipolar




Amplifiers

## Design Goals

Input		Output		Supply		
$V_{iMin}$	$V_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{CC}$	$V_{EE}$	$V_{ref}$
0 V	5 V	-12 V	+12 V	+15 V	-15 V	5 V
 
## Design Description

This design is intended to translate a small unipolar signal to a wide bipolar signal. A common application is to translate a 5-V DAC output to a  $\pm 12$ -V bipolar signal. The document provides equations needed to calculate component values for other voltage range requirements. Important error sources are covered using calculations and simulation.



## Design Notes

1. The OPA206 op amp was selected for excellent DC and AC characteristics as well as built-in robustness features. This topology works well for many different op amp selections.
2. Select 0.1% 20 ppm/°C resistors for good gain, offset accuracy, and drift.  
A calibration at room temperature can be used to minimize the gain error at room temperature, but gain drift can only be reduced by minimizing the resistor drift ( choosing resistors with  $TC \leq 20 \text{ ppm}/^\circ\text{C}$ ).
3. Place decoupling capacitors close to the device power supplies. The [OPAx206](#) data sheet provides layout suggestions, and this video on [Decoupling Capacitors](#) provides further details.

## Specifications

Parameter	Design Goal	Simulated (Without Buffered Voltage Divider)	Simulated (With Buffered Voltage Divider)
V <sub>outMin</sub>	-12 V	-11.8 V	-11.95 V
V <sub>outMax</sub>	+12 V	+11.92 V	+11.99 V
Bandwidth	50 kHz	48.5 kHz	48.5 kHz
Noise	N/A	32.9 $\mu\text{V}_{\text{RMS}}$	24.2 $\mu\text{V}_{\text{RMS}}$

## Design Steps

- Define the input and output conditions.  
For this example,  $V_{inMin} = 0\text{ V}$ ,  $V_{inMax} = 5\text{ V}$ ,  $V_{outMin} = -12\text{ V}$ ,  $V_{outMax} = 12\text{ V}$ .
- Select a reference voltage. Generate this voltage from a precision source such as a series or shunt voltage reference (for example [REF5050](#)). Typically, a power-supply voltage developed by a low dropout regulator does not have sufficient accuracy to act as a reference.  $V_{ref} = 5\text{ V}$  in this example.
- Choose a large resistance for  $R_f$ . Typical practical values range from  $50\text{ k}\Omega$  to  $1\text{ M}\Omega$ .  $R_f = 100\text{ k}\Omega$  in this example.
- Calculate gain based on the input range and output range.

$$G = \frac{V_{outMax} - V_{outMin}}{V_{inMax} - V_{inMin}} = \frac{12\text{ V} - (-12\text{ V})}{5\text{ V} - 0\text{ V}} = 4.8$$

- Calculate  $R_g$  based on  $R_f$  and signal gain.

$$R_g = \frac{R_f}{(G - 1)} = \frac{100\text{ k}\Omega}{(4.8 - 1)} = 26.31\text{ k}\Omega \quad (26.4\text{ k}\Omega \text{ standard value})$$

- Calculate the output of the voltage divider based on minimum signal. If this number is negative, use a different topology. Also, this number must be less than  $V_{ref}$  from step 2.

$$V_{div} = \frac{V_{outMin} - (V_{inMin} \times G)}{(-R_f/R_g)} = \frac{-12\text{ V} - (0\text{ V} \times 10)}{(-R_f/R_g)} = 3.168\text{ V}$$

- Calculate  $R_1$  and  $R_2$  to achieve the desired divider output. The equations used for this calculation assume that  $(R_1 \parallel R_2) = R_g/100$ , so that  $R_g \gg (R_1 \parallel R_2)$ . The reason this is done is that the voltage divider has an impact on gain. The actual gain including the voltage divider is 3.781, whereas the ideal gain was 4.8. The following equations show the algebraic rearrangement of the voltage divider equation to a ratio of  $R_1/R_2$ . This ratio is defined as  $\alpha$  and used throughout the calculation.

$$\left(\frac{R_2}{R_1 + R_2}\right)V_{ref} = V_{div} \text{ rearrange to } \frac{R_1}{R_2} = \frac{V_{ref}}{V_{div}} - 1$$

$$\alpha = \frac{R_1}{R_2} = \frac{V_{ref}}{V_{div}} - 1 = 0.583 \quad (\text{define } \alpha \text{ as } R_1/R_2, \text{ substitute } V_{ref} \text{ and } V_{div})$$

$$R_1 = \frac{R_g}{100}(\alpha + 1) = 418\ \Omega \quad (417\ \Omega \text{ standard value})$$

$$R_2 = R_1/\alpha = 714.9\ \Omega \quad (\text{or } 715\ \Omega \text{ standard value})$$

$$G_{loaded} = \frac{R_f}{R_g + (R_1 \parallel R_2)} + 1 = 4.75 \quad (\text{ideal gain was } 4.8)$$

- As an option, a buffer can be placed between the voltage divider and  $R_g$ . Doing this improves the accuracy and also eliminates the requirement that  $R_g \gg (R_1 \parallel R_2)$ . See accuracy difference in the [DC Transfer Characteristics](#) section. In this case, the value of  $R_f$  can be selected as a smaller value which improves noise. Also, the divider resistors are independent from the feedback, so any values can be used for  $R_1$  and  $R_2$  as selected and shown in step 7, provided that the ratio is correct. This allows selection of larger values of  $R_1$  and  $R_2$  to minimize divider current.
- A filter capacitor can be used across  $R_f$  to limit bandwidth and minimize noise ( $f_c = 50\text{ kHz}$  in this example).

$$C_f = \frac{1}{2\pi R_f f_c} = \frac{1}{2\pi(100\text{ k}\Omega)(50\text{ kHz})} = 31.8\text{ pF} \quad (33\text{ pF standard value})$$

## DC Transfer Characteristics

The following images show the DC Transfer function for the standard and buffered version of the circuit. Note that the buffered version is more accurate. Also note that the values selected in the buffered version, use the same ratios, but the magnitudes are adjusted. The buffered version decreased the feedback network impedance for better noise, and increased the divider network for better power dissipation. Note that the inaccuracy in the transfer function can be accounted for with a simple calibration (see the [Calibration](#) video).

 


Figure 1-1. DC Transfer Characteristics for Unbuffered Circuit

 


Figure 1-2. DC Transfer Characteristics for Buffered Circuit

## AC Transfer Characteristics

The capacitor  $C_f$  sets the cutoff frequency to 100 kHz. This causes the gain of the amplifier to roll-off until gain is 1 V/V or 0 dB. At higher frequency the bandwidth limitations of the amplifier causes gain to roll-off again. The expected bandwidth of 50 kHz compares well to the simulated 48.5 kHz. Additional detail on bandwidth limitations are given in the [Bandwidth](#) video series.

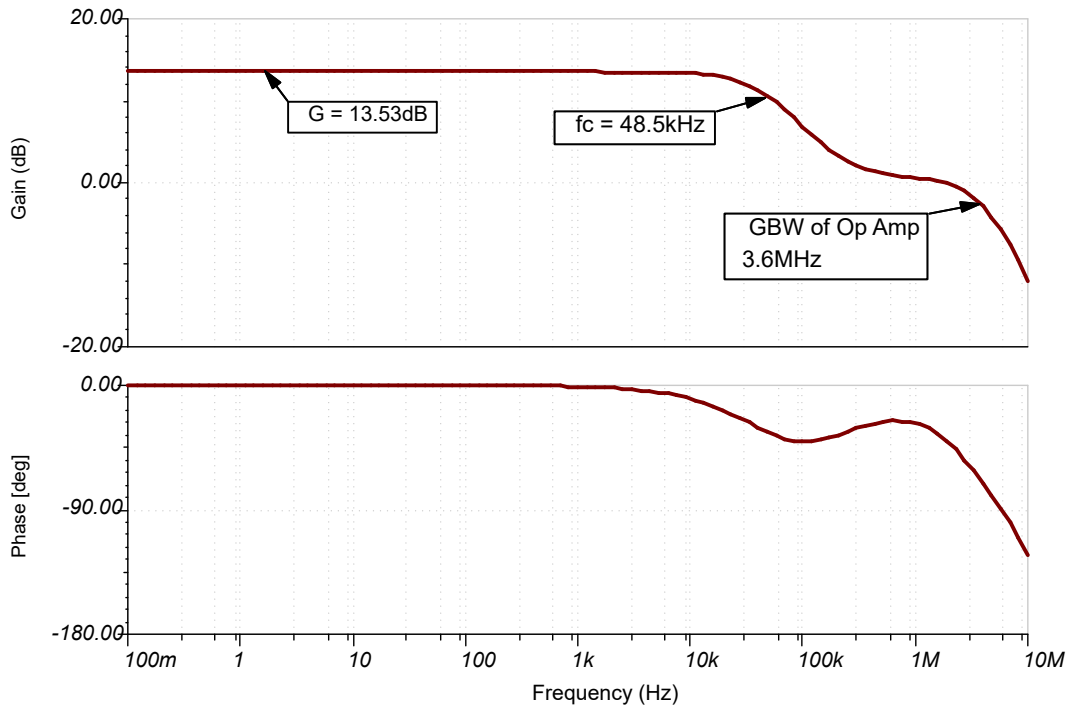


Figure 1-3. AC Transfer Characteristics for Level Translator

## Noise Simulation

Total noise is approximately  $32.9 \mu\text{V}_{\text{RMS}}$ . Peak-to-peak is approximately  $6 \times \text{RMS} = 197 \mu\text{V}_{\text{pp}}$ . For more information on noise analysis and optimization see the [Noise](#) video series. Note that the noise of the buffered version is lower because the voltage divider uses lower resistor values which minimizes total noise.


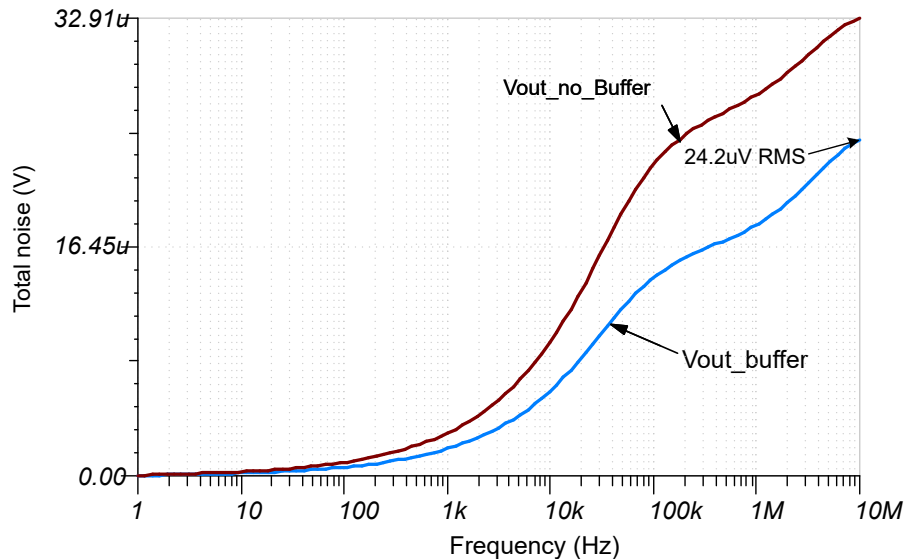
 


Figure 1-4. Total RMS Noise for Level Translator

## Stability

This circuit is stable for capacitive loads from 0 pF to 120 pF. The analysis below shows 48.2° of phase margin for a 120-pF load (45°C and better is considered stable). For more information on stability see the [Stability](#) video series.

 

**Figure 1-5. Stability of Level Translator Circuit**

## Design Featured Devices and Alternative Parts

This design works with most amplifiers that accept high-voltage  $\pm 15\text{-V}$  supplies. Depending on the application the key parameters can be different. The following table shows three different options representing different categories of devices. Package-trimmed devices have good offset and offset drift by adjusting internal device resistors, zero-drift devices use an internal calibration to reduce offset and drift, and general-purpose are optimized for best cost. When using a zero-drift option, a best practice is to keep the total feedback impedance less than  $10\text{ k}\Omega$  ( $R_f \parallel (R_g + R_1 \parallel R_2) < 10\text{ k}\Omega$ ). This is recommended to avoid translating bias current into offset voltage. Click on the *other possible devices* link for a list of other options in the same category.

Device	Key Features	Other Possible Devices
<a href="#">OPA206</a>	36-V supply, 3.6-MHz bandwidth, low noise ( $8\text{ nV}/\sqrt{\text{Hz}}$ ), rail-to-rail output, 240- $\mu\text{A}$ supply current, low offset $25\text{ }\mu\text{V}$ , $0.5\text{ }\mu\text{V}/^\circ\text{C}$ , e-trim™ op amp, with super-beta inputs and OVP	<a href="#">36-V e-trim™</a>
<a href="#">OPA182</a>	36-V supply, 2-MHz bandwidth, rail-to-rail input to -V/Out, low noise ( $8.8\text{ nV}/\sqrt{\text{Hz}}$ ), low offset $25\text{ }\mu\text{V}$ , $0.03\text{ }\mu\text{V}/^\circ\text{C}$ , zero-drift amplifier	<a href="#">36-V zero-drift</a>
<a href="#">LM358B</a>	36-V supply, 1.2-MHz bandwidth, rail-to-rail input to -V, general-purpose	<a href="#">36-V cost-optimized</a>

## Design References

1. See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.
2. See circuit TINA SPICE simulation file [sbomcf8](#).
3. See circuit PSPICE simulation file [sbomcf7](#).
4. For more information on many op-amp topics including common-mode range, output swing, bandwidth, and how to drive an ADC please visit [TI Precision Labs](#).
5. See the [OPAx206 Input-Overvoltage-Protected, 4- \$\mu\text{V}\$ , 0.08- \$\mu\text{V}/^\circ\text{C}\$ , Low-Power Super Beta, e-trim™ Op Amps](#) data sheet for layout guidelines.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated