

Small-Size INA500x Versus Discrete Difference Amps



Many designers often build discrete difference amplifiers using an op amp and discrete components to fit a design budget. These discrete designs tend to have more error and take more printed circuit board (PCB) space than the integrated counterparts. However, integrated difference amplifiers possibly do not meet the budgetary requirements of extremely cost-optimized products, nor does every design need the precision and accuracy that comes with the vast majority of integrated difference amplifiers. **INA500x** re-defines the difference amplifier landscape by offering an integrated design within the price range of a discrete design as shown in [Table 1](#). The gain used in [Table 1](#) is 0.5. The INA500x is able to achieve a lower gain error and higher common-mode rejection ratio (CMRR) than the discrete design through the use of precision matched integrated resistors.

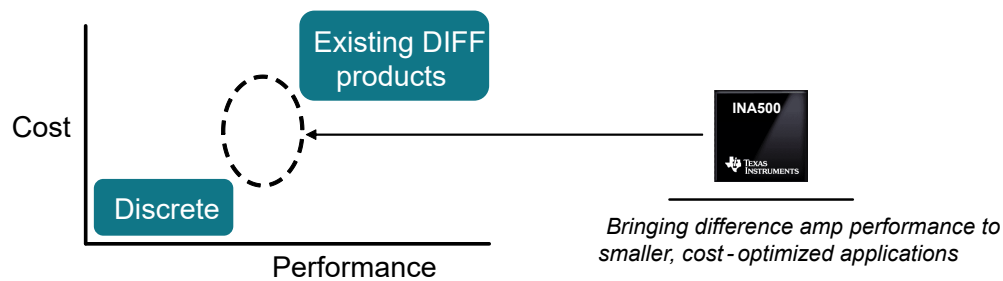


Figure 1. Difference Amplifier Landscape

Table 1. Difference Amplifier Key Specification Comparison

Key Specifications	Discrete	INA500	Existing Diff Amps
Gain error (max)	1.02 %	0.05 %	< 0.05 %
Gain error drift (max)	±200ppm/°C	±1ppm/°C	±0.5ppm/°C
CMRR (min)	32dB	77dB	> 80dB
Offset (max)	6mV	2.7mV	< 250uV
Web price ⁽¹⁾	\$ 0.12 ⁽²⁾	\$ 0.14	> \$ 0.88

(1) Web price as of April 2024

(2) Approximate price based on online price of general-purpose op amp (TLV6001) + 1% discrete resistors

In addition to the performance benefits, the INA500x also extends TI's difference amplifier package lineup with new smaller packages, such as the X2SON (DTQ), that help reduce the amount of PCB space compared to discrete designs by up to 67%, as shown in [Figure 2](#). This makes the INA500x the industries smallest difference amplifier, even compared to other integrated designs. The discrete design uses a typical layout with a resistor network and decoupling capacitors. All resistors and capacitors are 0402 package sized.

Figure 2 shows the PCB layout comparison of a discrete design using SOT-23-70 (left) vs INA500x in the SOT-23-SC70 (middle) vs INA500x in the X2SON (right).

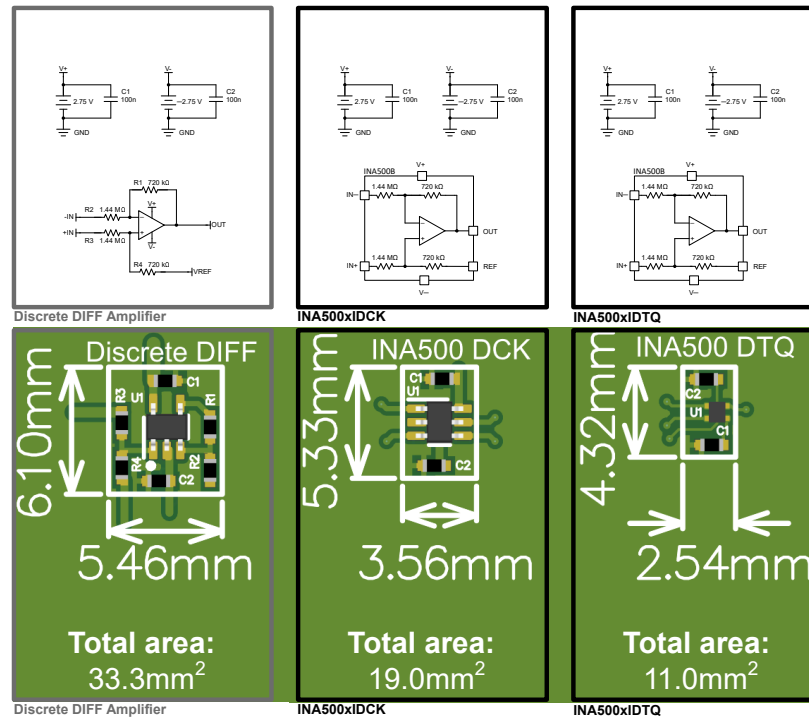


Figure 2. PCB Layout Comparison of Three Designs

Learn more about how INA500x can help reduce space and improve performance while simplifying the BOM, and start your evaluation with the following content:

Learn More

- Texas Instruments, [INA500 Cost and Size Optimized, Low Power, 1.7V to 5.5V Difference Amplifier with >1MΩ Input Impedance](#) data sheet.

Evaluate the Design

- Leverage existing [simulation models available in TINA-TI or PSpice for TI](#)

Generic Part Number	Orderable Part Number	Gain Option	Package
INA500	INA500AIDBVR	1	2.9 x 2.8mm (DBV)
	INA500AIDCKR	1	2.1 x 1.25mm (DCK)
	INA500AIDTQR	1	1.0 x 0.8mm (DTQ)
	INA500BIDBVR	0.5	2.9 x 2.8mm (DBV)
	INA500BIDCKR	0.5	2.1 x 1.25mm (DCK)
	INA500BIDTQR	0.5	1.0 x 0.8mm (DTQ)
	INA500CIDBVR	0.25	2.9 x 2.8mm (DBV)
	INA500CIDCKR	0.25	2.1 x 1.25mm (DCK)
	INA500CIDTQR	0.25	1.0 x 0.8mm (DTQ)

For additional assistance, ask questions to TI engineers on the [TI E2E™ Amplifiers Support Forum](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated