

Quickly Detecting Overcurrent Faults With Low-Side Current Shunt Measurement Required for SiC or GaN Switches



Rachel Scheller, Charles Barsh

High-Speed Amplifiers

As the electrification of automobiles rapidly increases, more advanced systems are integrated into vehicles. These electrified vehicles contain sensitive GaN and SiC switches that are susceptible to overcurrent conditions. Therefore, there is a need to implement a current-monitoring circuit that must react to peak overcurrent conditions, and in many cases, shut down in less than 1µs to prevent damage to the switches. Figure 1 illustrates how this need is addressed with a minimal delay time using a high-speed amplifier and comparator-based current-shunt monitoring circuit.

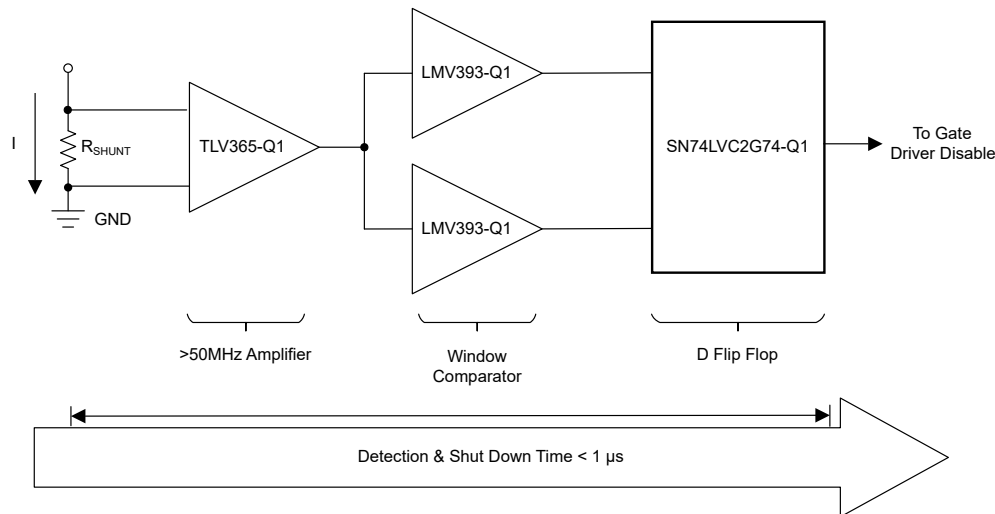


Figure 1. Typical Current-Detection Circuit

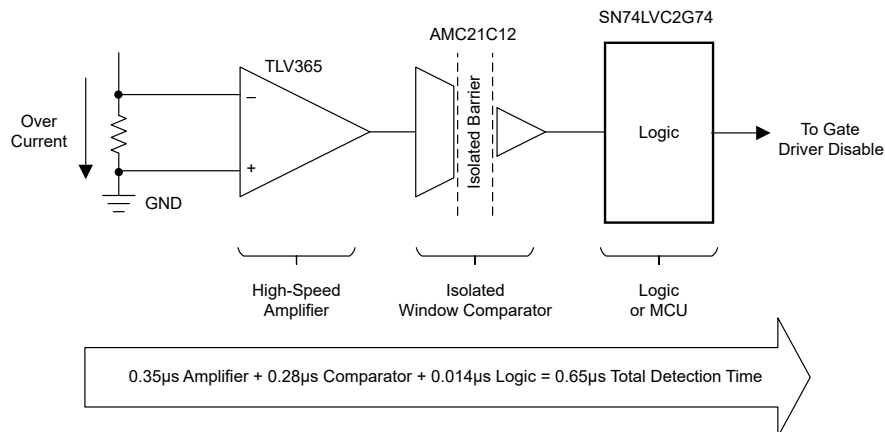


Figure 2. Typical Current-Detection Circuit With Isolation

What is a High-Speed Amplifier and Why Use One?

The propagation delay of a circuit varies drastically based upon the components selected. If a DC/DC converter uses average current control for power factor correction, for example, then a slower amplifier can be used. However, if there is a need to detect peak current, or if the system needs to react and shutdown in less than 1 μ s, then a high-bandwidth amplifier is required. In [Figure 3](#), the current waveforms of peak detection and average detection are overlaid. The reason using a higher-bandwidth amplifier for peak detection is necessary is the fact that the transient current spikes occur very quickly – when measuring average current, these spikes remain undetected.

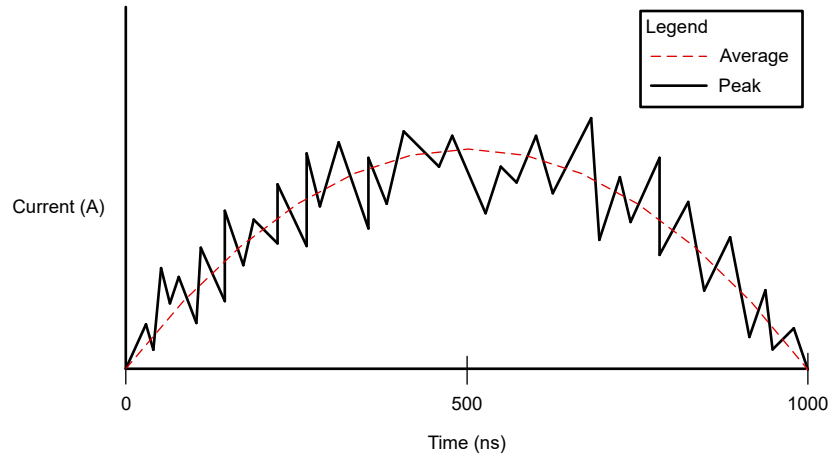


Figure 3. Average Current vs Peak Current Waveforms

Newer implementations of onboard chargers, DC/DC converters, and traction inverters take advantage of the reduced power consumption and faster switching frequencies provided with [Gallium Nitride and Silicon Carbide](#) switches. Many GaN switches are susceptible to failure from current spikes over 54A and at a duration of as little as 1 μ s. In [Figure 4](#), the rise times of a 10MHz and a 50MHz op amp are compared, showing that a high-bandwidth 50MHz op amp reduces propagation delay by 0.8 μ s. This allows for ample time to detect and respond to an overcurrent condition.

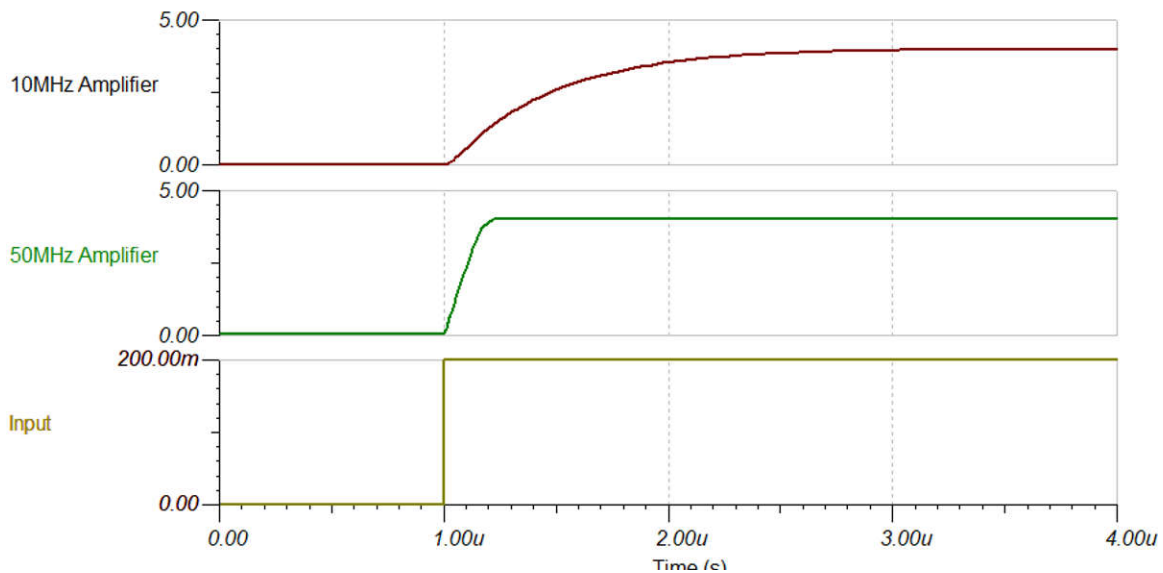


Figure 4. 10MHz Ideal Rise Time vs 50MHz Ideal Rise Time

To achieve detection and shutdown in less than 1µs, allocate 35% of the total response time to the amplification stage. If the amplifier requires a gain of 1V/V, then the required bandwidth of the amplifier is 1MHz; however, most shunt-based current monitoring circuits require gains in the range of 50V/V to reduce the power consumption of the shunt resistor. To achieve this level of gain, an amplifier with at least 50MHz is required, as Equation 1 demonstrates.

$$T_{\text{response}} = 35\% \times 1\mu\text{s} = 0.35\mu\text{s}$$

$$\text{Bandwidth}_{(\text{Hz})} = \frac{0.35^{[1]}}{T_{\text{response}}} = \frac{0.35^{[1]}}{0.35\mu\text{s}} = 1\text{MHz}$$

$$\text{GBW} = \text{Gain} \times \text{Bandwidth} = 50\frac{\text{V}}{\text{V}} \times 1\text{MHz} = 50\text{MHz} \tag{1}$$

[1] 0.35 is a constant value used to approximate bandwidth.

This is related to the time required for a capacitor to charge from 10% to 90%.

See the [Op Amp Slew Rate – TI Precision Labs](#) video for more details.

Texas Instruments (TI) offers a variety of amplifiers for different system requirements. Figure 5 is a graph demonstrating rise times of several amplifiers with increasing bandwidth, and Table 1 is a comparison chart of the rise time.

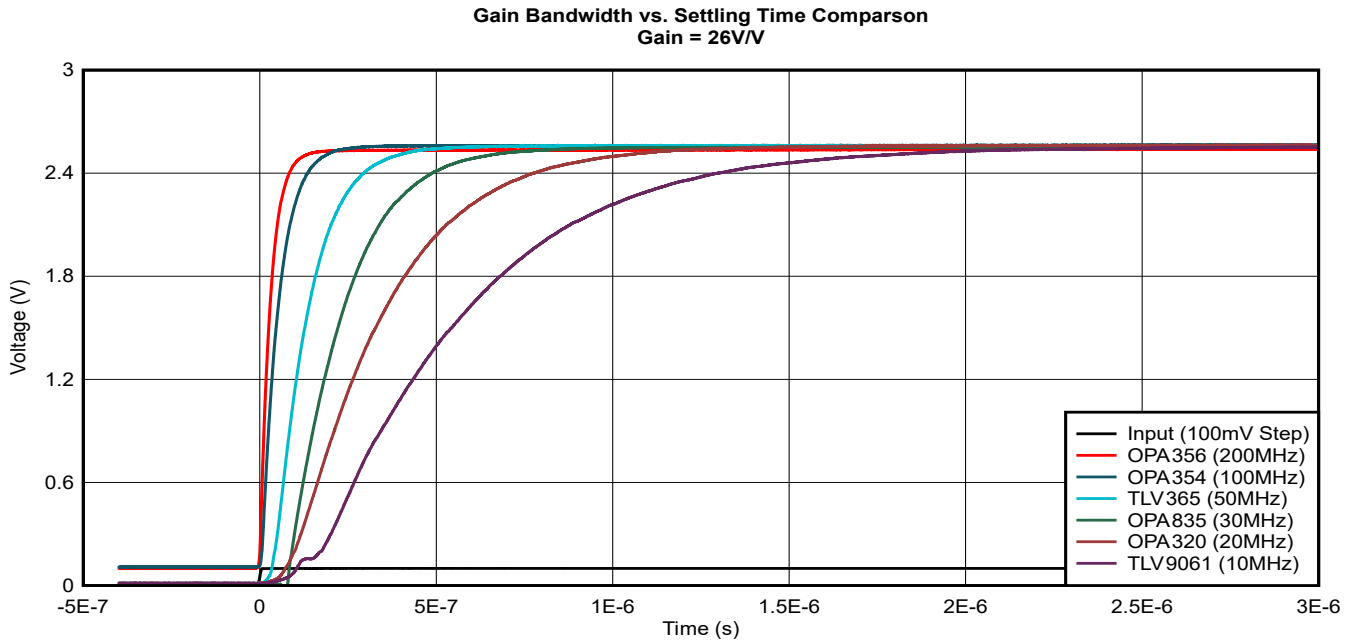


Figure 5. Rise Times of Several TI Amplifiers

Table 1. Rise Time Comparison Chart

Device	Gain Bandwidth	Change in Rise Time
TLV9061	10MHz	2000ns
OPA320	20MHz	1100ns
OPA835	30MHz	715ns
TLV365	50MHz	475ns
OPA354	100MHz	225ns
OPA355	200MHz	150ns

Some designers choose to cascade two or more lower-bandwidth amplifiers with different amplification stages to achieve the same amplification at a reduced cost. Using multiple lower-bandwidth amplifiers adds additional propagation delay and requires more space on the circuit board. High-bandwidth amplifiers historically were perceived to be costlier alternatives; however, with modern manufacturing capabilities at TI, these newer devices are able to be priced more competitively and are comparable to using multiple lower-bandwidth amplifiers.

Single Shunt versus Multi-shunt Current Sensing

A further way to reduce board space and potentially reduce cost is to implement a single shunt as opposed to using multiple shunts in a system. For a system in which multiple average current measurements are taken, utilizing a higher-bandwidth amplifier and tying these measurements together can reduce the number of amplifiers required. However, there are cases in which a multi-shunt configuration is required. For example, if measuring the individual current phases in a three-phase traction inverter is desired, then implement multiple high-bandwidth amplifiers to measure the peak current faster. Figure 6 and Figure 7 show typical setups of a single-shunt traction inverter and multi-shunt traction inverter.

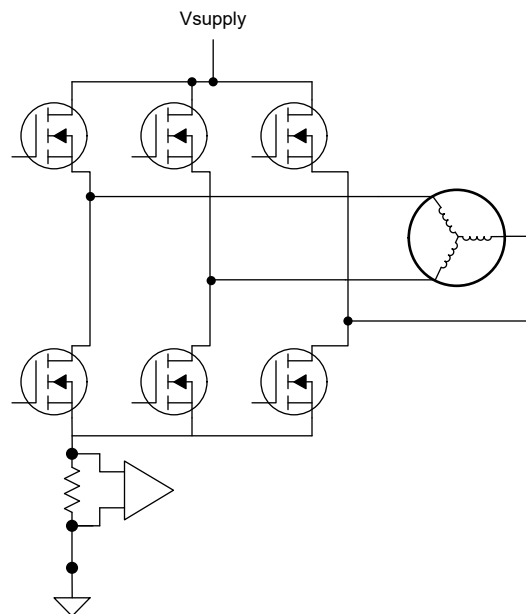


Figure 6. Single Shunt Implementation; Three Phases Tied Together

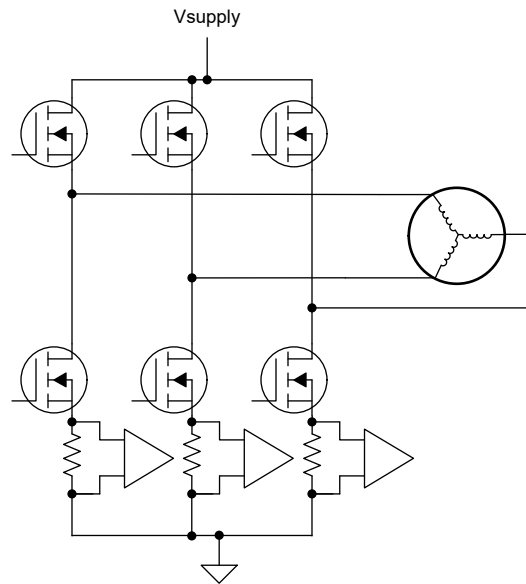


Figure 7. Multiple Shunt Implementation; Each Phase Current Measured Separately

Conclusion

Detecting and responding to overcurrent conditions in electrified vehicles in Sub-1 μ s is becoming increasingly important as more efficient GaN and SiC switches are implemented in these systems. When designing a system, choosing the right amplifier can help save board space, money, and reduce delay times. See TI's broad portfolio of automotive-qualified high-speed amplifiers that include a wide range of bandwidths and precision.

Table 2. Recommended Devices for Automotive Current-Sensing Applications

Device	Channel Count	Supply Voltage Range (V)	Gain Bandwidth Product (MHz)	Slew Rate (V/ μ s)	Minimum Stable Gain (V/V)
TLV365-Q1	1	2.2–5.5	50	27	1
OPA607-Q1	1	2.2–5.5	50	24	> 6
OPA2607-Q1	2	2.2–5.5	50	24	> 6
OPA354A-Q1	1	2.2–5.5	100	150	1
OPA2354A-Q1	2	2.2–5.5	100	150	1
OPA4354-Q1	4	2.2–5.5	100	150	1
OPA2863-Q1	2	2.7–12.6	50	105	1

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated