

Simple, high-performance, isolated power supply design with PSR (no-opto) flyback

Marshall Beck

July 2021

Agenda

- Isolation in industrial applications
- PSR flyback:
 - PSR vs conventional flyback, control/operation, and TI offerings
- PSR flyback simple design flow
- TI supporting content on PSR flyback design



Industrial – Isolation everywhere



Wide V_{IN}
24 VDC (15-42V)
PoE (36-57V)

Isolation

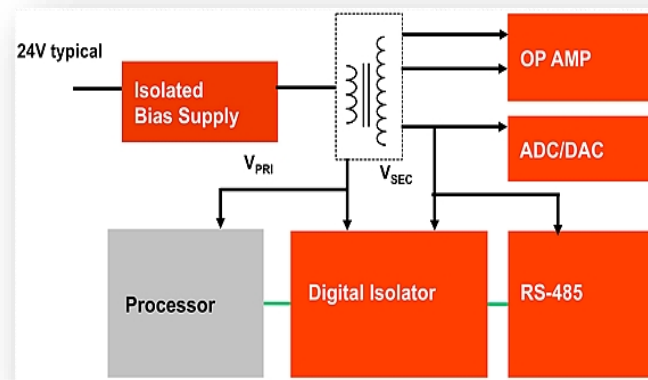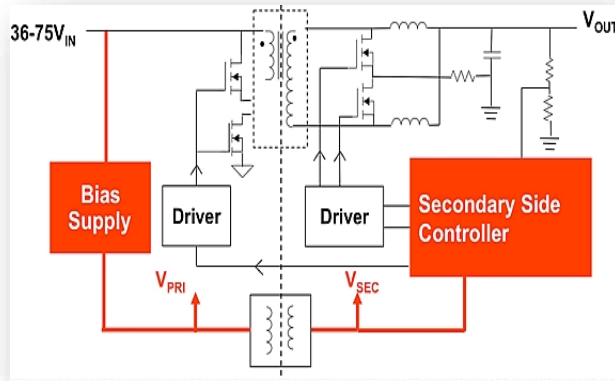IP Phone
IP Surveillance
Sensors
PLC
E-Meter
Solar
Telecom



Where to use isolation?

Isolation

- **Safety**


- Mandatory by safety standards to isolate the user from the hazardous voltage of a power supply. Protect user from ESD and surge events.
- Typical applications: IP camera, solar inverter, factory automation – field site

- **Break ground loop, mitigate noise**

- Installed to break the ground loop interference for noise-sensitive applications
- Typical applications : PLCs, solar inverters, building automation (ie. RS232/485, etc.)


- **Inversion, level shifting & multiple rails**

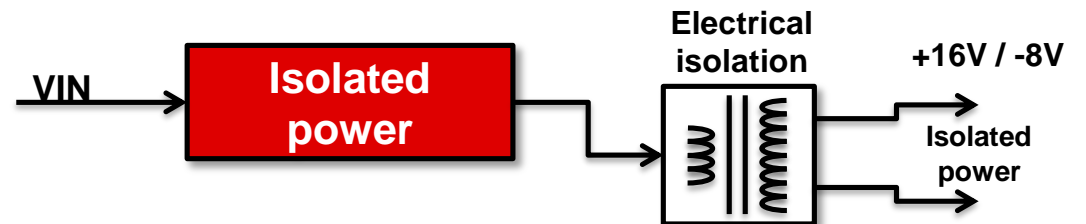- Isolated output voltage can be conveniently configured as multiple isolated outputs, as a negative voltage rail or as a level-shifted voltage rail.
- Typical applications : test and measurement, medical, e-bike, HVAC, motor drives



Isolated power – Simplify signal integrity!

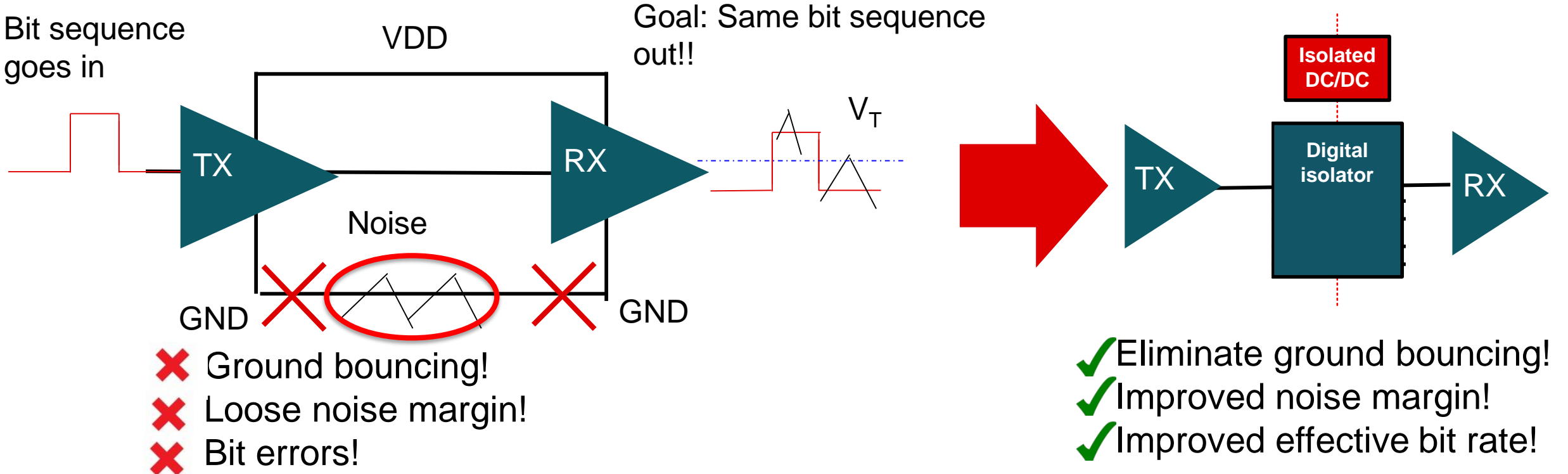
- Typical communication protocols: **RS422/485, RS232, RS285, LVDS, Ethernet**
- Long cabling causes transient voltage differences and **possible errors!**
- **Solution: Isolate the TX and RX power!**




Isolated power – Simplify your power tree!

- Isolated output voltages can be conveniently configured as **multiple isolated outputs**, as a **negative voltage rail** or as a **level-shifted voltage rail**.
- Example use cases:** Positive/negative rails for differential digital communications, op-amp, isolated bias supply for gate driver


Differential RX/TX Power

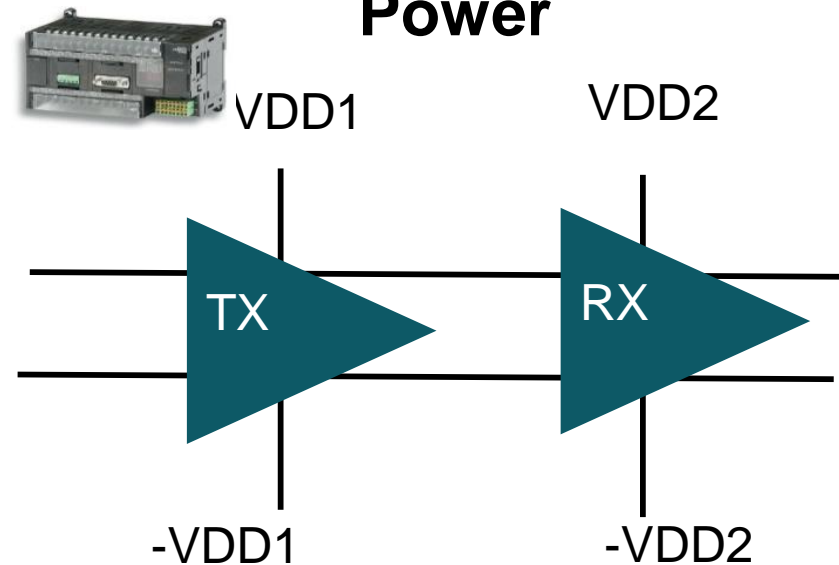


Signal conditioning (Op-amp, ADC/DAC)

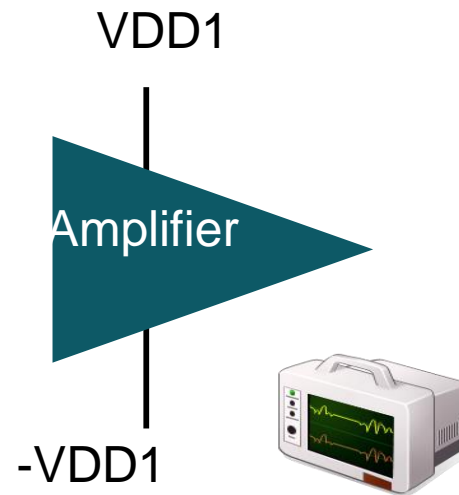

Isolated bias supply

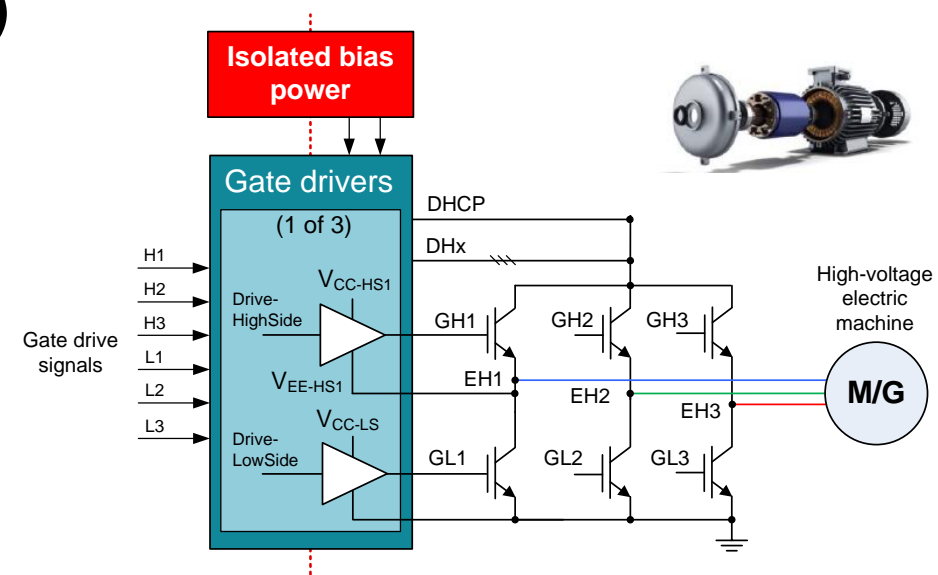

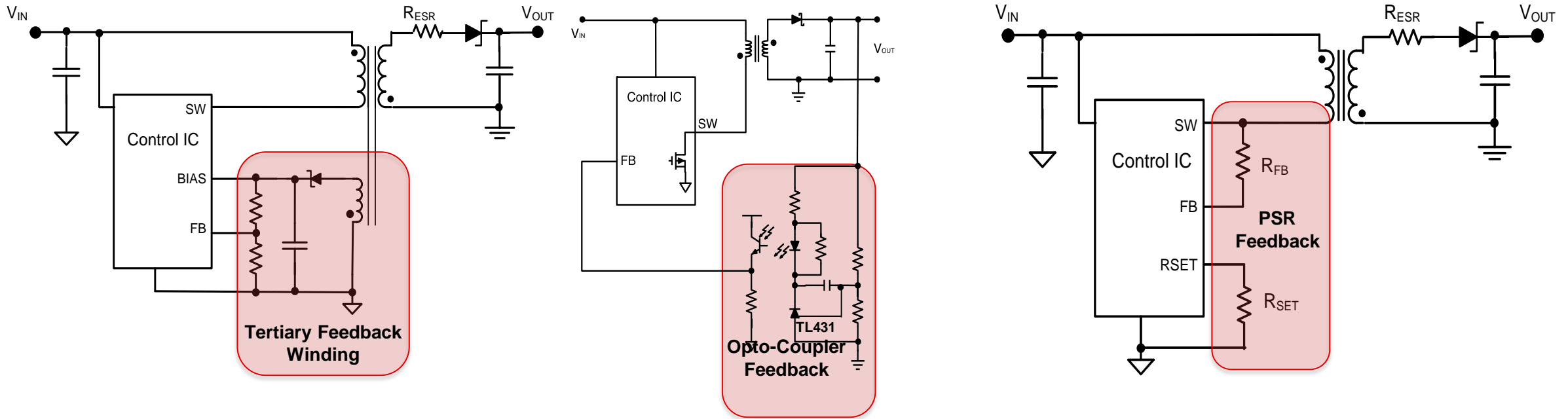Conventional PSR flyback vs. Aux-less PSR flyback




Conventional PSR flyback advantages:

- Increased design flexibility with external compensation and tertiary winding or opto-coupler feedback
- Operates in CCM (fixed frequency) or DCM mode


Aux-less PSR flyback advantages:

- Eliminates opto-coupler or tertiary winding with only one component crossing isolation barrier
- Extremely tight load regulation ($\pm 1\%$)
- Operates in DCM or Boundary Mode
- DCM and zero current switching enables high efficiency

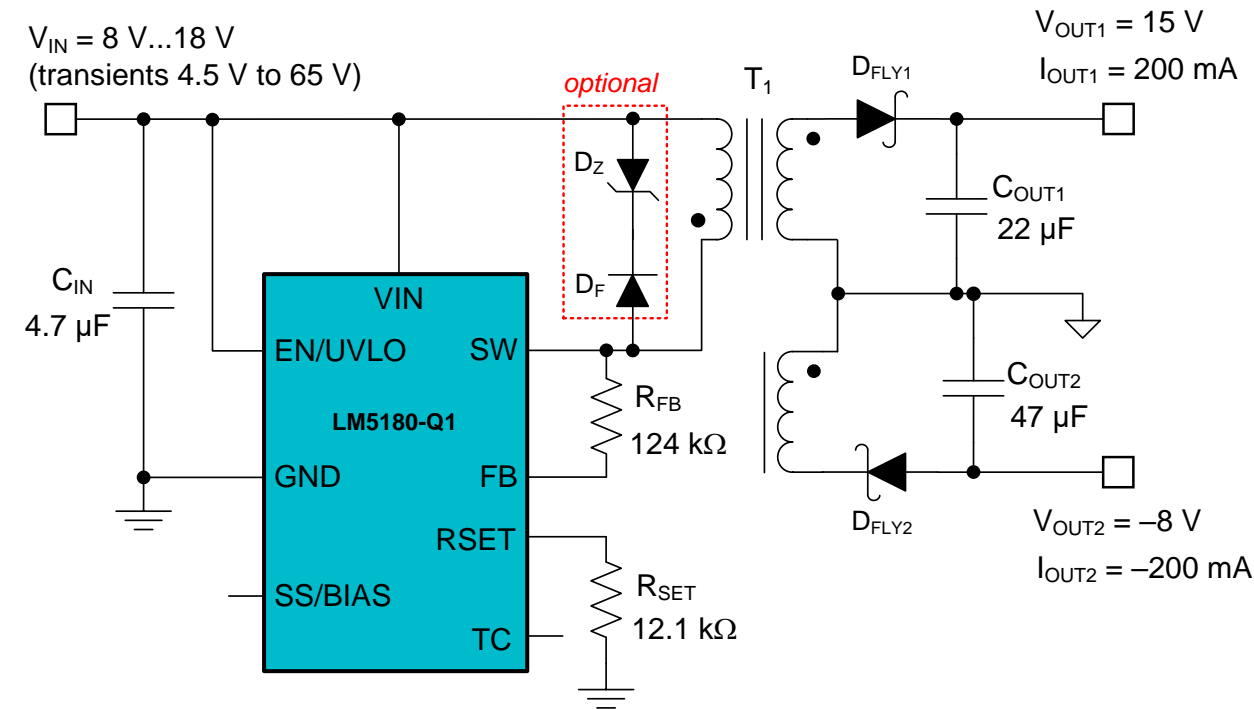
PSR flyback converter – no opto, no aux winding



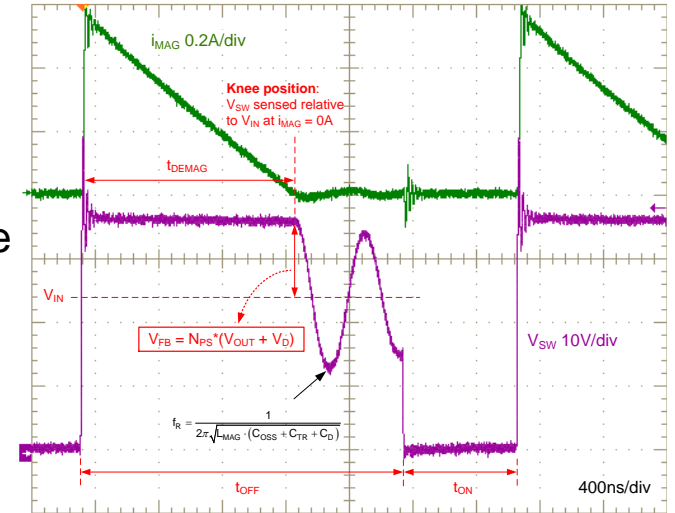PSR sensing – output voltage sampled using the primary-side SW voltage



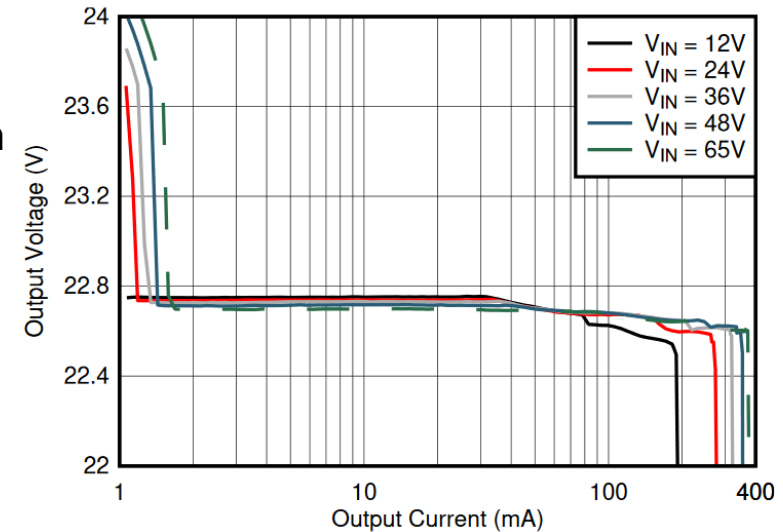Load regulation – sum of V_{OUT1} and V_{OUT2} with symmetrical loading



- No aux winding → easier magnetic design
- No optocoupler → higher temperature operation, longer lifetime
- Accurate output regulation → ideal for SiC gate drivers
- Leakage inductance tolerant → manage reinforced isolation creepage spacing

PSR flyback DC/DC family overview

PSR Flyback DC/DC Converter	Input Voltage Range	Peak Switch Current	Maximum Load Current $V_{OUT} = 12\text{ V}$, $N_{PS} = 1$, $V_{IN} = 13.5\text{ V}$	Package Option
<u>LM5181</u>	4.5 V to 65 V	0.75 A	180 mA	WSO8
<u>LM5180</u>	4.5 V to 65 V	1.5 A	360 mA	WSO8
<u>LM25180</u>	4.5 V to 42 V	1.5 A	360 mA	WSO8
<u>LM25183</u>	4.5 V to 42 V	2.5 A	600 mA	WSO8
<u>LM25184</u>	4.5 V to 42 V	4.1 A	1 A	WSO8

LM25183-Q1/LM25184-Q1



Highest power density 42V, 2.5A/4A primary side regulated (PSR) flyback converter with 65V integrated power MOSFET

Features



- Highest Power Density 42V PSR with tightest Output Regulation in its class
- **65V, 2.5A/4A internal power MOSFET**
- **4.5V–42V wide V_{IN} range** (abs max 45V)
 - 3.5V minimum V_{IN} after start-up
- **V_{OUT} accuracy $\pm 1\%$ achievable**
 - $V_{IN} = 6V-42V$, $V_{OUT} = 5V$, 2% load to full load
 - $T_A = -40^{\circ}C$ to $125^{\circ}C$
- **Boundary mode**, quasi-resonant operation
- Internal loop compensation, adjustable input UVLO
- External V_{CC} bias option for improved efficiency
- Adjustable or fixed internal 6ms soft-start
- Optional V_{OUT} temperature compensation
- **4 mm × 4 mm WSON-8** WF package, 0.8mm pitch
- **AEC-Q100 grade 1** \Rightarrow $125^{\circ}C$ operating ambient range

Applications


- **Factory automation, PLC**
- **Motor drive, telcom, solar, IP**

Benefits

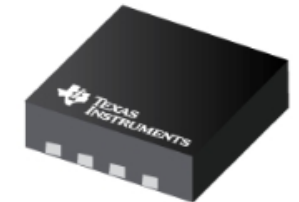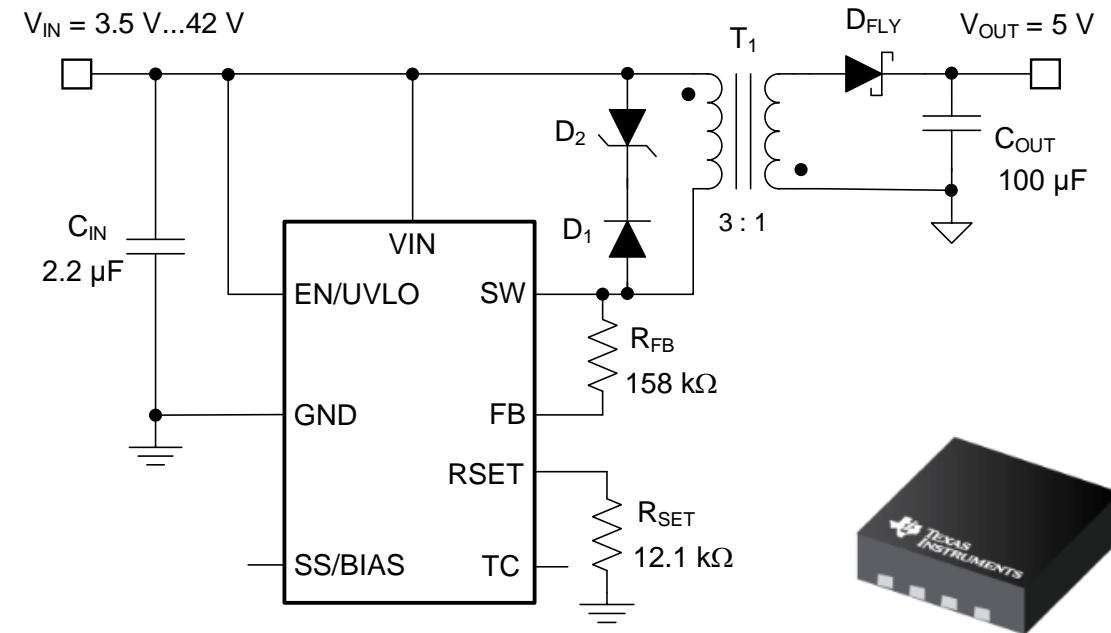- No opto-coupler or transformer auxiliary winding needed
- Accurate V_{OUT} regulation performance with sensing at zero current
- Low I_Q operation and external BIAS rail option enable high efficiency at light loads



LM25184 performance curves

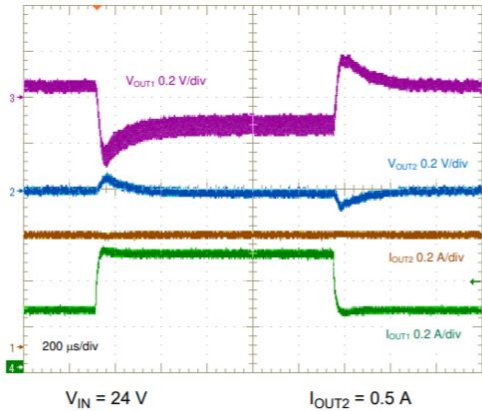

Modest F_{sw} enables good transient performance and small magnetics


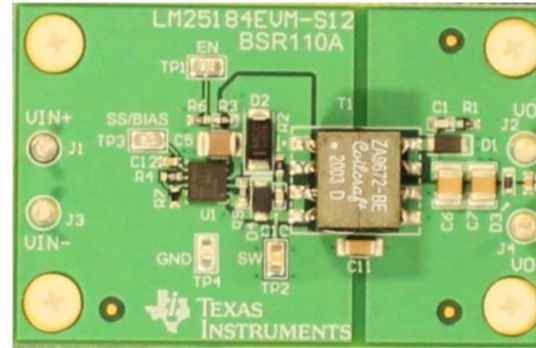


Figure 2. LM25184 EVM (Top Side), 56 mm × 36 mm

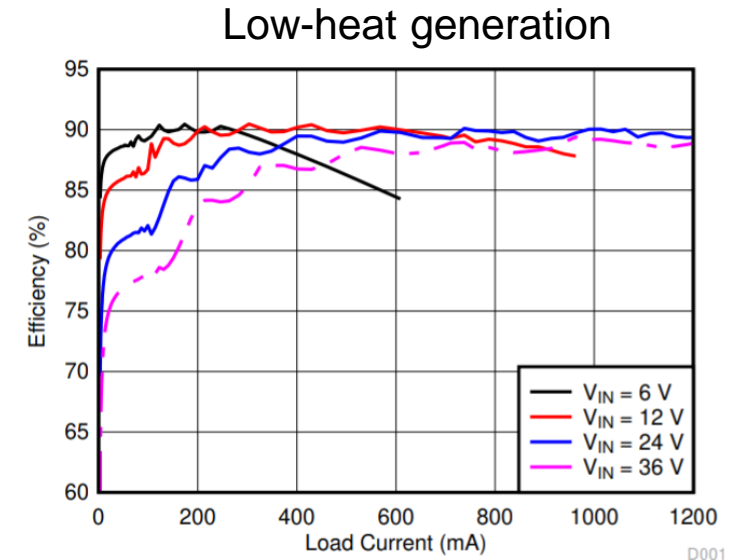

Typical Efficiency, $V_{OUT} = 12 V$

Figure 8-25. Positive Output Load Transient, 0.25 A to 0.5 A


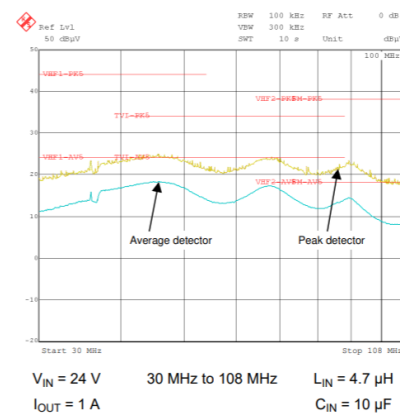
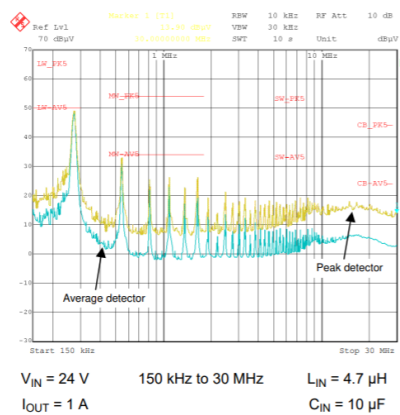



Figure 8-14. CISPR 25 Class 5 Conducted EMI Plot Figure 8-15. CISPR 25 Class 5 Conducted EMI Plot

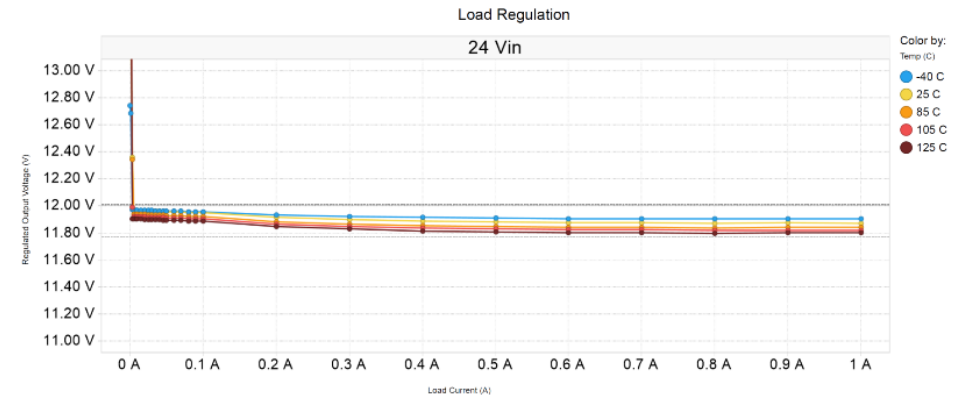

<1.7% variance from -40degC to 125degC

Passes stringent EMC standards with only differential filtering

TI's simple design flow

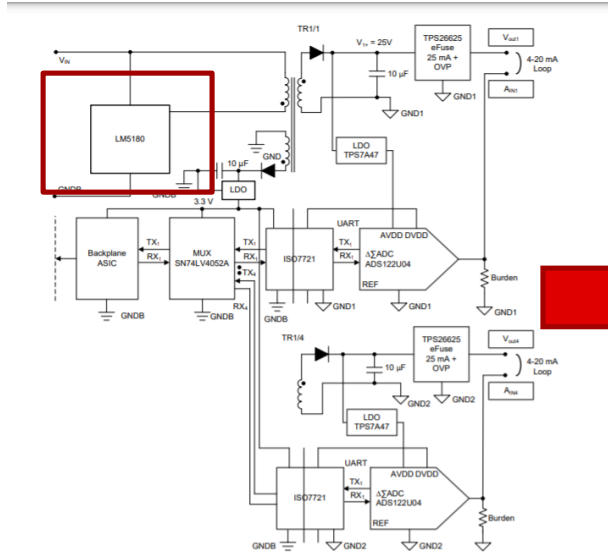

LM25183/4-Q1 PSR Flyback Converter Design Tool

Step 1: Operating Specifications

- Input Voltage - Min, V_{in-min} : 9 V
- Input Voltage - Nom, V_{in-nom} : 13.5 V
- Input Voltage - Max, V_{in-max} : 42 V
- Step-Up Output or Dual Output: none
- Output Voltage, V_{OUT} : 12 V
- Rated Output Current, I_{OUT} : 0.8 A

Step 2: Flyback Transformer

- Magnetizing Inductance, L_{mag} : 6.7 μ H
- Magnetizing Inductance, Loss: 7 μ H
- Primary Winding DCR: 40 m Ω
- Secondary Winding DCR: 48 m Ω
- Pri-Sec Leakage Inductance: 75 nH
- Transformer Turns Ratio, $N_1:N_2$: 1:1
- Diode Max Rev Voltage (Spkts Not Included): 54 V
- Diode Cpk at V_{in-max} : 37.3 nS
- Max Output Current at V_{in-max} : 0.84 A

Step 3: Input & Output Capacitors



- Minimum Input Capacitance: 4.1 μ F
- Input Capacitance, C_{in} : 10 μ F
- Input Capacitor ESR: 3 m Ω
- Resonant Input Voltage Ripple: 157 mV \sqrt{kHz}
- Minimum Output Capacitance: 25 μ F
- Output Capacitance, C_{out} : 47 μ F
- Output Capacitor ESR: 3 m Ω
- Resonant Output Voltage Ripple: 34 mV \sqrt{kHz}

Step 4: Feedback, Soft-start, TC, UVLO

- Recommended Feedback Resistor: 122.5 k Ω
- Selected Feedback Resistor, R_{FB} : 121 k Ω
- Soft-Start Time: 38 μ s
- Soft-Start Time: 47 μ s
- Soft-Start Capacitance, C_{SS} : 47 nF
- VOUT Thermal Compensation: none
- Node Voltage Drop Thermal Coefficient: 12.5 mV/C
- Thermal Compensation Resistor, R_{TC} : 243 k Ω
- Input UVLO Configuration: none
- Input UVLO Turn-On Threshold: 9 V
- Input UVLO Turn-Off Threshold: 4.5 V
- Upper UVLO Resistor, R_{UVLO} : 593 k Ω
- Lower UVLO Resistor, R_{LUVLO} : 65.6 k Ω

Step 5: Power Losses & Thermals

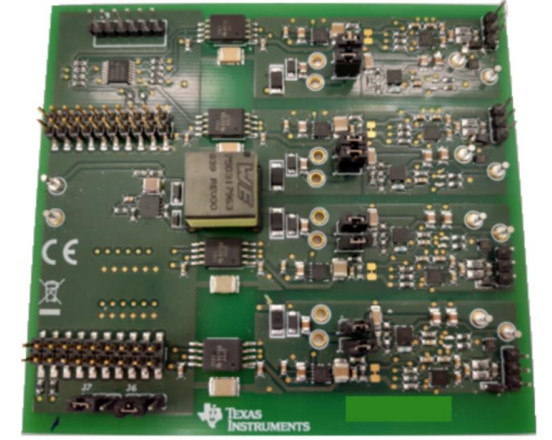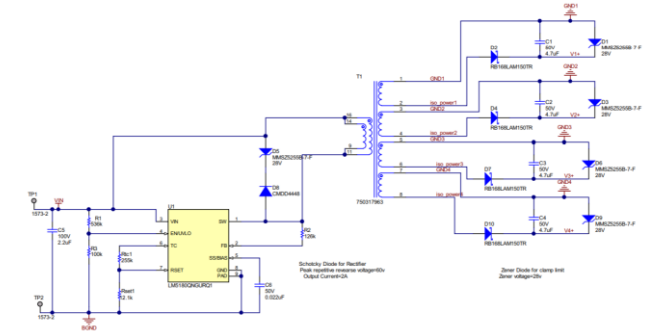- Diode Voltage Drop, $V_{D(on)}$: 0.25 V
- Flyback Diode Voltage Drop, $V_{D(on)}$: 0.4 V
- Estimated Thermal Impedance, θ_{JA} : 17 C/W
- Ambient Temperature, T_a : 25 C
- LM25183/4 Power Dissipation at Full Load, P_D : 350 mW
- LM25183/4 Junction Temperature at Full Load, T_J : 52 C



Design calculator tool

Input power conditions

Step 1: Operating Specifications LM25183


Input Voltage - Min, $V_{IN(min)}$	15 V
Input Voltage - Nom, $V_{IN(nom)}$	24 V
Input Voltage - Max, $V_{IN(max)}$	42 V
Single Output or Dual Outputs	DUAL
Output Voltage, V_{OUT1}	24 V
Rated Output Current, I_{OUT1}	0.1 A
Output Voltage, V_{OUT2}	24 V
Rated Output Current, I_{OUT2}	0.1 A

Input xfm spec



Step 2: Flyback Transformer

Minimum Magnetizing Inductance	18.2 μ H
Magnetizing Inductance, L_{MAG}	22 μ H
Primary Winding DCR	40 m Ω
Secondary Winding #1 DCR	40 m Ω
Secondary Winding #2 DCR	100 m Ω
Pri-Sec Leakage Inductance	75 nH
Turns Ratio, PRI : SEC1	1:1
Turns Ratio, SEC1 : SEC2	1
Max Output Power at $V_{IN(min)}$	10.44 W
Duty Cycle at $V_{IN(min)}$	61.9 %

Get SCH and BOM

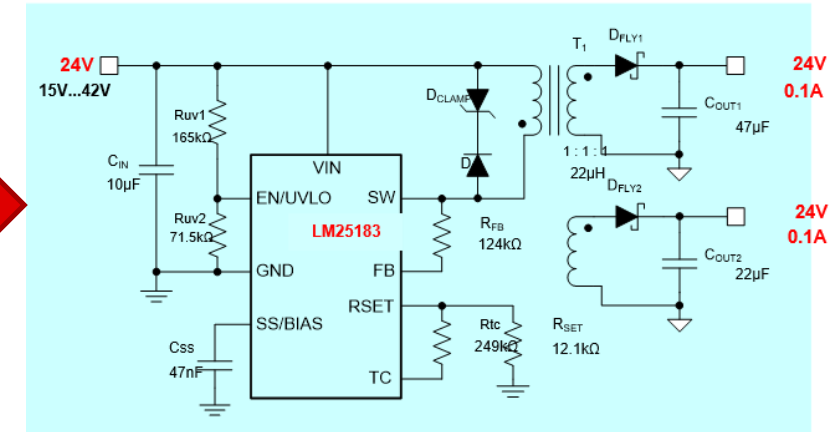

Evaluate performance

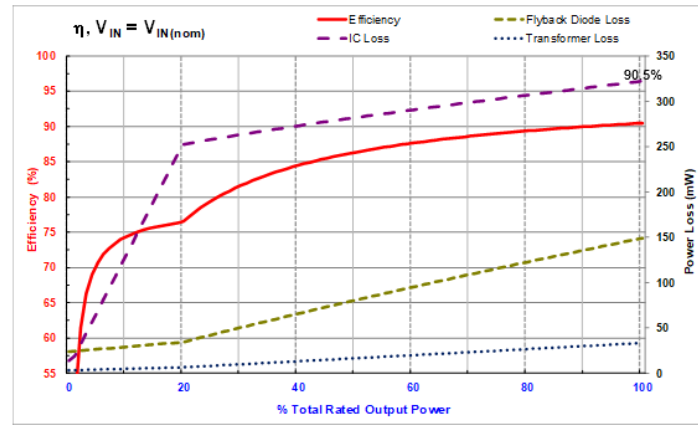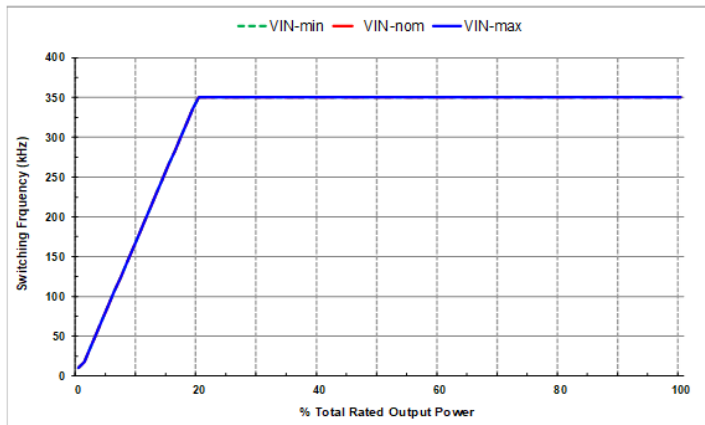

Ref Des	Value	Description	Size	Part Number	MFR	Footprint (mm)	Area (mm ²)
CIN	10 μ F	Capacitor, Ceramic, 10 μ F, 100V, X7R, 10%	1210	Std	Std	3.2 x 2.5	8.0
COUT1	47 μ F	Capacitor, Ceramic, 47 μ F, 50V, X7R, 10%	1210	Std	Std	3.2 x 2.5	8.0
COUT2	22 μ F	Capacitor, Ceramic, 22 μ F, 50V, X7R, 10%	1210	Std	Std	3.2 x 2.5	8.0
CSS	47nF	Capacitor, Ceramic, 47nF, 50V, X7R, 10%	0402	Std	Std	1.0 x 0.5	0.5
DFLY1	Diode	Rectifying Diode, Schottky	SMA	Std	Std	5.0 x 2.5	12.5
DFLY2	Diode	Rectifying Diode, Schottky	SC0123	Std	Std	3.6 x 1.8	6.5
Dc	Diode	Clamp Circuit Diode, Fast Recovery	SC0123	Std	Std	3.6 x 1.8	6.5
DCLAMP	24V	Clamp Circuit Diode, Zener, 24V	SC0123	Std	Std	3.6 x 1.8	6.5
DOUT	26.4V	Output Clamp Diode, Zener, 27V	SC0523	Std	Std	1.6 x 0.8	1.3
RSET	12.1k	Resistor, Chip, 12.1k Ω , 1/16W, 1%	0402	Std	Std	1.0 x 0.5	0.5
RFB	124k	Resistor, Chip, 124k Ω , 1/16W, 1%	0402	Std	Std	1.0 x 0.5	0.5
RUV1	165k	Resistor, Chip, 165k Ω , 1/16W, 1%	0402	Std	Std	1.0 x 0.5	0.5
RUV2	71.5k	Resistor, Chip, 71.5k Ω , 1/16W, 1%	0402	Std	Std	1.0 x 0.5	0.5
Rtc	249k	Resistor, Chip, 249k Ω , 1/16W, 1%	0402	Std	Std	1.0 x 0.5	0.5
T1	22 μ H	Transformer, 22 μ H, 1:1:1, 40m Ω Pri DCR, 3A Isat	10mm x 10mm	Various	Various	10 x 10	100
U1	LM25183	IC, LM25183, PSR Flyback Converter, 4.5V-42V Input	WSON-8	LM25183NGUR	TI	4.0 x 4.0	16.0

Total Solution Size (buffered by 25%) = 220.4 mm² =

Released reference designs

TIDA-010006


Isolated IGBT gate driver power supply using integrated switch PSR flyback controller

Features

- Isolated power supply for IGBT gate driving implemented in Fly back topology using controller with built-in switch
- Supports 6 IGBT gate drivers for 3-phase inverter
- Four isolated voltage rails: +15V / -9V (or) +15V/-5V
- Operates with unregulated 24V ($\pm 20\%$) input
- Output power: 1Watt per IGBT
- Functional isolation of 1.5kV DC between primary and secondary's as well as secondary's
- 5KV withstand voltage for 1 minute

Benefits

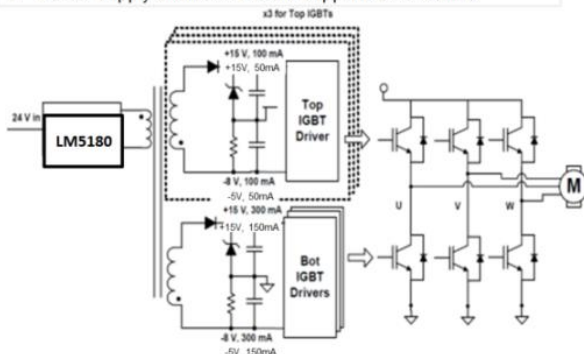- Compact design due to built-in switch
- Primary side regulation converter eliminates need for feedback circuitry, simplifies design
- Peak efficiency of $\sim 90\%$ at balanced full load
- High switching frequency reduces transformer size
- Power supply shutdown feature supports STO feature



Target Applications

- AC Inverters and Servo drives
- Solar and Wind Inverters
- UPS Systems

Tools & Resources

- TIDA-010006 and/or Tools Folder
- Design Guide
- Design Files: Schematics, BOM, Gerbers, Software, etc.
- Device Datasheets: LM5180

TIDA-020014


HEV/EV traction inverter power stage reference design with 3 types of IGBT/SiC bias supply solutions

Design Features

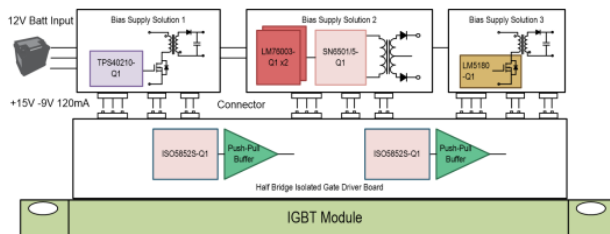- 4.5V to 45V input, +15V and -9V outputs, configurable into +20V, -4V outputs
- Directly driven by 12V car battery with increased safety level
- Wide-Vin during very low dips in input voltage of 4.5V and up to 45V DC
- No Opto coupler
- Low IQ operation at no-load current
- High efficiency at light loads

Design Benefits

- A comprehensive design with multiple bias supply solutions for IGBT/SiC isolated gate drivers in HEV/EV
- Multiple solutions including PSR Flyback Converter, Flyback Controller, Buck + Push-pull
- Small size, compact, cost effective
- Plug in connection to IGBT driver board for easy HV evaluation
- Compatible Isolated Gate Driver board included for customer evaluation



Tools & Resources

- Expected complexity of the TI Design
 - # of IC's: 5 (LM5180-Q1, TPS40210-Q1, LM76003-Q1*2, SN6501-Q1/SN6505-Q1, LM74700-Q1*3)
 - # of passives: ~ 140 into 3 boards
 - PCB dimensions: $\sim 40\text{mm} \times 40\text{mm}$ each board
 - # of PCB layers: 2
 - Firmware needs: N/A

TI Information – Selective Disclosure

TIDA-020015


4.5V to 70V input bias supply with power stage reference design for Automotive IGBT/SiC gate drivers

Design Features

- Directly driven by 12V car battery which eliminates risk from intermediate power rail failure
- VOUT accuracy $\pm 1\%$ achievable
- VIN = 4.5V–70V, VOUT = +15V & -9V, $\sim 180\text{mA}$, 5% regulation to full load
- TA = -40°C to 125°C
- Boundary mode, quasi-resonant operation
- Internal loop compensation
- no need to extra clamping circuit, fits both 12V battery & 48V battery inputs
- Tested for ISO 7637-2:2004 conducted transient immunity compliance, including Load Dump

Design Benefits

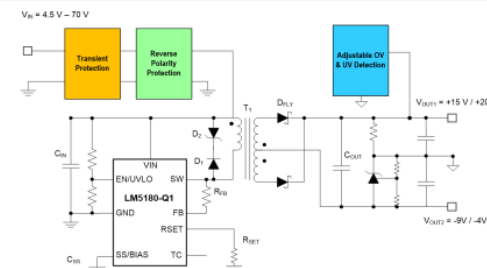- Easy-to-use, highly integrated, PSR flyback solution as Bias Power
- No opto-coupler or transformer auxiliary winding needed
- Low IQ operation at no-load current
- High efficiency at light loads
- Accurate VOUT regulation performance with sensing at zero current
- Low IQ operation and external BIAS rail option enable high efficiency at light loads



Tools & Resources

- Expected complexity of the TI Design
 - # of IC's: 2 (LM5180-Q1+LM74700-Q1)
 - # of passives: ~ 35
 - PCB dimensions: $\sim 40\text{mm} \times 40\text{mm}$
 - # of PCB layers: 2
 - Firmware needs: N/A

TI Information – Selective Disclosure

TIDACBL-0039 Intrinsic Safe Analog Input Module

Features

- 1 to 4 channel isolated Intrinsic Safe AI
- Supply for the Field Transmitters with output power limitation (short limited to 35mA)
- Input protected against miswiring (wiring to 24V)
- Transmitter supply: 26 +/-1V, Iout <35mA peak
- Input: short to L+ and GND protected, 24b accuracy

Benefits

- Short circuit protection on power output
- Mis-wiring protections on the Analog Input
- High-accuracy LM5180 allows to minimise heat dissipation from LDO (which can be low drop LDO)


Applications

- Robotics Analog Input Module for IS application
- PLC Analog Input Module

Additional details

- Definer: Ingolf Franck -> Ben Su
- Field: Takeshi Sasaki
- Key devices: LM5180, TPS2662, ADS122U04
- Why is this design considered: IS AI and how to protect inputs from shorts
- Public market info: IS application fast growing in Factory Automation
- Technical status: Design phase

TI Information – Selective Disclosure

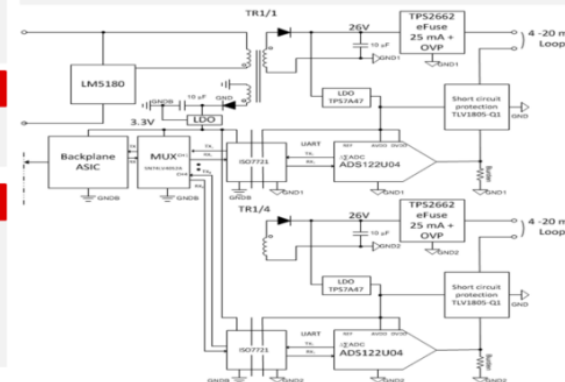

PSR flyback references

[LM25184 Single-Output EVM User's Guide](#)

[LM5180 Single-Output EVM User's Guide](#)

[LM5180 Dual-Output EVM User's Guide](#)

[How an Auxless PSR Flyback Converter can Increase PLC Reliability and Density](#)

[Why Use PSR-Flyback Isolated Converters in Dual-Battery mHEV Systems](#)

[PSR Flyback DC/DC Converter Transformer Design for mHEV Applications](#)

[Flyback Transformer Design Considerations for Efficiency and EMI](#)

[Under the Hood of Flyback SMPS Designs](#)

Conclusion

- **Isolated power sockets exist everywhere!**
 - **Medical and test & measurement, sensors in factory and building automation:** split rails for signal conditioning circuit (ie. op-amp, DAC/ADC)
 - **Factory automation, building automation, communications, and solar:** isolated power needed to ensure high signal integrity, with more and more sensors & faster speeds, signal integrity concerns only increase!
 - **Inverters in HVAC Systems, E-bike, Motor Drives:** Isolated gate driver requires isolated gate bias. SiC requires tighter regulation which is a great fit for No-opto PSR flyback.



Thank you!

PSR flyback converter – magnetic design considerations

Engaging with the magnetic component vendor

Key Specification	Symbol	Purpose
Turns ratio	N_{PS}	Optimize flyback duty cycle range
Switching frequency	F_{SW}	Control core loss
Magnetizing inductance	L_{MAG}	Set PSR flyback mode boundaries
Saturation current (at 20°C)	I_{SAT}	Prevent magnetic saturation
Primary and secondary DCRs (at 20°C)	R_{PRI}, R_{SEC}	Reduce copper loss
Winding arrangement – interleaving, # of layers		Minimize R_{AC} and L_{LEAK}
Leakage inductance	L_{LEAK}	Reduce power loss & voltage spikes
Interwinding capacitance	C_{P-S}	Mitigate common-mode EMI
Hi-pot test limits (dielectric withstand)	$V_{ISO(PRI-SEC)}$	Provide a robust design
Insulation rating – functional / basic / reinforced	IR	Comply with safety requirements
Operating temperature range	$T_{AMB} + T_{RISE}$	Ensure reliability
Mechanicals – pinout, footprint, height	$L \times W \times H$	Minimize size and cost

Flyback transformer losses

- **Copper** loss

- DC resistance – depends on the wire cross-section and length (N, MLT)
- AC resistance – depends on choice of wire diameter vs. F_{SW} and construction (layer stackup, proximity effects, gap effect)


- **Core** loss

- Related to core material characteristics, B_{DC} , B_{AC} , F_{SW}

- **External** loss


- Leakage inductance energy
$$P_{LEAK} = \frac{L_{LEAK} \cdot I_{SW-PK}^2}{2} \cdot F_{SW}$$
 - Large percentage of this power dissipated in external clamp circuit or RC snubber
 - Magnetizing energy also dissipated – depends on clamp level and leakage inductance

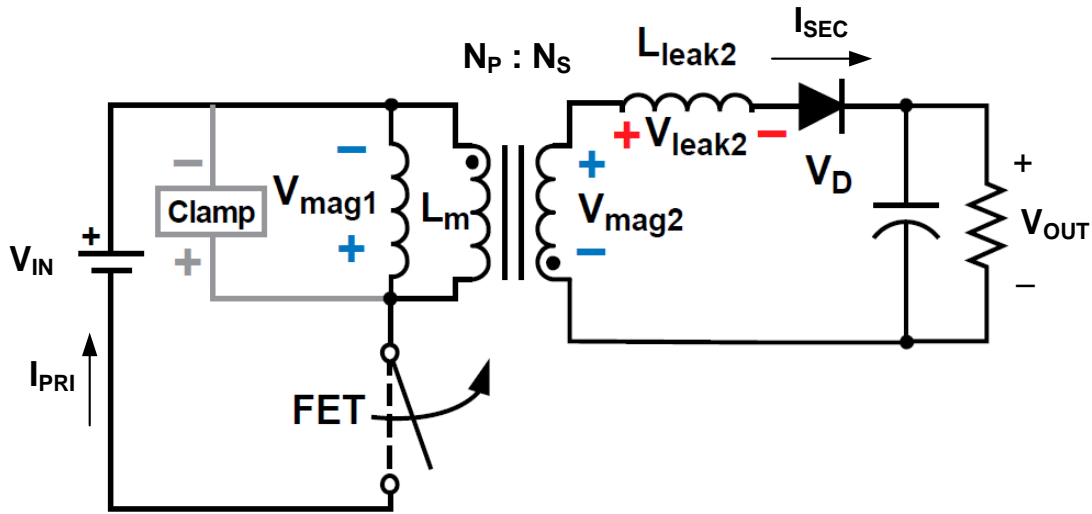Flyback transformer – impact of leakage inductance



Leakage inductance affects:

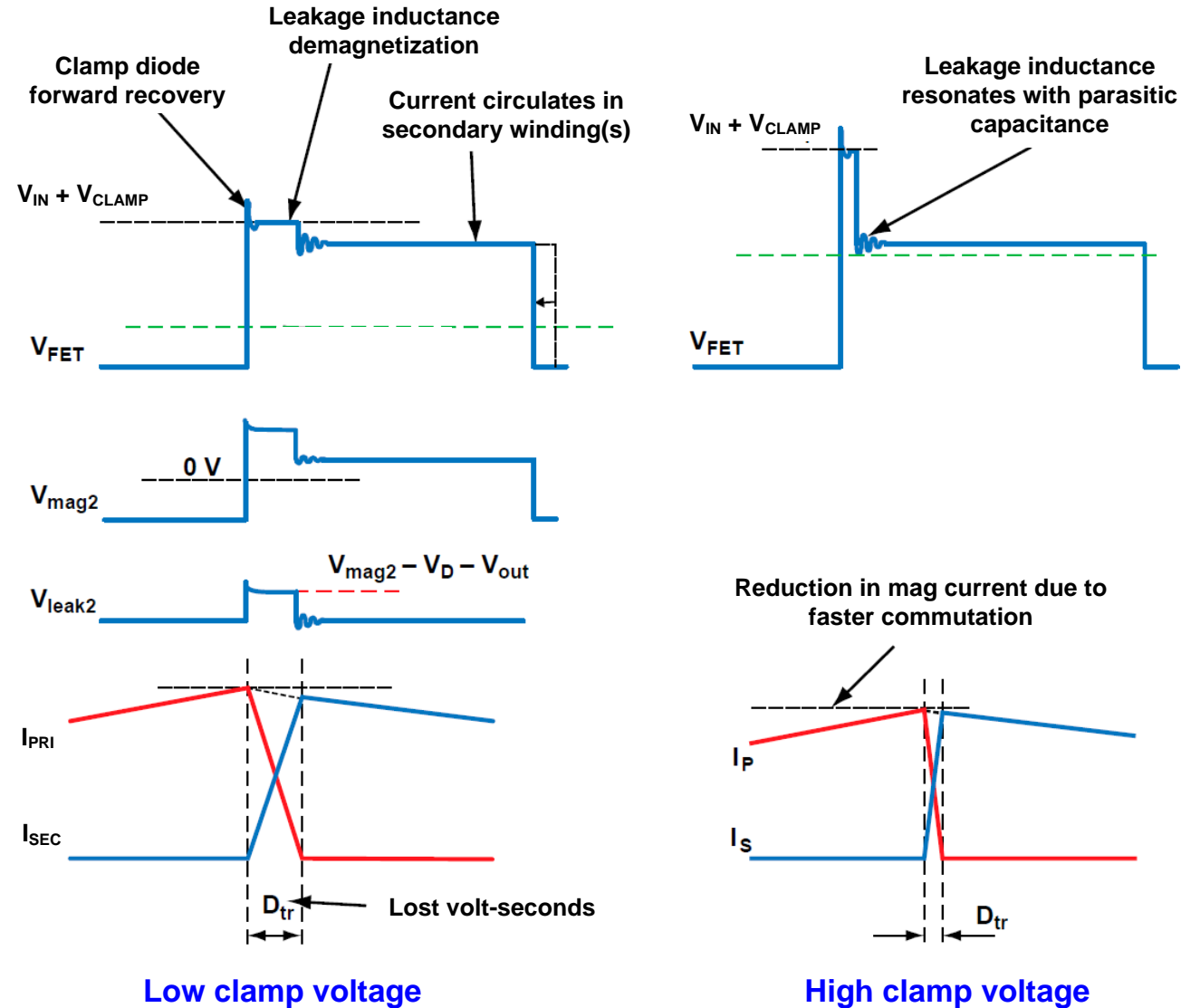- Conversion efficiency
- Voltage spikes during commutation
 - clamp circuits and snubbers
- Current slew rate & loss of volt-seconds
- H-field radiated EMI
- Cross regulation in multi-output designs



Flyback transformer design – impact on efficiency / x-reg


1. Guidelines to **optimize efficiency**

- Choose the transformer **turns ratio** for best efficiency and duty cycle range
- Minimize **leakage inductance** from primary to main (high-current) secondary
 - Interleave primary around secondary (or vice versa if $N_p < N_s$)
 - Reduces voltage spikes and power dissipation
 - Locate highest power secondary closest to primary (multi-output designs)
- Minimize transformer high-frequency **conduction loss**
 - Use bifilar or multifilar wires when necessary to reduce AC resistance
 - Interleave primary and secondary windings
 - Select core shape for minimum number of layers (wide bobbin width)

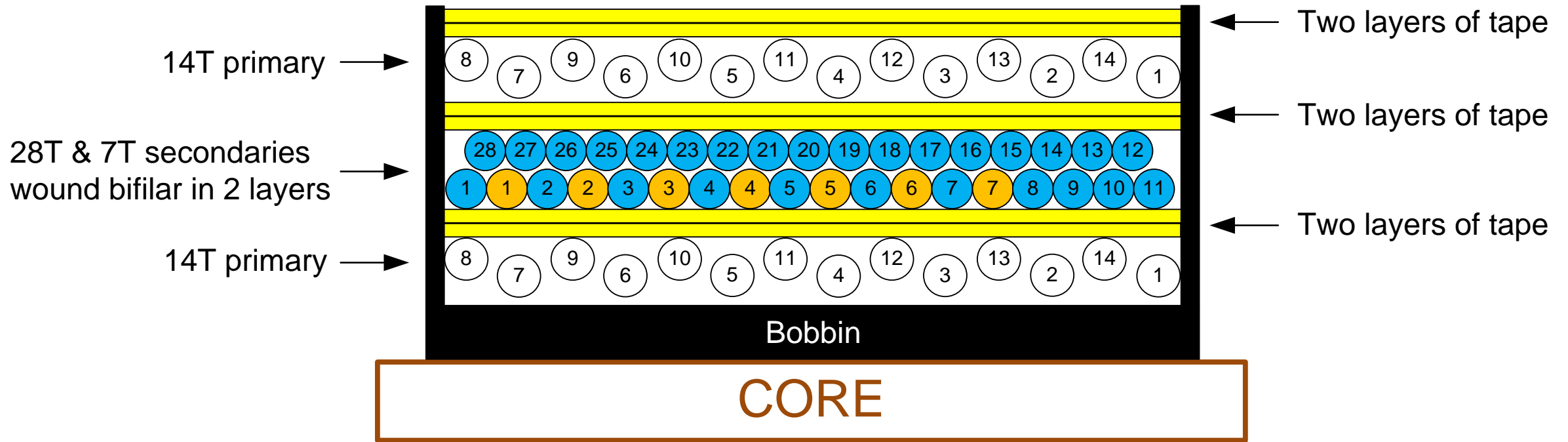2. Guidelines to **optimize cross regulation**

- Minimize **leakage inductance** *between secondary windings* as it impacts cross regulation and secondary current wave shapes
 - Wind two highest power secondaries **bifilar** for best coupling
 - Consider **DC or AC stacking** for same polarity outputs that share common GND


Dual-output transformer construction #1 14 : 28 : 7



Primary winding 50/50 parallel split

Parallel primary windings is a more convenient construction, but the **high dv/dt (noisy) SW node voltage** appears both on the inner and outer layers

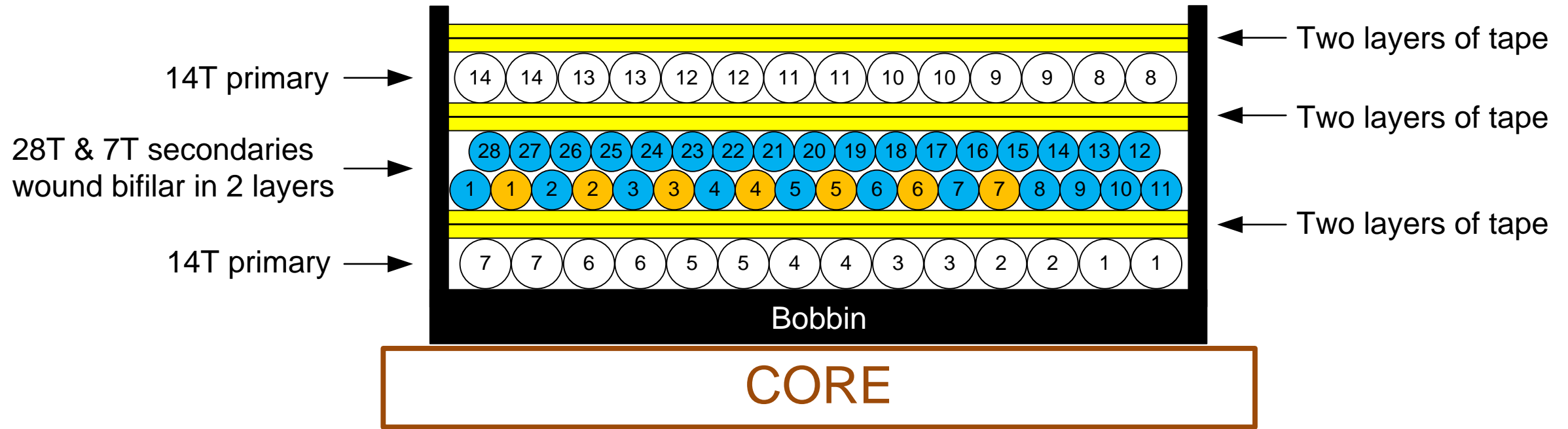Dual-output transformer construction #2 14 : 28 : 7



Primary winding 50/50 series split

- Wind first **half** of primary on inside layer nearest the bobbin and the other **half** on the outside
- Noisy node (SW) **shielded** on inside & quiet node (VIN) connects to outside layer
- Place windings with similar dv/dt adjacent to each other to reduce interwinding capacitance
- Better common-mode EMI performance

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated