

PR422
TMS320VC550x Design 5

FEATURES:

- Provides sequenced core and I/O voltages from 3.3 V input source.
- /RESET delay fixed at 65 ms minimum, 130 ms typical.
- All switching regulators for high efficiency operation.
- Small solution size.

IMPORTANT WEB LINKS:

- Link to the TI power management home page at <http://power.ti.com> then select the TI DSP Solutions link for more information and other reference designs.
- Link to datasheets at:
 - o <http://focus.ti.com/lit/ds/symlink/tps62300.pdf>
 - o <http://focus.ti.com/lit/ds/symlink/tps3103k33.pdf>


THEORY OF OPERATION:

PR422 consists of a series pass transistor for the I/O voltage and a TPS62300 buck regulator for the core voltage. A TPS62300 is used to convert the 3.3 V to the selected core voltage. A series pass transistor is used to switch a regulated 3.3 V supply to the I/O rail.

CIRCUIT LIMITATIONS AND CAPABILITIES:

The TPS62300 is capable of supplying 500 mA of core current.


POWER UP SEQUENCING:

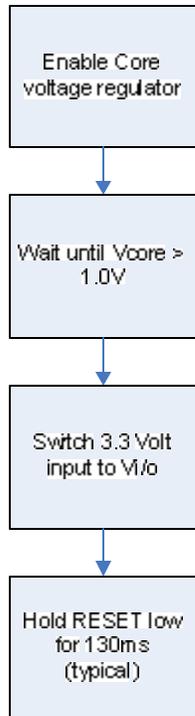

The circuit will switch the I/O voltage on about 200ms after the core voltage is above about 1.0V. The 1.0V threshold will vary with the characteristics of the transistors used in the sequencing circuit. Some systems may require a different time delay between the core and I/O voltage applications. Capacitor C3 can be adjusted to speed-up or slow down the turn on of the I/O voltage. The turn on time would be delayed by the RC time constant created by R3 and C3.


The sequencing circuits can be removed if sequencing is not required. Components R3, R4, C3, Q1 and Q2 can be removed and the 3.3 volt input tied directly to the I/O rail. This will not effect the minimum duration of the RESET signal.

WAVEFORMS:

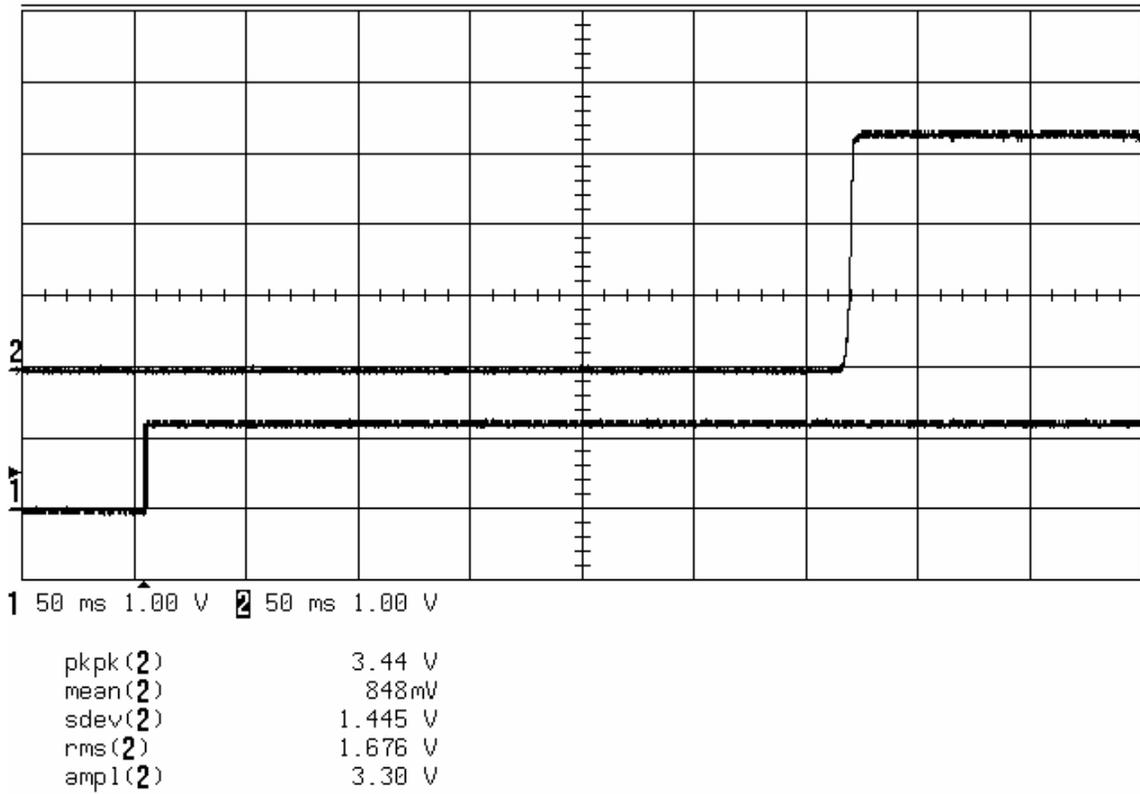


□ NORMAL

Figure 1 - Power up with $V_{IN} = 3.3$ V, $V_{core} = 1.2$ V @ 110 mA, $V_{i/o} = 3.3$ V @ 50 mA

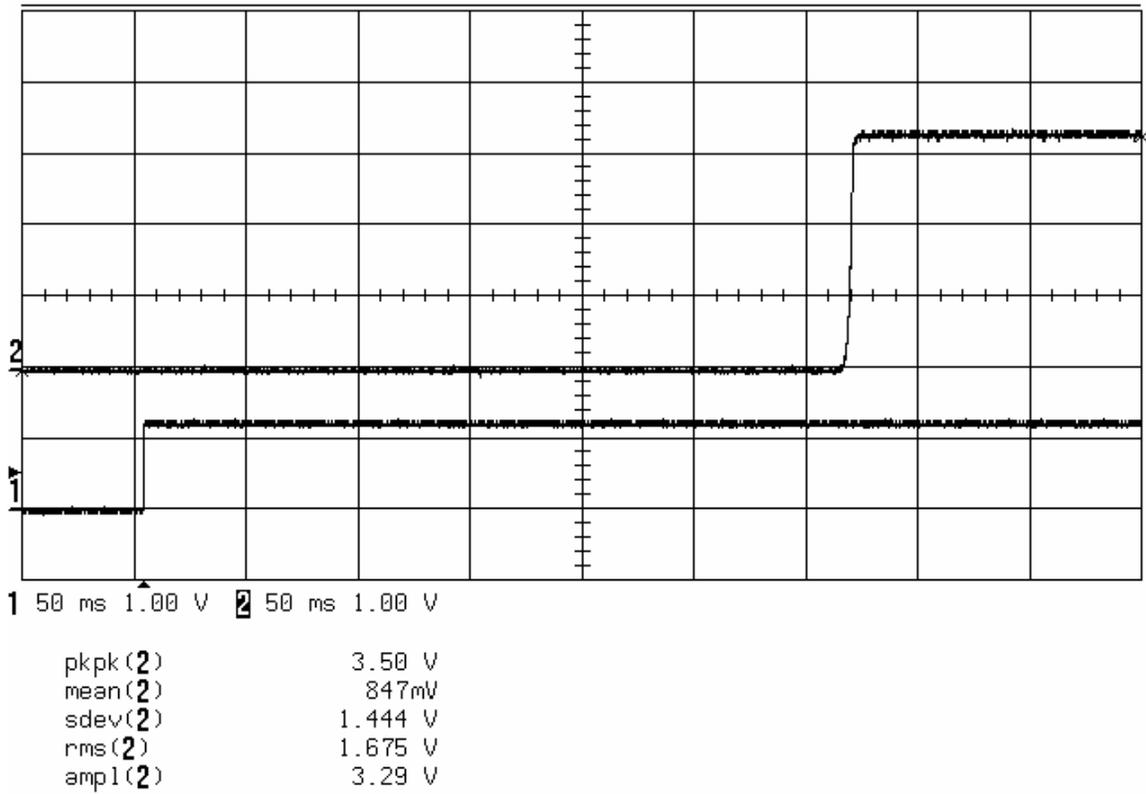

□ NORMAL

Figure 2 - Power up from Enable when $V_{IN} = 3.3$ V, $V_{core} = 1.2$ V @ 110 mA, $V_{i/o} = 3.3$ V @ 50 mA

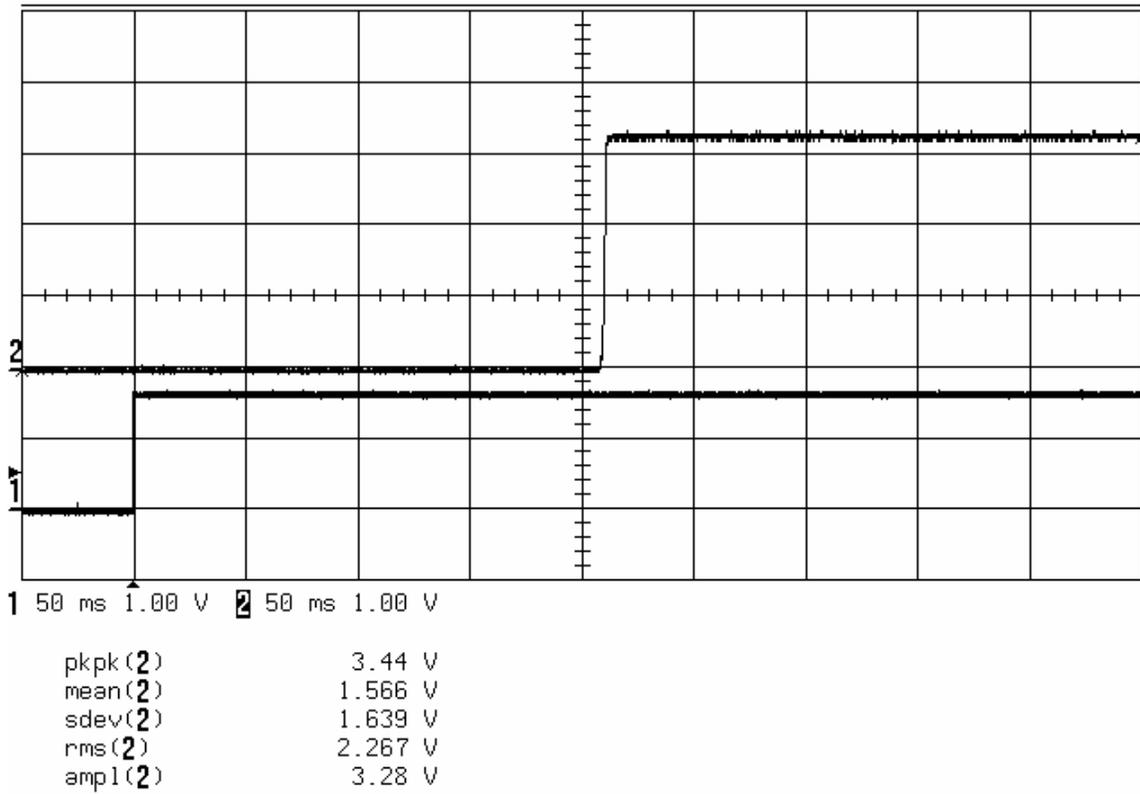

□ NORMAL

Figure 3 - Power up with $V_{IN} = 3.3$ V, $V_{core} = 1.6$ V @ 250 mA, $V_{i/o} = 3.3$ V @ 70 mA

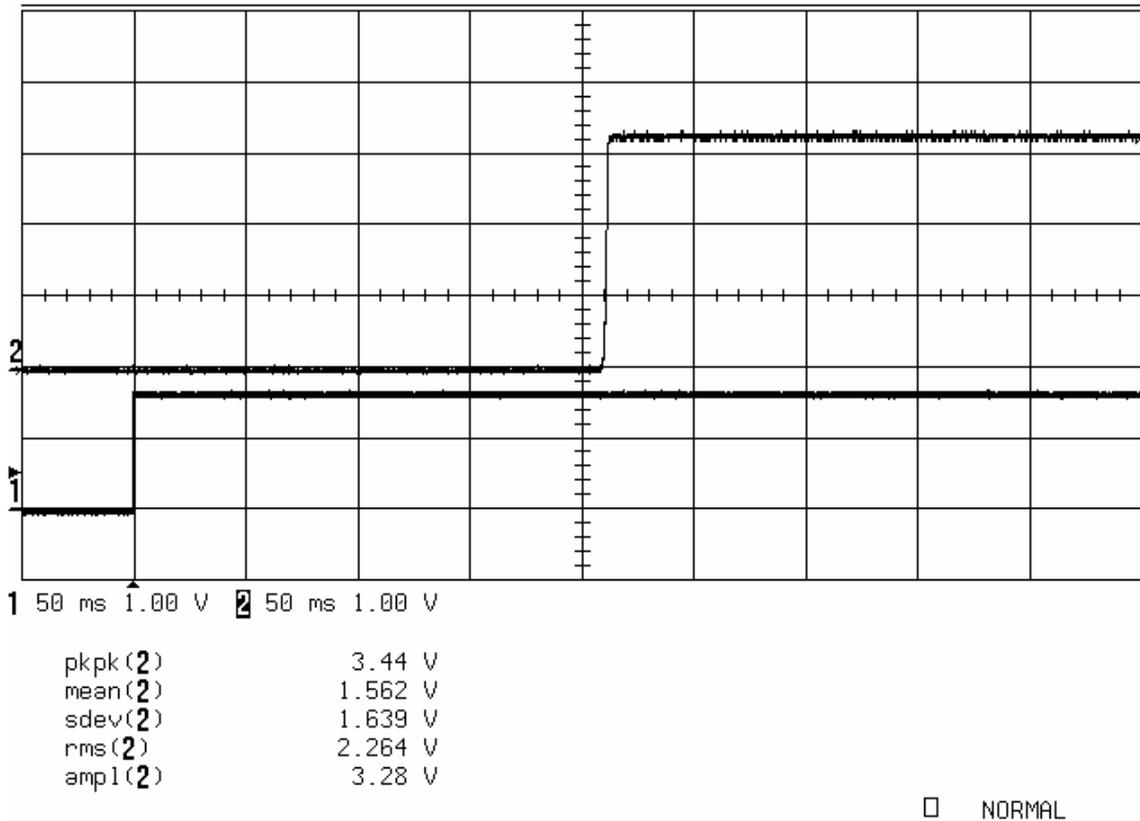



Figure 4 - Power up from Enable when $V_{IN} = 3.30\text{ V}$, $V_{core} = 1.6\text{ V}$ @ 250 mA, $V_{i/o} = 3.3\text{ V}$ @ 70 mA

TESTING METHOD:


The solution was tested on the bench and in an actual DSP circuit. Bench testing included start up into full DSP load, switched load from no load to full DSP load, and power up sequencing. The full DSP load is defined as the current draw a C550x DSP would present to the power supply under worst operating conditions. This full DSP load current is heavily dependent on board layout, firmware configurations, DSP clock speed, and core voltage. For testing purposes, the following values were assumed to be the full DSP load current.

Voltage (V)	Function	Full load current (mA)
1.2	core	110
1.6	core	256
3.3	I/O	70

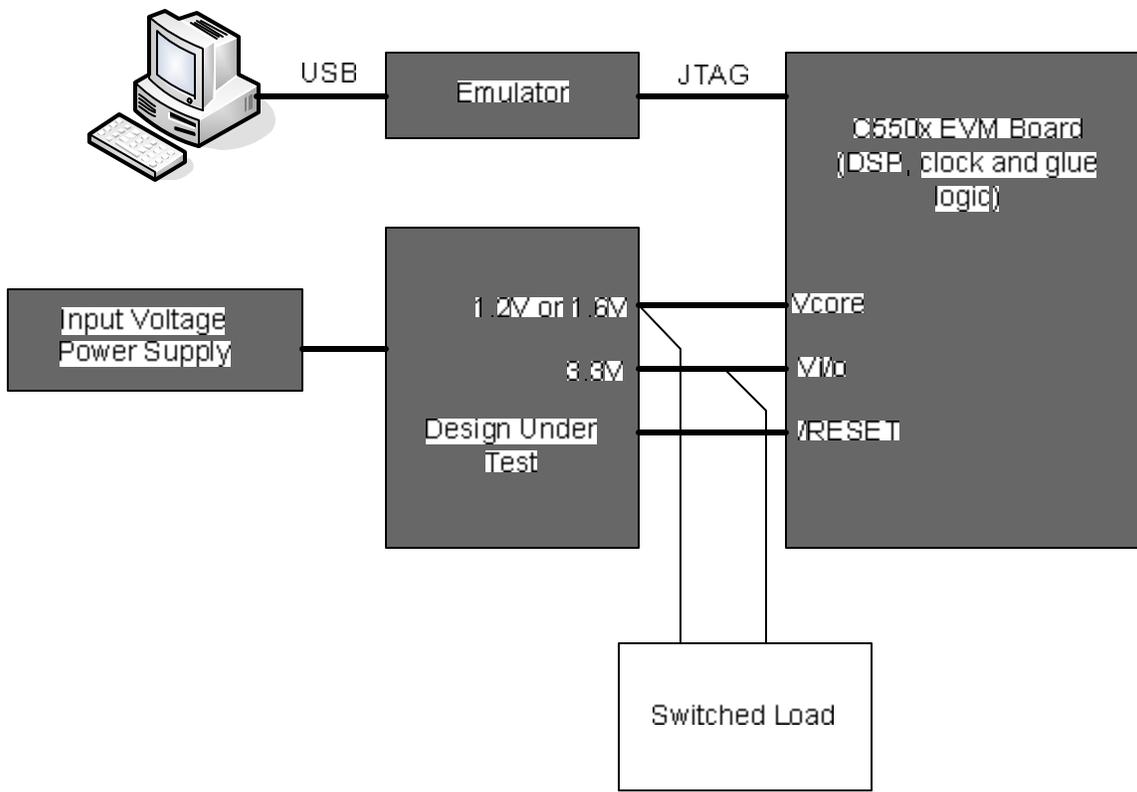The solution was also tested in an active DSP board. The following test setup was used for this testing:



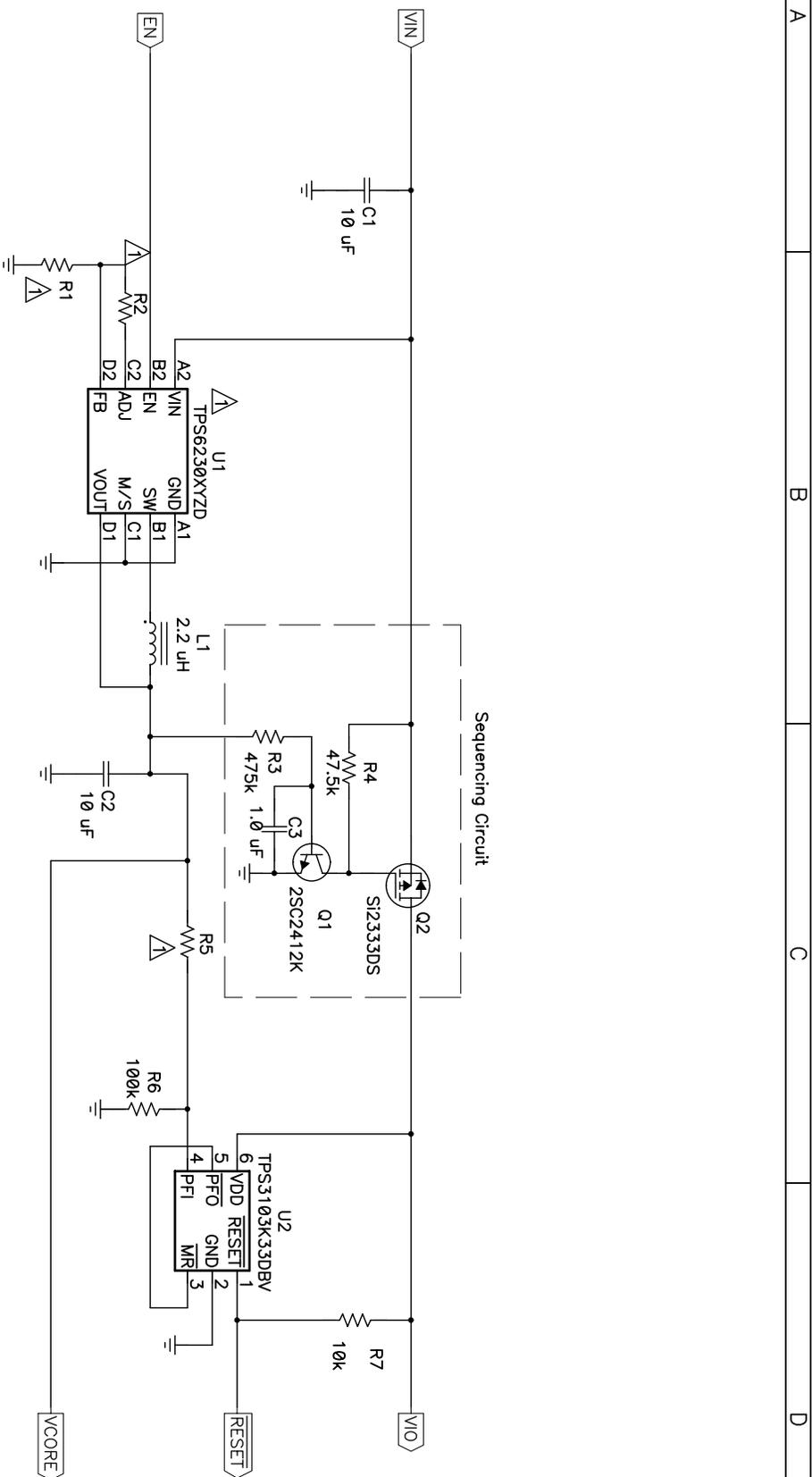Send an email to <mailto:dsppower@list.ti.com>



Sequencing Circuit

Voltage	U1	R1	R2	R5
1.2V	TPS62300	332k	332k	97.6k
1.6V	TPS62302	Open	Open	162k

Title	C5000 DSP Attach Design 5		
Size	for Vin = 3.3V		
Number	PR422	Rev	
Date	02/14/05	Drawn by	
Filename	pr422.sch	Sheet	of

Filename: PR422_bom.xls						
Date: 02/14/2005						
PR422 BOM						
COUNT						
-001	-002	RefDes	Description	Size	Part Number	MFR
2	2	C1, C2	Capacitor, Ceramic, 10-uF, 6.3-V, X5R, 10%	0805	GRM21BR60J106KE01	muRata
1	1	C3	Capacitor, Ceramic, 1.0-uF, 10-V, X5R, 10%	0603	GRM188R61A105KA61	muRata
1	1	L1	Inductor, SMT, 2.2-uH, 770-mA, 230-milliohms	0805	CB2016T2R2M	Taiyo Yuden
1	1	Q1	Transistor, NPN General Purpose, VCE 50V, VCB 60V, VEB 7V, IC 0.15A	SOT-23	2SC2412K	ROHM
1	1	Q2	MOSFET,P-ch, -12 V, 4 A, 51 milliohm	SOT23	Si2333DS	Vishay
1	0	R1	Resistor, Chip, 332k-Ohms, 1/16-W, 1%	0603	Std	Std
0	0		Resistor, Chip, xx-Ohms, 1/16-W, 1%	0603		
1	0	R2	Resistor, Chip, 332k-Ohms, 1/16-W, 1%	0603	Std	Std
0	0		Resistor, Chip, xx-Ohms, 1/16-W, 1%	0603		
1	1	R3	Resistor, Chip, 475k-Ohms, 1/16-W, 1%	0603	Std	Std
1	1	R4	Resistor, Chip, 47.5k-Ohms, 1/16-W, 1%	0603	Std	Std
1	0	R5	Resistor, Chip, 97.6k-Ohms, 1/16-W, 1%	0603	Std	Std
0	1		Resistor, Chip, 162k-Ohms, 1/16-W, 1%	0603	Std	Std
1	1	R6	Resistor, Chip, 100k-Ohms, 1/16-W, 1%	0603	Std	Std
1	1	R7	Resistor, Chip, 10k-Ohms, 1/16-W, 1%	0603	Std	Std
1	0	U1	IC, 3MHz Synchronous Step-Down Converter, 400mA	CSP-8	TPS62300YDZ	TI
1	1		IC, 3MHz Synchronous Step-Down Converter, 400mA	CSP-8	TPS62302YDZ	TI
1	1	U2	IC, Ultra Low Current/Supply, Voltage Supervisor	SOT23-6	TPS3103K33DBV	TI

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265