

When to use SSR or Isolated Gate Driver



Isolated gate drivers and isolated switch drivers (from TI's solid-state relay portfolio) both use a low voltage control signal to drive one or more FETs or IGBTs. The difference is isolated gate drivers use an external isolated bias supply to drive a FET while the isolated switch drivers use an internal bias supply to drive a FET.

Isolated Switch Driver Portfolio

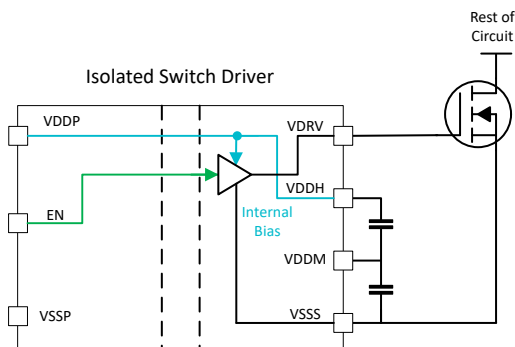


Figure 1-1. Isolated Switch Driver Simplified Diagram

Isolated Gate Driver Portfolio

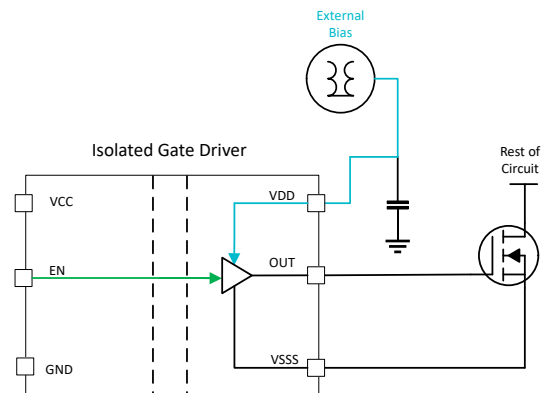


Figure 1-2. Isolated Gate Driver Simplified Diagram

An isolated gate driver is a very flexible solution due to the use of an external isolated bias supply. This device transfers signal across the isolation barrier which enables the external bias to drive a FET or IGBT. This external bias allows for high power applications as well as a wide range of frequencies to limit switching losses (for example, in power conversion systems). TI's isolated gate driver portfolio also offers devices with many monitoring features including short circuit detection, miller clamping, as well as ADC inputs that can be transmitted back to the MCU controlling the device.

TI's solid-state relay portfolio includes isolated switch drivers that are an optimized solution for applications that require less power transfer (for example, switching below 100kHz). These devices transfer power and signal across the isolation barrier to be used on the high voltage side, acting as an internal bias supply that is then used to drive a FET. This internal bias supply makes TI's solid-state relays a compact and cost-efficient solution when [replacing photorelays and electromechanical relays \(EMRs\) or contactors](#). TI's SSR do not integrate diagnostic communication (yet); excess power not being used for switching is available to power auxiliary monitoring circuits.

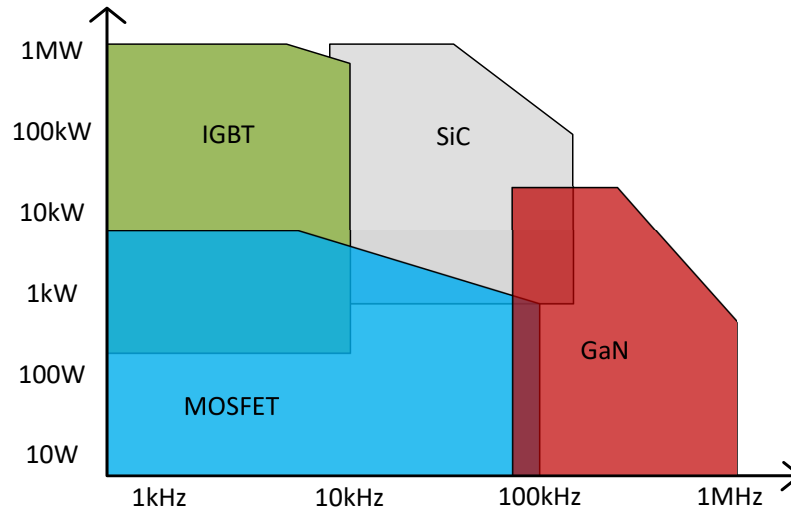


Figure 1-3. High Voltage Power Device Mapping

Figure 1-3 shows the typical frequencies and power needed to operate different FETs and IGBTs. Isolated gate drivers are able to operate SiC, GaN, MOSFET, and IGBT. Isolated switch drivers are able to operate IGBTs, SiC and MOSFETs; they are not suitable for operating GaN (intended for high frequency switching).

Table 1-1. Comparison of Isolated Gate Driver and Isolated Switch Driver

	Isolated Gate Driver	Isolated Switch Driver/SSR
<i>Isolated Bias Supply</i>	External	Internal (up to 65mW)
<i>Monitoring Features</i>	Integrated	External
<i>Propagation Delay</i>	As low as 19ns	As low as 3us
<i>Switching Frequency</i>	0Hz to ~20Mhz	0Hz to ~100kHz

Both isolated gate drivers and isolated switch drivers use low voltage control signals to drive FETs and IGBTs. Isolated gate drivers use an external bias supply which can be sized accordingly, to drive a FET or IGBT. Integrated monitoring features are available to provide protection or diagnostic information back to a low voltage MCU. In contrast, isolated switch drivers use an internal bias supply to make a compact and cost-optimized solution for low frequency switching applications (such as mechanical relay or photo relay replacement).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated