

# Save time and space in body motor design

**Featuring door, roof, trunk and seat applications**




Madison Eaker - body electronics and lighting systems

# Automotive body motors at a glance


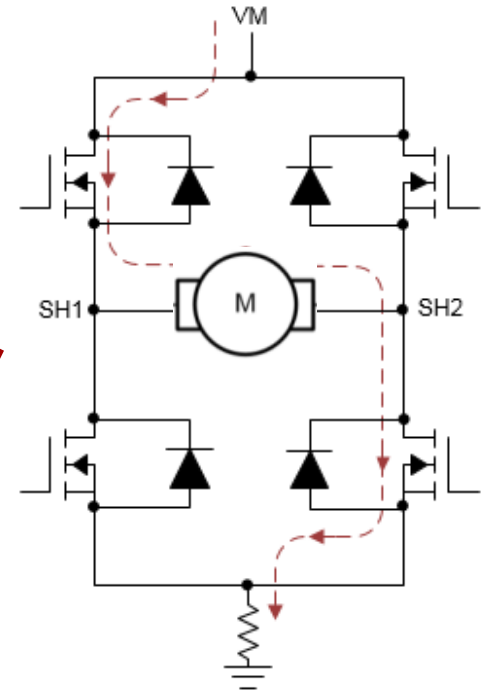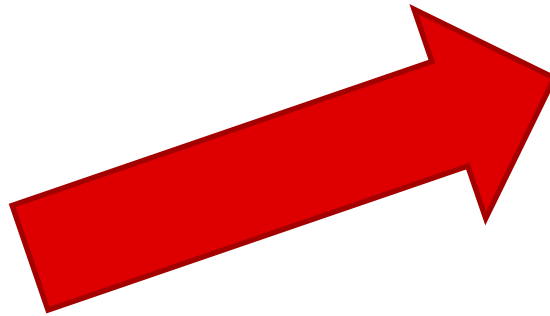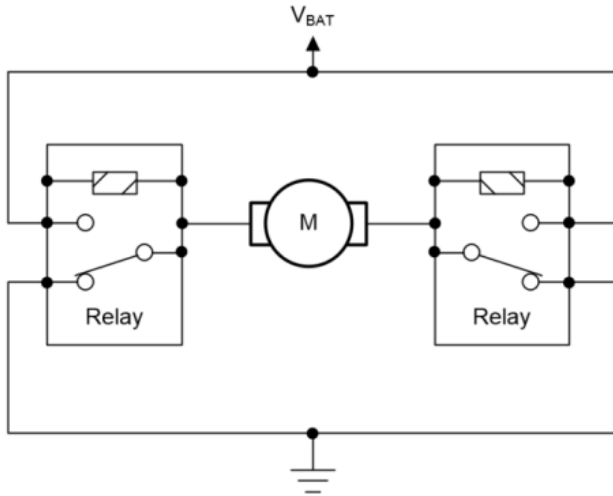
# Crossing the H-bridge

- Relays operate switches in an H-bridge
- Make a “clicking” sound
- Lack precise motor position and control



- MOSFET switching is faster than relays
- Allow PWM for speed control
- Higher reliability

# The *switch* to MOSFETs

## One big advantage: Enhanced motor control and performance

Suppress electromagnetic interference (EMI) from pulse-width-modulated (PWM) signals.

Thermal management to address heat generated from the current.

Current sensing to detect malfunctions and determine position and commutation.

Power-off braking to prevent damage to electronic components.

Diagnostics and protection to detect circuit continuity faults such as open and short circuits.

# Mitigating EMI with an H-bridge



Design challenges

- Control speed with pulse width modulation
- Low electromagnetic emissions
- Pass CISPR tests




## DRV8706-Q1



NEW

## DRV8706-Q1 EVM

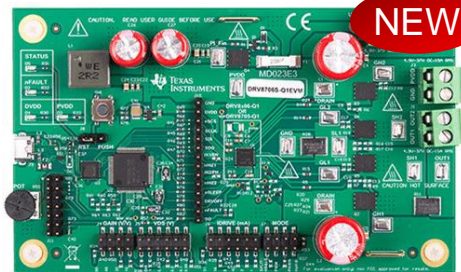

NEW

## Videos and Demos



NEW

Simplify EMI optimizations using Texas Instruments' Smart Gate Drive and Spread Spectrum Clocking feature!

On-line technical information at [training.ti.com](http://training.ti.com)

Other IC options: DRV8106-Q1, DRV8714-Q1, DRV8718-Q1

# Thermal design with motor drivers




## Design challenges

- Drive high power motors efficiently
- Operate at high temperatures
- Low power losses



## DRV8705-Q1

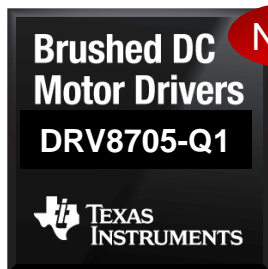

NEW


## DRV8705-Q1 EVM



NEW

From Integrated FET Motor Drives to multichannel gate drivers TI has the right device for your design

## Application notes

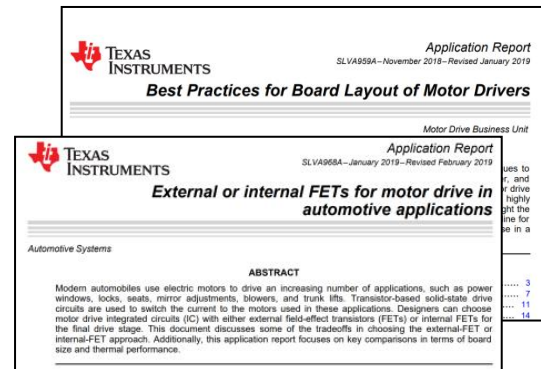

On-line technical information at [training.ti.com](http://training.ti.com)

# Current sensing



Design challenges

Monitor motor current to detect faults  
Motion feedback with ripple counting  
In-line or low-side sensing



## DRV8873-Q1



TI motor drives eliminate the need for external current sense amplifier and more to reduce your BOM and cost!

## DRV8873-Q1 EVM



## Application notes

**Low-Side Current Sense Circuit Integration**

**Advantages of integrated current sensing**  
Ryan Kehr, Motor Drives

**TEXAS INSTRUMENTS**

Monitoring and regulating current is a must for many brushed and stepper motor applications. For brushed motors, the current information can be used to determine changes in load conditions or for limiting startup and stall currents. For stepper motors, high levels of micro-stepping require current to be regulated for each step.

In Figure 1, current is plotted versus time depicting the startup profile for a brushed DC motor. In this case, current is limited to approximately 2 amperes before the motor reaches a steady state condition of less than 1 ampere. Without current regulation, this same motor peaks to over 14 amperes. This not only requires an over-designed power supply to support this transient, but the motor driver also needs to be rated to reliably handle the peak currents.

A low voltage signal path resistor compared to a power resistor requires much smaller board space and lowers the bill of materials (BOM). In addition to these benefits, there is no power loss across the resistor and one more heat source is eliminated from a design that is most likely already under thermal budget pressure.

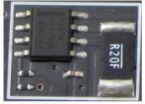


Figure 2. DRV8870 with External Shunt

On-line technical information at [training.ti.com](http://training.ti.com)

Other IC options: DRV8871-Q1, DRV8874-Q1 DRV8876-Q1

# Power off braking




## Design challenges

- Movement of mechanical parts
- Unpowered motors generate voltage
- Protect drive circuits from dangerous levels




## DRV8714-Q1

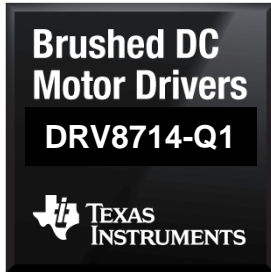

Integrated protection against back EMF when your system is On or OFF

## DRV8714-Q1 EVM

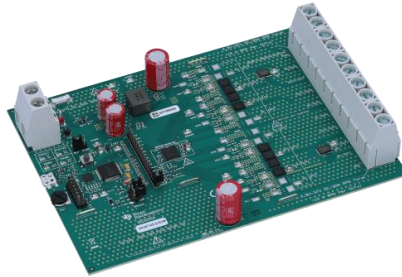

Other IC options: DRV8718-Q1

## Application note

**Tech Note**  
**Low Power Brake Mode**

TEXAS INSTRUMENTS

Franklin Cooper Jr.  
Brushed and Stepper Motor Drives

**Introduction**

Simple user error can lead to unintentional damage to a vehicle if proper precautions are not taken. Engineers must design robust solutions that can work effectively in a variety of scenarios. An easy-to-overlook problem is properly handling the voltage surge that can be generated by manually opening, closing or adjusting any part of the vehicle that is connected to a motor. If high enough, this voltage surge can cause damage to connected components. Engineers must therefore design a solution that can protect the system, either when the vehicle is powered on or even when it's powered off. Examples of how this issue can occur in the first place will be discussed next.

**Understanding the Problem**

A brushed DC motor works by using the applied voltage to generate a current that flows through the armature. The current flowing through the winding within the armature generates a magnetic field. This magnetic field pushes away from the internal permanent magnets in the motor which then results in

**Figure 1. Example scenarios where a motor may be externally driven**

On-line technical information at [training.ti.com](http://training.ti.com)



# Advanced diagnostics



## Design challenges

- Detect short-circuit faults to battery
- Detect faults in drive circuit
- Notify MCU for corrective action or safe mode



### Short to supply

Detects motor winding short-to-battery while the motor is not in motion and alerts the MCU promptly for corrective action.



### Short to ground

Detects motor winding short-to-ground while the motor is not in motion and alerts the MCU promptly for corrective action.



### Open Load Fault

Detects load getting disconnected at power-up or while in motion.

# Explore products

Control module	Load	Products
<u>Door</u>	Single window with BDC motor	DRV8705-Q1, DRV8706-Q1
	Door lock motor	DRV8714-Q1, DRV8718-Q1, DRV8873-Q1
	Dual window with BDC motor	
	Single window with BLDC motor	DRV8343-Q1
	Mirror X/Y motor	DRV8908-Q1, DRV8873-Q1
	Mirror fold motor	
<u>Roof</u>	Roof motor	DRV8705-Q1, DRV8706-Q1
	Multiple roof motor	DRV8714-Q1, DRV8718-Q1
<u>Trunk</u>	Single trunk lift BDC motor	DRV8705-Q1, DRV8706-Q1
	Multiple trunk lift BDC motors	DRV8714-Q1, DRV8718-Q1
	Single trunk lift BLDC motor	DRV8343-Q1
	Trunk cinch motor	DRV8873-Q1
<u>Seat</u>	Seat position adjust motor	DRV8714-Q1, DRV8718-Q1
	Lumbar support bladder pump motor	DRV8873-Q1, DRV8874-Q1
	Seat ventilation motor	DRV10983-Q1
	Seat base rotation motor	DRV8343-Q1

**Thank you!**



**©2020 Texas Instruments Incorporated. All rights reserved.**

The material is provided strictly "as-is" for informational purposes only and without any warranty.  
Use of this material is subject to TI's **Terms of Use**, viewable at [TI.com](https://www.ti.com)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2020, Texas Instruments Incorporated