



HIGH VOLTAGE SEMINAR

BING LU

ELECTRIC VEHICLES

**A SIMPLE, ROBUST AND LOW-EMI SOLUTION FOR
INVERTER GATE-DRIVER BIAS SUPPLIES**

Agenda

- Inverter and isolated gate driver bias supply architectures
- Different ways of creating isolated bias supply
 - Control method
 - Topology
 - Transformer
- LLC based open-loop isolated bias supply
 - Operation principles
 - Circuit variations
 - Voltage regulation
 - Multiple outputs
- Performance demonstration

Inverters in different applications



Traction inverter




UPS




Onboard charger



Motor drive

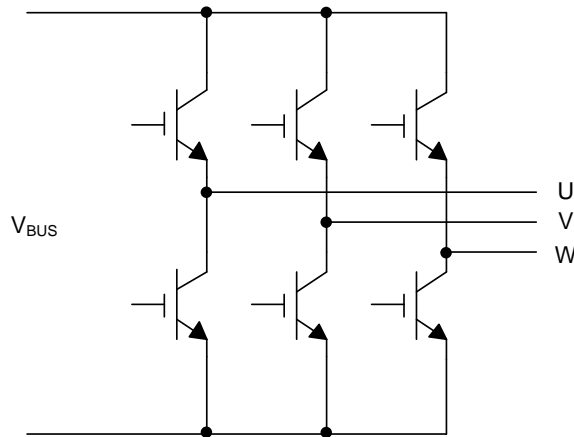


Example: inverter isolation bounds

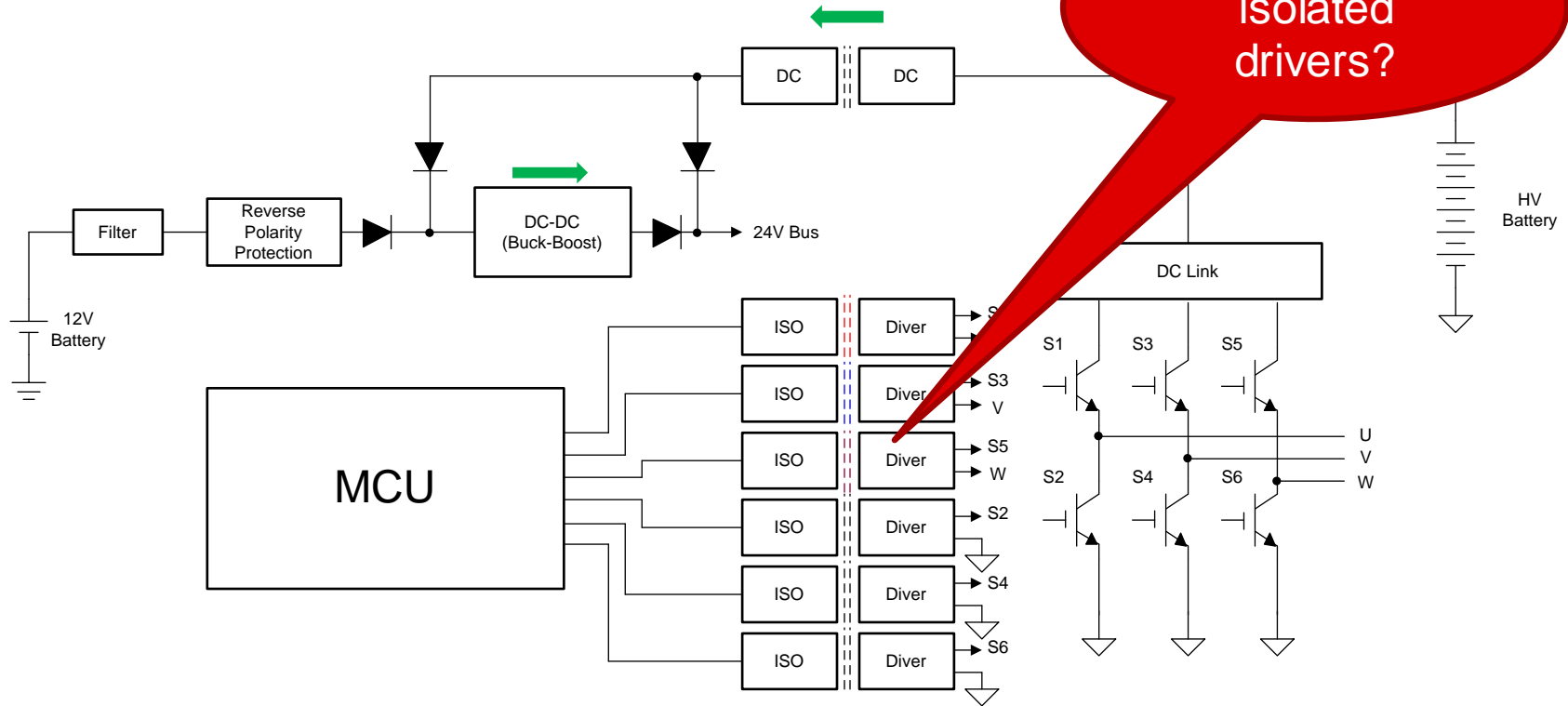


Different gate driver architectures


Centralized

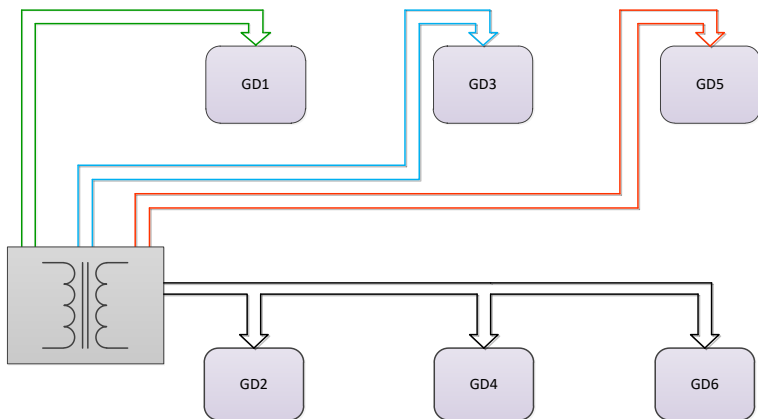

Semi-Distributed

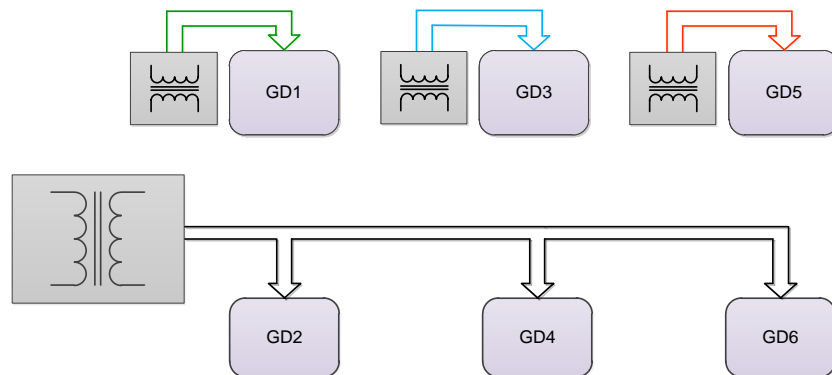


Distributed

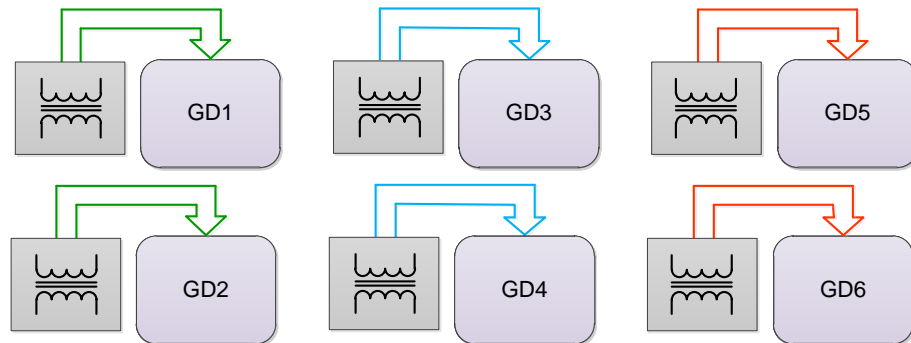


- Centralized system has lowest cost, but heavy and difficult to manage fault
- Distributed system distribute the weight and fault, but more expensive
- Semi-distributed is somewhere in the middle

Output voltage control

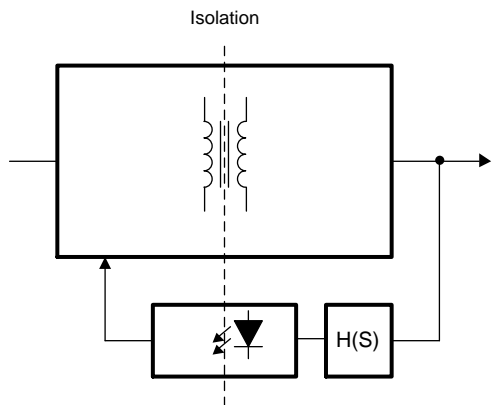


Close loop Secondary side feedback

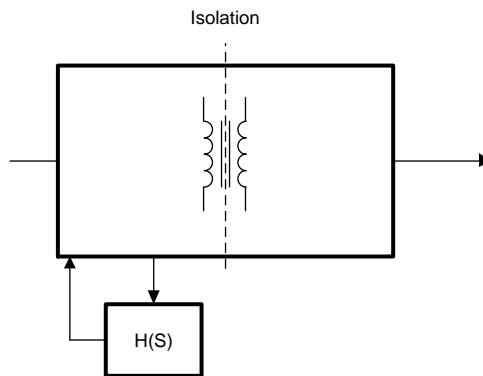- Well regulated output
- No need pre-regulator
- More components
- Less reliable due to the opto coupler



Close loop Primary side feedback

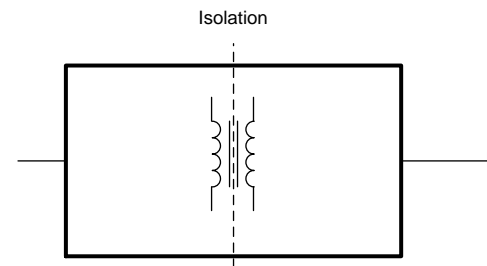- Semi regulated output
 - Determined by cross regulation
- No need pre-regulator
- Noise sensitive due to the output voltage sampling method




Open loop No feedback

- No control loop, robust operation
- Less noise
 - Coupling only through the transformer
- Unregulated output, need pre-regulator


Open-loop control provides a robust solution

Topologies used for isolated bias supply


Flyback

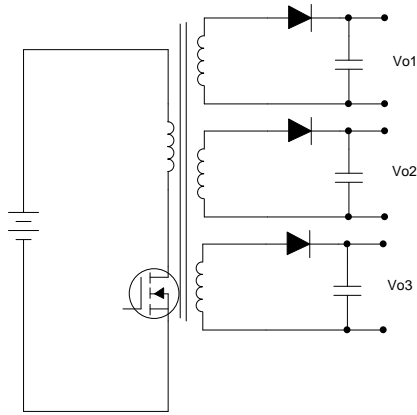



Push-pull

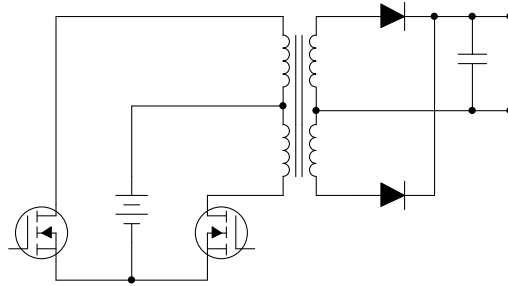


LLC

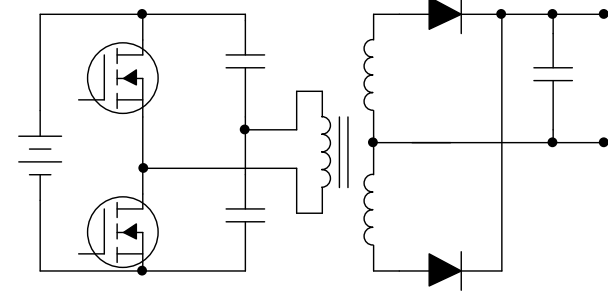

Flyback converter topology


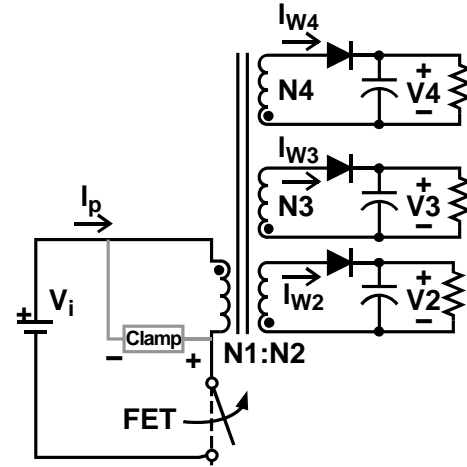
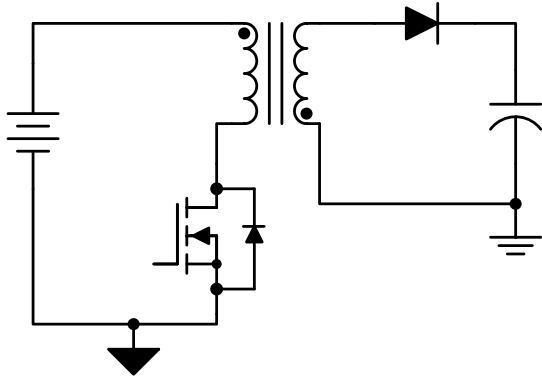


Basic Flyback Circuit

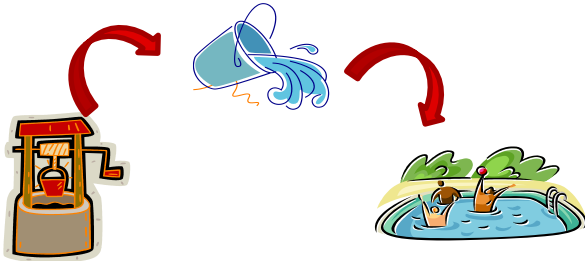


- Flyback can easily create multiple outputs
 - Voltage proportional to the turns ratio
 - Suitable for centralized architecture
- Can be controlled with opto feedback or primary side feedback
- Need well coupled transformer

Push-pull topology

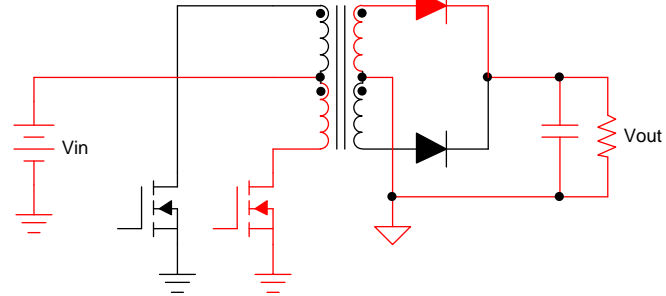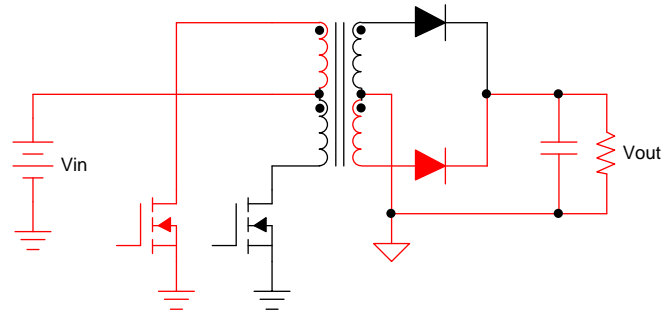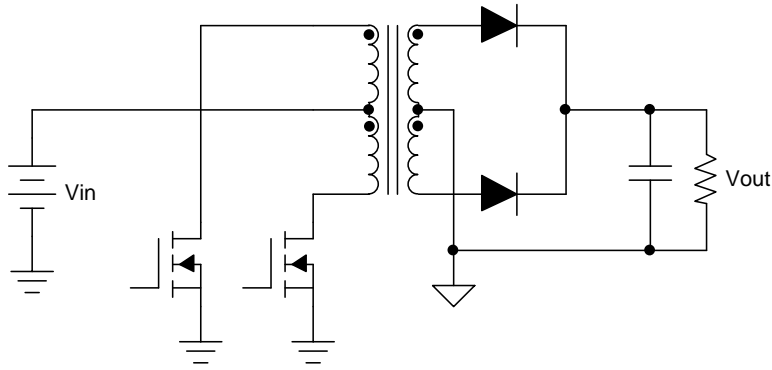


- With 50% duty cycle operation, in each half switching cycle, output is connected with input through the transformer
- Filter inductor is needed if the duty cycle is less than 50%
- Transformer needs to have low leakage inductance to avoid ringing and device over stress
- Good for distributed and semi-distributed architecture

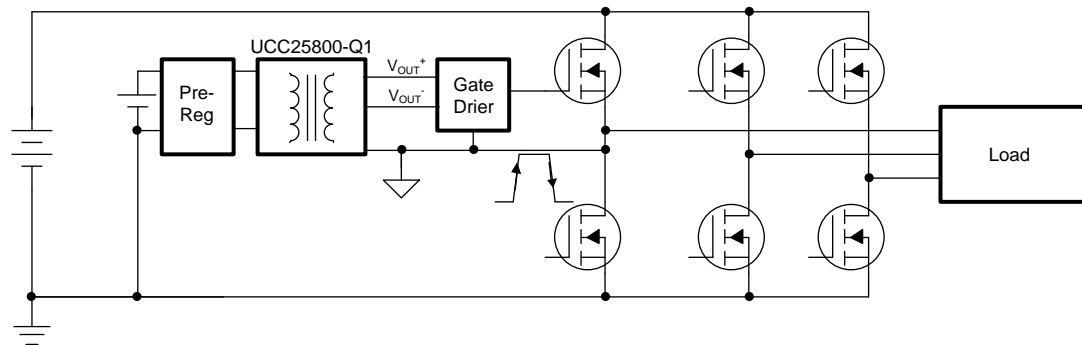
Transformer parameter impacts to system EMI



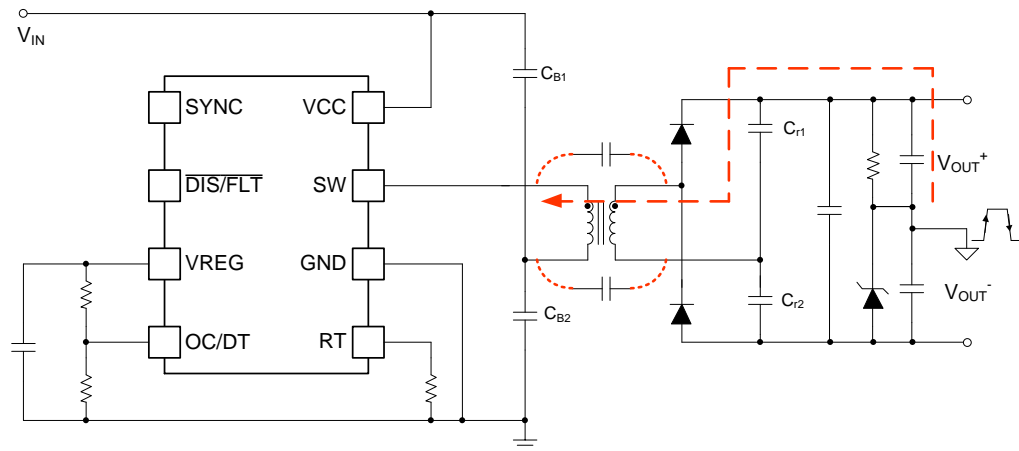
- High dv/dt couples through transformer parasitic capacitor to the primary side
- Higher EMI noise
- Extra loss
- More noise to the controller, CMTI issue
- It gets worse with SiC or GaN devices with higher dv/dt



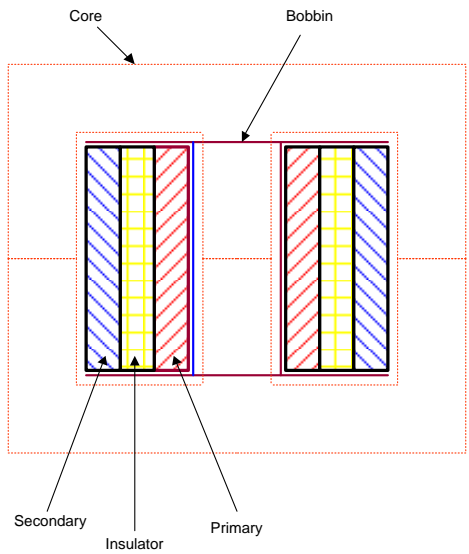
Transformer structure: less parasitic capacitance



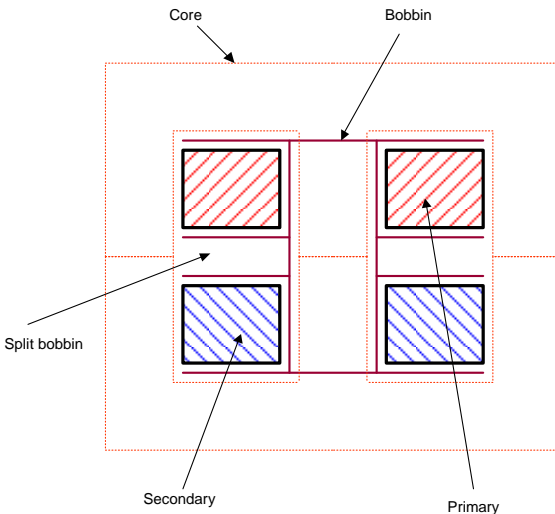The capacitance can be reduced by increasing the insulator thickness
Less effective due to the large surface area



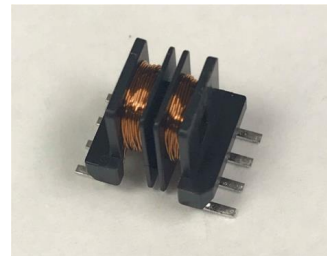
Split bobbin reduces the capacitance by reducing the surface area and increasing the distance
Much smaller capacitance can be achieved



Increasing the distance reduces the capacitance while increasing the leakage inductance


How topologies respond to leakage inductance

Flyback

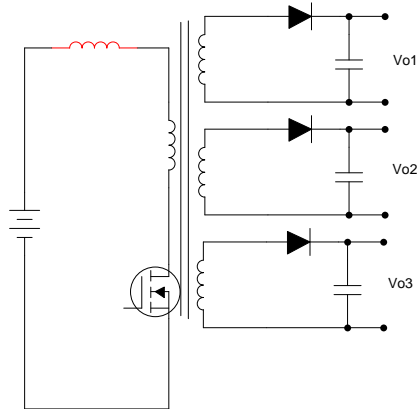


- Leakage energy can't be transferred to secondary side
- Leakage causes
 - More EMI noise due to ringing
 - More loss
 - More device stress
- Leakage needs to be minimized

Push-pull

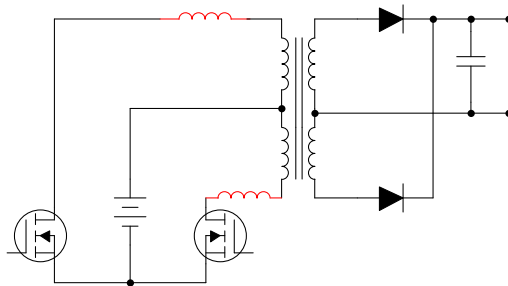


LLC

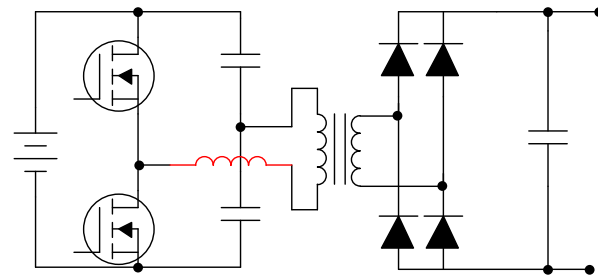

- Leakage is part of resonant circuit
- Leakage energy is fully recovered
- No extra ringing caused by the leakage
- **No limitations on the leakage inductance**



LLC converter

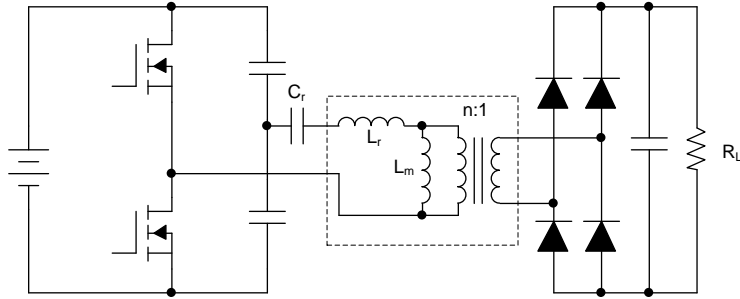

$$f_0 = \frac{1}{2\pi\sqrt{L_r C_r}}$$

$$Q_e = \frac{\sqrt{L_r/C_r}}{R_e}$$

$$R_e = \frac{8n^2}{\pi^2} R_L$$

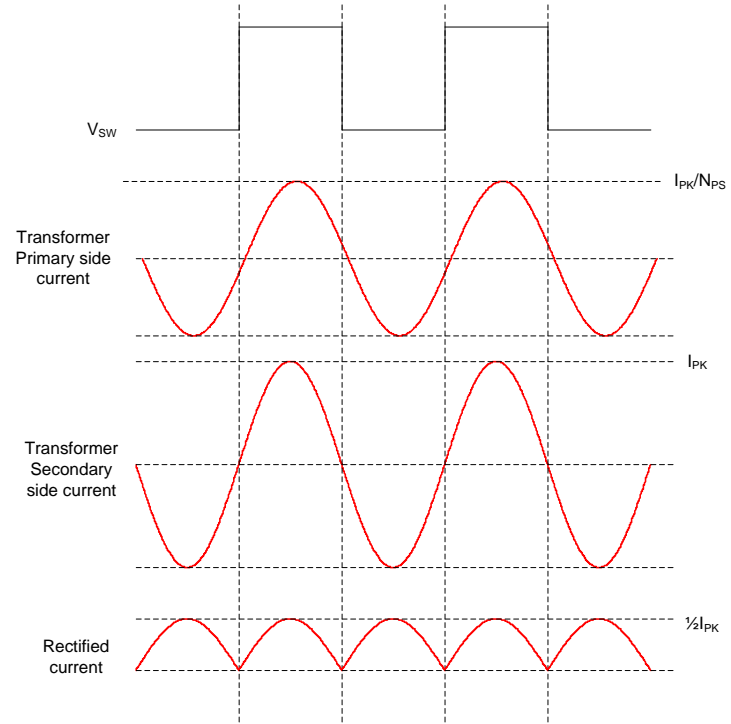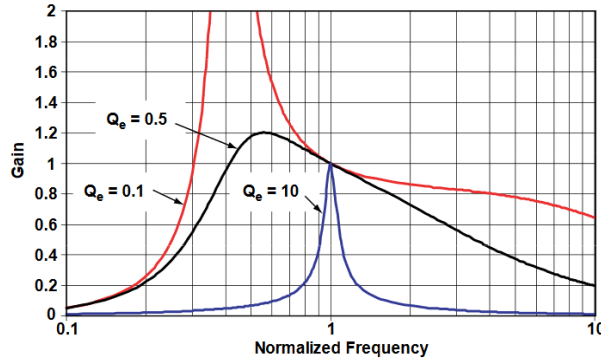


- At resonant frequency, the impedance of resonant tank is equal to zero, input and output is shorted through the transformer. Fixed frequency open-loop control is possible
- The leakage inductance of the transformer can be used as the resonant inductor

Transformers for isolated bias supply


	LLC Transformer	Push-Pull Transformer	Three-winding Flyback	Two-winding PSR Flyback	Half-Bridge
		<p>Pri1* Pri2* Sec1* Sec2*</p> <p>Secondary side windings need thicker insulation</p>	<p>Core Bobbin</p> <p>Secondary Thick insulation Aux Primary</p>	<p>Core Bobbin</p> <p>Insulator Primary Secondary</p>	<p>Core Bobbin</p> <p>Insulator Secondary Primary</p>
C_{Pri-Sec}	<2pF	~10 pF	~20 pF	~20 pF	~20 pF
CMTI	>150V/ns	Worse than LLC	Worse than LLC	Much worse than LLC	Much worse than LLC
Cost	1X	>1.15	>1.3X	>1.18X	>1.18X
EMI	Best	Good	Poor	Poor	Poor
Regulation	Good	Good	Better	Best	Good

LLC converter provides an order of amplitude capacitance reduction


LLC converter variations

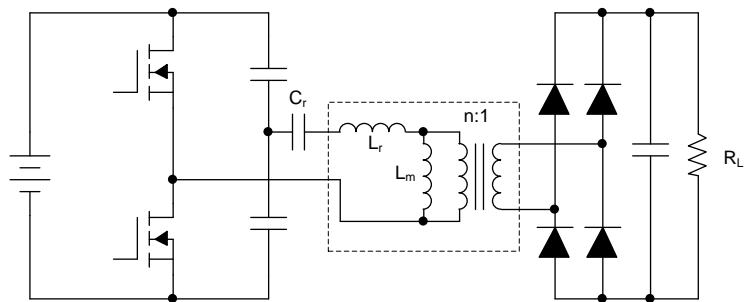


Transformer variations

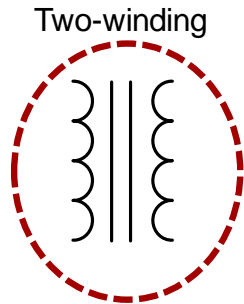

Center-tap

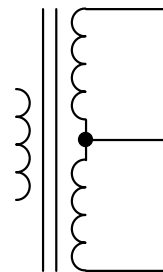


Multi-output

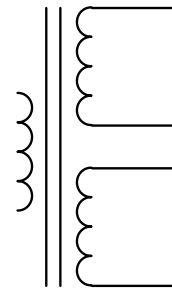


Rectification Variations


Full-wave

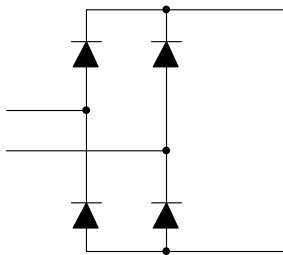


Center-tap

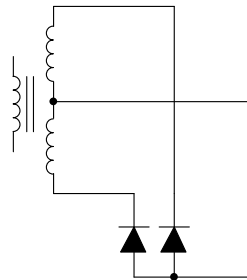



Voltage-doubler

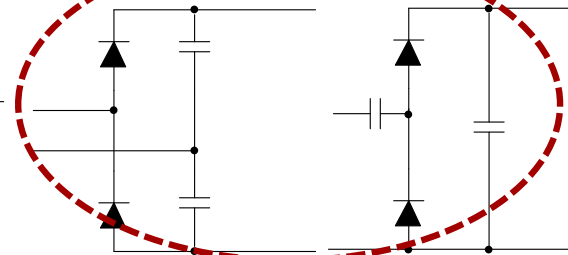


Primary vs. Secondary side resonant

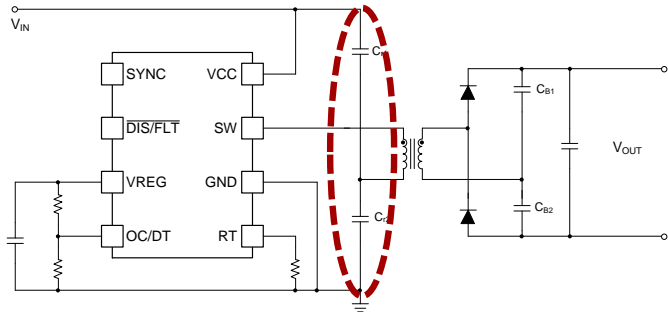

Primary side resonant

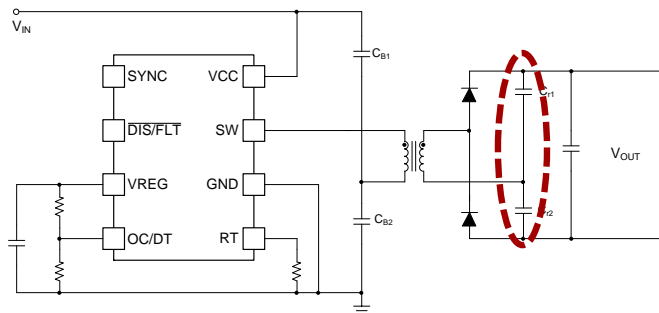
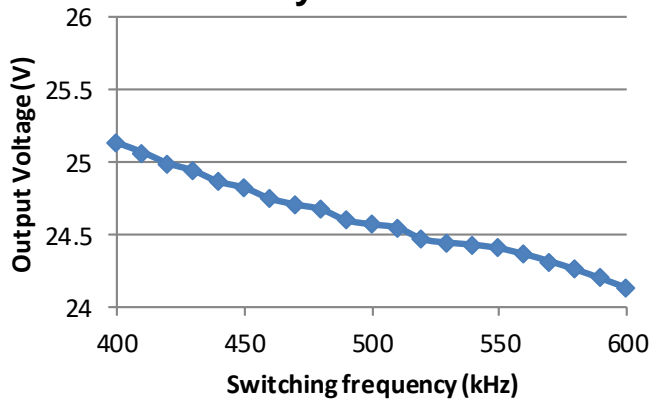


Secondary side resonant

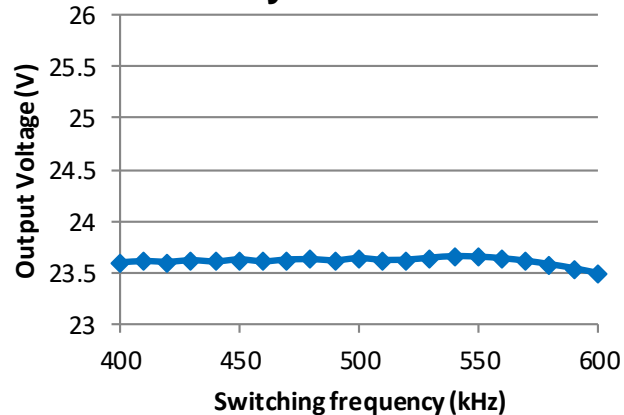

Secondary side resonant is less sensitive to switching frequency error


Open-loop LLC voltage regulation

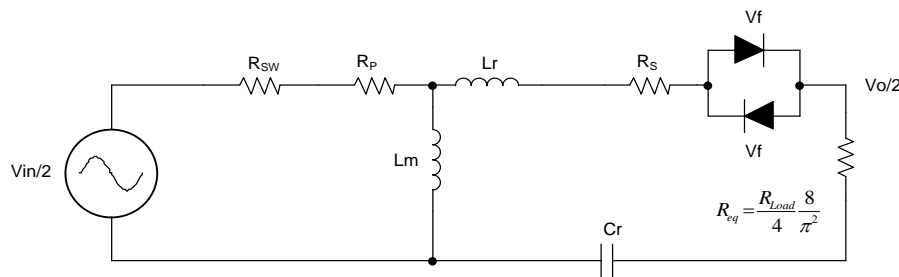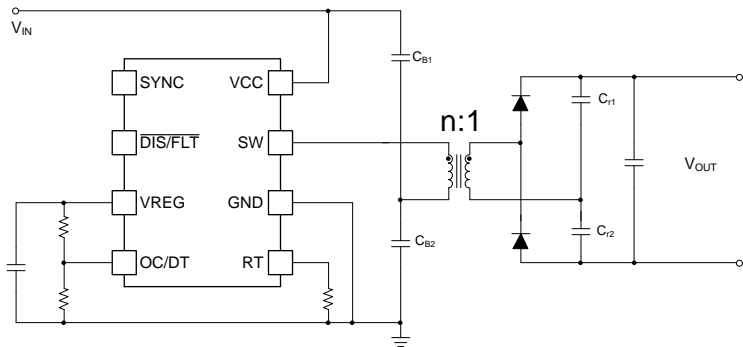

$$\frac{v_o}{v_{in}} \approx \frac{L_m}{L_m + L_{rp}} \frac{v_{in}}{n} - \frac{\pi^2}{2} \left(\frac{R_{SW}}{n^2} + \frac{R_P}{n^2} + R_S \right) \cdot I_O - 2v_f$$

- The voltage regulation is determined by transformer turns ratio and resistive loss, as well as the diode drop
- It is critical to keep the resistive loss low to get best load regulation


Illustration of voltage regulation

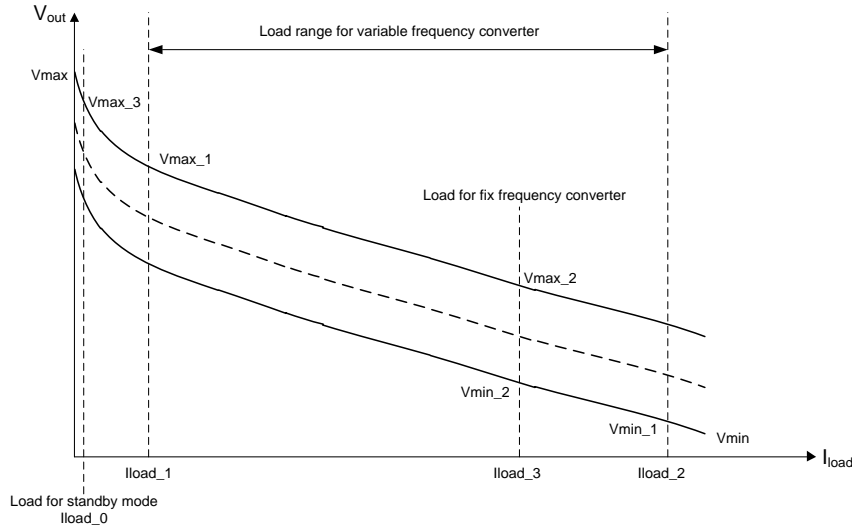

- For a fix switching frequency inverter, the gate driver load is fixed
 - The output voltage regulation can be very tight
- For a variable frequency inverter, the gate driver load varies
 - The output voltage varies more
- The standby mode load voltage tends to go up
 - It could be too high that need extra help from a Zener diode
 - It is mainly determined by the diode junction capacitor


	Normal operation		Standby mode load	Vout		
	Min load	Max load		Min	Max	Standby max
Fixed Fre.	I_{load_3}	I_{load_3}	I_{load_0}	V_{min_2}	V_{max_2}	V_{max_3}
Var. Fre.	I_{load_1}	I_{load_2}	I_{load_0}	V_{min_1}	V_{max_1}	V_{max_3}

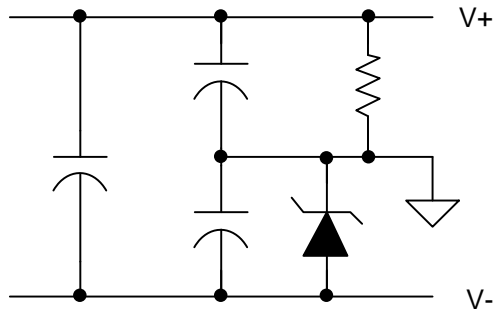Split single output voltage into dual outputs




Zener split

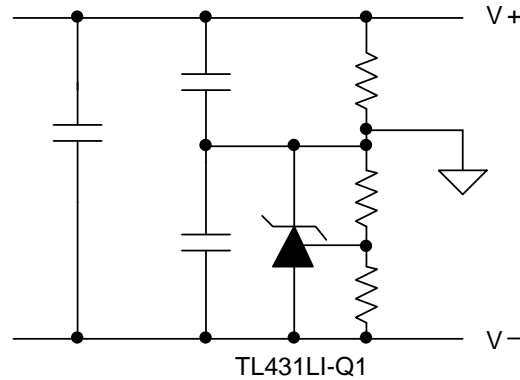- **Lowest cost**
- **Unregulated outputs**



Shunt Regulator

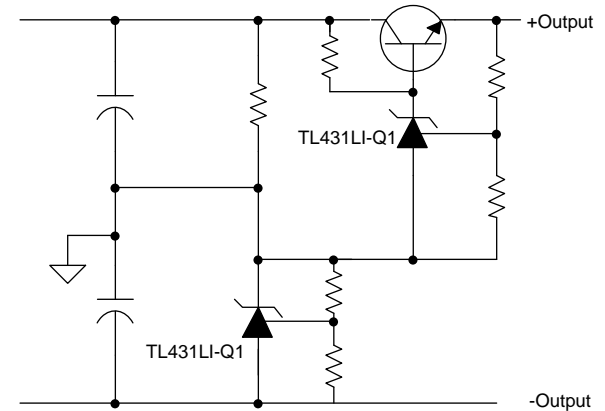- **Higher cost**
- **Regulated negative output**
- **Unregulated positive output**



Shunt Regulator & Linear regulator

- **Highest cost**
- **Regulated output**

UCC25800-Q1

Sampling



Low-cost LLC transformer driver with high performance

Features

- Operation from 9 V to 34 V (40 V Abs Max)
- 6 W from 24-V input, Up to 10 W from 34-V input
- Integrated half-bridge MOSFETs
- Programmable fixed switching frequency up to 1.2 MHz
 - 1.2 MHz default, resistor settable 100 kHz – 1 MHz
 - Frequency accuracy +/-6% maximum over temperature
 - External SYNC function
- Drive multiple transformers with one UCC25800-Q1
- Automatic dead time adjustment with programmable maximum
- Integrated soft-start
- Disable pin with fault code output
- Two-level over current protection
 - Programmable via external resistor
 - UCC25800L is latched after over current
 - UCC25800R is retry after over current
- Over Temperature Protection
 - 160°C Junction
 - 10°C Hysteresis
- AEC Q100 Qualified

Benefits

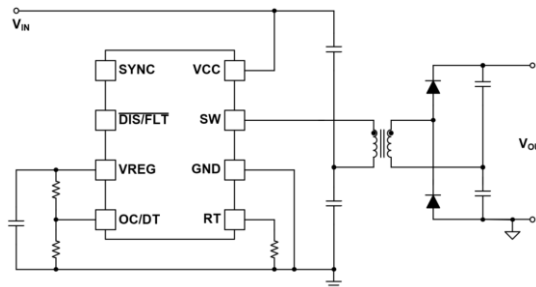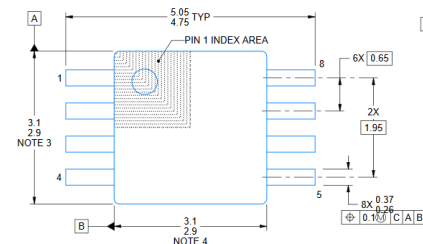- Low common mode noise due to minimal interwinding capacitance in transformer
- Simple design, highly integrated, no bootstrap capacitor
- High switching frequency for smaller size and more robustness




[Disclaimer: Specs, features & pinouts subject to change without prior notice.]

UCC25800-Q1 measurement data


UCC25800 EVM with LM5156 Pre-Regulator




Predictable Startup of +/- rails

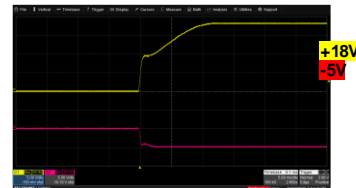

1% Load Regulation

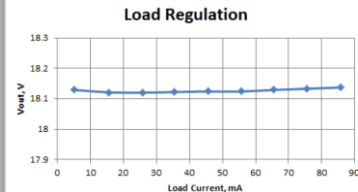


Surpasses CISPR 25 Class 5 EMI Standard

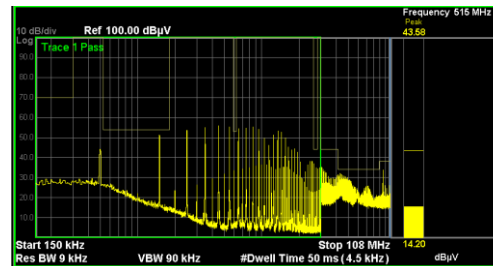


Pass - LLC Board Only with Filter

PARAMETER	SPECIFICATIONS
Input voltage range	6V – 26V
Output voltage and current	+18V / -5V
Switching frequency	2.2MHz and 500 kHz
Isolation	Yes, 2500 VAC (1 sec)
Topology	SEPIC + Open loop LLC transformer driver

Multiple outputs


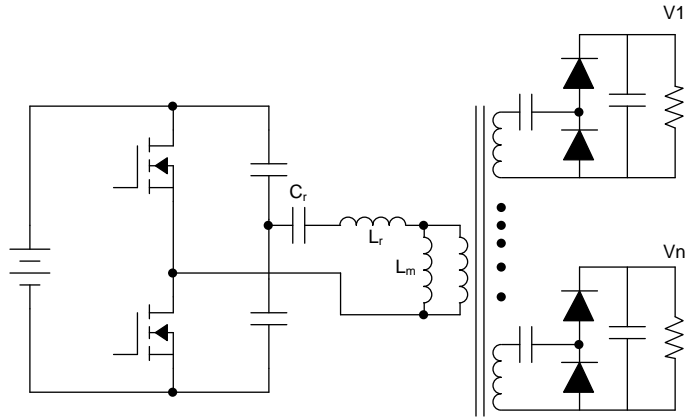


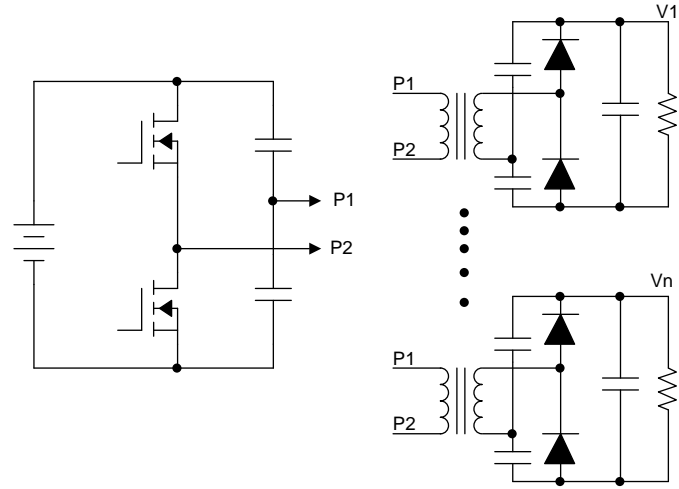Driving one transformer with multiple secondary side windings




Driving multiple two winding transformers

Example: driving multiple transformers

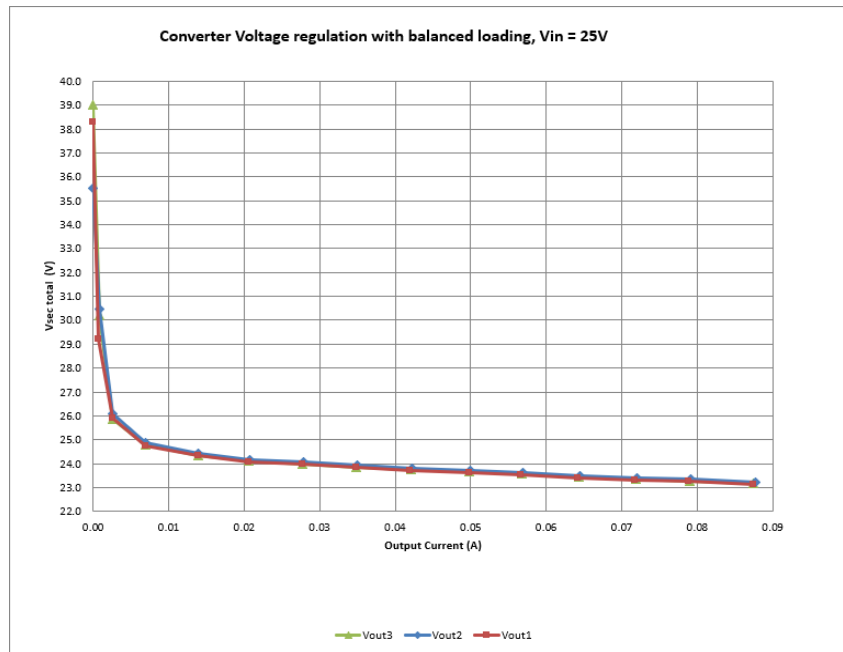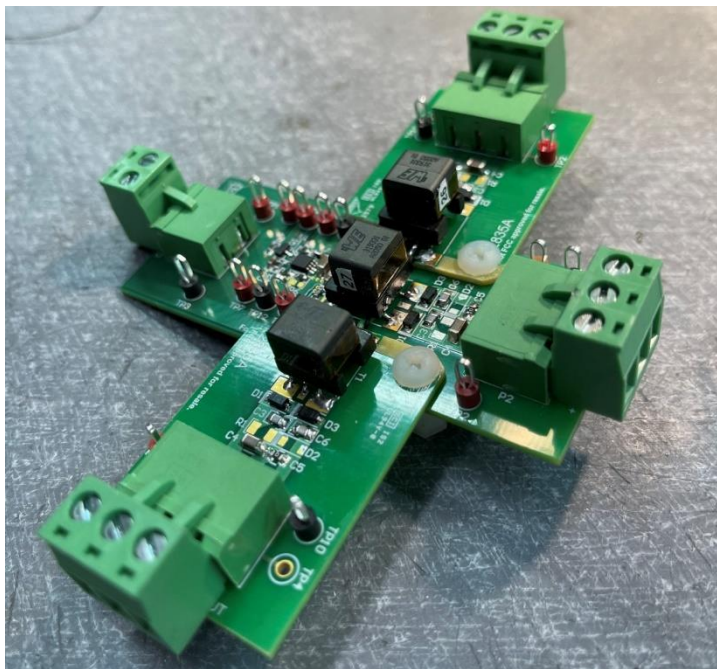


Single primary side power stage drives three transformers and secondary side circuits
Three matched output voltages are created

EMI noise performance comparison

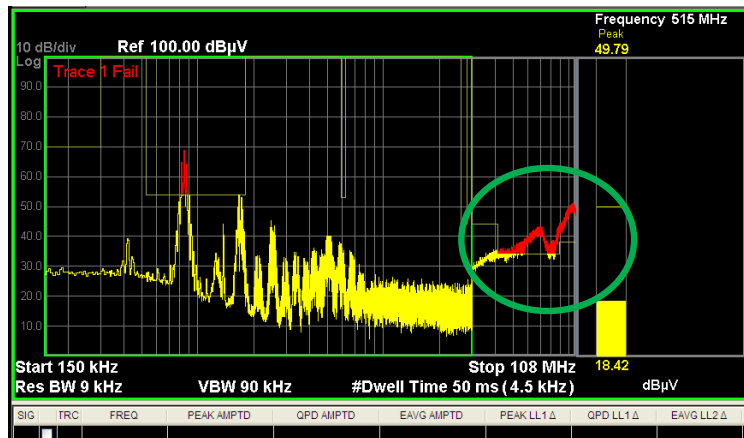


5-V push-pull

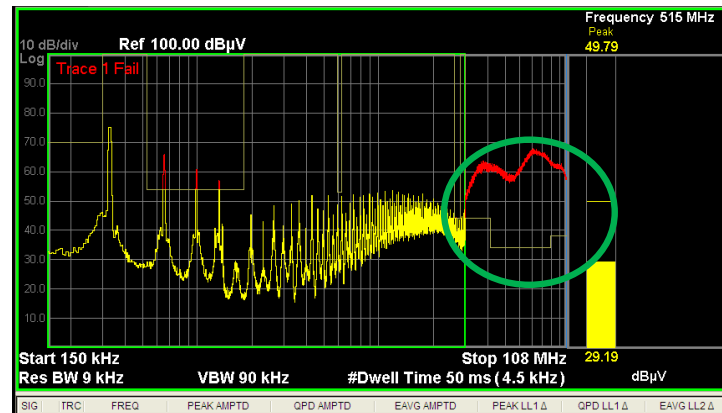

24-V Flyback

24-V LLC

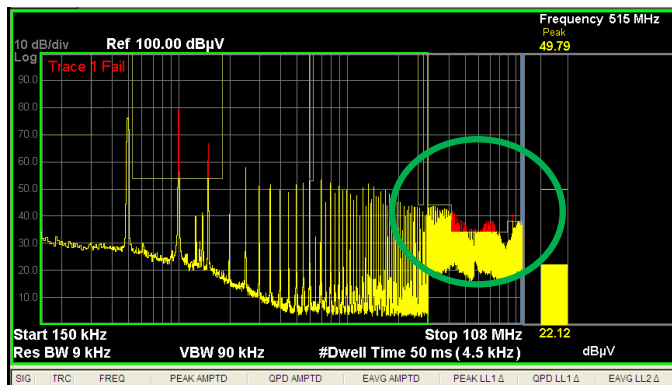


LLC has much lower high frequency EMI noise


*No EMI filter added

EMI noise when connected with inverter

Flyback



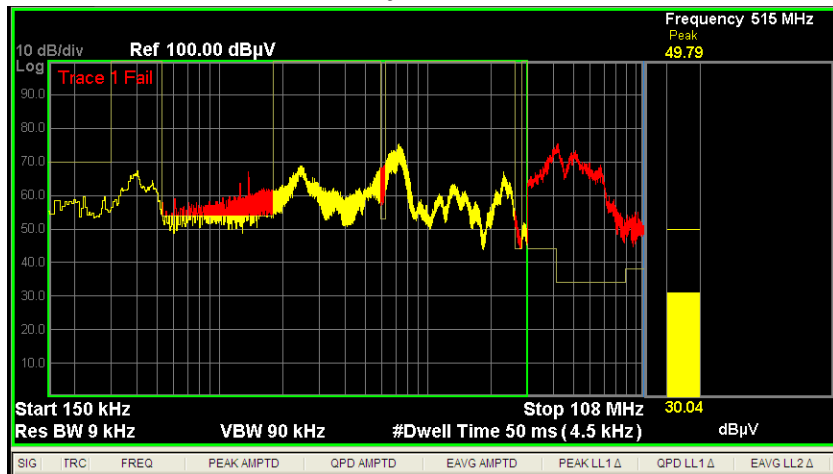


LLC

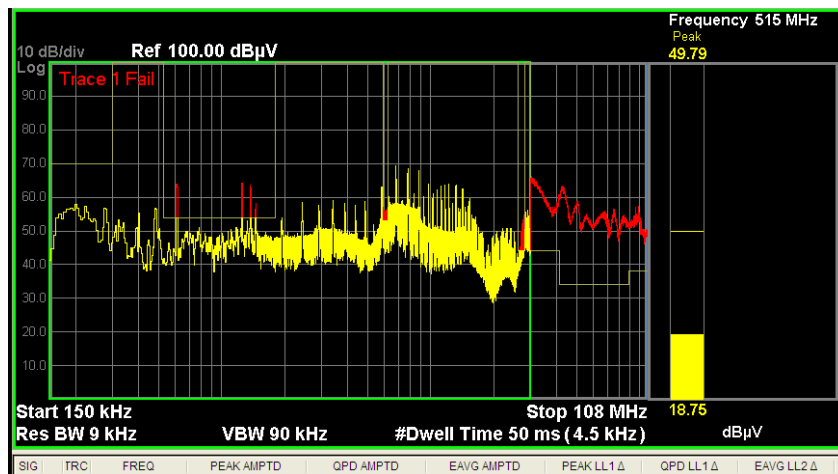


When connected with inverter and bias the isolated gate drivers, LLC solution provides a much lower EMI noise due to the less parasitic capacitance

CMTI performance

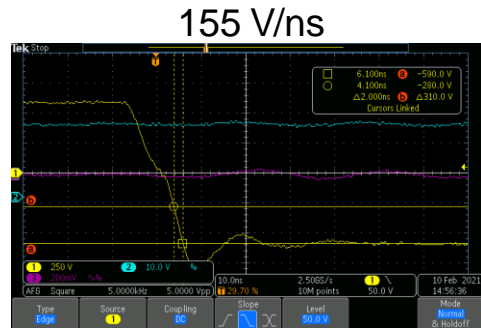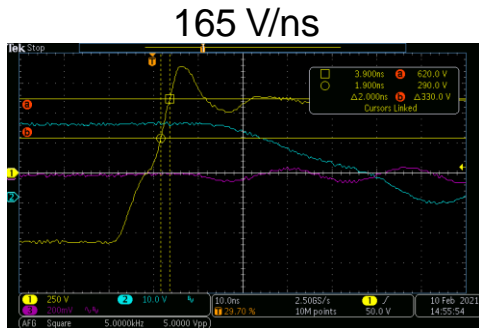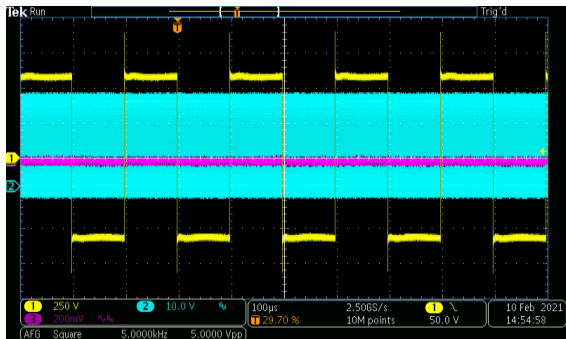


Switch node

Strike voltage

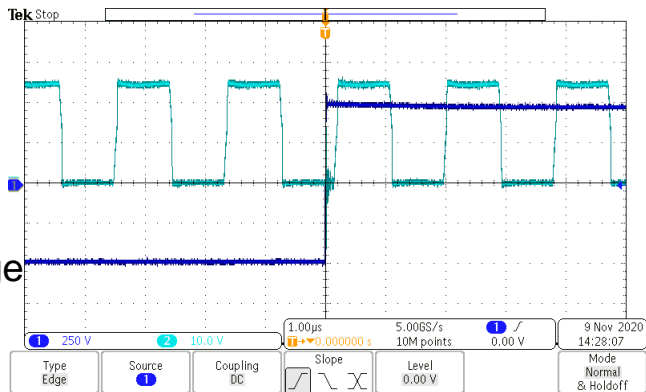

Switch node


Strike voltage

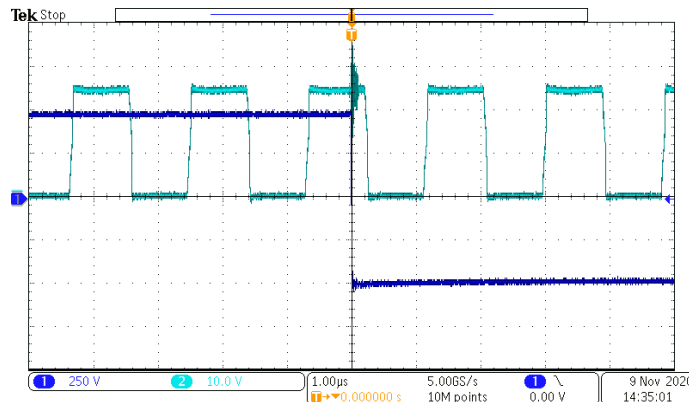

Operation is not affected by >150 V/ns CMTI

Transformer design considerations

- Transformer design is simple
 - Two windings
 - Turns ratio is roughly the voltage ratio between the input and output voltage (plus the diode drop)
 - Square voltage on primary side, setting up the volt-second rating
 - Lowest R_{ac} possible
 - No airgap
- Once the transformer is made, measure the leakage inductance from secondary side
 - Short the primary side while measuring
- Match the leakage inductance with resonant capacitor

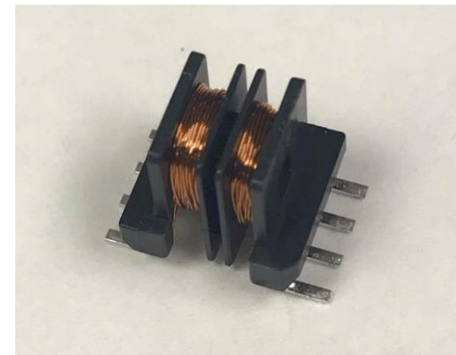

Part number (Würth)	Turn ratio	Leakage inductance	Input / Output
750319331	1:1	1.4 μH	24 V/24 V
750319177	1.67:1	1.48 μH	15 V/24 V
750319177	1:1.67	0.53 μH	24 V/15 V

Summary

- Isolated bias supply is needed for biasing the isolated gate drivers in the inverters
 - Open loop control provides a robust solution, less noise sensitive
- LLC topology is able to utilize the transformer leakage inductance and minimize the transformer primary side to secondary side parasitic capacitance
 - Less EMI noise
- The open loop LLC converter provides a simple, robust solution
 - Less EMI
 - High CMTI
 - Good voltage regulation
 - Multiple output capability



©2021 Texas Instruments Incorporated. All rights reserved.

The material is provided strictly "as-is" for informational purposes only and without any warranty.
Use of this material is subject to TI's **Terms of Use**, viewable at [TI.com](https://www.ti.com)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated