

High-Performance Analog Products

Analog Applications Journal

Fourth Quarter, 2010



IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

Contents

Introduction	4
Data Acquisition	
Clock jitter analyzed in the time domain, Part 2	5
High-speed ADCs are often used in undersampling applications. At higher input frequencies, clock jitter can become a dominant factor in limiting SNR. This article presents a method of calculating the ADC's SNR by using the combined clock and aperture jitter determined in Part 1. The results are then compared against actual measurements.	
The IBIS model: A conduit into signal-integrity analysis, Part 1	11
TI is developing a new arsenal of digital input/output buffer information specification (IBIS) simulation models to meet a variety of customer needs. This article, the first of a three-part series, shows the fundamental elements of IBIS models and how they are generated in the SPICE environment.	
Power Management	
A low-cost, non-isolated AC/DC buck converter with no transformer	16
Off-line equipment such as a smart meter or a power monitor has electronics that require non-isolated DC power under 10 W. Until recently, the typical low-power DC rail circuit was extremely inefficient and cumbersome to design. This article presents a unique solution for an ultra-low-cost DC power rail with an innovative gate-drive circuit for a hysteretic buck controller.	
Save power with a soft Zener clamp	19
Flyback converters are popular because they are inexpensive, they can be isolated, and they can have multiple output voltages. Multiple outputs, however, can be a problem if tight regulation is required on more than the main output. This article shows how a soft Zener clamp can be used as a compromise in limiting output voltages when the load on the main output voltage suddenly changes.	
Interface (Data Transmission)	
Interfacing high-voltage applications to low-power controllers	20
Industrial applications often require interfacing high-voltage potentials to input ports of low-voltage microcontrollers and processors. This article is about a new generation of interface circuits called digital-input serializers. These low-power and cost-effective devices can sense input voltages ranging from 6 V up to 300 VDC and can convert them into 5-V serial data streams.	
Amplifiers: Op Amps	
Using single-supply fully differential amplifiers with negative input voltages to drive ADCs	26
Split-supply amplifiers are not required to amplify signals that swing around ground. This article discusses how to use a fully differential amplifier (FDA) like the THS4521 with a single +5-V supply to condition single-ended input signals that swing around ground (± 0 V) to drive a differential-input ADC. A link to a TINA-TI™ SPICE file is included to illustrate implementation.	
Index of Articles	29
TI Worldwide Technical Support	34

To view past issues of the
***Analog Applications Journal*, visit the Web site**
www.ti.com/aaj

Introduction

Analog Applications Journal is a collection of analog application articles designed to give readers a basic understanding of TI products and to provide simple but practical examples for typical applications. Written not only for design engineers but also for engineering managers, technicians, system designers and marketing and sales personnel, the book emphasizes general application concepts over lengthy mathematical analyses.

These applications are not intended as “how-to” instructions for specific circuits but as examples of how devices could be used to solve specific design requirements. Readers will find tutorial information as well as practical engineering solutions on components from the following categories:

- Data Acquisition
- Power Management
- Interface (Data Transmission)
- Amplifiers: Op Amps

Where applicable, readers will also find software routines and program structures. Finally, *Analog Applications Journal* includes helpful hints and rules of thumb to guide readers in preparing for their design.

Clock jitter analyzed in the time domain, Part 2

By Thomas Neu

Systems and Applications Engineer

Introduction

Part 1 of this three-part article series focused on how to accurately estimate jitter from a clock source and combine it with the aperture jitter of an ADC. In this article, Part 2, that combined jitter will be used to calculate the ADC's signal-to-noise ratio (SNR), which will then be compared against actual measurements.

Measurements with filtered sampling clock

An experiment was set up to see how well the measured clock phase noise matched the clock jitter extracted from the ADC's measured SNR. As shown in Figure 11, a Texas Instruments (TI) CDCE72010 with a Toyocom 491.52-MHz VCXO was used to generate a 122.88-MHz sampling clock, and the filtered phase-noise output was measured with the E5052A from Agilent. Two different TI data converters (ADS54RF63 and ADS5483) were evaluated by using an input frequency whose SNR was predominantly limited by the sampling-clock jitter. The size of the fast Fourier transform (FFT) was chosen to be 131,000 points.

The plot in Figure 12 illustrates the measured output phase noise of the filtered CDCE72010 LVCMOS output. An FFT size of 131,000 points sets the lower integration bandwidth to ~500 Hz. The upper integration limit is set by the bandpass filter, whose effect is clearly visible in the phase-noise plot. Phase noise beyond the bandpass-filter limit shown in the plot is the noise floor of the E5052A and should not be included in the jitter calculation. The integration of the filtered phase-noise output resulted in a clock jitter of ~90 fs.

Next, a baseline for the thermal noise was established. Both ADCs were sampled with a filtered sampling clock directly from the clock-source generator with ~35 fs of jitter, and the CDCE72010 was bypassed. The input frequency was set to 10 MHz, where no impact on the SNR from clock jitter was expected. Then the aperture jitter for each ADC was determined by increasing the input frequency to where

Figure 11. Test setup for correlation with filtered clock


 


Figure 12. Measured phase noise of the filtered clock

 

the SNR was mainly jitter-limited. Since the sampling-clock jitter is much lower than the estimated ADC aperture jitter, the calculation should be very accurate. It is also important to remember that the output amplitude of the clock


source should be increased (but not so much that it exceeds the maximum ratings of the ADC), boosting the slew rate of the clock signal until the SNR levels off.

Since it is known that the external clock jitter from the filtered output of the clock-source generator is ~35 fs, the ADC aperture jitter can be calculated by using the measured SNR results and solving Equations 1, 2, and 3 in Part 1 (Reference 1) for aperture jitter. Please see Equation 4 below. The measured SNR results as well as the calculated aperture jitter for each ADC are listed in Table 3.

With the ADC aperture jitter and the sampling-clock jitter of the CDCE72010, the ADC's SNR can be calculated and compared against the actual measurement. Using the ADC aperture jitter permits the sampling-clock jitter of the CDCE72010 to be calculated from the measured SNR values, as illustrated in Table 4. At first glance the predicted SNR values are somewhat close to the measured values. However, comparing the calculated sampling-clock jitter for the two ADCs against the measured value of 90 fs reveals a different picture. There is quite a bit of mismatch.

The reason for the mismatch is that the calculated aperture jitter is based on the fast slew rate of the clock-source generator. The bandpass filter on the LVCMOS output of the CDCE72010 eliminates the higher-order harmonics of

Figure 13. Impact of clock filter on sampling clock's slew rate

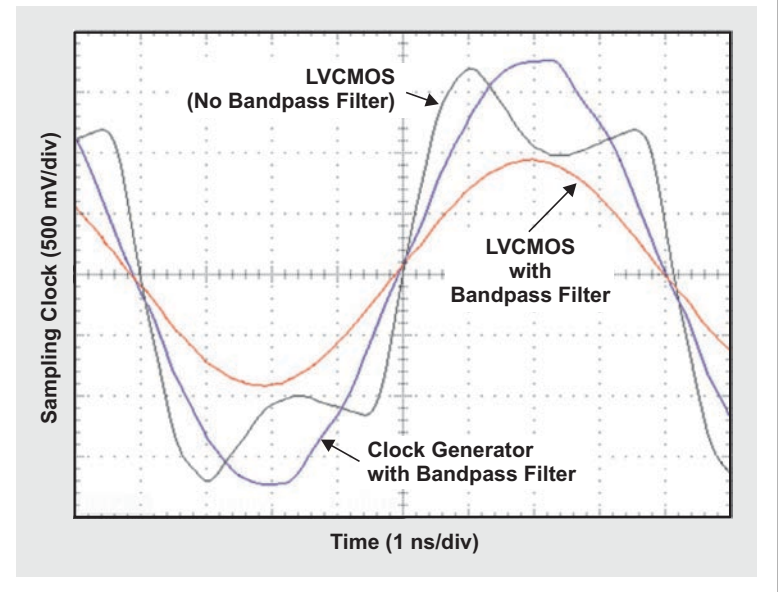

the clock signal that help create fast rising and falling edges. The scope plot in Figure 13 demonstrates how the bandpass filter drastically reduces the slew rate of the unfiltered LVCMOS output and turns the square wave into a sine wave.

$$t_{\text{Aperture_ADC}} = \sqrt{\left[\frac{\sqrt{\left(10^{\frac{\text{SNR}_{\text{Measured}}}{20}}\right)^2 - \left(10^{\frac{\text{SNR}_{\text{Thermal Noise}}}{20}}\right)^2}}{2\pi \times f_{\text{IN}}}\right]^2 - (t_{\text{Jitter,Clock_Input}})^2} \quad (4)$$

Table 3. Measured SNR and calculated jitter

DEVICE	THERMAL NOISE (MEASURED SNR AT $f_{\text{IN}} = 10$ MHz) (dBFS)	MEASURED SNR AT HIGH f_{IN} (JITTER-LIMITED) (dBFS)	CALCULATED APERTURE JITTER (fs)
ADS54RF63	64.4	61.0 ($f_{\text{IN}} = 1$ GHz)	~115
ADS5483	79.1	78.2 ($f_{\text{IN}} = 100$ MHz)	~85


Table 4. SNR results with 90-fs clock jitter

DEVICE	CALCULATED SNR WITH 90-fs CLOCK JITTER (dBFS)	MEASURED SNR (dBFS)	CALCULATED JITTER FROM MEASURED SNR (fs)
ADS54RF63 ($f_{\text{IN}} = 1$ GHz)	59.9	58.7	~130
ADS5483 ($f_{\text{IN}} = 100$ MHz)	77.8	77.1	~125

One way to improve the slew rate is to add a low-noise RF amplifier with a fair amount of gain between the LVCMOS output of the CDCE72010 and the bandpass filter (see Figure 14). The amplifier should be placed before the filter so that its noise contribution to the clock signal is limited to the filter bandwidth and not to the clock input bandwidth of the ADC. Since the amplifier in the next experiment has a gain of 21 dB, a variable attenuator was added after the bandpass filter to match the slew rate of the filtered LVCMOS signal to the filtered output of the clock generator. The attenuator also protects the clock input of the ADCs from exceeding the maximum ratings.

With the low-noise RF amplifier included in the clock's input path, the SNR measurement at high input frequency was repeated for both data converters. The results are shown in Table 5. It can be observed that the measured SNR matches the predicted SNR very well. Using Equation 5 below provided calculated clock-jitter values that are within 5 fs of the 90-fs clock jitter, which was derived from the phase-noise measurement.

Figure 14. RF amplifier added in front of bandpass filter to reduce slew rate

 

Experiment with unfiltered sampling clock


To stress the importance of filtering the sampling clock, the clock bandpass filter was removed from the CDCE72010 output in the next experiment. The E5052A phase-noise analyzer was used to capture the clock phase noise as shown in the setup in Figure 15. Unfortunately, however,

Table 5. SNR results with 90-fs clock jitter and RF amplifier

DEVICE	CALCULATED SNR WITH 90-fs CLOCK JITTER (dBFS)	MEASURED SNR WITH RF AMPLIFIER (dBFS)	CALCULATED JITTER FROM MEASURED SNR (fs)
ADS54RF63 ($f_{IN} = 1$ GHz)	59.9	60.0	~85
ADS5483 ($f_{IN} = 100$ MHz)	77.8	77.6	~95

$$t_{\text{Jitter,Clock_Input}} = \sqrt{\left[\frac{\sqrt{\left(10^{-\frac{\text{SNR}_{\text{Measured}}}{20}}\right)^2 - \left(10^{-\frac{\text{SNR}_{\text{Thermal Noise}}}{20}}\right)^2}}{2\pi \times f_{IN}} \right]^2 - (t_{\text{Aperture_ADC}})^2} \quad (5)$$

Figure 15. Test setup for unfiltered sampling-clock input

 

the analyzer measures the phase noise only up to a 40-MHz offset of the carrier frequency and doesn't give any clue about the phase-noise characteristic beyond that point.

To set the correct upper integration limit when an unfiltered clock is used, the sampling theory has to be reviewed again. The unfiltered clock output of the CDCE72010 looks like a square wave with fast rising and falling edges caused by the higher-order harmonics of the fundamental sinusoid of the clock frequency. These harmonics have lower amplitude than the fundamental, and their amplitude decreases as the harmonic order increases.

At the sampling instant, both the fundamental sine wave and the higher-order harmonics mix with the input signal as illustrated in Figure 16. (For simplification, only one harmonic is shown.) Therefore, the phase noise around

the third-order harmonic (for example) mixes with the input signal, and the third harmonic creates a mixing product as well. However, since the third harmonic of the clock signal has lower amplitude, the amplitude of this mixing product is also reduced.

When the two sampled signals are combined, it can be seen that the overall degradation of the phase noise caused by the third harmonic becomes minimal once the amplitude difference exceeds ~3 dB. Since the crossover point between the fundamental and the third harmonic is at $2 \times f_s$, integrating the wideband phase noise to $2 \times f_s$ should give a fairly accurate result.

As shown later in Figure 19, the phase noise of the unfiltered LVCMOS output of the CDCE72010 levels out around -153 dBc/Hz, starting at an offset frequency of

Figure 16. Clock fundamental and its harmonics mix with input signal at sampling instant

 


Table 6. SNR results with 1.27-ps clock jitter


DEVICE	CALCULATED SNR WITH 1.27-ps CLOCK JITTER (dBFS)	MEASURED SNR (dBFS)	CALCULATED JITTER FROM MEASURED SNR (fs)
ADS54RF63 ($f_{IN} = 1$ GHz)	42.8	51.35	~450

~10 MHz, which is likely due to the thermal noise of the LVCMOS output buffer. The ADS54RF63 EVM has a clock input bandwidth of ~1 GHz (limited by the transformer); hence, theoretically the phase noise should be integrated to ~1 GHz (rolling off at 3 dB at a 900-MHz offset). This would result in ~1.27 ps of sampling-clock jitter and would reduce the SNR at $f_{IN} = 1$ GHz to ~42.8 dBFS!

The actual SNR measurement was quite a bit better than that, as demonstrated in Table 6. There is a huge gap between the calculated clock jitter and the SNR compared to the actual measurement. This suggests that the phase noise of the LVCMOS output indeed is limited well before the 900-MHz offset boundary set by the transformer.

To prove that the phase noise of the unfiltered clock signal needs to be integrated to roughly twice the sampling frequency, the following experiment was set up: Different low-pass filters were added between the CDCE72010 output and the clock input of the ADS54RF63.

It is important to remember that a low-pass filter with a bandwidth of less than 3x the clock frequency reduces the slew rate of the clock signal just like the bandpass filter did in the earlier experiment. The low-pass filter eliminates the higher-order harmonics that produce the faster rise time and slew rate of the clock signal, thus increasing the aperture jitter of the ADC. For that reason, the same low-noise RF amplifier from the earlier experiment was added to the clock path, and the slew rate was matched to the signal generator by using the variable attenuator (see Figure 17).

 Figure 17. RF amplifier added in front of low-pass filter to reduce slew rate

Using low-pass filters with different corner frequencies on the sampling clock of the ADS54RF63 (as depicted in Figure 18) resulted in the interesting values in Table 7. The results of this experiment suggest that the phase-noise impact of the LVCMOS output on the clock jitter is limited to roughly 200 to 250 MHz, which corresponds to an 80- to 130-MHz offset from the 122.88-MHz clock signal and is approximately 2x the sampling frequency. Therefore,

Table 7. Measured SNR for ADS54RF63

FILTER TYPE	MEASURED SNR AT $f_{IN} = 1$ GHz (dBFS)
Unfiltered Clock	51.35
140-MHz Low-Pass Filter	54.01
200-MHz Low-Pass Filter	51.81

 
Figure 18. Different low-pass filters limit phase noise

Table 8. SNR results with 445-fs clock jitter

DEVICE	CALCULATED SNR WITH 445-fs CLOCK JITTER (dBFS)	MEASURED SNR (dBFS)	CALCULATED JITTER FROM MEASURED SNR (fs)
ADS54RF63 ($f_{IN} = 1$ GHz)	51.6	51.35	~460
ADS5483 ($f_{IN} = 100$ MHz)	71.2	70.60	~480

Table 9. Measured SNR with filtered and unfiltered clock

DEVICE	BANDPASS-FILTERED CLOCK (dBFS)	UNFILTERED CLOCK (dBFS)	BANDPASS-FILTERED CLOCK WITH EXTERNAL AMPLIFIER (dBFS)
ADS54RF63 ($f_{IN} = 1$ GHz)	58.7	51.35	60.0
ADS5483 ($f_{IN} = 100$ MHz)	77.1	70.60	77.6

extending the wideband phase noise out to a 123-MHz offset results in a clock jitter of ~445 fs, as can be seen in Figure 19. Ideally the lower integration limit should be at 500 Hz (because of the chosen 131,000-point FFT); however, the jitter contribution from a 500-Hz to 1-kHz offset is extremely low, so it was neglected here in this measurement for simplification.

With the adjusted phase-noise plot, the calculated jitter matches the SNR measurement results very well, to within 10 to 30 fs for both the ADS54RF63 and the ADS5483 (see Table 8). Considering that there is probably a minor clock-jitter contribution from the phase noise around the third harmonic, the calculated SNR is a very close estimation.

Conclusion

This article has shown how to properly estimate a data converter’s SNR when a filtered or unfiltered clock source is used. The results are summarized in Table 9.

While a bandpass filter on the clock input is necessary to minimize the clock jitter, experiments showed that it reduces the clock slew rate and degrades the aperture jitter of the ADC. Therefore, the optimum clocking solution consists of a bandpass filter to limit the phase-noise contribution as well as some amplification of the clock amplitude and slew rate to minimize the aperture jitter of the ADC.

Part 3 of this article series will show some practical implementations on how to boost the performance of existing clocking solutions.

Reference

For more information related to this article, you can download an Acrobat® Reader® file at www.ti.com/lit/litnumber and replace “*litnumber*” with the **TI Lit. #** for the materials listed below.

Document Title

TI Lit. #

1. Thomas Neu, “Clock jitter analyzed in the time domain, Part 1,” *Analog Applications Journal* (3Q 2010) slyt379


Related Web sites

dataconverter.ti.com

www.ti.com/sc/device/partnumber

Replace *partnumber* with ADS5483, ADS54RF63, or CDCE72010

Figure 19. Unfiltered phase noise extrapolated to 123-MHz offset

 

The IBIS model: A conduit into signal-integrity analysis, Part 1

By Bonnie Baker

Senior Applications Engineer

Texas Instruments (TI) is developing a new arsenal of digital input/output buffer information specification (IBIS) simulation models to meet a variety of customer needs. This style of model (Figure 1) might be used in a simulation environment to help solve board-level overshoot, undershoot, or crosstalk problems, to name a few. On a more fundamental level, IBIS models provide useful product information, such as the pin capacitance and parasitics or the rise/fall times of the digital output buffers.

This article, Part 1 of a three-part series, shows the fundamental elements of IBIS models and how they are generated in the SPICE environment. Part 2 will investigate IBIS-model validation. Part 3 will show how IBIS users investigate signal-integrity issues and problems during the development phase of a printed circuit board (PCB).

As Figure 1 shows, the IBIS model contains the package parasitics and the silicon input capacitance (C_{comp}) for all pins. The IBIS model also includes tables of data that represent the product's DC operation within the product's operating range and beyond the power supplies (power-clamp, ground-clamp, pullup, and pulldown boxes). In addition, the output-model structure in Figure 1 provides tables that represent the AC or transient response (rising ramp and falling ramp) within the operating range of the product.

An IBIS model includes AC and DC tables that reflect the operation of the product. This type of model has pin- and package-parasitics elements that complete the interface to the PCB. The simulation model produces the performance of the digital buffer's interaction with the PCB but omits

interactions with nodes inside the chip. The IBIS model simulates the system-level PCB behavior, specifically modeling the connection from the outside world to the product's digital input/output (I/O) buffers.


Foundations of the IBIS model

An IBIS model contains information relating to the digital buffers of an IC chip. The core of the IBIS model contains the product buffer's DC information in the form of current-voltage (I-V) tables, and its AC information in the form of voltage-time (V-t) tables. If these tables are generated with the product's SPICE deck, it is possible to include nominal, strong, and weak corners with variations in process, supply voltage, and temperature. Table 1 shows an example of six corners for the DAC8812, which is a dual serial-input, 16-bit multiplying digital-to-analog converter. Three of these corners (1, 2, and 3) are centered around a nominal digital power-supply voltage (V_{DD}) of 3.3 V. The other

Table 1. Process, voltage, and temperature corners for DAC8812 IBIS model

CORNER NUMBER	PROCESS	VOLTAGE (V)	TEMPERATURE (°C)
1	Weak	3.0	85
2	Nominal	3.3	25
3	Strong	3.6	-40
4	Weak	4.5	85
5	Nominal	5.0	25
6	Strong	5.5	-40

Figure 1. Block diagram of IBIS model with digital I/O buffers

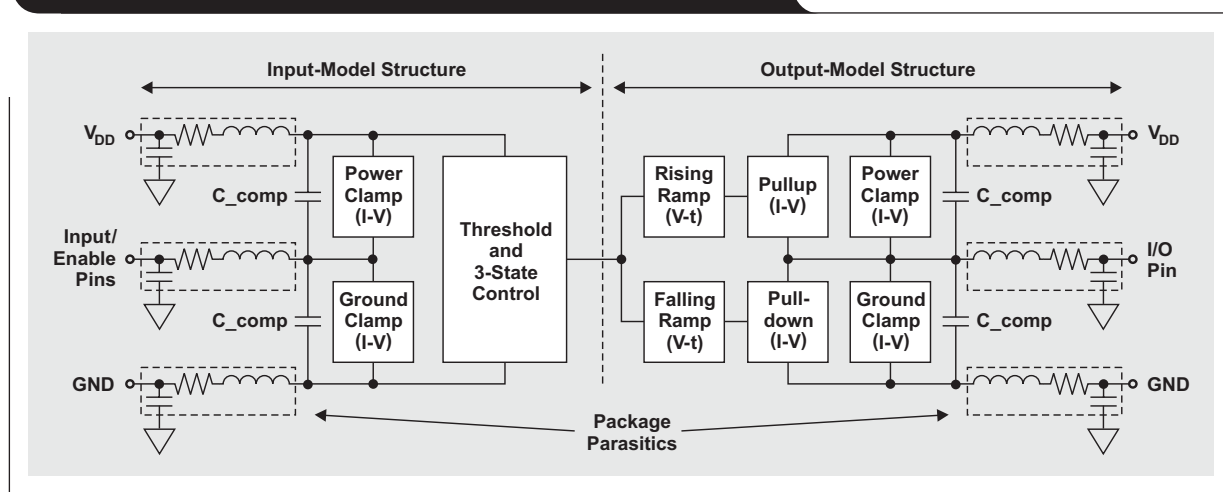

three corners (4, 5, and 6) are centered around a nominal V_{DD} of 5.0 V.


An IBIS model created at the bench is limited to the tests from one to a few devices. The bench-tested IBIS models usually do not show silicon-process variations.

IBIS models can contain data for any of several different buffer types: input, output, I/O, tri-state, terminator, output_open_source, output_open_sink, I/O_open_source, I/O_open_sink, input_ECL, output_ECL, and I/O_ECL.

The voltage at an input or output buffer's pin in the DC tables extends beyond the supply voltage (V_{DD}) from $-V_{DD}$ to $2 \times V_{DD}$. This exercises the product buffer's ESD structures beyond the supply voltage. In this manner, IBIS models are capable of showing the overshoot and undershoot responses of poorly terminated PCB signals. IBIS models contain I-V data for input and output buffers.


The example of an input buffer in Figure 2 shows the input buffer, the ESD cells, and the buffer's capacitance (C_{comp}). An IBIS model for an input buffer provides I-V tables of data that extend beyond ground and the supply

Figure 2. Example of input buffer's basic functionality for an IBIS model

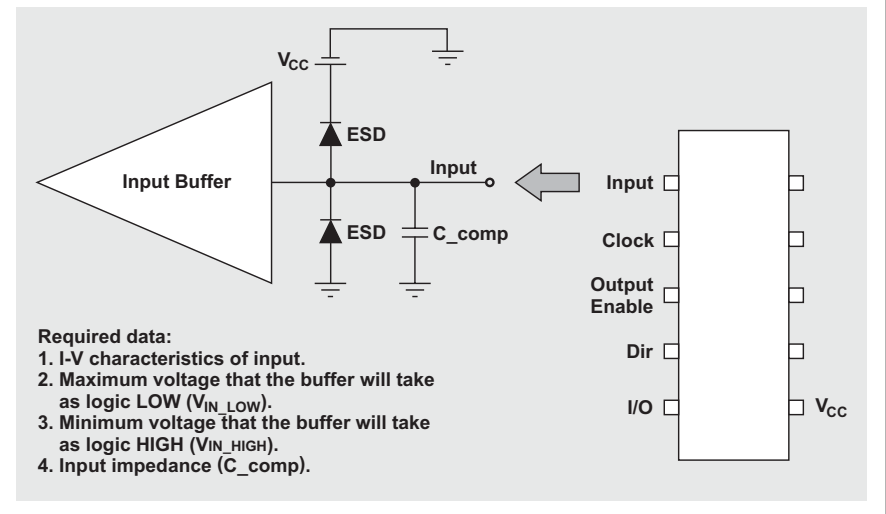

voltage (V_{DD}). Note that the IBIS model does not require circuitry beyond the immediate interface. IBIS models do not reflect the product's interior logic and interactions. Figure 3 shows a composite graphical example of an input buffer's power-clamp and ground-clamp I-V tables from an IBIS model.

Figure 3. Graphical representation of IBIS model's I-V tables

 

V-t tables represent the AC behavior of an output buffer like the one in Figure 4. With V-t tables, the output buffer's pin remains inside the product's power-supply rails. IBIS models are capable of simulating the buffer within its operating range, exhibiting accurate simulations of rise and fall times.

Figure 4 shows the pullup and pull-down circuitry as well as the input capacitance of a two-state output buffer. With the output buffer, an IBIS model will typically have I-V tables as well as V-t tables. Once again, the IBIS model does not require circuitry beyond the immediate interface because the model does not reflect the product's interior logic and interactions. Figure 5 shows a graphical example of the rising-time waveform from an IBIS model's V-t table.

Figure 4. Example of two-state output buffer's basic functionality for an IBIS model


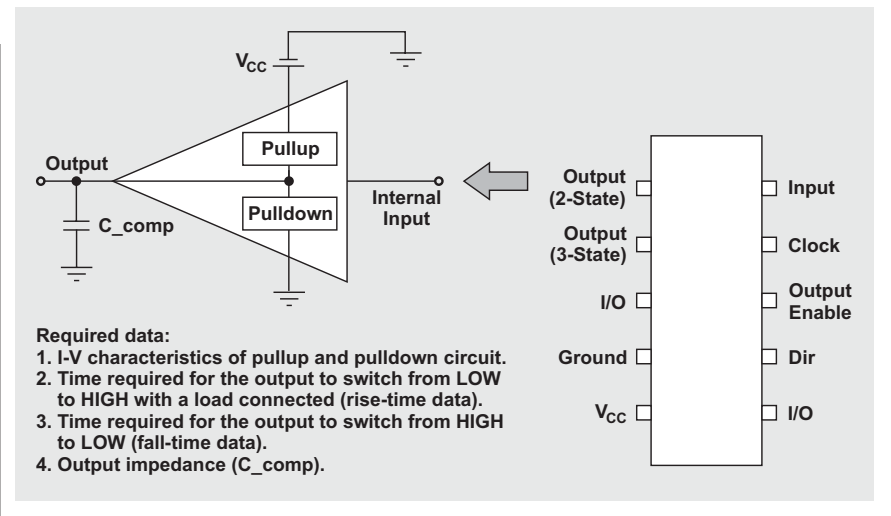


Figure 5. Graphical representation of rising time from IBIS model's V-t table

 

Format of IBIS model

The format of the IBIS model starts with a header, which is generated by hand and includes a description of the relevant IC or ICs. Following the IC description is general information about the model, including origination date, model source, and user notes. Figure 6 shows an example header of an IBIS model for TI's TMP512 and TMP513, which are temperature and supply-system monitors with an SMBus interface. The "Notes" section is the most important portion of the IBIS model header, where details of the model creation are found along with the basic format of the digital buffers.

The model header is followed by detailed information about the package(s) for the product(s), including values for pin resistance, inductance, and capacitance. To find the total capacitance for a specific pin, the capacitance values in this section are combined with the capacitance (C_{comp}) values called out next in the buffer tables. The core of the IBIS model follows with I-V and V-t tables buffer by buffer.

Extracting single-ended SPICE buffer data

The last section of this article will explain how to obtain the I-V and switching information (V-t) from a buffer's transistor-level model. An automated simulation template, an extraction tool (such as S2IBIS3), or manual simulations can be used. This discussion will include only totem-pole CMOS structures.

Extracting I-V data from SPICE simulations

To extract the I-V data for an IBIS model from a SPICE input buffer, the buffer pad is connected to an independent voltage source (V_{SOURCE}). Once the buffer's input is set to its desired state (LOW, HIGH, or OFF), V_{SOURCE} is exercised with a DC-analysis function over the sweep range of $-V_{SWEEP}$ to $2 \times V_{SWEEP}$, where the V_{SWEEP} limit is set by the product's supply voltage (V_{DD}). For instance, if the buffer is powered by a 5-V supply, the range of V_{SWEEP} will be -5 V to 10 V. While performing this sweep, the simulator records the current that goes into the buffer.

If the buffer is configured in a high-impedance state (OFF), the data collected produces the ground-clamp and power-clamp tables. The data in the ground-clamp table is referenced to ground, and the data in the power-clamp table is referenced to V_{DD} .

Extracting the I-V data for an output buffer's IBIS model results in a pulldown table and a pullup table. Data for the pulldown table is collected while the buffer is in an output LOW state. Data for the pullup table is collected while the buffer is in an output HIGH state. Data in the pulldown table is referenced to ground, and data in the pullup table is referenced to V_{DD} .

Figure 6. IBIS model header for TMP512 and TMP513

```

*****
|Texas Instruments Incorporated
|Temperature and Supply System Monitors SMBus interface
|
|Marketing part#      Digital Voltage   Analog Voltage   Package   # Pins
|                    Range             Range            Type
|TMP512AIDG4         2.1V to 3.6V    3.0V to 26V    SO-14     14
|TMP512AIDRG4        2.1V to 3.6V    3.0V to 26V    SO-14     14
|
|TMP513AIDG4         2.1V to 3.6V    3.0V to 26V    SO-16     16
|TMP513AIDRG4        2.1V to 3.6V    3.0V to 26V    SO-16     16
|TMP513AIRSATG4     2.1V to 3.6V    3.0V to 26V    QFN-16    16
|TMP513AIRSARG4     2.1V to 3.6V    3.0V to 26V    QFN-16    16
*****
|[IBIS Ver]          4.0
|[File name]         tmp512_3.ibs
|[File Rev]          1.0
|[Date]              04/14/2010
|[Source]            Texas Instruments Incorporated.
                    Analog-eLab , HPA
                    12500 TI Blvd
                    Dallas, TX -75243
                    For Support e-mail: elab_ibis@list.ti.com

|[Notes]             Revision History:
                    1.0: 04/14/2010
                    - Initial version of the model
                    - Initial Model generated from simulations in TISPICED
                    - Model not matched to measurements
                    - Non-monotonic warnings - combined pulldown and pullup data
                    The GPIO non-monotonic current delta is less than 1 mA in a
                    full-scale range of ~95 mA. Given these conditions, these
                    warnings are deemed insignificant.
                    1.1: 04/18/2010 corrected spelling errors

|[Disclaimer]
|
|This product is designed as an aid for customers of Texas Instruments.
|No warranties, either expressed or implied, with respect to this third
|party software (if any) or with respect to its fitness for any
|particular purpose is claimed by Texas Instruments or the author. The
|software (if any) is provided solely on an "as is" basis. The entire
|risk as to its quality and performance is with the customer
|
|[Copyright] (C) Copyright 2009 Texas Instruments Incorporated.
                    All rights reserved.

```

Extracting V-t data from SPICE simulations

When a CMOS buffer is modeled, the required simulations that relate to the ramp rate and V-t tables are straightforward. For each simulation corner (typical, minimum, and maximum), there are four V-t data sets. Data for two of the waveforms is gathered by switching the buffer output from LOW to HIGH with the load referenced to a low voltage. Data for the other two waveforms is collected with a load referenced to V_{DD} . For the latter two curves, the buffer's output switches from HIGH to LOW. From these simulations, the ramp rate or dV/dt ratio is extracted as the device is switching HIGH against a low-voltage reference and switching LOW against a high-voltage reference.

Required and recommended IBIS-model curves

There is a variety of buffer types that the IBIS standard describes with I-V and V-t tables. Tables 2 and 3 from Reference 1 list the required and recommended buffer data for each type of buffer.

Conclusion

An IBIS model assists PCB designers during their evaluations of signal-integrity issues and problems. The model's silicon-based DC and AC data facilitates the evaluation of over-power-supply behavior as well as rise- and fall-time behavior. In Part 2, the validity of the IBIS model will be evaluated by verifying that it meets IBIS standards and by comparing it to SPICE simulations.

References

1. The IBIS Open Forum. (2005, Sept. 15). *IBIS Modeling Cookbook for IBIS Version 4.0* [Online]. Available: www.eda.org/ibis/cookbook/cookbook-v4.pdf
2. Roy Leventhal and Lynne Green, *Semiconductor Modeling for Simulating Signal, Power, and Electromagnetic Integrity*. New York: Springer Science+Business Media, LLC, 2006.

Related Web sites

dataconverter.ti.com
www.ti.com/sc/device/DAC8812
www.ti.com/sc/device/TMP512
www.ti.com/sc/device/TMP513

Table 2. Required and recommended I-V data versus IBIS buffer types

Model type	[Pullup]	[Pulldown]	[POWER Clamp]	[GND Clamp]	Notes
Input	n/a	n/a	Recommended	Recommended	
I/O	Required	Required	Recommended	Recommended	
I/O_open_sink I/O_open_drain	n/a	Required	Recommended	Recommended	1
I/O_open_source	Required	n/a	Recommended	Recommended	1
Open_sink Open_drain	n/a	Required	Recommended	Recommended	4
Open_source	Required	n/a	Recommended	Recommended	4
Output	Required	Required	Recommended	Recommended	4
3-state	Required	Required	Recommended	Recommended	2
Series_switch	n/a	n/a	n/a	n/a	3
Series	n/a	n/a	n/a	n/a	3
Terminator	n/a	n/a	Recommended	Recommended	3
Input ECL	n/a	n/a	Recommended	Recommended	
I/O ECL	Required	Required	Recommended	Recommended	2
Output ECL	Required	Required	Recommended	Recommended	4
3-state ECL	Required	Required	Recommended	Recommended	2

1. Keywords listing "n/a" may be included if the currents are set to 0 for all voltage points
2. Functionally similar to I/O, but without input threshold information (V_{inh} , V_{inl} , etc.)
3. Special syntax required; use of clamp data on pins that also feature buffers using these Model_types is allowed
4. Clamp data may technically be excluded; however, this data aids analysis of reflections arriving at the driving buffer

Table 3. Required and recommended V-t data versus IBIS buffer types

Model type	[Rising Waveform]		[Falling Waveform]		Notes
	Load to Vcc	Load to GND	Load to Vcc	Load to GND	
Input	n/a	n/a	n/a	n/a	
I/O	Recommended	Recommended	Recommended	Recommended	
I/O_open_drain	Recommended	n/a	Recommended	n/a	1
I/O_open_source	n/a	Recommended	n/a	Recommended	1
I/O_open_sink I/O_open_drain	Recommended	n/a	Recommended	n/a	1
Open_source	n/a	Recommended	n/a	Recommended	
Open_sink Open_drain	Recommended	n/a	Recommended	n/a	
3-state	Recommended	Recommended	Recommended	Recommended	
Series_switch	n/a	n/a	n/a	n/a	2
Series	n/a	n/a	n/a	n/a	2
Output	Recommended	Recommended	Recommended	Recommended	
Terminator	n/a	n/a	n/a	n/a	
Input ECL	n/a	n/a	n/a	n/a	
I/O ECL	Recommended (to Vcc - 2)		Recommended (to Vcc - 2)		3
Output ECL	Recommended (to Vcc - 2)		Recommended (to Vcc - 2)		3
3-state ECL	Recommended (to Vcc - 2)		Recommended (to Vcc - 2)		3

1. The presence of internal terminations may require adding waveforms in place of "n/a"
2. Special syntax required
3. For ECL, the fixture is Vcc-2; multiple waveforms to various voltages using the same load impedance may be useful in some contexts

Tables 2 and 3 from Reference 1 reproduced with permission of the IBIS Open Forum and TechAmerica.

D2 and high-voltage resistors R2 and R3. After the 5-V rail is up, Schottky diode D4 allows the 5-V output rail to power the controller.

Power FET Q4 must have a high enough V_{DS} voltage rating not to be damaged by the input voltage, and a high enough current rating to handle $I_{PMOS(RMS)} = I_{OUT(max)} \times \sqrt{D_{max}}$. It must also be in a package capable of dissipating $P_{Cond} = (I_{OUT(max)} \times \sqrt{D_{max}})^2 \times R_{DS(on)}$. Traditionally, high-voltage p-channel FETs have had a gate capacitance or turn-on/off times that were too large, a drain-to-source resistance ($R_{DS(on)}$) that was too high, a threshold voltage (V_{TH}) that was too large, and/or have simply been too expensive to make a circuit like the one in Figure 1 practical (i.e., efficient enough relative to cost). Since the high line of $230 V_{RMS} + 10\%$ tolerance comes from the 350-V_{PK} AC line, the FET, filter, and input capacitors need to be rated for 400 V.

The FQD2P40 is a relatively new, 400-V p-channel MOSFET. With an $R_{DS(on)}$ of 5.0Ω from a 10-V gate drive and a total gate charge of less than 13 nC, this FET can easily be switched by the controller—with relatively fewer conductive and switching losses than older FETs—with the help of the innovative drive circuit consisting of Q2, Q3, C4, and D3. The converter's rectifying Schottky diode, D5, is selected with a voltage rating capable of blocking the input voltage, a peak-current rating slightly higher than the output voltage, and an average current rating of $I_{Diode(Avg)} = (1 - D) \times I_{OUT(max)}$. With a D_{max} of $5 V/120 V = 0.04$ and such low output power, the peak-current rating and the power dissipation are not a concern in either switch.

The buck power stage's LC filter is designed as explained in the TPS6420x family data sheet. With the input voltage being much larger than the output voltage, all of the TPS6420x controllers will run in minimum-on-time mode. Equation 1 computes the recommended buck-converter

inductance at high line, assuming that $K = 0.4$ for the inductor's ripple-current factor.

$$L = \frac{(V_{IN} - V_{OUT}) \times t_{on(min)}}{\Delta I_L} = \frac{(230 V - 5 V) \times 0.65 \mu s}{0.4 \times 0.750 A} \quad (1)$$

$$= 488 \mu H \rightarrow 470 \mu H$$

The relatively high K value minimizes inductor size and proves to be acceptable because the steady-state output-ripple requirement for this particular application was no larger than $0.02 \times V_{OUT}$, or 100 mV_{PP} at high load. Being hysteretic, the TPS6420x controllers typically work best with some ripple on the output voltage. An output capacitor with at least 50-m Ω ESR is recommended and would produce a ripple voltage of $\Delta V_{PP(ESR)} = \Delta I_L \times R_{ESR}$, which typically far exceeds the capacitive component of the voltage ripple. The measured ripple for this application is shown in Figure 2.

Because the TPS64203 is hysteretic, its output voltage will have higher ripple at lower output power when it is running in pulsed-frequency mode. The measured operating frequency of the converter is approximately 32 kHz, which agrees with the predicted value of


$$f_{SW} = \frac{D_{min}}{t_{on(min)}} = \frac{5 V/250 V}{0.65 \mu s} = 31 \text{ kHz.}$$

How the drive circuit works

Bipolar transistor Q1 and resistors R4 and R5 form a constant-current-driven level shifter that allows the low-voltage TPS64203 controller to operate the discrete gate-drive circuit formed by Q2 and Q3. Like the controller, the level shifter is powered by Zener diode D2 at start-up and the regulated 5-V rail, through Schottky diode D4, after start-up. Power FET Q4's gate must be overdriven just enough to provide the required output current with an acceptable $R_{DS(on)}$. Too much drive increases switching losses, while too little increases conduction losses. From a review of the FQD2P40 data sheet and some trial and error, $V_{GS} \cong 12 V$ was selected.

Capacitor C4 and diode D3 are critical to the drive circuit's functionality. Resistor R5 is selected to set the gate-drive level of 12 V below the voltage at the rectifier's output. Diode D3 clamps capacitor C4 to this level. Specifically, when U1's switch pin outputs a low signal to turn on the power FET, the signal gets level shifted to the base of Q3. Transistor Q3 turns on and quickly charges Q4's gate-to-source capacitance, C_{GS} , to 12 V. Without C4 and D3, turning off Q4 would have required Q3 to be an expensive, high-voltage bipolar transistor with its drain tied to ground. When U1's switch pin outputs a high signal to turn off the power FET, the signal gets level shifted to the base of Q2. Q2 turns on, effectively tying Q4's gate to the input voltage. It is important to note that without capacitor C4 acting as a local power supply, transistors Q2 and Q3 would not be able to provide the fast current spikes necessary to quickly—and therefore efficiently—pull up or pull down Q4's gate

Figure 2. Output ripple at $V_{IN} = 250 VDC$ and $I_{OUT} = 500 mA$

 

capacitance. Also, the level shifter's current, I_{LS} , set by R4, must be high enough to move Q4's gate charge, Q_{Gate} , during the $t_{on(min)}$. That is,

$$\frac{I_{LS} = V_{Z(D4)} - V_{BE}}{R4} \gg \frac{Q_{Gate}}{t_{on(min)}}$$

Capacitor C4 is sized to be much larger than Q4's gate capacitance, but it must be small enough that it can be recharged during the shorter of the controller's minimum on and off times. Figure 3 shows the gate and drain turn-on/off times during one switching cycle with an input voltage of 300 V and a 500-mA load. Measured conversion efficiency is shown in Table 1.

Current limit and soft start

In low-voltage applications, the TPS6420x uses a high-side current-limit circuit to compare the drop across a current-sense resistor, placed between the VIN and ISENSE pins, to a reference voltage. If the voltage across the sense resistor exceeds that voltage, the circuit turns off the switch, thereby implementing a pulse-by-pulse current limit. In a high-voltage application, the current-limit circuit cannot be used without overvoltage on the ISENSE pin, so the ISENSE pin is tied high to VIN. Therefore, the circuit in Figure 1 does not have a current limit. A high-side series fuse is recommended to provide short-circuit protection.

In typical applications during start-up, the TPS64203's current-limit value is slowly ramped up to provide a current-limited, controlled soft start. In this application, the current-limit circuit and therefore the soft start are disabled; therefore, the start-up inrush current may be large and the output voltage may overshoot slightly, as shown in Figure 4.

Conclusion

Using a level shifter and gate driver with a localized power source allows the use of a low-voltage buck controller to provide a DC voltage from an AC power source. Conversion efficiency near 60% can be achieved by using a simple circuit and no transformer. This circuit can also be used for DC/DC conversion where the input DC voltage is above the maximum rating of the TPS6420x.

Related Web sites

power.ti.com
www.ti.com/sc/device/TPS64200

Figure 3. Q4 gate and drain voltages during one switching cycle


 


Table 1. Measured conversion efficiency

V _{IN} (V)	I _{IN} (A)	P _{IN} (W)	I _{OUT} (A)	V _{OUT} (V)	P _{OUT} (W)	EFFICIENCY (%)
100	0.043	4.3	0.5	5.023	2.5115	58.40698
200	0.021	4.2	0.5	5.023	2.5115	59.79762
300	0.015	4.5	0.5	5.023	2.5115	55.81111
100	0.066	6.6	0.75	5.023	3.76725	57.07955
200	0.031	6.2	0.75	5.023	3.76725	60.7621
300	0.022	6.6	0.75	5.023	3.76725	57.07955

Figure 4. Start-up into a 10-Ω load with V_{IN} = 300 V

 

Save power with a soft Zener clamp

By John Betten


Applications Engineer and
Senior Member, Technical Staff

Flyback converters are wildly popular due to their low cost, their isolation, and the ease with which additional output voltages can be implemented. For multiple-output flybacks, one output voltage—typically the highest-power output—is tightly regulated by means of feedback to the control circuit. Additional outputs are usually added by tightly coupling transformer windings to the main regulated winding. Linear regulators or DC/DC switchers may be added, or the outputs can be left unregulated. This last option is the most efficient, but many times voltage regulation suffers when the outputs are heavily or lightly loaded while the main output voltage has the opposite load level. This cross-regulation problem is highly dependent on the transformer leakage and winding structure, as well as on other parasitic circuit components. One of the worst scenarios is when the main output is heavily loaded and the unregulated winding is completely unloaded. Any voltage ringing present on the transformer's secondary winding is often peak-detected by the output rectifier, causing the unregulated output voltage to greatly increase. It is not uncommon for the output voltage to rise to twice its nominal voltage in this situation. This can be catastrophic to any downstream load that cannot tolerate a higher voltage or that does not present minimal loading at all times to dissipate the leakage energy.

Several solutions can remedy this no-load overvoltage condition. The simplest solution would be to add a preload to the unregulated output in the form of a resistor. This will load the output enough to dissipate the leakage energy and to lower the output voltage to an acceptable level. Unfortunately, this load will always be present and causes a loss of efficiency that is often considered unacceptable.

A second option is to simply add a Zener diode to the unregulated output. The diode's voltage rating must be set higher than the nominal output voltage after the typical 5% or 10% part tolerance is included. This means the diode won't conduct or dissipate power until the output voltage rises high enough. While this may seem like an ideal solution, several potential problems exist. Once the Zener diode conducts, its impedance drops significantly and provides little resistance to current flow. The current flow into the diode, and hence the power dissipated in it, is determined by parasitic circuit components and thus is

Figure 1. Zener diode with resistor provides soft clamp for no-load output voltage

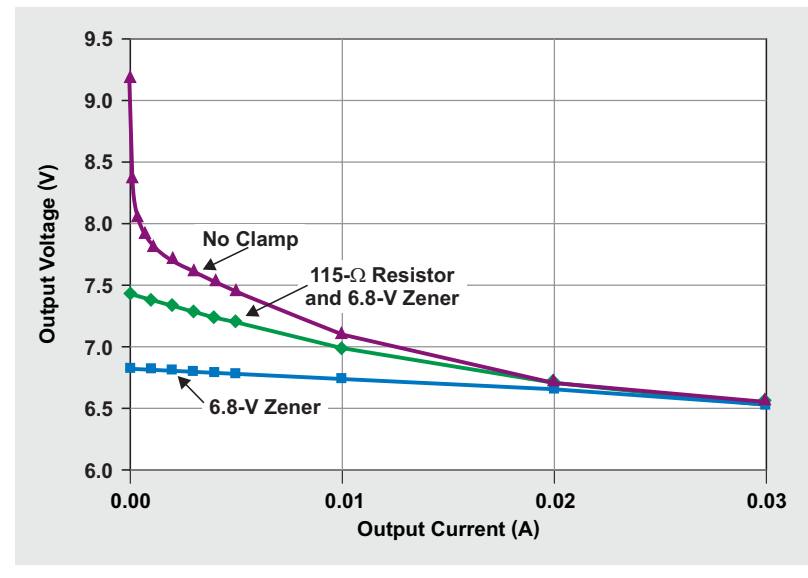

hard to control. Higher-power converters can potentially source a large current and easily destroy a Zener diode. For this reason, it is risky to add a small Zener diode and difficult to calculate the power dissipated.

Another option is to use a snubber to dissipate the leakage energy. This generally dissipates more power than using a preload resistor and does not always provide as much no-load voltage reduction on the output.

A soft Zener clamp, which consists of a resistor in series with a Zener diode, can provide a good compromise. It can clamp the unregulated output voltage to a level that is lower than that of the unclamped output voltage but higher than that of a Zener diode alone. To determine the resistor's value, the output can be loaded with just enough current to reduce the high output voltage to the desired safe level. Figure 1 shows an example where the desired no-load output voltage is 7.4 V. The series resistor's value can be calculated by subtracting the Zener diode's nominal voltage from this voltage and dividing the result by the preload current. The benefit of this circuit is that it does not dissipate power at loads that would typically be seen in operation. Under extreme cross-load conditions, this circuit clamps the "runaway" output voltage to a much more predictable level.

Related Web site

power.ti.com

Interfacing high-voltage applications to low-power controllers

By Thomas Kugelstadt
Senior Applications Engineer

A common requirement of industrial applications is to interface high-voltage potentials, such as signal outputs of sensor switches and AC rectifiers, to the peripheral input ports of low-voltage microcontrollers (MCUs) and digital signal processors. A new generation of interface circuits providing this function are digital-input serializer (DIS) devices. They can sense digital input voltages ranging from as low as 6 VDC up to 300 VDC and convert them into 5-V serial data streams while consuming almost 80% less power than a discrete design. This capability makes DIS devices the most power- and cost-efficient solution in industrial interface applications.

This article explains the functional principle of a DIS and its configuration in a typical industrial interface design.

Functional principle


Understanding the operational principle of a DIS is faster accomplished by seeing the device in the context of an entire interface design as shown in Figure 1. A high-voltage supply in the range of 10 to 34 V supplies the sensor switches, S0 to S7, and the DIS. The ON/OFF status of each sensor switch is detected by the eight parallel field

inputs of the device, then internally processed and made available to the low-voltage inputs of a parallel-in, serial-out shift register. An MCU provides the necessary control signal to the serial interface of the DIS via a digital isolator. Firstly, a load pulse at the $\overline{\text{LD}}$ input latches the switch's status information into the shift. Then a clock signal applied to the CLK input serially shifts the register content out of the DIS into a controller register via the isolator.

S0 to S7 comprise a wide range of sensor switches, such as proximity switches, relay contacts, limit switches, push buttons, and many more. While the input resistors, $R_{\text{IN}0}$ to $R_{\text{IN}7}$, are optional, they can serve two purposes when implemented. One is that in high-voltage applications, some industrial standards might require input resistors as a safety precaution to prevent fire hazards in the event of an input short circuit. The other purpose is to raise the ON/OFF threshold voltage of a sensor switch.

Internally, each input signal is checked for signal strength and stability. A current comparator detects whether the input current is higher than a predefined leakage threshold, and a voltage comparator checks whether the input voltage is higher than an internally

Figure 1. Stand-alone digital-input system

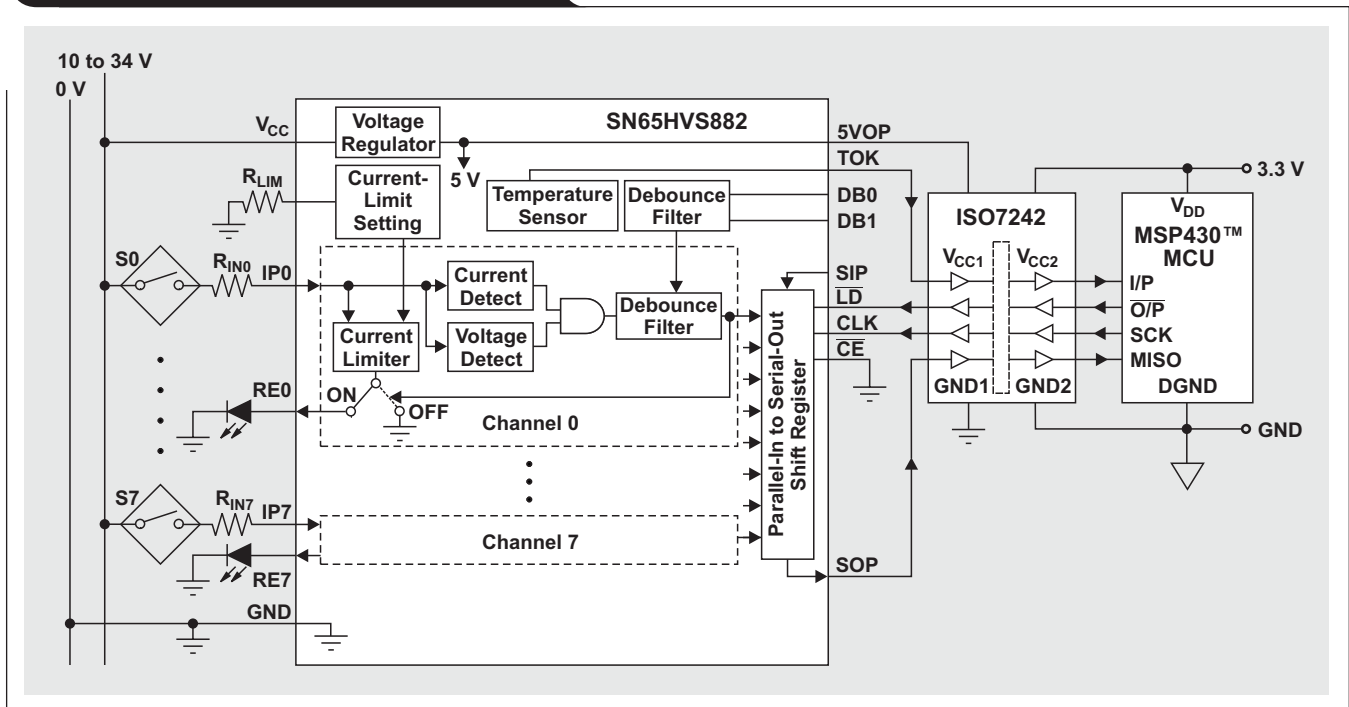

fixed reference voltage. If both comparator outputs are logic high, a programmable debounce filter checks whether the new input status is caused by a short but strong noise transient, or whether the signal presence outlasts the debounce time and thus presents a true input signal.

For a true input signal, the filter output presents the corresponding logic level to the parallel inputs of the shift register and also switches the output of the internal current limiter accordingly. For an OFF condition (when the switch is open), the filter output is low, and the output of the current limiter is switched to ground. For an ON condition, the filter output is high, and the output of the current limiter is connected to a signal-return output (RE). Connecting a light-emitting diode (LED) to an RE output allows for the visible indication of a switch's status.

Input configuration

To configure a DIS for various applications, the current and voltage capability of its input, IPx, must be known, as well as its switching thresholds. For that purpose, Figure 2 shows a more detailed block diagram of a channel's input stage. During a sensor switch's OFF-to-ON transition, the two parameters of interest are the positive-going voltage

threshold at a device input, V_{IP-ON} , and its selected current limit, I_{IN-LIM} .

While V_{IP-ON} is internally fixed at 5.2 V, I_{IN-LIM} can be adjusted via an external precision resistor, R_{LIM} . Note that setting the current limit affects all device inputs equally. I_{IN-LIM} is derived from a reference current, I_{REF} , via a current mirror, making $I_{IN-LIM} = 72 \times I_{REF}$. I_{REF} is determined by the ratio of an internal bandgap reference to the resistor value, R_{LIM} ($I_{REF} = V_{REF}/R_{LIM}$). The current limit can therefore be expressed as a function of R_{LIM} :


$$I_{IN-LIM} = 72 \times \frac{1.25 \text{ V}}{R_{LIM}} = \frac{90 \text{ V}}{R_{LIM}} \quad (1)$$

Solving for R_{LIM} then provides the required resistor value for a desired current limit:

$$R_{LIM} = \frac{90 \text{ V}}{I_{IN-LIM}} \quad (2)$$

For low-voltage applications using a 12-V supply, setting the current limit via R_{LIM} might be the only calculation required. Because the device inputs can tolerate voltages of up to 34 V, switching the 12-V supply directly to a digital

Figure 2. Simplified block diagram of a single-channel input stage

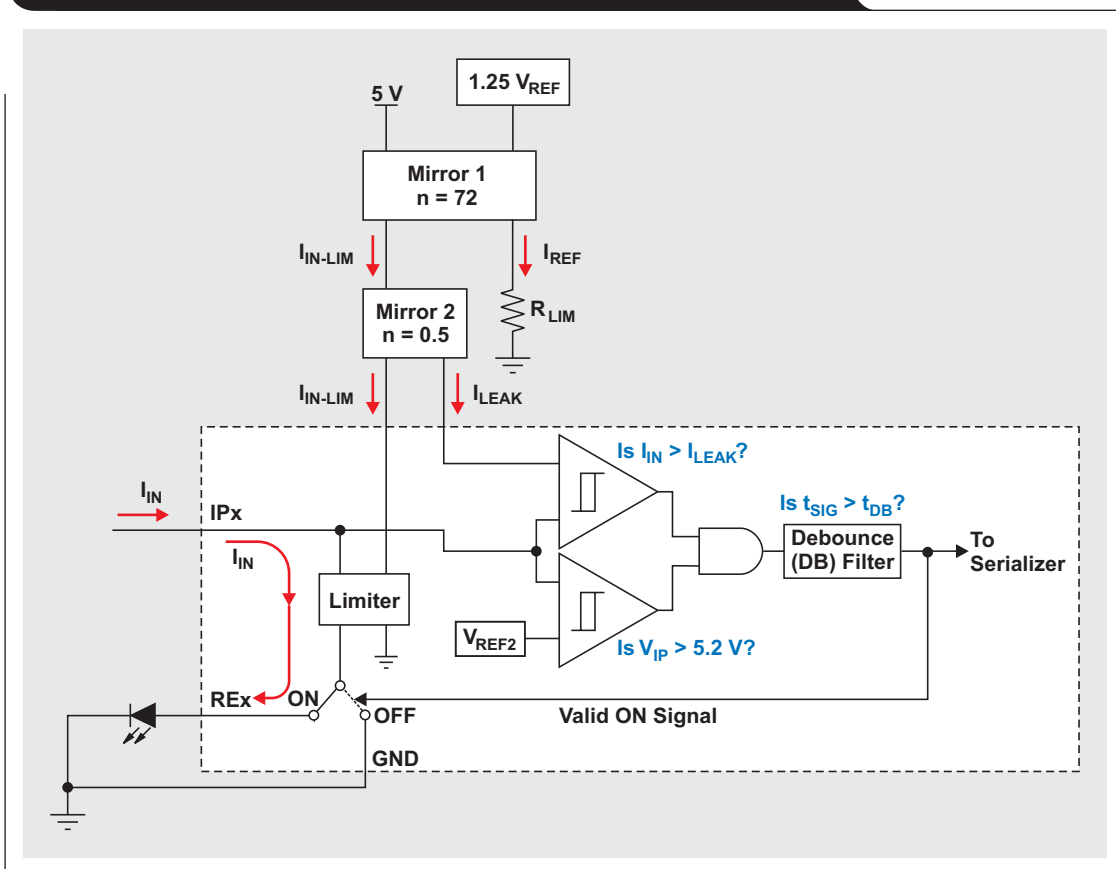

input causes no damage to the device. With $V_{IP-ON} = 5.2\text{ V}$, the ON threshold lies almost in the middle of the 12-V input-voltage range. Figure 3 shows the schematic of this simple circuit design. With the low-current LED indicator requiring a forward current of $I_{IN-LIM} = 2\text{ mA}$, R_{LIM} is determined via Equation 2 to be $45\text{ k}\Omega$, with the closest 1% value being $44.8\text{ k}\Omega$.

However, for high-voltage designs using a supply of 24 V or more, an input resistor is needed to raise the ON threshold into the middle of the input-voltage range. Figure 4 presents this case, with the input-current limit assumed to be 2 mA. The input resistor now separates the device's input voltage, V_{IP} , from the field input voltage, V_{IN} , thus raising the actual ON threshold to $V_{IN-ON} = V_{IP-ON} + R_{IN} \times I_{IN-LIM}$. Inserting the specified 5.2-V threshold for V_{IP-ON}

and expressing I_{IN-LIM} through Equation 1 yields $V_{IN-ON} = 5.2\text{ V} + R_{IN} \times 90\text{ V}/R_{LIM}$. Solving for R_{IN} then provides the required input-resistor value for a desired ON threshold:

$$R_{IN} = (V_{IN-ON} - 5.2\text{ V}) \times \frac{R_{LIM}}{90\text{ V}} \quad (3)$$

In order to set the ON threshold in the circuit in Figure 4 to $V_{IN-ON} = 12\text{ V}$, the input resistor is determined via Equation 3:

$$R_{IN} = (12\text{ V} - 5.2\text{ V}) \times \frac{44.8\text{ k}\Omega}{90\text{ V}} = 3.385\text{ k}\Omega,$$

with the closest 1% value being $3.4\text{ k}\Omega$.

This simple design methodology can be applied to input voltages of up to 60 V. Higher voltages, however, will increase V_{IP} above its specified maximum of 34 V, so a

Figure 3. Switch ON condition: $V_{IP-ON} = 5.2\text{ V}$, $I_{IN-LIM} = 90\text{ V}/R_{LIM}$


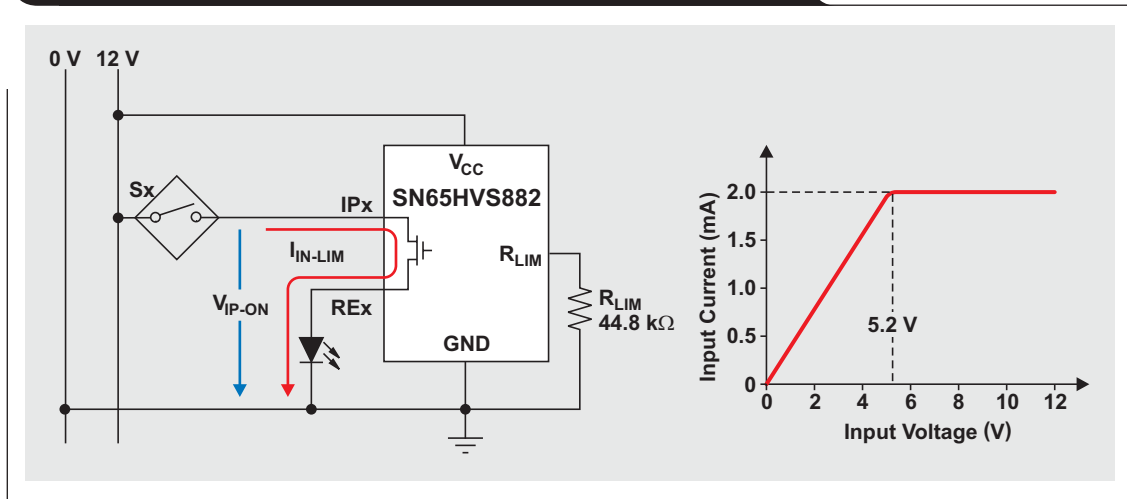


Figure 4. Switch ON condition: $V_{IN-ON} = 12\text{ V}$, $I_{IN-LIM} = 2\text{ mA}$

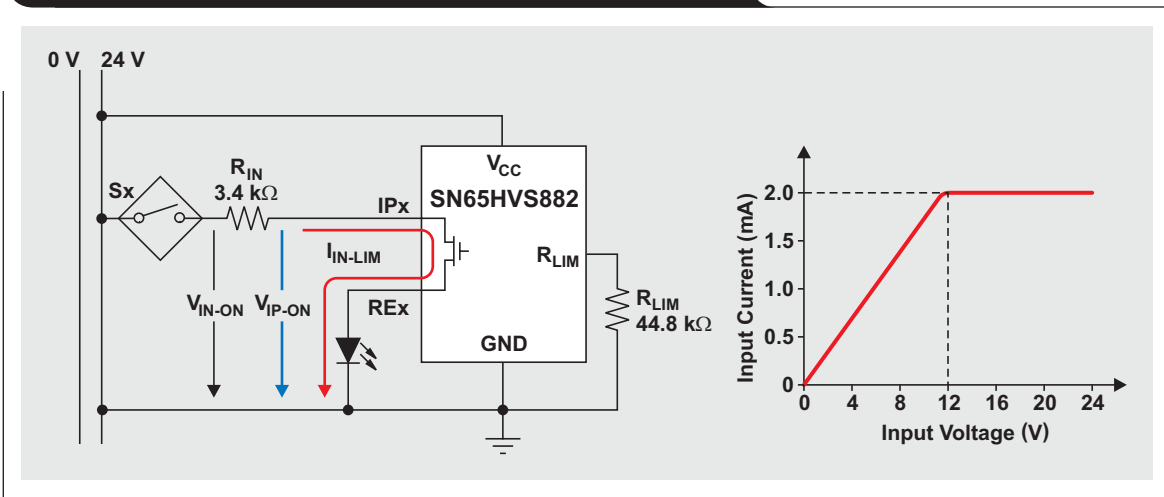

clamping element in the form of a Zener diode is required to prevent the device input from overvoltage stress. Figure 5 gives an example of a mains voltage detector, often used in building automation systems. Here the AC mains voltage of 240 V_{rms} is rectified, thus yielding a peak input of 340 VDC. At such high voltages it is necessary to minimize the I²R losses within the input resistor. Therefore, the current limit is simply set to 0.5 mA by making R_{LIM} = 90 V/0.5 mA = 180 kΩ.

The ON threshold is set to 150 V by making R_{IN} = (150 V – 5.2 V) × 180 kΩ/90 V = 289.6 kΩ, with 291 kΩ as the closest 1% value. At V_{IN-ON} = 150 V, V_{IP-ON} = 5.2 V, and current limiting sets in. Beyond the ON threshold, V_{IP} increases linearly until the Zener voltage of approximately 30 V is reached. At that moment, the Zener diode starts

clamping; and the Zener current, I_Z, adds to the current limit (I_{IN-LIM}) to make up the total input current, I_{IN}.

Serial interface

Reading the status information of the digital field inputs is easy and can be performed by using either shift register timing or serial peripheral interface timing.

When shift register timing is used, a short low-active pulse applied to the load input (\overline{LD}) latches the status information of the digital inputs into the shift register. A subsequent clock signal at CLK, consisting of eight consecutive clock cycles, serially shifts the data out of the DIS register into the input register of an MCU. Each data shift occurs at the rising edge of the clock signal (Figure 6).

Figure 5. Switch ON condition: V_{IN-ON} = 150 V, I_{IN-LIM} = 0.5 mA


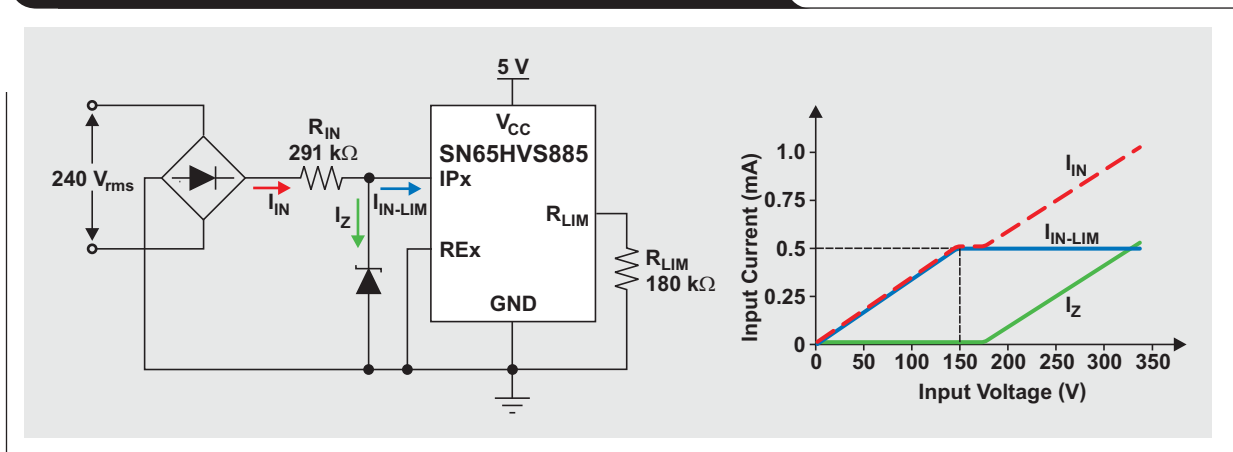


Figure 6. Serial-interface operation using shift register timing

 

Designing input modules with a high channel count is possible by daisy-chaining multiple DIS devices. In this case the serial output of a leading device is connected with the serial input of a following device. Figure 7 shows the simplicity of a daisy-chained, 64-channel digital-input module requiring only three interface lines.

Powering the interface

DIS devices allow for a variety of power-supply configurations. When powered from an industrial 24-V bus, the DIS

can supply 5-V regulated output to digital isolators and MCUs. For 5-V controllers (Figure 8a), the direct connection of supply and serial interface (SIF) lines is straightforward. However, 3.3-V controllers require a low-dropout regulator (LDO) for the supply line and a voltage divider in the serial output (SOP) line (Figure 8b). Control signals from a 3.3-V controller towards the DIS are correctly interpreted.

In applications without a bus supply, it is possible to back-supply a DIS by driving the 5-V output as a supply

Figure 7. Daisy-chained, 64-channel digital-input module

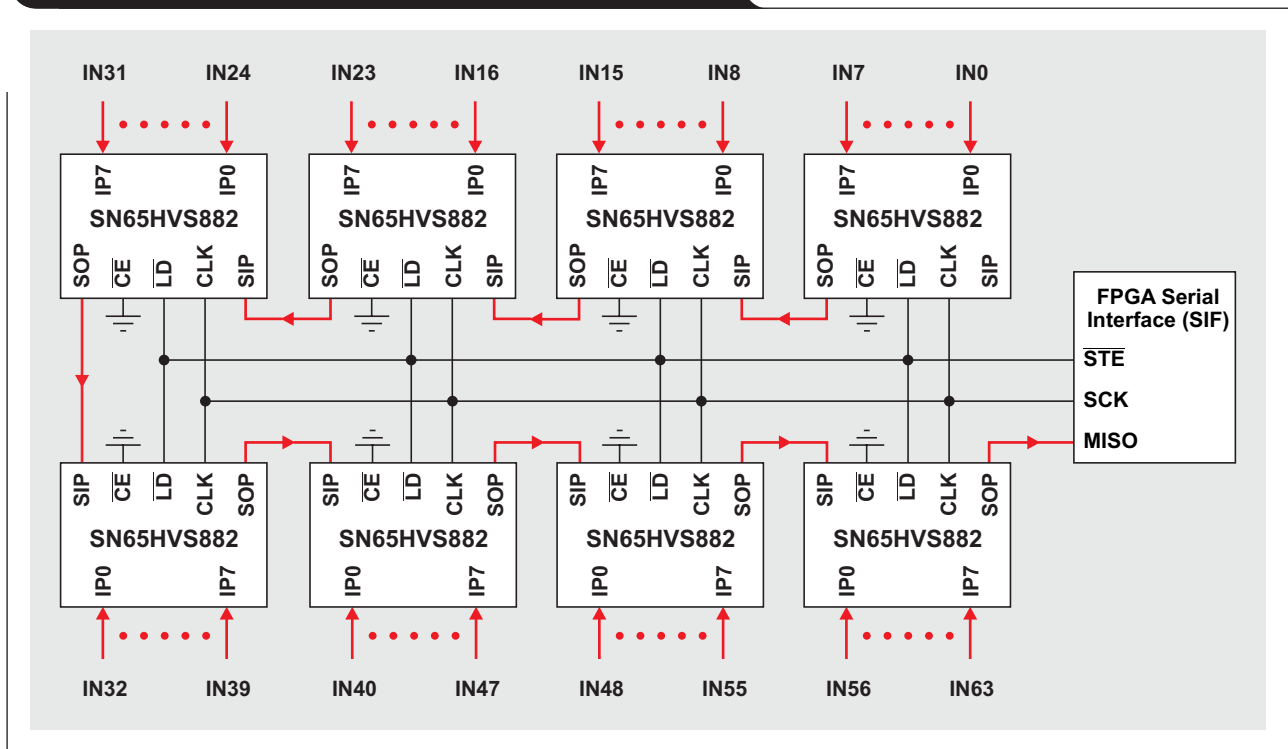


Figure 8. Bus-powered digital-input system

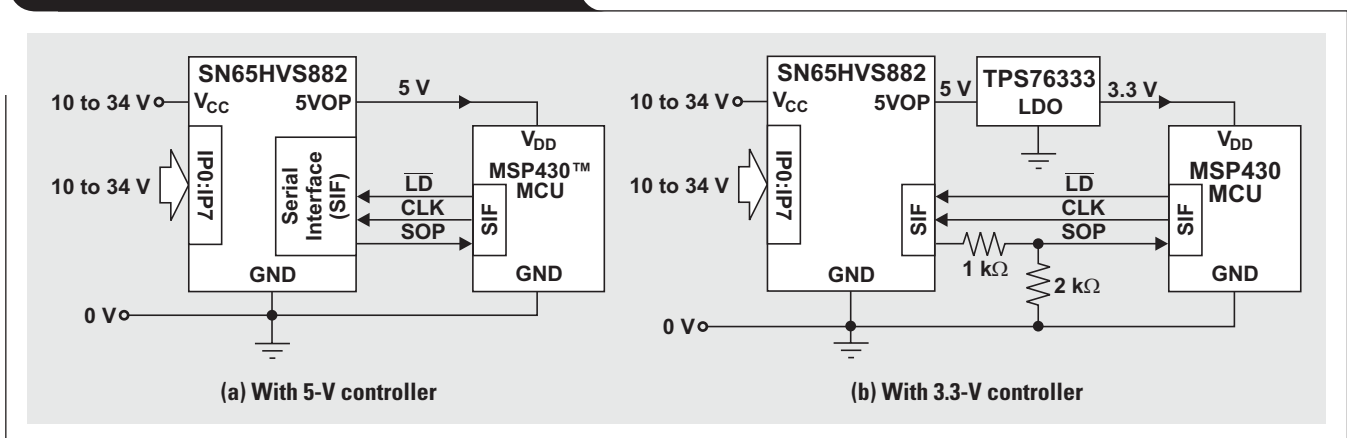
 


Figure 9. Back-supplied digital-input system

input while leaving the normal V_{CC} supply pin floating. Figure 9 shows two back-supply options for interfacing to a 3.3-V controller. In Figure 9a, the 5-V system supply powers the DIS directly but requires an LDO to supply the controller. In Figure 9b, a 3.3-V supply powers the controller directly but requires a charge pump to boost the supply voltage to the required 5-V level of the DIS.

Conclusion

DIS devices represent the most versatile solution for interfacing a low-power controller to high DC voltages. Supporting the interface design between low-voltage controllers and high-voltage applications, the SN65HVS88x family of DIS devices provides a wide variety of features, such as undervoltage detection, current limiting, debounce filtering, thermal protection, parity generation, and a single 5-V supply.

References

For more information related to this article, you can download an Acrobat® Reader® file at www.ti.com/lit/litnumber and replace “*litnumber*” with the **TI Lit. #** for the materials listed below.

- | Document Title | TI Lit. # |
|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------|
| 1. Thomas Kugelstadt. (June 28, 2008). New digital input serializers catapult channel count of digital input modules. <i>EE Times</i> Industrial Control DesignLine [Online]. Available: http://www.eetimes.com | — |
| 2. SN65HVS880 User's Guide | slau271 |

Related Web sites

interface.ti.com

www.ti.com/msp430

www.ti.com/sc/device/partnumber

Replace *partnumber* with ISO7242A, SN65HVS880, TPS60241, or TPS76333

Using single-supply fully differential amplifiers with negative input voltages to drive ADCs

By Jim Karki

Member, Technical Staff, High-Performance Analog

Introduction

Fully differential amplifiers (FDAs) with a single +5-V supply can be easily used to convert single-ended signals that swing around ground to differential signals that are level-shifted to match the input common-mode requirements of differential-input ADCs. There is no real trick to it, but typically it is best to use a device like the THS4521 with an input common-mode voltage range (V_{ICR}) that includes ground. A circuit is proposed and analyzed to show how an FDA with a single +5-V supply can be used to implement the design.

FDAs have been compared to two standard inverting single-ended-output operational amplifiers (op amps) configured in differential architecture and tied together via a common-mode output loop. While this is valid as a concept, there are important differences. For this discussion, an important difference to remember is that when a standard single-ended-output op amp in inverting configuration is used, the input common mode is controlled; but when an FDA is used, the output common mode is controlled.

When a standard single-ended-output op amp in inverting configuration is used, the positive input is not driven from the source and is usually tied to ground or some other reference voltage. The input common-mode voltage at the input pins of the op amp is held at the voltage

applied to the positive input by negative feedback, where the op amp drives the error voltage across its input pins to 0 V. This is usually referred to as a virtual short, which is an important concept in op amp theory.

When an FDA is used to convert a single-ended input to a differential output, the alternate input that is not driven by the source is driven by the output through the feedback network. The virtual-short concept is still valid, but the inputs are no longer tied to a reference and move around with the signal. The output common-mode voltage is controlled by the input to the V_{OCM} pin.


In the following discussion, it is assumed that the reader is familiar with FDA concepts and use. For more information on FDA fundamentals, please see Reference 1.

Circuit analysis

Proposed circuit

The proposed circuit for a single-ended bipolar input signal is shown in Figure 1. V_{S+} is the power supply to the amplifier; and the negative supply input is grounded. V_{IN} is the input-signal source. It is shown as a ground-referenced signal swinging around ground (± 0 V) and is thus a bipolar signal. R_G and R_F are the main gain-setting resistors for the amplifier. V_{OUT+} and V_{OUT-} are the differential output signals to the ADC. They are 180° out of phase and are level-shifted to V_{OCM} .

Figure 1. Single-ended bipolar input circuit

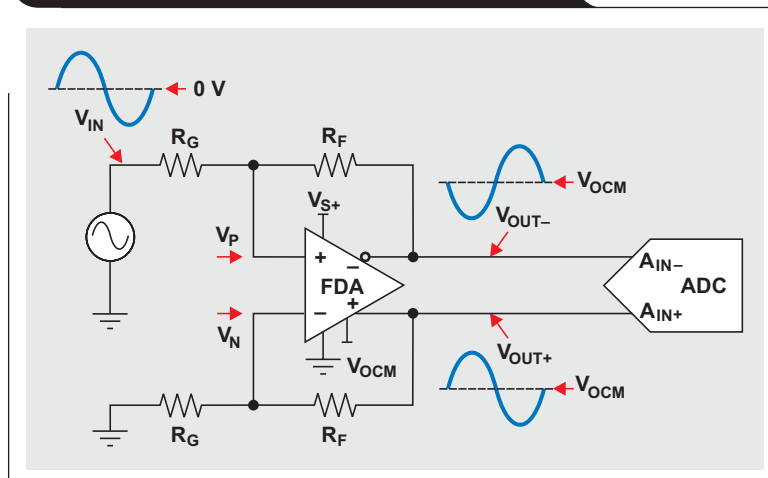

Analysis

For analysis, it is convenient to assume that the FDA is an ideal amplifier with no offset and with infinite gain.

The gain from the single-ended input to the differential output is set by R_F and R_G :

$$\frac{V_{OUT\pm}}{V_{IN}} = \frac{R_F}{R_G} \quad (1)$$

Note that there is no multiplication by 2 as with other devices and circuit architectures that can also be used to convert single-ended inputs to differential outputs.

Each single-ended output is half the differential-output common-mode voltage ($+V_{OCM}$):

$$V_{OUT+} = \frac{V_{IN}}{2} \times \frac{R_F}{R_G} + V_{OCM}$$

and

$$V_{OUT-} = \frac{-V_{IN}}{2} \times \frac{R_F}{R_G} + V_{OCM}$$

For proper operation, the input voltages at V_P and V_N must not exceed the input common-mode voltage range (V_{ICR}) of the amplifier, and the outputs must be able to support the voltage-swing requirements of the ADC input. Violating V_{ICR} will lead to nonlinear operation that increases distortion and is sometimes mistaken for output-saturation problems.

To verify that the V_{ICR} is not violated, the virtual-short concept can be used to calculate the voltage at either FDA input pin, since $V_P \approx V_N$. Either of the following two equations can be used, but Equation 3 is easiest.

$$V_P = V_{OUT-} \times \frac{R_G}{R_G + R_F} + V_{IN} \times \frac{R_F}{R_G + R_F} \quad (2)$$

$$V_N = V_{OUT+} \times \frac{R_G}{R_G + R_F} \quad (3)$$

Due to the difference in output and input common-mode voltage, the feedback circuit draws a current equal to the difference in the common-mode voltages divided by $R_F + R_G$. If the gain-setting resistors on the two sides of the FDA are not matched, the difference in common-mode voltage will also cause an offset in the output. So it is important to use resistors with a low tolerance of 1% or better.

Example

To see how the circuit works, assume that the input signal is $2 V_{PP}$ and the ADC to be driven is the ADS1278. The ADS1278's full-scale differential input is $5 V_{PP}$, and the input common-mode voltage is $+2.5 V$. The THS4521 with a single $+5-V$ supply can be used as the FDA.

It must first be verified that the THS4521 can support the required voltages. The maximum gain to avoid saturating the ADC is $2.5 V/V$. Equation 1 can be used to set R_F at $1 k\Omega$ and R_G at 400Ω . To set the ADC's required input common-mode voltage at $+2.5 V$, the V_{OCM} of the THS4521 can simply be bypassed to ground with a $0.1-\mu F$ capacitor,

because V_{OCM} defaults to midsupply ($+2.5 V$) if not driven. Each output will then swing $2.5 V_{PP}$ ($\pm 1.25 V$) around $+2.5 V$, so the outputs need to support $+1.25 V$ to $+3.75 V$. A check of the THS4521 data sheet shows that the required output-voltage range is within specification. Note that other converters with different requirements for the input common-mode voltage will need the V_{OCM} pin to be DC-biased to meet those requirements.

Equation 2 can be used to calculate V_P at the positive and negative peaks of the input signal. At $V_{IN} = -1 V$, $V_{OUT-} = +3.75 V$.

$$V_P = 3.75 V \times \frac{400 \Omega}{1400 \Omega} - 1 V \times \frac{1000 \Omega}{1400 \Omega} = +0.357 V$$

At $V_{IN} = +1 V$, $V_{OUT-} = +1.25 V$.

$$V_P = 1 V \times \frac{400 \Omega}{1400 \Omega} + 1.25 V \times \frac{1000 \Omega}{1400 \Omega} = +1.071 V$$

Alternatively, Equation 3 can be used to calculate V_N at the positive and negative peaks of the input signal. At $V_{IN} = -1 V$, $V_{OUT+} = +1.25 V$.

$$V_N = 1.25 V \times \frac{400 \Omega}{1400 \Omega} = +0.375 V$$

At $V_{IN} = +1 V$, $V_{OUT+} = +3.75 V$.

$$V_N = 3.75 V \times \frac{400 \Omega}{1400 \Omega} = +1.071 V$$

The voltages calculated for V_P and V_N are the same as predicted. A check of the THS4521 data sheet shows that the required input-voltage range is within specification.

Even though the input signal swings negative below ground, no negative voltages are required at the FDA pins. When used for conversion from single-ended to differential, the input common-mode voltage to the FDA is modulated with the signal. In contrast, when the input and output are both differential, variation of the input common-mode voltage is much lower and approximately equal to the weighted average (set by R_F and R_G) of the output common-mode and input common-mode voltages.

What happens to V_{ICR} when the gain is decreased or increased?

- When the gain decreases, the input voltages (V_P and V_N) are driven closer to the output voltage. For a gain of 1, V_{ICR} equals half the output swing on either output. Attenuation, where the gain is less than 1, is a special case; please see Reference 2 for more information.
- When the gain increases, the input voltages (V_P and V_N) are driven closer to the input source voltage. As the gain increases, R_F becomes larger and/or R_G becomes smaller; and, assuming that the output-voltage swing is the same, the input-signal swing becomes smaller. V_{ICR} equals the input common mode of the source, which in this case is $0 V$, or ground. For a more practical example, given the same $5-V_{PP}$ differential output as before but with the input reduced so the required gain is 10, $V_{ICR} = +0.114 V$ to $+0.341 V$.

Simulation

It is always a good idea to simulate circuit ideas to catch errors and verify that assumptions are valid. Figure 2 shows the result of a transient analysis from TINA-TI™. To see this simulation, go to <http://www.ti.com/lit/zip/slyt394> and click Open to view the WinZip directory online (or click Save to download the WinZip file for offline use). If you have the TINA-TI software installed, you can open the file THS4521_SE_to_DIFF.TSC to view the example. To download and install the free TINA-TI software, visit www.ti.com/tina-ti and click the Download button.

Conclusion

Parameters were established for a bipolar single-ended source that needs to be amplified and level-shifted to drive an ADC with a +2.5-V input common-mode voltage and a full-scale input of up to 6 V_{PP}. A good option for driving such an ADC is an FDA with a single +5-V supply, a V_{ICR} ranging from -0.1 V to +2 V, and an output voltage ranging from +1 V to +4 V. The THS4521 is an excellent choice for this application, with specifications for a single +5-V supply as follows:

- Input-voltage range = 0 to +3.5 V (minimum to maximum over a temperature range of -40°C to +85°C)
- Output-voltage range = +0.2 to +4.65 V (minimum to maximum over a temperature range of -40°C to +85°C)

Table 1 shows the TI ADCs that are compatible with the output-drive characteristics and performance of the THS4521.

When an FDA with a single +5-V supply is used to drive an ADC with a single +5-V supply (like the THS4521 driving the ADS1278), the potential problem of saturating the ADC’s inputs is avoided because its outputs cannot exceed the power-supply voltage.

Please refer to the “Application Information” section of Reference 3 for details on how the THS4521 performs when driving some of these ADCs and for other applica-

Table 1. TI ADCs compatible with THS4521

CONVERTER TYPE	DEVICES
Successive approximation register (SAR)	ADS8317/8, ADS8321, ADS8361/4/5, ADS7861/2/3/4/5/9
Delta-sigma	ADS1251/2/3/4/8, ADS1281/2, ADS1158, ADS1271/4/8, ADS1174/8
Audio	PCM1804, PCM3110, PCM3160/8, PCM4201/2/4

tion information.

References


For more information related to this article, you can download an Acrobat® Reader® file at www.ti.com/lit/litnumber and replace “litnumber” with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. James Karki, “Fully-differential amplifiers,” Application Report.	sloa054
2. Jim Karki, “Using fully differential op amps as attenuators, Part 2: Single-ended bipolar input signals,” <i>Analog Applications Journal</i> (3Q 2009).	slyt341
3. “Very low power, negative rail input, rail-to-rail output, fully differential amplifier,” THS4521 Data Sheet	sbos458

Related Web sites

- amplifier.ti.com
- www.ti.com/sc/device/ADS1278
- www.ti.com/sc/device/THS4521
- TINA-TI file for example:
www.ti.com/lit/zip/slyt394
- To download TINA-TI software:
www.ti.com/tina-ti

Figure 2. TINA-TI™ simulation of example circuit

 

Index of Articles

Title	Issue	Page	Lit. No.
Data Acquisition			
Aspects of data acquisition system design	August 1999	1	SLYT191
Low-power data acquisition sub-system using the TI TLV1572	August 1999	4	SLYT192
Evaluating operational amplifiers as input amplifiers for A-to-D converters	August 1999	7	SLYT193
Precision voltage references	November 1999	1	SLYT183
Techniques for sampling high-speed graphics with lower-speed A/D converters	November 1999	5	SLYT184
A methodology of interfacing serial A-to-D converters to DSPs	February 2000	1	SLYT175
The operation of the SAR-ADC based on charge redistribution	February 2000	10	SLYT176
The design and performance of a precision voltage reference circuit for 14-bit and 16-bit A-to-D and D-to-A converters	May 2000	1	SLYT168
Introduction to phase-locked loop system modeling	May 2000	5	SLYT169
New DSP development environment includes data converter plug-ins	August 2000	1	SLYT158
Higher data throughput for DSP analog-to-digital converters	August 2000	5	SLYT159
Efficiently interfacing serial data converters to high-speed DSPs	August 2000	10	SLYT160
Smallest DSP-compatible ADC provides simplest DSP interface	November 2000	1	SLYT148
Hardware auto-identification and software auto-configuration for the TLV320AIC10 DSP Codec — a “plug-and-play” algorithm	November 2000	8	SLYT149
Using quad and octal ADCs in SPI mode	November 2000	15	SLYT150
Building a simple data acquisition system using the TMS320C31 DSP	February 2001	1	SLYT136
Using SPI synchronous communication with data converters — interfacing the MSP430F149 and TLV5616	February 2001	7	SLYT137
A/D and D/A conversion of PC graphics and component video signals, Part 1: Hardware	February 2001	11	SLYT138
A/D and D/A conversion of PC graphics and component video signals, Part 2: Software and control	July 2001	5	SLYT129
Intelligent sensor system maximizes battery life: Interfacing the MSP430F123 Flash MCU, ADS7822, and TPS60311	1Q, 2002	5	SLYT123
SHDSL AFE1230 application	2Q, 2002	5	SLYT114
Synchronizing non-FIFO variations of the THS1206	2Q, 2002	12	SLYT115
Adjusting the A/D voltage reference to provide gain	3Q, 2002	5	SLYT109
MSC1210 debugging strategies for high-precision smart sensors	3Q, 2002	7	SLYT110
Using direct data transfer to maximize data acquisition throughput	3Q, 2002	14	SLYT111
Interfacing op amps and analog-to-digital converters	4Q, 2002	5	SLYT104
ADS82x ADC with non-uniform sampling clock	4Q, 2003	5	SLYT089
Calculating noise figure and third-order intercept in ADCs	4Q, 2003	11	SLYT090
Evaluation criteria for ADSL analog front end	4Q, 2003	16	SLYT091
Two-channel, 500-kSPS operation of the ADS8361	1Q, 2004	5	SLYT082
ADS809 analog-to-digital converter with large input pulse signal	1Q, 2004	8	SLYT083
Streamlining the mixed-signal path with the signal-chain-on-chip MSP430F169	3Q, 2004	5	SLYT078
Supply voltage measurement and ADC PSRR improvement in MSC12xx devices	1Q, 2005	5	SLYT073
14-bit, 125-MSPS ADS5500 evaluation	1Q, 2005	13	SLYT074
Clocking high-speed data converters	1Q, 2005	20	SLYT075
Implementation of 12-bit delta-sigma DAC with MSC12xx controller	1Q, 2005	27	SLYT076
Using resistive touch screens for human/machine interface	3Q, 2005	5	SLYT209A
Simple DSP interface for ADS784x/834x ADCs	3Q, 2005	10	SLYT210
Operating multiple oversampling data converters	4Q, 2005	5	SLYT222
Low-power, high-intercept interface to the ADS5424 14-bit, 105-MSPS converter for undersampling applications	4Q, 2005	10	SLYT223
Understanding and comparing datasheets for high-speed ADCs	1Q, 2006	5	SLYT231
Matching the noise performance of the operational amplifier to the ADC	2Q, 2006	5	SLYT237
Using the ADS8361 with the MSP430 USI port	3Q, 2006	5	SLYT244
Clamp function of high-speed ADC THS1041	4Q, 2006	5	SLYT253
Conversion latency in delta-sigma converters	2Q, 2007	5	SLYT264
Calibration in touch-screen systems	3Q, 2007	5	SLYT277
Using a touch-screen controller's auxiliary inputs	4Q, 2007	5	SLYT283

Title	Issue	Page	Lit. No.
Data Acquisition (Continued)			
Understanding the pen-interrupt (PENIRQ) operation of touch-screen controllers	2Q, 2008	5	SLYT292
A DAC for all precision occasions	3Q, 2008	5	SLYT300
Stop-band limitations of the Sallen-Key low-pass filter	4Q, 2008	5	SLYT306
How the voltage reference affects ADC performance, Part 1	2Q, 2009	5	SLYT331
Impact of sampling-clock spurs on ADC performance	3Q, 2009	5	SLYT338
How the voltage reference affects ADC performance, Part 2	3Q, 2009	13	SLYT339
How the voltage reference affects ADC performance, Part 3	4Q, 2009	5	SLYT355
How digital filters affect analog audio-signal levels	2Q, 2010	5	SLYT375
Clock jitter analyzed in the time domain, Part 1	3Q, 2010	5	SLYT379
Clock jitter analyzed in the time domain, Part 2	4Q, 2010	5	SLYT389
The IBIS model: A conduit into signal-integrity analysis, Part 1	4Q, 2010	11	SLYT390
Power Management			
Stability analysis of low-dropout linear regulators with a PMOS pass element	August 1999	10	SLYT194
Extended output voltage adjustment (0 V to 3.5 V) using the TI TPS5210	August 1999	13	SLYT195
Migrating from the TI TL770x to the TI TLC770x	August 1999	14	SLYT196
TI TPS5602 for powering TI's DSP	November 1999	8	SLYT185
Synchronous buck regulator design using the TI TPS5211 high-frequency hysteretic controller	November 1999	10	SLYT186
Understanding the stable range of equivalent series resistance of an LDO regulator	November 1999	14	SLYT187
Power supply solutions for TI DSPs using synchronous buck converters	February 2000	12	SLYT177
Powering Celeron-type microprocessors using TI's TPS5210 and TPS5211 controllers	February 2000	20	SLYT178
Simple design of an ultra-low-ripple DC/DC boost converter with TPS60100 charge pump	May 2000	11	SLYT170
Low-cost, minimum-size solution for powering future-generation Celeron™-type processors with peak currents up to 26 A	May 2000	14	SLYT171
Advantages of using PMOS-type low-dropout linear regulators in battery applications	August 2000	16	SLYT161
Optimal output filter design for microprocessor or DSP power supply	August 2000	22	SLYT162
Understanding the load-transient response of LDOs	November 2000	19	SLYT151
Comparison of different power supplies for portable DSP solutions working from a single-cell battery	November 2000	24	SLYT152
Optimal design for an interleaved synchronous buck converter under high-slew-rate, load-current transient conditions	February 2001	15	SLYT139
–48-V/+48-V hot-swap applications	February 2001	20	SLYT140
Power supply solution for DDR bus termination	July 2001	9	SLYT130
Runtime power control for DSPs using the TPS62000 buck converter	July 2001	15	SLYT131
Power control design key to realizing InfiniBand™ benefits	1Q, 2002	10	SLYT124
Comparing magnetic and piezoelectric transformer approaches in CCFL applications	1Q, 2002	12	SLYT125
Why use a wall adapter for ac input power?	1Q, 2002	18	SLYT126
SWIFT™ Designer power supply design program	2Q, 2002	15	SLYT116
Optimizing the switching frequency of ADSL power supplies	2Q, 2002	23	SLYT117
Powering electronics from the USB port	2Q, 2002	28	SLYT118
Using the UCC3580-1 controller for highly efficient 3.3-V/100-W isolated supply design	4Q, 2002	8	SLYT105
Power conservation options with dynamic voltage scaling in portable DSP designs	4Q, 2002	12	SLYT106
Understanding piezoelectric transformers in CCFL backlight applications	4Q, 2002	18	SLYT107
Load-sharing techniques: Paralleling power modules with overcurrent protection	1Q, 2003	5	SLYT100
Using the TPS61042 white-light LED driver as a boost converter	1Q, 2003	7	SLYT101
Auto-Track™ voltage sequencing simplifies simultaneous power-up and power-down	3Q, 2003	5	SLYT095
Soft-start circuits for LDO linear regulators	3Q, 2003	10	SLYT096
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 1	3Q, 2003	13	SLYT097
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 2	4Q, 2003	21	SLYT092
LED-driver considerations	1Q, 2004	14	SLYT084
Tips for successful power-up of today's high-performance FPGAs	3Q, 2004	11	SLYT079
A better bootstrap/bias supply circuit	1Q, 2005	33	SLYT077
Understanding noise in linear regulators	2Q, 2005	5	SLYT201
Understanding power supply ripple rejection in linear regulators	2Q, 2005	8	SLYT202
Miniature solutions for voltage isolation	3Q, 2005	13	SLYT211
New power modules improve surface-mount manufacturability	3Q, 2005	18	SLYT212

Title	Issue	Page	Lit. No.
Power Management (Continued)			
Li-ion switching charger integrates power FETs	4Q, 2005	19	SLYT224
TLC5940 dot correction compensates for variations in LED brightness	4Q, 2005	21	SLYT225
Powering today's multi-rail FPGAs and DSPs, Part 1	1Q, 2006	9	SLYT232
TPS79918 RF LDO supports migration to StrataFlash® Embedded Memory (P30)	1Q, 2006	14	SLYT233
Practical considerations when designing a power supply with the TPS6211x	1Q, 2006	17	SLYT234
TLC5940 PWM dimming provides superior color quality in LED video displays	2Q, 2006	10	SLYT238
Wide-input dc/dc modules offer maximum design flexibility	2Q, 2006	13	SLYT239
Powering today's multi-rail FPGAs and DSPs, Part 2	2Q, 2006	18	SLYT240
TPS61059 powers white-light LED as photoflash or movie light	3Q, 2006	8	SLYT245
TPS65552A powers portable photoflash	3Q, 2006	10	SLYT246
Single-chip bq2403x power-path manager charges battery while powering system	3Q, 2006	12	SLYT247
Complete battery-pack design for one- or two-cell portable applications	3Q, 2006	14	SLYT248
A 3-A, 1.2-V _{OUT} linear regulator with 80% efficiency and P _{LOST} < 1 W	4Q, 2006	10	SLYT254
bq25012 single-chip, Li-ion charger and dc/dc converter for Bluetooth® headsets	4Q, 2006	13	SLYT255
Fully integrated TPS6300x buck-boost converter extends Li-ion battery life	4Q, 2006	15	SLYT256
Selecting the correct IC for power-supply applications	1Q, 2007	5	SLYT259
LDO white-LED driver TPS7510x provides incredibly small solution size	1Q, 2007	9	SLYT260
Power management for processor core voltage requirements	1Q, 2007	11	SLYT261
Enhanced-safety, linear Li-ion battery charger with thermal regulation and input overvoltage protection	2Q, 2007	8	SLYT269
Current balancing in four-pair, high-power PoE applications	2Q, 2007	11	SLYT270
Power-management solutions for telecom systems improve performance, cost, and size	3Q, 2007	10	SLYT278
TPS6108x: A boost converter with extreme versatility	3Q, 2007	14	SLYT279
Get low-noise, low-ripple, high-PSRR power with the TPS717xx	3Q, 2007	17	SLYT280
Simultaneous power-down sequencing with the TPS74x01 family of linear regulators	3Q, 2007	20	SLYT281
Driving a WLED does not always require 4 V	4Q, 2007	9	SLYT284
Host-side gas-gauge-system design considerations for single-cell handheld applications	4Q, 2007	12	SLYT285
Using a buck converter in an inverting buck-boost topology	4Q, 2007	16	SLYT286
Understanding output voltage limitations of DC/DC buck converters	2Q, 2008	11	SLYT293
Battery-charger front-end IC improves charging-system safety	2Q, 2008	14	SLYT294
New current-mode PWM controllers support boost, flyback, SEPIC, and LED-driver applications	3Q, 2008	9	SLYT302
Getting the most battery life from portable systems	4Q, 2008	8	SLYT307
Compensating and measuring the control loop of a high-power LED driver	4Q, 2008	14	SLYT308
Designing DC/DC converters based on SEPIC topology	4Q, 2008	18	SLYT309
Paralleling power modules for high-current applications	1Q, 2009	5	SLYT320
Improving battery safety, charging, and fuel gauging in portable media applications	1Q, 2009	9	SLYT321
Cell balancing buys extra run time and battery life	1Q, 2009	14	SLYT322
Using a portable-power boost converter in an isolated flyback application	1Q, 2009	19	SLYT323
Taming linear-regulator inrush currents	2Q, 2009	9	SLYT332
Designing a linear Li-Ion battery charger with power-path control	2Q, 2009	12	SLYT333
Selecting the right charge-management solution	2Q, 2009	18	SLYT334
Reducing radiated EMI in WLED drivers	3Q, 2009	17	SLYT340
Using power solutions to extend battery life in MSP430 applications	4Q, 2009	10	SLYT356
Designing a multichemistry battery charger	4Q, 2009	13	SLYT357
Efficiency of synchronous versus nonsynchronous buck converters	4Q, 2009	15	SLYT358
Fuel-gauging considerations in battery backup storage systems	1Q, 2010	5	SLYT364
Li-ion battery-charger solutions for JEITA compliance	1Q, 2010	8	SLYT365
Power-supply design for high-speed ADCs	1Q, 2010	12	SLYT366
Discrete design of a low-cost isolated 3.3- to 5-V DC/DC converter	2Q, 2010	12	SLYT371
Designing DC/DC converters based on ZETA topology	2Q, 2010	16	SLYT372
Coupled inductors broaden DC/DC converter usage	3Q, 2010	10	SLYT380
Computing power going "Platinum"	3Q, 2010	13	SLYT382
A low-cost, non-isolated AC/DC buck converter with no transformer	4Q, 2010	16	SLYT391
Save power with a soft Zener clamp	4Q, 2010	19	SLYT392

Title	Issue	Page	Lit. No.
Interface (Data Transmission)			
TIA/EIA-568A Category 5 cables in low-voltage differential signaling (LVDS)	August 1999	16	SLYT197
Keep an eye on the LVDS input levels	November 1999	17	SLYT188
Skew definition and jitter analysis	February 2000	29	SLYT179
LVDS receivers solve problems in non-LVDS applications	February 2000	33	SLYT180
LVDS: The ribbon cable connection	May 2000	19	SLYT172
Performance of LVDS with different cables	August 2000	30	SLYT163
A statistical survey of common-mode noise	November 2000	30	SLYT153
The Active Fail-Safe feature of the SN65LVDS32A	November 2000	35	SLYT154
The SN65LVDS33/34 as an ECL-to-LVTTL converter	July 2001	19	SLYT132
Power consumption of LVPECL and LVDS	1Q, 2002	23	SLYT127
Estimating available application power for Power-over-Ethernet applications	1Q, 2004	18	SLYT085
The RS-485 unit load and maximum number of bus connections	1Q, 2004	21	SLYT086
Failsafe in RS-485 data buses	3Q, 2004	16	SLYT080
Maximizing signal integrity with M-LVDS backplanes	2Q, 2005	11	SLYT203
Device spacing on RS-485 buses	2Q, 2006	25	SLYT241
Improved CAN network security with TI's SN65HVD1050 transceiver	3Q, 2006	17	SLYT249
Detection of RS-485 signal loss	4Q, 2006	18	SLYT257
Enabling high-speed USB OTG functionality on TI DSPs	2Q, 2007	18	SLYT271
When good grounds turn bad— isolate!	3Q, 2008	11	SLYT298
Cascading of input serializers boosts channel density for digital inputs	3Q, 2008	16	SLYT301
RS-485: Passive failsafe for an idle bus	1Q, 2009	22	SLYT324
Message priority inversion on a CAN bus	1Q, 2009	25	SLYT325
Designing with digital isolators	2Q, 2009	21	SLYT335
Magnetic-field immunity of digital capacitive isolators	3Q, 2010	19	SLYT381
Interfacing high-voltage applications to low-power controllers	4Q, 2010	20	SLYT393
Amplifiers: Audio			
Reducing the output filter of a Class-D amplifier	August 1999	19	SLYT198
Power supply decoupling and audio signal filtering for the Class-D audio power amplifier	August 1999	24	SLYT199
PCB layout for the TPA005D1x and TPA032D0x Class-D APAs	February 2000	39	SLYT182
An audio circuit collection, Part 1	November 2000	39	SLYT155
1.6- to 3.6-volt BTL speaker driver reference design	February 2001	23	SLYT141
Notebook computer upgrade path for audio power amplifiers	February 2001	27	SLYT142
An audio circuit collection, Part 2	February 2001	41	SLYT145
An audio circuit collection, Part 3	July 2001	34	SLYT134
Audio power amplifier measurements	July 2001	40	SLYT135
Audio power amplifier measurements, Part 2	1Q, 2002	26	SLYT128
Precautions for connecting APA outputs to other devices	2Q, 2010	22	SLYT373
Amplifiers: Op Amps			
Single-supply op amp design	November 1999	20	SLYT189
Reducing crosstalk of an op amp on a PCB	November 1999	23	SLYT190
Matching operational amplifier bandwidth with applications	February 2000	36	SLYT181
Sensor to ADC — analog interface design	May 2000	22	SLYT173
Using a decompensated op amp for improved performance	May 2000	26	SLYT174
Design of op amp sine wave oscillators	August 2000	33	SLYT164
Fully differential amplifiers	August 2000	38	SLYT165
The PCB is a component of op amp design	August 2000	42	SLYT166
Reducing PCB design costs: From schematic capture to PCB layout	August 2000	48	SLYT167
Thermistor temperature transducer-to-ADC application	November 2000	44	SLYT156
Analysis of fully differential amplifiers	November 2000	48	SLYT157
Fully differential amplifiers applications: Line termination, driving high-speed ADCs, and differential transmission lines	February 2001	32	SLYT143
Pressure transducer-to-ADC application	February 2001	38	SLYT144
Frequency response errors in voltage feedback op amps	February 2001	48	SLYT146
Designing for low distortion with high-speed op amps	July 2001	25	SLYT133
Fully differential amplifier design in high-speed data acquisition systems	2Q, 2002	35	SLYT119

Title	Issue	Page	Lit. No.
Amplifiers: Op Amps (Continued)			
Worst-case design of op amp circuits	2Q, 2002	42	SLYT120
Using high-speed op amps for high-performance RF design, Part 1	2Q, 2002	46	SLYT121
Using high-speed op amps for high-performance RF design, Part 2	3Q, 2002	21	SLYT112
FilterPro™ low-pass design tool	3Q, 2002	24	SLYT113
Active output impedance for ADSL line drivers	4Q, 2002	24	SLYT108
RF and IF amplifiers with op amps	1Q, 2003	9	SLYT102
Analyzing feedback loops containing secondary amplifiers	1Q, 2003	14	SLYT103
Video switcher using high-speed op amps	3Q, 2003	20	SLYT098
Expanding the usability of current-feedback amplifiers	3Q, 2003	23	SLYT099
Calculating noise figure in op amps	4Q, 2003	31	SLYT094
Op amp stability and input capacitance	1Q, 2004	24	SLYT087
Integrated logarithmic amplifiers for industrial applications	1Q, 2004	28	SLYT088
Active filters using current-feedback amplifiers	3Q, 2004	21	SLYT081
Auto-zero amplifiers ease the design of high-precision circuits	2Q, 2005	19	SLYT204
So many amplifiers to choose from: Matching amplifiers to applications	3Q, 2005	24	SLYT213
Getting the most out of your instrumentation amplifier design	4Q, 2005	25	SLYT226
High-speed notch filters	1Q, 2006	19	SLYT235
Low-cost current-shunt monitor IC revives moving-coil meter design	2Q, 2006	27	SLYT242
Accurately measuring ADC driving-circuit settling time	1Q, 2007	14	SLYT262
New zero-drift amplifier has an I_Q of 17 μ A	2Q, 2007	22	SLYT272
A new filter topology for analog high-pass filters	3Q, 2008	18	SLYT299
Input impedance matching with fully differential amplifiers	4Q, 2008	24	SLYT310
A dual-polarity, bidirectional current-shunt monitor	4Q, 2008	29	SLYT311
Output impedance matching with fully differential operational amplifiers	1Q, 2009	29	SLYT326
Using fully differential op amps as attenuators, Part 1: Differential bipolar input signals	2Q, 2009	33	SLYT336
Using fully differential op amps as attenuators, Part 2: Single-ended bipolar input signals	3Q, 2009	21	SLYT341
Interfacing op amps to high-speed DACs, Part 1: Current-sinking DACs	3Q, 2009	24	SLYT342
Using the infinite-gain, MFB filter topology in fully differential active filters	3Q, 2009	33	SLYT343
Using fully differential op amps as attenuators, Part 3: Single-ended unipolar input signals	4Q, 2009	19	SLYT359
Interfacing op amps to high-speed DACs, Part 2: Current-sourcing DACs	4Q, 2009	23	SLYT360
Operational amplifier gain stability, Part 1: General system analysis	1Q, 2010	20	SLYT367
Signal conditioning for piezoelectric sensors	1Q, 2010	24	SLYT369
Interfacing op amps to high-speed DACs, Part 3: Current-sourcing DACs simplified	1Q, 2010	32	SLYT368
Operational amplifier gain stability, Part 2: DC gain-error analysis	2Q, 2010	24	SLYT374
Operational amplifier gain stability, Part 3: AC gain-error analysis	3Q, 2010	23	SLYT383
Using single-supply fully differential amplifiers with negative input voltages to drive ADCs	4Q, 2010	26	SLYT394
Low-Power RF			
Using the CC2430 and TIMAC for low-power wireless sensor applications: A power-consumption study	2Q, 2008	17	SLYT295
Selecting antennas for low-power wireless applications	2Q, 2008	20	SLYT296
General Interest			
Synthesis and characterization of nickel manganite from different carboxylate precursors for thermistor sensors	February 2001	52	SLYT147
Analog design tools	2Q, 2002	50	SLYT122
Spreadsheet modeling tool helps analyze power- and ground-plane voltage drops to keep core voltages within tolerance	2Q, 2007	29	SLYT273

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(972) 644-5580
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm

Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+886-2-2378-6808
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

E042210

DLP is a registered trademark and Auto-Track, E2E, FilterPro, MSP430, SWIFT, and TINA-TI are trademarks of Texas Instruments. Acrobat and Reader are registered trademarks of Adobe Systems Incorporated. The *Bluetooth* word mark and logos are owned by the Bluetooth SIG, Inc., and any use of such marks by Texas Instruments is under license. Celeron is a trademark and StrataFlash is a registered trademark of Intel Corporation. InfiniBand is a service mark of the InfiniBand Trade Association. ZigBee is a registered trademark of the ZigBee Alliance. All other trademarks are the property of their respective owners.