

# High-efficiency AC adapters for USB charging

By Adnaan Lokhandwala

Product Manager

## USB charging for electronic gadgets

Universal serial bus (USB) charging has become a common means for powering electronic gadgets. The AC power adapter/battery charger for many new consumer devices like smartphones, tablets, and e-readers is in the 5- to 25-W power range and presents a USB Standard-A receptacle. The adapter output voltage of 5 V has become the preferred choice for compatibility with PC/desktop-port charging and communication. The current dominant interface is via a standard (mini or Micro-B) USB cable or, in some cases, a nonstandard connector. With battery charging gaining consumer attention, the odd “wall wart” is transforming into a “cool,” light, sleek, green charger. Beyond meeting standard regulatory requirements, original equipment manufacturers are pushing the performance envelope on adapter efficiency and no-load power, which is also known as vampire power. For example, leading manufacturers of mobile-phone chargers have agreed to a five-star (<30 mW of no-load power) charger-rating system. This makes it easy for consumers to compare and choose the most energy-efficient chargers.

Recently, there has been much talk about standardizing the input to mobile phones and creating a universal charger to charge any cell phone. In 2006, China issued a new regulation aimed at standardizing the wall charger and its connecting cable. Similarly, the GSM Association (GSMA) is now leading the Universal Charging Solution adapter initiative for powering mobile phones with a micro USB connector. The common charger is required to provide 5 V  $\pm$  5%, a minimum of 850 mA, and <150 mW of no-load


power. It must also comply with the USB Implementers Forum (USB-IF) Battery Charging Specification 1.1 (BC1.1).<sup>\*</sup> Besides providing ease of use for consumers, the standardized charger could potentially eliminate a multitude of duplicate chargers. Additionally, AC adapters with multiple USB outlets offer consumers the convenience of charging multiple devices without the need for a dedicated charger for each gadget. Chargers with higher output current also allow the possibility of fast battery charging, a key advantage over standard USB 2.0 ports that are limited to 500 mA. The increasing demand for these improvements, along with the continued push towards adapter designs with a smaller form factor, makes thermal management in this “black box” a huge challenge for power-supply designers.

## Power-supply architecture

For the power levels under consideration here, the flyback topology shown in Figure 1 is the preferred choice today due to its simplicity and low cost. The conduction loss on the secondary-side Schottky-diode rectifier (Figure 1a) becomes a limiting factor in achieving high-efficiency, compact adapter designs. For instance, in a typical 5-V/3-A adapter, the power loss in the diode rectifier alone at full load can be 30 to 40% of the total system losses (neglecting the compounding effect of secondary losses on increased primary-side losses). Implementing a synchronous rectifier (SR) for the output (Figure 1b) can increase the overall efficiency of the converter and, because much less heat is generated (fundamentally important in adapter designs), ease system thermal management.

<sup>\*</sup>USB-IF BC1.2 extends the charging-current range from 1.5 A to 5 A.

Figure 1. Simplified flyback topology

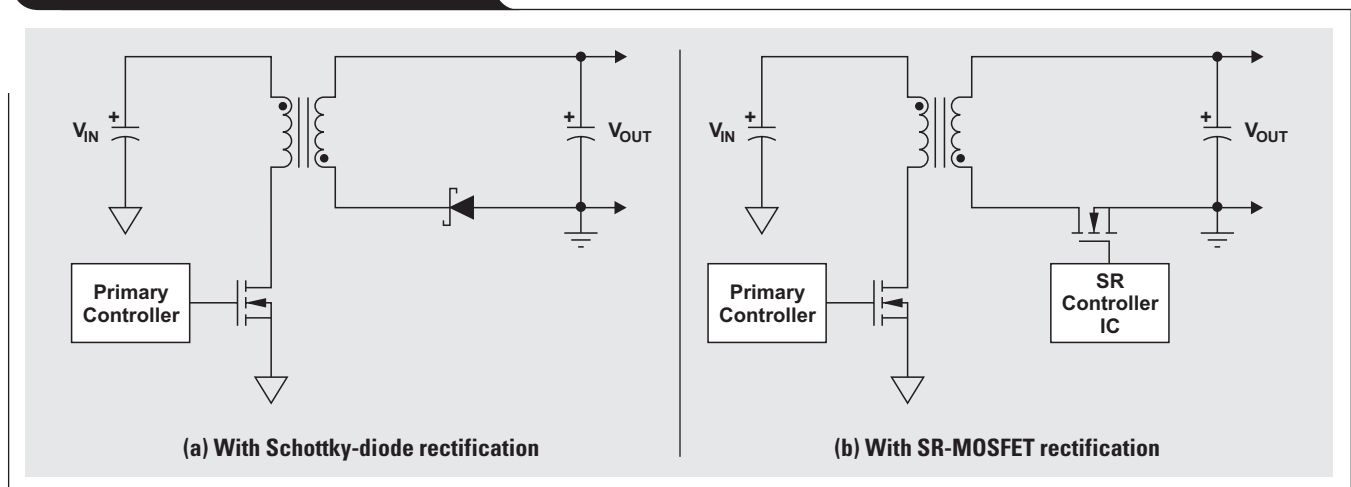

The conceptually simple change of adding an SR to the classic flyback topology can significantly reduce overall system power losses. The power level at which such a modification is practical has been decreasing with the rapid advancement in power MOSFET technology. Hence, synchronous rectification is now applicable to an ever-growing range of products. The lower power dissipation of an SR allows designers to take advantage of smaller components that have less heat sinking, thus increasing power density while lowering assembly costs, product size, and shipping weight.


Note that if the SR MOSFET is allowed to switch during no-load/standby conditions, the system power performance could be compromised. The SR-MOSFET switching losses, in addition to the quiescent power required by the SR controller IC, can be limiting factors in achieving the best possible system no-load performance.

### Green output rectification: Full load to no load


This article will now discuss how an IC such as the Texas Instruments (TI) UCC24610 Green Rectifier™ controller can simplify USB charger designs and enable high system efficiency across the full load range. Simplified system waveforms for a flyback converter with and without synchronous rectification are shown in Figure 2. The waveforms are the results of a control scheme that directly senses the MOSFET drain-to-source voltage ( $V_{DS}$ ). This control method is widely adopted today instead of other implementation choices such as primary-side synchronization or synchronous control from a secondary-side current transformer. Having the SR controller's turn-off threshold ( $V_{THOFF}$ ) as close as possible to zero in this control scheme allows maximum conduction time in the MOSFET channel.

Flyback converters can be designed to operate in different modes depending on the end-application requirements. For designs operating in continuous-conduction mode (CCM), the current in the transformer secondary does not fall to zero before the primary-side MOSFET is turned on, which results in a period of cross-conduction. When synchronous rectification is implemented in such converters, it is imperative that the SR MOSFET be turned off as soon as the primary-side switch turns on. This prevents reverse conduction and limits additional power losses and device stresses. Instead of waiting for the  $V_{THOFF}$  threshold detection, the synchronizing function in the Green Rectifier detects the primary-side turn-on transition and turns off the SR MOSFET. Figure 3 illustrates how the SR-gate turn-off transition is now controlled by a synchronizing signal from the primary side and not by  $V_{DS}$  sensing.

**Figure 2. Simplified flyback waveforms with Schottky-diode and SR-MOSFET output rectification**

 

**Figure 3. Typical CCM flyback waveforms with primary-side synchronization**

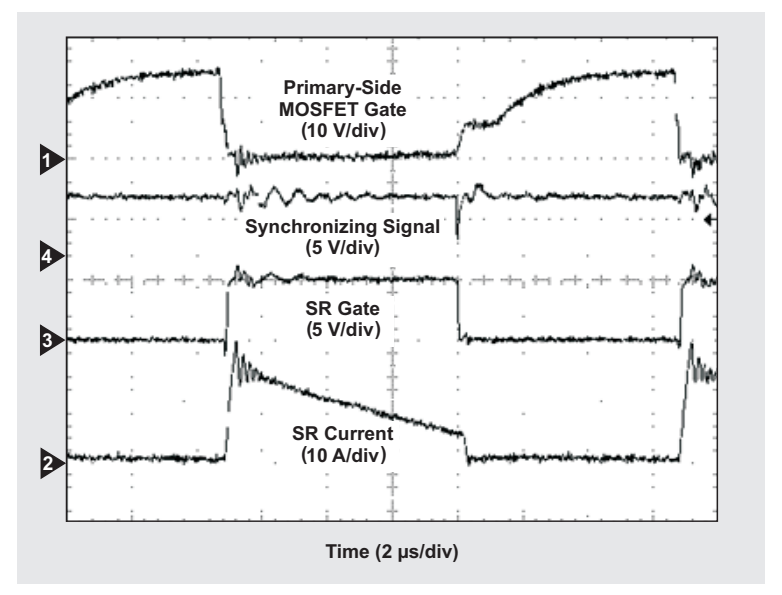

As described earlier, implementing synchronous rectification could possibly compromise light-load efficiency and no-load power consumption. The major contributors to loss at light or no load are SR-MOSFET switching and SR controller-IC bias. The Green Rectifier overcomes these issues with (1) an automatic light-load-detection circuit that disables gate switching of the SR MOSFET when its conduction time falls below a certain threshold, and (2) an EN function to put the IC in sleep mode and disable

quiescent power loss. The light-load-detection circuit compares the SR conduction time and the programmed minimum ON time (MOT) for every switching cycle. When the load decreases, the secondary conduction time becomes shorter than the MOT, and the next SR gate pulse is disabled. Further reduction in no-load power can be achieved by using the EN function of the controller IC. A simple averaging circuit on the MOSFET drain voltage can be used to put the IC in sleep mode at a no-load condition that limits the IC's bias-current consumption to 100  $\mu$ A. An additional 10 mW of no-load power consumption can be saved with this approach. The last gasp in improving no-load performance is to add a low-current Schottky diode in parallel with the SR MOSFET.


As an example, a USB charger with a 3-A current rating was designed using two controller chipsets, TI's UCC28610 and UCC24610, for a tablet-PC end application. The reference design for this charger, the PMP4305, can be seen at the Web site listed at the end of this article. The UCC24610 is good for applications with a 5-V flyback switch-mode power supply and can operate within the specified USB voltage range of 4.75 to 5.25 V. Hence, this SR controller was biased directly from the converter output, eliminating the need for an auxiliary winding on the main power transformer. The controller also allowed external programming of two blanking timers to prevent SR false triggering from  $V_{DS}$  ringing sensed during the turn-on and turn-off transitions. Figure 4 shows typical power-stage waveforms of the PMP4305 at full load. The IC control scheme was not affected by the severe ringing on the  $V_{DS}$  signal at turn-on because the programmable MOT timer disabled the  $V_{THOFF}$  comparator during this period.

A comparison of the efficiency of SR-MOSFET versus Schottky-diode output rectification at 115- and 230-V AC line conditions is shown in Figure 5. Implementing synchronous rectification enables over 80% efficiency from full load down to about 25% of full load. Additionally, for this load range, an SR configuration can achieve a three- to five-point improvement in efficiency over Schottky-diode rectification.


## Conclusion

USB power charging for consumer devices is gaining traction. A universal standard for 10- to 25-W chargers with USB outlets that power multiple devices eliminates the need for a new wall charger with every new gadget purchase. High-efficiency AC/DC converters are needed to satisfy the push towards high-density, small-form-factor adapters. Devices like the UCC24610 Green Rectifier can help improve AC/DC converter efficiency and enable the high-density USB-charger designs.

**Figure 4. Full-load waveforms from PMP4305**

 

**Figure 5. Comparison of system efficiency with Schottky diode versus synchronous rectifier (SR)**

 

## Related Web sites

[power.ti.com](http://power.ti.com)

[www.ti.com/product/UCC24610](http://www.ti.com/product/UCC24610)

[www.ti.com/product/UCC28610](http://www.ti.com/product/UCC28610)

Reference design for tablet-PC charger:

[www.ti.com/tool/PMP4305](http://www.ti.com/tool/PMP4305)

# TI Worldwide Technical Support

---

## Internet

### TI Semiconductor Product Information Center Home Page

[support.ti.com](http://support.ti.com)

### TI E2E™ Community Home Page

[e2e.ti.com](http://e2e.ti.com)

## Product Information Centers

<b>Americas</b>	Phone	+1(972) 644-5580
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	<a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a>

### Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	<a href="http://www.ti.com/asktexas">www.ti.com/asktexas</a>
Direct Email	<a href="mailto:asktexas@ti.com">asktexas@ti.com</a>

### Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>
	Domestic	<a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>

### Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
<b>Note:</b> Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	<a href="mailto:tiasia@ti.com">tiasia@ti.com</a> or <a href="mailto:ti-china@ti.com">ti-china@ti.com</a>
Internet	<a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A011012

E2E and Green Rectifier are trademarks of Texas Instruments. All other trademarks are the property of their respective owners.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2012, Texas Instruments Incorporated