

# How unmatched impedance at the clock input of an RF ADC affects SNR and jitter

By Thomas Neu  
System Engineer

## Introduction

Modern high-speed data acquisition systems, such as phased-array radars or high-speed digitizers, continue to push higher both the bandwidth and input-frequency requirements without any sacrifice of dynamic range performance. System designers need to deliver the highest possible signal-to-noise ratio (SNR) in order to optimize system performance down to a tenth of a decibel.

However, it is well known that as input frequencies increase, the analog-to-digital converter (ADC) SNR becomes increasingly sensitive to the sampling-clock’s timing uncertainty—or jitter. This applies to slower speed but high-precision ADCs with 16-bit resolution or more, and very high SNR. This situation also applies to high-speed 12- and 14-bit ADCs that have a wide bandwidth front-end to sample signals at multiple gigahertz. The SNR degradation follows a well known formula of:

$$SNR = 20\log(2\pi \times f_{IN} \times t_{jitter}),$$

where  $t_{jitter}$  is the combination of both external and internal aperture jitter. Figure 1 shows SNR dependency on the input frequency and the total amount of clock jitter for an ADC with 76-dB thermal noise

## What is aperture jitter?

In simple terms, the ADC clock input has both thermal and flicker noise components that get added to the clock signal, as in Figure 2a. The smaller the clock slew rate, the more dominant the noise factors when latching the clock signal. Therefore, the faster the rising edge of the clock signal, the less frequency error is present during the sampling instant at the zero crossing (Figure 2b). When using a sine-wave clock signal, the slew rate and amplitude are directly related to each other.

Designing for optimum ADC-aperture jitter for modern RF-sampling converters operating at 2+ GSPS can consequently become challenging. The system designer has to ensure delivery of a large-amplitude clock signal to the ADC while addressing RF issues. Examples of these issues include excessive board attenuation (the higher the frequency the higher the attenuation), higher voltage standing-wave ratio (VSWR), and lack of impedance matching.

Figure 1. ADC SNR versus jitter


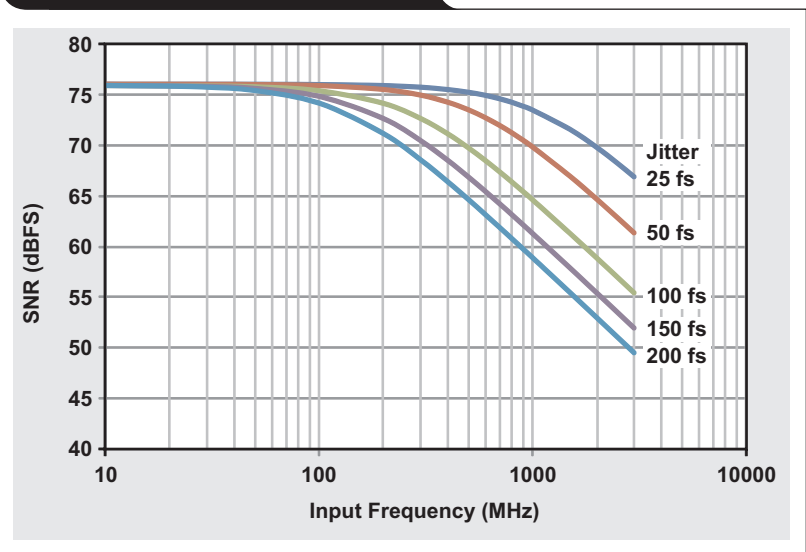


Figure 2. ADC clock-input noise sources

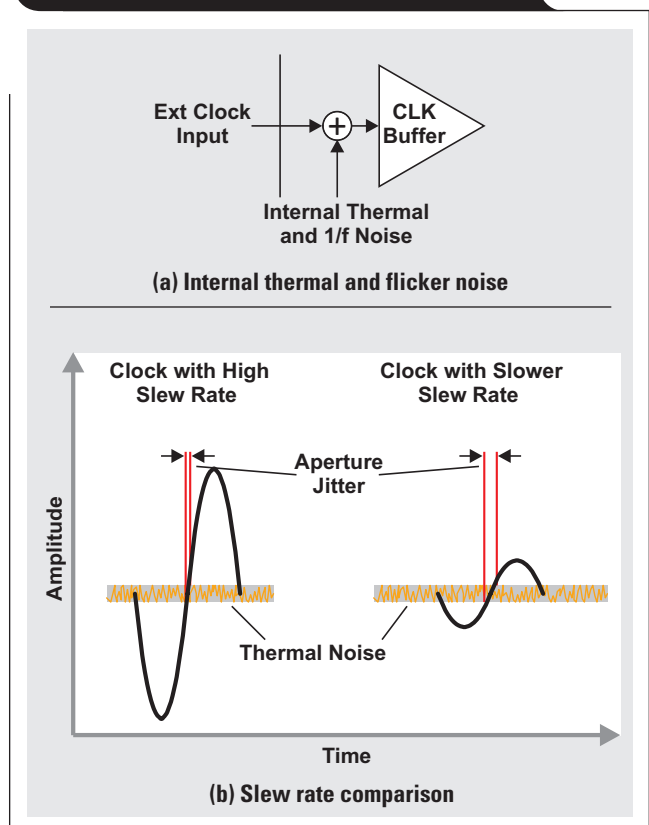

While there are a few ways to improve and optimize external jitter, such as using a low-jitter clock source or an external bandpass filter, the ADC aperture jitter depends primarily on the clock amplitude. See the example in Figure 3.


### Impact of reduced clock amplitude

When examining the frequency spectrum of a sampled sine wave in a fast Fourier transform (FFT), the impact of the clock amplitude to the ADC aperture jitter becomes clearly visible as shown in Figure 4. For Figure 4, the ADC sampling rate was 2.949 GSPS with an input signal of 1.81 GHz at  $-2$  dBFS, and clock amplitudes of  $500$  mV<sub>PP</sub> and  $1$  V<sub>PP</sub>. The full Nyquist-zone fast-Fourier transform (FFT) (Figure 4a) shows a uniform increase of the overall noise floor. When normalizing the FFT to the sine-wave frequency (Figure 4b), note that there is an increase in the  $1/f$  noise component of the ADC aperture jitter. This needs to be taken into consideration when designing systems with certain noise power targets at specific offset frequencies, such as global system for mobile communication (GSM) or long-term evolution (LTE) base stations or radar receivers.


### Is impedance matching required on the clock input?

Input impedance matching can be a simple but very effective way to significantly boost the clock amplitude and improve the ADC aperture jitter. An RF-sampling ADC typically has integrated termination resistors. Otherwise, in order to minimize reflection, the termination resistor should be placed as close to the end of the transmission line as possible. At higher clock frequencies, increased degradation can


**Figure 3. Aperture dependency on clock amplitude from ADC32RF45 data sheet**

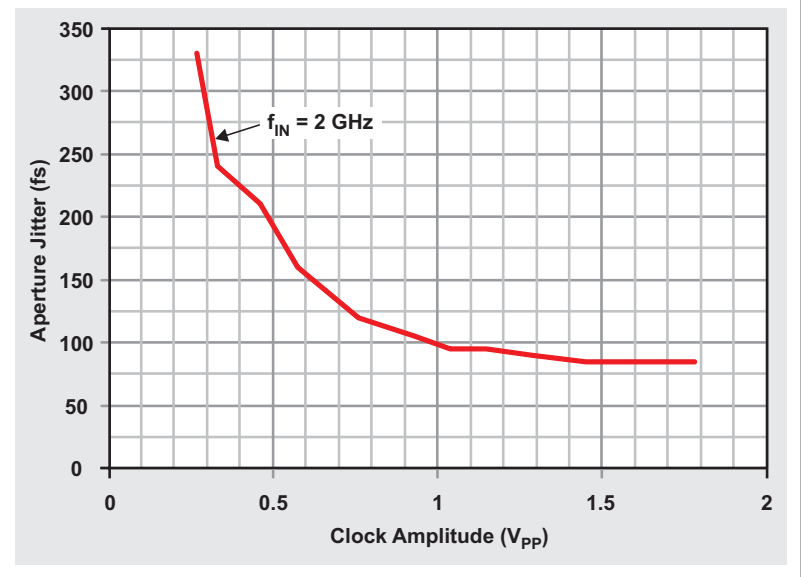

**Figure 4. Fast-Fourier transform (FFT) of an ADC**

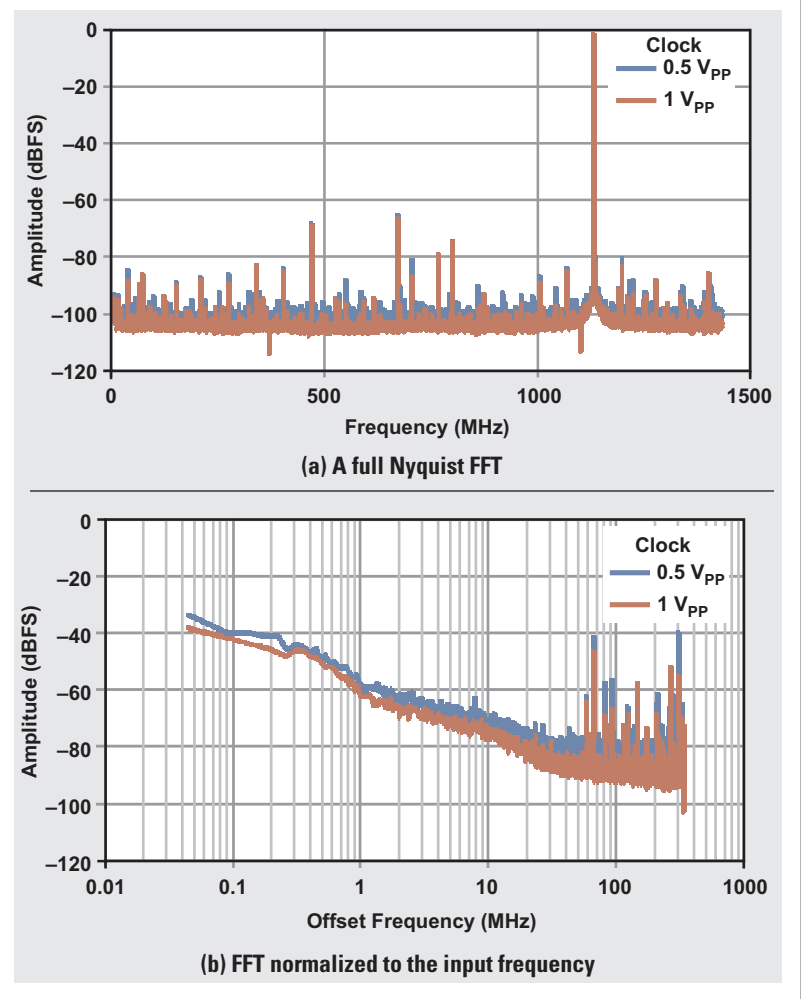

**Figure 5. Smith chart of the clock input impedance versus frequency of the ADC**

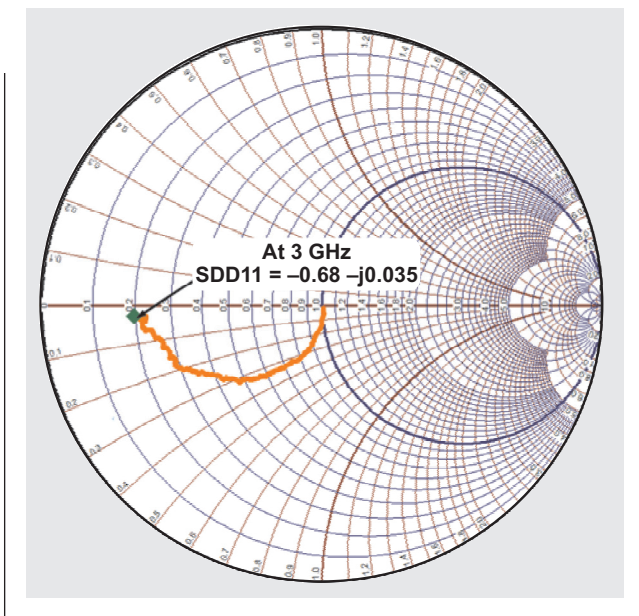

be attributed to the board and internal layout in addition to increased routing parasitics of the termination impedance. This is reflected in the Smith chart of the ADC32RF45 clock input in Figure 5.


In this example, with a clock frequency of 3 GHz, the internal differential 100-Ω termination looks more like a complex impedance of about 20 Ω. This reduced load impedance significantly impacts the amplitude in two different aspects:

1. The reduced load impedance makes it much harder for the clock source to deliver sufficient clock amplitude to the clock-input buffer for optimum ADC aperture jitter.
2. The load impedance is significantly different from the source and transmission-line impedance. This mismatch causes unwanted reflections and noise on the ADC’s clock input. Due to the impedance mismatch, the resulting voltage divider delivers significantly less amplitude compared to the power match. In a power match, the load and source impedances match, resulting in a 50/50 voltage divider to deliver maximum amplitude to the load.

Fortunately, a simple first-order matching network with two or three passive components can be designed to match the ADC clock-input impedance at the desired sampling rate to the impedance of the transmission line (typically 50 Ω, single-ended).

The external matching circuit for the ADC32RF45 at a frequency of 3 GHz for a power match could consist of a differential ≈1.05-pF shunt capacitor (2.1-pF single-ended), and ≈1.1-nH series inductors at the clock input of the ADC (Figure 6a). This transforms the complex load impedance

**Figure 6. Clock-input loss simulation with and without matching network**

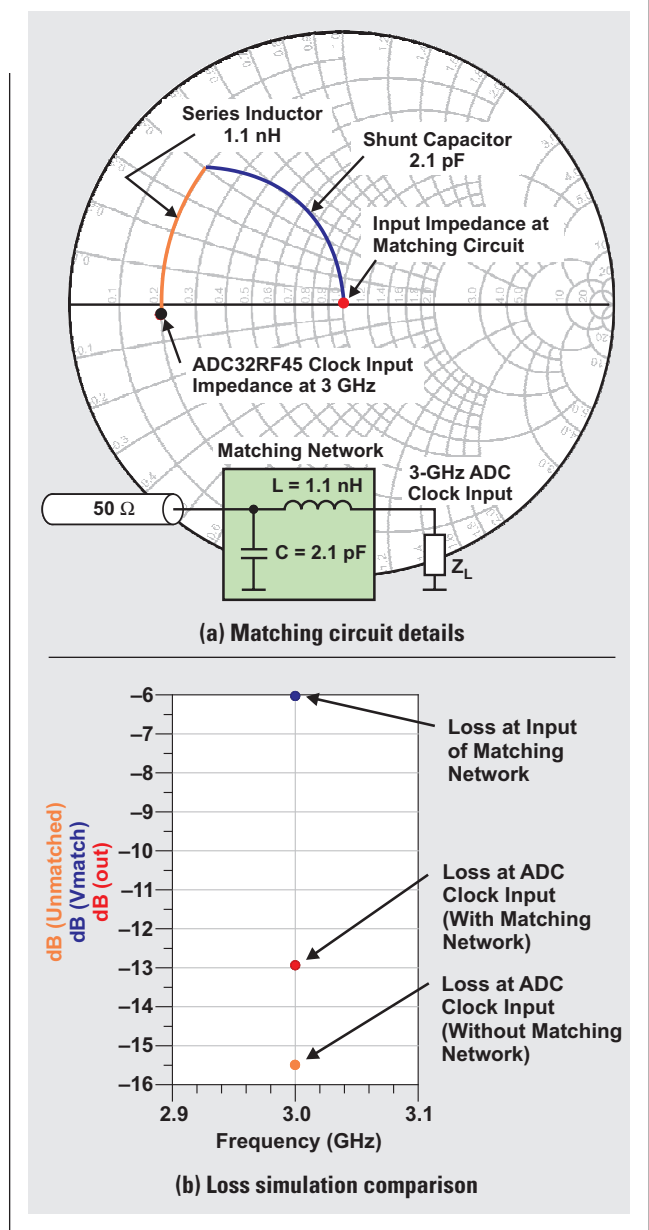

of about 10 Ω back to 50 Ω (100-Ω differential) for a clock frequency of 3 GHz. There are free online tools available to assist with this exercise.

This power match now delivers maximum amplitude at the new load’s input, which consists of a matching circuit plus load impedance. Additionally the matched load presents a larger load impedance to the clock generator, which enables it to provide a larger output amplitude. However, there is still a voltage divider present between the matching circuit and the load impedance. Hence, some amplitude loss will always be present as illustrated in Figure 6b. When compared to a similar setup without a matching

circuit, the amplitude delivered to the clock input with a matching circuit improved by 2.5 dB. Note that the clock source also delivers a higher amplitude, driving a 100- $\Omega$  load instead of a 20- $\Omega$  load.

## Conclusions

The amplitude of the sampling clock is a critical parameter since it is directly tied to the ADC aperture jitter. This is made clear when trying to maximize the receiver dynamic range and to achieve the advertised SNR performance of modern RF-sampling converters, such as the ADC32RF45. As the converter clock frequencies increase, the system designer has to counter additional attenuation from the PCB material as well as limited amplitude-drive capabilities from the clocking sources. A simple matching circuit at the clock input can avoid a heavy load for the clocking device while the matched impedances ensure that maximum amplitude is delivered to the load.

## References

1. Tommy Neu, "Direct RF conversion: From vision to reality," Texas Instruments White Paper (SLYY068), May 2015.
2. Robert Keller, "Signal chain basics #45: Is high-speed ADC clock jitter being over-specified for communication systems?" Planet Analog, September 2, 2010.
3. Overview of RF sampling with high-speed ADCs.

## Related Web sites

Product information:

**ADC32RF45**

Visit [www.ti.com/aaj](http://www.ti.com/aaj) to see all AAJ articles.

## TI Worldwide Technical Support

### Internet

#### TI Semiconductor Product Information Center Home Page

support.ti.com

#### TI E2E™ Community Home Page

e2e.ti.com

### Product Information Centers

<b>Americas</b>	Phone	+1(512) 434-1560
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

#### Europe, Middle East, and Africa

Phone		
European Free Call	00800-ASK-TEXAS (00800 275 83927)	
International	+49 (0) 8161 80 2121	
Russian Support	+7 (4) 95 98 10 701	

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

#### Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

### Asia

Phone	<u>Toll-Free Number</u>
<b>Note:</b> Toll-free numbers may not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
International	+86-21-23073444
Fax	+86-21-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)