

Understanding Voltage References: Simple Current Sink



Zachary Richards

Generating DC currents of arbitrary magnitude is a simple and straightforward process using operational amplifier feedback and a voltage reference. To this point, we have addressed several external opamp architectures for realizing individual or networks of current sources and sinks. In this final installment of the series, we will address an architecture which utilizes feedback from within the voltage reference itself. Let's begin by considering the voltage reference's symbol and its actual functional block diagram as displayed in [Figure 1](#) below.

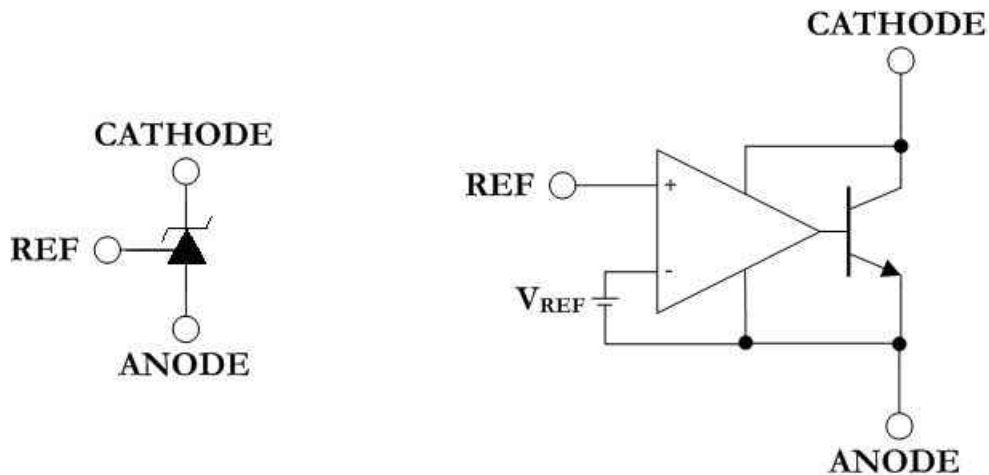


Figure 1. Voltage Reference and Its Functional Block Diagram

We have borrowed the symbol for the Zener diode because that's essentially how the voltage reference behaves; however, this behavior is achieved through clever design rather than simple device physics alone. Consider the self-referenced (cathode-reference-tied) configuration that was utilized in previous posts and shown in [Figure 2](#) below.

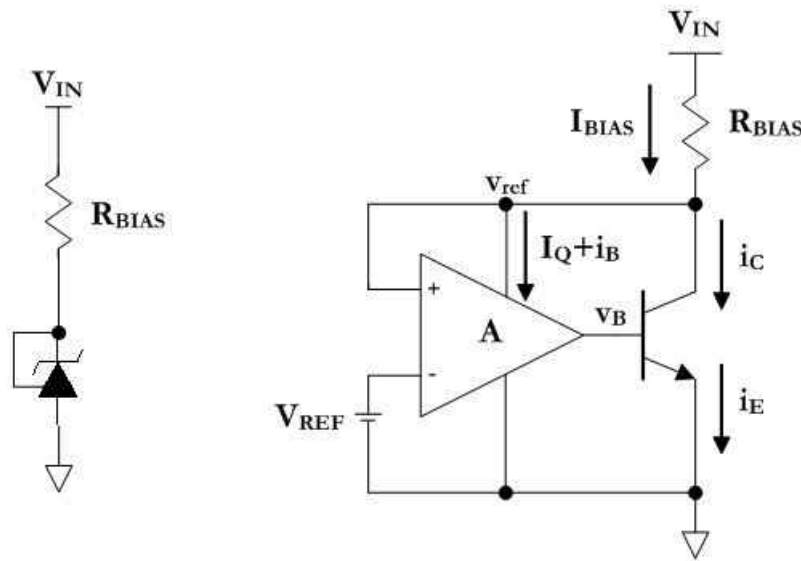


Figure 2. Voltage Reference Typical Operation

So, what can we say about this set up? First of all, we can greatly simplify and define the situation with all the currents in [Figure 2](#) as shown in Equation 1.

$$I_{BIAS} = I_Q + i_B + i_C = I_Q + i_E \quad (1)$$

That is, I_{BIAS} is the summation of the opamp quiescent current, I_Q , and the emitter current, i_E , of the bipolar junction transistor (BJT). Equation 2 further simplifies this by acknowledging that the opamp quiescent current will be negligible compared to the emitter current during normal operation.

$$I_{BIAS} \approx i_E \quad (2)$$

Equations 3 and 4 define the emitter current beginning with the diode equation for the base-emitter junction and assuming forward bias operation with nominal ideality factor.

$$i_E = I_S \cdot (e^{\frac{v_{BE}}{V_T}} - 1) \approx I_S \cdot e^{\frac{v_{BE}}{V_T}} \quad (3)$$

$$I_{BIAS} \approx I_S \cdot e^{\frac{v_{BE}}{V_T}} \quad (4)$$

As indicated by Equation 4 above, there must be some base-emitter voltage present to maintain I_{BIAS} . This of course implies that there is a non-zero difference between v_{ref} and V_{REF} in [Figure 2](#); we will account for this by defining v_{ref} in Equation 5 in terms of V_{REF} and a small perturbation voltage, ϵ_v .

$$v_{ref} = V_{REF} + \epsilon_v \quad (5)$$

We can now define ϵ_v in terms of the base-emitter voltage and opamp gain as shown in Equations 6 and 7.

$$v_{BE} = A \cdot (V_{REF} + \epsilon_v - V_{REF}) = A \cdot \epsilon_v \quad (6)$$

$$\epsilon_v = \frac{v_{BE}}{A} \quad (7)$$

Clearly ϵ_v drops to zero in the ideal opamp case; however, let's consider some very conservative values. Equation 8 below solves Equation 7 assuming the v_{BE} required to maintain I_{BIAS} is 0.5V and the gain of the opamp is a mediocre 10^4 .

$$\epsilon_v = \frac{0.5V}{10^4} = 50\mu V \quad (8)$$

For a 1.25V voltage reference, this represents an error of some four thousandths of a percent or 40ppm—that is, such an error can be safely regarded as negligible.

Now consider what happens to ϵ_v when we increase the input voltage, and therefore I_{BIAS} ; specifically, suppose we double I_{BIAS} from some arbitrary operating point as illustrated by Equations 9 and 10.

$$I_{BIAS1} = I_S \cdot e^{\frac{v_{BE1}}{V_T}} \quad (9)$$

$$I_{BIAS2} = I_S \cdot e^{\frac{v_{BE2}}{V_T}} = 2 \cdot I_{BIAS1} \quad (10)$$

The change in v_{BE} required to support doubling I_{BIAS} can now be derived by dividing Equation 10 by Equation 9 and simplifying terms as follows in Equations 11 through 13.

$$\frac{I_{BIAS2}}{I_{BIAS1}} = \frac{I_S \cdot e^{\frac{v_{BE2}}{V_T}}}{I_S \cdot e^{\frac{v_{BE1}}{V_T}}} = \frac{e^{\frac{v_{BE2}}{V_T}}}{e^{\frac{v_{BE1}}{V_T}}} = 2 \quad (11)$$

$$\frac{v_{BE2}}{V_T} - \frac{v_{BE1}}{V_T} = \ln(2) \quad (12)$$

$$\Delta v_{BE} = V_T \cdot \ln(2) \quad (13)$$

Finally, we can derive an equation for the change in ϵ_v required to support doubling I_{BIAS} as shown in Equations 14 and 15.

$$\Delta v_{BE} = A \cdot \epsilon_{v2} - A \cdot \epsilon_{v1} = A \cdot \Delta \epsilon_v \quad (14)$$

$$\Delta \epsilon_v = \frac{\Delta v_{BE}}{A} = \frac{V_T \cdot \ln(2)}{A} \quad (15)$$

Substituting in the room temperature value of the thermal voltage, V_T , and assuming (again) the mediocre opamp gain of 10^4 we can solve Equation 15 for a conservative value of $\Delta \epsilon_v$ required for doubling I_{BIAS} , resulting in Equation 16 below.

$$\Delta\varepsilon_v = \frac{V_T \cdot \ln(2)}{A} = \frac{17.92mV}{10^4} = 1.792\mu V \quad (16)$$

In this case, every time I_{BIAS} is doubled the voltage at v_{ref} increases by only $1.792\mu V$. It is this multiplication of opamp gain with the exponential IV characteristic of the base-emitter diode which mimics Zener breakdown behavior.

Connecting the voltage reference differently we can leverage its internal opamp to generate a simple current sink as shown in [Figure 3](#) below.

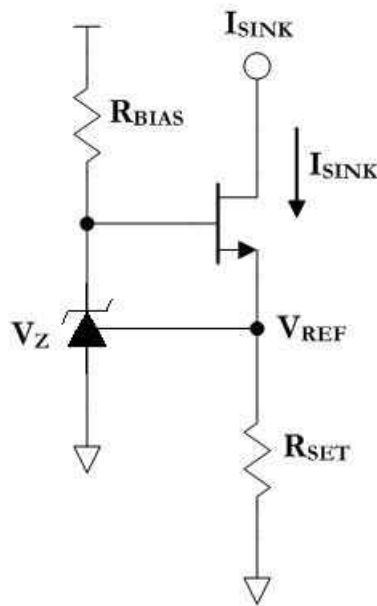


Figure 3. Simple Voltage Reference Derived Current Sink

To visualize what's going on here, consider the functional diagram inserted in place of the symbol as shown in [Figure 4](#) below.

 


Figure 4. Simple Current Sink Functional Diagram

Notice that the V_{IN} , R_{BIAS} , and BJT circuit essentially acts as an inverting output stage for the opamp. Therefore, we can collapse the total combination into a new opamp symbol with a new gain, A_T , and reversed input polarity as shown below in [Figure 5](#).

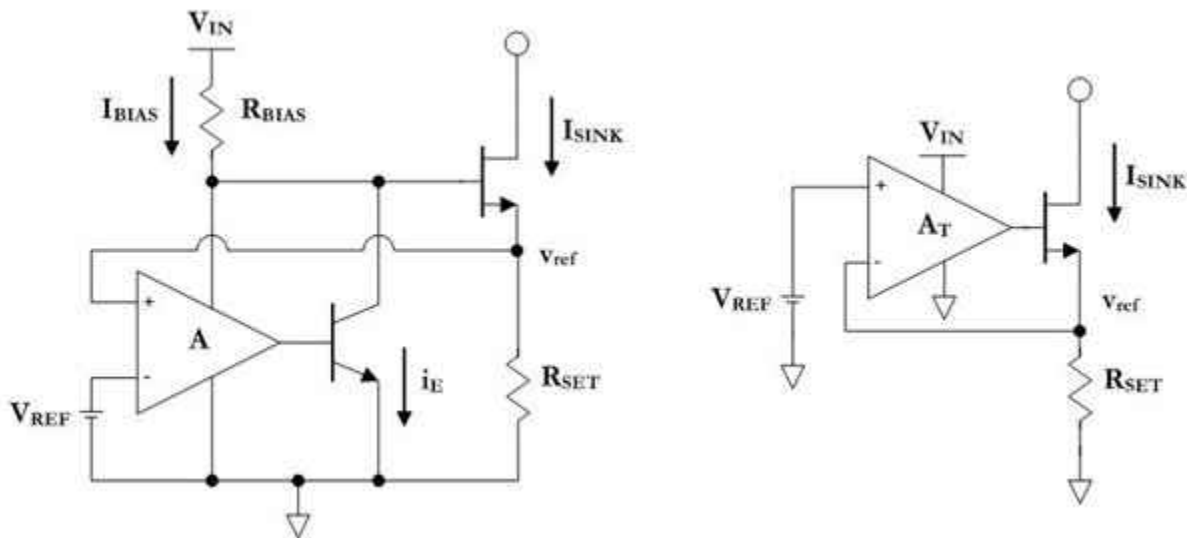


Figure 5. Simple Current Sink Functional Diagram and Equivalent Circuit

Thus, we have arrived at the same current sink circuit discussed in the first post in this series.

Throughout this series we have investigated the important topic of generating current references from voltage references. The [first](#) post covers precision, single sources and sinks of arbitrary magnitude (which can, of course, be used to implement bias networks); the [second](#) and [third](#) posts discuss a method by which bias networks might be derived with a single feedback device if a tradeoff of precision and component count is workable; and finally, this post discusses a greatly simplified method of implementing the current sink (specifically) discussed in the first post. The architectures discussed throughout this series are a handy addition to any design toolbox, and Texas Instruments has a wide variety of voltage references which can be used to realize these designs.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated