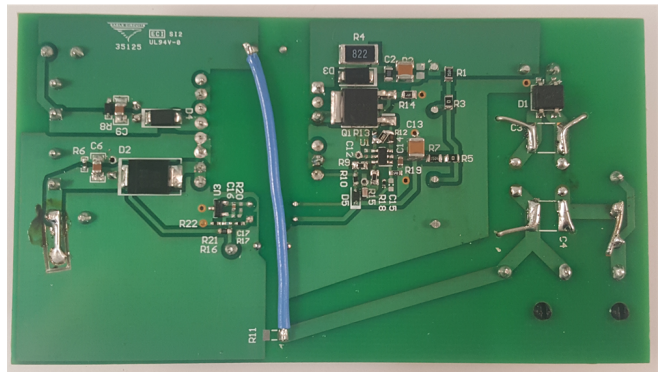
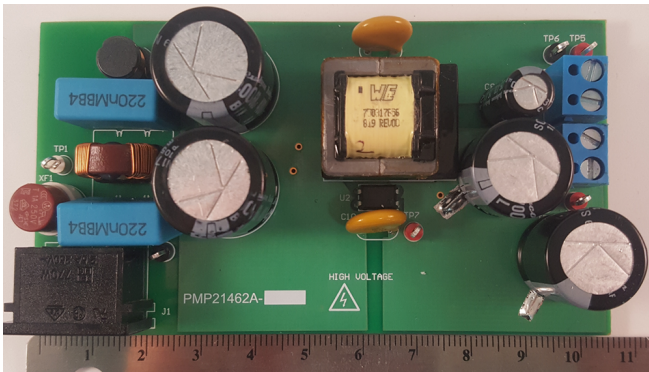


Test Report: PMP21462 12-Watt, Magnetically Resistant, Quasi-Resonant Flyback Reference Design



Description

PMP21462 is a quasi-resonant flyback developed to be resistant to large magnetic fields near the transformer. It has a regulated 4-V output that can handle up to 2 A of current and secondary 10-V output that can handle 0.4 A.



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
V_{IN}	90-490 V _{AC}
V_{OUT}	4 V / 2 A , 10 V / 400 mA
Nominal switching frequency	26 kHz

1.2 Considerations

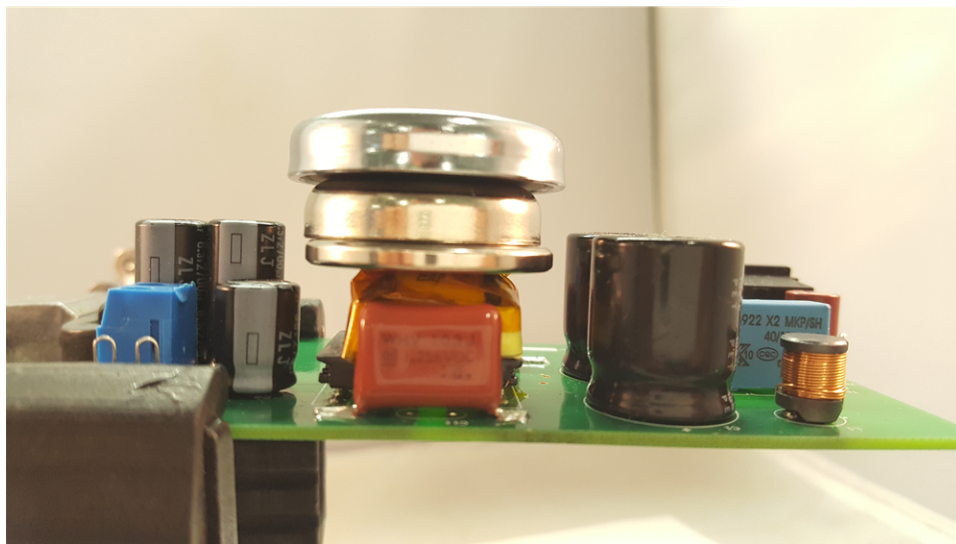


Figure 1. Magnets on Top of Transformer

2 Testing and Results

2.1 Efficiency Graphs

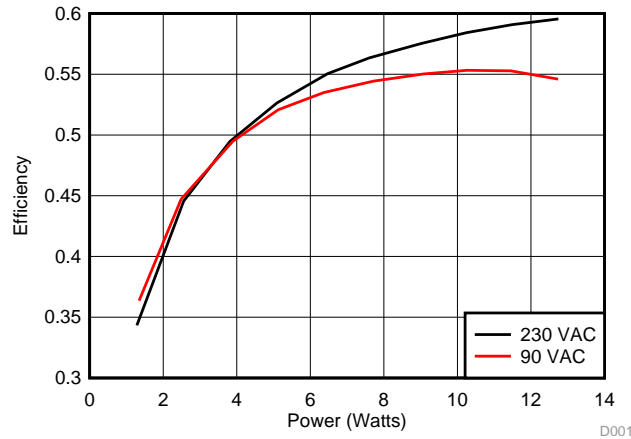


Figure 2. Efficiency of Design at Various Loads

2.2 Efficiency Data

Table 2. 230-V_{AC} Efficiency Data

V _{in} (V _{rms})	I _{in} (mArms)	P _{in} (W)	PF	V _{out} (4 V)	I _{out} (A)	V _{out} (10 V)	I _{out} (a)	P _{out} (W)	EFFICIENCY
230.9	53.99	3.741	0.3	4.081	0.2	11.7	0.04	1.284	0.343
230.9	73.18	5.736	0.34	4.069	0.392	11.71	0.082	2.555	0.445
230.9	92.36	7.712	0.362	4.063	0.593	11.72	0.12	3.816	0.495
230.9	111.43	9.672	0.376	4.059	0.798	11.72	0.158	5.091	0.526
230.9	131.37	11.757	0.388	4.057	1.012	11.71	0.202	6.471	0.550
230.9	147.89	13.494	0.396	4.055	1.178	11.68	0.242	7.603	0.563
230.9	168.43	15.674	0.403	4.054	1.41	11.67	0.283	9.019	0.575
230.9	185.91	17.538	0.409	4.053	1.599	11.66	0.323	10.247	0.584
230.9	203.7	19.432	0.414	4.053	1.792	11.65	0.362	11.480	0.591
230.9	222	21.4	0.418	4.052	2.002	11.64	0.398	12.745	0.596

Table 3. 90-V_{AC} Efficiency Data

V _{in} (V _{rms})	I _{in} (mArms)	P _{in} (W)	PF	V _{out} (4 V)	I _{out} (A)	V _{out} (10 V)	I _{out} (a)	P _{out} (W)	EFFICIENCY
90.4	92.95	3.695	0.44	4.086	0.211	11.74	0.041	1.343	0.364
90.36	134.14	5.562	0.459	4.074	0.38	11.73	0.08	2.487	0.447
90.31	184.32	7.869	0.473	4.065	0.614	11.75	0.119	3.894	0.495
90.26	226.7	9.846	0.481	4.061	0.798	11.72	0.161	5.128	0.521
90.22	269.9	11.909	0.489	4.059	1.006	11.73	0.195	6.371	0.535
90.17	313.8	14.169	0.501	4.057	1.214	11.71	0.238	7.712	0.544
90.13	354.4	16.496	0.517	4.056	1.423	11.68	0.283	9.077	0.550
90.09	389.7	18.549	0.528	4.055	1.605	11.66	0.322	10.262	0.553
90.05	427.7	20.72	0.538	4.054	1.789	11.64	0.361	11.455	0.553
90	474.2	23.33	0.546	4.052	2	11.64	0.398	12.737	0.546

2.3 Thermal Images

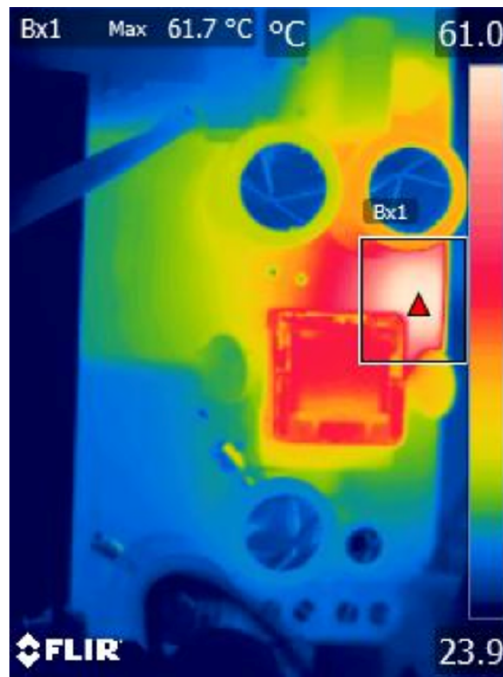


Figure 3. 90-V_{AC}, 60 Hz Front Side Thermal Picture

Figure 3 shows testing done at a nominal load of 4 V/0.2 A and 10 V/ 0.02 A.

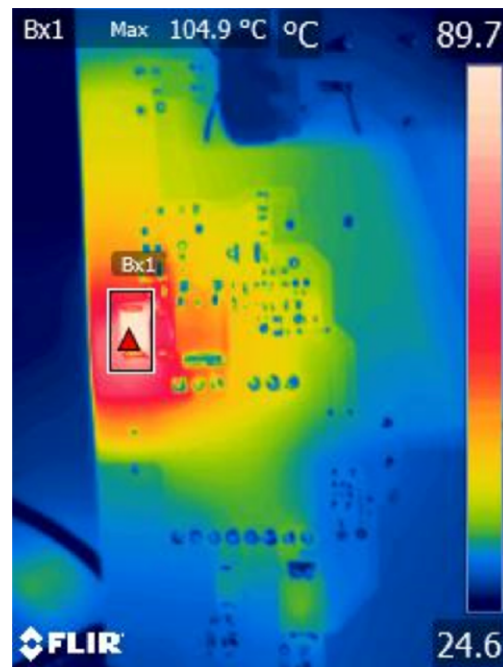


Figure 4. 90-V_{AC}, 60 Hz Back Side Thermal Picture

Figure 4 shows testing done at a nominal load of 4 V/0.2 A and 10 V/0.02 A.

3 Waveforms

3.1 Switching

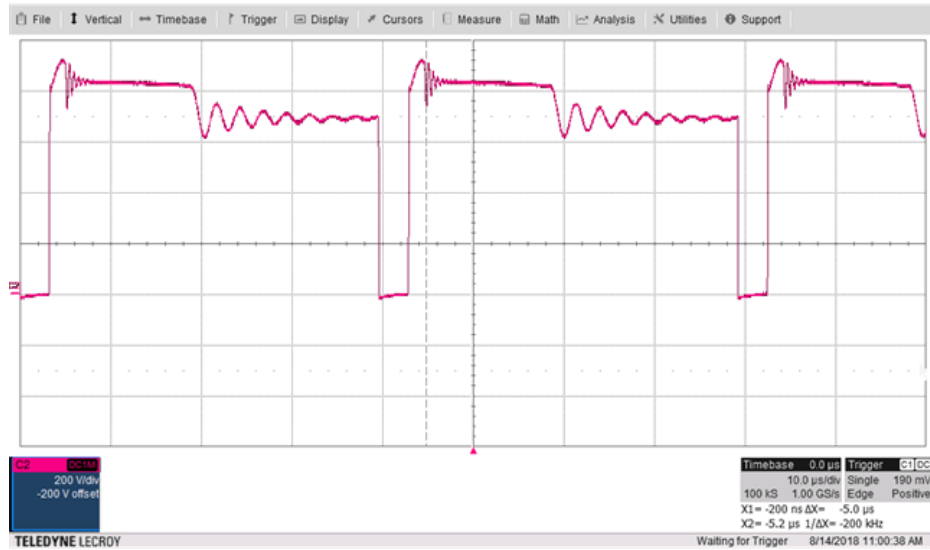


Figure 5. Switch Node Tested at 690 V_{DC}

Measurement was taken across the drain to source voltage of primary side MOSFET (Q1) in Figure 5.

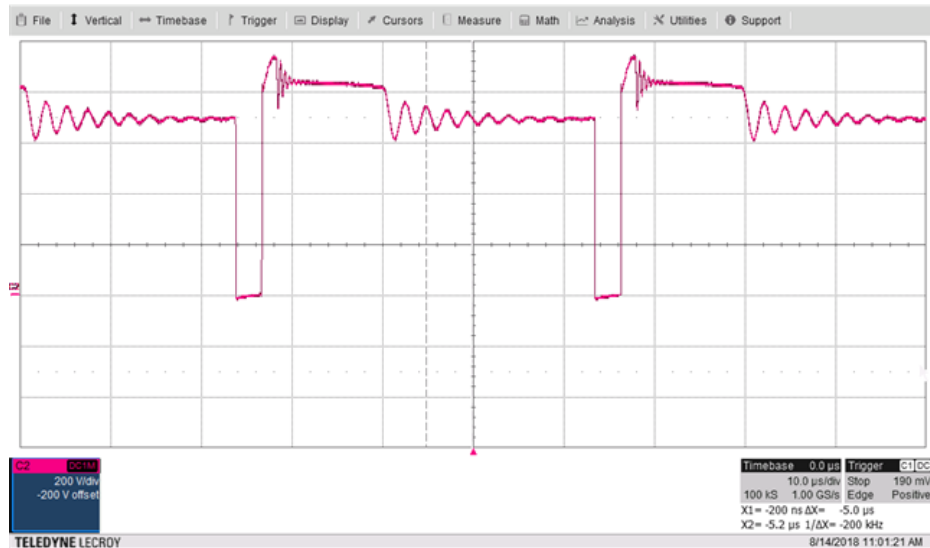


Figure 6. Switch Node Tested at 690 V_{DC} With Applied Magnetic Field

Measurement was taken across the drain to source voltage of primary side MOSFET (Q1) in Figure 6.

3.2 Diode Stress

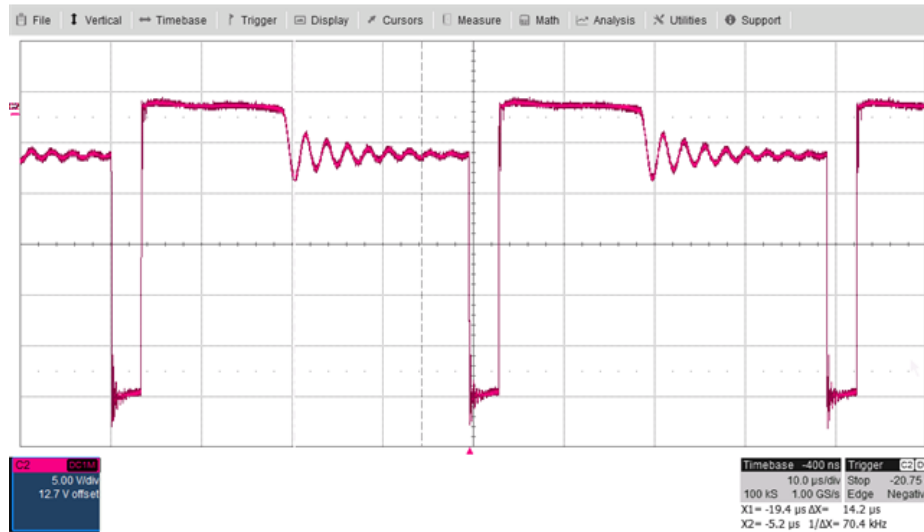


Figure 7. 4-V Output Diode (D2) Voltage Stress

Figure 7 shows testing done at 690-V_{DC} input with fully loaded output.

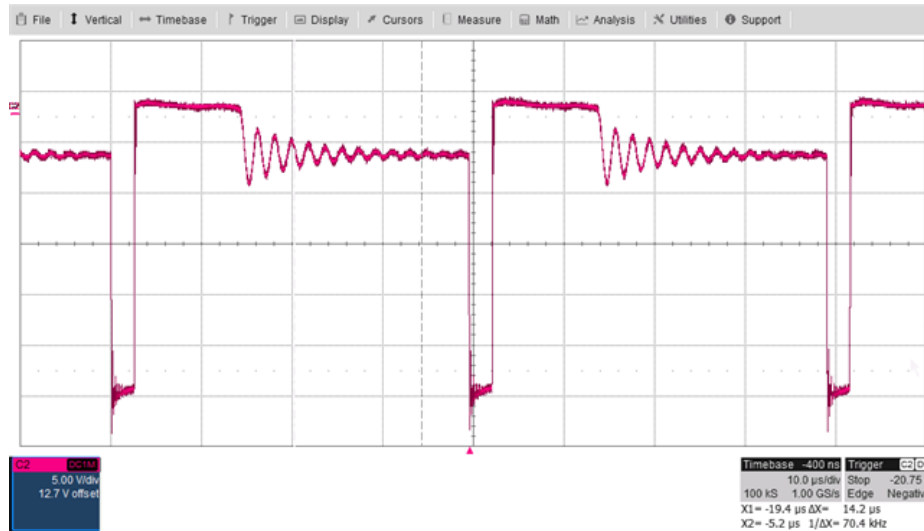


Figure 8. 4-V Output Diode (D2) Voltage Stress With Applied Magnetic Field

Figure 8 shows testing done at 690-V_{DC} input with fully loaded output.

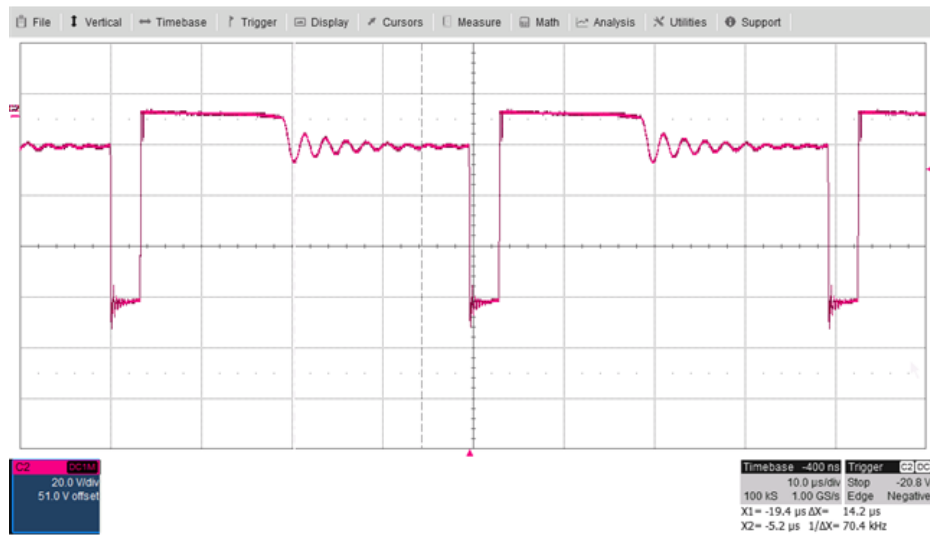


Figure 9. 10-V Output Diode (D4) Voltage Stress

Figure 9 shows testing done at 690-V_{DC} input with fully loaded output.

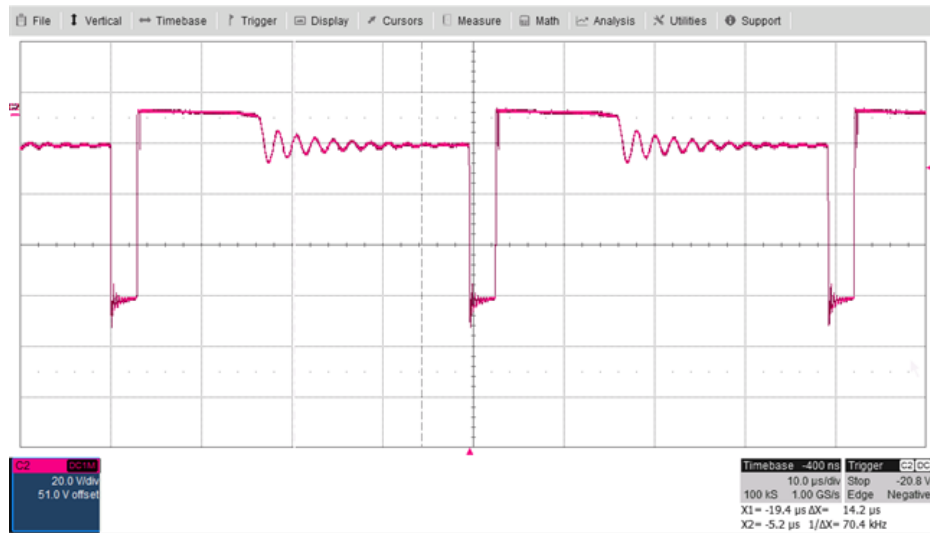


Figure 10. 10-V Output Diode (D4) Voltage Stress With Applied Magnetic Field

Figure 10 shows testing done at 690-V_{DC} input with fully loaded output.

3.3 Output Voltage Ripple



Figure 11. Ripple on 4-V Line

Figure 11 shows ripple tested at 230-V_{AC} input and fully loaded output.

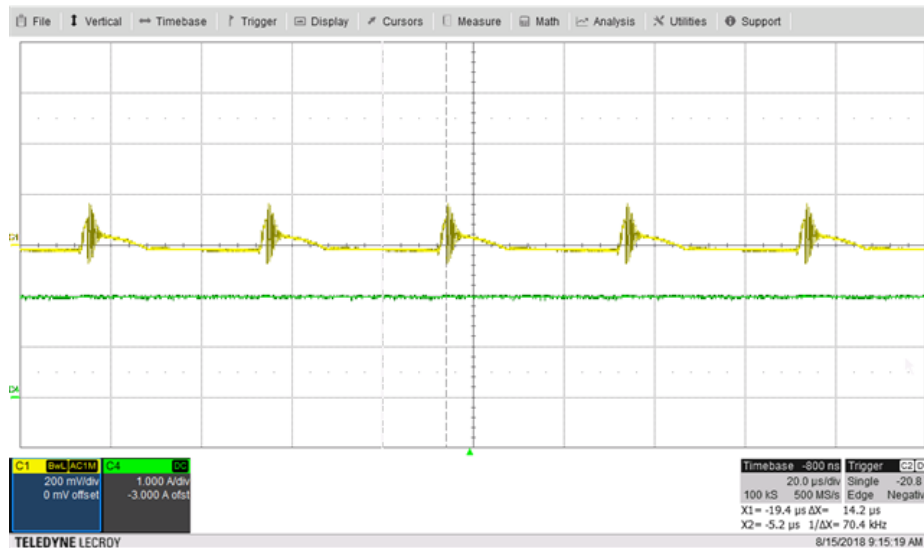


Figure 12. Ripple on 4-V Line With Applied Magnetic Field

Figure 12 shows ripple tested at 230-V_{AC} input and fully loaded output.

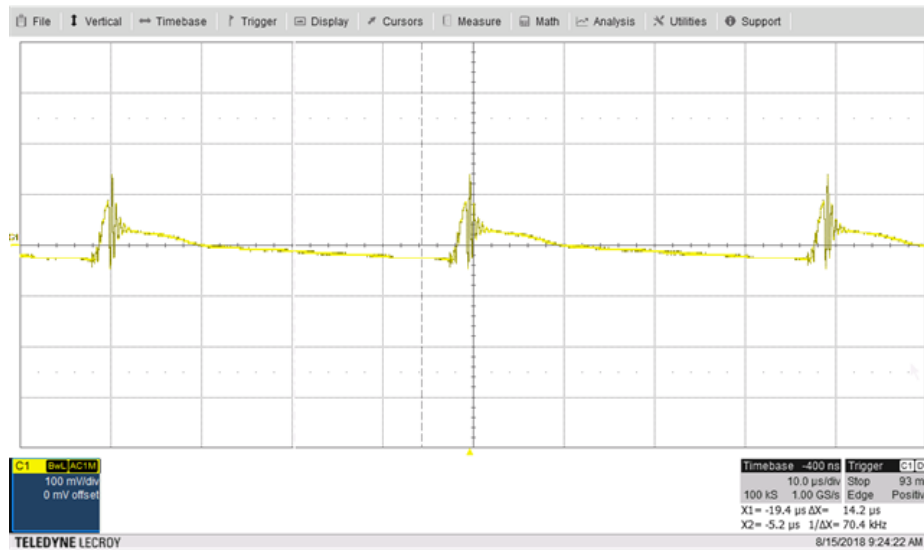


Figure 13. Ripple on 12-V Line

Figure 13 shows ripple tested at 230-V_{AC} input and fully loaded output.

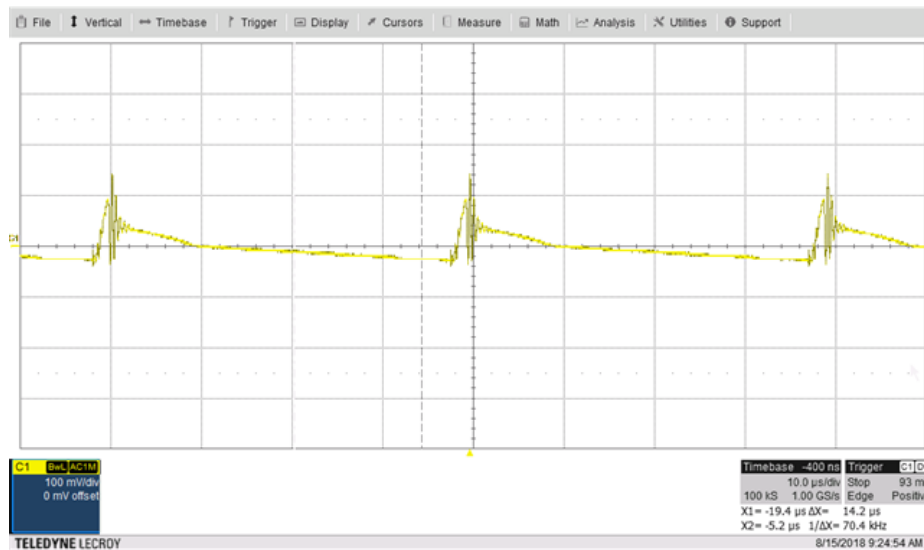


Figure 14. Ripple on 12-V Line With Applied Magnetic Field

Figure 14 shows ripple tested at 230-V_{AC} input and fully loaded output.

3.4 Bode Plot

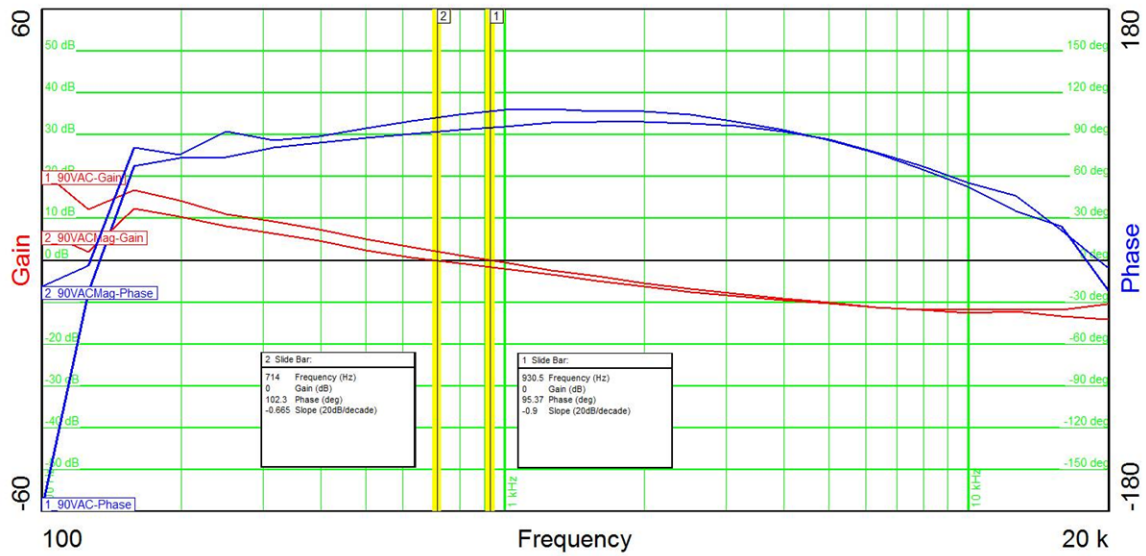


Figure 15. Bode Plot at 90 V_{AC}

Figure 15 shows testing done at 90-V_{AC} input and fully loaded output.

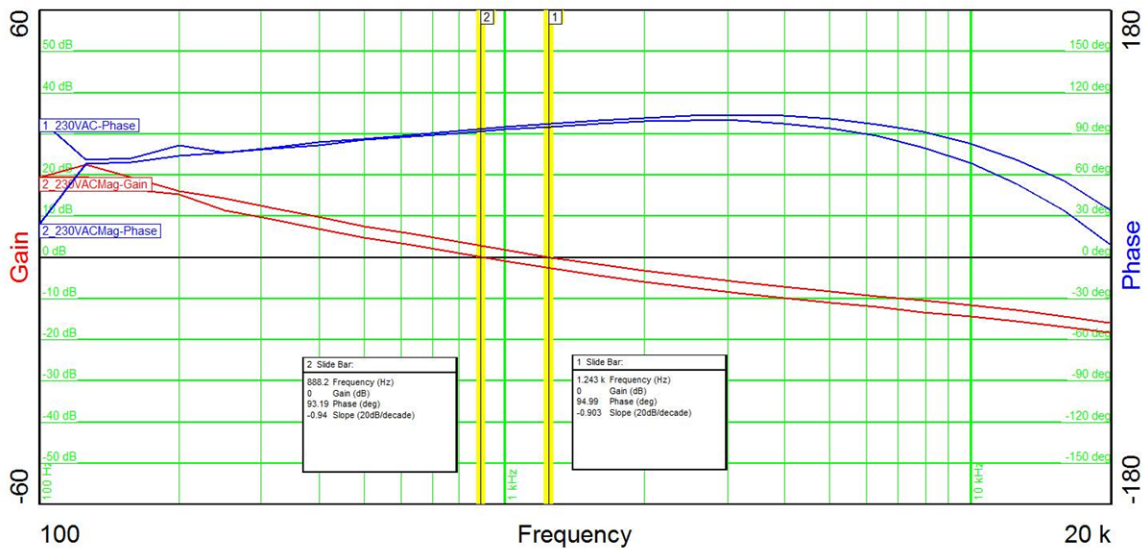


Figure 16. Bode Plot at 230 V_{AC}

Figure 16 shows testing done at 230-V_{AC} input and fully loaded output.

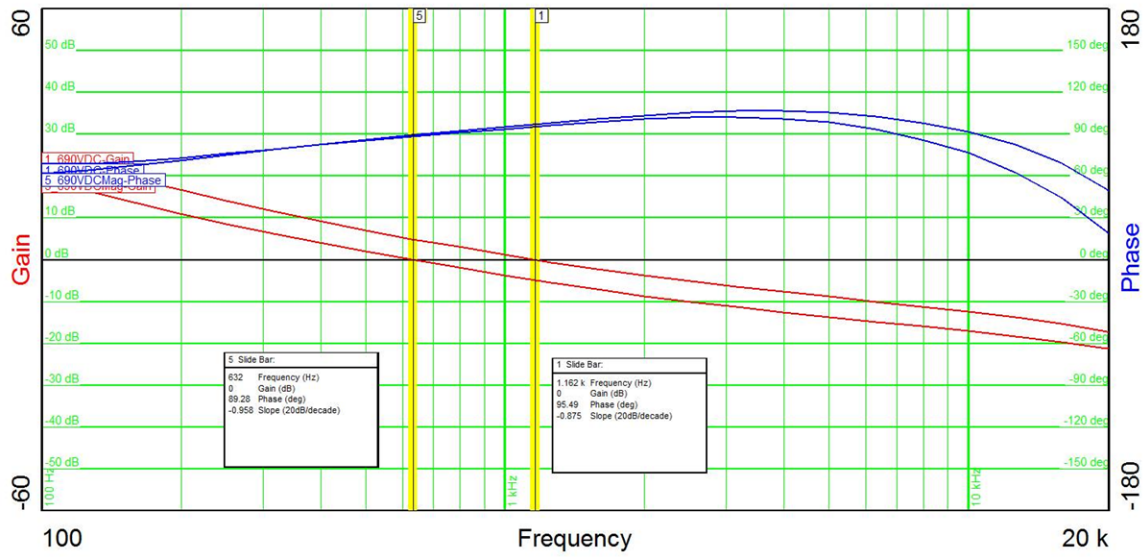


Figure 17. Bode Plot at 690 V_{DC}

Figure 17 shows testing done at 690-V_{DC} input and fully loaded output.

3.5 Load Transients

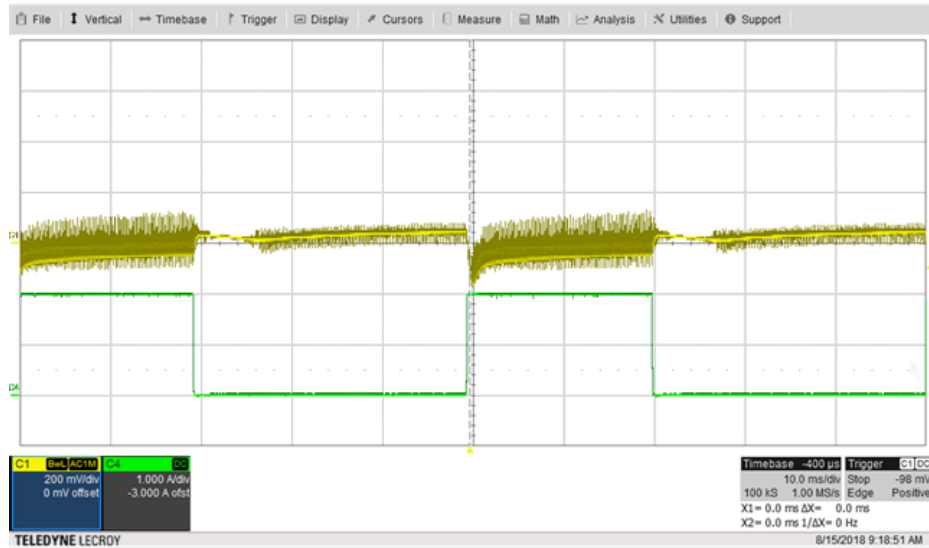


Figure 18. Load Transient on 4-V Line

Figure 18 shows load transient on a 4-V line switching between 0 A and 2 A.

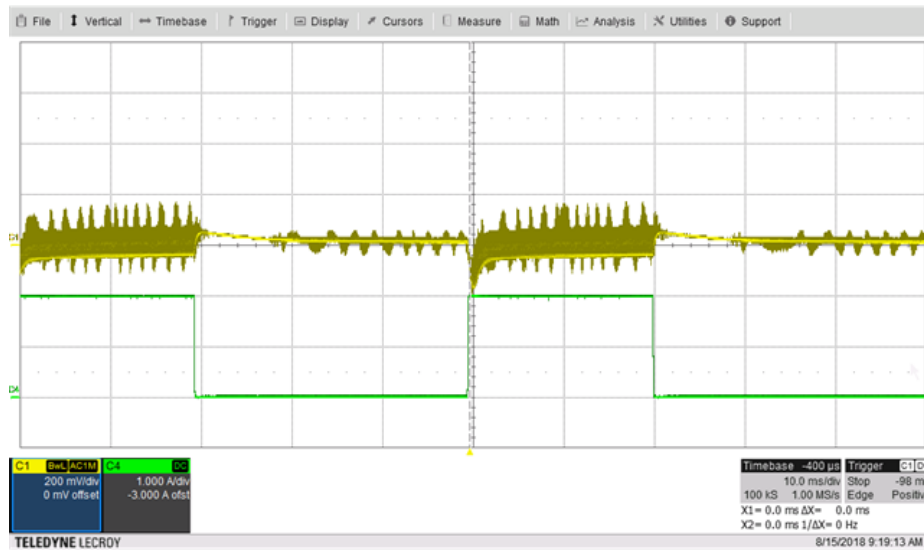


Figure 19. Load Transient on 4-V Line With Applied Magnetic Field

Figure 19 shows load transient on a 4-V line switching between 0 A and 2 A.

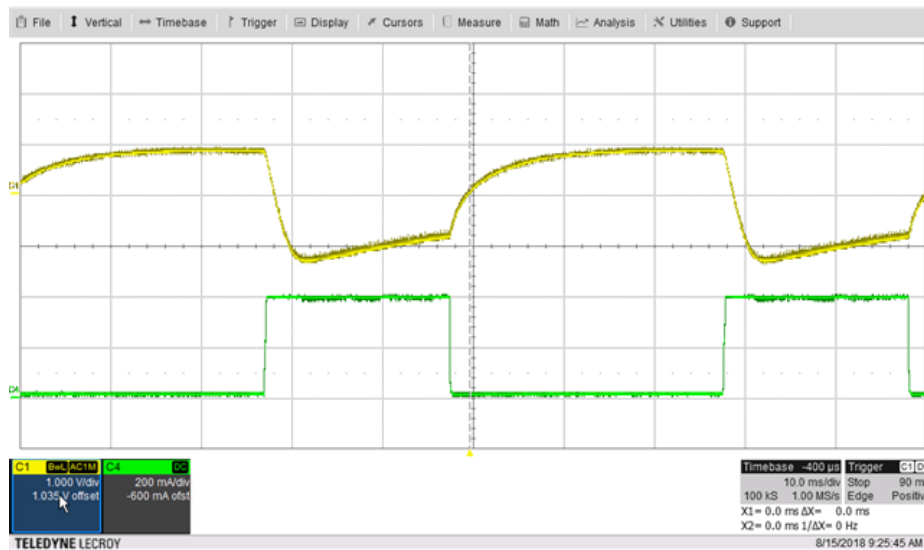


Figure 20. Load Transient on 10-V Line

Figure 20 shows load transient on a 10-V line switching between 0 A and 400 mA.

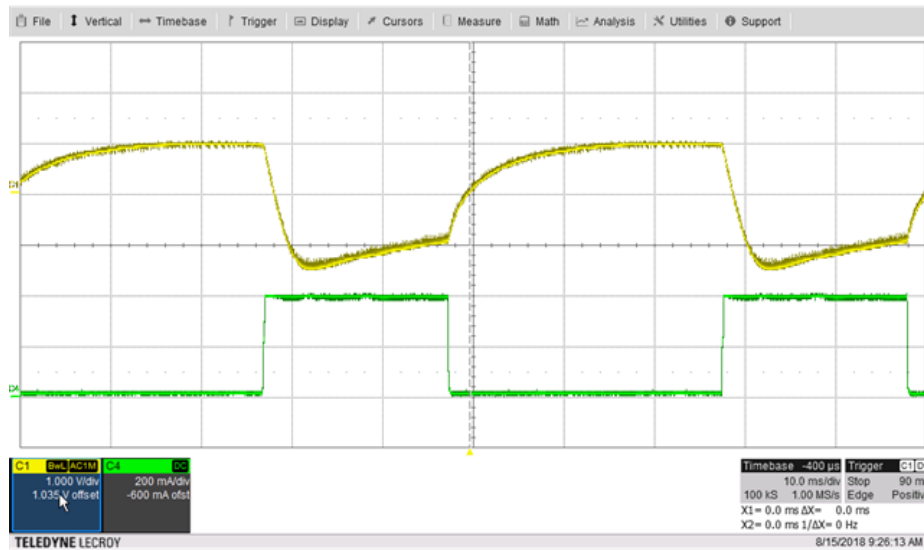


Figure 21. Load Transient on 10-V Line With Applied Magnetic Field

Figure 21 shows load transient on a 10-V line switching between 0 A and 400 mA.

3.6 Start-up and Shutdown

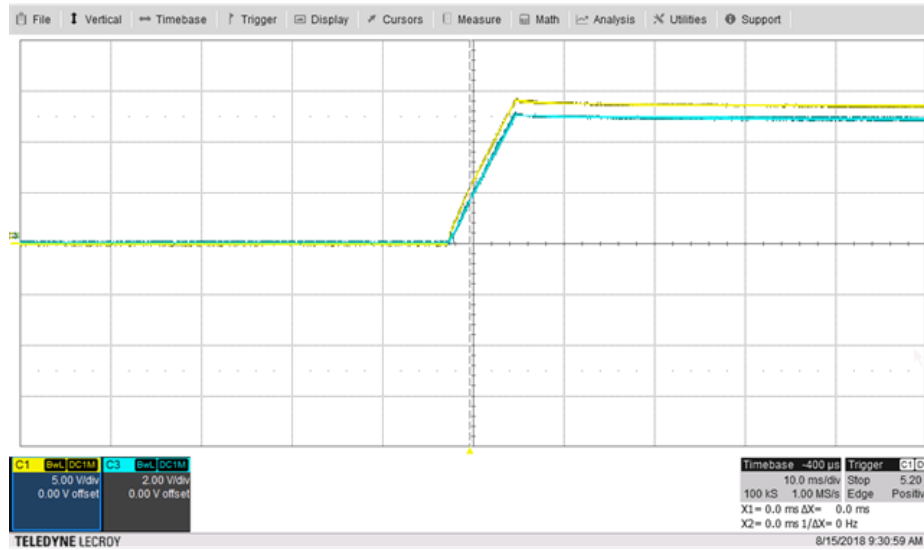


Figure 22. Start-up With No Load

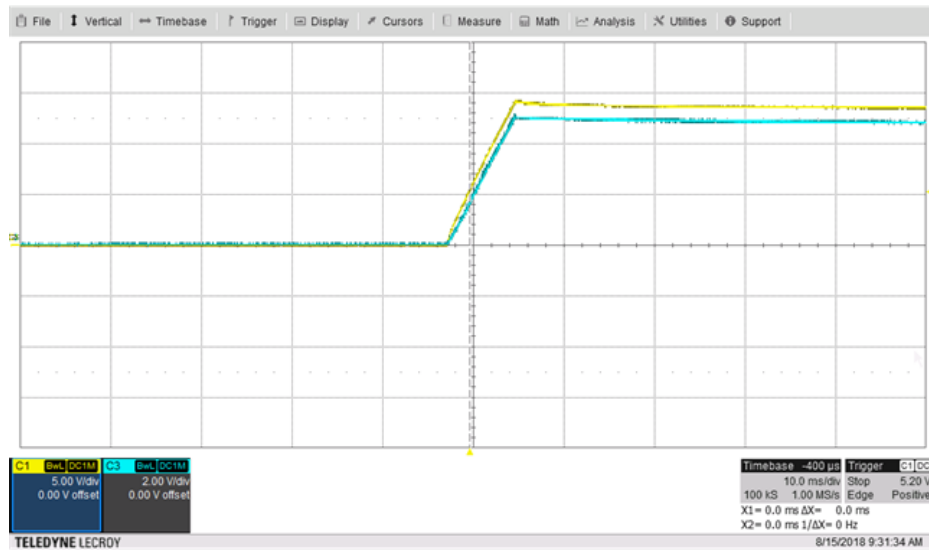


Figure 23. Start-up With No Load With Applied Magnetic Field

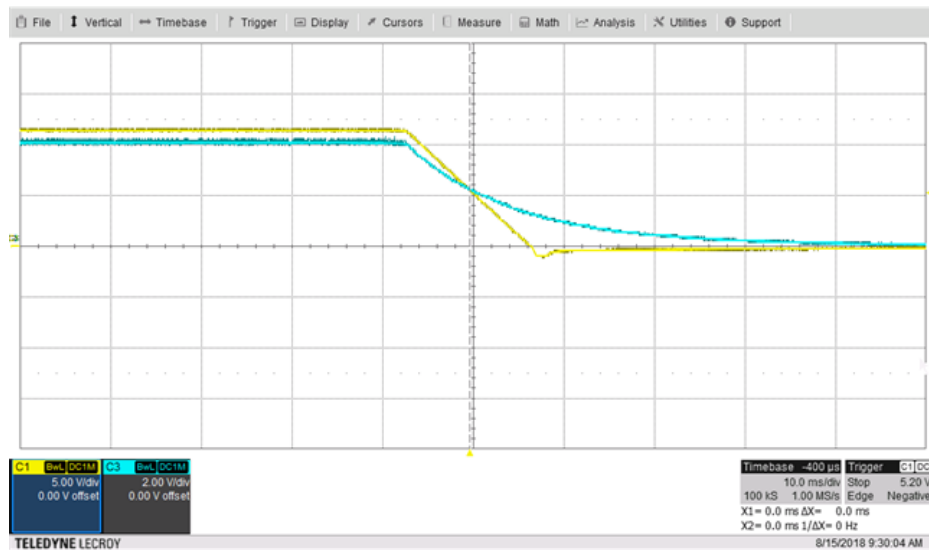


Figure 24. Shutdown With Full Load

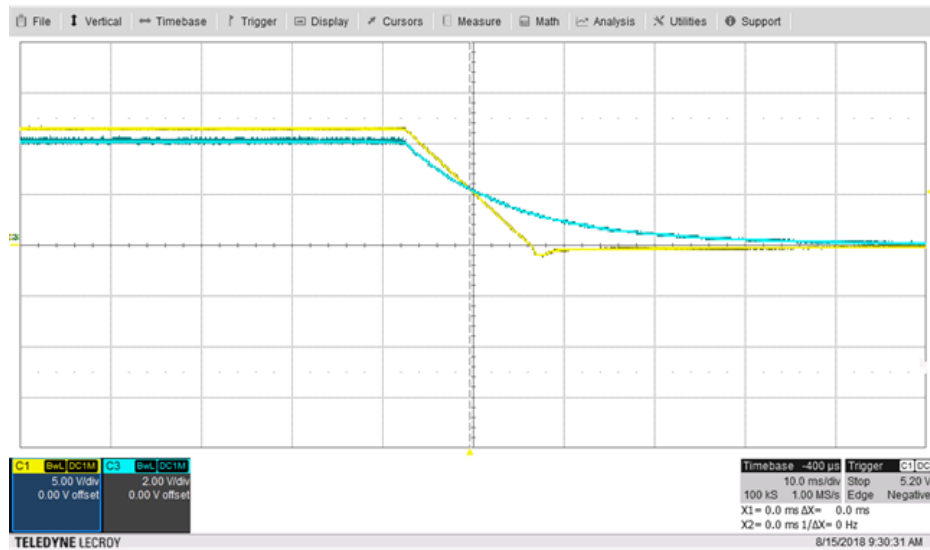


Figure 25. Shutdown With Full Load With Applied Magnetic Field

3.7 Conducted EMI

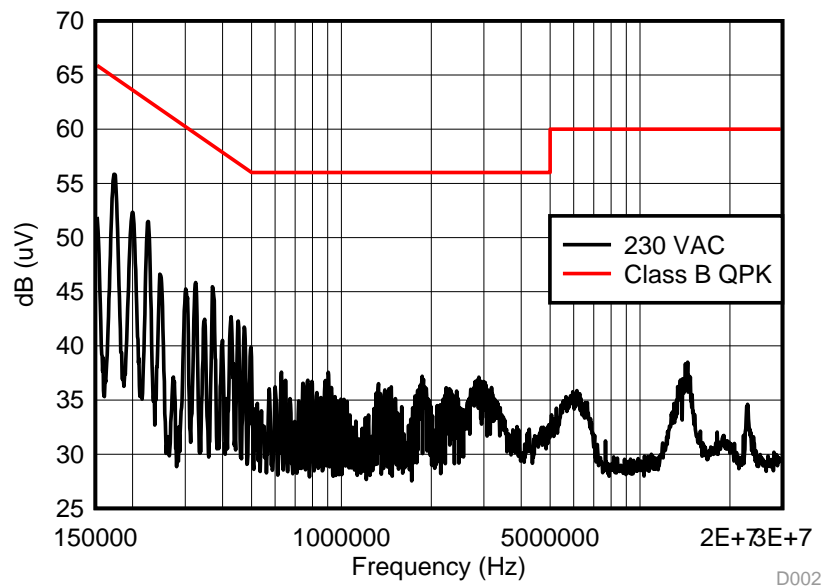


Figure 26. EMI at 230 V_{AC}

Figure 26 shows testing done at 230-V_{AC} input and fully loaded output.

3.8 Short Circuit Recovery

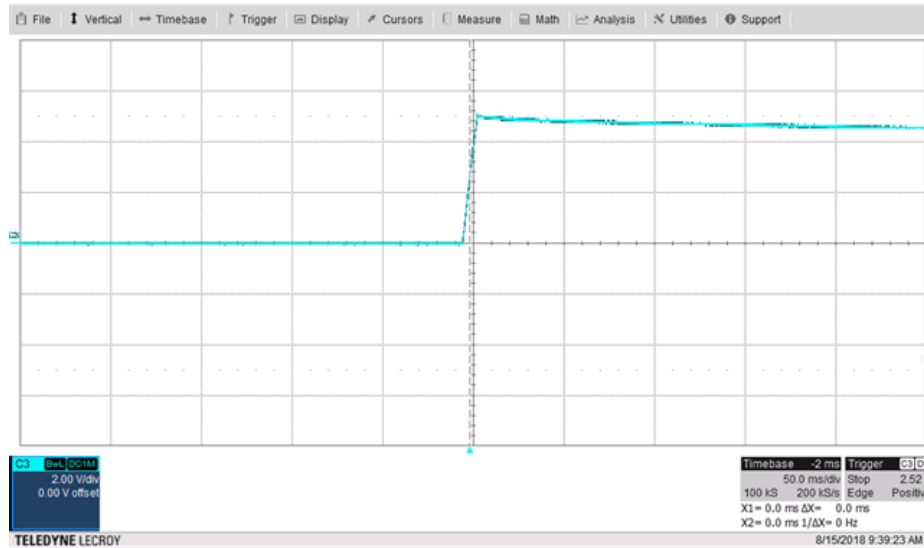


Figure 27. Short Circuit Recovery

Figure 27 shows testing done at 230-V_{AC} input.

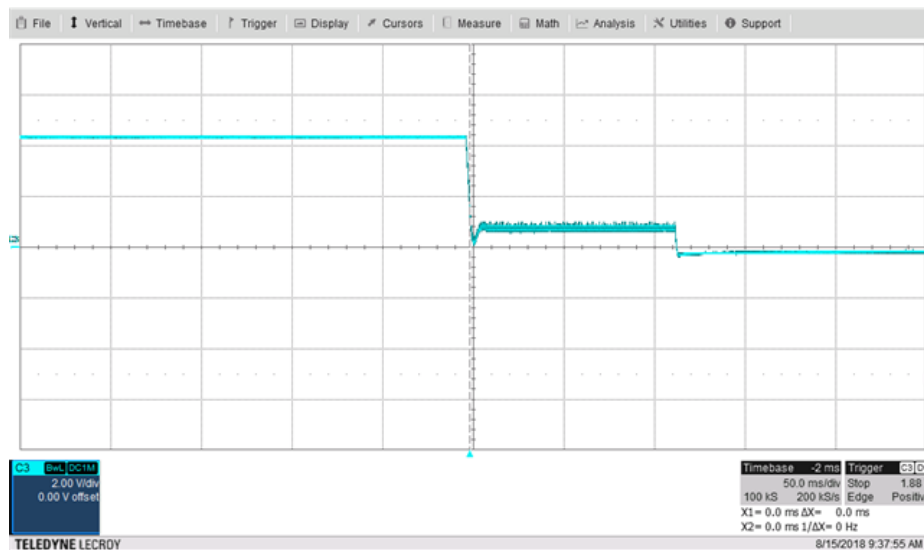


Figure 28. Short Circuit Applied

Figure 28 shows testing done at 230-V_{AC} input.

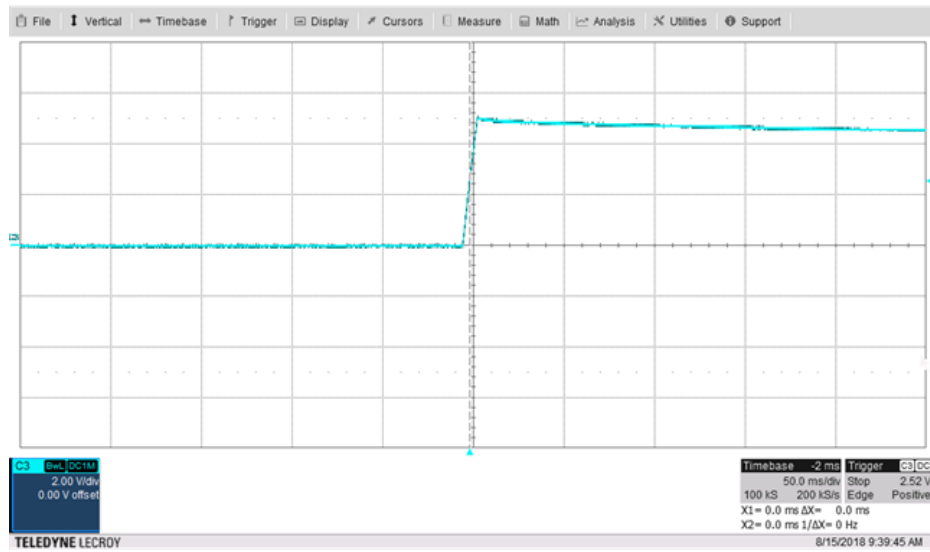


Figure 29. Short Circuit Recovery With Applied Magnetic Field

Figure 29 shows testing done at 230-V_{AC} input.

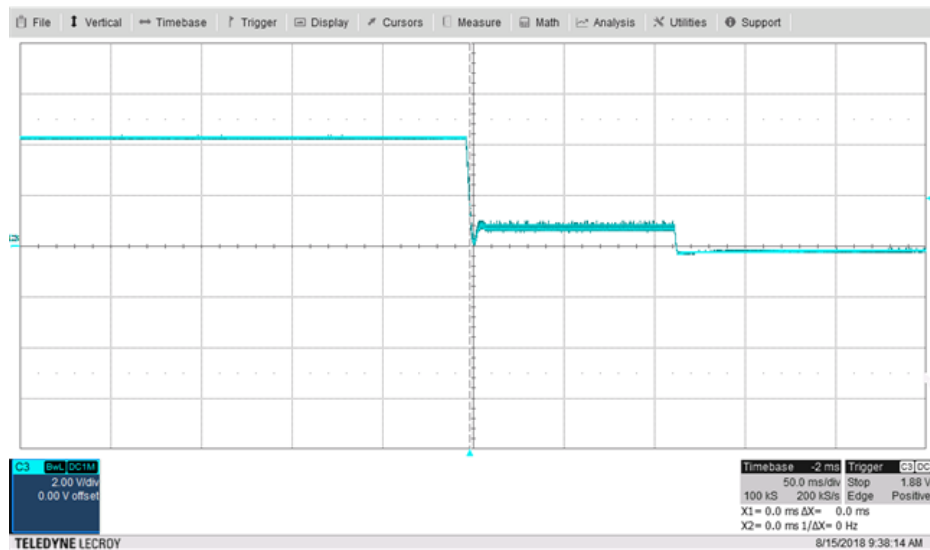


Figure 30. Short Circuit Applied With Applied Magnetic Field

Figure 30 shows testing done at 230-V_{AC} input.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated