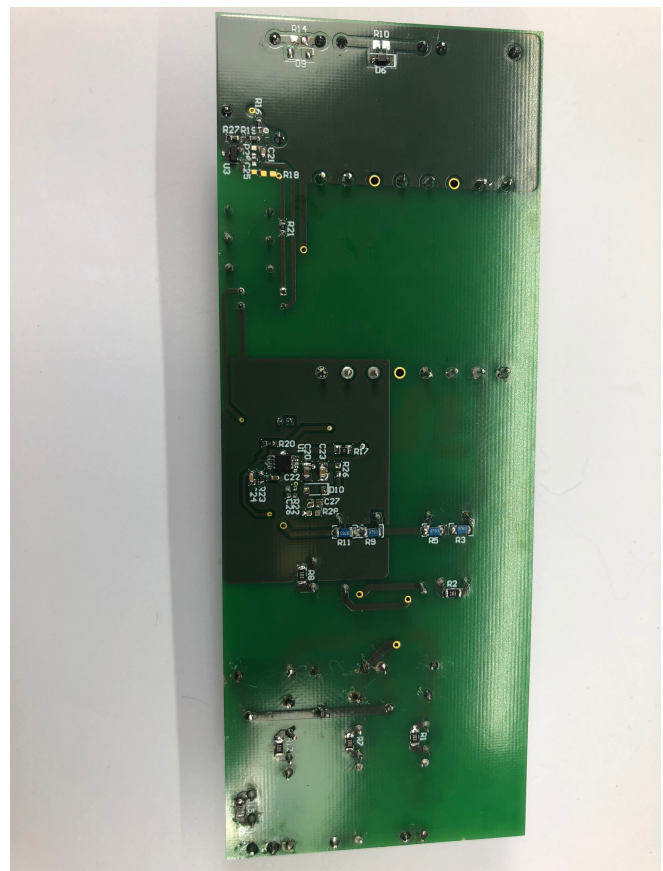


Test Report: PMP30495 58-VAC - 255-VAC 3-Phase Input Multiple Output Flyback Reference Design



Description

The PMP30495 is a power supply reference design with a 3-phase input (58VAC-255VAC [Line-to-Neutral]; 100VAC-440VAC [Line-to-Line]) and multiple isolated outputs (12V@705mA; 12V@733mA; 35V@25mA). The continuous maximum output power is 12.8W. The controller LM5021 operates at a fixed switching frequency of 100kHz. An optional skip cycle mode reduces input power and increases efficiency at light load conditions.



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements


Table 1. Voltage and Current Requirements

| PARAMETER | SPECIFICATIONS |
|-----------------------------|-----------------------------------|
| V_{IN} | 3Phase: 58VAC-255VAC Line-Neutral |
| V_{OUT} | 12V@705VA; 12V@733mA; 35V@25mA |
| Nominal switching frequency | 100kHz |

2 Testing and Results


2.1 Efficiency Graphs

Figure 1. Efficiency vs. Input Voltage

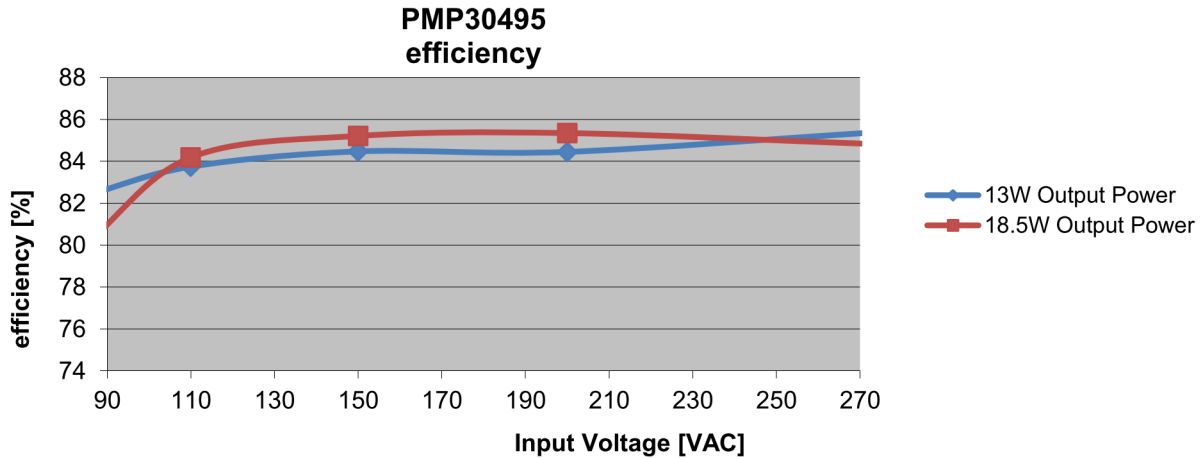


2.2 Load Regulation

Figure 2. Load Regulation regulated output 12Vout1

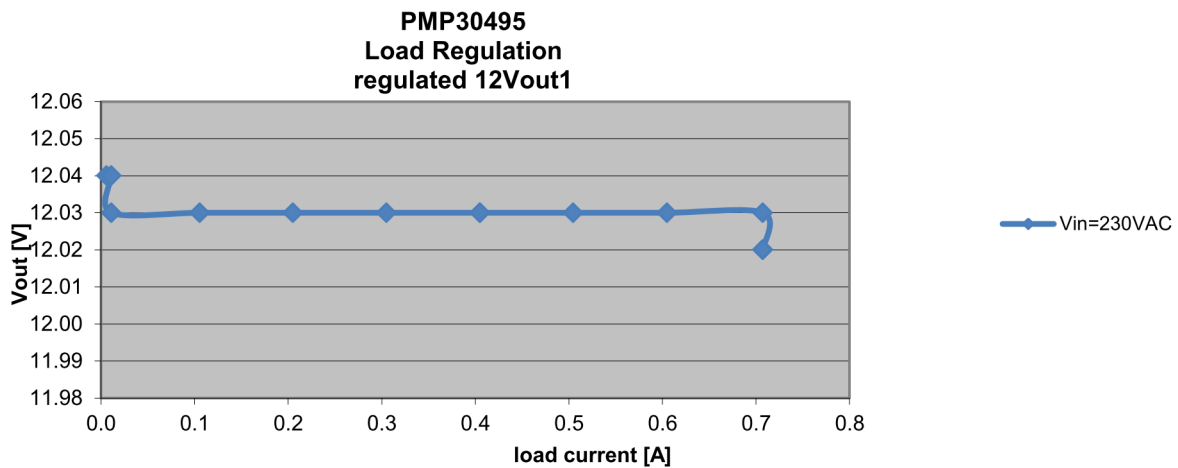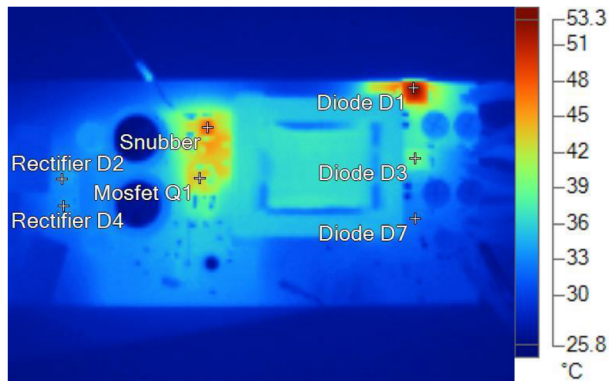


2.3 Thermal Images

The images below show the infrared images taken from the FlexCam after 15min at 13W load output power.

Figure 3. Thermal Image Top View


1360_Vin=230VAC 12V@0.71A 12V@0.24A
35V@25mA Top.is2

| Name | Temperature |
|--------------|-------------|
| Snubber | 48.2°C |
| Diode D1 | 53.3°C |
| Diode D3 | 39.4°C |
| Diode D7 | 32.3°C |
| Mosfet Q1 | 43.8°C |
| Rectifier D2 | 33.8°C |
| Rectifier D4 | 33.5°C |

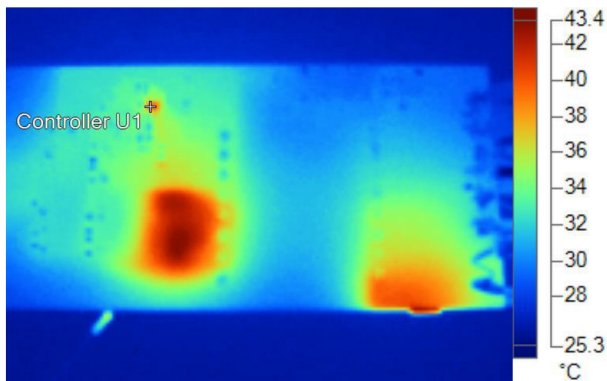Figure 4. Thermal Image Bottom View


1361_Vin=230VAC 12V@0.71A 12V@0.24A
35V@25mA Bottom.is2

| Name | Temperature |
|---------------|-------------|
| Controller U1 | 39.8°C |


2.4 Dimensions

158mm x 61mm

3 Waveforms


3.1 Switching

Figure 5. Switchnode

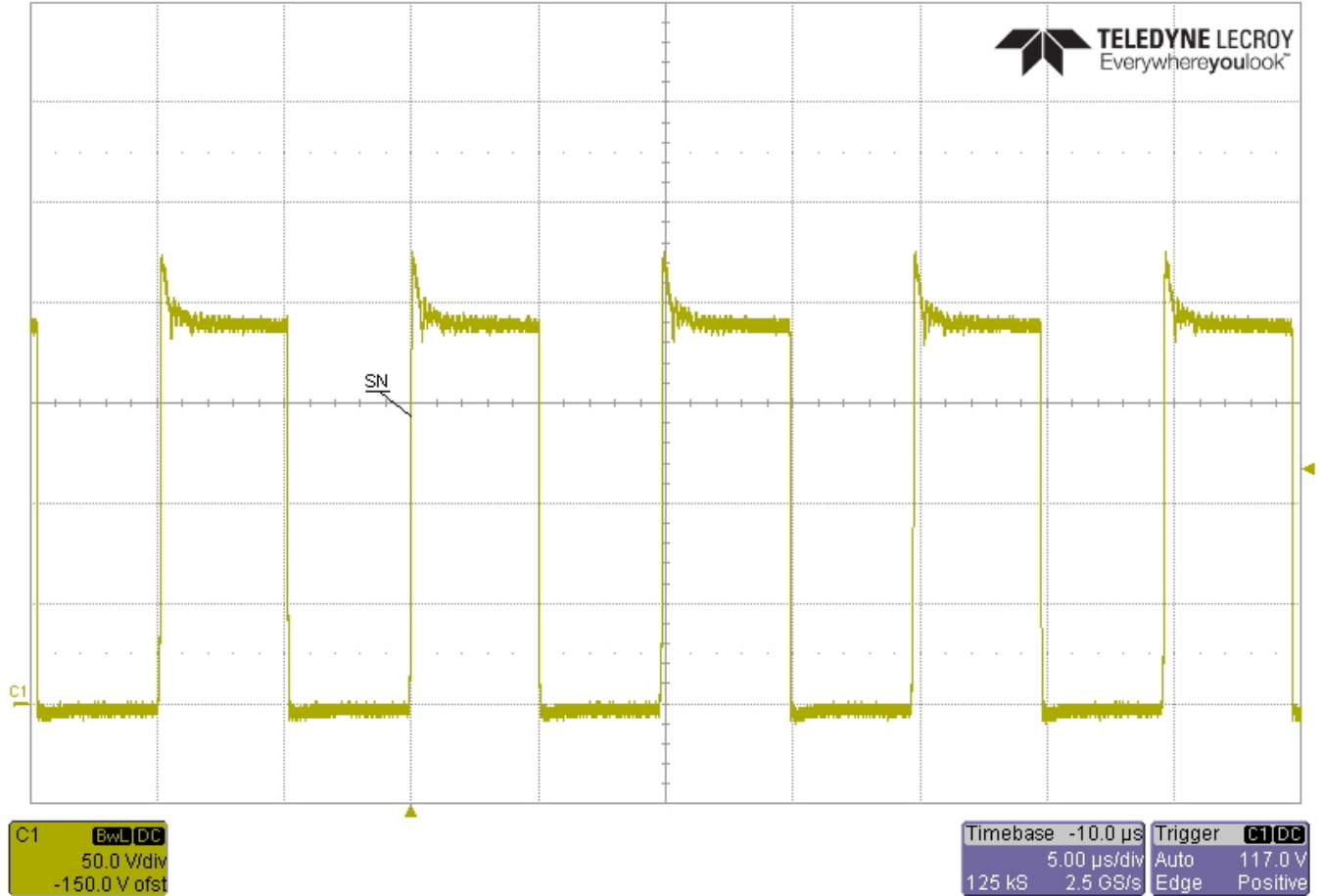


- Input Voltage = 100VDC
- Output Power = 12.8W

Figure 6. Switchnode

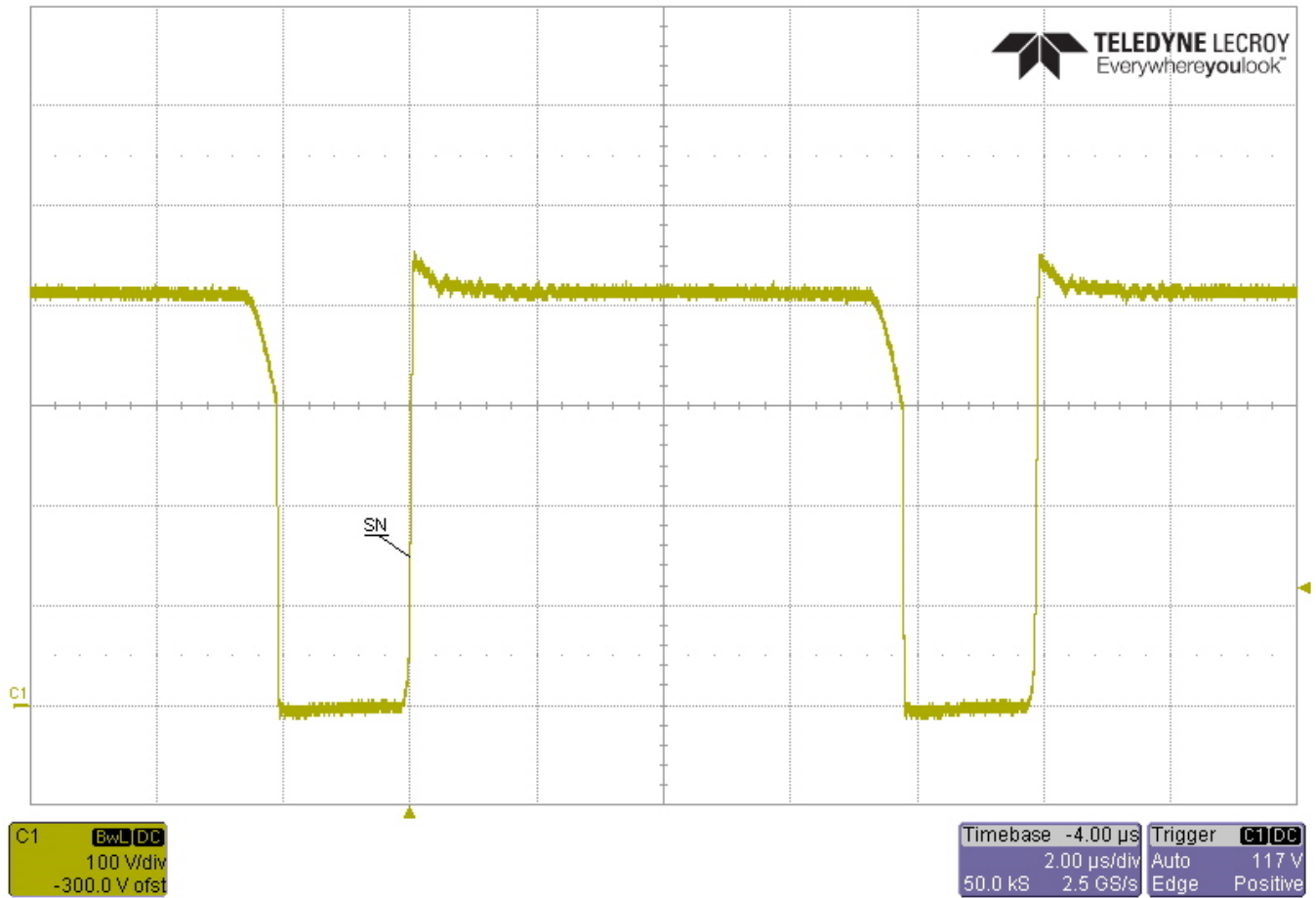

- Input Voltage = 325VDC
- Output Power = 12.8W


Figure 7. Switchnode

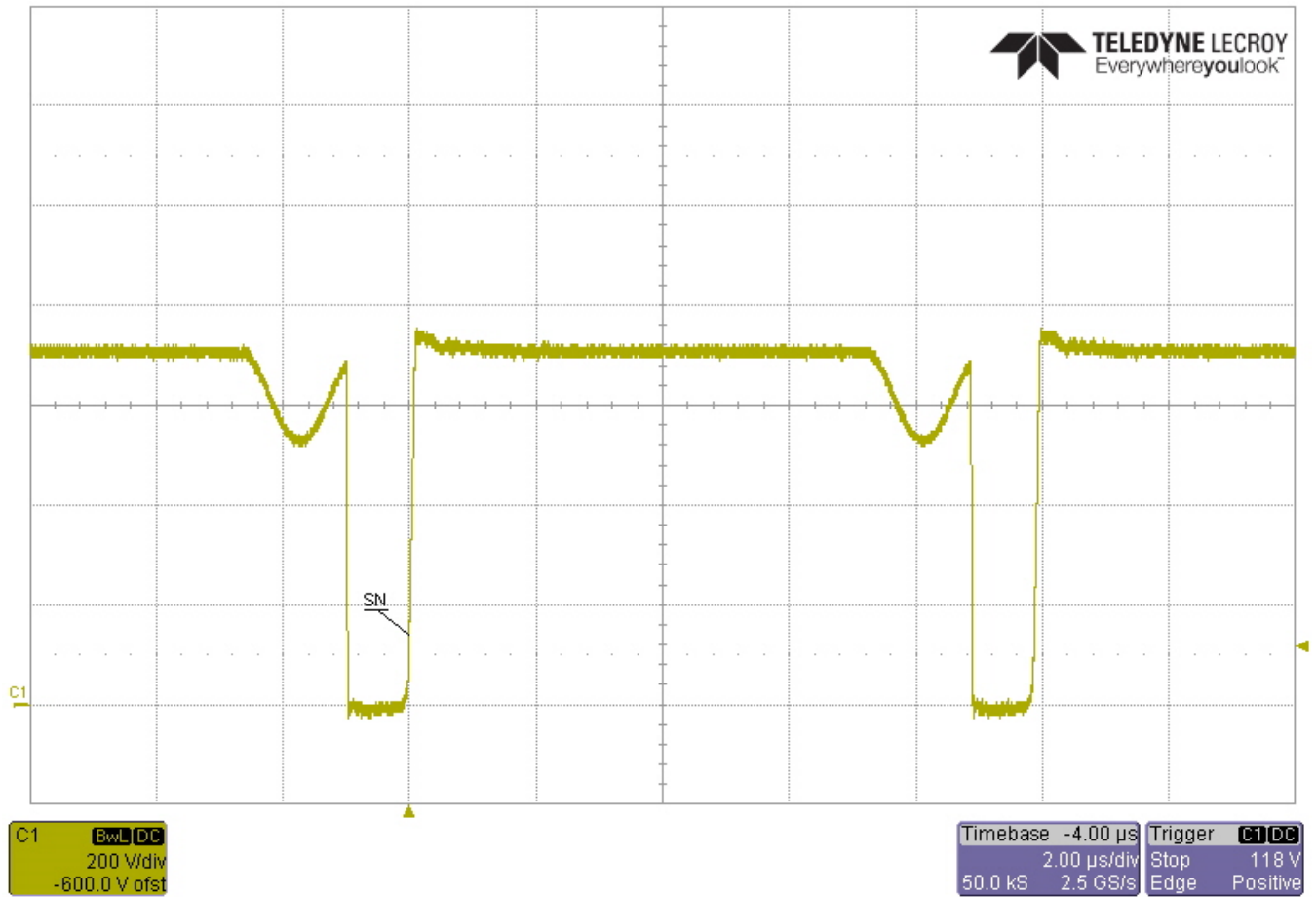

- Input Voltage = 623VDC
- Output Power = 12.8W

3.2 Output Voltage Ripple


Figure 8. Output Ripple

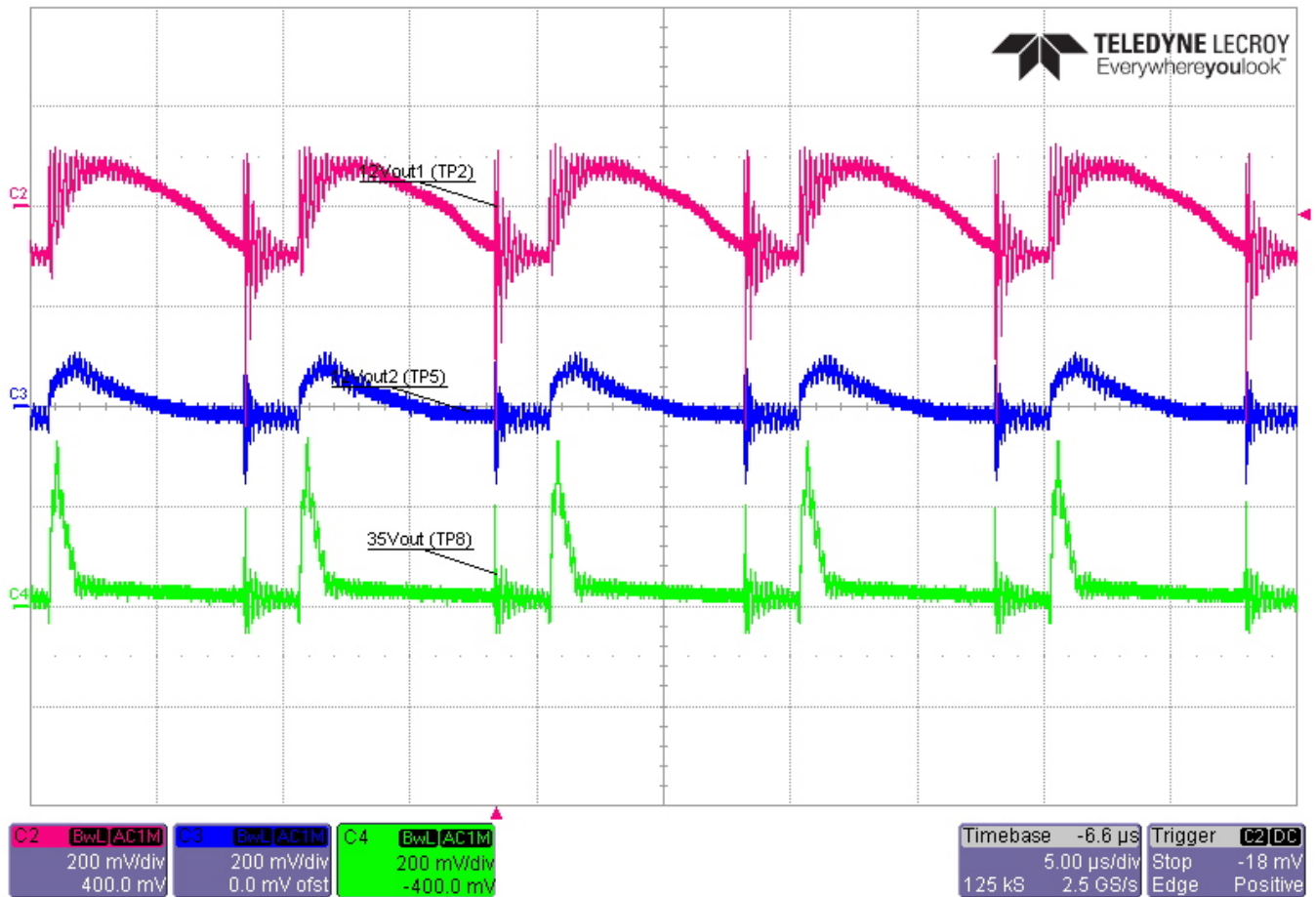

- Input Voltage = 230VAC
- Load Current 12Vout1= 705mA
- Load Current 12Vout2 = 235mA
- Load Current 35Vout = 25mA

3.3 Bode Plot

Figure 9. Total Open Loop

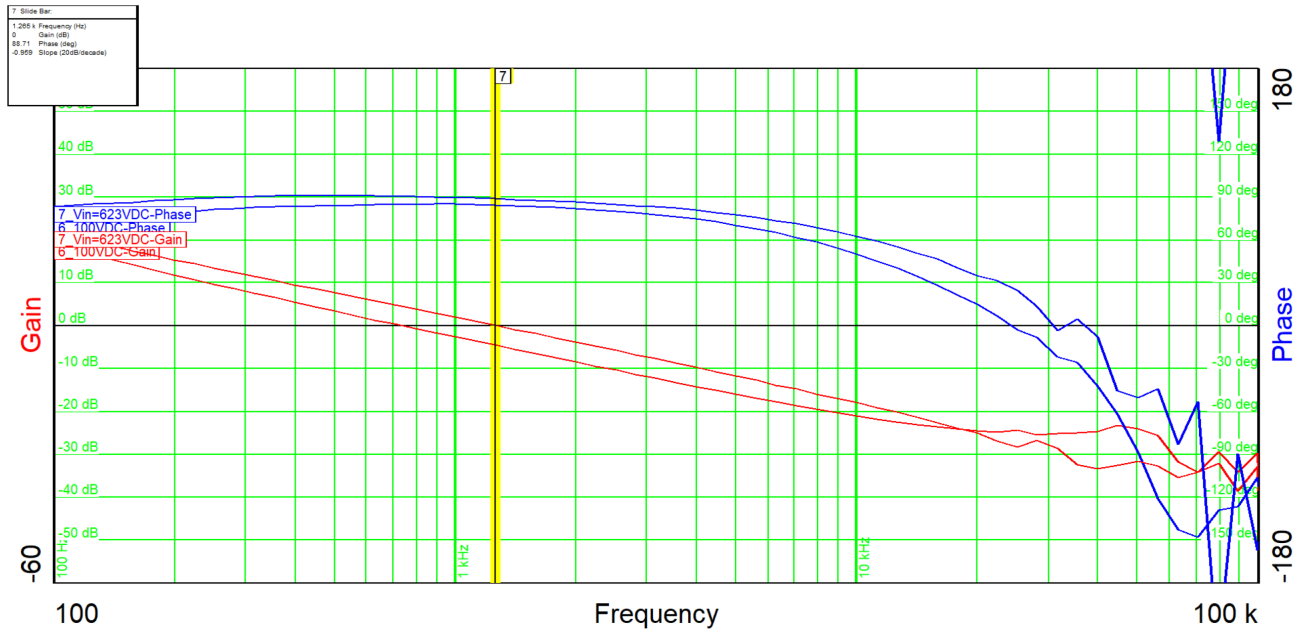

Input Voltage = 100VDC:


- Output Power = 18W
- Bandwidth = 0.7kHz
- Phasemargin = 85°
- Gain Margin > 20dB

Input Voltage = 623VDC:

- Output Power = 18W
- Bandwidth = 1.3kHz
- Phasemargin = 89°
- Gain Margin > 20dB

3.4 Load Transients


Figure 10. Load Step Response Regulated Output 12Vout1

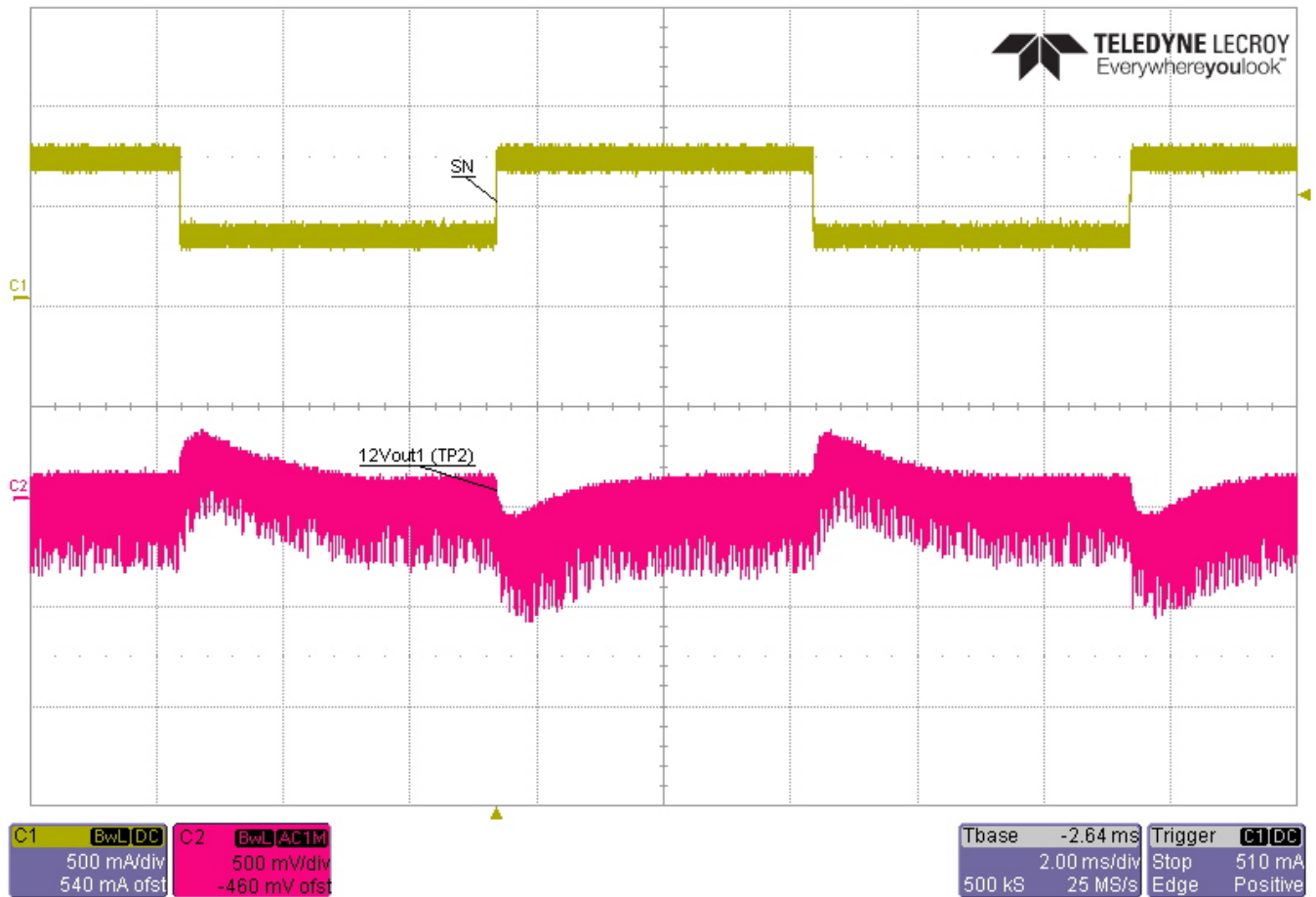

- Input Voltage 230VAC
- Load Current 12Vout1= 300mA - 700mA


3.5 Start-up Sequence

Figure 11. Startup

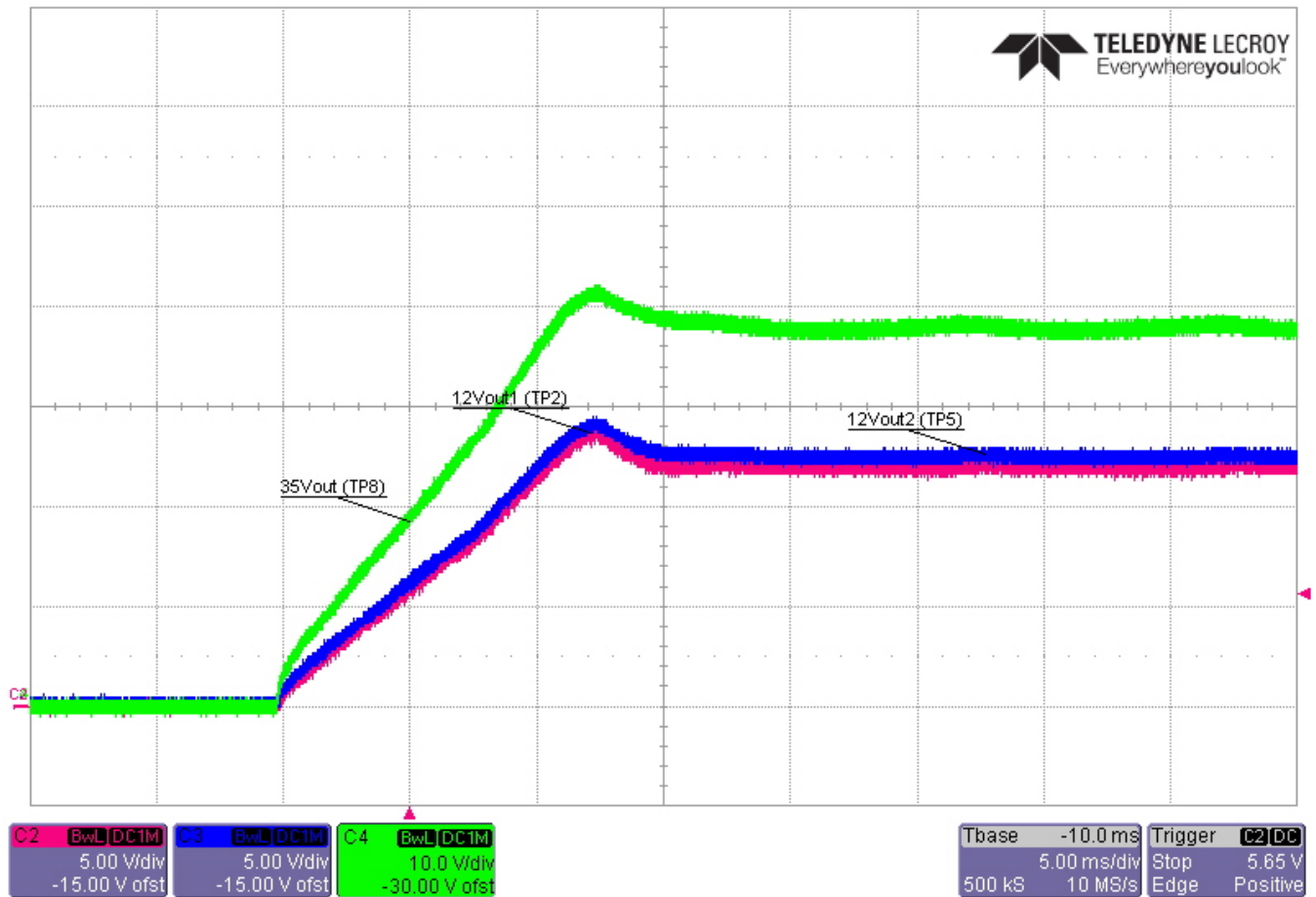


- Input Voltage = 85VAC
- Output Power = 12.8W

Figure 12. Startup

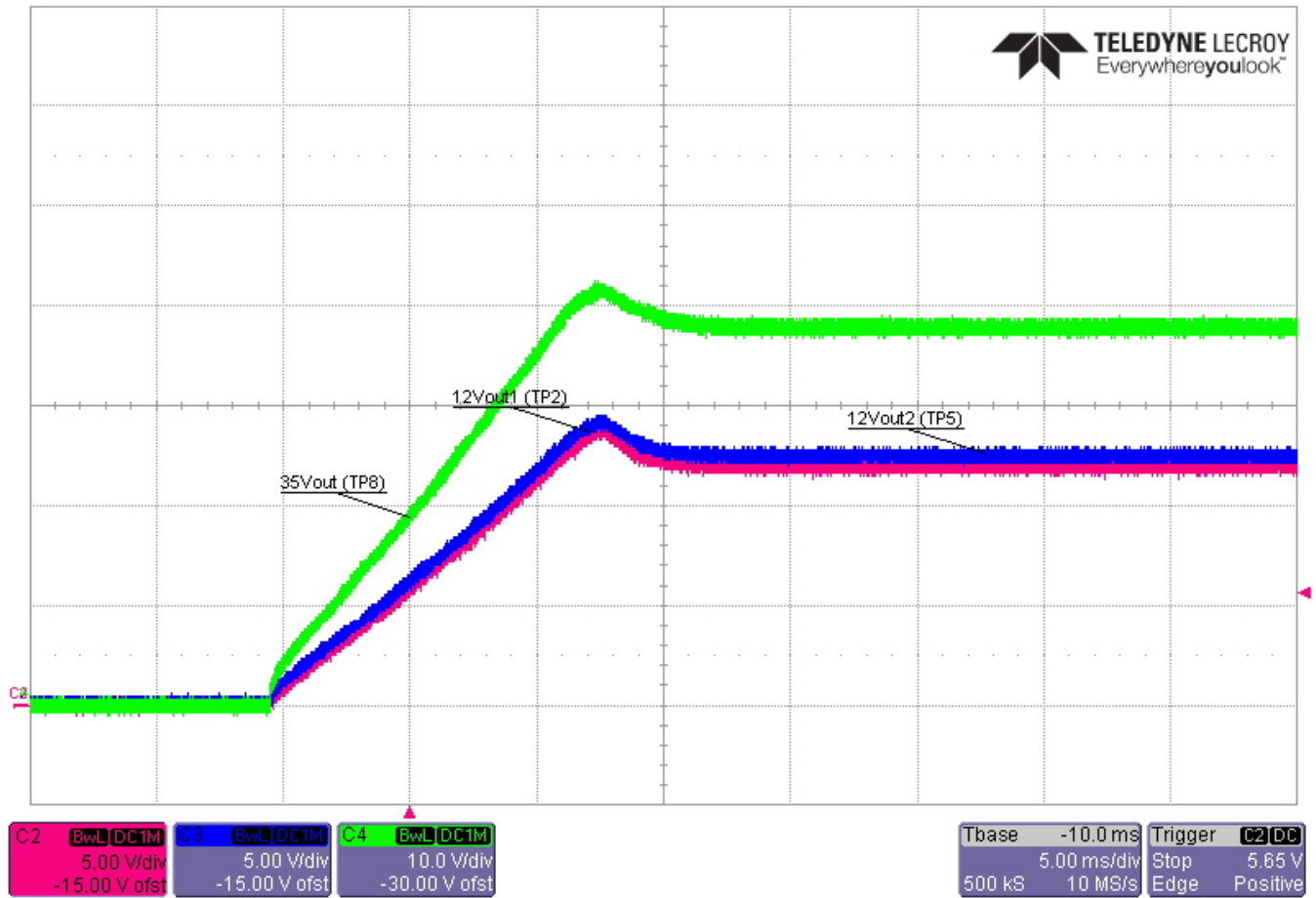

- Input Voltage = 100VDC
- Output Power = 12.8W


Figure 13. Startup

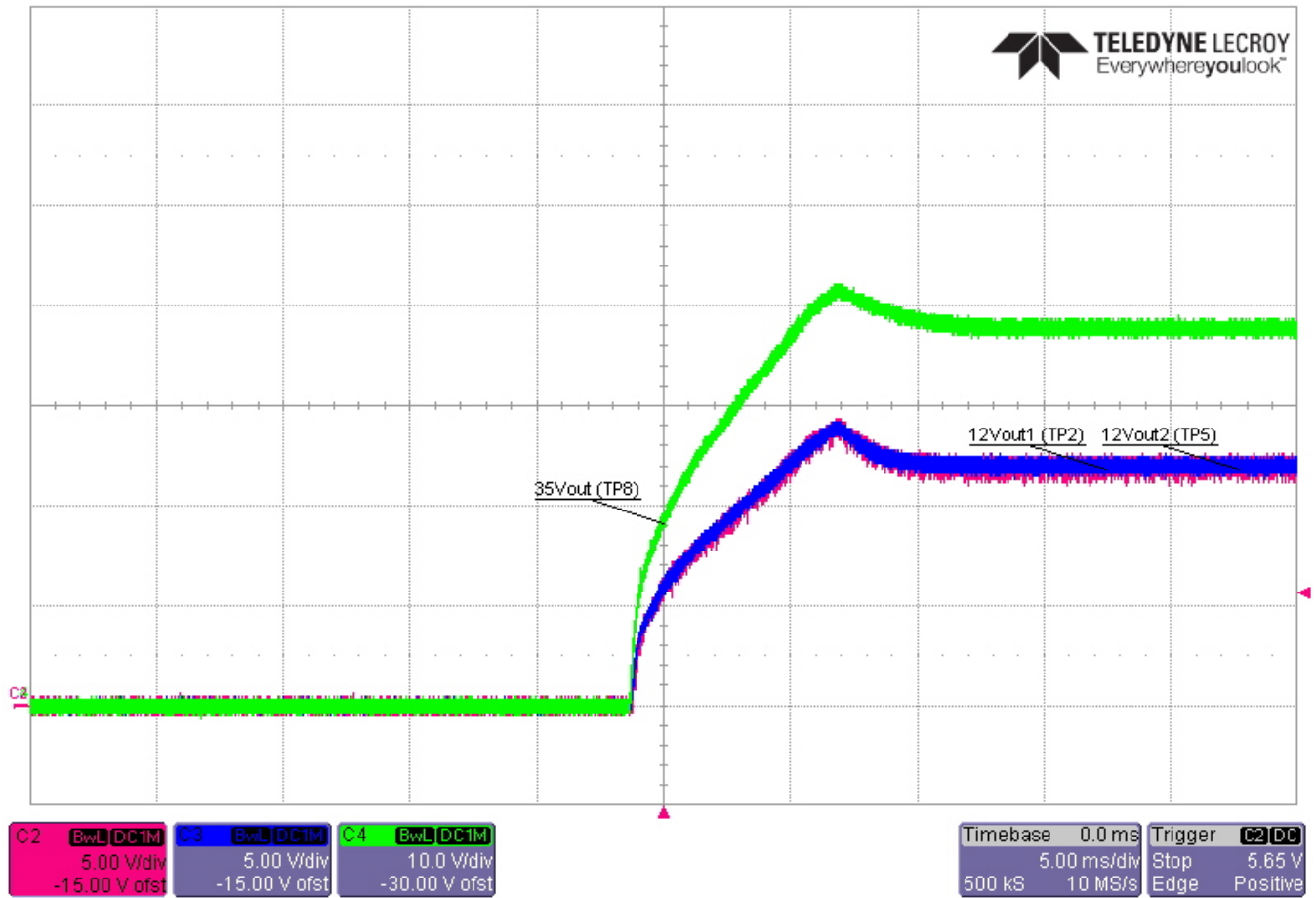

- Input Voltage = 623VDC
- Output Power = 12.8W

3.6 Shutdown


Figure 14. Shutdown

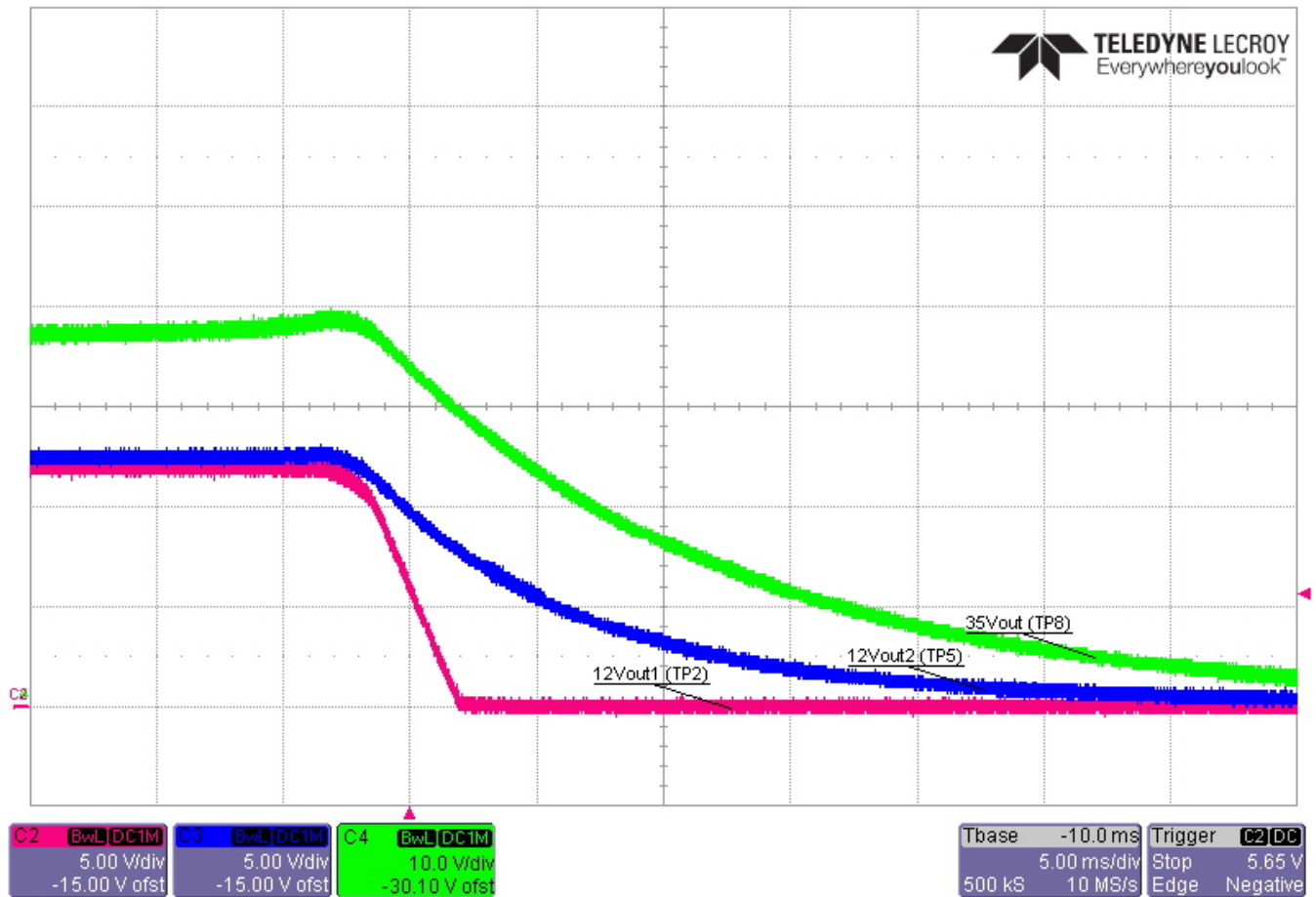

- Input Voltage = 230VAC
- Output Power = 12.8W

3.7 Input Ripple Voltage

Figure 15. Bulk Voltage

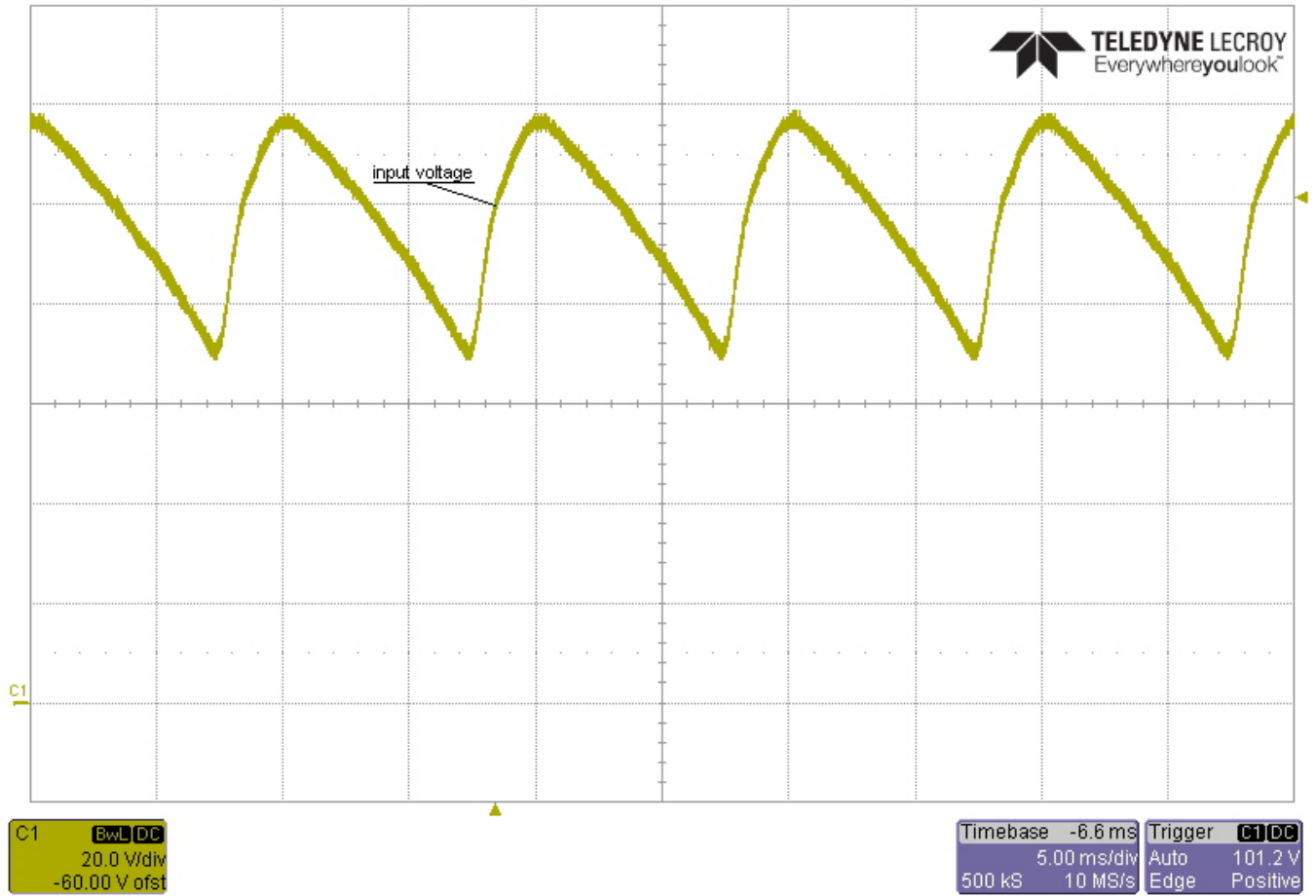

- Input Voltage = 85VAC
- Output Power = 12.8W

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated