


Test Report: PMP30465

30-W SEPIC reference design with extended input voltage range



Description

This reference design is a wide input voltage range SEPIC converter delivering up to 30 W continuous output power; using a cost effective discrete startup circuitry the design is able to be supplied up to 80 V input. Another discrete UVLO circuitry prevents from large input currents at low input voltage. So the power supply is able to handle an input range 1:8. The internal driver of the controller is boosted by a small external push pull stage using bipolar transistors. Using a coupled inductor from stock results in less amount and stress for the flying capacitors. Beside this no additional damping RC network needs to be added here.

 

An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
V_{IN}	10 V-80 V
V_{OUT}	12 V
Nominal switching frequency	200 kHz
Max Output Current	3 A

1.2 Considerations

The switching frequency is about 225 kHz. The circuit switches on at 9.2 V and off at 8.5 V. Unless otherwise mentioned a resistor was used as load. The output current was adjusted to 3A.

2 Testing and Results

2.1 Efficiency Graphs

Figure 1. Efficiency cs Load Current



 


Figure 2. Loss vs Output Current

 

2.2 Load Regulation

Figure 3. Output Voltage vs Output Current

 

2.3 Line Regulation

Figure 4. Output Voltage vs Input Voltage



 


Figure 5. Efficiency and Loss vs Input Voltage

 


2.4 Thermal Images


Figure 6. Thermal Image of 10 V Input Voltage and 3 A Output Voltage

 

Name	Temperature
D6	80.4° C
L1	96.6° C
Q5	85.8° C
R13	85.3° C

 Figure 7. Thermal Image of 45 V Input Voltage and 3 A Output Voltage


Name	Temperature
D6	72.8° C
L1	82.4° C
Q5	75.5° C

 Figure 8. Thermal Image of 45 V Input Voltage and 2 A Output Voltage


Name	Temperature
D6	54.6° C
L1	63.0 °C
Q5	58.5° C

 
 
Figure 9. Thermal Image of 45 V Input Voltage and 1 A Output Voltage


Figure 10. Thermal Image of 80 V Input Voltage and 3 A Output Voltage




Name	Temperature
D6	82.8° C
L1	91.1° C
Q5	92.8° C

3 Waveforms

3.1 Switch Node Q5


Waveform below shows the switch node voltage measured at 45 V input voltage from Q5 drain to GND

Figure 11. Switchnode at 45 V Input Voltage

 

20 V/div (full bandwidth)

1 μ s/div

 


20V/div; 50ns/ major div

3.2 Q5 Gate


The waveform below shows the voltage measured from Q5 gate to GND

Figure 12. Gate at 45 V Input Voltage

 


2 V/div (full bandwidth); 1 μ s/Div

 Below is the same waveform with a different time axis.



100 ns/div

 Below is the same waveform with a different time axis.




50 ns/div

3.3 Diode D6


The waveform below are showing the voltage at the diode D6 referenced to VOUT.

Figure 13. Diode D6 with 45 V Input Voltage

 


20 V/div (full bandwidth); 1 μ s/div

 Below there is the same waveform with a different time axis.



100 ns/div

 Below there is the same waveform with different time axis.



50ns/div

3.4 Output Voltage Ripple

Below are the waveforms at VOUT at different input voltages. Also the effect of an added 100nF capacitor is shown.

All measurements were done with 20 MHz bandwidth.

3.4.1 10 V Input Voltage

Figure 14. VOUT at 10 V Input Voltage


 


Figure 15. VOUT at 10 V Input Voltage and a Added 100nF Capacitor at VOUT

 

200mV/div (AC, 20MHz bandwidth setting)

2μs/div

3.4.2 45V Input Voltage

Figure 16. VOUT at 45 V Input Voltage


 


Figure 17. VOUT at 45 V Input Voltage and a Added 100nF Capacitor at VOUT

 

3.4.3 80 V Input Voltage

Figure 18. VOUT at 80 V Input Voltage


 



Figure 19. VOUT at 80 V Input Voltage and a Added 100 nF Capacitor at VOUT

 

3.5 Input Voltage

Measured with 20MHz bandwidth (AC)

Figure 20. VIN at 10 V, 45 V and 80 V Input Voltage

 

channel 1 (red) 10 V input voltage -> 200mV/div; 2µs/div
 channel 2 (blue) 45 V input voltage -> 200mV/div; 2µs/div
 channel 3 (dark red) 80 V input voltage -> 200mV/div; 2µs/div

3.6 Bode Plot

Figure 21. Loop Response @ 10 V Input Voltage


 


Figure 22. Loop Response @ 45 V Input Voltage

 


Vin	10 V	45 V
Bandwidth (kHz)	2.5	3.9
Phase Margin	70	83
slope (20dB/decade)	0.95	0.99
gain margin (dB)	-11.1	-22.7
slope (20 dB/decade)	-0.58	-1.2
freq (kHz)	16	49

3.7 Load Transients

The electronic load was switching from 1.5 A to 3 A with a frequency of 150 Hz.


Figure 23. Transient @ 10V Input Voltage

 

channel 1: Output Voltage (10 kHz bandwidth) -> 100mV/div; 1ms/div

channel 2: Output Current (20 MHz bandwidth) -> 1A/div; 1ms/div


Figure 24. Transient @ 45 V Input Voltage

 

channel 1: Output Voltage (10kHz bandwidth) -> 100mV/div; 1ms/div

channel 2: Output Current (20MHz bandwidth) -> 1A/div; 1ms/div

Figure 25. Transient @ 80 V Input Voltage

 


channel 1: Output Voltage (10 kHz bandwidth) -> 100mV/div; 1ms/div
 channel 2: Output Current (20 MHz bandwidth) -> 1A/div; 1ms/div

3.8 Start-up Sequence

The power supply was switched on.

Figure 26. Start-up @ 45V Input Voltage

 


channel 1: input voltage -> 10 V/div; 0.1s

channel 2: output voltage -> 5 V/div;0.1s

3.9 Shut-down

The power supply was switched off.

Figure 27. Shut-down @ 45 V Input Voltage

 


channel 1: input voltage -> 10V/div; 4ms/div

channel 2: output voltage -> 5V/div ; 4ms/div

4 Addendum

For improving the EMI behaviour did following modifications

 - improved GND-connection of the gate-driver circuit
- changed gate resistor from 10R to 33.2R (R11)
- added snubber to rectifier (D6)
- added MLCCs to VOUT



The following subsections are some details.


4.1 Gate Resistor

The following measurements were done with 20 V input voltage

4.1.1 Gate Resistor = 10R

The following picture shows the waveform before any modification

Figure 28. Gate to GND with R11=10R

 


2V /div (full bandwidth)

50ns/div


4.1.2 Gate Resistor = 33.2R

Below there is the waveform with 33.2R gate resistor with the same settings as above.

Figure 29. Gate to GND with R11=33.2R

 

Measured from Gate to source is shown in following picture (same settings as above).

 Figure 30. Gate to Source with R11=33.2R


4.2 Rectifier


After changing the gate resistor a snubber 10R + 470 pF was added.

The following picture are measured at the rectifier D6 (referenced to VOUT) with following settings.

- 10V/div (full bandwidth)
- 50ns/div


4.2.1 No Snubber

Figure 31. Diode D6 without Snubber @ 45 V Input Voltage

 

4.2.2 With Snubber 10R + 470 pF


Figure 32. Diode D6 with Snubber @ 45 V Input Voltage

 

4.3 Output Voltage

For further improvements of the VOUT-ripple additional MLCC capacitors were added to VOUT . The following waveforms are showing VOUT without and with rectifier snubber and with additional MLCC capacitors (1 μ F, 100 nF and 10 nF soldered on bottom side of the pcb).

Figure 33. VOUT at 45 V Input Voltage

 

channel 1: without snubber -> 200 mV/div (20MHz bandwidth); 2 μ s/div

channel 2: with snubber -> 200 mV/div (20MHz bandwidth); 2 μ s/div

channel3: with snubber and added caps -> 200 mV/div (20 MHz bandwidth); 2 μ s/div

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated