


Test Report: PMP30600-TH

20-A Automotive Pre-Regulator Reference Design With Extended Input Voltage Range for Trucks



Description

This reference design is a 100 W synchronous buck converter primarily to supply automotive loads. The IC is LM5146-Q1 in fixed frequency operation at 100 kHz to ensure low noise operation. To minimize conducted emissions an input filter prevents from reflected ripple. Furthermore a RC snubber attenuates noise in the RF band to reduce radiated emissions. To reduce system EMI the design is prepared either to synchronize other converters (output) or just to be externally synchronized (input). The power stage itself withstands surge voltages up to 75Vpk.

 

An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
Input Voltage Range	10 V to 36 V (75 V surge)
Output Voltage	5 V
Maximum Output Current	20 A
Calculated Switching Frequency	100 kHz

1.2 Considerations*

The circuit is built on PCB PMP30600RevA.

2 Testing and Results

2.1 Efficiency Graphs

The efficiency is shown in the Figure 1 below. The input voltage was set to 28V


 


Figure 1

Full load efficiency 94.32%, calculated 94.8%;
Deviation by self heating of inductor and switching losses

Maximum efficiency 96.01% at 7.5A.

 Efficiency $\geq 94\%$ in a range 2.5A to 20A, so 12.5% load to 100% load



2.2 Load Regulation

The load regulation of the output is shown in the Figure 2 below. The input voltage was set to 28V.

 



Figure 2

Min. Vout 5.039V, max Vout 5.045V,

Output voltage variation 6.0mV, so 0.12%, negligible.

 
2.3 Thermal Images

Thermal image at 28V input and full load 20Amp after 30 minutes continuous operation [Rt = 25c]:



Name	Temperature		
	10A	15A	20A
Q1	47.0°C	63.1°C	84.7°C
Q2	47.1°C	63.4°C	84.4°C
Q3	45.8°C	61.3°C	82.7°C
Q4	45.5°C	59.6°C	80.7°C
L1	39.8°C	49.0°C	60.5°C
L2	44.9°C	57.6°C	75.5°C

 Temperature rise is below 50K, a proper design of the power stage with maximum efficiency results in relaxed thermal stress because inductor and MOSFETs are almost same temperature; good balance.



Filter inductor and RC snubber have been placed externally

2.4 Dimensions

The extensions of the board are 79 mm x 62 mm.

3 Waveforms

3.1 Switching

3.1.1 Low Side FET

With input voltage set to 28V and 20A lout results in the waveform shown in Figure 3


 



Figure 3

Maximum input voltage is 39V and the overshoot is around 11V.
 Vds rating of BSC117N08NS5 and BSC061N08NS5 are 80V – enough margins.
 RC snubber circuit was implemented to demonstrate RF suppression:

 
Measure ringing frequency at switch node w/ RF probe (no GND leads, use GND clip), here 80MHz – could cause trouble , radiated emissions:



 - 1) **add capacitor from switch node to GND to achieve half of the prior frequency,** here 0.68nF
- 2) **add resistor in series to achieve half of the prior overshoot,** here 3.3Ω reduced overshoot from 11V to 7V:



 Clamping network 0.68nF / 3.3 Ohm reduces RF content at the switch node, less EMI !



By experience could be said that a drop in efficiency from 0.2% to 0.5% is typically caused by adding the RC snubber circuit. For a middle power design like PMP30600 geometry 1206 or 1210 might fit, but for high power designs be aware of losses up to 500mW:

- 0603 <100mW
- 0805 <150mW
- 1206 <200mW
- 1210 <250mW
- 1812 <500mW
- 2010 <750mW
- 2512 <1W

3.1.2 High Side FET Source - Drain (referenced to VIN)

With input voltage set to 24V and 20A Iout results in the waveform shown in Figure 1

 


Figure 4

3.1.3 Gate to Source of MOS-FET (High-Side)

With input voltage set to 28V and 20A Iout results in the waveform shown in Figure 3.

 


Figure 5 High side

3.1.4 Gate to Source of MOS-FET (Low-Side)

With input voltage set to 28V and 20A Iout results in the waveform shown in Figure 6.

 


Figure 6 Low side

3.2 Output Voltage Ripple

The output ripple voltage is shown in Figure 7. The image was taken with 20A load 28V at the input. The output ripple voltage is roughly 50mV.

 


Figure 7

3.3 Input Ripple Voltage

The input ripple voltage is shown in Figure 8. This was taken with 20A full load 28V at the input.


 
 


Figure 8

Input voltage ripple is around 3.5V.

Reflected ripple = conducted emissions, EMI

 
Finally the input voltage by using PI filter 47uF – 1uH – 5x 4.7uF;
 A small ceramic capacitor 100nF was added to the electrolytic to suppress glitches:



Input voltage is reduced to 200mV; reduction rate is 1/17.
 A tremendous reduction of reflected ripple resulted in better EMI behavior !
 The inductor prevents the source from seeing the pulse currents – less conducted emissions.

 3.4 Bode Plot

Figures below shows the loop response with 20A load and 28V input – $f_{co}=20\text{kHz}$



The crossover frequency 20kHz fits exactly to the first calculation by hand, the phase margin is more than 60 degrees. Slope at crossover is close to -1.

REMEMBER:

This analysis is a small signal analysis, shows the small signal behavior of the power supply.

The only true analysis is a large signal analysis, the system response on a load transient!

3.5 Load Transients

The Figure 9 shows the response to load transients. The load is switching from 10A to 20A. The input voltage was set to 28V

 


Figure 9

The voltage drop caused by 10A is around 150mV, so around 3% of the output voltage 5V; The combination output capacitor to loop bandwidth matches.

A proper calculation of the error amplifier compensation results in a stable design. For series production a phase margin >60 degrees and a gain margin <-15dB is recommended.

3.6 Start-up Sequence

The startup waveform is shown in the Figure 10. The input voltage was set at 24 V, with 20 A load at the output. The power supply was connected.

 


Figure 10

3.7 Shutdown Sequence

The shutdown waveform is shown in the Figure 11. The input voltage was set at 24 V, with 20 A load at the output. The power supply was disconnected.

 


Figure 11

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated