

# Half-Bridge LLC Dual-Output Bias-Supply Pair Reference Design



## Description


This reference design uses a single UCC25800-Q1 to drive two LLC transformers. Each isolated output feeds into a TPS7A39 dual-channel positive and negative output LDO. PMP23124 can be used to bias two wide band gap FETs that require a positive and negative voltage to drive. Each output can be loaded to 2.8 W.

## Features

- Combined PD and PWM controller
- Primary side regulation (no optocoupler)
- Input power limiting
- Converters can be paralleled for increased power
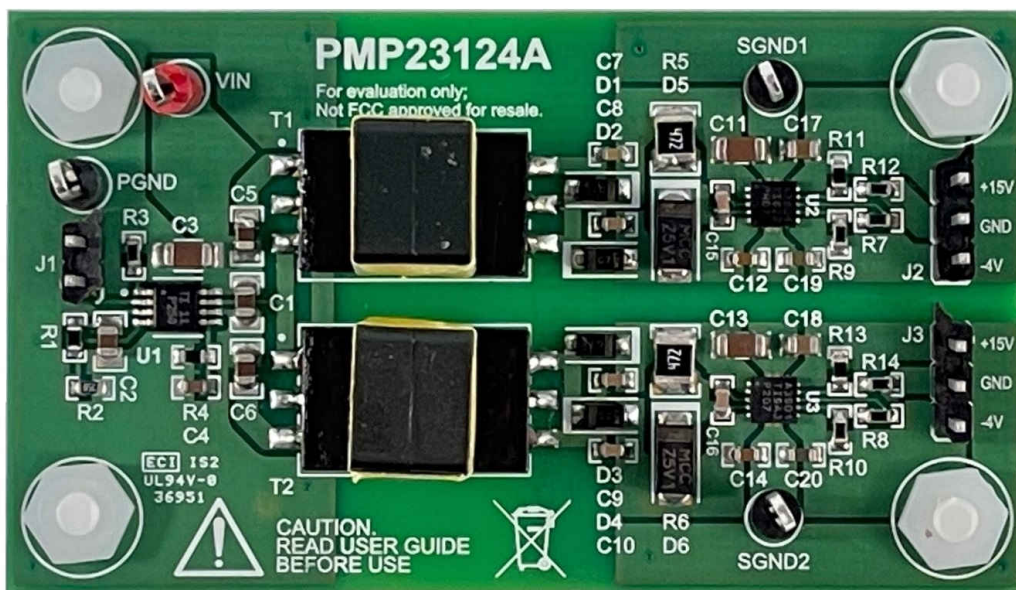
## Applications

- IP network camera
- WLAN, Wi-Fi® access point



Top Photo

## 1 Test Prerequisites

### 1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

Parameter	Specifications
Input Voltage	+15-V input, $\pm 5\%$
Output Voltage	+15 V, -4-V split rail outputs
Max Current	150 mA

### 1.2 Required Equipment

- AC Power Supply
- Electronic Load
- AC Power Meter
- Digital Multimeter
- Oscilloscope

### 1.3 Considerations

- A resistive load connected between the positive and negative outputs was used for all tests
- Unless noted, all waveforms were captured at full load with a 12- $V_{DC}$  input

### 1.4 Dimensions

The PCB is a two-layer, 1-oz per layer design. The dimensions are 1.5 in  $\times$  2.625 in with a maximum component height of 0.35 in.


### 1.5 Test Setup

- DC source capable of 25 V, 1 A
- Resistive loads rated for at least 1 W


## 2 Testing and Results

### 2.1 Load Regulation Graphs

Figure 2-1 and Figure 2-2 show the respective positive and negative voltage regulation graphs.

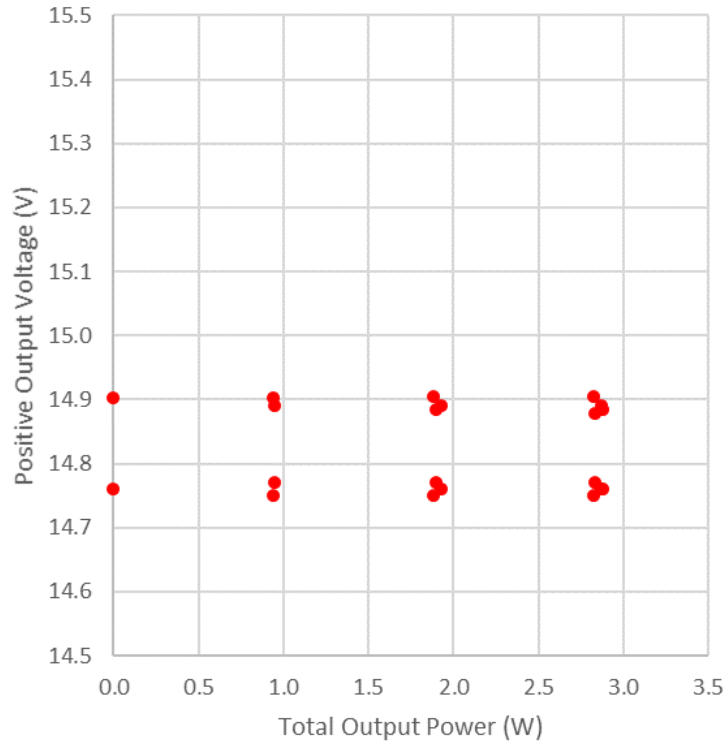

**Figure 2-1. Positive Voltage Regulation**

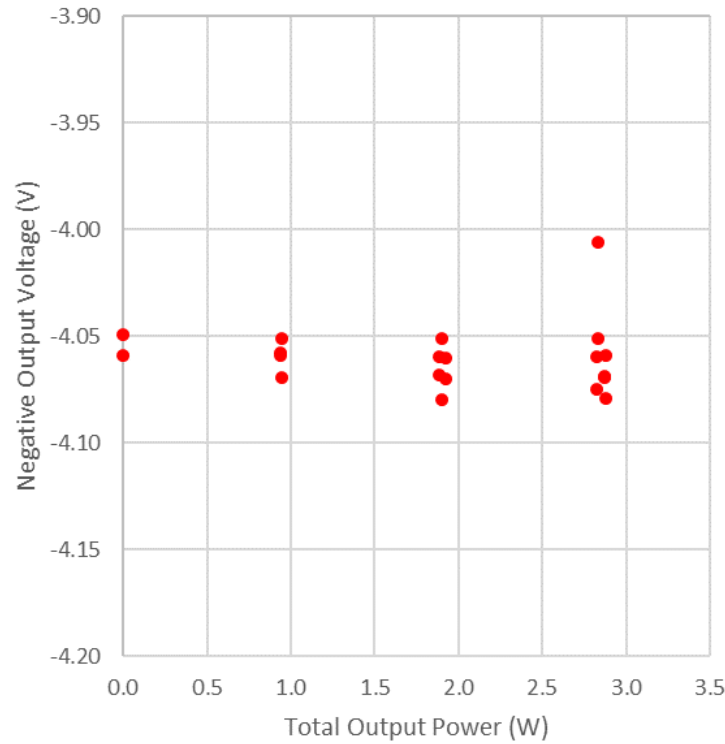

**Figure 2-2. Negative Voltage Regulation**

## 2.2 Efficiency Graphs

Figure 2-3 shows the efficiency graph.

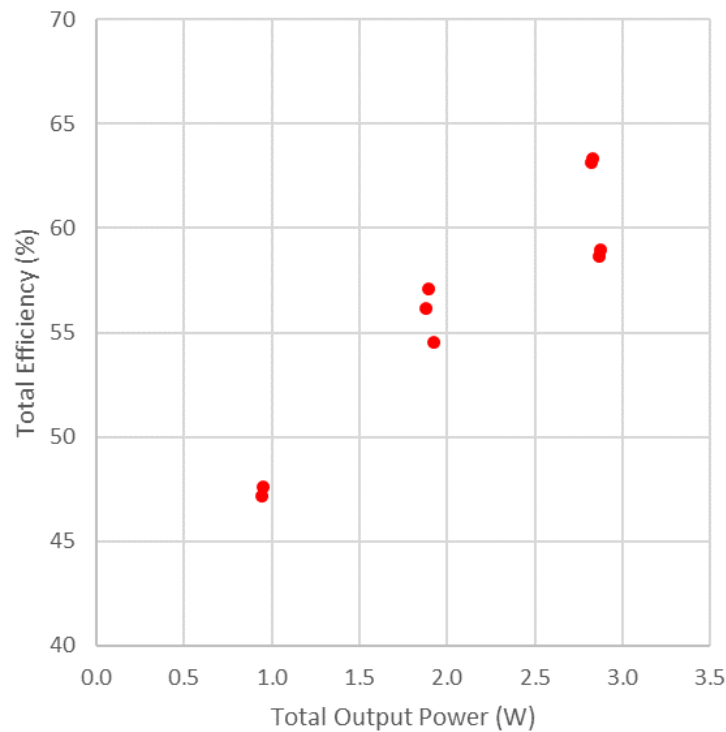


Figure 2-3. Efficiency Graph

## 2.3 Efficiency Data

Efficiency data is shown in the following table.

Table 2-1. Efficiency Data

Input Voltage Setting	Positive Output 1 Voltage (V)	Negative Output 1 Voltage (V)	Output 1 Current (mA)	Output 1 Power (W)	Positive Output 2 Voltage (V)	Negative Output 2 Voltage (V)	Output 2 Current (mA)	Total Output Power (W)	Input Power (W)	Efficiency (%)	Power Loss (W)
15 V <sub>DC</sub>	14.76	-4.049	0	0	14.90	-4.059	0	0	0.525	0	0.525
	14.75	-4.058	50	0.94	14.90	-4.059	0	0	1.993	47.194	1.052
	14.75	-4.068	100	1.882	14.90	-4.059	0	0	3.353	56.129	1.471
	14.75	-4.075	150	2.824	14.90	-4.060	0	0	4.472	63.149	1.648
	14.77	-4.051	0	0	14.89	-4.069	50	0.948	1.993	47.577	1.045
	14.77	-4.051	0	0	14.89	-4.080	100	1.896	3.323	57.073	1.426
	14.77	-4.051	0	0	14.88	-4.006	150	2.833	4.472	63.342	1.639
	14.76	-4.060	50	0.941	14.89	-4.070	52	0.986	3.532	54.562	1.605
	14.76	-4.059	50	0.941	14.88	-4.079	102	1.934	4.874	58.993	1.999
	14.76	-4.069	100	1.883	14.89	-4.070	52	0.986	4.889	58.680	2.020

## 2.4 Thermal Images

### Measurements

Bx1	Max	75.9 °C
Bx2	Max	43.2 °C

### Parameters

Emissivity	0.94
Ref. temp.	20 °C

09/16/21 08:37:40 PM

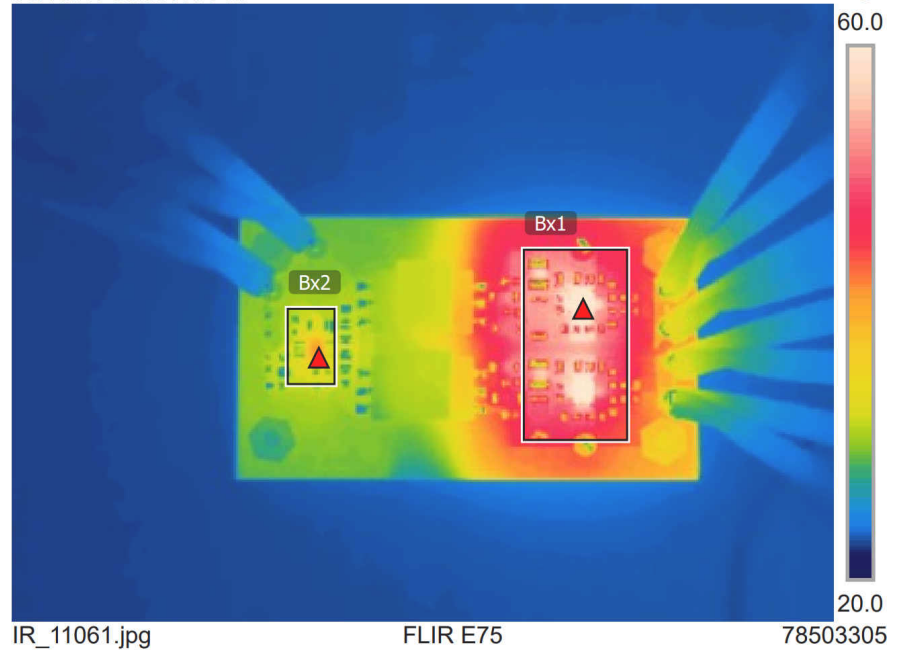


Figure 2-4. Thermal Image

Bx1: Dual LDO Output  
Bx2: LLC Converter

## 3 Waveforms

### 3.1 Switching

The following waveform shows the primary switching at 2.6 W.

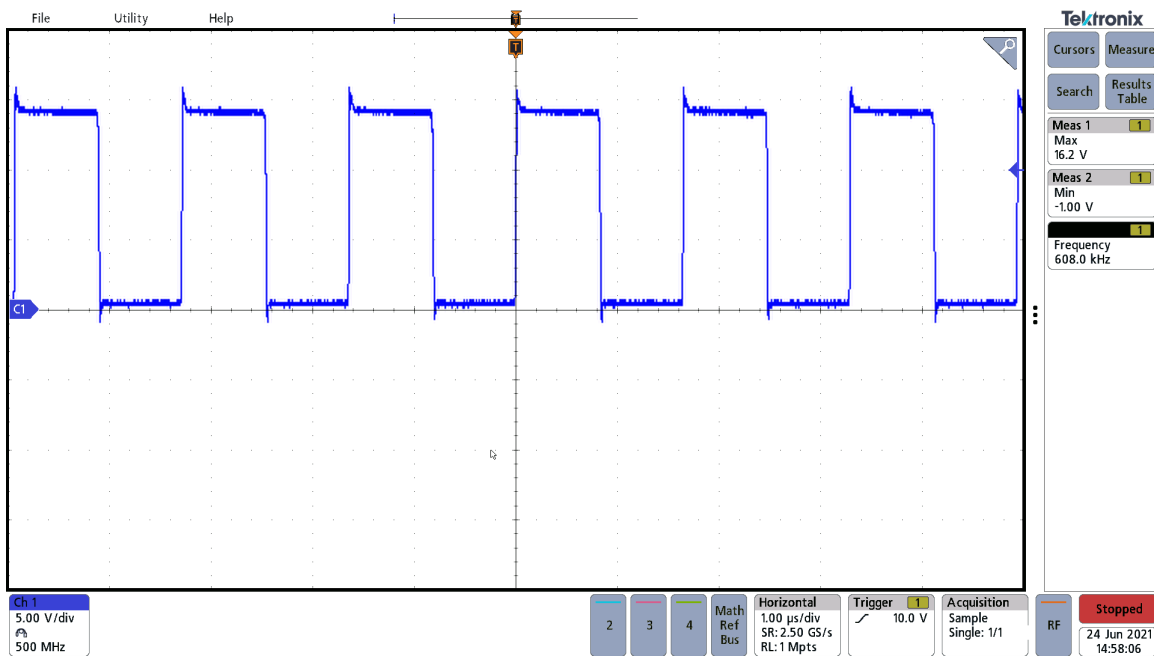
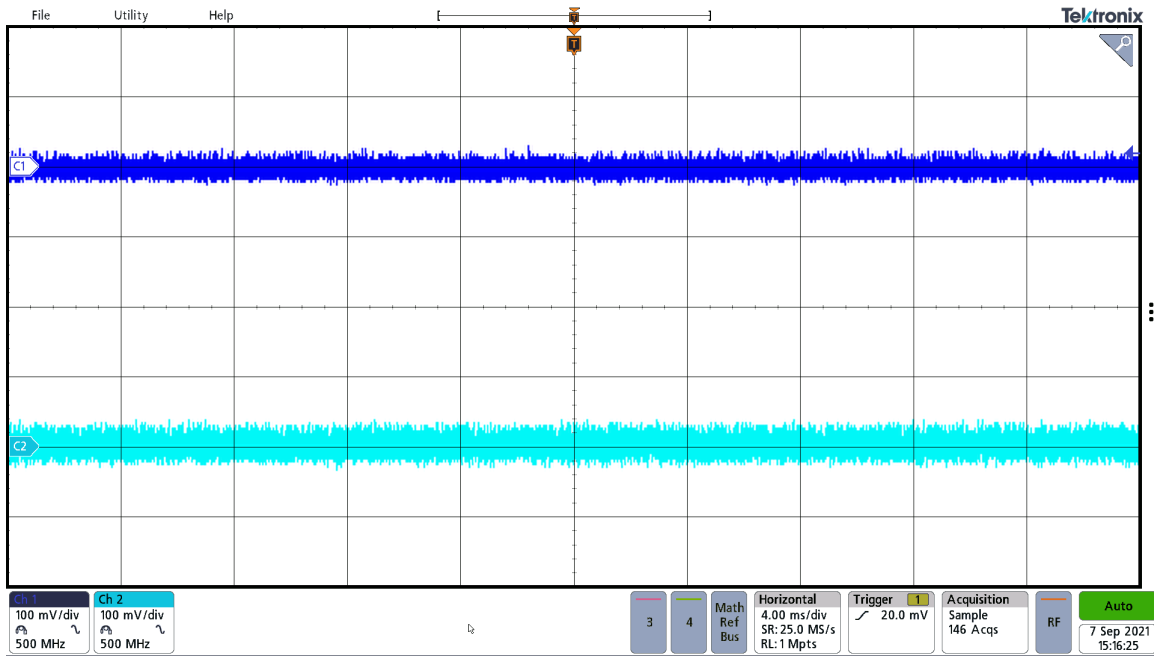


Figure 3-1. Primary Switching 2.6 W

### 3.2 Output Voltage Ripple

Figure 3-2 shows the PMP23124 output voltage ripple waveform.

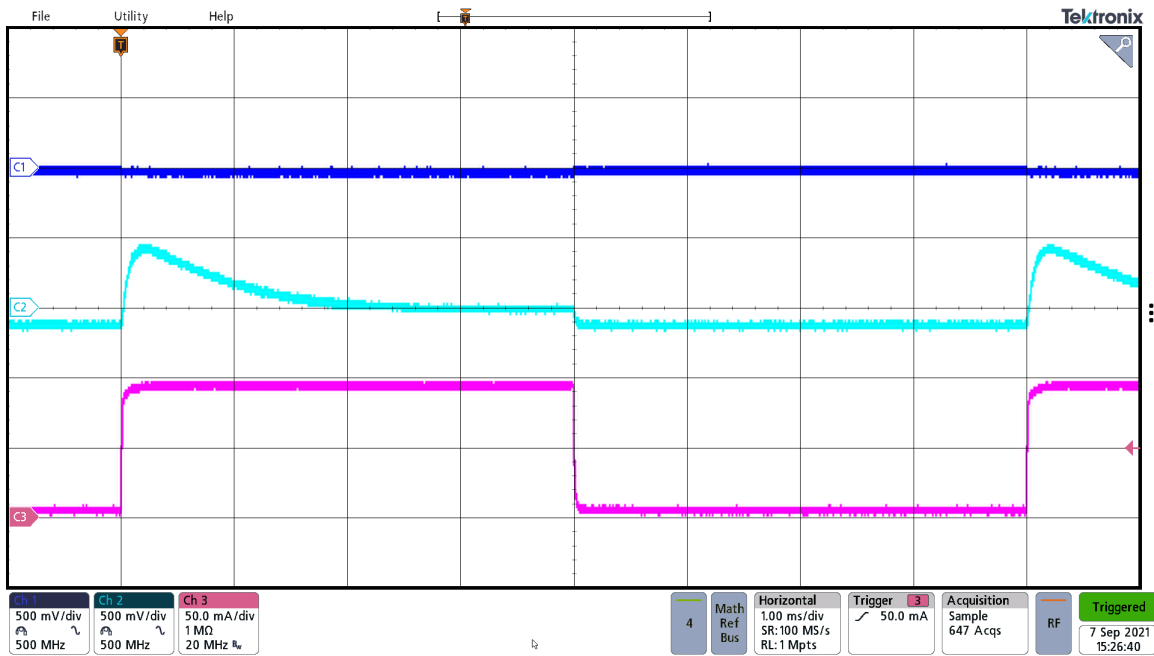


**Figure 3-2. Output Voltage Ripple**

Channel 1 (blue): +15-V output (AC coupled)  
Channel 2 (cyan): -4-V output (AC coupled)

### 3.3 Load Transients


The following waveform illustrates the PMP23124 load transient.



**Figure 3-3. Load Transient**


### 3.4 Start-up Sequence

Figure 3-4 shows the Start-up Rise Time waveform. Figure 3-5 shows the start-up with  $V_{IN}$  waveform

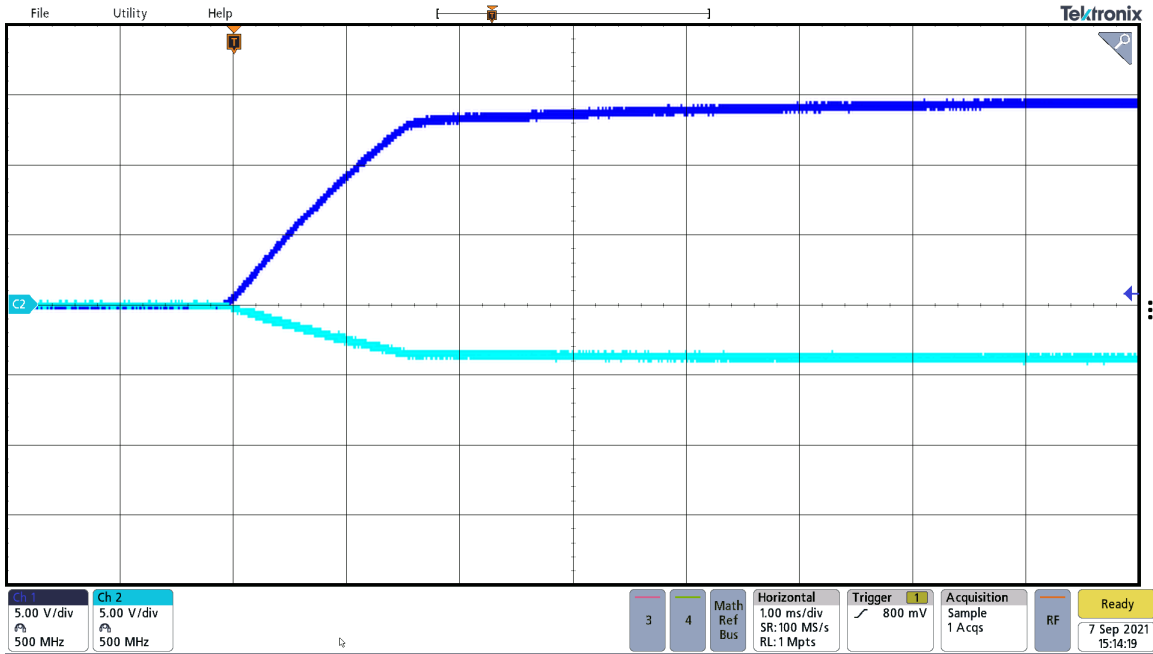

Channel 1 (blue): +15-V output  
 Channel 2 (cyan): -4-V output

Figure 3-4. Start-up Rise Time

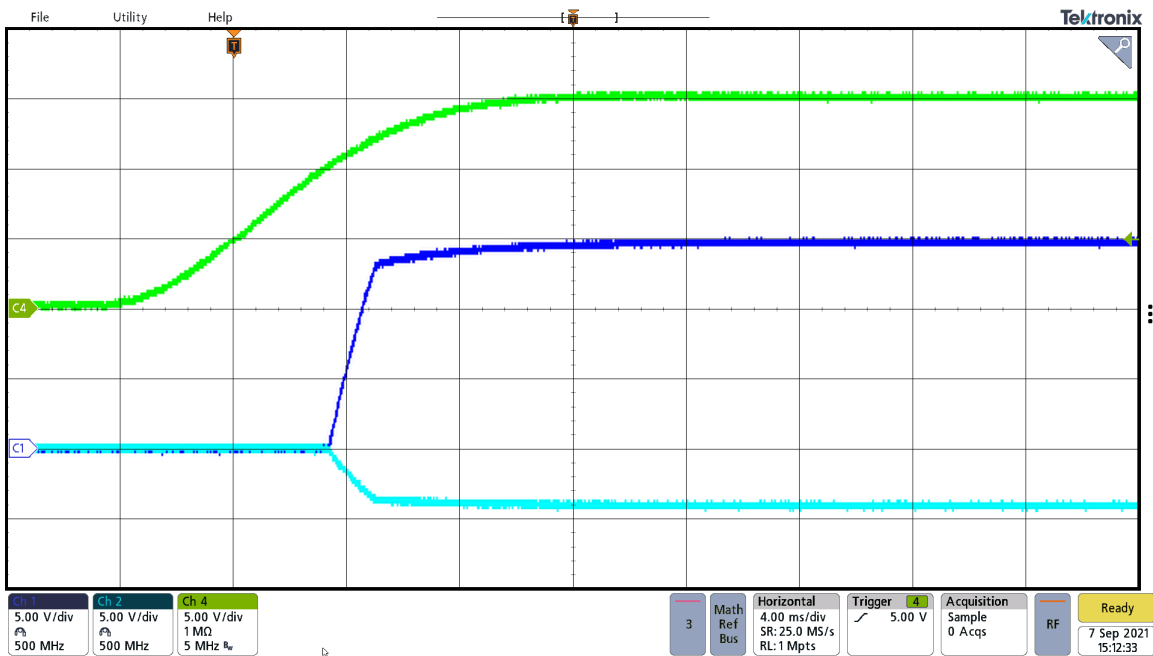

Channel 1 (blue): +15-V output  
 Channel 2 (cyan): -4-V output

Figure 3-5. Start-Up With  $V_{IN}$

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated