

TI Designs: TIDA-00243 Dual Mode Wireless Receiver



Operating the TIDA-00243 in CC mode while driving a charger IC (The wireless RX circuit was in parallel with a USB circuit)

Using the TIDA-00243 SFF board

Output voltage 5.3 Vdc

Diode drop 0.3 Vdc

Current Limit 500 mAmps

Modifications

Dual Mode R4 - removed

ILIM R3 - 220 resistor to set to 1000mA

(ILIM R3 - 1K resistor to set to 500mA)

VIREG R7 - 110k Ohm resistor

VO_REG R11 - 110k Ohm resistor

Parts

A diode was added in series with the output to protect the wireless RX from the USB input circuit - MBR0520L

Before charge

Measured voltage out of the RX before charge 5.302 Vdc

Max charge Current

Measured current at max charge 520 mAdc

Measured voltage out of the RX during charge 4.764 Vdc


Measured voltage after the diode before charge 4.443 Vdc

In regulation Charge

Measured current while in taper phase 400 mAdc

Measured voltage out of the RX during charge 4.281 Vdc

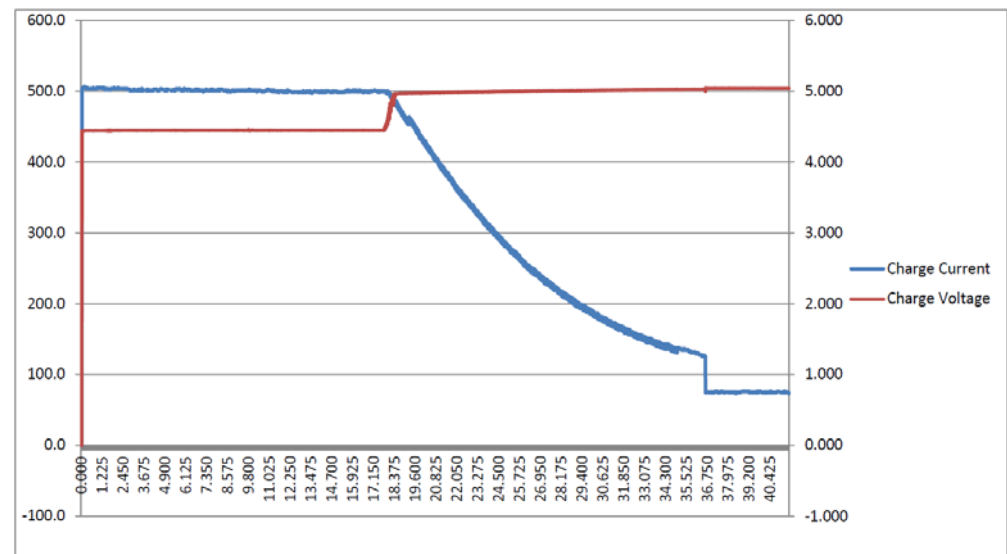Measured voltage after the diode before charge 4.987 Vdc



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated