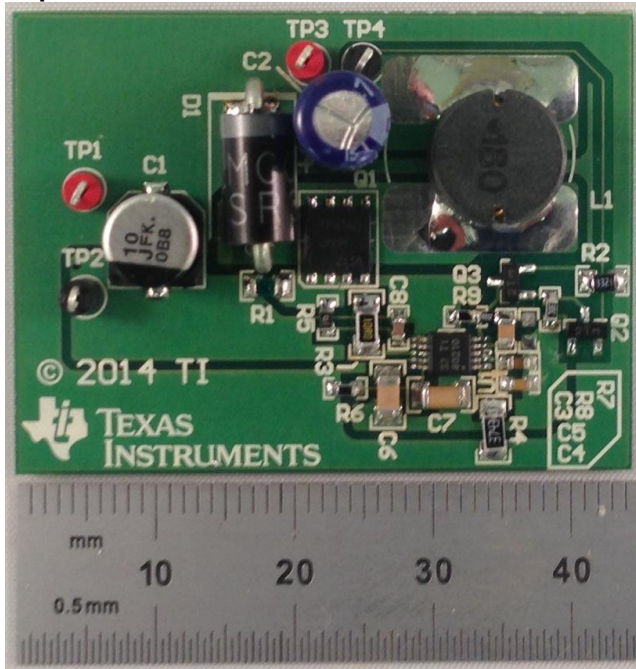



1 Photo

The photographs below show the PMP9624 Rev C assembly. This circuit was built on a PMP9624 Rev A PCB, which is a single layer board.

Top Side




Bottom Side

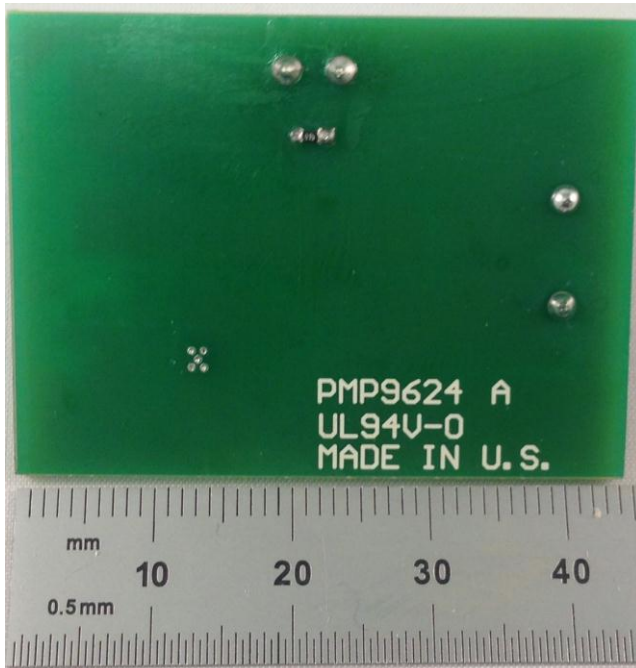

2 Converter Efficiency

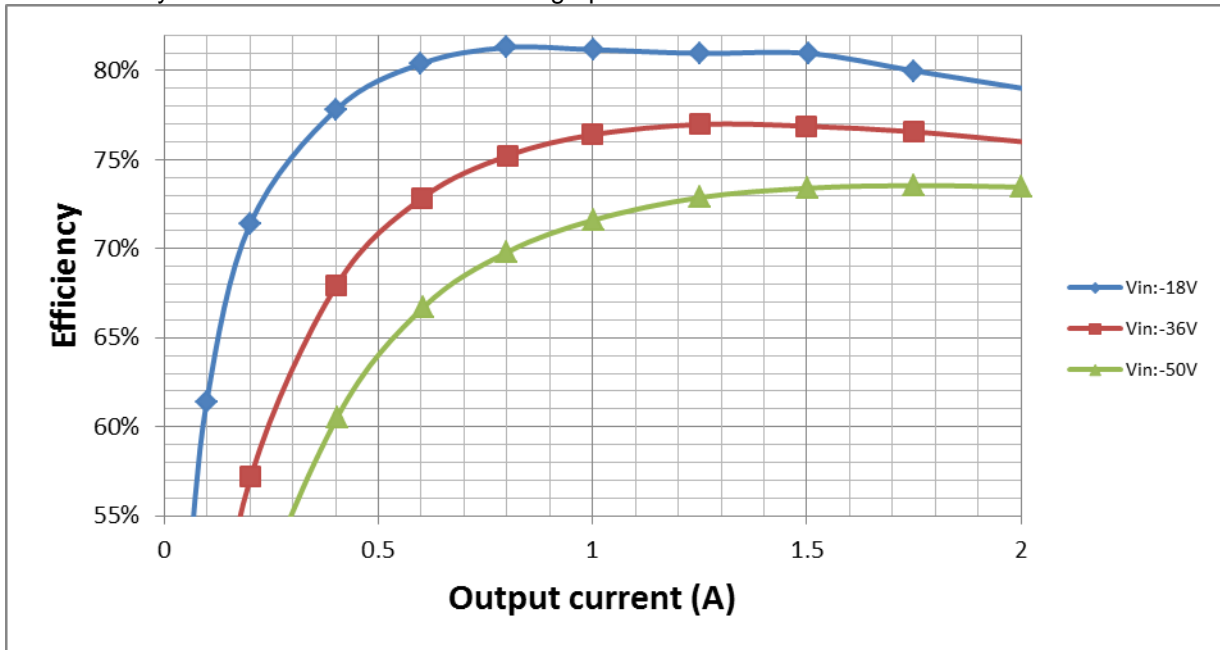The efficiency data is shown in the tables and graph below.



$V_{in} = -18V_{DC}$

Vin (V)	Iin(mA)	Pin(W)	Vout (V)	Iout(A)	Pout(W)	Losses(W)	Efficiency (%)
17.931	469.7	8.372	3.306	2.001	6.615306	1.756694	79.02%
17.942	406	7.237	3.308	1.75	5.789	1.448	79.99%
17.951	345.1	6.148	3.31	1.504	4.97824	1.16976	80.97%
17.961	287.3	5.114	3.31	1.251	4.14081	0.97319	80.97%
17.968	230	4.084	3.312	1.001	3.315312	0.768688	81.18%
17.977	184.28	3.26	3.313	0.8	2.6504	0.6096	81.30%
17.986	140.85	2.474	3.315	0.6	1.989	0.485	80.40%
17.996	99	1.709	3.316	0.401	1.329716	0.379284	77.81%
18.007	57.93	0.929	3.315	0.2	0.663	0.266	71.37%
18.009	39.32	0.5346	3.316	0.099	0.328284	0.206316	61.41%
18.012	31.59	0.3364	3.316	0.051	0.169116	0.167284	50.27%
18.012	25.86	0.09329	3.317	0	0	0.09329	0.00%

V_{in}=-36V_{DC}

Vin (V)	Iin(mA)	Pin(W)	Vout (V)	Iout(A)	Pout(W)	Losses(W)	Efficiency (%)
36.05	241.5	8.592	3.257	2.005	6.530285	2.061715	76.00%
36.07	209.6	7.446	3.258	1.75	5.7015	1.7445	76.57%
36.09	179.35	6.356	3.26	1.499	4.88674	1.46926	76.88%
36.11	150.08	5.299	3.261	1.251	4.079511	1.219489	76.99%
36.14	121.87	4.271	3.263	1	3.263	1.008	76.40%
36.16	100.3	3.48	3.264	0.802	2.617728	0.862272	75.22%
36.18	79.42	2.702	3.265	0.603	1.968795	0.733205	72.86%
36.21	59.4	1.933	3.267	0.402	1.313334	0.619666	67.94%
36.23	40.79	1.154	3.267	0.202	0.659934	0.494066	57.19%
36.24	32.56	0.7486	3.267	0.101	0.329967	0.418633	44.08%
36.24	29.24	0.5523	3.267	0.051	0.166617	0.385683	30.17%
36.25	25.36	0.18523	3.268	0	0	0.18523	0.00%


V_{in}=-50V_{DC}

Vin (V)	Iin(mA)	Pin(W)	Vout (V)	Iout(A)	Pout(W)	Losses(W)	Efficiency (%)
50.08	178.21	8.772	3.222	2	6.444	2.328	73.46%
50.1	156.27	7.673	3.223	1.751	5.643473	2.029527	73.55%
50.13	134.96	6.599	3.225	1.502	4.84395	1.75505	73.40%
50.15	113.87	5.531	3.227	1.249	4.030523	1.500477	72.87%
50.18	94.03	4.518	3.229	1.002	3.235458	1.282542	71.61%
50.2	78.33	3.703	3.231	0.8	2.5848	1.1182	69.80%
50.23	63.68	2.928	3.233	0.604	1.952732	0.975268	66.69%
50.25	49.81	2.158	3.234	0.404	1.306536	0.851464	60.54%
50.28	36.39	1.334	3.235	0.2	0.647	0.687	48.50%
50.28	30.77	0.929	3.235	0.1	0.3235	0.6055	34.82%
50.29	27.8	0.6586	3.235	0.05	0.16175	0.49685	24.56%
50.29	25.02	0.2859	3.237	0	0	0.2859	0.00%


3 Thermal Images

The thermal images below show a top view and bottom view of the board. The ambient temperature was 20°C with no forced air flow. The output was at full load: -3.3V/2A.

3.1 $V_{in}=-18V$

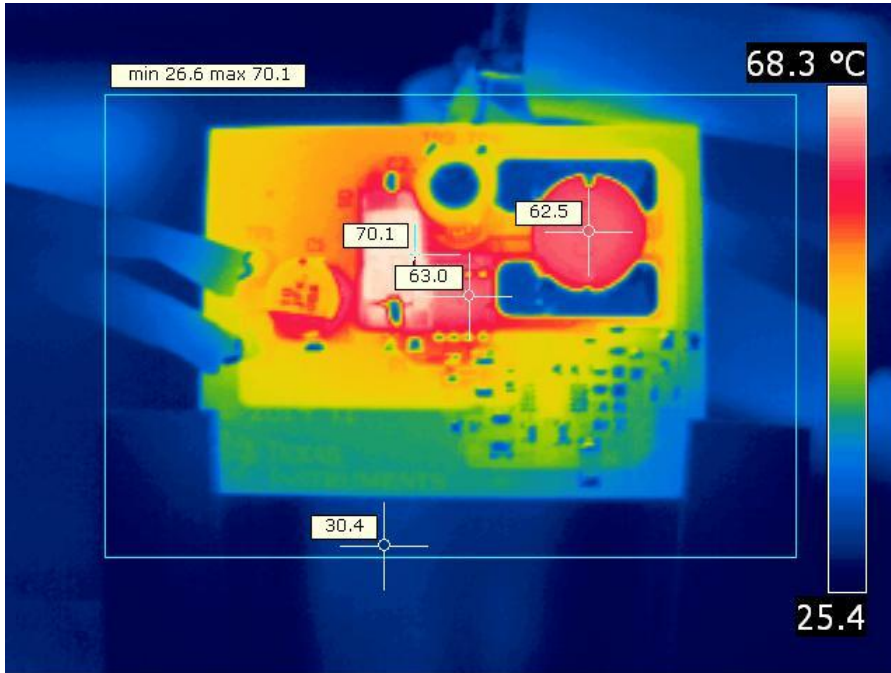

3.2 $V_{in}=-50V$

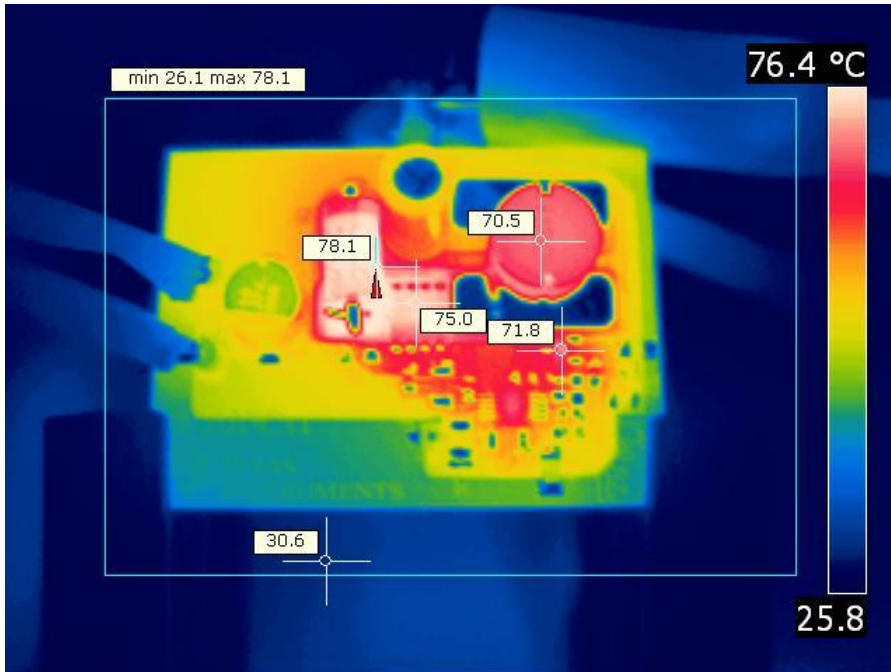


4 Startup

The output voltages during startup are shown in the image below, where CH1 is the input voltage and CH3 is the output voltage.

4.1 -18Vin: no load




4.2 -18Vin: -3.3V_{out}/2A

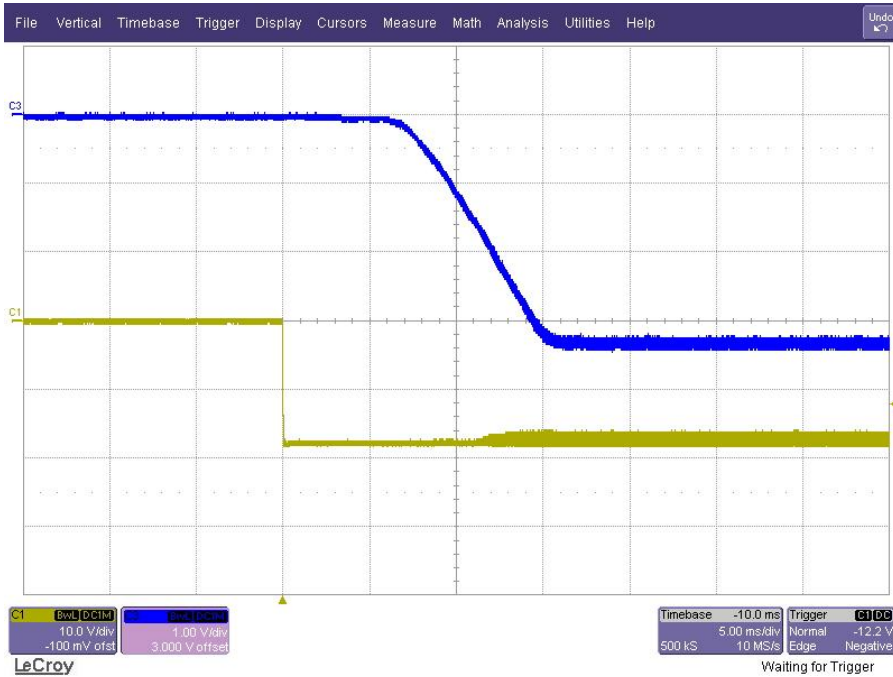


4.3 -36Vin: no load



4.4 -36Vin: -3.3V_{out}/2A

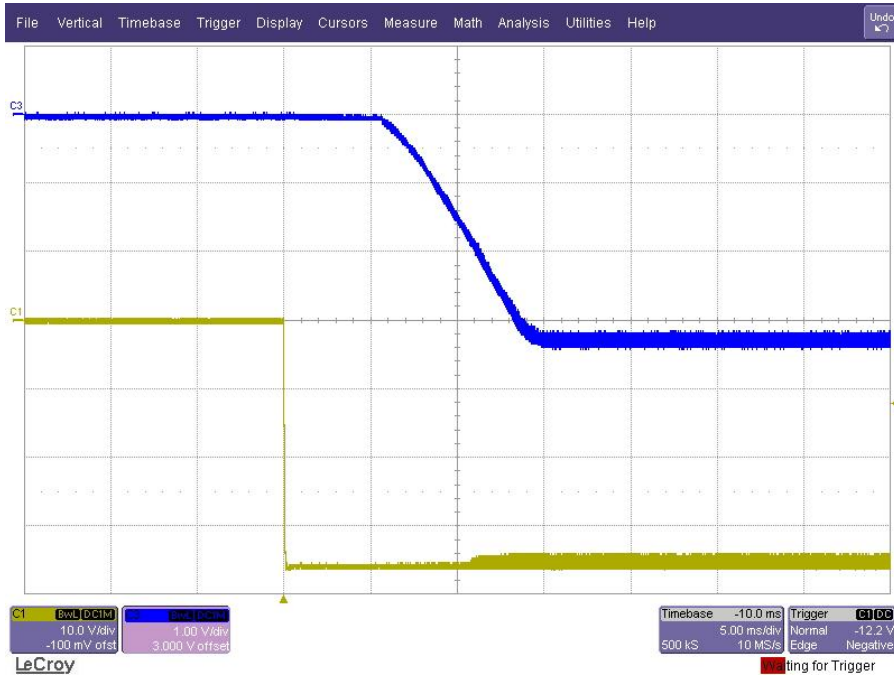

4.5 -50Vin: no load

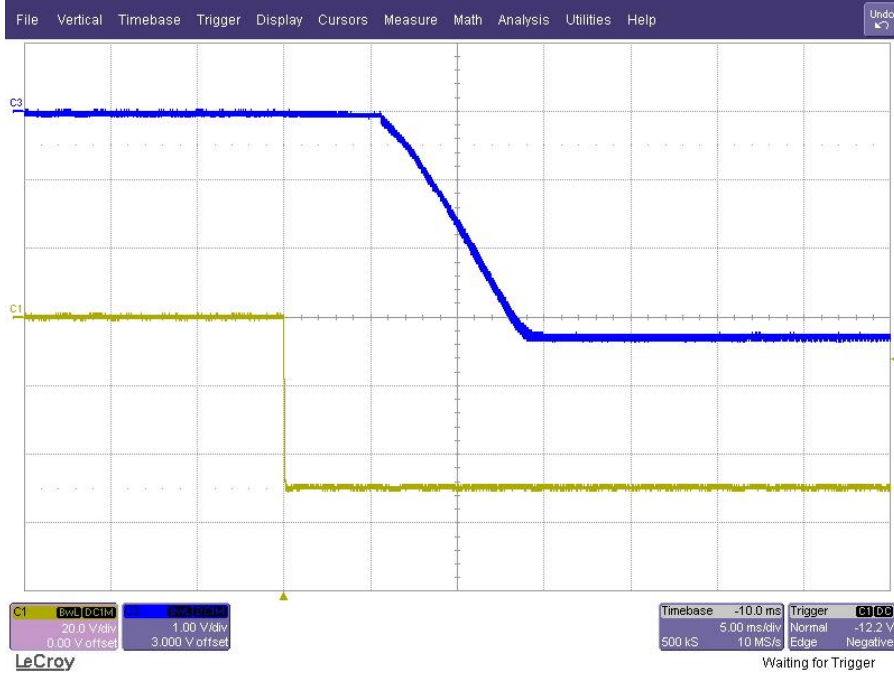


4.6 -50Vin: -3.3V_{out}/2A




5 Turn off

The output voltages at turn off transient are shown in the image below.


5.1 -18Vin: -3.3V_{out}/2A

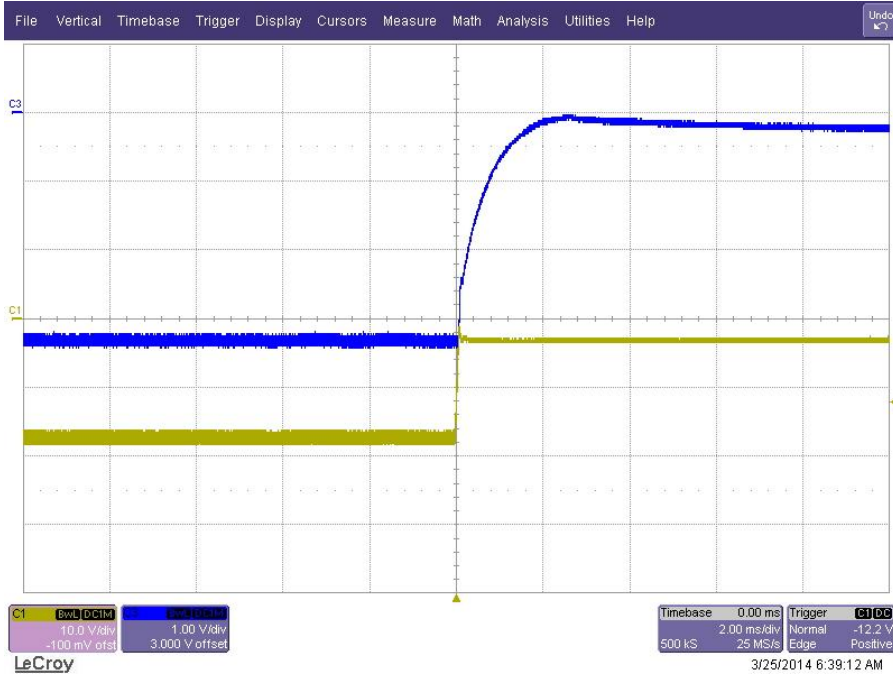

5.2 -36Vin: -3.3V_{out}/2A

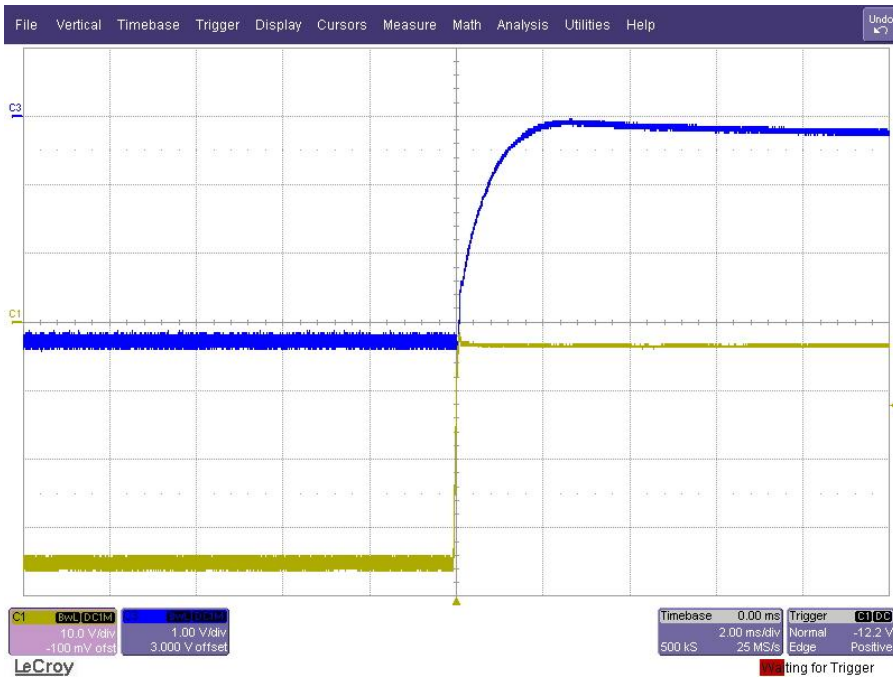


5.3 -50Vin: -3.3V_{out}/2A

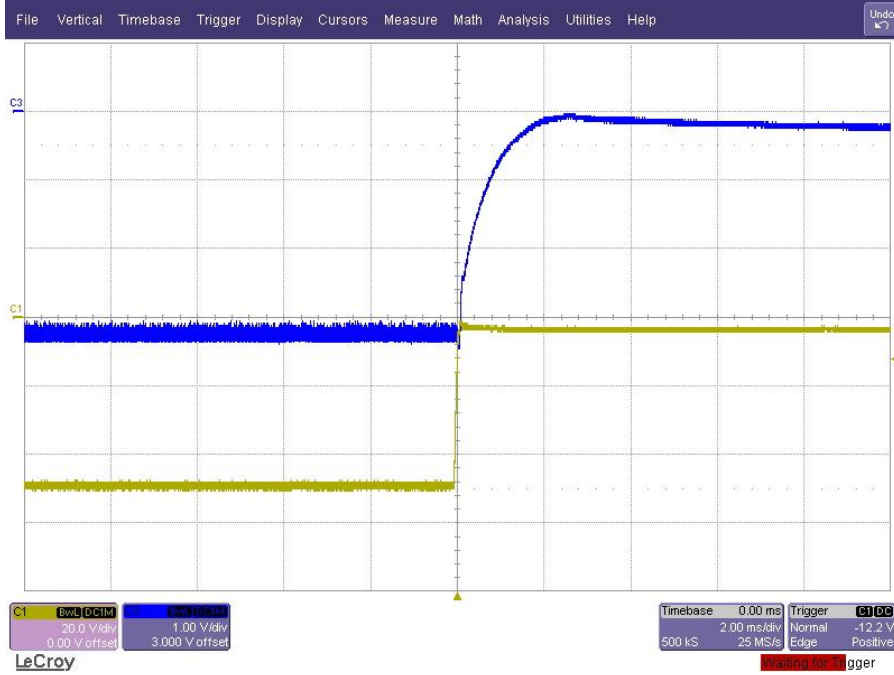


6 Output Ripple Voltages - Full Load

The output ripple voltages are shown in the plots below.


6.1 -18Vin: -3.3V_{out}/2A

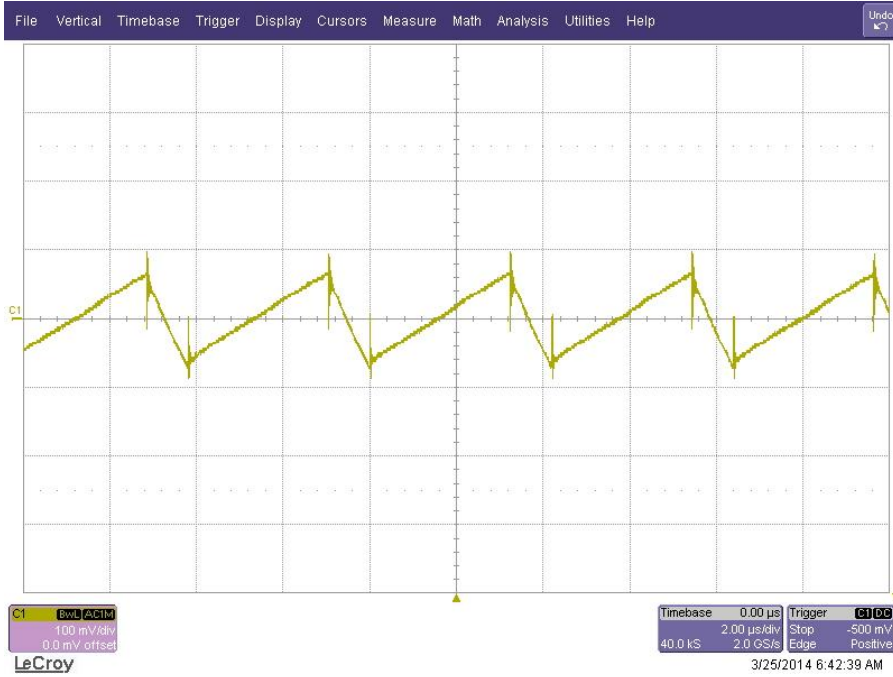

6.2 -36Vin: -3.3V_{out}/2A


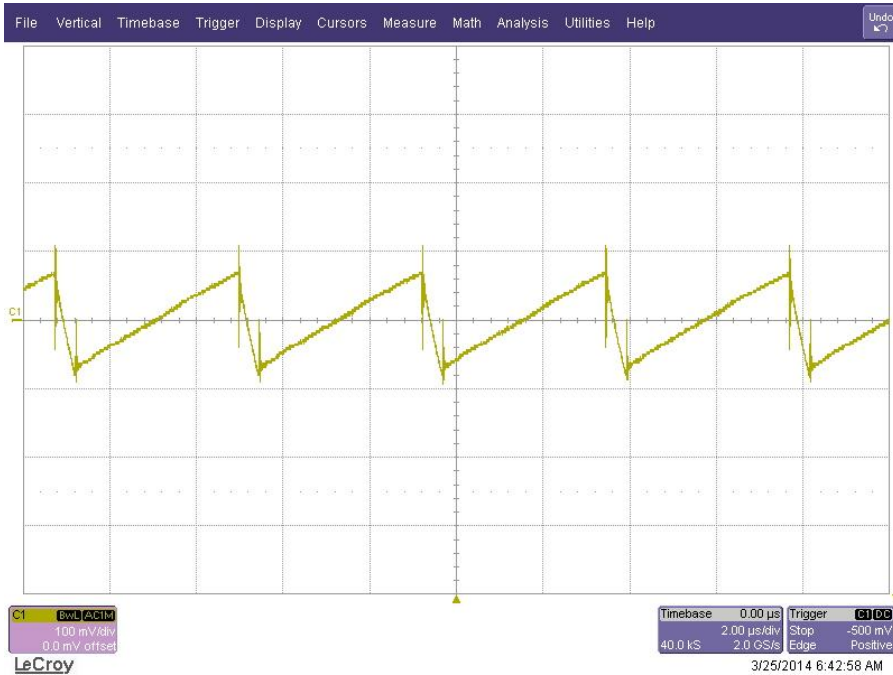


6.3 -50Vin: -3.3V_{out}/2A

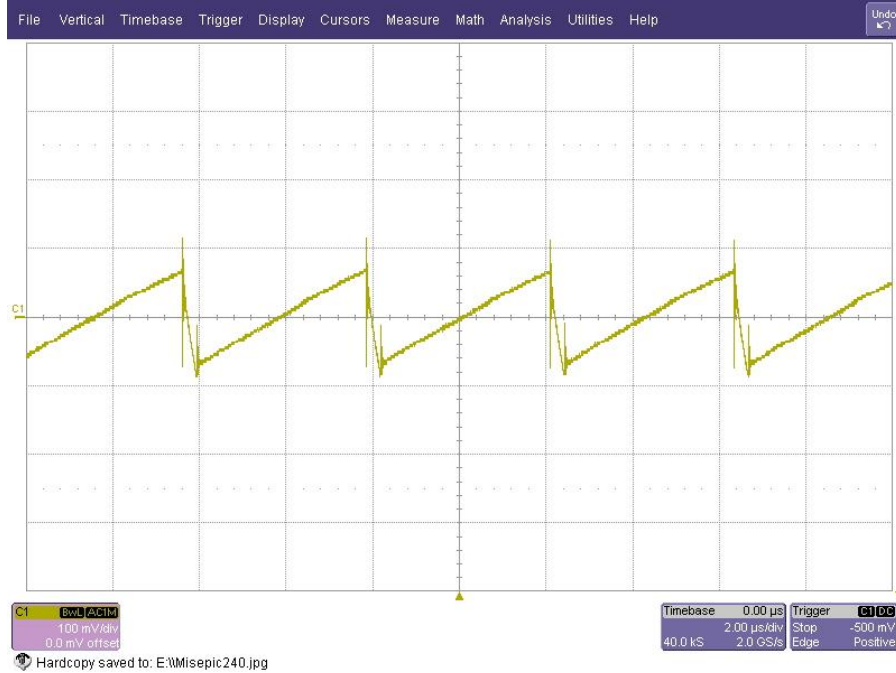

7 Load Transient

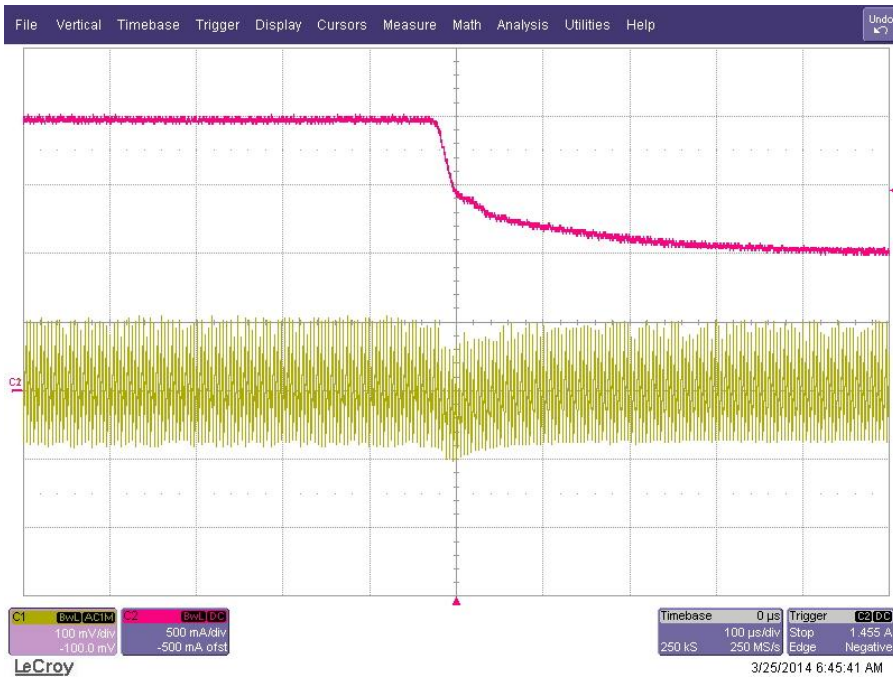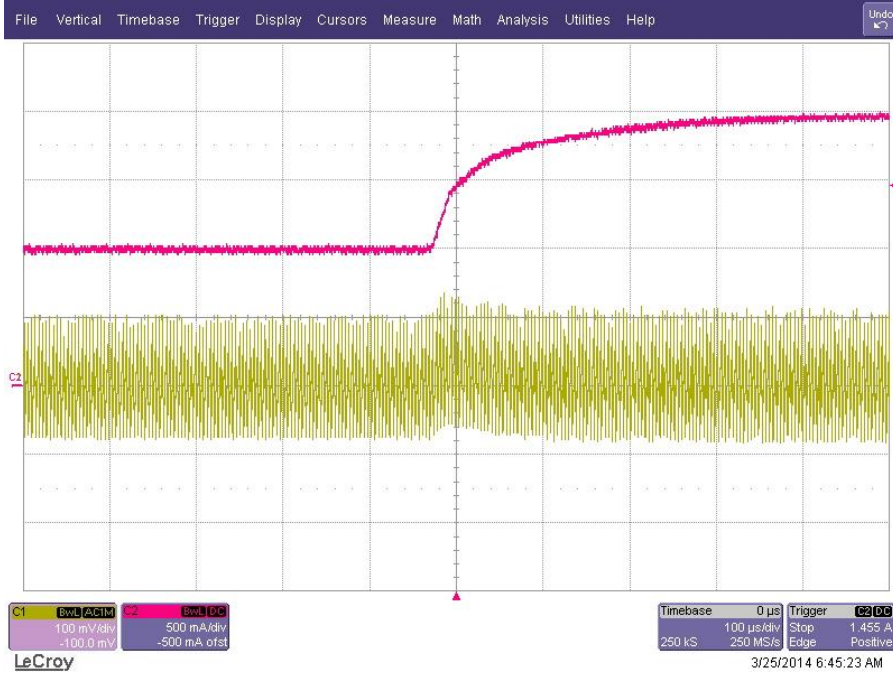
The image below shows $-3.3V_{out}$ voltage response to a **1A to 2A** load transient at $-36V_{in}$.




8 Switching Waveforms

The image below shows key switching waveforms of PMP9624RevA. The waveforms are measured with 2A output current with respect to TP2.

8.1 MOSFET Q1 @ -18V_{in}

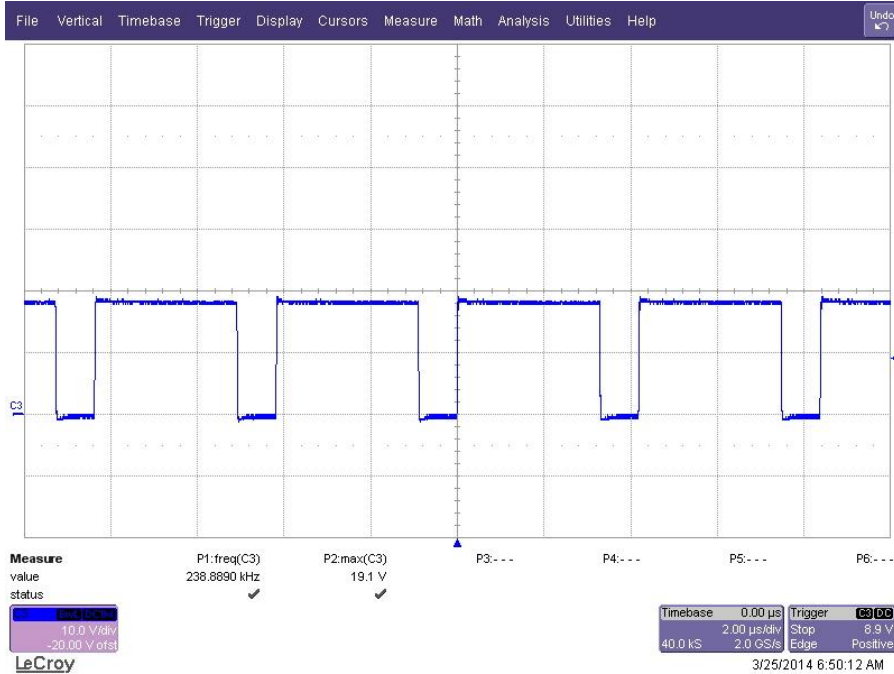

8.2 MOSFET Q1 @ -50V_{in}

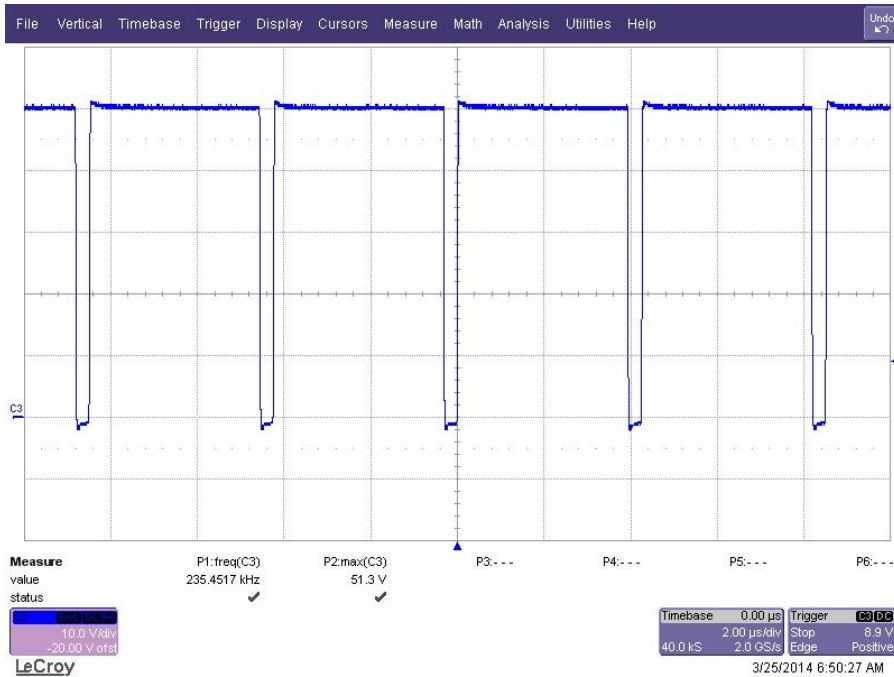

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated