 


- 1 Photo of the prototype: the PCB used for this design is the same as the PCB of PMP10397 Rev\_A





## 2 Startup

The output voltage behavior for 5V and 15V outputs is shown in the images below. The input voltage was set to 325Vdc. The outputs were fully loaded for the upper picture and unloaded for the bottom one.

**Ch.3: 5V Output (2V/div, 20ms/div, 20MHz BWL)**


**Ch.4: 15V Output (5V/div, 20MHz BWL)**

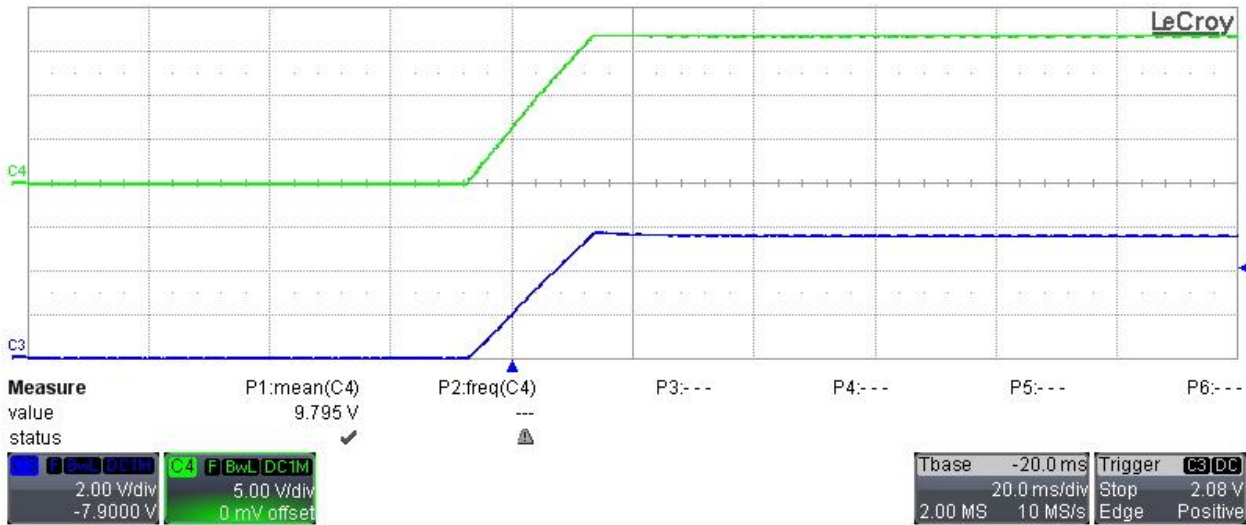 
 
### 3 Efficiency

The efficiency data are shown in the tables and graphs below.

The input voltage has been set to DC peak value of 85Vac, 120Vac, 230Vac and 440Vac, respectively equivalent to 120Vdc, 170Vdc, 325Vdc and 622Vdc. Both outputs have been loaded from 0 to full load proportionally.



Vin (V)	Iin (mA)	V5 (V)	I5 (mA)	V15 (V)	I15(mA)	Pout (W)	Pin (W)	Eff. (%)
120	2.46	5.495	0.0	16.74	0.0	0.00	0.30	0.0%
120	6.79	5.287	32.4	16.73	10.2	0.34	0.81	42.0%
120	10.39	5.228	61.8	16.71	20.1	0.66	1.25	52.9%
120	21.31	5.139	150.0	16.66	50.0	1.60	2.56	62.7%
120	40.09	5.072	302.3	16.64	100.7	3.21	4.81	66.7%



Vin (V)	Iin (mA)	V5 (V)	I5 (mA)	V15 (V)	I15(mA)	Pout (W)	Pin (W)	Eff. (%)
170	1.76	5.529	0.0	16.78	0.0	0.00	0.30	0.0%
170	4.65	5.285	32.4	16.72	10.0	0.34	0.79	42.8%
170	7.14	5.228	61.8	16.70	20.2	0.66	1.21	54.4%
170	14.62	5.144	150.0	16.67	50.3	1.61	2.49	64.8%
170	27.52	5.081	302.4	16.66	101.9	3.23	4.68	69.1%

Vin (V)	Iin (mA)	V5 (V)	I5 (mA)	V15 (V)	I15(mA)	Pout (W)	Pin (W)	Eff. (%)
325	1.03	5.523	0.0	16.73	0.0	0.00	0.33	0.0%
325	2.61	5.289	32.4	16.73	10.1	0.34	0.85	40.1%
325	3.85	5.240	61.8	16.71	20.0	0.66	1.25	52.6%
325	7.63	5.162	150.0	16.70	50.2	1.61	2.48	65.0%
325	14.09	5.093	302.3	16.69	100.0	3.21	4.58	70.1%

Vin (V)	Iin (mA)	V5 (V)	I5 (mA)	V15 (V)	I15(mA)	Pout (W)	Pin (W)	Eff. (%)
622	0.922	5.855	0.0	17.62	0.0	0.00	0.57	0.0%
622	1.87	5.291	32.4	16.72	10.0	0.34	1.16	29.1%
622	2.51	5.228	61.8	16.70	20.4	0.66	1.56	42.5%
622	4.46	5.163	150.0	16.69	50.8	1.62	2.77	58.5%
622	7.95	5.093	302.3	16.68	100.8	3.22	4.94	65.1%
  
#### 4 Output Voltage Regulation versus Output Power

The output voltage variation versus total load, for the four input voltages, is plotted below.



### 5 Cross Regulation


The output voltage variation, by unbalancing the outputs, has been measured with the converter supplied at 325Vdc. The results are shown in the table below:

5V Current	15V Current	5V Voltage	15V Voltage
50mA	0	5.099V	16.88V
300mA	100mA	5.093V	16.69V
300mA	0	5.046V	18.38V
50mA	100mA	6.057V	16.67V


### 6 Output Ripple Voltage

The output ripple voltage on both outputs have been measured by supplying the converter @ 85Vac, 60Hz (worst case) and 325Vdc with both outputs fully loaded (20MHz BWL for all waveforms).

**Ch.3: 5V Output (20mV/div, 5ms/div, AC coupling), Vin = 85Vac, 60Hz**

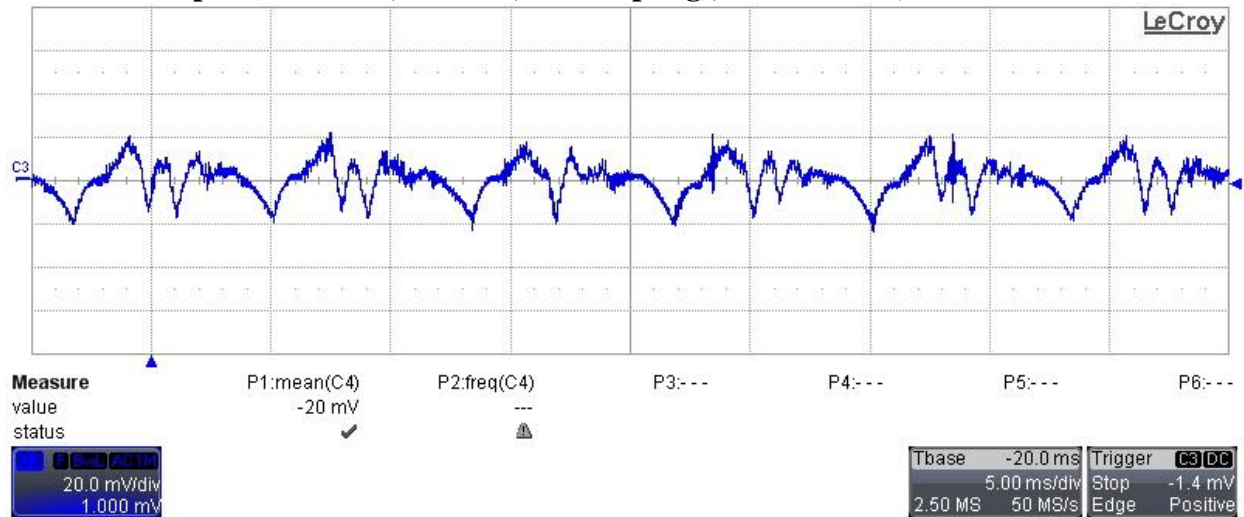


**Ch.3: 15V Output (20mV/div, 5ms/div, AC coupling), Vin = 85Vac, 60Hz**

 




**Ch.3: 5V Output (20mV/div, 500us/div, AC coupling), Vin = 325Vdc**

 

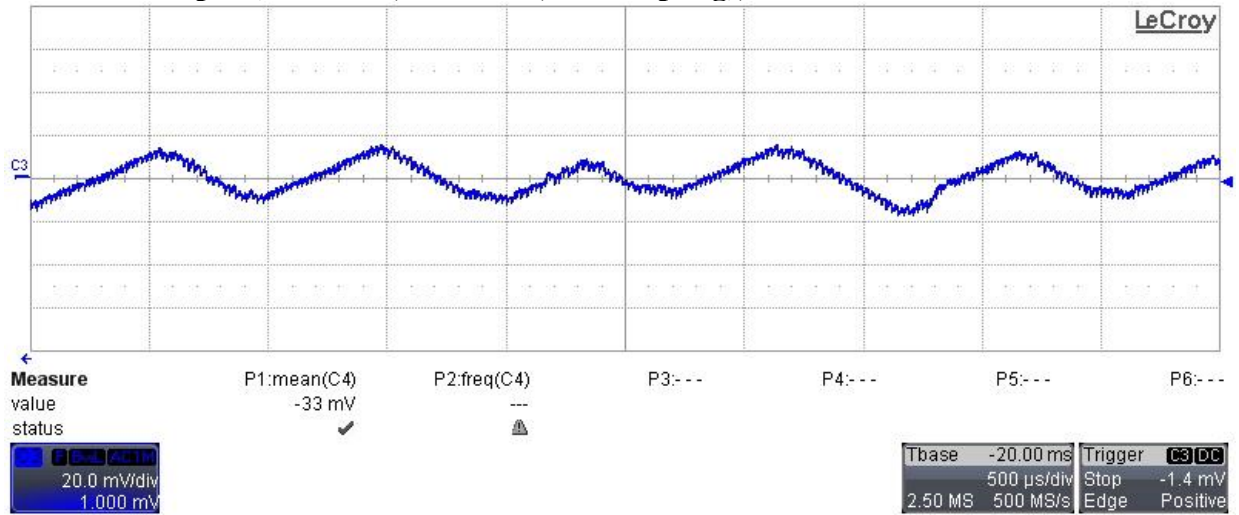
**Ch.3: 15V Output (20mV/div, 500us/div, AC coupling), Vin = 325Vdc**


 
## 7 Switch-node

The image below shows the collector voltage of Q1, taken at 622Vdc input and full load on both outputs.

Ch.2: Q1 Collector Voltage (200V/div, 10us/div, DC coupling, 200MHz BWL)



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated