
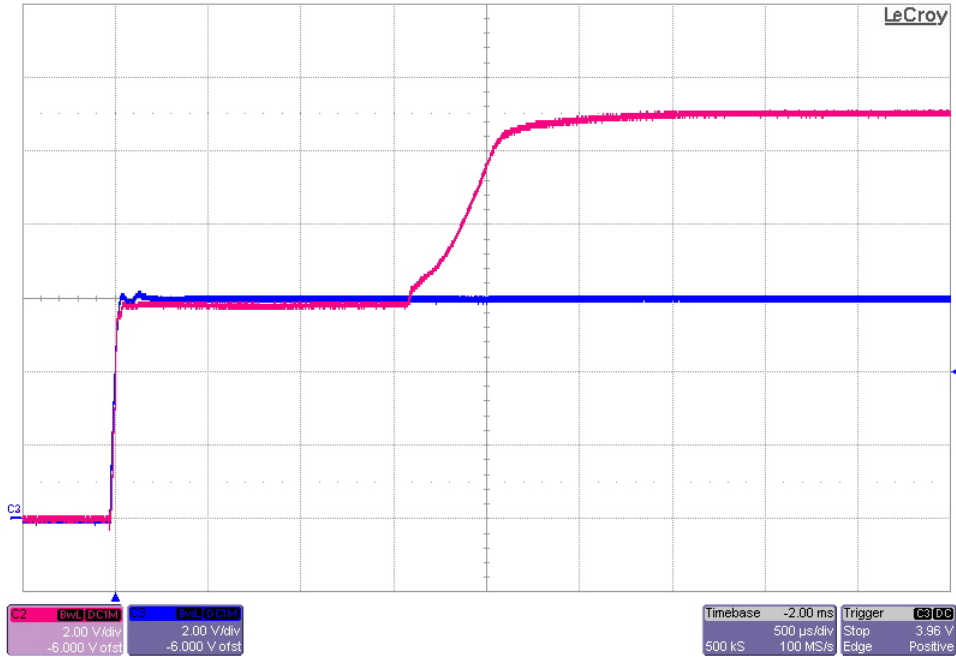


1 Startup

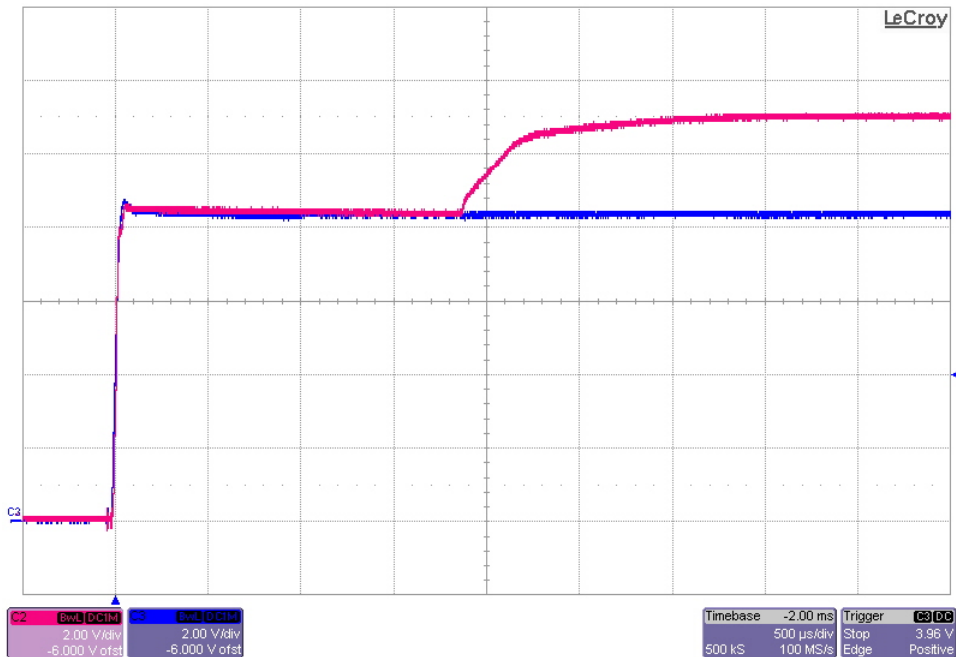
The photo below shows the output voltage startup waveform after the application of 6V in with the 11V output loaded to 0A. (2V/DIV, 500uS/DIV)




The photo below shows the output voltage startup waveform after the application of 8.4V in with the 11V output loaded to 0A. (2V/DIV, 500uS/DIV)



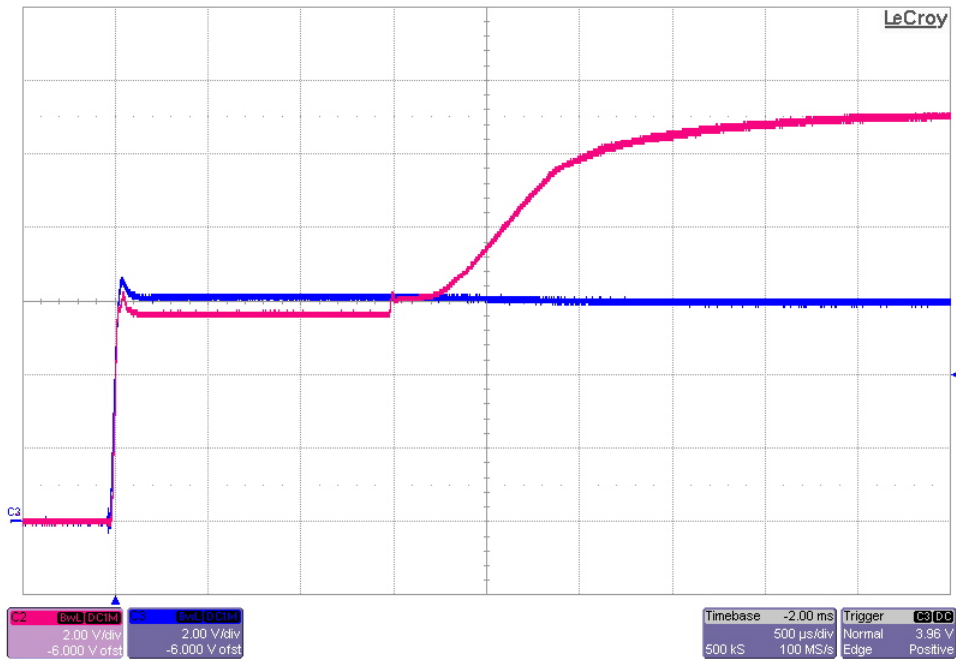The photo below shows the output voltage startup waveform after the application of 6V in with the 11V output loaded to 1.2A. (2V/DIV, 500uS/DIV)




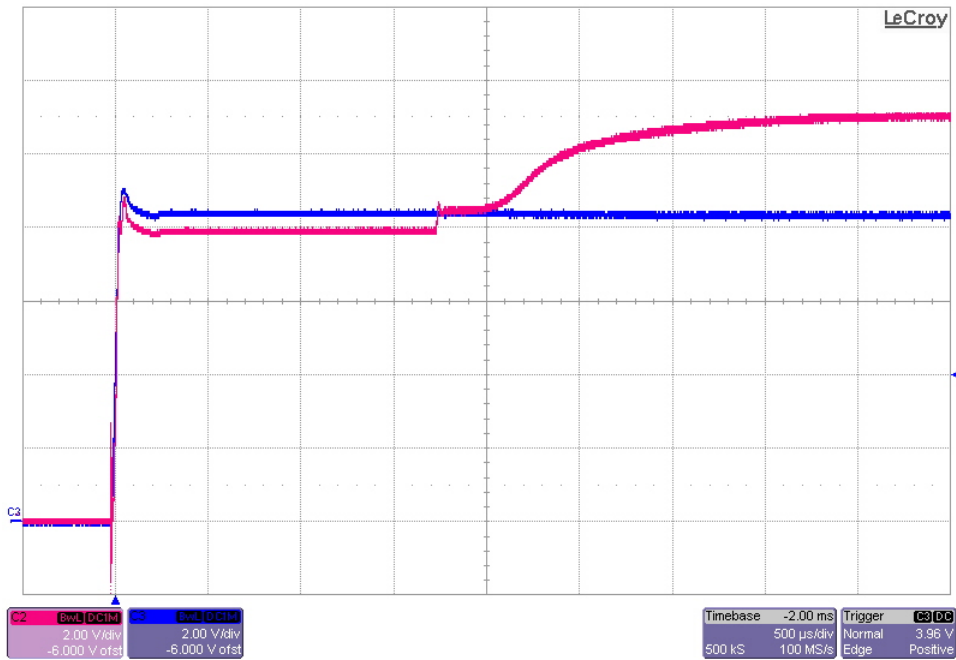The photo below shows the output voltage startup waveform after the application of 8.4V in with the 11V output loaded to 1.2A. (2V/DIV, 500uS/DIV)




2 Efficiency

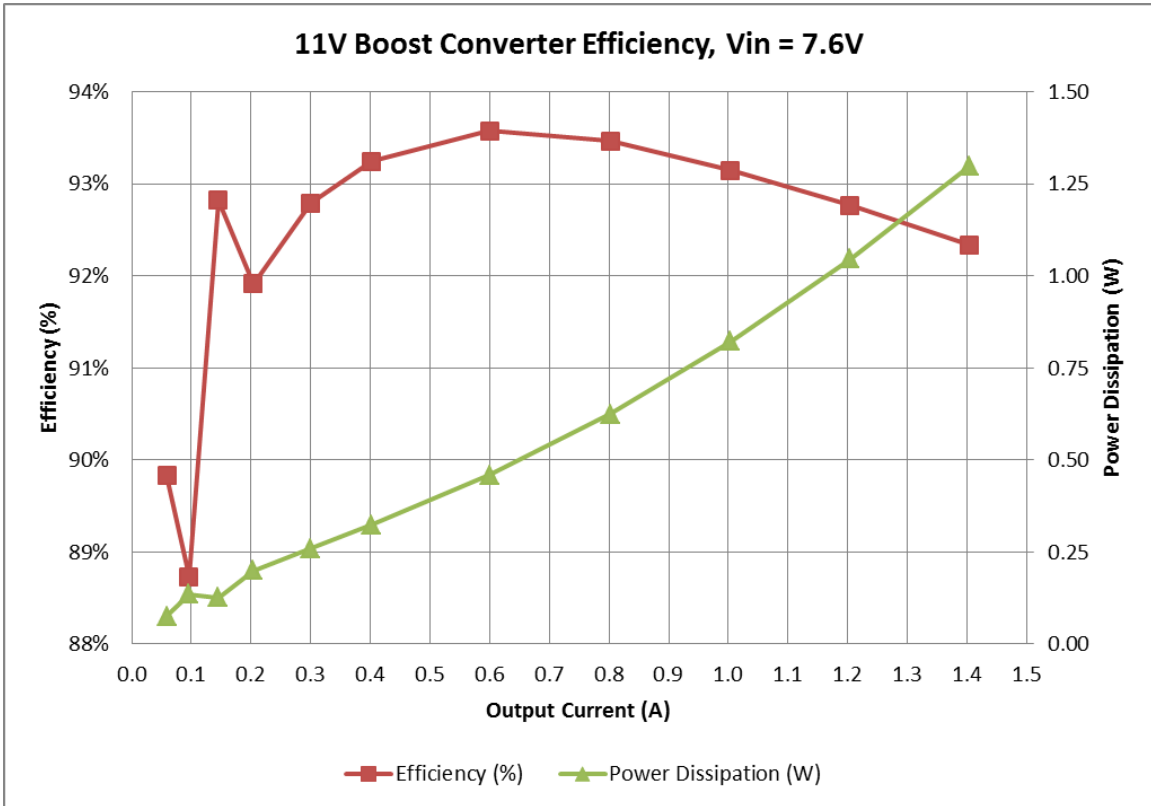The TPS55340 11V@1.2A boost converter efficiency is shown in the figure below.




3 Output Ripple Voltage

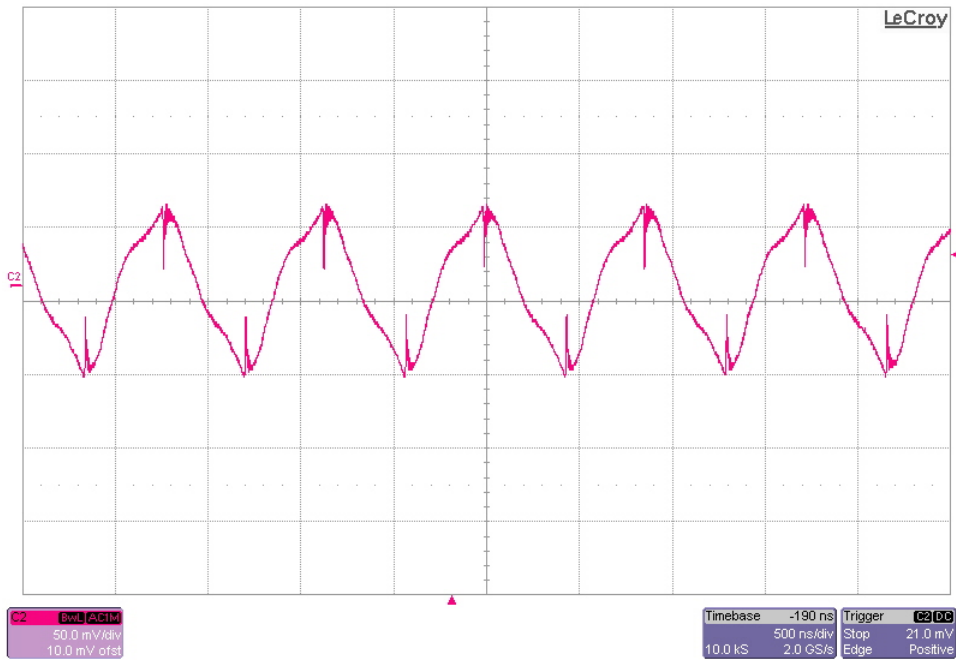The output ripple voltage is shown in the figure below. The image was taken with the 11V output loaded to 1.2A and the input voltage set to 6V. (50mV/DIV, 500nS/DIV)




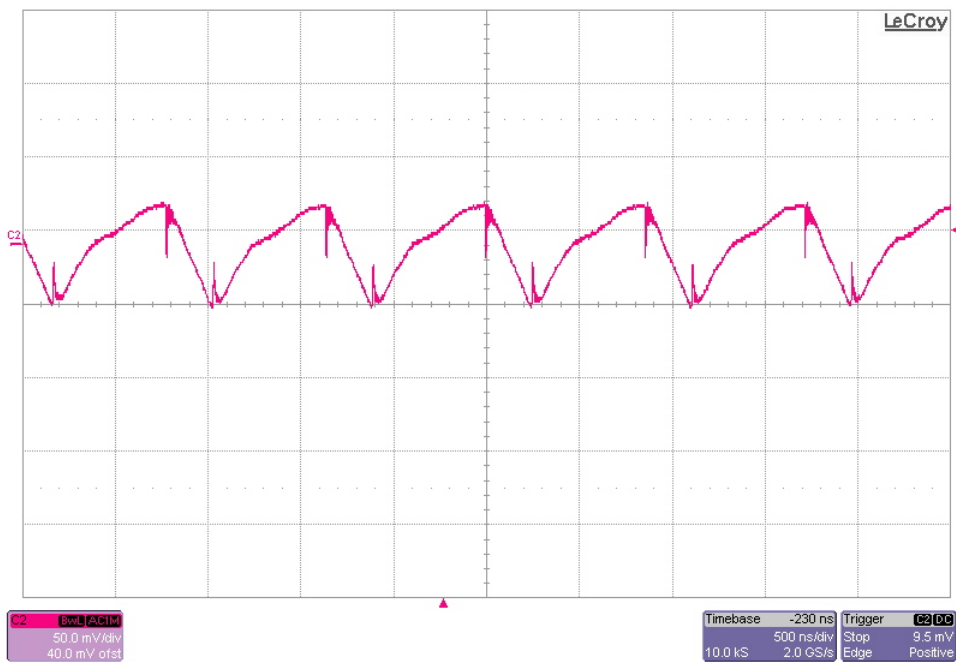The output ripple voltage is shown in the figure below. The image was taken with the 11V output loaded to 1.2A and the input voltage set to 8.4V. (50mV/DIV, 500nS/DIV)




4 Load Transients

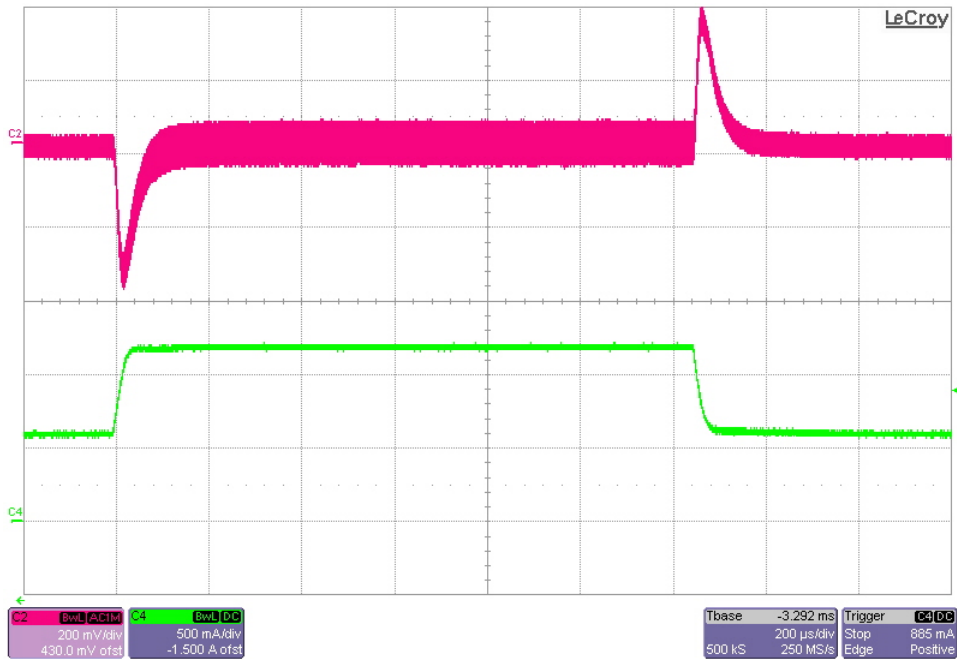
The photo below shows the output voltage (ac coupled) when the load current is stepped between 0.6A and 1.2A. $V_{in} = 6V$. (200mV/DIV, 500mA/DIV, 200uS/DIV)



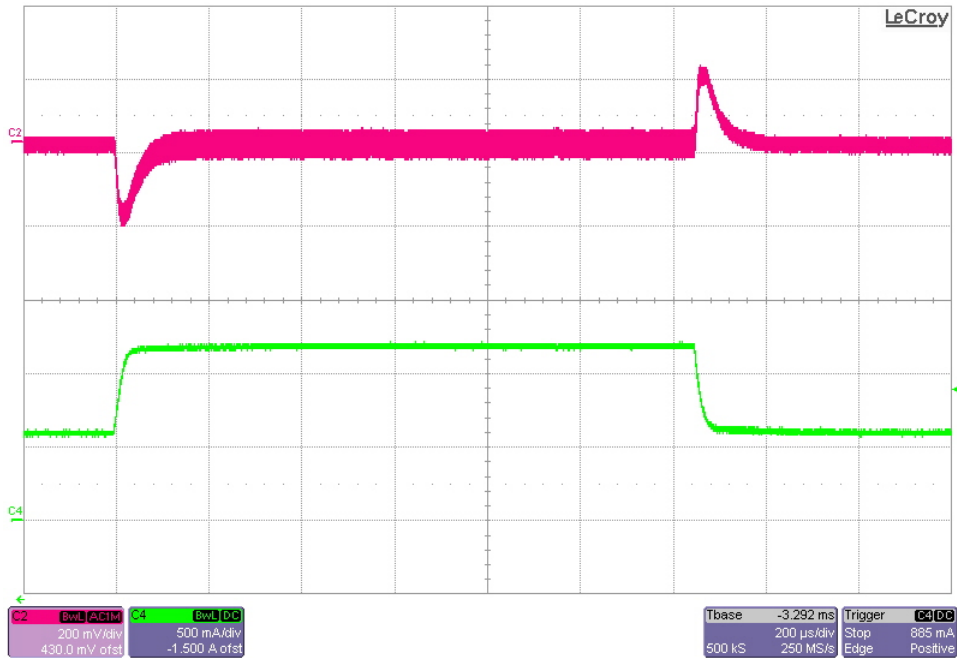
The photo below shows the output voltage (ac coupled) when the load current is stepped between 0.6A and 1.2A. $V_{in} = 8.4V$. (200mV/DIV, 500mA/DIV, 200uS/DIV)



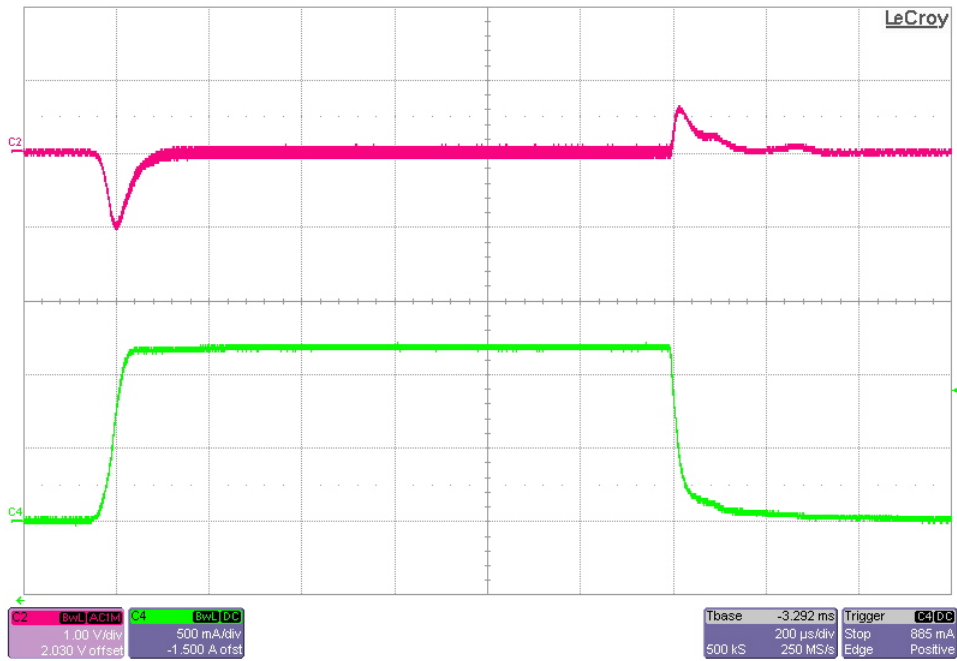The photo below shows the output voltage (ac coupled) when the load current is stepped between 0A and 1.2A. $V_{in} = 6V$. (1V/DIV, 500mA/DIV, 200uS/DIV)




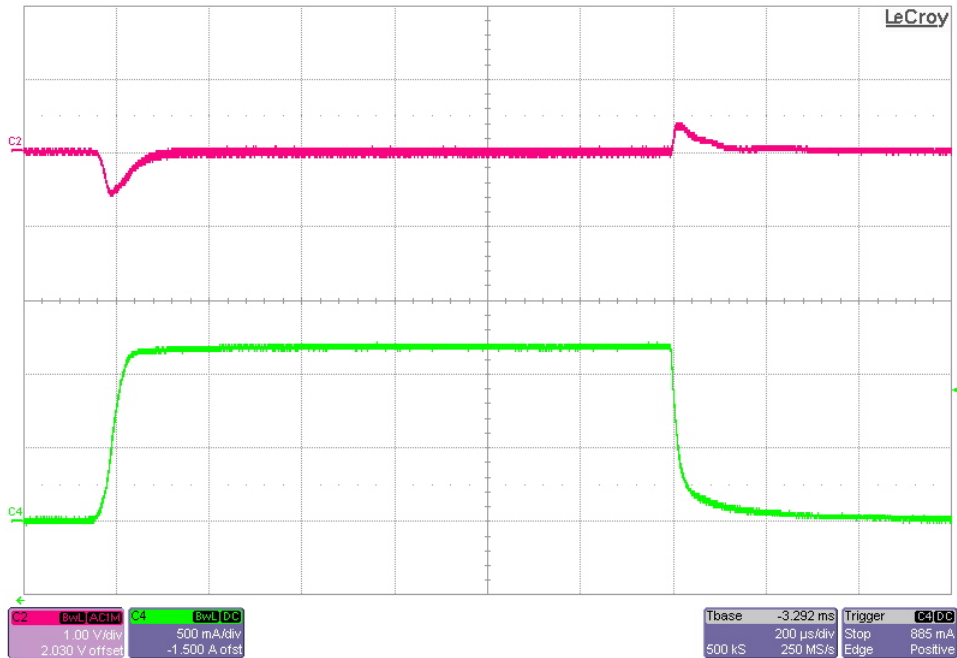The photo below shows the output voltage (ac coupled) when the load current is stepped between 0A and 1.2A. $V_{in} = 8.4V$. (1V/DIV, 500mA/DIV, 200uS/DIV)




5 Switch Node Waveforms

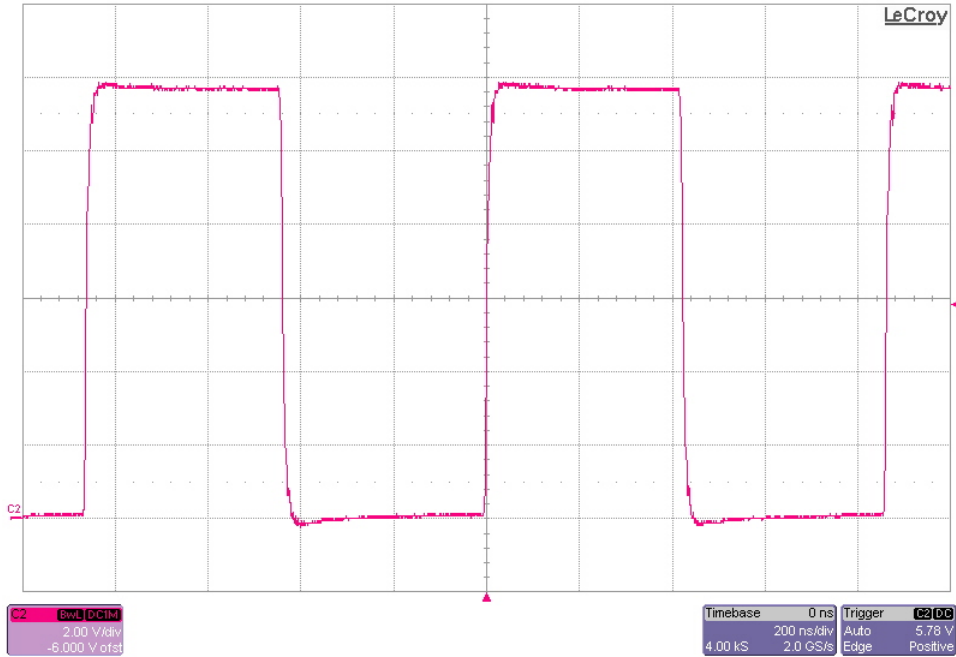
The photo below shows the switch node voltage (TP1). The input voltage is 6V and the 11V output is loaded to 1.2A. (2V/DIV, 200nS/DIV)



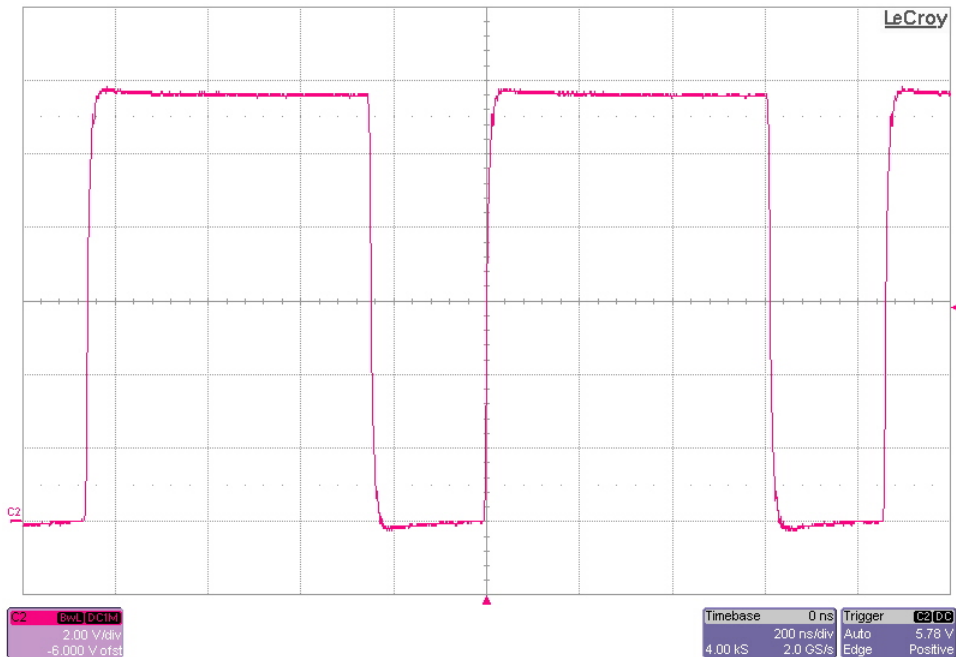
The photo below shows the switch node voltage (TP1). The input voltage is 8.4V and the 11V output is loaded to 1.2A. (2V/DIV, 200nS/DIV)



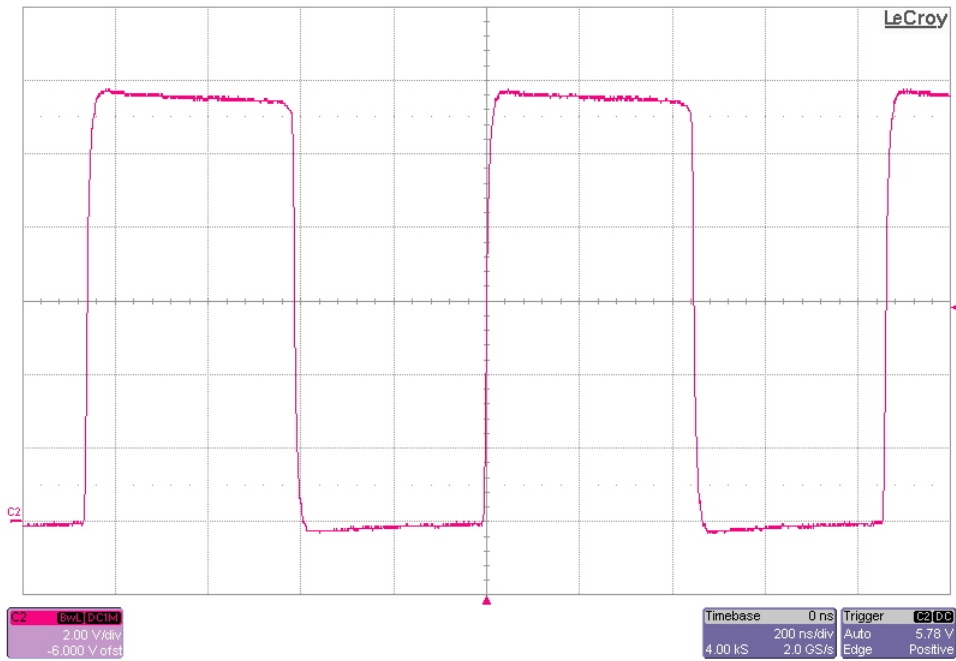The photo below shows the switch node voltage (TP1). The input voltage is 6V and the 11V output is loaded to 0.165A (beginning operation in DCM). (2V/DIV, 200nS/DIV)



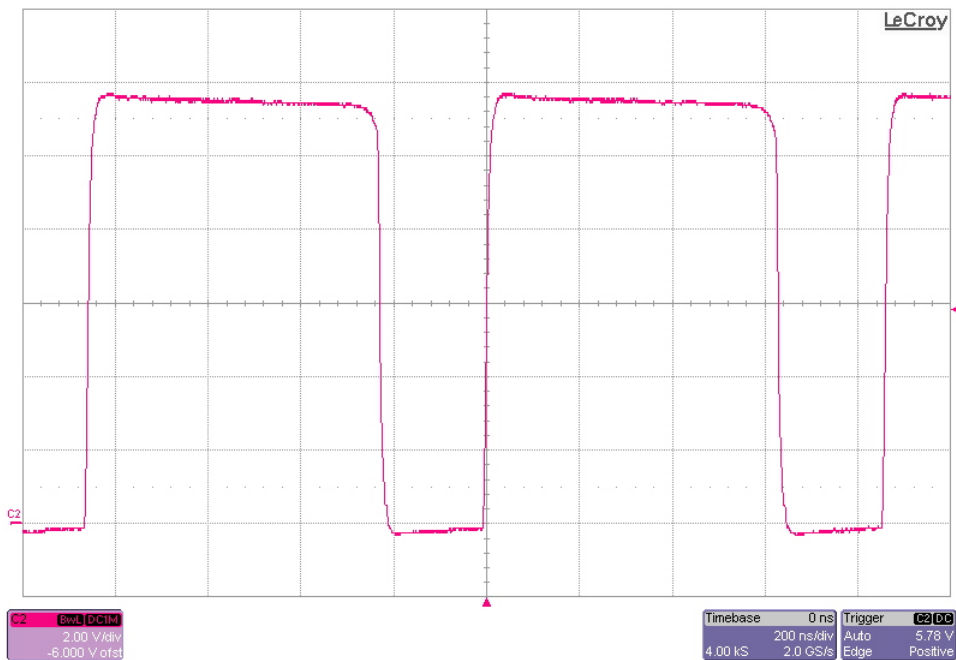The photo below shows the switch node voltage (TP1). The input voltage is 8.4V and the 11V output is loaded to 0.180A (beginning operation in DCM). (2V/DIV, 200nS/DIV)




6 Control Loop Gain / Stability

The plot below shows the boost converter's loop gain and phase margin when the 11V output is loaded to 1.2A.

Vin = 6V
Vin = 8.4V

Band Width = 20.3KHz
Band Width = 34.1KHz

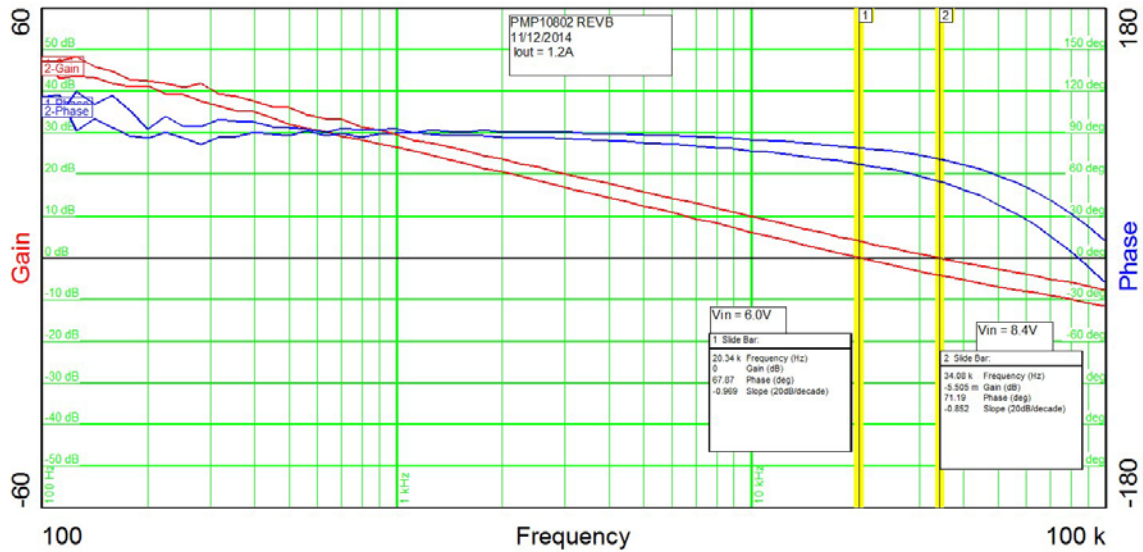Phase Margin = 68 degrees
Phase Margin = 71 degrees




The plot below shows the boost converter's loop gain and phase margin when the 11V output is loaded to 0.25A.

Vin = 6V
Vin = 8.4V


Band Width = 24.3KHz
Band Width = 37.2KHz

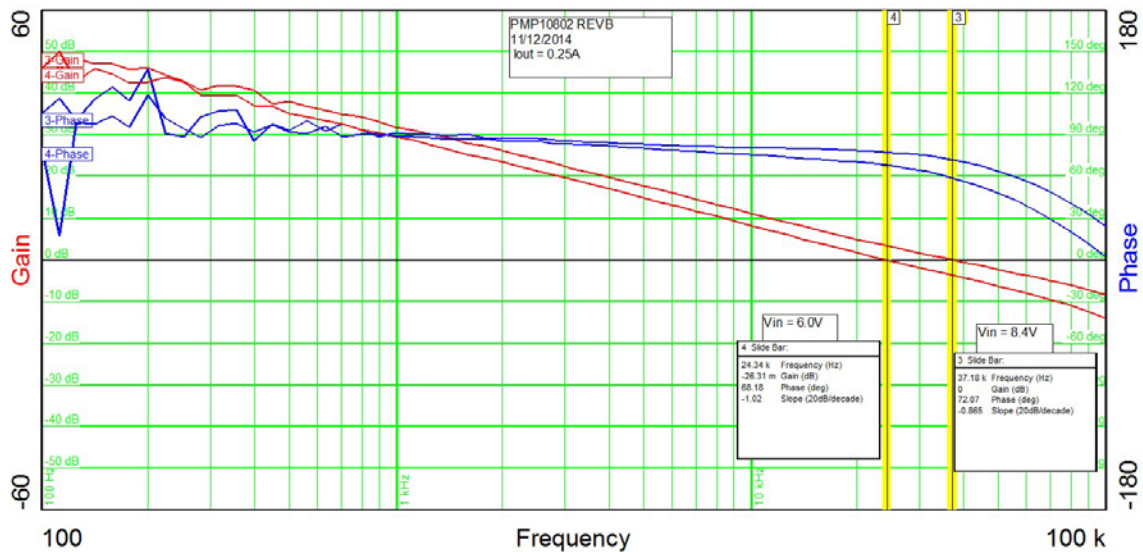Phase Margin = 68 degrees
Phase Margin = 72 degrees




7 Photo

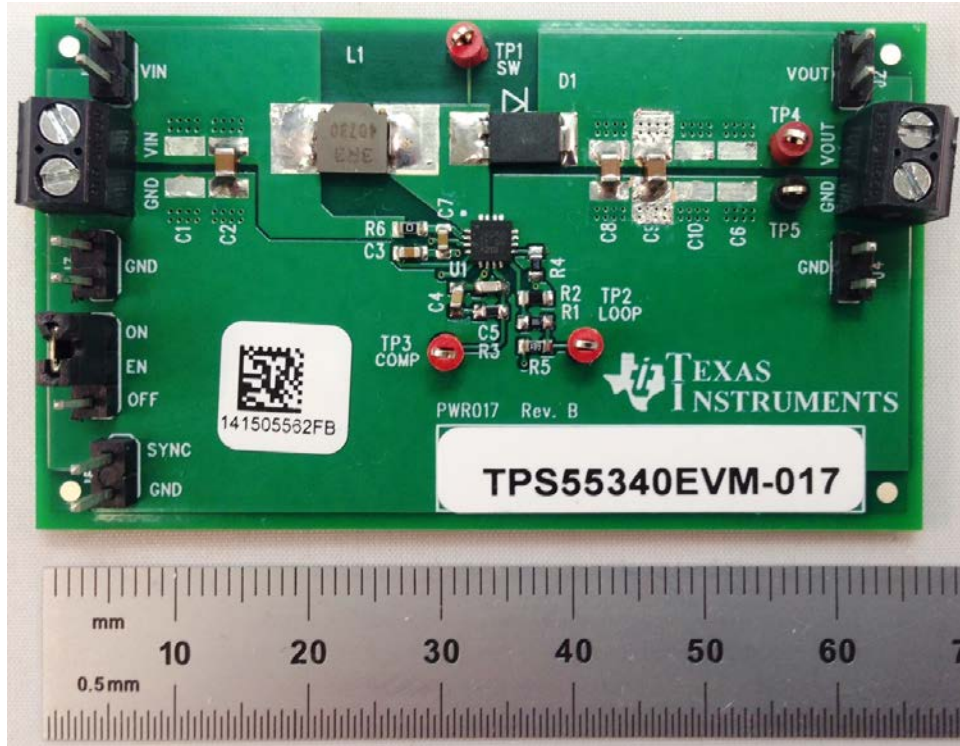The photo below shows the PMP10802 REVB assy built on the TPS55340-017 EVM.



8 Thermal Image

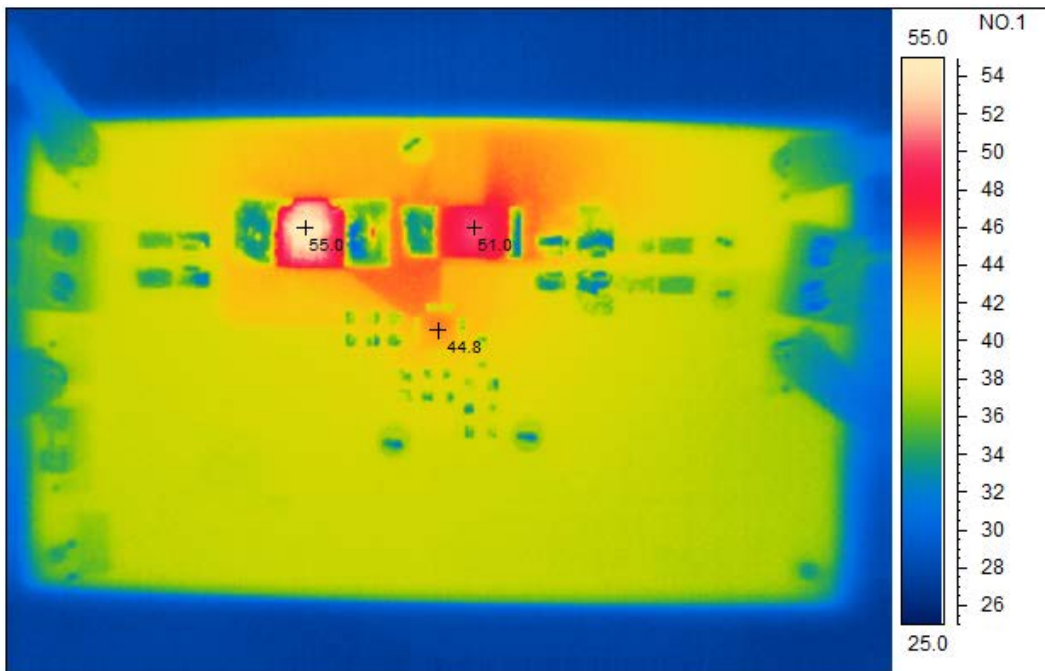The thermal image below shows sustained operation while at a 6V input / 1.2A output, with no airflow.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated