

## TI Designs: TIDA-01335

# Ultra-Small IO-Link Sensor Transmitter With RTD Front-End Reference Design



### Description

This reference design demonstrates the IO-Link communication in a small form factor of a 6-mm PCB width with integrated protection and an RTD sensor front end. The highly integrated and tiny IO-Link PHY offers ESD, EFT, and surge protection as well as reverse polarity protection. The built-in LDO and configurable output current provide easy and flexible system implementation and offers at the same time low power dissipation due to the ultra-low residual voltage. The 24-bit sigma-delta analog-to-digital converter (ADC) captures the RTD value (PT100 temperature sensor), which is converted in the MCU and sent through IO-Link to the IO-Link master.

### Resources

<a href="#">TIDA-01335</a>	Design Folder
<a href="#">TIOL111</a>	Product Folder
<a href="#">MSP430FR5738</a>	Product Folder
<a href="#">ADS1220</a>	Product Folder

### Features



- IO-Link PHY With Integrated:
  - 3.3- or 5-V LDO
  - Reverse Polarity Protection
  - ESD, EFT, and Surge Protection According to IEC 61000-4
- 50- to 350-mA Configurable Output Current Limit
- IO-Link V1.1 and V1.0 (TMG Stack)
- Small PCB Board Width of 6 mm
- RTD Performance: 0.17°C

### Applications

- [Factory Automation and Control](#)
- [Displacement Transmitter](#)
- [Temperature Transmitter](#)
- [Flow Transmitter](#)
- [Level Transmitter](#)
- [Pressure Transmitter](#)



[ASK Our E2E Experts](#)

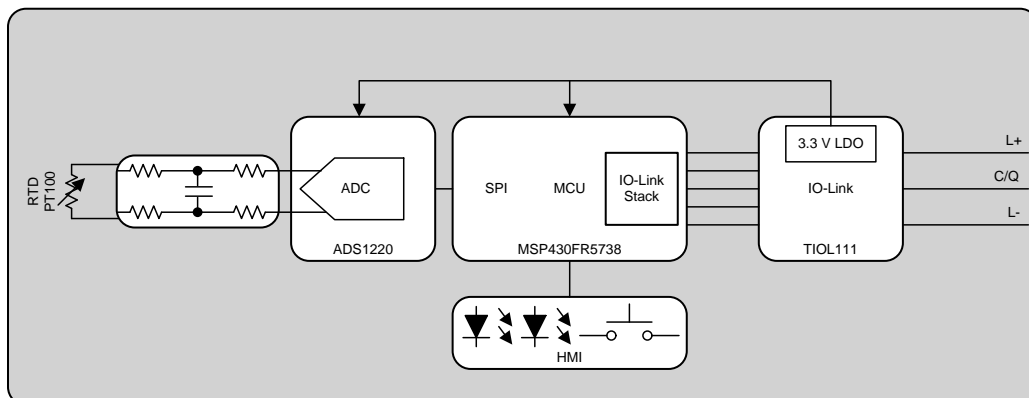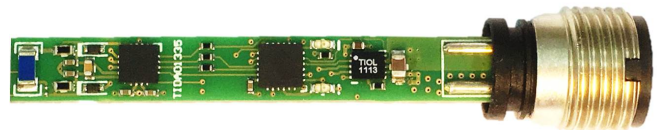

Copyright © 2017, Texas Instruments Incorporated



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

## 1 System Description

In Factory Automation and Control systems, the IO-Link interface is becoming more and more popular. Applications that usually have a switching output, either NPN or PNP, are upgraded with the IO-Link standard. With this upgrade, two possible scenarios can be addressed:

1. Extend the switching output with the capability to program and configure the field transmitter with IO-Link.
2. Completely communicate with the IO-Link protocol between the field transmitter and PLC.

For the IO-Link communication, a stack is implemented in the MCU, which is also part of this system design. To easily showcase the functionality, a resistance temperature detector (RTD) sensor (in particular, a PT100 element) is connected to the 24-bit ADC, so the sensor data is sent through the IO-Link interface. When the system is connected to an IO-Link master system, the temperature information is shown in the master software.

In addition, this reference design allows one to set a temperature threshold level either with the switch button or configured using IO-Link through the IO-Link master. Two LEDs indicating the status of the system, whether the IO-Link communication is established or in case an error occurs.

The highly integrated IO-Link PHY with a size of only 2.5 mm × 3 mm provides reverse polarity protection and helps designers meet system compliance with the International Electrotechnical Commission (IEC) 61000-4 standard. The built-in EMC protection allows for:

- ±16-kV IEC 61000-4-2 ESD Contact Discharge
- ±4-kV IEC 61000-4-4 Electrical Fast Transient (EFT)
- ±1.2-kV/500-Ω IEC 61000-4-5 Surge

With the capability of using the onboard LDO with either a 3.3-V or 5-V output, the remaining system can be supplied with up to 20 mA. In this reference design, the integrated 3.3-V LDO supplies the MCU and the 24-bit ADC with power from the voltage input, which covers a range from 7 to 36 V with a ±65-V tolerant transient.


This feature set is key for very small field transmitters, like the 6-mm wide PCB in this reference design, which easily fits in a M12-sized tube.

## 1.1 Key System Specifications

PARAMETER	SPECIFICATIONS / COMMENTS
<b>ANALOG FRONT-END</b>	
PT100	3-wire mode
Current excitation	Programmable (10, 50, 100, 250, 500, 1000, 1500 $\mu$ A)
Reference resistor	3.24 k $\Omega$ , Tol = 0.1 %, TC = 10 ppm/C
Resolution	24-bit ADC
<b>DIGITAL PROCESSING</b>	
Temperature calculation	Look up table, based on the Callendar-Van Dusen equation
IO-Link stack	TMG
	V1.1 and V1.0
	Supports COM3
<b>INTERFACE</b>	
Communication	IO-Link
SIO	NPN, PNP
	50- to 350-mA configurable current limit
<b>ALARM</b>	
Fault indicator (open drain)	Overcurrent
	Temperature
	Power supply
<b>POWER SUPPLY</b>	
Operating voltage	7- to 36-V DC
	$\pm$ 65-V transients < 100 $\mu$ s
LDO	3.3-V output voltage
	20-mA output current

## 2 System Overview

### 2.1 Block Diagram

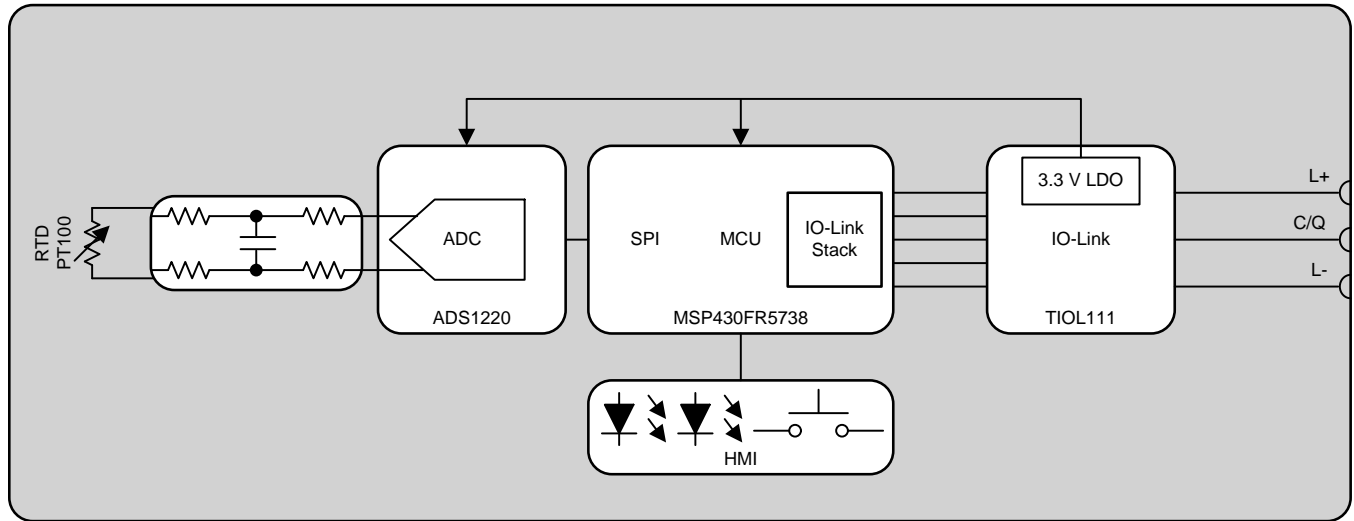

Copyright © 2017, Texas Instruments Incorporated


Figure 1. TIDA-01335 Block Diagram

## 2.2 Design Considerations

### 2.2.1 IO-Link Interface

The highly integrated IO-Link PHY TIOL111 requires only a small amount of external components. In this reference design, C10, C11, and C13 are placed at the inputs. C9 is the output capacitor of the integrated LDO, and R16 is the resistor setting the maximum output current. The two output signals WAKE and FAULT are open-drain outputs. The needed pullup resistors are inside the MSP430™.

Figure 2 shows the schematic of the IO-Link interface. J2 is the M12 connector.

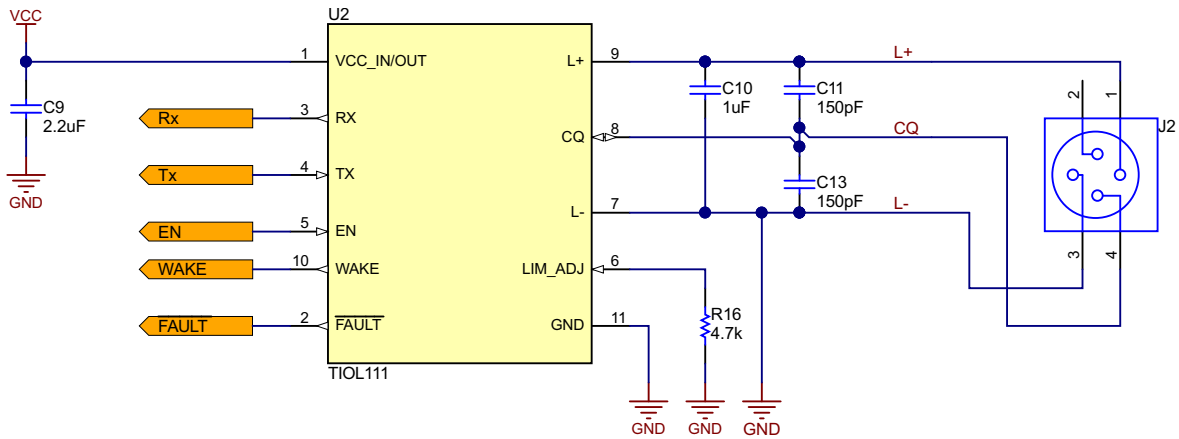

Copyright © 2017, Texas Instruments Incorporated

Figure 2. IO-Link Interface and 3.3-V Output

The TIOL111 device comes in three different versions:


- TIOL111-3: IO-Link PHY with an integrated LDO, providing 3.3 V
- TIOL111-5: IO-Link PHY with an integrated LDO, providing 5 V
- TIOL111: IO-Link PHY without an integrated LDO

This reference design uses the 3.3-V LDO version, which is capable of providing up to a 20-mA output current. This current is sufficient to power the MCU and ADC as well as to supply the LEDs.
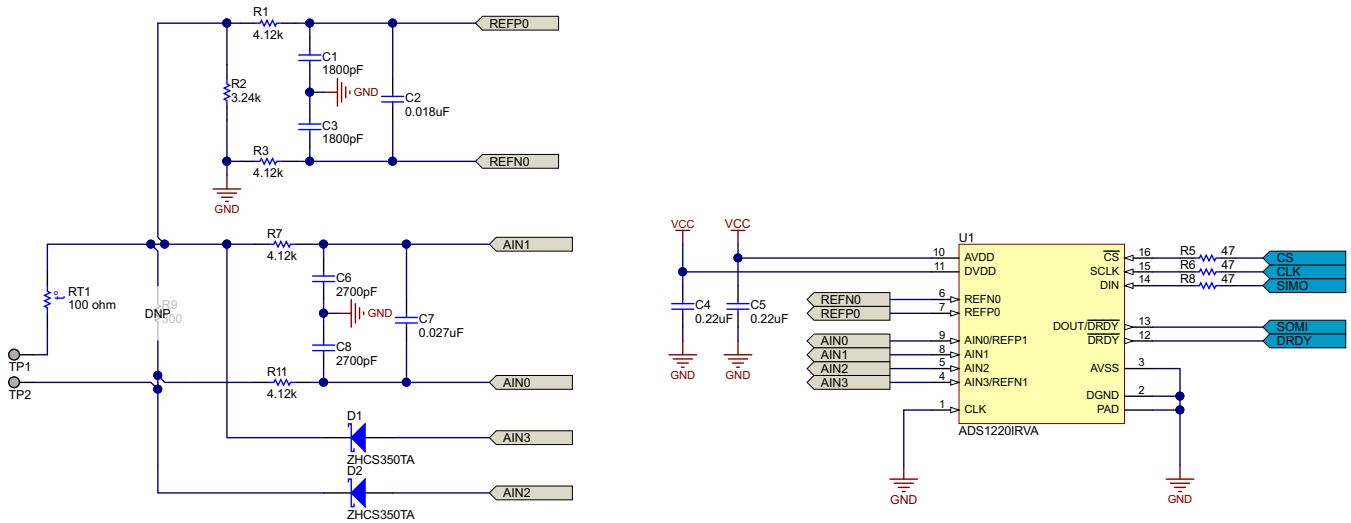
### 2.2.2 RTD Front End

The main focus of this reference design is the realization of the IO-Link interface including the IO-Link stack. To have real world sensor data to transmit using the IO-Link interface, a temperature sensor is also part of this design. The board contains a PT100 element as the temperature sensor.

For the excitation current and to measure the RTD resistance value, this reference design uses the ADS1220. With two integrated, programmable excitation current sources and a programmable PGA, the 24-bit ADC is a perfect fit in this application.



Copyright © 2017, Texas Instruments Incorporated

**Figure 3. Analog Front-End Circuitry**


Figure 3 shows the circuitry of the analog front end. Resistor R9 is only needed for calibration purposes. With  $R9 = 300 \Omega$ , it is used to run a gain calibration. For this purpose, the PT100 element has to be disconnected. This can be realized by removing the short between TP1 and TP2 once calibration is done or not needed. R9 has to be removed and TP1 shorted with TP2.

The excitation current from the ADS1220 is provided through the two diodes D1 and D2, developing a reference voltage across R2. This 3.24-k $\Omega$  precision resistor has a 0.1% tolerance with a temperature coefficient of 10 ppm/C and generates the reference voltage for the ADC, enabling a ratiometric measurement.
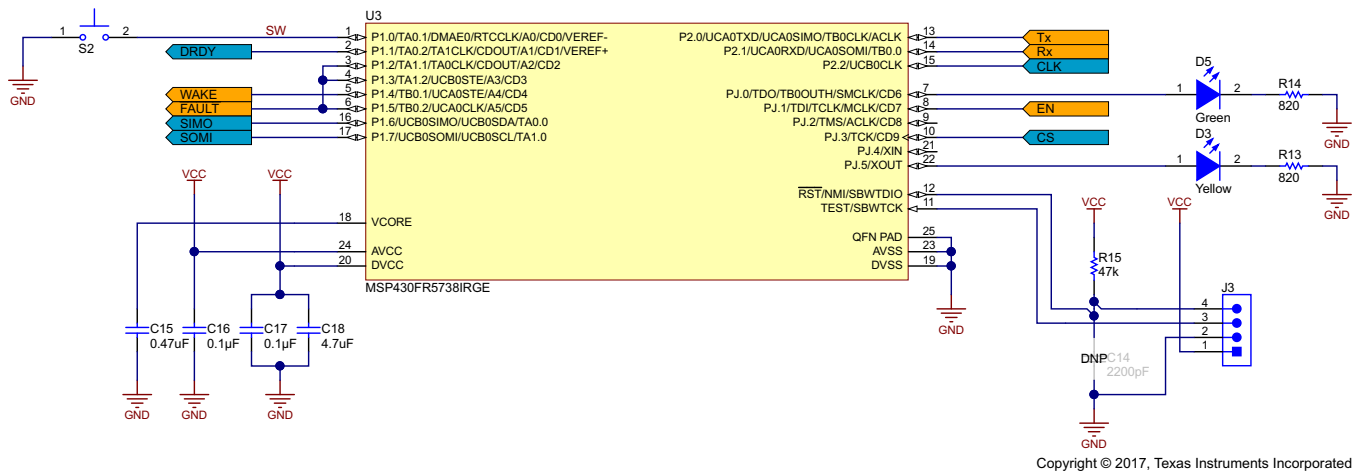
### 2.2.3 Digital Processing

For calculating the temperature, based on the measured RTD resistance, the MSP430FR5738 is part of the design. A look-up table (LUT) translates the measured voltage levels into the respective temperature values according to Calendar-Van Dusen equations. For this, the MCU gets a data set once the ADC provides the data ready (DRDY) information. Once calculated, the temperature data is transmitted through the IO-Link interface.

Also in the MSP430FR5738, the IO-Link stack is running. Once an IO-Link connection is established between the TIDA-01335 reference design and an IO-Link master, the green LED D5 is blinking. With the pushbutton S1, it is possible to set a temperature threshold. Once this threshold is reached, the information is also sent through IO-Link to the master. With the IO-Link master GUI, it is possible to read out this temperature threshold and overwrite the temperature threshold with the GUI. Figure 4 shows the schematic of the digital processing section.



Copyright © 2017, Texas Instruments Incorporated

Figure 4. Digital Processing Section

## 2.3 Highlighted Products

The following subsections detail each circuit block in the TIDA-00559 block diagram. For more information on each of these devices, see their respective product folders at [TI.com](http://ti.com).

### 2.3.1 TIOL111: IO-Link Device Transceiver With Integrated Surge Protection


The TIOL111 family of transceivers implements the IO-Link interface for industrial bidirectional, point-to-point communication. When the device is connected to an IO-Link master through a three-wire interface, the master can initiate communication and exchange data with the remote node while the TIOL111 acts as a complete physical layer for the communication.

These devices are capable of withstanding up to 1.2 kV (500  $\Omega$ ) of IEC 61000-4-5 surge and feature integrated reverse polarity protection. A simple pin-programmable interface allows easy interfacing to the controller circuits. The output current limit can be configured using an external resistor. Fault reporting and internal protection functions are provided for undervoltage, overcurrent, and overtemperature conditions.

Key features of this device include:

- 7- to 36-V supply voltage
- PNP, NPN, or IO-Link configurable output
  - IEC 61131-9 COM1, COM2, and COM3 data rate support
- Low residual voltage of 1.75 V at 250 mA
- 50- to 350-mA configurable current limit
- Tolerant to  $\pm 65$ -V transients < 100  $\mu$ s
- Reverse polarity protection of up to 55 V on L+, CQ, and L–
- Integrated EMC protection on L+ and CQ:
  - $\pm 16$ -kV IEC 61000-4-2 ESD Contact Discharge
  - $\pm 4$ -kV IEC 61000-4-4 EFT
  - $\pm 1.2$ -kV/500- $\Omega$  IEC 61000-4-5 Surge
- Fast demagnetization of inductive loads up to 1.5 H
- Large capacitive load driving capability
- < 2- $\mu$ A CQ leakage current
- < 1.5-mA quiescent supply current
- Integrated LDO options for up to 20-mA current:
  - TIOL111: No LDO
  - TIOL111-3: 3.3-V LDO
  - TIOL111-5: 5-V LDO
- Overtemperature warning and thermal protection
- Remote wake-up indicator
- Fault indicator
- Extended ambient temperature:  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$
- 2.5-mm $\times$ 3-mm 10-pin VSON package



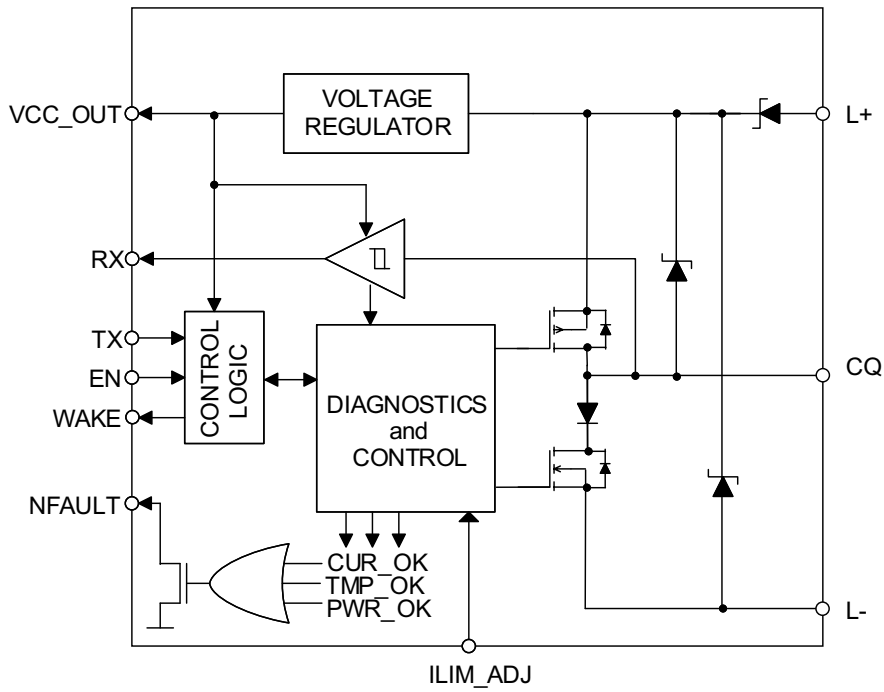

Copyright © 2016, Texas Instruments Incorporated


**Figure 5. TIOL111-3 With 3.3-V Voltage Regulator**

### 2.3.2 MSP430FR5738

The TI MSP430FR573x family of ultra-low-power microcontrollers consists of multiple devices that feature embedded FRAM nonvolatile memory, an ultra-low-power 16-bit MSP430 CPU, and different peripherals targeted for various applications. The architecture, FRAM, and peripherals, combined with seven low-power modes, are optimized to achieve extended battery life in portable and wireless sensing applications. FRAM is a new nonvolatile memory that combines the speed, flexibility, and endurance of SRAM with the stability and reliability of flash, all at lower total power consumption. Peripherals include a 10-bit ADC, a 16-channel comparator with voltage reference generation and hysteresis capabilities, three enhanced serial channels capable of I<sup>2</sup>C, SPI, or UART protocols, an internal DMA, a hardware multiplier, an RTC, five 16-bit timers, and digital I/Os.

Key features of this device include:

- Embedded MCU 16-bit RISC architecture up to 24-MHz clock:
  - Wide supply voltage range (2 to 3.6 V)
  - Optimized ultra-low-power modes (81.4  $\mu$ A/MHz in active and 320 nA in shutdown (LPM4.5))
  - Ultra-low-power ferroelectric RAM
  - 16-KB nonvolatile memory
  - Ultra-low-power writes
  - Fast write at 125 ns per word (16kB in 1 ms)
  - Built-in error coding and correction (ECC) and MPU
  - Universal memory = program + data + storage
  - 10<sup>15</sup> write cycle endurance
- Intelligent digital peripherals:
  - 32-bit hardware multiplier (MPY)
  - Three-channel internal DMA
  - RTC with calendar and alarm functions
  - 16-bit Cyclic redundancy checker (CRC)
  - High-performance analog
  - Enhanced serial communication

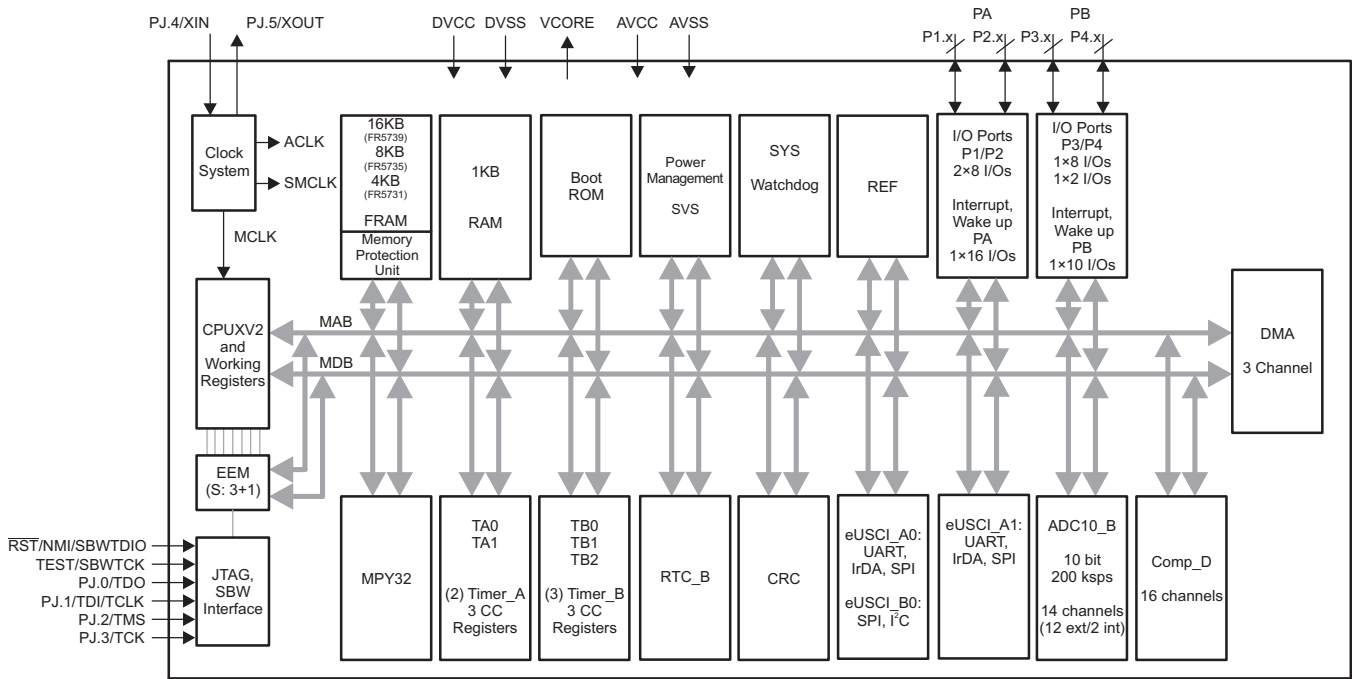

Copyright © 2016, Texas Instruments Incorporated

**Figure 6. Functional Block Diagram MSP430FR5738**

### 2.3.3 ADS1220: 24-Bit, 2kSPS, Four-Channel, Low-Power Delta-Sigma ADC With PGA and $V_{REF}$ for Small Signal Sensors


The ADS1220 is a precision, 24-bit, ADC that offers many integrated features to reduce system cost and component count in applications measuring small sensor signals. The device features two differential or four single-ended inputs through a flexible input multiplexer (MUX), a low-noise, programmable gain amplifier (PGA), two programmable excitation current sources, a voltage reference, an oscillator, a low-side switch, and a precision temperature sensor.

The device can perform conversions at data rates up to 2000 samples-per-second (SPS) with single-cycle settling. At 20 SPS, the digital filter offers simultaneous 50-Hz and 60-Hz rejection for noisy industrial applications. The internal PGA offers gains up to 128 V/V. This PGA makes the ADS1220 ideally-suited for applications measuring small sensor signals, such as RTDs, thermocouples, thermistors, and resistive bridge sensors. The device supports measurements of pseudo- or fully-differential signals when using the PGA. Alternatively, the device can be configured to bypass the internal PGA while still providing high input impedance and gains up to 4 V/V, allowing for single-ended measurements.

Power consumption is as low as 120  $\mu$ A when operating in duty-cycle mode with the PGA disabled. The ADS1220 is offered in a leadless VQFN-16 or a TSSOP-16 package and is specified over a temperature range of  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$ .

Key features of this device include:

- Low current consumption:
  - Duty-cycle mode: 120  $\mu$ A
  - Normal mode: 415  $\mu$ A
- Wide supply range: 2.3 to 5.5 V
- Programmable gain: 1 to 128 V/V
- Programmable data rates: up to 2 kSPS
- Simultaneous 50-Hz and 60-Hz rejection at 20 SPS with a single-cycle settling digital filter
- Low-noise PGA: 90 nV<sub>RMS</sub> at 20 SPS
- Dual-matched programmable current-sources: 10 to 1500  $\mu$ A
- Internal 2.048-V reference: 5 ppm/ $^{\circ}\text{C}$  (typical) drift
- Internal oscillator: 2% (maximum) accuracy
- Internal temperature sensor
- Two differential or four single-ended inputs
- SPI-compatible interface
- Package: 3.5 mm  $\times$  3.5 mm  $\times$  0.9 mm QFN

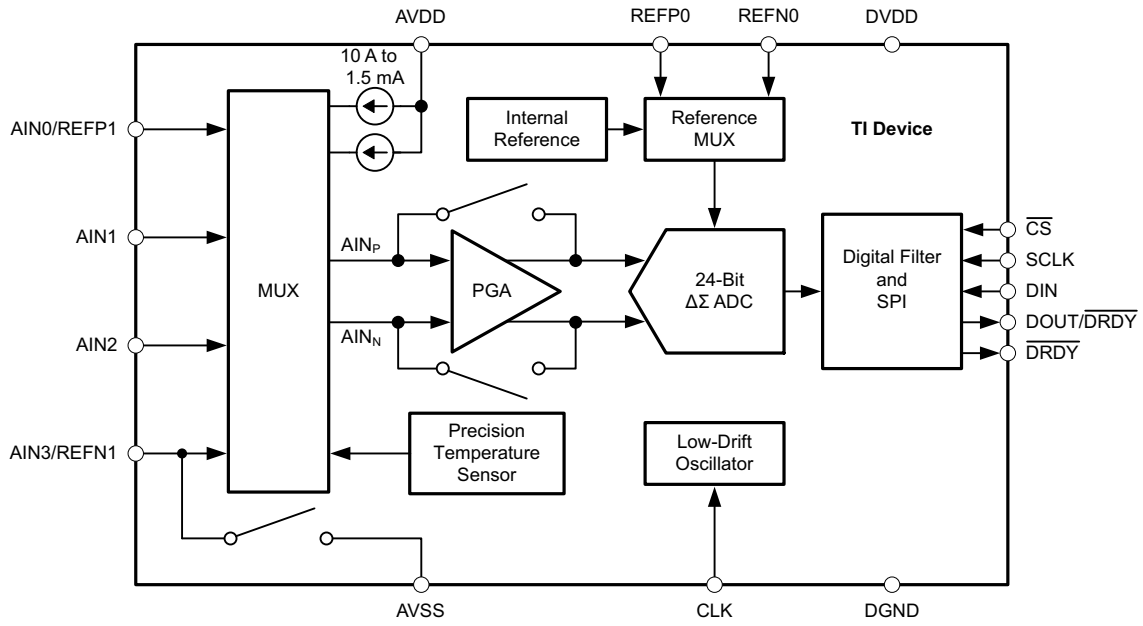


Copyright © 2016, Texas Instruments Incorporated

**Figure 7. Functional Block Diagram of ADS1220**
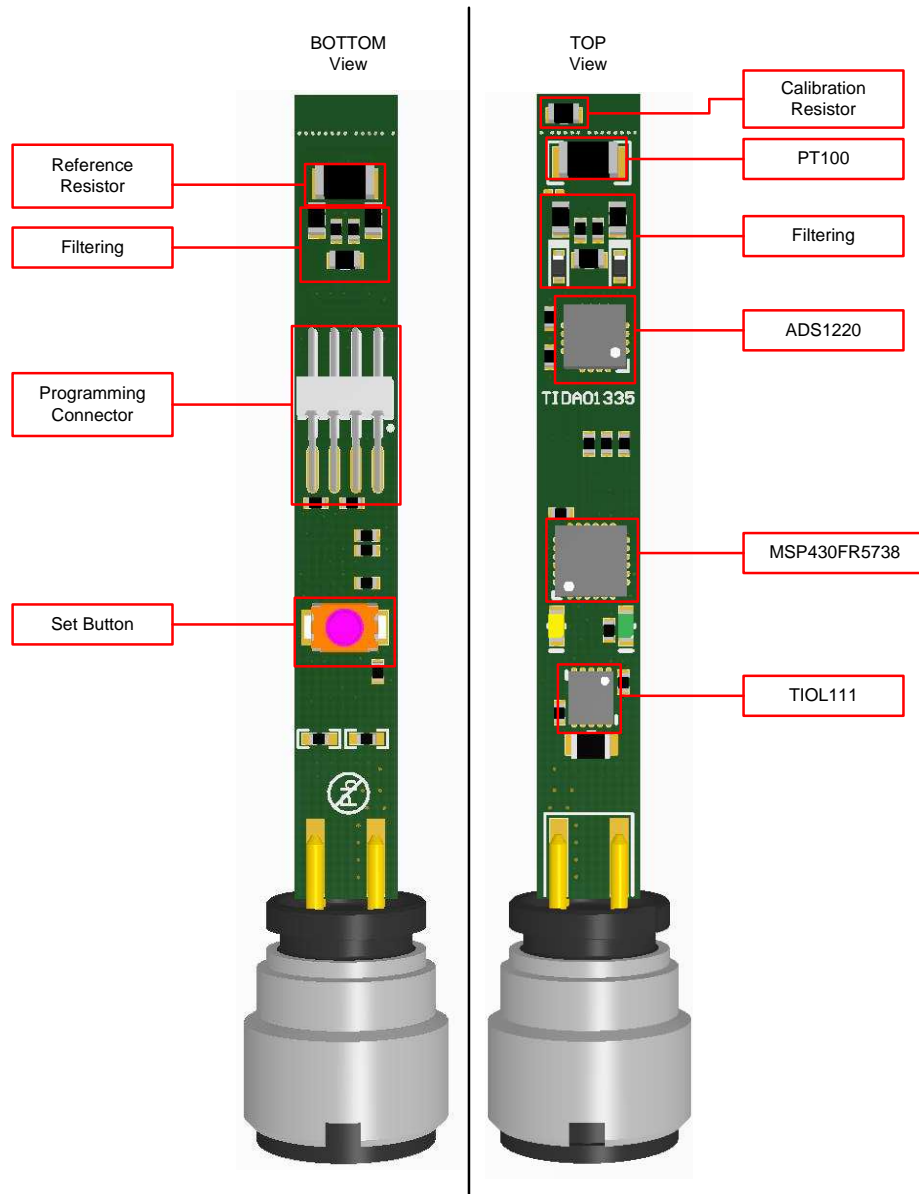
### 3 Hardware, Software, Testing Requirements, and Test Results

In [Figure 8](#), the different building blocks of TIDA-01335 are highlighted.




Copyright © 2017, Texas Instruments Incorporated

**Figure 8. TIDA-01335 Board Description**


In the bottom view:

- Reference resistor (see Figure 9): The resistor R2 is a precise reference resistor. The excitation current develops a voltage across R2, which is used as a reference voltage for the ADC. This approach allows for a ratiometric measurement. It is important to have a stable resistor because the resistor value of the RTD is a ratio to R2. In this reference design, R2 has a tolerance of 0.1% with a temperature coefficient of 10ppm/C.
- Filtering (see Figure 9)
- Programming connector (see Figure 10)
- Set button: When pressing this button, the current temperature is used as a temperature threshold. The value can also be read out using IO-Link.

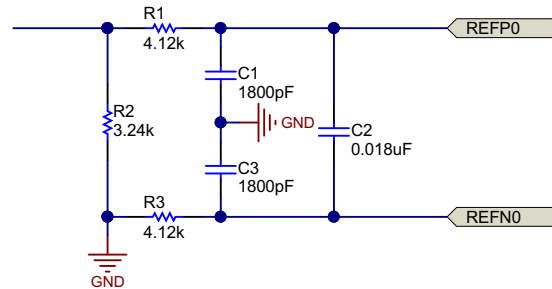

Copyright © 2017, Texas Instruments Incorporated

Figure 9. Reference Resistor and Filtering

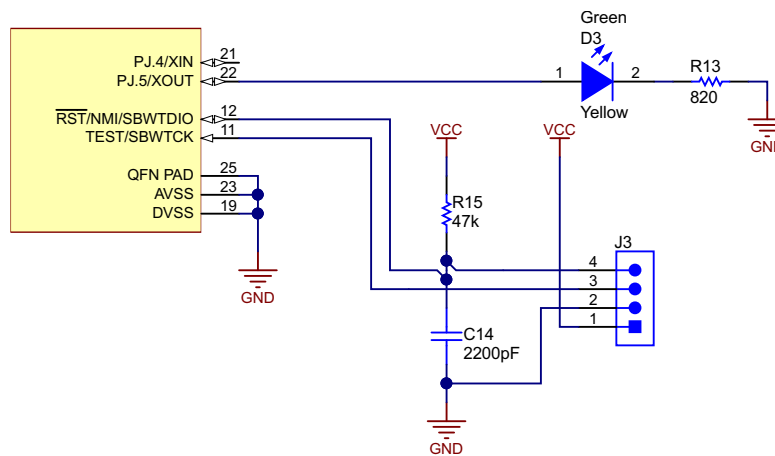

Copyright © 2017, Texas Instruments Incorporated

Figure 10. Programming Connector

In the top view:

- Calibration resistor: Resistor R9 is not populated per default. The resistor can be used for gain calibration of the ADC.
- PT100: The PT100 is the temperature sensing element.
- ADS1220: ADC to capture the voltage across the RTD
- MSP430FR5738: The MCU calculates the temperature based on the voltage across the RTD and the look-up table. The MSP430 also has the IO-Link stack for the IO-Link communication.
- TIOL111: This is the IO-Link PHY

### 3.1 Required Hardware and Software


To get the TIDA-01335 reference design up and running, the following hardware and software is needed:

- TIDA-01335 reference design
- IO-Link master:
  - Example: TMG USB IO-Link Master V2
  - Software for IO-Link master
- M12 cable to connect the reference design and IO-Link master
- MSP430 programmer
  - Example: [MSP-FET](#)
- PC
- IO-Link stack
- IO-Link IODD files
- Optional:
  - Precision reference resistor for calibrating the analog front end
  - Precision digital multimeter (DMM)

### 3.2 Testing and Results

#### 3.2.1 Test Setup

Figure 11 shows how to connect the reference design. The MSP-FET is only required for programming or debugging the MSP430. The M12 cable connects the reference design with the IO-Link master, which is also connected through USB to the PC. The PC has the IO-Link master software installed. For details on the installation of the GUI, see the user manual of the IO-Link master software.

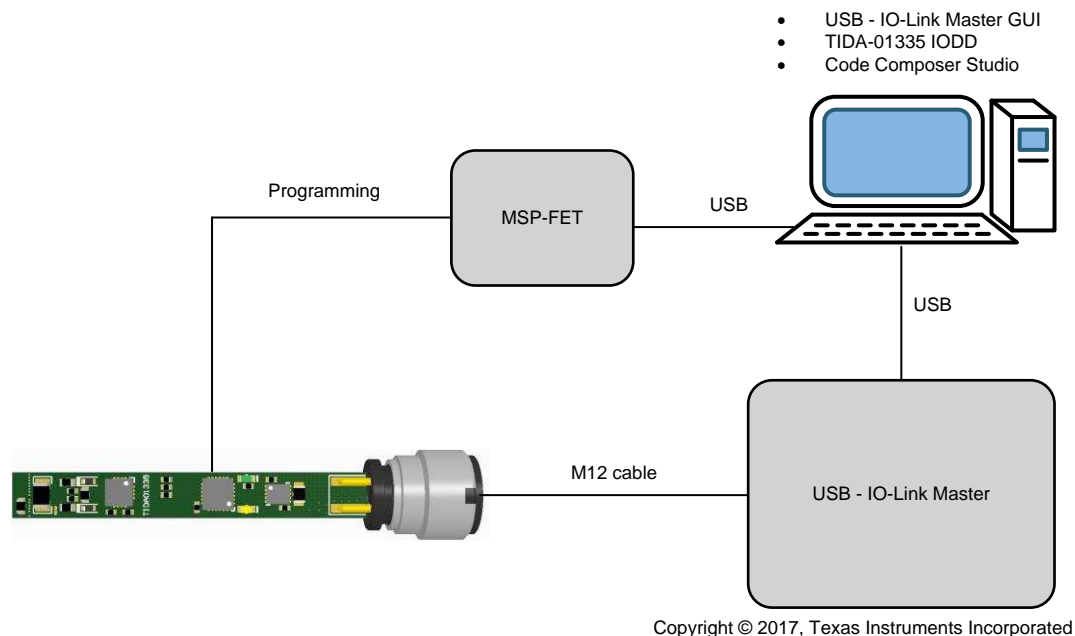

**Figure 11. Test Setup of Reference Design**



### 3.2.2 Test Results

Figure 12 through Figure 18 show the different steps to configure the IO-Link master GUI. Note that these steps are only valid for the IO-Link master used here. When the reference design is connected as per Figure 11, launch the GUI and follow these steps:

1. Click the "Search Master" button (see Figure 12).
2. Double-click in the pop-up window on the IO-Link master, which is connected to the system. Typically, this is only one entry as long as only one IO-Link master is connected to the PC (see Figure 13).
3. Drag the "TIDA-01335" IODD file and drop it in the "IO-Link" row. See the manual on how to load the specific IODD files (see Figure 14).
4. Go to the Vendor and Device information in the IO-Link row. Click on the "Go Online" button to establish a connection between the PC and the IO-Link master. If successful, the color of the button turns green (see Figure 15).
5. Double-click in the "Topology" window on "TI Design TIDA-01335" to open the details of this reference design (see Figure 16).
6. The green button in the upper left corner indicates a proper connection between the IO-Link master and IO-Link device (see Figure 17).
7. By clicking on the "Process Data" tab, the information of the reference design are shown. For this design, the temperature of the RTD sensor is shown, as well as the threshold of the low and high temperature limits (see Figure 18).

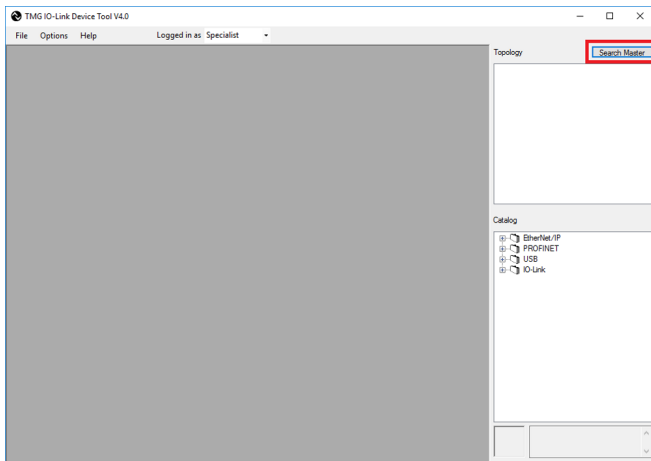


Figure 12. IO-Link Master GUI 1

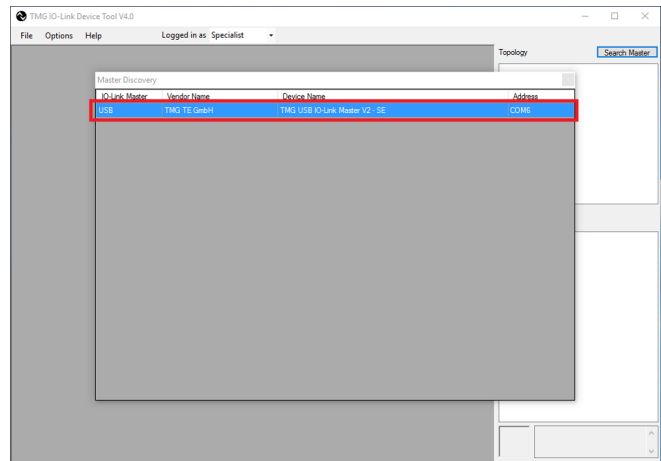


Figure 13. IO-Link Master GUI 2

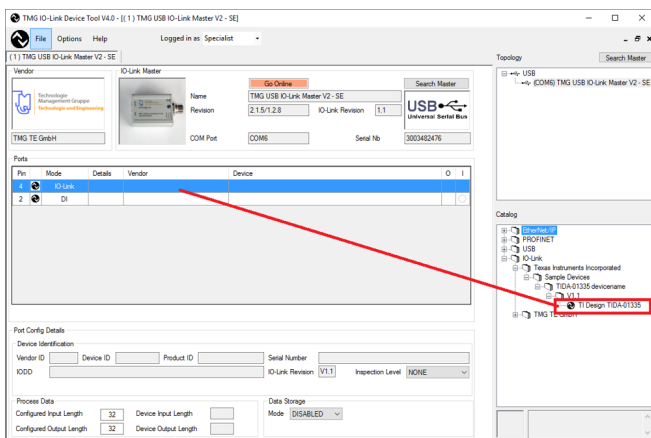


Figure 14. IO-Link Master GUI 3

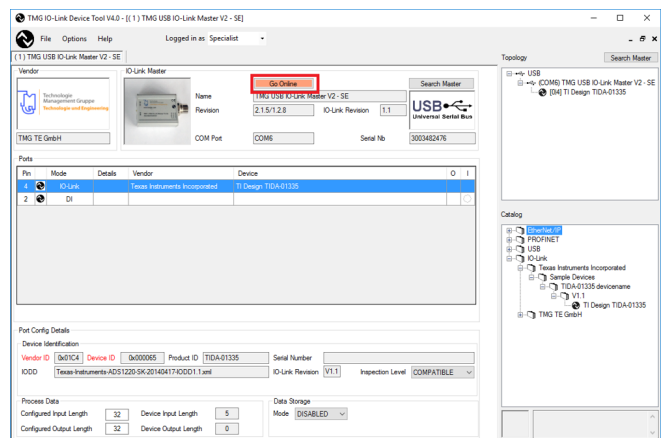


Figure 15. IO-Link Master GUI 4

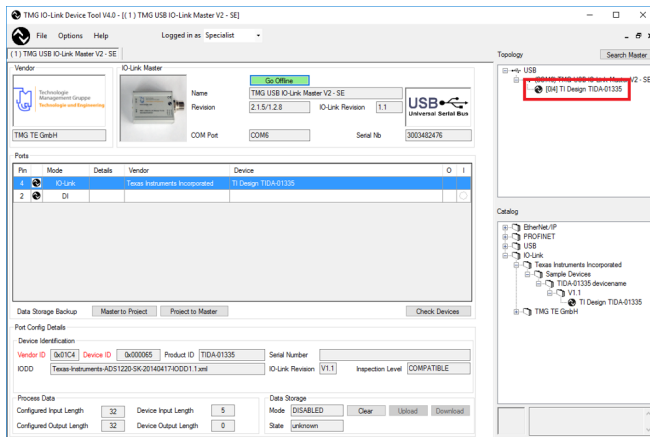


Figure 16. IO-Link Master GUI 5

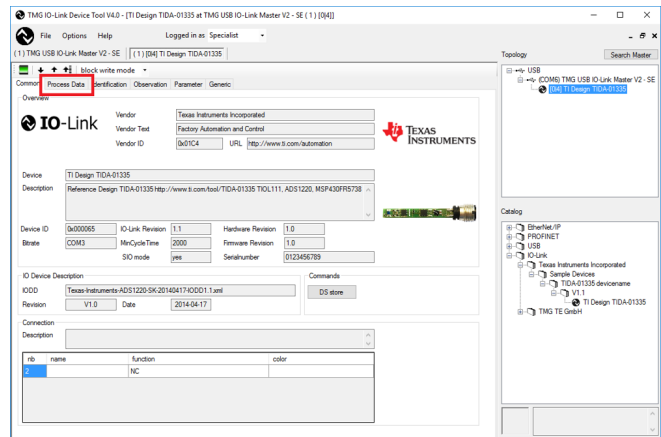


Figure 17. IO-Link Master GUI 6

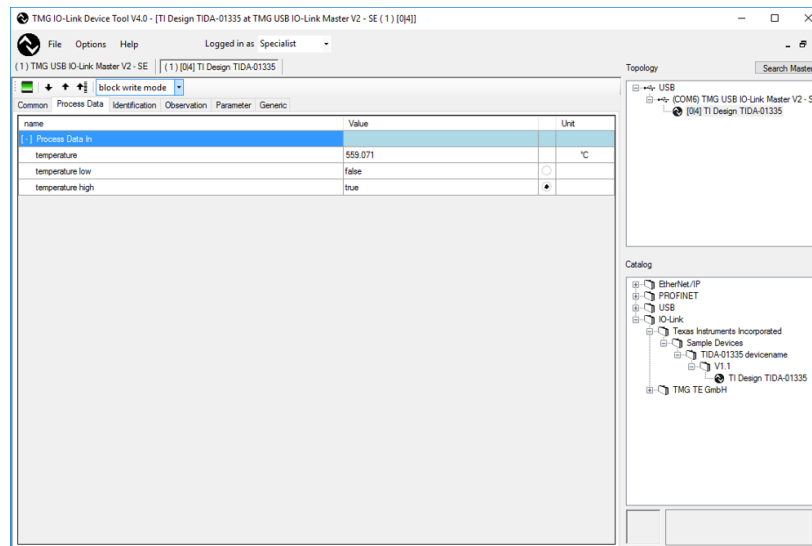


Figure 18. IO-Link Master GUI 7

## 4 Design Files

### 4.1 Schematics

To download the schematics, see the design files at [TIDA-01335](#).

### 4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01335](#).

### 4.3 PCB Layout Recommendations

#### 4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01335](#).

### 4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01335](#).

### 4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01335](#).

### 4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01335](#).

## 5 Software Files

To download the software files, see the design files at [TIDA-01335](#).

## 6 Related Documentation

This design did not use any documentation.

### 6.1 Trademarks

MSP430 is a trademark of Texas Instruments.  
All other trademarks are the property of their respective owners.

## 7 About the Author

**ALEXANDER WEILER** is a systems engineer at Texas Instruments, where he is responsible for developing reference design solutions for the industrial segment. Alexander brings to this role his extensive experience in high-speed digital, low-noise analog, and RF system-level design expertise. Alexander earned his diploma in electrical engineering (Dipl.-Ing.(FH)) from the University of Applied Science in Karlsruhe, Germany.

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated