

# TI Designs: PMP20176

## Four-Phase, 140-A Reference Design for Intel® Stratix® 10 GX FPGAs Using TPS53647



### Description

This reference design focuses on providing a compact, high-performance, multiphase solution suitable for powering Intel®Stratix® 10 GX FPGAs with a specific focus on the 1SG280-1IV variant. Integrated PMBus™ allows for easy output voltage setting and telemetry of key design parameters. The design enables programming, configuration, smart VID adjustment, and control of the power supply, while providing monitoring of input and output voltage, current, power, and temperature. TI's Fusion Digital Power™ Designer is used for programming, monitoring, validation, and characterization of the FPGA power design.

### Resources


<a href="#">PMP20176</a>	Design Folder
<a href="#">TPS53647</a>	Product Folder
<a href="#">CSD95472Q5MC</a>	Product Folder
<a href="#">Fusion Digital Power Designer</a>	Product Folder

### Features


- All Ceramic Output Capacitors
- D-CAP+™ Modulator for Superior Current-Sharing Capabilities and Transient Response
- Peak Efficiency of 91.5% at 400 kHz,  $V_{IN} = 12\text{ V}$ ,  $V_{OUT} = 0.9\text{ V}$ ,  $I_{OUT} = 60\text{ A}$
- Excellent Thermal Performance Under No Airflow Conditions
- Overvoltage, Overcurrent, and Overtemperature Protection
- PMBus Compatibility for Output Voltage Setting and Telemetry for  $V_{IN}$ ,  $V_{OUT}$ ,  $I_{OUT}$ , and Temperature
- PMBus and Pinstrapping Programming Options
 
### Applications

- [FPGA Core Rail Power](#)
- [Ethernet Switches](#)
- [Firewalls and Routers](#)
- [Telecom and Base Band Units](#)
- [Test and Measurement](#)



 Copyright © 2017, Texas Instruments Incorporated



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

## 1 System Description

The PMP20176 is a high-efficiency, power-dense design featuring a four-phase buck controller and TI's proprietary Smart Power Stages optimized for use in Intel® Stratix® 10 GX FPGA core rail applications. These FPGAs are typically used in enterprise switching, telecom infrastructure, test and measurement, and cloud computing infrastructure environments with high utilization percentages that call for the high current and fast transient response that this design provides.

A 400-kHz switching frequency maintains a thermal design current efficiency of 90.1% while a high crossover frequency of 149 kHz produces a fast transient response with no stability issues. The TPS53647 controller uses the D-CAP+™ multiphase modulator for fast transient response capabilities and tight regulation of the output voltage. The D-CAP+ modulator offers reliable current balancing between the four phases of the design that provide stability over a wide range of operating conditions and simple type-II compensation of the control loop. Additionally, the TPS53647 is compatible with TI's Smart Power Stages, such as the CSD95472 used in this design, which offer optimized driver-FET solutions for high efficiency and integrated current-monitoring circuitry. These smart power stages are responsible for saving layout area and eliminating the requirement for external current-sensing components.

Design modifications can be made in the WEBENCH® Designer if a lower-power Stratix 10 GX FPGA is used, or a different output capacitor mix is desired.


### 1.1 Key System Specifications

**Table 1. Key System Specifications**

PARAMETER	SPECIFICATIONS
Input supply	12 V $\pm$ 10%
Nominal output voltage	0.9 V
DC regulation	<1.2%
DC ripple	2% max
AC ripple	$\pm$ 5%
Maximum output current	140 A
Thermal design current	100 A
Maximum load step	75 A at 500 A/ $\mu$ s
Number of phases	Four
Switching frequency	400 kHz

## 2 System Overview

### 2.1 Block Diagram

 

Copyright © 2017, Texas Instruments Incorporated

**Figure 1. PMP20176 Block Diagram**

## 2.2 Highlighted Products

### 2.2.1 TPS53647 – Four-Phase, D-CAP+™ Step-Down Buck Controller With NVM and PMBus™ Interface for ASIC Power and High-Current Point-of-Load

**Features:**

- 8-bit selectable boot voltage through pinstrap or non-volatile memory (NVM)
- One-, two-, three-, or four-phase operation
- 1.8-V or 3.3-V compatible PMBus™ system interface for fault monitoring and voltage, current, power, and temperature telemetry
- D-CAP+ modulator and eight independent levels of overshoot and undershoot reduction for excellent transient response
- Adjustable voltage positioning
- Dynamic phase shedding with programmable current threshold
- 6x6-mm, 40-pin, QFN PowerPAD™ integrated circuit package

### 2.2.2 CSD95472Q5MC – 60-A Synchronous Buck NexFET™ Smart Power Stage With DualCool™ Package

**Features:**

- 60-A continuous current capability
- Low power loss of 2.3 W at 30 A
- High-frequency operation up to 1.25 MHz
- 3.3-V and 5-V pulse-width modulation (PWM) compatible
- Temperature-compensated bidirectional current sense
- Analog temperature output
- Integrated bootstrap diode and optimized deadtime
- 5-mm x 6-mm SON, low inductance, DualCool™ packaging

### 3 Getting Started Hardware and Software

#### 3.1 Hardware

The hardware for the design is as follows:

- 12-V supply capable of 20 A
- 5-V supply capable of 1 A
- Function generator capable of pulses with < 1- $\mu$ s rise times (optional)
- Oscilloscope with differential and passive probes
- Digital multimeter
- Three 25-A Intel Mini Load Slammers and associated control board (optional)

The function generator must be used if the onboard clock generator is not used to drive the onboard load transient generator. Intel mini load slammers can be used in place of the entire onboard load circuitry if desired.

#### 3.2 Software

This design uses TI's Digital Fusion Power Designer software.

#### 3.3 Test Setup

Figure 2 shows the PMP20176 test setup.

 


Figure 2. PMP20176 Test Setup

## 4 Test Results

### 4.1 Efficiency and Power Loss

Peak efficiencies of 91.9% ( $V_{IN} = 10.8\text{ V}$ ), 91.5% ( $V_{IN} = 12\text{ V}$ ), and 91.1% ( $V_{IN} = 13.2\text{ V}$ ) have been measured for this design, as Figure 3 shows. At a thermal design current (TDC) of 100 A, the efficiencies were 90.3%, 90.1%, and 89.9% for  $V_{IN} = 10.8\text{ V}$ , 12 V, and 13.2 V, respectively. When the load current is set to the maximum current of 140 A, the efficiency is 87.8% for  $V_{IN} = 10.8\text{ V}$ , 87.7% for  $V_{IN} = 12\text{ V}$ , and 87.6% for  $V_{IN} = 13.2\text{ V}$ . The curve in Figure 3 and Figure 4 includes the losses associated with the 5-V power stage VDD rail as well as the power losses associated with the inductors of each phase.

 


Figure 3. PMP20176 Efficiency Curves:  $V_{OUT} = 0.9\text{ V}$ , 400 kHz

 


Figure 4. PMP20176 Power Loss Curves:  $V_{OUT} = 0.9\text{ V}$ , 400 kHz

## 4.2 Phase Ringing and Loop Stability

To ensure that the power MOSFETs inside the CSD95472 are not being damaged during normal operation, the phase nodes are probed at various output currents to ensure that any ringing is safely within the data sheet limits. No anomalies were observed during testing and Figure 5 shows one such measurement with the load current set to 40 A. A peak voltage of 20.7 V with a duration of < 10 ns is measured, which places the ringing safely within the data sheet limits. Figure 6 provides the results for measuring the switching frequency and shows it to be within the data sheet limits with no double pulsing or excessive jitter, which indicate that the system is stable.

To check the stability further, the control loop bode plot is obtained using a network analyzer with 49° of phase margin being measured at the 149-kHz unity gain frequency (see Figure 7).

 


Figure 5. Phase Node Ringing With 40-A Load

 


Figure 6. Phase Node Pulses

 


Figure 7. Bode Plot: 50-A Load,  $V_{IN} = 12$  V

### 4.3 Thermal Performance

The design was placed in a 25°C environment under 100-A and 140-A loads at an output voltage of 0.9 V until it reached thermal equilibrium before taking measurements of the power stages and inductors using an infrared camera. Neither airflow or heatsinks are used at the TDC current to test a worst-case scenario. A setup more closely mimicking an end application was used when the 140-A current was applied.

 


Figure 8. 100-A Load Thermal Performance, No Airflow

 


Figure 9. 140-A Load Thermal Performance, ≈350 LFM

### 4.4 Transient Response

A load step of 75 A was applied to the TPS53647 regulator under two test conditions. The first test condition is from 4 A to 79 A and the second test condition is from 65 A to the maximum load of 140 A. Under both conditions the load frequency was swept from 1 kHz to 1 MHz to check the stability under a wider range of operational corners. With no DC load line and an AC tolerance of  $\pm 5\%$ , a peak-to-peak voltage swing of 90 mVpp is allowed at the nominal output voltage of 0.9 V. No stability issues were observed during testing and the output voltage remained within the regulation window.

 


Figure 10. 4-A to 79-A Transient, 1-kHz Load Frequency

 


Figure 11. 4-A to 79-A Transient, 1-MHz Load Frequency

 


Figure 12. 65-A to 140-A Transient, 1-kHz Load Frequency

 


Figure 13. 65-A to 140-A Transient, 1-MHz Load Frequency

Table 2. Transient Response Validation Results

LOAD STEP	TRANSIENT SPECIFICATION AT NOMINAL OUTPUT VOLTAGE	MEASURED RESULTS
4 A to 79 A, 1 kHz	90 mV <sub>pp</sub>	82 mV <sub>pp</sub>
4 A to 79 A, 1 MHz	90 mV <sub>pp</sub>	62 mV <sub>pp</sub>
65 A to 140 A, 1 kHz	90 mV <sub>pp</sub>	86.7 mV <sub>pp</sub>
65 A to 140 A, 1 MHz	90 mV <sub>pp</sub>	31.3 mV <sub>pp</sub>

#### 4.5 Start-Up and Shutdown

Start-up and shutdown waveforms were taken at 4-A and 100-A loads while monitoring the enable, output voltage, and power good signals. For the high-current shutdown scenario,  $V_{OUT}$  is dragged below ground because the electronic load attached to the output of the regulator tries to maintain the 100-A load. Such behavior does not occur in real applications.

In the following scopeshots, C2 is the Enable signal, C3 is the  $V_{OUT}$  signal, and C4 is the PGOOD signal.

 


Figure 14. 4-A Start-Up

 


Figure 15. 4-A Shutdown

 


Figure 16. 100-A Start-Up

 


Figure 17. 100-A Shutdown

### 4.6 Protection Circuitry

The TPS53647 device also performed admirably when testing the on-chip protection mechanisms for this application. The overcurrent and overtemperature protection features work as intended when triggered and prevent the load and power stages from damage. Upon hitting the overcurrent limit, the controller enters hiccup mode and attempts to restart. Figure 18 shows a single shutdown and Figure 19 shows the hiccup mode. A successful power-up only occurred after removing the high current. After the overtemperature threshold was crossed, the output voltage decayed to 0 V (according to the load current) until the part had cooled off and a restart was triggered. In Figure 20 and Figure 21, a recovery time of 12 seconds was observed after the overtemperature fault occurred. For all testing, the PGOOD signal toggles low when the event occurs to signal a fault until  $V_{OUT}$  is brought back into regulation.

During overcurrent events,  $V_{OUT}$  is dragged below ground because the electronic load attached to the output of the regulator tries to maintain the load. Such behavior does not occur in real applications.

In the following scopeshots, C2 is the  $V_{OUT}$  signal and C4 is the PGOOD signal.

 


Figure 18. Single Overcurrent Shutdown

 


Figure 19. Overcurrent Shutdown With Hiccup Mode

 


Figure 20. Single Overcurrent Shutdown as Seen in Fusion GUI

 


Figure 21. Overtemperature Shutdown With Recovery

 


Figure 22. Overtemperature Shutdown and Recovery as Seen in Fusion GUI

## 5 VOUT\_COMMAND Alignment Procedure Between FPGA and TPS53647

The TPS53647 supports Intel's VR12.0/12.5 VID (Voltage Identification) tables while Stratix 10 chips support the SmartVID 10-mV step VID table. With the FPGA default settings its VID codes don't match those of the TPS53647. For the testing in this report TI's software and USB-TO-GPIO cable were used so there was no conflict. In a real application however, the FPGA and TPS53647 must be configured properly in order to enable correct output voltage positioning between devices.

1. Ensure the TPS53647 is set up to use the Intel VR12.5 VID Table through either the correct pin-strap resistor or via NVM programming
  - a. See Section 7.5 on page 31 of the controller datasheet for more information on programming the TPS53647
2. Using Intel's Quartus Prime Software, configure the FPGA to use the PMBus Direct Format
  - a. Contact Intel support for the procedure if exact steps are needed
3. Set the proper Direct Coefficients (M, B, and R) to select the correct scaling and offset values such that the SmartVID block of the FPGA follows the VR12.5 VID Table
  - a.  $M = 0x0064$  (100d),  $B = 0xFFCF$  (-49d),  $R = 0x0000$  (0d)
  - b. Note VID Code 0 (0.00V) is not supported
  - c. Refer to Table 1 on page 25 of the TPS53647 datasheet for the VR12.5 VID Table

## 6 Design Files

### 6.1 Schematics

To download the schematics, see the design files at [PMP20176](#).

### 6.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [PMP20176](#).

### 6.3 PCB Layout Recommendations

Follow all the layout instructions as specified in the respective data sheet for each part when laying out a design using the TPS53647 controller and CSD95472 Smart Power Stage. Some other guidelines to consider include:

- Keep the layout for all four phases identical to ensure optimal current balancing and thermal performance between phases.
- Route noisy traces such as PWM and the PMBus lines on a separate layer than the sensitive analog sense lines such as VSP, VSN, COMP, IMON, and so forth.
- Use quality capacitors for both the input and output decoupling to obtain the maximum performance possible with respect to DC ripple and transient response. Capacitors must be voltage rated to at least 16 V on  $V_{IN}$  and 2.5 V on  $V_{OUT}$  with a dielectric rating of X5R or better.
- Ensure that the VOUT and GND nodes are routed on multiple layers of copper and connected with enough vias to handle the current requirements for the best thermal performance. Following this guideline allows for the maximum amount of heat to flow out of the power stages and inductors into the board.

#### 6.3.1 Layout Prints

To download the layer plots, see the design files at [PMP20176](#).

### 6.4 Gerber Files

To download the Gerber files, see the design files at [PMP20176](#).

### 6.5 Assembly Drawings

To download the assembly drawings, see the design files at [PMP20176](#).

## 7 Software Files

To download the Fusion Digital Power Designer software, see the following [tool folder](#).

## 8 Related Documentation

1. Texas Instruments, [TPS53647 4-Phase, D-CAP+, Step-Down, Buck Controller with NVM and PMBus™ Interface for ASIC Power and High-Current Point-of-Load](#), TPS53647 Data Sheet (SLUSC39)
2. Texas Instruments, [CSD95472Q5MC Synchronous Buck NexFET™ Smart Power Stage](#), CSD95472Q5MC Data Sheet (SLPS599)
3. Intel, [Intel® Arria® 10 GX, GT, and SX Device Family Pin Connection Guidelines](#), PCG-01017 ([https://www.altera.com/content/dam/altera-www/global/en\\_US/pdfs/literature/dp/arria-10/pcg-01017.pdf](https://www.altera.com/content/dam/altera-www/global/en_US/pdfs/literature/dp/arria-10/pcg-01017.pdf))
4. Intel, [Power Reduction Features in Arria 10 Devices](#), AN-711 ([https://www.altera.com/content/dam/altera-www/global/en\\_US/pdfs/literature/an/an711.pdf](https://www.altera.com/content/dam/altera-www/global/en_US/pdfs/literature/an/an711.pdf))
5. Intel, [SmartVID Controller IP Core User Guide](#), UG-SVID ([https://www.altera.com/content/dam/alterawww/global/en\\_US/pdfs/literature/ug/ug\\_smartvid.pdf](https://www.altera.com/content/dam/alterawww/global/en_US/pdfs/literature/ug/ug_smartvid.pdf))
6. Intel, [25A Mini Slammer](#), Product Page ([https://designintools.intel.com/25A\\_Mini\\_Slammer\\_p/q6uj9a00ms25.htm](https://designintools.intel.com/25A_Mini_Slammer_p/q6uj9a00ms25.htm))

### 8.1 Trademarks

Fusion Digital Power, D-CAP+, PowerPAD, DualCool are trademarks of Texas Instruments. WEBENCH is a registered trademark of Texas Instruments. Intel, Stratix are registered trademarks of Intel Corporation. PMBus is a trademark of SMIF, Inc.

### Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

**Changes from A Revision (November 2017) to B Revision** **Page**

- Added [Section 5](#) ..... 17

**Changes from Original (August 2017) to A Revision** **Page**

- Updated to specify Stratix® 10 FPGAs with 1SG280-11V variant instead of SG2800-11V ..... 1

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated