

TI Designs - Precision: Verified Design

Single-Supply Analog Input Module Reference Design with 16-Bit, 8-Channel ADC for PLC



TI Designs–Precision

TI Designs–Precision are analog solutions created by TI's analog experts. Verified Designs offer the theory, component selection, simulation, complete printed circuit board (PCB) schematic and layout, bill of materials, and measured performance of useful circuits. Circuit modifications that help to meet alternate design goals are also discussed.

Design Resources



Design Archive	All design files
TINA-TI	SPICE simulator
ADS8688	Product folder
INA333	Product folder
OPA320	Product folder
OPA376	Product folder

Circuit Description

This design is for a 16-bit, 8-channel analog input module for industrial programmable logic controller (PLC) systems. The circuit is realized with an 8-channel, 16-bit, successive-approximation-register (SAR), analog-to-digital converter (ADC) with an integrated precision reference and analog front-end (AFE) circuit. The design explains the design process for implementing different voltage ranges, different current ranges, and temperature inputs for industrial PLC systems.



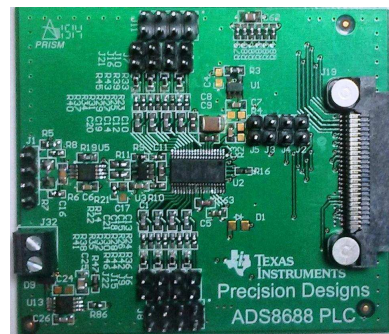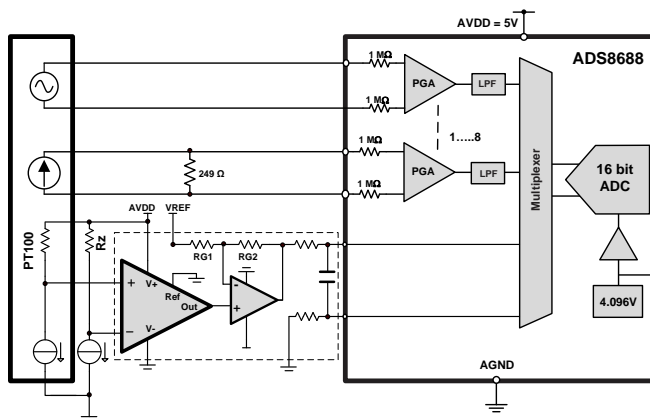[Ask The Analog Experts](#)
 TINA-TI®
 WEBENCH® [Design Center](#)
[TI Precision Designs Library](#)



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

TINA-TI is a trademark of Texas Instruments, Inc.
 WEBENCH is a registered trademark of Texas Instruments, Inc.
 TINA-TI is a registered trademark of Texas Instruments.

1 Design Summary

The primary objective is to design a single-supply (5 V), 8-channel, analog input module. This design can be used to measure bipolar voltage ranges of ± 10 V, ± 5 V, and ± 2.5 V, unipolar voltage ranges of 0 V to 5 V and 0 V to 10 V, a bipolar current range of ± 20 mA, and a unipolar current range of 4 mA to 20 mA. The design also has a provision to measure temperature using resistance temperature detectors (RTDs). The key specifications of the design are:

- System supply voltage: 5.5 V dc to 40 V dc
- ADC supply voltage (AVDD): 5 V dc
- Digital supply voltage (DVDD): 3.3 V dc
- Response time (for the ADC): 2 μ s
- System input signal:
 - Voltage inputs: ± 10 V, ± 5 V, ± 2.5 V, 0 V to 5 V, 0 V to 10 V
 - Current inputs: 4 mA to 20 mA, ± 20 -mA dc current
 - Temperature input: Pt100 RTD (a 200- Ω potentiometer is used to simulate an RTD).

The design goals and performance are summarized in [Table 1](#). The measured ac performance for voltage inputs (± 10 V) is illustrated in [Figure 1](#).

Table 1. Comparison of Design Goal, Simulation, and Measured Performance

PARAMETER		GOAL	SIMULATED, CALCULATED	MEASURED
VOLTAGE INPUTS				
Total error (% FSR), without calibration	For voltage ranges of ± 10 V	$\pm 0.1\%$	$\pm 0.056\%$	0.042%
Calibrated error		$\pm 0.05\%$	—	0.002%
CURRENT INPUTS				
Total error (% FSR), without calibration	For current ranges of ± 20 mA	$\pm 0.15\%$	$\pm 0.122\%$	0.028%
Calibrated error		$\pm 0.05\%$	—	0.007%
TEMPERATURE INPUT				
Total error ($^{\circ}$ C), without calibration	For temperature ranges of -40° C to 160° C	$\pm 2^{\circ}$ C	$\pm 1.56^{\circ}$ C	1.4 $^{\circ}$ C
Calibrated error		$\pm 0.5^{\circ}$ C	—	0.38 $^{\circ}$ C

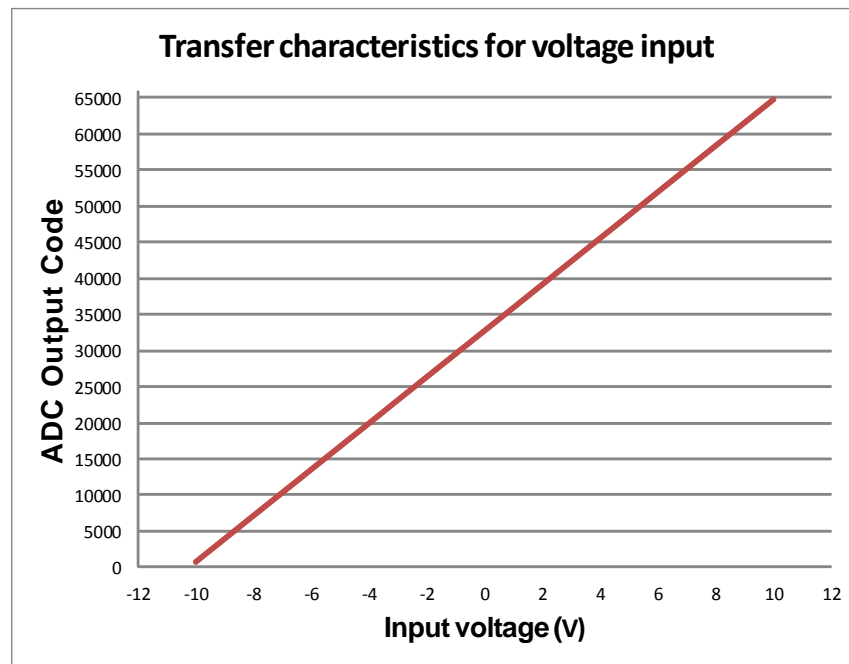


Figure 1. Transfer Characteristics for the ± 10 -V Voltage Input Range

2 Theory of Operation

2.1 Overview of the Programmable Logic Controller (PLC)

The PLC is a programmable logic controller used to control industrial processes and machines. A basic PLC system consists of an analog input module, a CPU, and an analog output module. The analog input module interfaces with sensors (pressure, temperature, flow, and so forth) and converts the analog sensor output into digital. The CPU processes these digital values and provides a digital output that is converted by the analog output module for the actuators to control the industrial process. An example block diagram for the PLC is shown in Figure 2.

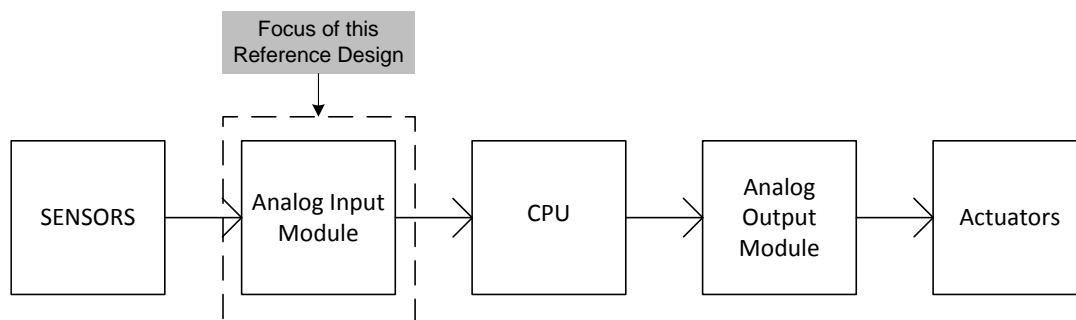


Figure 2. Example Block Diagram for the PLC

The input for the analog input module can be as small as 10 mV from temperature sensors and can be as high as ± 10 V from actuator controllers. The analog input module consists of a signal-conditioning circuit for filtering and amplification (or attenuation) of input signals, an ADC for conversion of analog signals into digital, and a circuit for isolation from the CPU and power-supply circuit.

The outputs of the analog output module are either the voltage outputs of ± 10 V, ± 5 V, 0 V to 10 V, and 0 V to 5 V for controlling the relays and actuators or are current outputs of ± 20 mA, 0 mA to 20 mA, and 4 mA to 20 mA for process control. The analog output module consists of a digital-to-analog converter (DAC) for converting digital values from the CPU to analog, a signal-conditioning circuit to bring the output of the DAC to the desired voltage or current output range, and an isolation circuit for isolation from the CPU and power-supply circuit.

2.2 Analog Input Module

This TI Design discusses the design of a single-supply analog input module for the PLC. The key requirements for the analog input module for the PLC are high-voltage inputs and high-input impedance. Typically, a resolution of 12 to 16 bits with an overall accuracy of 0.1% to 0.2% is required for the analog input modules. Figure 3 shows the block diagram for the analog input module.

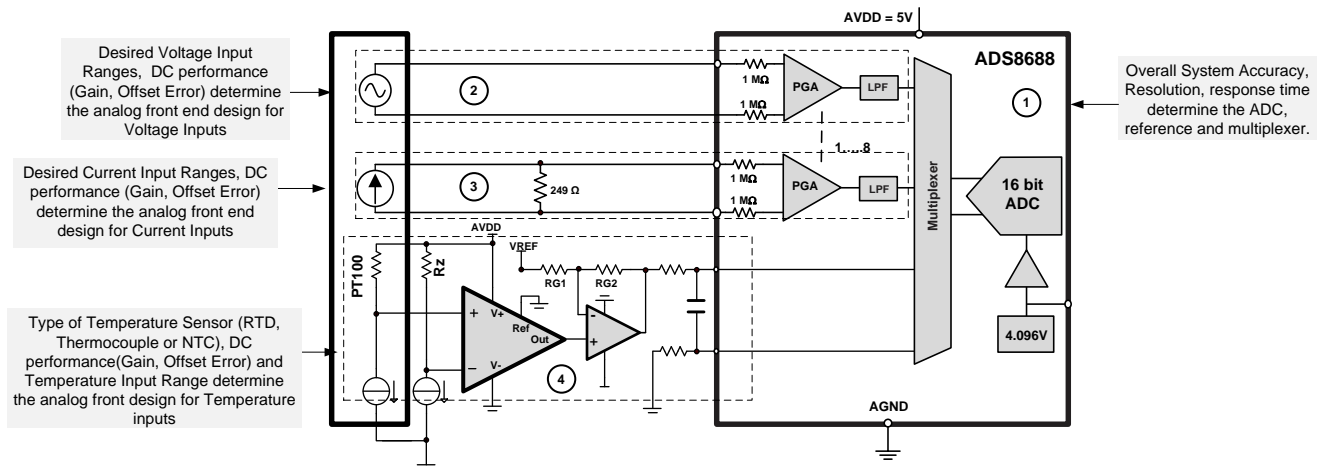


Figure 3. Block Diagram for the Analog Input Module

2.3 Considerations for Selecting the Architecture of the Analog Input Module

The analog input module for the PLC is generally used to measure the output of pressure sensors, rotatory encoders, proximity switches, temperature sensors, and so forth. These sensors are installed in the field to measure process variables (such as temperature, pressure, flow, and so forth) and the output of these sensors is either voltage or current output. Design the analog input module to measure the voltage and current outputs from these sensors.

A 24-V power bus is generally available for powering the analog input module. The 24-V field power bus can typically vary from 20 V to 30 V and can have transients up to 42 V. The noise or ripple on a 24-V bus can potentially couple in to input through the AFE or through the ADC. Therefore, an AFE and an ADC with high PSRR are preferred for the analog input module and a low-noise converter or linear regulator with transient immunity up to 42 V is used for powering analog input modules.

With the increasing number of input channels per module, the power and space available per channel is reduced. The analog input module for the PLC must measure an input voltage of ± 10 V and a traditional AFE requires a bipolar supply (± 15 V or ± 12 V) to measure a signal of ± 10 V. To generate a bipolar supply, an additional power converter is required. The additional power converter increases the power and space requirements of the analog input module. An AFE and ADC operating on a single supply (for example, 5 V) eliminates the need for an additional power converter and helps in reducing the space and power requirements for the analog input module.

System design goals (such as response time, resolution, accuracy, power consumption, and size) decide the architecture for the analog input module.

The processing cycle for a conventional PLC system is shown in [Figure 4](#).

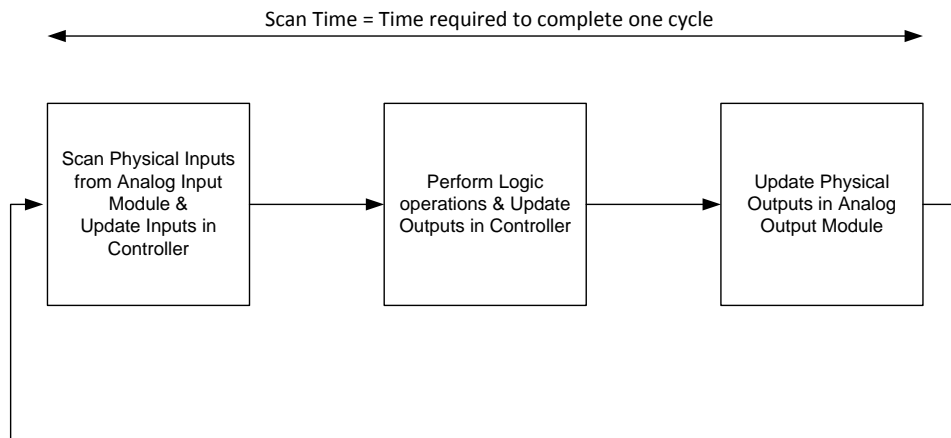


Figure 4. PLC Process Cycle

2.3.1 Scan Time

Scan time is the time difference between two consecutive readings that the PLC controller takes from a particular analog input channel. Scan time is typically the sum of response times of individual blocks of the PLC system. Scan time is generally in the order from a few milliseconds to 100 milliseconds. As the throughput per channel of the analog input module decreases, the scan time achieved for the PLC system increases.

2.3.2 Architectures for Analog Input Module

There can be two architectures for designing the analog input module for a PLC:

- Simultaneous sampling with a separate ADC for each channel.
Simultaneous sampling is useful in systems that require signals to be sampled at the same instant. Because a separate ADC is used for each channel, the throughput (samples per second) from each channel is equal to the throughput of the ADC and the total throughput achieved from this architecture is the sum of the throughput of the ADCs on each channel. Power measurement is a common application in simultaneous sampling. Current and voltage signals are simultaneously sampled for calculating power. Simultaneous sampling requires an ADC for each channel, which leads to larger circuit size and higher power consumption.
- Single ADC with multiplexed inputs.
A single ADC with multiplexed inputs samples the signal on each channel one by one in a sequence. The total throughput achieved from this architecture is the throughput of the ADC. The throughput of the ADC is divided among all the channels and the throughput per channel gets reduced. This architecture requires one ADC, one multiplexer, and multiple AFEs. This architecture generally has lower power and smaller circuit size than a simultaneous sampling architecture.

The second architecture is selected for this design report for its lower power consumption and smaller solution size. Because the throughput per channel in the second architecture with a single ADC gets reduced, an ADC with higher throughput is required to meet the scan time requirement. A SAR ADC with a sufficient throughput (> 100 kSPS, typically) is able to meet the scan time requirement of a typical PLC system.

2.4 Design Considerations for Voltage Inputs

The key requirement for the voltage inputs of an analog input module for the PLC is that they must accept voltage ranges of ± 10 V, ± 5 V, and ± 2.5 V. Because the analog input module has a single ADC for all the input ranges, a programmable gain amplifier (PGA) is required to scale and level shift the signals to the analog input ranges of the ADC. The PGA also scales the input signals to within the supply voltage and makes the operation of the analog input module possible on a single supply. Figure 5 provides the simplified circuit of a PGA and Equation 1 gives the dc transfer function of a PGA.

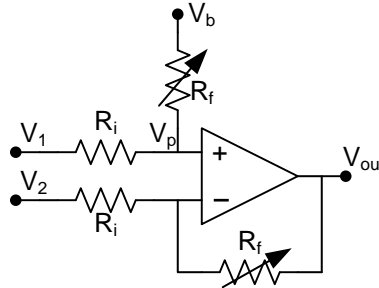


Figure 5. Simplified Circuit for a PGA

$$V_{out} = \frac{R_f}{R_i} \times (V_1 - V_2) + V_b$$

where:

- V_1, V_2 are input voltages to the PGA, and
- V_b is the bias voltage to level shift the output of the PGA.

(1)

The ADC output code can be calculated from Equation 2:

$$\text{ADC_Output_Code} = \left[\frac{R_f}{R_i} \times (V_1 - V_2) + V_b \right] \times \frac{1}{V_{FSR}} \times (2^N - 1)$$

where

- V_{FSR} is full-scale input range of the ADC and
- N is the resolution of the ADC.

(2)

2.5 Design Considerations for the Current Inputs

In industrial process control, analog 4-mA to 20-mA and ± 20 -mA inputs are widely used for measuring process variables such as pressure and temperature. The benefits of the current loop are that the accuracy of the signal is not affected by voltage drops in interconnecting wiring. Even if there is significant voltage drop resulting from the wire resistance, the current-loop transmitter maintains the proper current up to its maximum voltage capability. A precision resistor is required to convert the current into voltage so that it can be measured by an ADC. The value of the precision resistor can be calculated from Equation 3.

$$R_s = \frac{R_i}{R_f} \times \frac{V_{FSR}}{I_{S-max}}$$

where

- V_{FSR} is the full-scale input range of the ADC,
 - I_{S-max} is the full-scale value of the current, and
 - V_{FSR} is the full-scale input of the ADC.
- (3)

A simplified circuit for current measurements is shown in Figure 6. The dc transfer function for current input is stated in Equation 4 and the ADC output code can be calculated from Equation 5.

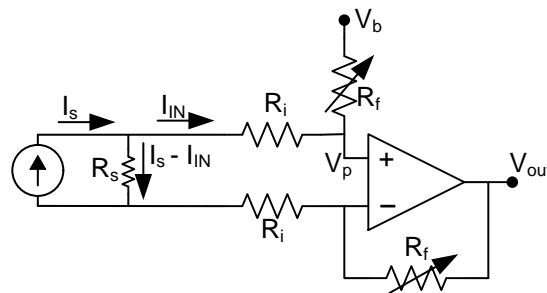


Figure 6. Simplified Circuit for Current Measurements

$$V_{out} = \frac{R_f}{R_i} \times (I_s - I_{IN}) \times R_s + V_b$$

where:

- V_{FSR} is the full-scale input range of the ADC,
 - I_s is the full-scale current, and
 - R_s is the sense resistor for measuring current.
- (4)

$$ADC_OUTPUT_CODE = \left(\frac{R_f}{R_i} \times (I_s - I_{IN}) \times R_s + V_b \right) \times \frac{1}{V_{FSR}} \times (2^N - 1)$$

where

- V_{FSR} is the full-scale input range of the ADC and
 - N is the resolution of the ADC.
- (5)

Process variables such as pressure and temperature are nearly static in nature. The dc specifications (gain error, offset error, and INL error) of the analog input module become critical in designing the analog input module for measuring these variables. Gain error, offset error, and INL error contribute to the overall accuracy of the analog input module. As an example, the current output (± 20 mA) from a pressure sensor must be measured with an accuracy of 20 μ A for an overall accuracy of $\pm 0.1\%$ of the analog input module. For dc (static) conditions, the major portion of error is contributed by the gain error, the offset error, and INL. Total error for static conditions is calculated as the root of sum of squares of gain error, offset error, and INL.

2.6 Design Considerations for the Temperature Input

RTDs are sensors that are used to measure temperature by correlating resistance of the element with the temperature. According to the IEC751/ITS-90 standard, the resistance of a platinum resistance temperature detector can be derived from [Equation 6](#).

For $T = -200^{\circ}\text{C}$ to 0°C

$$R_T = R_0 \times [1 + A \times T + B \times T^2]$$

For $T = 0^{\circ}\text{C}$ to 850°C

$$R_T = R_0 \times [1 + A \times T + B \times T^2 + C(1 - T)^3]$$

Where

- R_T is RTD resistance at temperature T .
- R_0 is RTD resistance at 0°C .
- $A = 3.9083 \times 10^{-3} \text{ }^{\circ}\text{C}^{-1}$
- $B = -5.775 \times 10^{-7} \text{ }^{\circ}\text{C}^{-2}$
- $C = -4.182 \times 10^{-12} \text{ }^{\circ}\text{C}^{-4}$

(6)

A simplified schematic for temperature measurement using an RTD is shown in [Figure 7](#).

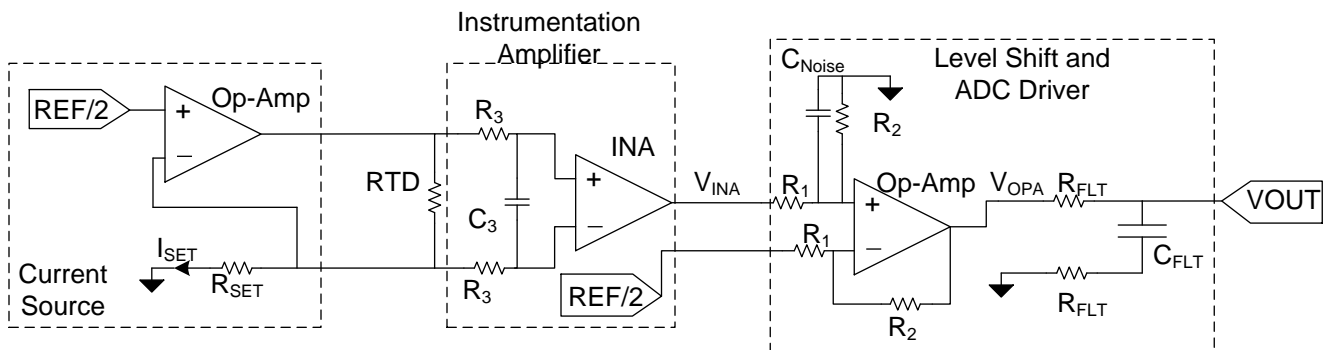


Figure 7. Simplified Schematic for Temperature Measurement using an RTD

A current source is required for exciting the RTD. A low-noise, low-offset, and low-drift operational amplifier is required to make a precise current source for exciting the RTD. The value of I_{SET} is kept at 1 mA to limit the self-heating of the RTD. The excitation current can be derived from [Equation 7](#).

$$I_{\text{SET}} = \frac{V_{\text{REF}/2}}{R_{\text{SET}}} \quad (7)$$

A low-noise, high-input impedance instrumentation amplifier is required to amplify the voltage across the RTD. The gain required for this stage can be derived from [Equation 8](#).

$$G_{\text{INA}} = \frac{V_{\text{FSR}}}{(I_{\text{SET}} \times R_{\text{RTD-MAX}})}$$

where:

- I_{SET} is the excitation current for the RTD,
- $R_{\text{RTD-MAX}}$ is the maximum resistance of the RTD for the selected temperature range, and
- V_{FSR} is the full-scale input range of the ADC.

(8)

[Equation 9](#) states the dc transfer function for the instrumentation amplifier stage:

$$V_{\text{INA}} = I_{\text{SET}} \times R_{\text{RTD}} \times G_{\text{INA}}$$

where

- G_{INA} is the gain of the instrumentation amplifier

(9)

For the temperature range of -40°C to 160°C :

$$R_{\text{RTD-MIN}} = 84.27 \text{ } \Omega \text{ at } T = -40^{\circ}\text{C}.$$

$$R_{\text{RTD-MAX}} = 161.05 \text{ } \Omega \text{ at } T = 160^{\circ}\text{C}.$$

Because the analog input module is designed to operate on a single supply, the output of the instrumentation amplifier can only swing between 0 V and the supply voltage (AVDD). An ADC with a single-ended input and full-scale input range less than the AVDD supply is required for temperature measurement in this analog module.

The output of the instrumentation gain stage covers only a fraction of the full-scale input range of the ADC. Therefore, the output of the instrumentation gain stage must be level shifted and amplified to match the full-scale input range of the ADC. Equation 10 states the dc transfer function for this stage.

$$V_{OPA} = (V_{INA} - V_{REF/2}) \times \frac{R_2}{R_1}$$

where:

- V_{OPA} is the output voltage of the operational amplifier and
- V_{INA} is the output voltage of the instrumentation amplifier. (10)

Equation 11 states the complete transfer equation for the temperature input and the ADC output code for the temperature input can be calculated from Equation 12.

$$V_{OUT} = \frac{R_2}{R_1} \times \left[G_{INA} \times \frac{V_{REF}}{2} \times \frac{1}{R_{SET}} \times R_{RTD} - \frac{V_{REF}}{2} \right]$$
 (11)

$$ADC_Output_Code = \frac{R_2}{R_1} \times \left[G_{INA} \times \frac{V_{REF}}{2} \times \frac{1}{R_{SET}} \times R_{RTD} - \frac{V_{REF}}{2} \right] \times \frac{1}{V_{FSR}} \times (2^N - 1)$$
 (12)

The REF / 2 voltage is generated by a resistor divider from the V_{REF} voltage and buffered with an operational amplifier to provide a low-impedance REF / 2 source for driving the inverting input of the ADC driver. Figure 8 provides the schematic for the REF / 2 source.

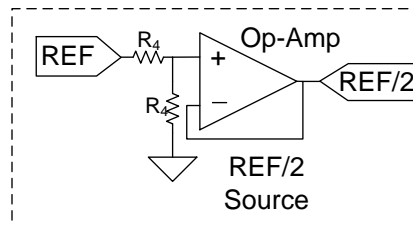


Figure 8. Schematic for the REF / 2 Source

The design considerations for driving a SAR ADC can be found in section 2 of TI Design [TIDU181](#).

2.6.1 Noise Analysis

The last stage for the circuit illustrated in [Figure 7](#) is a level shift and ADC driver stage. The operational amplifier is configured for a differential input and a single-ended output. The total integrated noise at the output of the operational amplifier configured as a differential amplifier can be estimated by [Equation 13](#).

$$V_{\text{AMP-NOISE}} = \sqrt{\left[\left\{ 2 \cdot (I_n R_2)^2 + \left(e_n \cdot \left(\frac{R_1 + R_2}{R_1} \right) \right)^2 + 8kTR_2 \left(\frac{R_1 + R_2}{R_1} \right) \right\} \times \text{ENB} + \left(E_{\text{INAOUT}} \cdot \frac{R_2}{R_1} \right)^2 + \left(E_{\text{REF}/2} \cdot \frac{R_2}{R_1} \right)^2 + \left(\frac{V_{1/f_{\text{AMP-PP}}}}{6.6} \right)^2 \right]}$$

where:

- $V_{\text{AMP-NOISE}}$ is the total integrated RMS noise at the output of the operational amplifier,
- I_n is the white current noise specification of the operational amplifier ($A/\sqrt{\text{Hz}}$),
- V_n is the white voltage noise specification of the operational amplifier ($V/\sqrt{\text{Hz}}$),
- E_{INAOUT} is the total noise at the output of the instrumentation amplifier (V RMS),
- $E_{\text{REF}/2}$ is the total noise at the REF / 2 output (VRMS),
- $V_{1/f_{\text{AMP-PP}}}$ is the flicker noise specification of the operational amplifier specified as peak-to-peak noise (V_{pp}), and
- ENB is the effective noise bandwidth.

$$\text{ENB} = \frac{1}{2\pi \cdot 2 \cdot R_{\text{FLT}} \cdot C_{\text{FLT}}} \cdot \frac{\pi}{2} \quad (13)$$

Details for noise analysis in operational amplifiers can be found in application report [SLVA043](#).

For an ADC with an input range of V_{FSR} , the RMS value of the input-referred noise can be found from the specified value of SNR in the data sheet by using [Equation 14](#).

$$V_{\text{n_ADC_RMS}} = \frac{V_{\text{FSR}}}{2\sqrt{2}} \times 10^{-\frac{\text{SNR}(\text{dB})}{20}}$$

where:

- $V_{\text{n_ADC_RMS}}$ is the RMS noise at the input of the ADC and
- V_{FSR} is the full-scale input range of the ADC. (14)

The total noise for a temperature measurement system is the root sum square (RSS) of the noise at the output of the amplifier and the input-referred noise of the ADC. The system noise for a temperature input can be calculated using [Equation 15](#).

$$V_{\text{SYS-NOISE}} = \sqrt{[V_{\text{AMP-NOISE}}^2 + V_{\text{n_ADC_RMS}}^2]} \quad (15)$$

3 Component Selection

3.1 Selection of ADC

The analog input module requires a SAR ADC with multiplexed inputs, a programmable input voltage range on each input, and high input impedance. The ADC must be capable of accepting input ranges of $\pm 10\text{V}$, $\pm 5\text{V}$, 0V to 5V , and 0V to 2.5V and must include an integrated reference. The ADC must have a throughput greater than 500 kSPS to achieve a response time of $2\ \mu\text{s}$. The gain error, offset error, and INL of the ADC must be less than 0.05% FSR to achieve an overall accuracy of 0.1% .

With all these requirements, the [ADS8688](#) is found to be suitable for this design. Each channel of the ADS8688 can be programmed to any of the above voltage ranges by programming the registers of the device. The ADS8688 also provides a constant input impedance of $1\ \text{M}\Omega$ for channels AIN_0P to AIN_7P. The auxiliary channel of the ADS8688 with a single-ended input range of V_{REF} makes the device suitable for temperature input.

3.2 Voltage Inputs

The ADS8688 can directly accept voltage inputs of $\pm 10.24\text{ V}$, $\pm 5.12\text{ V}$, $\pm 2.56\text{ V}$, 0 V to 10.24 V , and 0 V to 5.12 V . Any additional components are not required for voltage inputs.

3.3 Current Inputs

A precision resistor is required to convert the current into voltage. The input range selected for current measurements is $\pm 5.12\text{ V}$ for a $\pm 20\text{-mA}$ current input. A lower input range is selected to provide headroom for the voltage drop across connecting wires and to provide flexibility in selecting the voltage supply for the current-loop transmitter. According to [Equation 3](#), the value of the precision resistance for the current input of $\pm 20\text{ mA}$ and 4 mA to 20 mA comes out to be $256\ \Omega$. The tolerance of the current-sensing resistor directly affects the gain error in current measurement, and thus a 0.1% , $249\text{-}\Omega$ resistor is used for sensing current for current inputs.

3.4 Temperature Input

An ADC with a single-ended input and full-scale input range less than the AVDD supply is required for the temperature input in a single-supply analog module. Therefore, the auxiliary channel of the ADS8688 is selected for the temperature input because this channel has a full-scale input range of V_{REF} (4.096 V).

3.4.1 Current Source

The key specifications for the amplifier for the current source are low noise, low offset, and low drift. The amplifier must be able to provide an output current of 1 mA . The [OPA376](#) amplifier is a low-noise amplifier with outstanding dc precision and ac performance. The OPA376 offers a low offset voltage ($25\ \mu\text{V}$, max), low noise ($7.5\text{ nV}/\sqrt{\text{Hz}}$), and low drift ($2\ \mu\text{V}/^\circ\text{C}$ max). These features make the device suitable for a precision current source. The value of R_{SET} can be calculated by [Equation 7](#) as $2.048\text{ k}\Omega$.

A $2\text{-k}\Omega$ (0.1%) resistor is selected for R_{SET} .

3.4.2 Instrumentation Gain Stage

The key requirements for this stage are low noise, low offset, low offset drift, and single-supply operation.

The [INA333](#) has low offset (25 μV), excellent offset voltage drift (0.1 $\mu\text{V}/^\circ\text{C}$), low noise density (50 $\text{nV}/\sqrt{\text{Hz}}$), and can operate from a single supply. The INA333 has auto calibration techniques that ensure precision over the industrial temperature range. These features make the INA333 ideal for temperature measurement applications using RTDs.

The gain required for the instrumentation stage can be calculated from [Equation 8](#). The selected temperature range is -40°C to 160°C . $R_{\text{RTD-MAX}} = 161.05 \Omega$ at $T = 160^\circ\text{C}$. $G_{\text{INA}} = 25.46 \text{ V/V}$.

The value for the gain-setting resistor for the INA333 can be calculated by [Equation 16](#).

$$R_G = 100 \text{ k}\Omega / (G_{\text{INA}} - 1) \quad (16)$$

A 4.12-k Ω (0.1%) resistor is selected for R_G .

3.4.3 REF / 2 Source

The key specifications for the amplifier for the REF / 2 source are low noise, low offset, and low drift. The OPA376 amplifier is a low-noise amplifier with outstanding dc precision and ac performance. The OPA376 offers a low offset voltage (25 μV , max), low noise (7.5 $\text{nV}/\sqrt{\text{Hz}}$), and low drift (2 $\mu\text{V}/^\circ\text{C}$ max).

3.4.4 Level Shift and ADC Driver Stage

The gain required for the level shift and ADC driver stage can be found by [Equation 10](#) with $V_{\text{OPA}} = V_{\text{REF}}$ and $V_{\text{INA}} = V_{\text{REF}}$. The gain for this stage is estimated to be 2 V/V. The tolerance of resistors R2 and R1 for setting gain contribute to the gain error. R2 and R1 are selected to be 4.02 k Ω and 2.00 k Ω , respectively, with a tolerance of 0.1%. The amplifier is selected to be the [OPA320](#), R_{FLT} to be 50 Ω , and C_{FLT} to be 3 nF, as per the design guidelines provided in section 2 of TI Design [TIDU181](#).

Using [Equation 13](#), the total noise at the output of the ADC driver configured as a differential amplifier is estimated to be:

$V_{\text{AMP-NOISE}} = 32.2 \mu\text{V}$ RMS with:

- $I_N = 0.6 \text{ fA}/\sqrt{\text{Hz}}$, $E_N = 8.5 \text{ nV}/\sqrt{\text{Hz}}$, and $V_{1/f_AMP_PP} = 2.8 \mu\text{V}_{PP}$ for the OPA320.
- $R_2 = 4.02 \text{ k}\Omega$, $R_1 = 2 \text{ k}\Omega$, and $T = 298 \text{ K}$.
- $\text{ENB} = 0.8333 \text{ MHz}$ for $R_{\text{FLT}} = 50 \Omega$ and $C_{\text{FLT}} = 3 \text{ nF}$.
- $E_{\text{INA-OUT}} = 5.49 \mu\text{V}$ RMS and $E_{\text{REF/2}} = 7.188 \mu\text{V}$ RMS from simulation results in [Section 4.1.4](#) and [Section 4.1.5](#).

Using [Equation 14](#), the input-referred noise for the auxiliary channel of the ADS8688 is calculated to be 57.3 μV_{rms} .

With [Equation 15](#), the total system noise for the temperature input is estimated to be 65.7 μV_{rms} .

4 Simulation and Circuit Performance Calculations

4.1 TINA-TI Simulation

4.1.1 DC Transfer Characteristics for Voltage inputs

The TINA-TI schematic shown in Figure 9 is used to simulate the dc transfer characteristics. The input range is selected by setting the voltage for the MODE pin. A dc voltage source is connected at the analog inputs of the ADS8688 model for simulating the voltage output. Figure 10 provides the simulation result for dc transfer characteristics for a voltage range of ± 10 V.

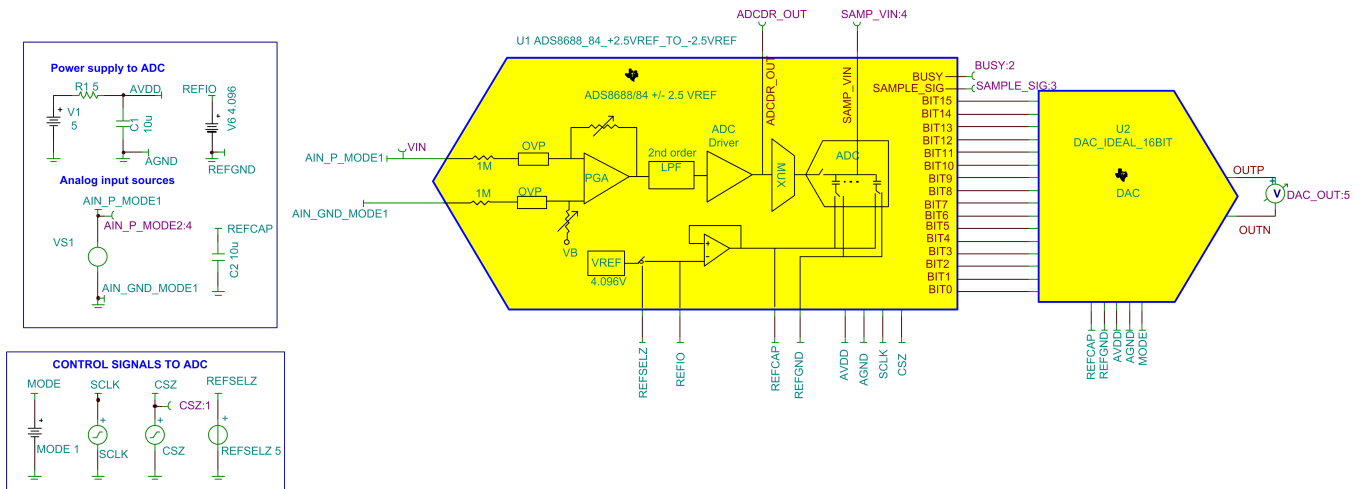


Figure 9. TINA-TI Schematic for the ADS8688 with Voltage Inputs

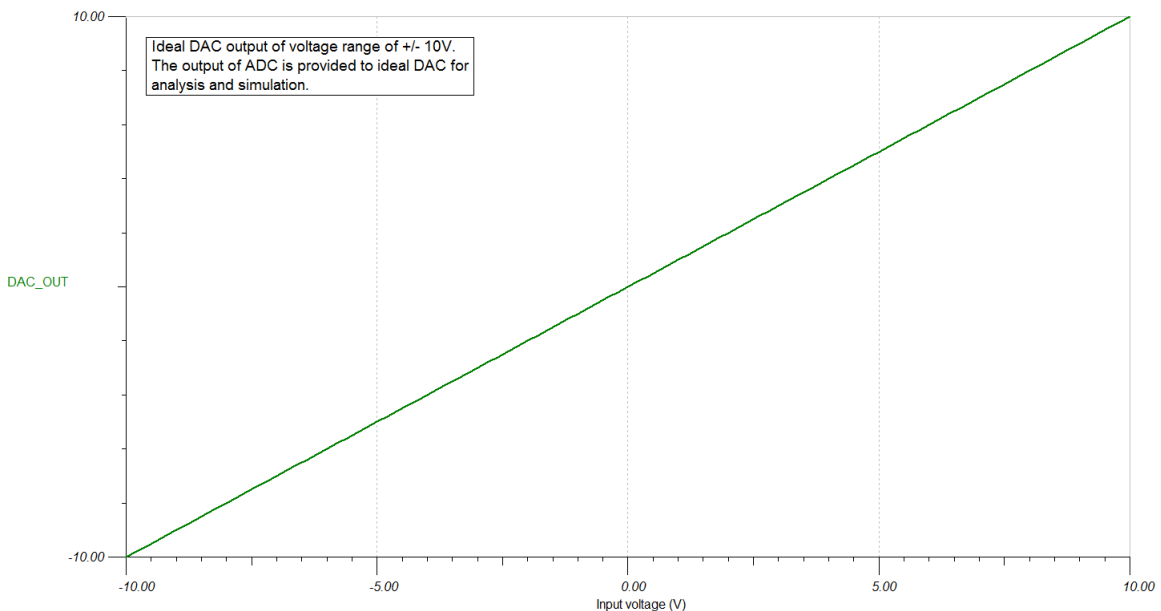


Figure 10. TINA-TI Simulation Result: DC Transfer Characteristics for Voltage Inputs

4.1.2 DC Transfer Characteristics for Current Inputs

The TINA-TI schematic shown in Figure 11 is used to simulate the dc transfer characteristics. The model of the ADS8688 in TINA-TI is used with a current-sense resistance for simulation. The input range is selected by setting the voltage for the MODE pin. A dc current source is connected at the analog inputs of the ADS8688 model for simulating the current-loop output.

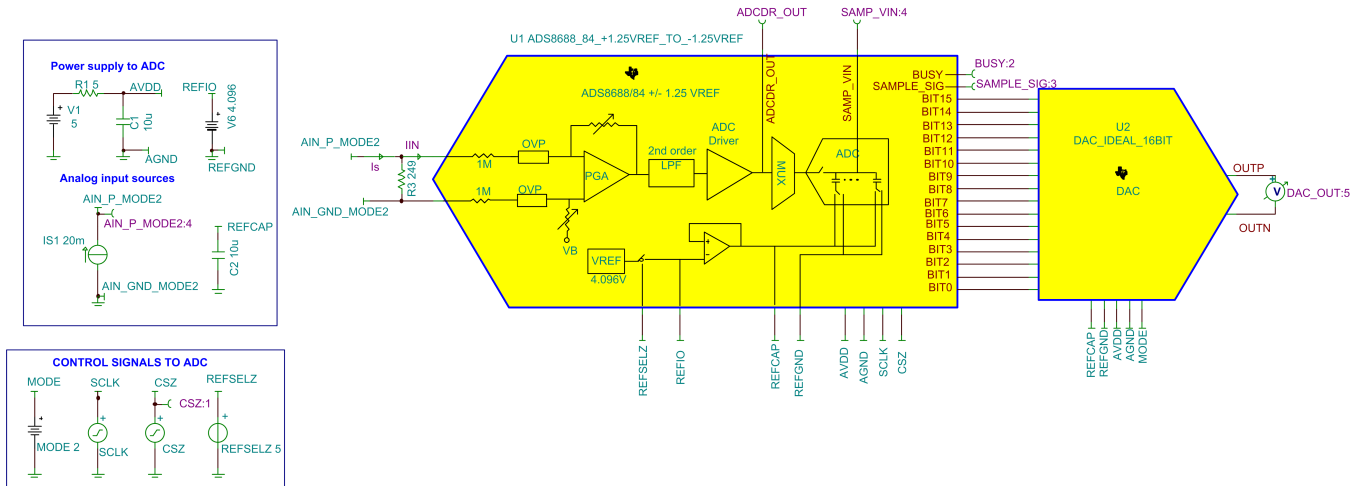


Figure 11. TINA-TI Schematic for the ADS8688 with Current Inputs

Figure 12 shows the dc transfer characteristics for the circuit illustrated in Figure 11 for current range of ± 20 mA.

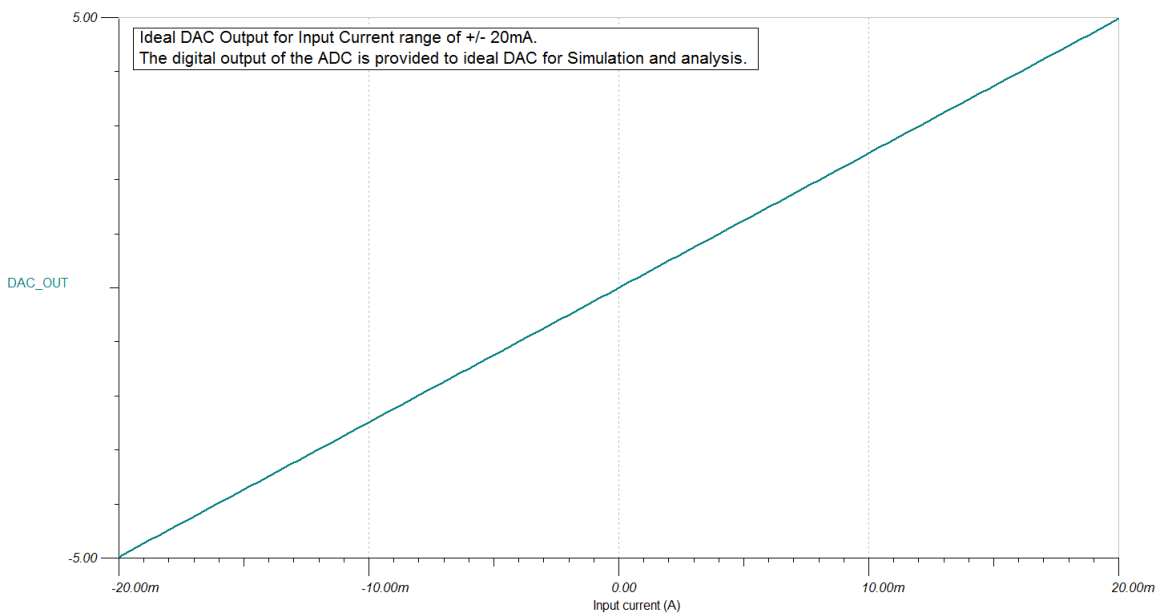


Figure 12. TINA-TI Simulation Result: DC Transfer Characteristics for Current Inputs

4.1.3 DC Transfer Characteristics for Temperature Inputs

The TINA-TI schematics illustrated in Figure 13 and Figure 15 are used to check the dc transfer characteristics for stages of temperature input. Figure 14 and Figure 16 illustrate the simulation results. DC transfer characteristics are plotted for an RTD resistance of 85 Ω to 161 Ω. DC transfer characteristics are simulated to check for saturation of the output when the output reaches close to the supply rails. The ideal gain for this stage is also calculated from the dc transfer characteristics.

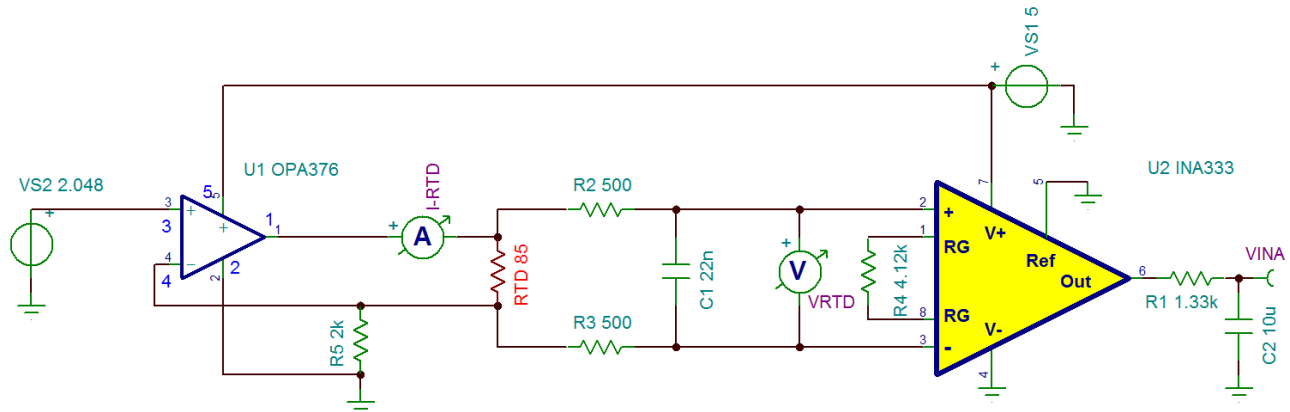


Figure 13. TINA-TI Schematic for the RTD Current Source and Instrumentation Amplifier

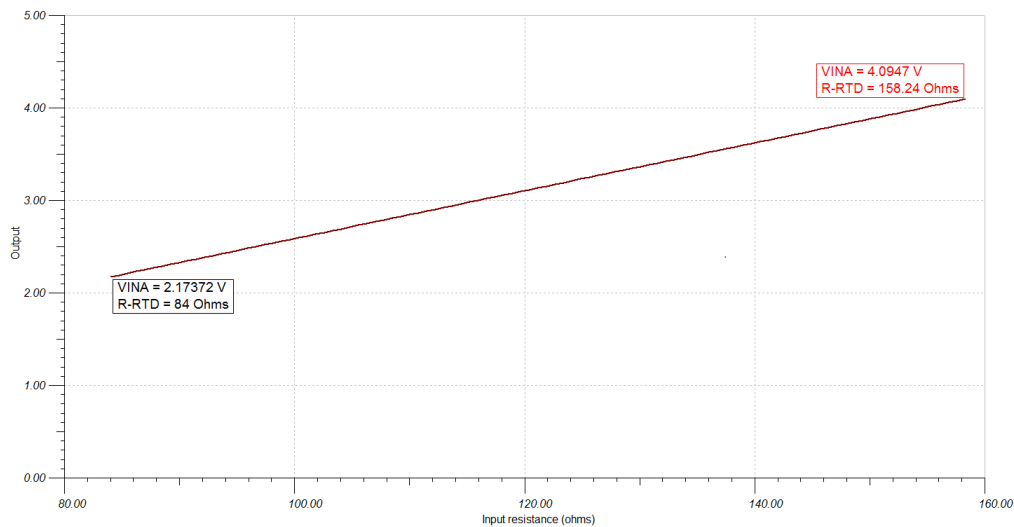


Figure 14. TINA-TI Simulation Result: DC Transfer Characteristics for the RTD Current Source and Instrumentation Amplifier

The ideal gain for this stage is calculated as $\Delta V_{INA} / \Delta R_{-RTD}$. The gain for this stage is calculated to be 25.875 mV/Ω.

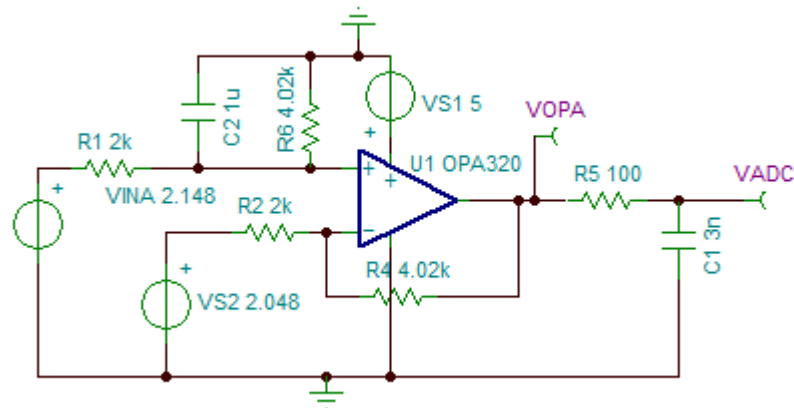


Figure 15. TINA-TI Schematic for the Level Shift and ADC Driver Stage

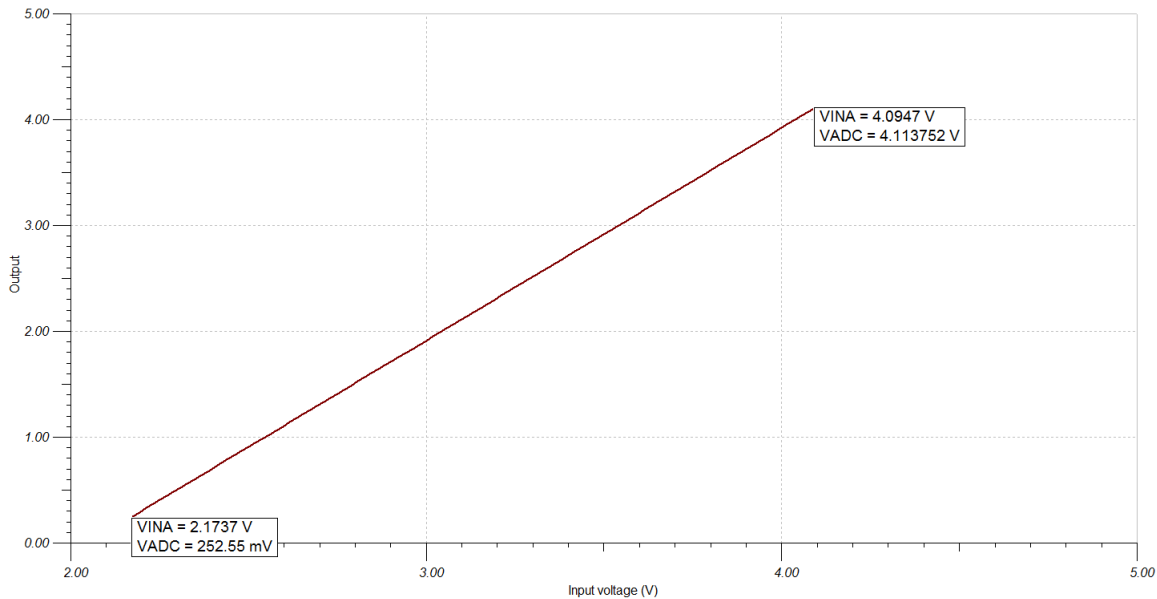


Figure 16. TINA-TI Simulation Result: DC Transfer Characteristics for the Level Shift and ADC Driver Stage

The ideal gain for this stage is calculated as $\Delta V_{ADC} / \Delta V_{INA}$. The gain for this stage is estimated to be 2.0099 V/V.

The total gain for the temperature input is the multiplication of the gain of the two stages. The total gain is calculated to be 52.006 mV/Ω.

4.1.4 Noise Simulation for the REF / 2 Source

Figure 17 shows the TINA-TI schematic for the REF / 2 source and Figure 18 provides the total noise (Vrms) at the output of the REF / 2 source.

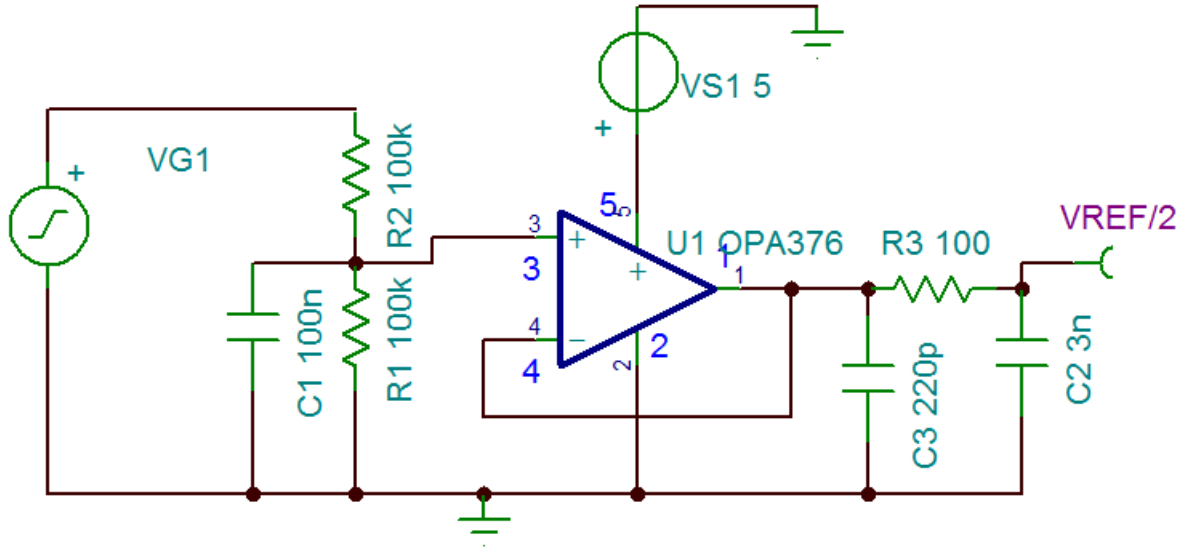


Figure 17. TINA-TI Schematic for the REF / 2 Source

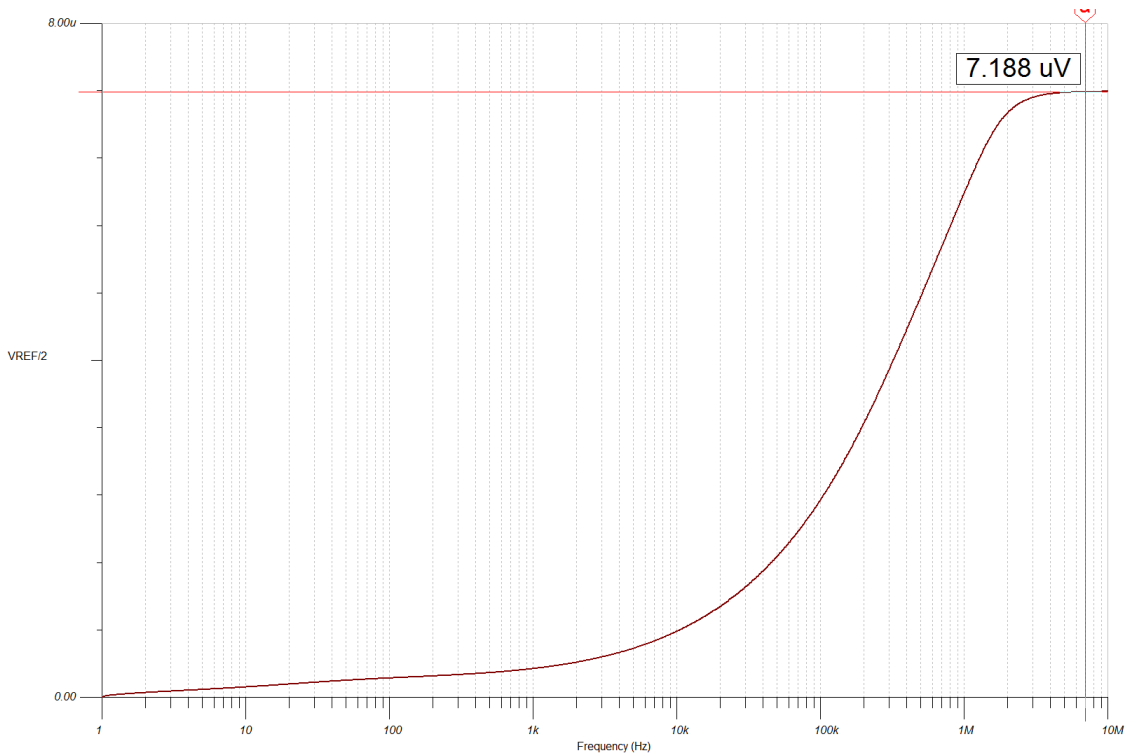


Figure 18. Total Noise at the Output of the REF / 2 Source

4.1.5 Noise Simulation for the Instrumentation Amplifier Stage

Figure 19 shows the TINA-TI™ for the current source and the INA333. The noise at the output of the INA333 is simulated in TINA-TI to get the total system noise for the temperature input. Figure 20 provides the total noise at the output of INA333. A low-pass RC filter is placed at the output of the INA333 to limit noise.

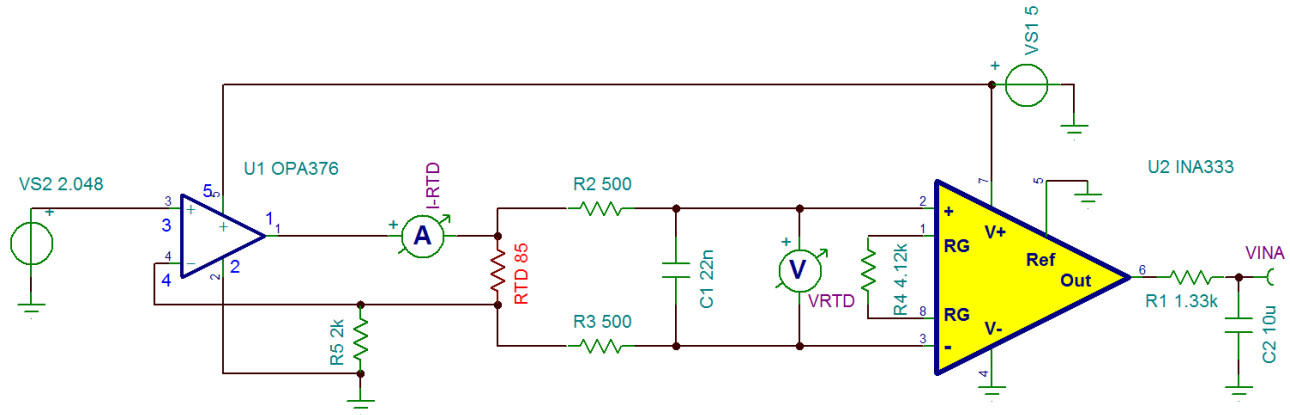


Figure 19. TINA-TI Schematic for the Current Source and the INA333

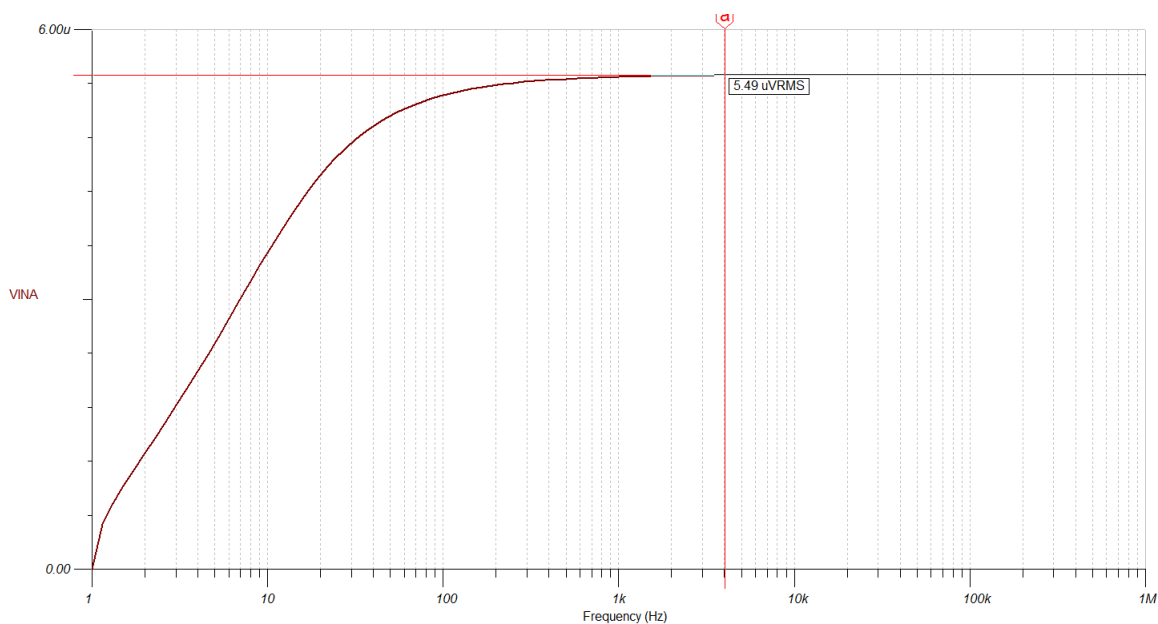


Figure 20. Total Noise at the Output of the INA333

4.2 Circuit Performance Calculations

The total error is calculated for voltage, current, and temperature inputs in the sections below.

4.2.1 Analyzing Total Error for Voltage Inputs

Table 2. Total Error for Voltage Inputs

Error Source	Error Contributed (%FSR)	Comments	Calculated Error (% FSR)
Gain error contributed by the PGA and ADC	$GE_{ADC_PGA}\%$	Gain error is specified as $\pm 0.05\%$ FSR for the ADS8688.	$\pm 0.05\%$
Offset error contributed by the ADC and PGA	$(R_f / R_i \times OE_{ADC_PGA}) / V_{FSR}\%$	Offset error is specified as ± 0.75 mV for the ADS8688. R_f / R_i is the gain of the PGA. $V_{FSR} = V_{REF}$.	$\pm 0.004\%$
Gain error contributed by the initial accuracy of the reference	$Ref_error / V_{REF}\%$	Ref_error is the error in the initial voltage of the reference. Ref_error is specified as ± 1 mV for the ADS8688.	$\pm 0.024\%$
INL contributed by the ADC and PGA	$INL_{ADC_PGA} / (2^N)\%$	INL is specified as ± 2 LSB for the ADS8688.	$\pm 0.003\%$
Total Error (Root of Sum of Squares)			$\pm 0.056\%$

For the voltage input range of ± 10 V, the input range of ± 10.24 V is selected for the ADS8688. The PGA has a gain (R_f / R_i) of 0.2 for the input range of ± 10.24 V.

4.2.2 Analyzing Total Error for Current Inputs

Table 3. Total Error Analysis for Current Inputs

Error Source	Error Contributed (%FSR)	Comments	Calculated Error (%FSR)
Gain error caused by tolerance of the sense resistor, R_s	$t\%$	t is the tolerance of the sense resistor. $t = 0.1\%$.	$\pm 0.1\%$
Gain error caused by input impedance of the PGA ⁽¹⁾	$I_{IN} / I_S\%$	I_{IN} is the current into the pin of the PGA, I_S is the full-scale input current.	$\pm 0.04\%$
Gain error contributed by the PGA and ADC	$GE_{ADC_PGA}\%$	Gain error is specified as $\pm 0.05\%$ FSR for the ADS8688.	$\pm 0.05\%$
Offset error caused by input impedance of the PGA ⁽¹⁾	$(R_f / R_i \times I_{IN} \times R_s) / V_{FSR}\%$	Offset error caused by current from the PGA pins when $I_s = 0$. R_f / R_i is the gain of the PGA. $V_{FSR} = V_{REF}$.	$\pm 0.012\%$
Offset error contributed by the ADC and PGA	$(R_f / R_i \times OE_{ADC_PGA}) / V_{FSR}\%$	Offset error is specified as ± 1 mV for the ADS8688. $V_{FSR} = V_{REF}$.	$\pm 0.0097\%$
Gain error contributed by initial accuracy of the reference	$Ref_error / V_{REF}\%$	Ref_error is the error in initial voltage of the reference. Ref_error is specified as ± 1 mV for the ADS8688.	$\pm 0.024\%$
INL contributed by the ADC and PGA	$INL_{ADC_PGA} / (2^N)\%$	INL is specified as ± 2 LSB for the ADS8688.	$\pm 0.003\%$
Total Error (Root of Sum of Squares)			$\pm 0.122\%$

⁽¹⁾ I_{IN} can be calculated from the equation given in the Electrical Characteristics table in the ADS8688 data sheet ([SBAS582](#)).

For the current input range of ± 20 mA, the input range of ± 5.12 V is selected for the ADS8688. The PGA has a gain (R_f / R_i) of 0.4 for the input range of ± 5.12 V.

4.2.3 Analyzing Total Error for Temperature Inputs

Table 4. Total Error Analysis for Temperature Inputs

Error Source	Error Contributed (%FSR)	Comments	Calculated Error (%FSR)
Errors in the REF / 2 Source			
Offset error of the operational amplifier	$OE_{OPA} / (V_{REF} / 2)\%$	Offset error is specified as 25 μ V for the OPA376.	$\pm 0.0012\%$
Reference error	$Ref_error / V_{REF}\%$	Ref_error is the error in the initial voltage of the reference. Ref_error is specified as ± 1 mV for the ADS8688.	$\pm 0.024\%$
Tolerance of resistors ⁽¹⁾	$t / \sqrt{2}\%$	t is the tolerance of the resistors. t = 1%.	$\pm 0.7\%$
Errors in the Current Source			
Tolerance of R_S	t%	t is the tolerance of the resistor for setting the RTD current. t = 0.1%.	$\pm 0.1\%$
Offset error of the operational amplifier	$OE_{OPA} / (V_{REF} / 2)\%$	Offset error is specified as 25 μ V for the OPA376.	$\pm 0.0012\%$
Errors in the Level Shift and ADC Driver			
Offset error of the operational amplifier	$OE_{OPA} / (V_{REF} / 2)\%$	Offset error is specified as 150 μ V for the OPA320.	$\pm 0.007\%$
Tolerance of gain setting resistors R1, R2 ⁽²⁾	$\sqrt{2} t\%$	t is the tolerance of the resistors R1, R2. t = 0.1%.	$\pm 0.14\%$
Errors in the AUX Channel of the ADS8688			
Offset error	$OE_{ADC} / V_{FSR}\%$	Offset error is specified as 10 mV for the AUX channel of the ADS8688. $V_{FSR} = V_{REF}$.	$\pm 0.24\%$
Gain error	$GE_{ADC}\%$	Gain error is specified as 0.2 % for the AUX channel of the ADS8688.	$\pm 0.2\%$
INL	$INL_{ADC} / (2^N)\%$	INL is specified as ± 4 LSB for the AUX channel of the ADS8688.	$\pm 0.006\%$
Total Error (Root of Sum of Squares)			$\pm 0.78\%$ or $\pm 1.56^\circ\text{C}$

⁽¹⁾ See Section 10.1.

⁽²⁾ See Section 10.2.

For the temperature input, the auxiliary channel of the ADS8688 is used. For the temperature input range of -40°C to 160°C , the full-scale input range is 200°C .

5 PCB Design

The printed circuit board (PCB) schematic and bill of materials can be found in [Section 10](#).

Use a ground plane underneath the device and partition the PCB into analog and digital sections. Avoid crossing digital lines with the analog signal path and keep the analog input signals and the reference input signals away from noise sources. In this board layout, the analog input and reference signals are routed on the top layer of the board and the digital connections are routed on the bottom of the board.

The power sources to the ADS8688 must be clean and well-bypassed. Avoid placing vias between the AVDD and DVDD pins and the bypass capacitors. Connect all the ground pins to the ground plane using short, low-impedance paths.

There are two decoupling capacitors used for the REFCAP pin. The first is a small 1- μ F ceramic capacitor placed close to the device pins for decoupling the high-frequency signals and the second is a 22- μ F ceramic capacitor to provide the charge required by the reference circuit of the ADS8688. Both of these capacitors must be directly connected to the pins of the device without any vias between the pins and the capacitors.

The PCB layout for this design is shown in [Figure 21](#).

5.1 PCB Layout

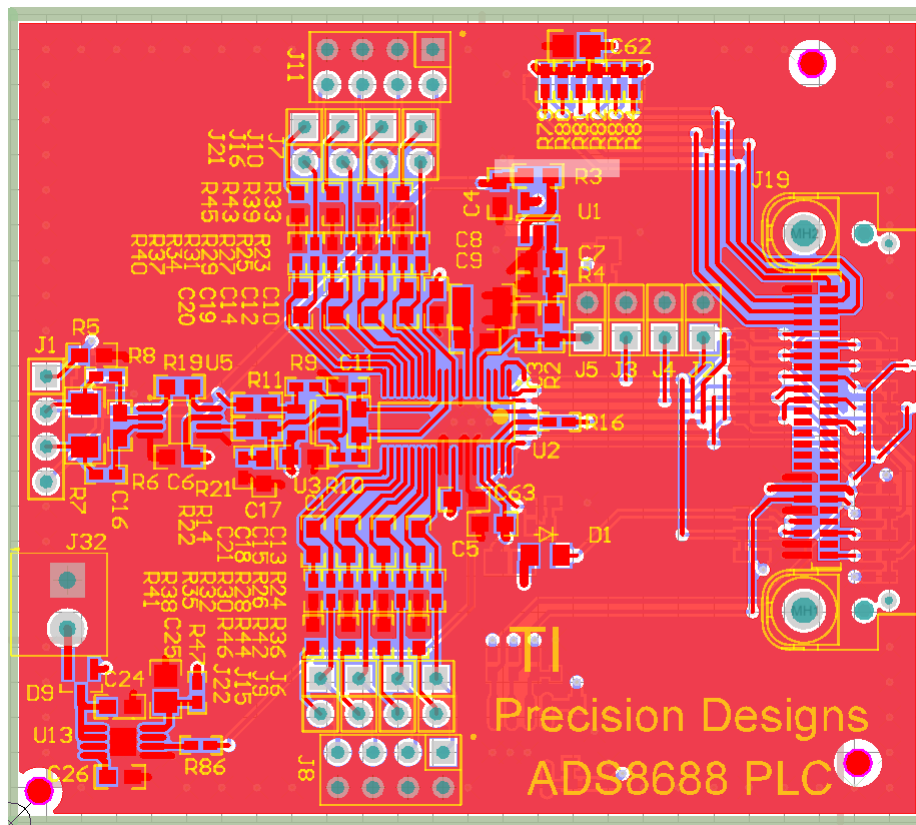


Figure 21. PCB Layout

6 Verification and Measured Performance

The measurement results for verification of this TI Precision Design are listed in this section.

6.1 Measured Performance for Voltage Inputs

The performance for the voltage inputs is measured by providing dc voltage from -10 V to 10 V and capturing the output code of the ADS8688. With $R_f / R_i = 0.2$, $V_b = 2.048\text{ V}$, $V_{FSR} = 4.096\text{ V}$, and $N = 16$, for an input range of $\pm 10.24\text{ V}$ in the ADS8688, Equation 2 can be simplified as Equation 17:

$$\text{ADC_Output_Code} = \frac{(0.2 \times V_{IN} + 2.048)}{4.096} \times 65535 \quad (17)$$

Figure 22 and Figure 23 provide the transfer characteristics and total error for voltage input. The total error is calculated as the difference between the expected output code obtained from Equation 17 and the measured output code. The reference and offset of the ADS8688 are calibrated to obtain the calibrated total error.


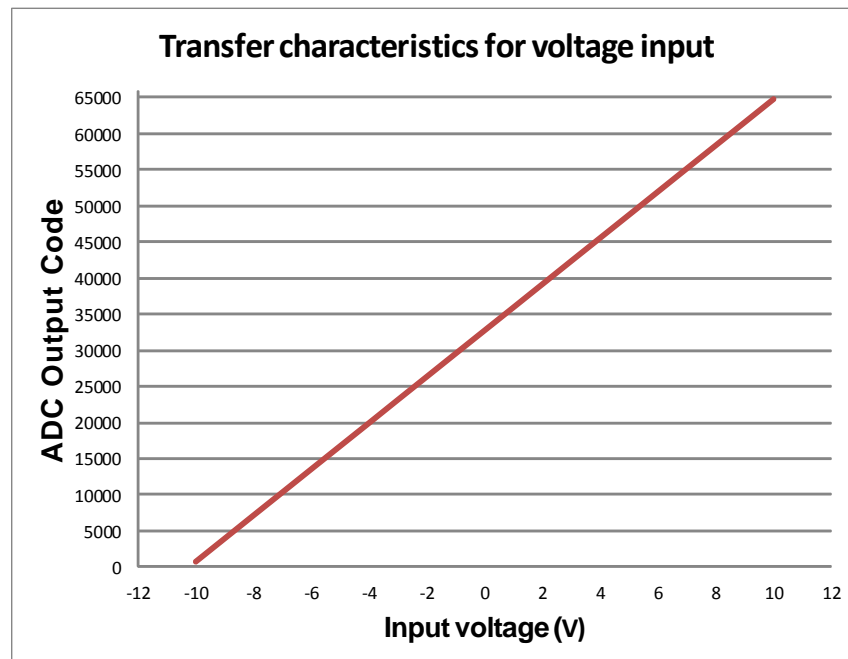


Figure 22. Transfer Characteristics for Voltage Inputs

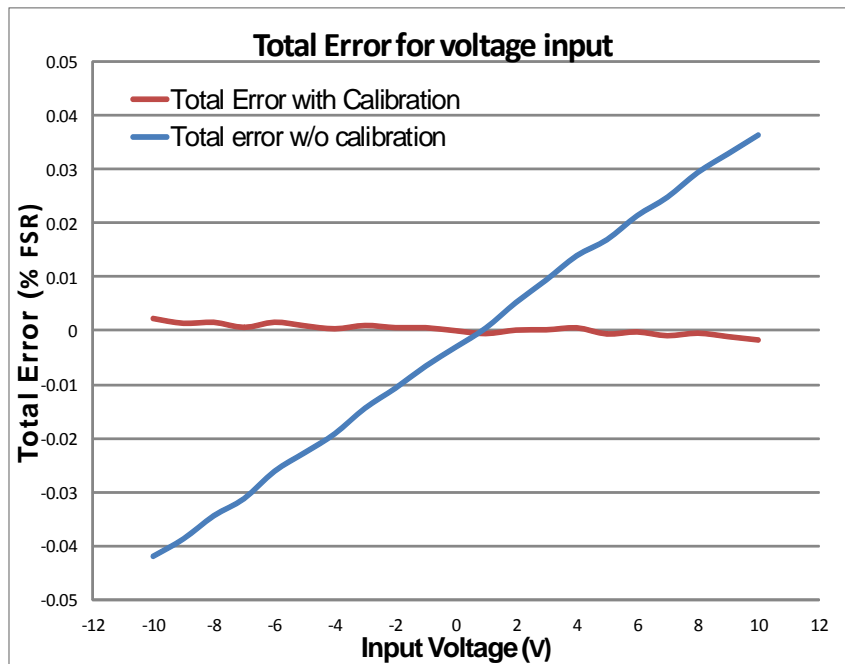

Max total error without calibration = -0.042%, max total error with calibration = 0.002%

Figure 23. Total Error for Voltage Inputs

6.2 Measured Performance for Current Inputs

The performance for the current inputs is measured by providing dc current from -20 mA to 20 mA and capturing the output code of the ADS8688. With $R_f / R_i = 0.4 \text{ V}$, $V_b = 2.048 \text{ V}$, $V_{FSR} = 4.096 \text{ V}$, and $N = 16$ for an input range of $\pm 5.12 \text{ V}$ in the ADS8688, Equation 5 can be simplified as Equation 18:

$$\text{ADC_OUTPUT_CODE} = \left(\frac{0.4 \times (I_s - I_{IN}) \times R_s + 2.048}{4.096} \right) \times 65535 \quad (18)$$

Figure 24 and Figure 25 provide the transfer characteristics and total error for current input. The total error is calculated as difference between the expected output code obtained from Equation 18 and the measured output code. The reference of the ADS8688 and current sense resistor (R_s) are calibrated to obtain the calibrated total error.


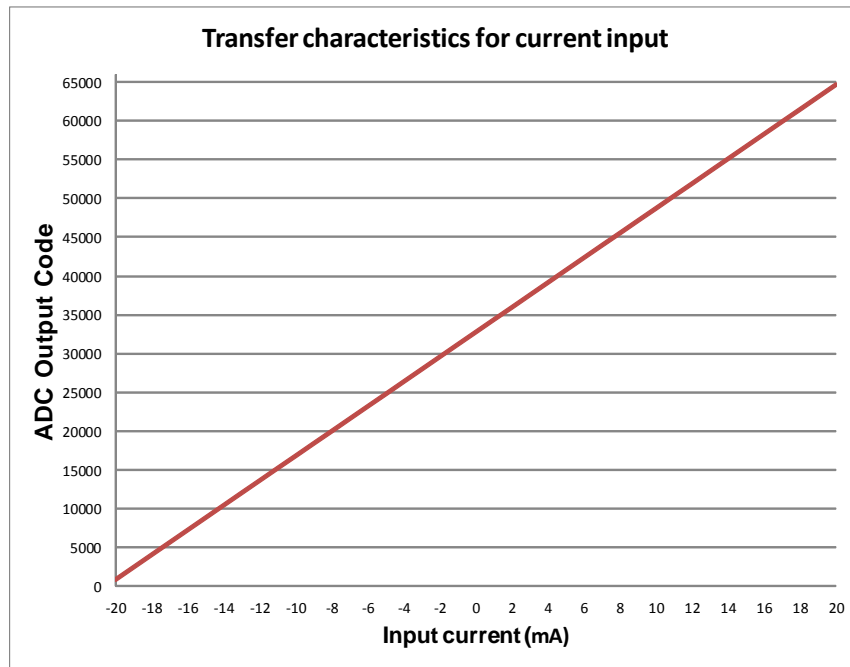


Figure 24. Transfer Characteristics for Current Input

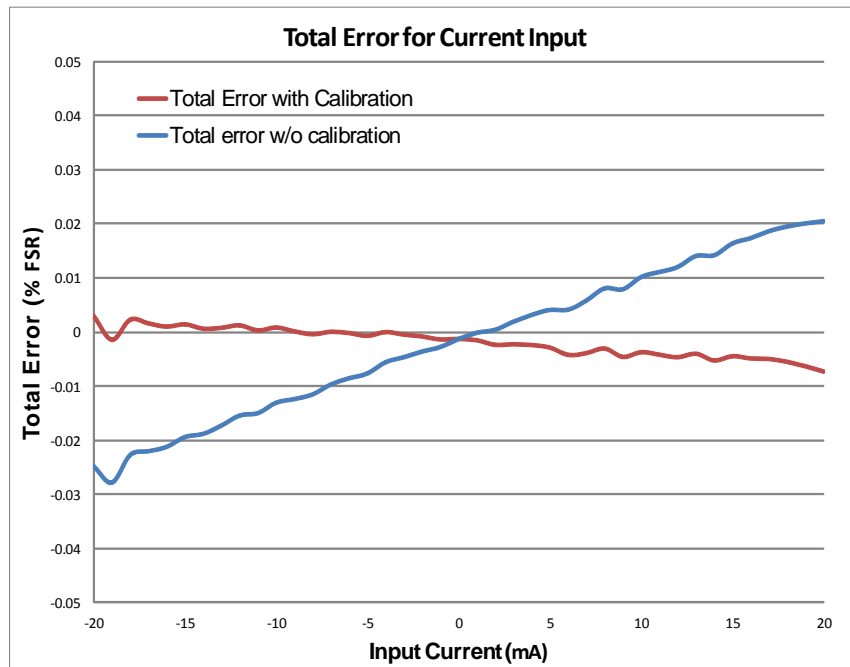

Max total error without calibration = -0.028% , max total error with calibration = -0.007%

Figure 25. Total Error for Current Input

6.3 Measured Performance for the Temperature Input

The performance for the temperature input is measured by connecting a potentiometer of 200 Ω in place of a Pt100 RTD and varying the resistance from 85 Ω to 160 Ω. With $R_2 / R_1 = 2.01$ V, $G_{INA} = 25.27$ V/V, $V_{FSR} = 4.096$ V, and $N = 16$ for an input range of 0 V to 4.096 V for the AUX channel in the ADS8688, Equation 2 can be simplified as Equation 19:

$$\text{ADC_Output_Code} = 1.005 \times \left[\frac{25.27 \times R_{RTD}}{2000} - 1 \right] \times 65535 \tag{19}$$

Figure 26 and Figure 27 provide the transfer characteristics and total error for temperature input. The total error is calculated as the difference between the expected output code obtained from Equation 19 and the measured output code. The REF / 2 source and the current source are calibrated to obtain the calibrated total error.


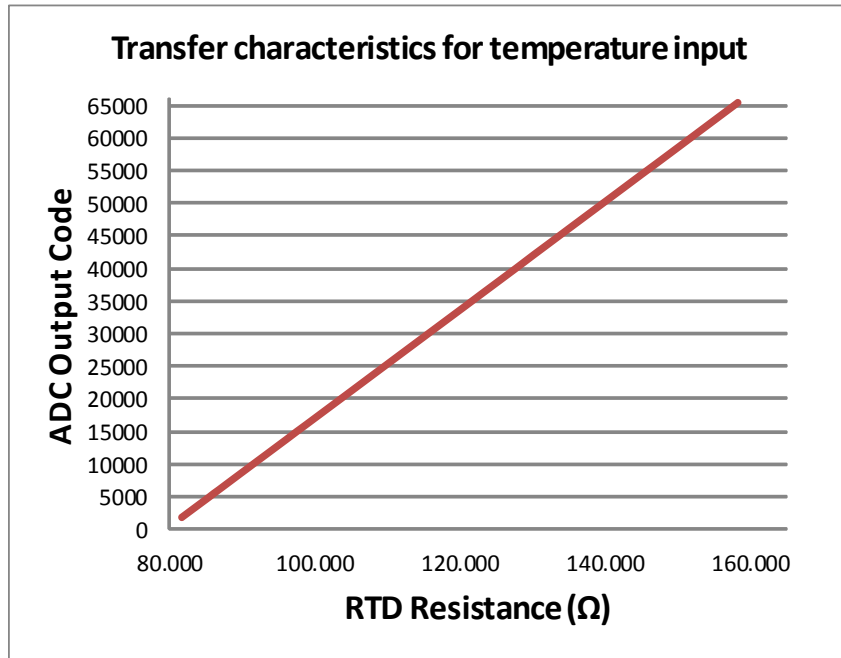



Figure 26. Transfer Characteristics for Temperature Input

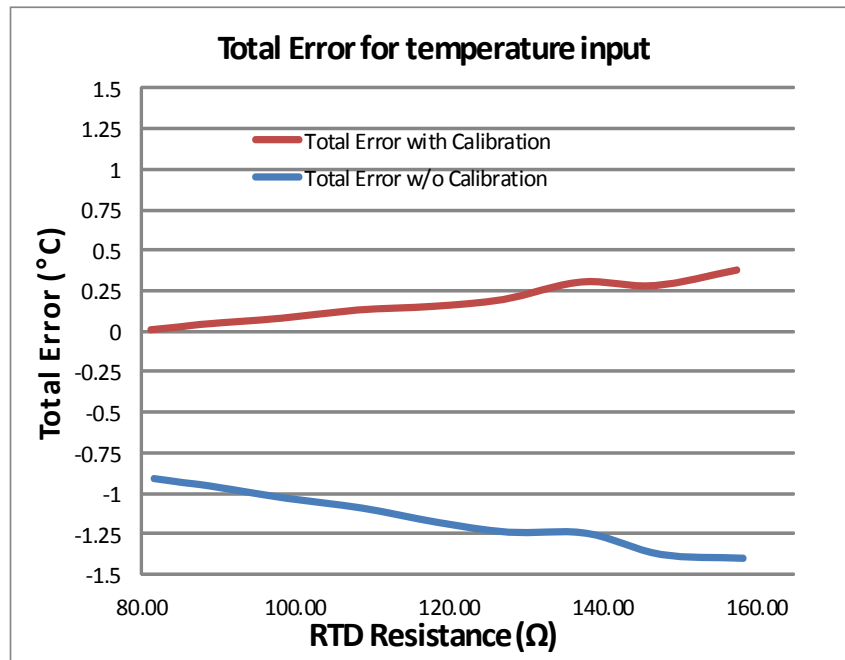

Max total error without calibration = -1.4°C , max total error with calibration = 0.38°C

Figure 27. Total Error for Temperature Input

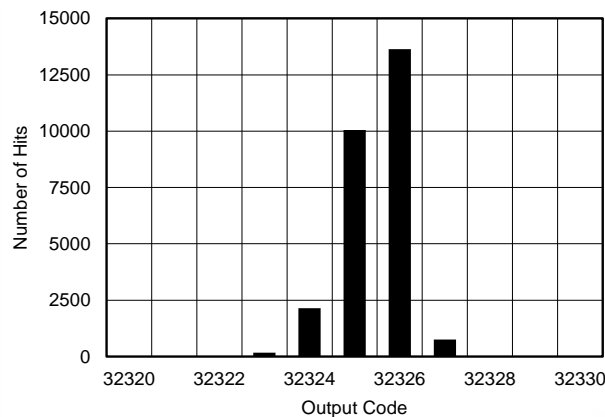The system noise for the temperature input is measured by capturing 32768 samples for an input close to mid scale. Figure 28 shows the histogram of samples captured. The system noise is calculated using the sigma of the codes and LSB size. The system noise is found to be $57.5 \mu\text{Vrms}$.



Sigma = 0.92, mean code = 32325.78, peak code = 32326

Figure 28. DC Histogram for the Temperature Input

7 Modifications

7.1 Improving the Temperature Drift

The temperature drift can be improved by using an external reference for the ADS8688 and a zero-drift operational amplifier for the REF / 2 source and current source. Table 5 and Table 6 provide suggestions for an external reference and alternative operational amplifier for the current source and REF / 2 source.

Table 5. External Reference for the ADS8688

REFERENCE	INITIAL ACCURACY (%)	NOISE (μV_{PP}) (F = 0.1 Hz to 10 Hz)	MAX TEMPERATURE DRIFT (ppm/ $^{\circ}\text{C}$)
REF5040I	± 0.05	12	3

Table 6. Alternative Operational Amplifier for the Current Source and REF/2 Source

ALTERNATIVE OP AMP	MAX OFFSET VOLTAGE (μV)	NOISE (μV_{PP}) (F = 0.1 Hz to 10 Hz)	MAX OFFSET VOLTAGE DRIFT ($\mu\text{V}/^{\circ}\text{C}$)
OPA378	50	0.4	0.25

7.2 Increasing the Temperature Range for Temperature Input

The components selected for this design are based on the design goals outlined at the beginning of the design process. The temperature input is designed for a Pt100 RTD for a temperature range of -40°C to 160°C . The temperature input can be optimized for a complete temperature range of -200°C to 850°C by changing the circuit for the temperature input as per the schematic shown in Figure 29. Table 7 provides the value of R_G for a temperature range of -200°C to 850°C .

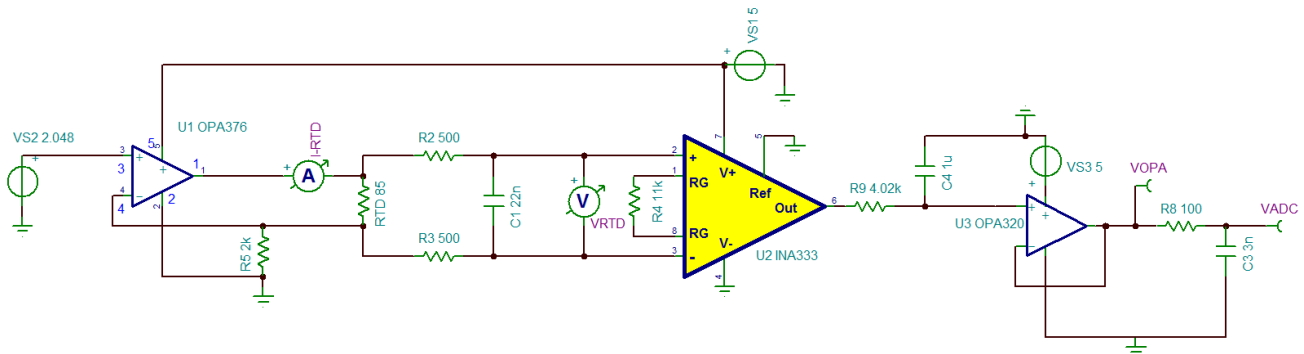


Figure 29. Schematic for the Temperature Input for the Range of -200°C to 850°C

Table 7. Selecting Different Temperature Ranges for the Temperature Input

S.NO.	MINIMUM TEMPERATURE	$R_{\text{RTD-MIN}}$	MAXIMUM TEMPERATURE	$R_{\text{RTD-MAX}}$	R_G
1.	-200°C	18.52 Ω	850°C	390.48 Ω	11 k Ω

8 About the Author

Lokesh Ghulyani is a systems engineer in the SAR-ADC team at Texas Instruments (TI) based in Bangalore, India. Prior to this role, he worked as an analog application engineer at TI. Lokesh earned his Bachelor of Technology Degree from the Indian Institute of Technology, Varanasi in India.

9 References and Acknowledgments

1. *Noise Analysis in Operational Amplifier Circuits (SLVA043B)*. Available: [SLVA043B](#)
2. Vaibhav Kumar and Rafael Ordonez. *16-bit, 400KSPS, 4-Channel Multiplexed Data Acquisition System for High Voltage Inputs with Lowest Distortion (TIDU181)*. Available: [TIDU181](#)
3. Collin Wells and Janet Sun. *Analog input module for industrial outputs and temperature sensors reference design (TIDU491)* Available: [TIDU491](#)

10 Appendix

10.1 Error Due to Tolerance of Resistors in REF / 2 Source

The transfer function for the circuit shown in [Figure 30](#) can be calculated as [Equation 20](#).

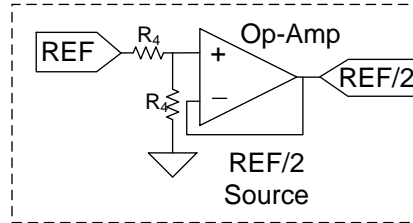


Figure 30. REF / 2 Source Circuit Diagram

$$V_{REF/2} = V_{REF} \times \frac{R_4(1 + t_1)}{R_4(1 + t_1) + R_4(1 + t_2)}$$

where

- t_1 and t_2 are the tolerance of individual resistors. (20)

[Equation 20](#) is simplified in the following steps:

$$V_{REF/2} = V_{REF} \times \frac{(1 + t_1)}{(2 + t_1 + t_2)}$$
(21)

$$V_{REF/2} = \frac{V_{REF}}{2} \times \frac{(1 + t_1)}{\left(1 + \frac{(t_1 + t_2)}{2}\right)}$$
(22)

$$V_{REF/2} = \frac{V_{REF}}{2} \times \left(1 + \frac{(t_1 - t_2)}{2}\right)$$
(23)

Because t_1 and $t_2 \ll 1$, the maximum value of tolerance $\left[\frac{(t_1 - t_2)}{2}\right]$ is $\frac{[|t_1| + |t_2|]}{2}$ or t .

The R.S.S value of tolerance is $\frac{\sqrt{t_1^2 + t_2^2}}{2}$ or $t/\sqrt{2}$.

10.2 Errors Due to Tolerance of Resistors in Level Shift and ADC Driver

The transfer function for the circuit shown in [Figure 31](#) can be calculated as [Equation 24](#).

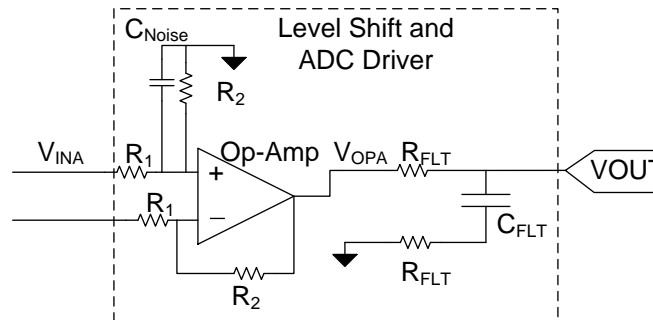


Figure 31. Level Shift and ADC Driver Circuit Diagram

$$V_{OUT} = (V_{INA} - V_{REF/2}) \times \frac{R_2(1 + t_1)}{R_1(1 + t_2)}$$

where

- t_1 and t_2 are the tolerance of individual resistors. (24)

[Equation 24](#) is simplified in the following steps:

$$V_{OUT} = K \times \frac{2R(1 + t_1)}{R(1 + t_2)}$$

where

- $R_2 = 2R, R_1 = R$. (25)

$$V_{OUT} = K \times 2(1 + t_1 - t_2) \tag{26}$$

Because t_1 and $t_2 \ll 1$, the maximum value of tolerance is $|t_1| + |t_2|$ or $2t$.

R.S.S value of tolerance is $\sqrt{t_1^2 + t_2^2}$ or $\sqrt{2}t$.

10.3 Electrical Schematic and Bill of Materials

The electrical schematic and bill of materials for this design are respectively shown in Figure 32 and Table 8.

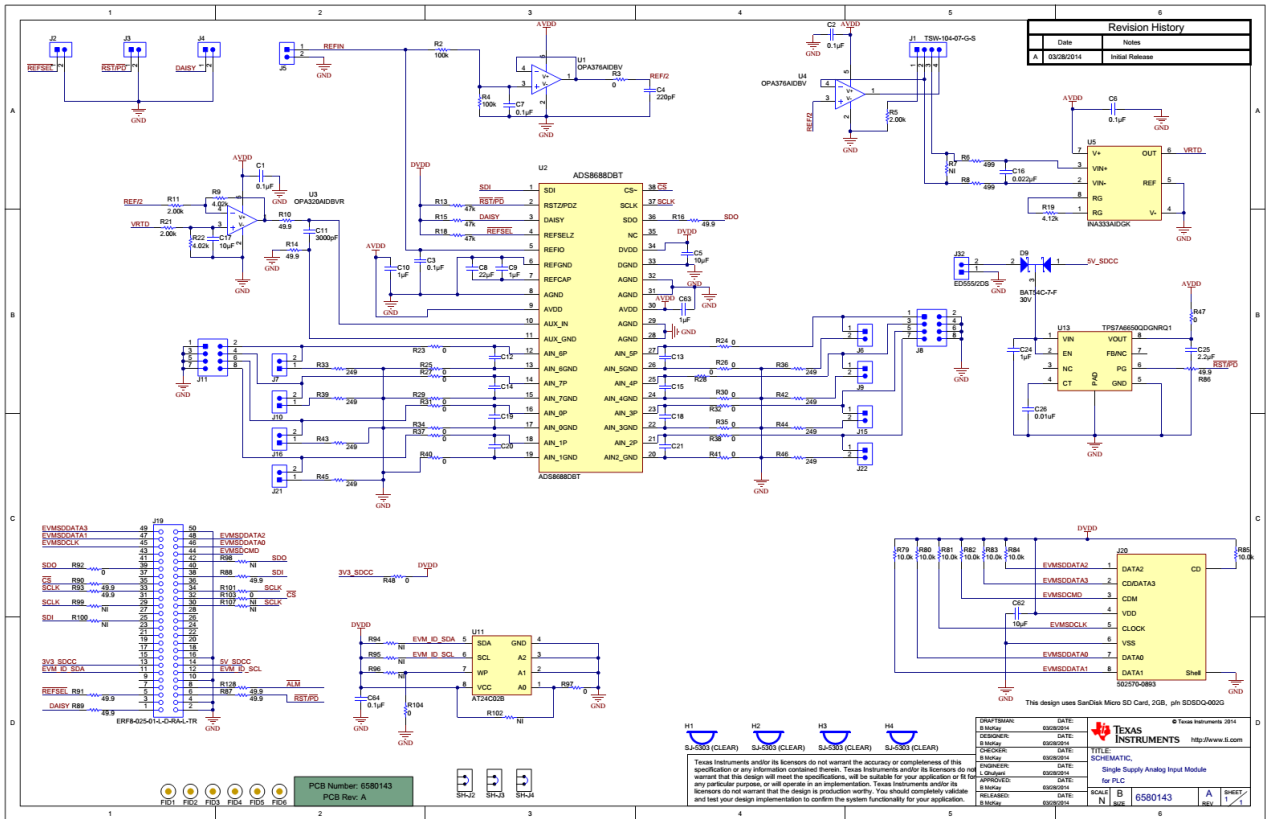


Figure 32. Electrical Schematic

Table 8. Bill of Materials

Designator	Quantity	Value	Description	Package Reference	PartNumber	Manufacturer
IPCB	1		Printed Circuit Board		6580143	Any
C1, C2, C3, C6, C7	5	0.1uF	CAP, CERM, 0.1uF, 25V, +/-5%, X7R, 0603	0603	06033C104JAT2AAVX	AVX
C4	1	220pF	CAP, CERM, 220pF, 100V, +/-10%, X7R, 0603	0603	06031C221KAT2A	AVX
C17	1	10uF	CAP, CERM, 10uF, 10V, +/-20%, X5R, 0603	0603	C1608X5R1A106M	TDK
C24	1	1uF	CAP, CERM, 1uF, 10V, +/-10%, X5R, 0603	0603	C0603C105K8PACTU	Kemet
C5	1	10uF	CAP, CERM, 10uF, 6.3V, +/-20%, X5R, 0603	0603	C0603C106M9PACTU	Kemet
C8	1	22uF	CAP, CERM, 22uF, 16V, +/-20%, X7R, 1210	1210	C3225X7R1C226M	TDK
C9, C63	2	1uF	CAP, CERM, 1uF, 16V, +/-10%, X7R, 0603	0603	C1608X7R1C105K	TDK
C10	1	1uF	CAP, CERM, 1uF, 16V, +/-10%, X5R, 0603	0603	C0603C105K4PACTU	Kemet
C11	1	3000pF	CAP, CERM, 3000pF, 50V, +/-5%, C0G/NP0, 0603	0603	GRM1885C1H302JA01D	MuRata
C26	1	0.01uF	CAP, 10000pF, 0603, 5%, 50V, C0G	0603	C1608C0G1H103J080AA	TDK
C12, C13, C14, C15, C18, C19, C20, C21	8	NI	Capacitor Not Installed	0603	NA	NA
C16	1	0.022uF	CAP, CERM, 0.022uF, 25V, +/-10%, X7R, 0603	0603	C0603C223K3RACTU	Kemet
C25	1	2.2uF	CAP, CERM, 2.2uF, 16V, +/-10%, X7R, 0805	0805	C0805C225K4RACTU	Kemet
C62	1	10uF	CAP, CERM, 10uF, 10V, +/-10%, X7R, 0805	0805	GRM21BR71A106KE51L	MuRata
C64	1	0.1uF	CAP, CERM, 0.1uF, 50V, +/-10%, X7R, 0603	0603	06035C104KAT2A	AVX
D1	1	LTST-C170UKT	Diode, LED, Red, 2.1-V, 14.2-mcd, 20ma, 0805	0805	LTST-C170UKT	Lite On
D9	1	30V	Diode, Schottky, 30V, 0.2A, SOT-23	SOT-23	BAT54C-7-F	Diodes Inc.
FID1, FID2, FID3, FID4, FID5, FID6	6		Fiducial mark. There is nothing to buy or mount.	Fiducial	N/A	N/A
H1, H2, H3, H4	4		Bump, Hemisphere, 0.44 X 0.20, Clear	Transparent Bump	SJ-5303 (CLEAR)	3M
J1	1		Header, TH, 100mil, 4x1, Gold plated, 230 mil above insulator	4x1 Header	TSW-104-07-G-S	Samtec
J2, J3, J4, J5, J6, J7, J9, J10, J15, J16, J21, J22	12		Header, TH, 100mil, 2x1, Gold plated, 230 mil above insulator	2x1 Header	TSW-102-07-G-S	Samtec
J8, J11	2		Header, TH, 100mil, 4x2, Gold plated, 230 mil above insulator	4x2 Header	TSW-104-07-G-D	Samtec
J19	1		Receptacle, Micro High Speed Socket Strip, 0.8mm, 25x2, R/A, SMT	Conn Micro High Speed Socket Strip SKT 50 POS 0.8mm, RA	ERF8-025-01-L-D-RA-L-TR	Samtec, Inc.
J20	1		SD Memory Card Connector	N/A	502570-0893	Molex
J32	1		Terminal Block, 6A, 3.5mm Pitch, 2-Pos, TH	7.0x8.2x6.5mm	ED555/2DS	On-Shore Technology
R2, R4	2	100k	RES, 100k ohm, 1%, 0.1W, 0603	0603	ERJ-3EKF1003V	Panasonic
R3	1	0	RES, 0 ohm, 5%, 0.1W, 0603	0603	CRCW06030000Z0EA	Vishay-Dale

Table 8. Bill of Materials (continued)

Designator	Quantity	Value	Description	Package Reference	PartNumber	Manufacturer
R6, R8	2	499	RES, 499 ohm, 0.1%, 0.063W, 0402	0402	CRCW0402499RFKED	Vishay-Dale
R9, R22	2	4.02k	RES, 4.02k ohm, 0.1%, 0.063W, 0402	0402	RT0402BRD074K02L	Yageo
R10, R14, R16, R86, R87, R88, R89, R90, R91, R93, R128	11	49.9	RES, 49.9 ohm, 1%, 0.063W, 0402	0402	CRCW040249R9FKED	Vishay-Dale
R5, R11, R21	3	2.00k	RES, 2.00k ohm, 0.1%, 0.1W, 0603	0603	RT0603BRD072KL	Yageo
R13, R15, R18	3	47k	RES, 47k ohm, 5%, 0.063W, 0402	0402	CRCW040247K0JNED	Vishay-Dale
R19	1	4.12k	RES, 4.12k ohm, 0.1%, 0.1W, 0603	0603	RT0603BRD074K12L	Yageo
R23, R24, R25, R26, R27, R28, R29, R30, R31, R32, R34, R35, R37, R38, R40, R41	16	0	RES, 0 ohm, 5%, 0.1W, 0603	0402	CRCW06030000Z0EA	Vishay-Dale
R33, R36, R39, R42, R43, R44, R45, R46	8	249	RES, 249 ohm, 0.1%, 0.1W, 0603	0603	RG1608P-2490-B-T5	Susumu Co Ltd
R47, R48, R92, R97, R101, R104	6	0	RES, 0 ohm, 5%, 0.063W, 0402	0402	RC0402JR-070RL	Yageo America
R79, R80, R81, R82, R83, R84, R85	7	10.0k	RES, 10.0k ohm, 1%, 0.063W, 0402	0402	CRCW040210K0FKED	Vishay-Dale
R7, R94, R95, R96, R98, R99, R100, R102, R103, R107	10	NI	Resistor, Uninstalled	0402	NI	NI
SD1	1		SanDisk MicroSD Card, 2GB	N/A	SDSQ-002G	SanDisk
SH-J2, SH-J3, SH-J4	3	1x2	Shunt, 100mil, Gold plated, Black	Shunt	969102-0000-DA	3M
U1, U4	2		Low-Noise, Low Quiescent Current, Precision Operational Amplifier e-trim Series, DBV0005A	DBV0005A	OPA376AIDBV	Texas Instruments
U2	1		16 bit 500KSPS 8 Channel SAR ADC	TSSOP-38	ADS8688IDBT	TI
U3	1	OPA320AIDBVR	IC, Precision, 20MHz, 0.9pA, Low-Noise, RRIO, CMOS Op-Amp	SOT23-5	OPA320AIDBVR	TI
U5	1		Micro-Power (50mA), Zero-Drift, Rail-to-Rail Out Instrumentation Amplifier	DGK0008A	INA333AIDGK	Texas Instruments
U11	1	AT24C02B	IC, 2K, Serial EEPROM	SO-8	AT24C02B	Atmel
U13	1		High-Voltage Ultralow-Iq Low-Dropout Regulator, DGN0008D	DGN0008D	TPS7A6650QDGNRQ1	Texas Instruments

Revision History

Changes from Original (May 2015) to A Revision	Page
• Added text reference for Figure 20	18
• Added footnotes to Table 4	20
• Changed figure numbers to correct ones in second paragraph of <i>Measured Performance for Current Inputs</i> section	23
• Added column headers to first column of Table 5 and Table 6	27
• Added text reference for Table 7	27
• Added <i>Error Due to Tolerance of Resistors in REF / 2 Source</i> section	29
• Added <i>Errors Due to Tolerance of Resistors in Level Shift and ADC Driver</i> section	30

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.