

# Power-Supply Margining Circuit for LDOs Using a Precision DAC




Uttama Kumar Sahu

## Design Goals

Power Supply (VDD)	Nominal Output	Margin High	Margin Low
5V	3.3V	3.3V + 10%	3.3V – 10%
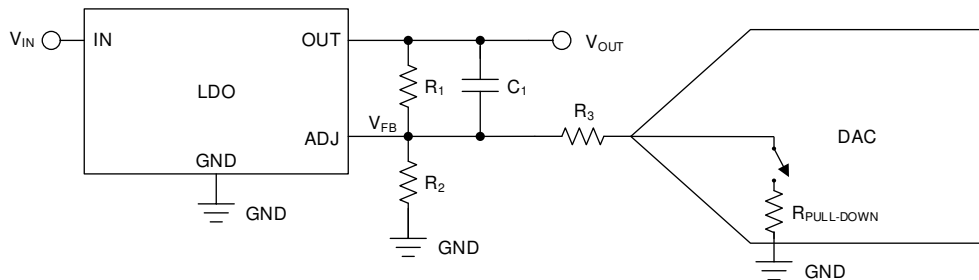
## Design Description

A power-supply margining circuit is used for tuning the output of a power converter. This is done either to adjust the offset and drift of the power supply output or to program a desired value at the output. Adjustable power supplies like Low-Dropout Regulators (LDOs) and DC/DC converters provide a feedback or adjust input that is used to set the desired output. A precision voltage output digital-to-analog converter (DAC) is designed for controlling the power-supply output linearly. The following image shows an example power-supply margining circuit. Typical applications of power-supply margining is in [test and measurement](#), [communications equipment](#), and [power delivery](#).



## Design Notes

1. Choose a DAC with the required resolution, pull-down resistor value, and output range.
2. Derive the relationship of the DAC output to  $V_{OUT}$ .
3. Choose  $R_1$  based on typical current through the feedback circuit.
4. Calculate the start-up or nominal value of  $V_{DAC}$  considering the power-down and power-up conditions of the DAC.
5. Select  $R_2$ , and  $R_3$  such that the desired start-up output voltage is met along with the DAC output voltage range for the desired tuning range.
6. Calculate the margin low and margin high DAC outputs.
7. Choose a compensation capacitor to achieve the desired step response.

## Design Steps

1. Select the LDO TPS79501 device for the calculations. The DAC53608 device is an ultra-low cost, 10-bit, 8-channel, unipolar output DAC designed for such applications
2. The output voltage of the power supply is given by:

$$V_{OUT} = V_{REF} + I_1 R_1 = V_{REF} + (I_2 + I_3) R_1$$

where

- $I_1$  is the current flowing through  $R_1$
- $I_2$  is the current flowing through  $R_2$
- $I_3$  is the current flowing through  $R_3$

DACs in this application typically include power-down mode, which includes an internal pulldown resistor at the voltage output. Hence, replacing the values of the currents in the previous equation yields:

- When the DAC is in *Power Down* mode:

$$V_{OUT} = V_{REF} + \left( \left( \frac{V_{REF}}{R_2} \right) + \left( \frac{V_{REF}}{R_3 + R_{PULL-DOWN}} \right) \right) R_1$$

- When the DAC output is powered-up:

$$V_{OUT} = V_{REF} + \left( \left( \frac{V_{REF}}{R_2} \right) + \left( \frac{V_{REF} - V_{DAC}}{R_3} \right) \right) R_1$$

For DAC53608,  $R_{PULL-DOWN}$  is 10k $\Omega$ . For the LDO part number TPS79501, the value of  $V_{REF}$  is 1.225V.

3.  $R_1$  can be calculated by the following method.

The current through the FB pin of TPS79501 is 1 $\mu$ A. To make this current negligible,  $I_1$  should be  $\gg I_{FB}$ . Choose  $I_1$  to be 50 $\mu$ A. Calculate  $R_1$  as follows:

$$R_1 = \frac{V_{OUT} - V_{REF}}{I_1} = 41.5 \text{ k}\Omega$$

The nominal value of  $I_1$  can be given by:

- When the DAC is in *Power Down* mode

$$I_{1-Nom} = \left( \frac{V_{REF}}{R_2} \right) + \left( \frac{V_{REF}}{R_3 + 10 \text{ k}\Omega} \right)$$

- When the DAC output is powered-up

$$I_{1-Nom} = \left( \frac{V_{REF}}{R_2} \right) + \left( \frac{V_{REF} - V_{DAC}}{R_3} \right)$$

The values of  $I_1$  at *Margin High* and *Margin Low* outputs are given by:

$$I_{1-HIGH} = \frac{V_{OUT-HIGH} - V_{REF}}{R_1} = 57.95 \mu\text{A}$$

$$I_{1-LOW} = \frac{V_{OUT-LOW} - V_{REF}}{R_1} = 42.05 \mu\text{A}$$

$$I_{1-HIGH} - I_{1-Nom} = I_{1-Nom} - I_{1-LOW} = 7.65 \mu\text{A}$$

4. The nominal or startup value of  $V_{DAC}$  can be calculated using the following method:

To make sure the 10-k $\Omega$  resistor does not impact when the DAC is transitioning from power-down to power-up, the power-up value for the DAC voltage can be calculated with:

$$\frac{V_{REF}}{R_3 + 10 \text{ k}\Omega} = \frac{V_{REF} - V_{DAC}}{R_3}$$

The previous equation can be further simplified to:

$$V_{DAC} = V_{REF} \left( \frac{10 \text{ k}\Omega}{R_3 + 10 \text{ k}\Omega} \right)$$

5. The values of  $R_2$  and  $R_3$  can be calculated as follows:

If the power-up or nominal value of  $V_{DAC}$  is kept at one-third of  $V_{REF}$ , that is, 408.3mV, then  $R_3$  is  $2 \times 10\text{k}\Omega = 20\text{k}\Omega$ .  $R_2$  can be calculated as:

$$\frac{V_{REF}}{R_2} + \frac{V_{REF}}{R_3 + 10\text{k}\Omega} = 50\mu\text{A}$$

Replacing the value of  $R_3$ ,  $R_2$  can be calculated to equal 133k $\Omega$ .


6. Subtracting the *Margin High* and *Nominal* values of  $I_1$  and the corresponding equations, we get

$$\frac{V_{REF} - V_{DAC}}{R_3} - \frac{V_{REF}}{R_3 + 10 \text{ k}\Omega} = 7.95 \mu\text{A}$$


So, the *Margin High* value of  $V_{DAC}$  is 249mV and similarly, the *Margin Low* value can be calculated as 567mV from the following equation:

$$\frac{V_{REF}}{R_3 + 10 \text{ k}\Omega} - \frac{V_{REF} - V_{DAC}}{R_3} = 7.95 \mu\text{A}$$

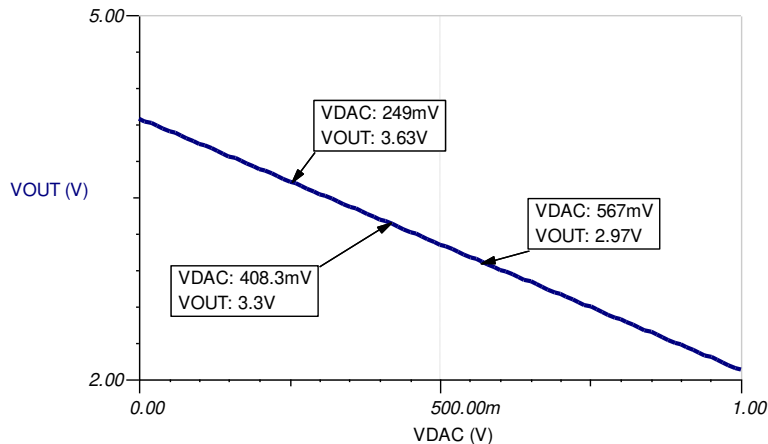
7. The step response of this circuit without a compensation capacitor has some overshoot and ringing as shown in the following curves. This kind of transient response can cause errors at the load circuits. To minimize this, use a compensation capacitor  $C_1$ . The value of this capacitance is usually obtained through simulation. A comparative output shows the waveforms with a compensation capacitor of 22pF.



**DC Transfer Characteristics**

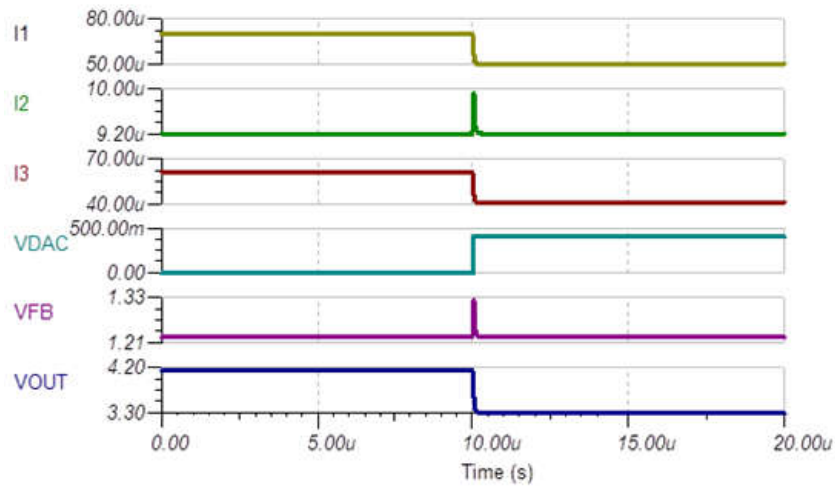
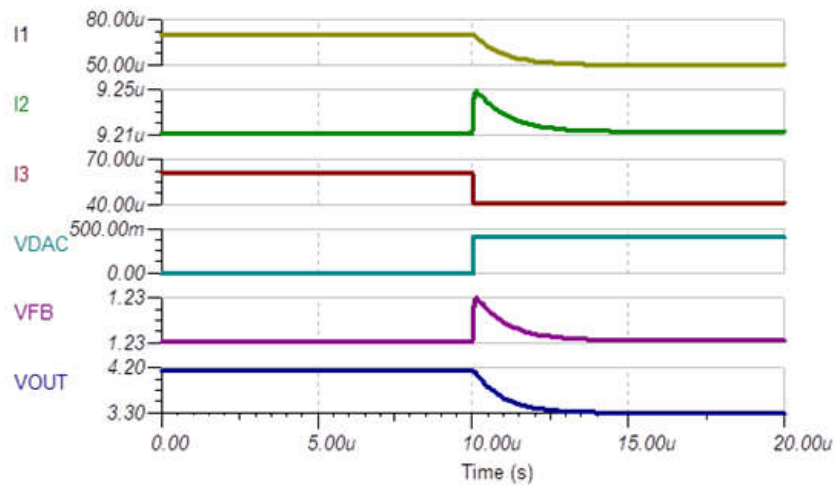
### Small Signal Step Response Without Compensation



### Small-Signal Step Response With $C_1 = 22\text{pF}$

### Design Featured Devices and Alternative Parts

Device	Key Features	Link
DAC53608	8-channel 10-bit, I2C interface, buffered-voltage-output DAC	<a href="#">10-Bit, 8-channel, I2C, voltage output DAC in tiny QFN package</a>
DAC60508	8-channel, true 12-bit, SPI, voltage-output DAC with precision internal reference	<a href="#">True 12-Bit, 8-channel, SPI, Vout DAC in tiny WCSP package with precision internal reference</a>
DAC60501	12-bit, 1-LSB INL, DAC with precision internal reference	<a href="#">True 12-bit, 1-ch, SPI/I2C, voltage-output DAC in WSON package with precision internal reference</a>
DAC8831	16-bit, ultra-low power, voltage output DAC	<a href="#">16-Bit, Ultra-Low Power, Voltage Output Digital to Analog Converter</a>
TPS79501-Q1	Automotive catalog single output LDO, 500mA, adj.(1.2 to 5.5V), low-noise, high PSRR	<a href="#">Automotive 500mA, adjustable low-dropout voltage regulator with enable</a>

## Design References

Texas Instruments, [SBAM415 TINA source files](#), software support

## Trademarks

All trademarks are the property of their respective owners.

## Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

---

<b>Changes from Revision A (September 2019) to Revision B (September 2024)</b>	<b>Page</b>
--	-------------

---

- Updated the format for tables, figures, and cross-references throughout the document ..... 1
- 

<b>Changes from Revision * (January 2019) to Revision A (September 2019)</b>	<b>Page</b>
--	-------------

---

- Updated circuit image and [equation](#) ..... 1
-

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated