

Designing a Fast Charging and Discharging Supercapacitor Backup System for Automotive Applications



Charles Harthan

Emerging electric vehicle (EV) drivetrains are shaking up the way cars are built, but how do EVs affect the design of other components besides the powertrain? Many EVs are adding backup power systems in the charging inlet and microcontroller unit (MCU) farm systems for emergency power when the main car battery is unavailable. As shown in [Figure 1](#), the charging inlet is the port where the charging cable is inserted into the EV, and within the charging inlet, a motor clamps the charging cable to the EV to verify a secure connection during charging. A backup power system for the motor is required for North American Charging Standard (NACS) charging inlets because the charging inlets are ASIL-D rated. MCU farms are the brains of the vehicles controlling systems like airbags, emergency braking and sensors. Having the backup power for these critical systems in case the car battery gets disconnected is necessary. Although NACS charging inlets and MCU farms have different functionality, both are critical for driver safety and utilize supercapacitors for backup power due to the quick rechargeability. To design these supercapacitor backup systems, engineers face the challenges of quick charging while managing power loss, accurate charging to utilize the supercapacitors' full capacity and boosting the supercapacitors quickly to support the backup functionality.



Figure 1. EV Charging Inlet

Choosing the right charger topology based on application specifications

Supercapacitors must be charged quickly to make sure backup power is available soon after the car turns on, but how does one choose the right charger topology based on the system requirements? Equation 1 relates the voltage and charge time which helps select the right charger topology for charging inlets and MCU farms. In [Equation 1](#), I is the charge current, C is total capacitance, dV is the supercapacitor voltage and dT is the charge time.

$$I = C \times \frac{dV}{dT} \quad (1)$$

Typically, MCU farms have a higher charge voltage of 48V compared to the 10V of charging inlets to provide backup power for a longer period of time and a shorter charge time of < 60 seconds. Therefore, the MCU farm application requires more charge current resulting in greater power loss compared to the charging inlet. To support higher power dissipation, a switching charge controller is an effective charger topology for the MCU farm. The switching behavior helps reduce heat due to power loss while the controller topology places the switching FETs external to the charger to improve power capability. The charging inlet application can use a linear charger since the power loss is smaller. Linear chargers also help reduce the total components since linear chargers do not require inductors and MOSFETs like a switching charge controller.

Help maximize the charge on the supercapacitors

Another key challenge to address is charging the supercapacitors as close to the full charge as possible. All charging designs have a charge voltage accuracy specification that details how far above or below the actual charge voltage can be compared to the target charge voltage. Ambient temperature affects the charge voltage accuracy as well. Some ICs can have a 1% charge voltage accuracy at 25°C ambient temperature, but the accuracy can get worse at higher and lower ambient temperatures. Charge voltage accuracy is important to the charging inlet and MCU farm applications. The supercapacitors have less charge to use during backup mode if the actual charge voltage is less than expected. If the charge voltage is higher than expected, then the supercapacitor can be charged above what is rated, which can degrade the capacitor. Figure 2 highlights how the available energy in a supercapacitor increases or decreases exponentially with the charge voltage accuracy. Looking specifically at the 1% to 2% charge voltage accuracy range, the graph shows how a 1% change in charge voltage accuracy can double the energy overcharge or undercharge of the supercapacitors. Therefore, charge voltage accuracy must be considered when designing supercapacitor systems like charging inlets and MCU farms to maximize the available charge in the supercapacitors without sacrificing longevity.

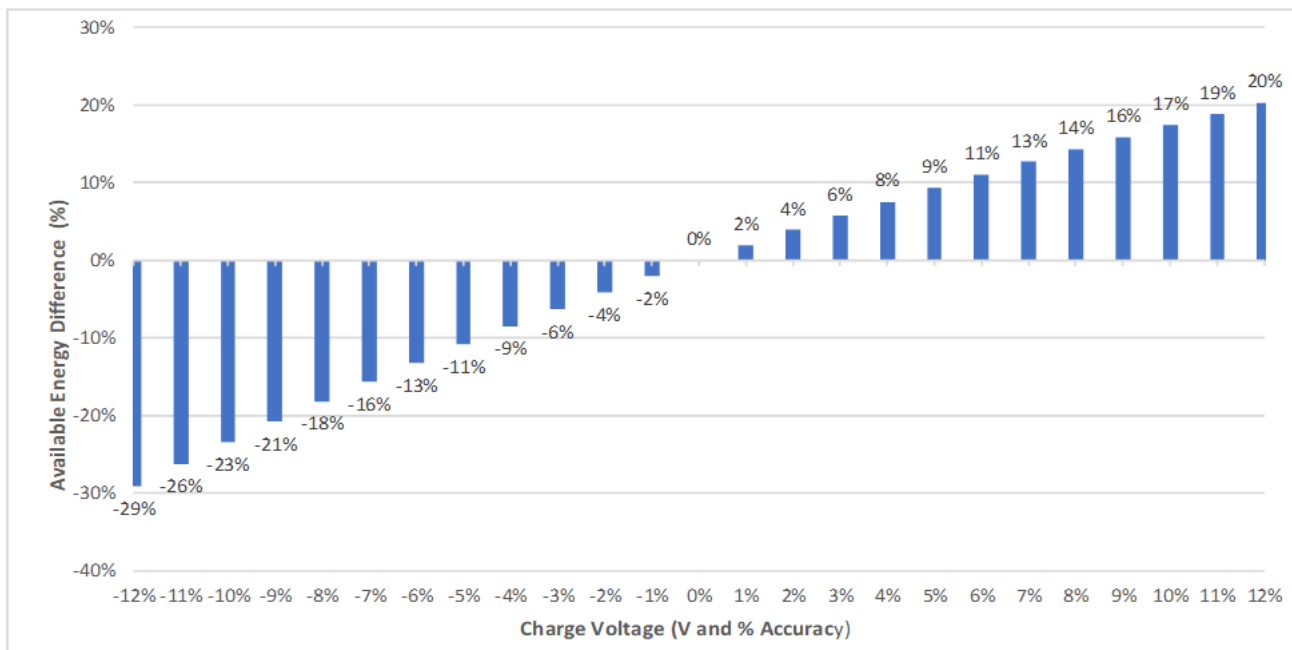


Figure 2. Available Energy Difference vs Charge Voltage

Boosting the supercapacitor voltage to power the system in backup mode

Another design challenge for supercapacitor systems is boosting to the supercapacitors' voltage to a level high enough to power the system. For charging inlets, the supercapacitors are charged to a total of 10V while the motor driver to unlock the door typically needs 60W (10V, 6A), so a boost converter is needed to step up the power while the supercapacitors are discharging. Two ways to implement boosting are shown in the block diagrams below: charging and boosting on the same IC or charging and boosting on separate ICs. The block diagram is the same for MCU farms except the Motor Driver component is replaced by MCUs. The main benefit of the charger and boost combined is reducing the total number of components and simplifying system design.

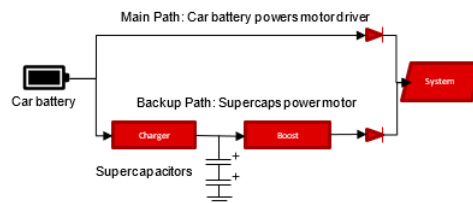


Figure 3. Charger and Boost Separate Block Diagram

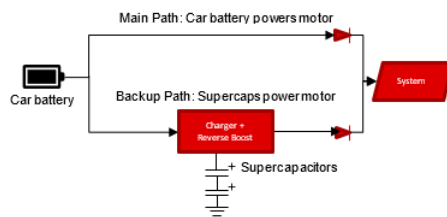


Figure 4. Charger and Boost Combined Block Diagram

BQ25173-Q1 and BQ25856-Q1 supercapacitor chargers

BQ25173-Q1 and BQ25856-Q1 are linear and switching supercapacitor chargers that can be used in automotive applications like charging inlets and MCU farms. BQ25173-Q1 can charge 1-4 supercapacitors in series and has the following benefits:

- Minimize current draw from car battery and supercapacitors with 2uA input quiescent current and 350nA quiescent current
- Charge supercapacitors to the target charge voltage with +/-1% charge voltage accuracy from -40°C - 125°C ambient temperature
- No electromagnetic interference (EMI) with linear charging topology
- Achieve charge current > 1A and better thermal performance with parallel BQ25173-Q1s

BQ25173-Q1 needs to be paired with a boost IC like in the charger + boost separate block diagram. BQ25856-Q1 is an excellent choice for higher power charging applications like MCU farms and comes with the following benefits:

- Supports high input and output voltage applications with up to 70V tolerance on the input and output
- Capable of charging and boosting supercapacitors with forward and reverse power modes
- Quickly charge the supercapacitors with up to 20A of charge current in forward and reverse mode
- Help charge supercapacitors to the target charge voltage with +/-0.5% charge voltage accuracy from -40°C - 125°C ambient temperature

The wide Vin range of the BQ25856-Q1 charge controller supports direct connection to 12V or 48V car batteries and the reverse boost mode function saves an additional boost converter IC while providing uninterrupted system power. BQ25173-Q1 and BQ25856-Q1 supercapacitor chargers help provide designs for low and high power supercapacitor backup applications.

Conclusion

Supercapacitor backup power is getting more popular as more systems in EVs are electrically driven, and charging inlets and MCU farms are two examples that require backup power. The BQ25173-Q1 and BQ25856-Q1 are two supercapacitor charger options that can be used in automotive backup applications. BQ25173-Q1 is a good option for EMI sensitive systems with linear topology and requires an external boost IC to discharge the supercapacitors. BQ25856-Q1 is a switching charge controller option for high power applications, and the reverse mode function can boost the supercapacitors to provide uninterrupted power to back up the system. BQ25173-Q1 and BQ25856-Q1 can help engineers design a variety supercapacitor backup systems for electrically powered car systems.

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated