

Step-Down Converter with Cable Voltage Drop Compensation

Juergen Neuhaeusler, Carsten Thiele

ABSTRACT

Output voltages of DCDC converters typically are precisely regulated at the location the feedback divider is connected. In case of longer connections to the load which, for example, is not on the same PCB the precision of the regulation suffers from the way the connection is established. If weight and connection count is critical, using sense wires or traces from the converter to the load is not an option. The weight also restricts the cross section of the wires which can be used. This means voltage drop which depends on the load current must be expected. Since this voltage drop cannot be fed back to the converter, compensation can only be done by adjusting the output voltage of the converter to match the voltage drop along the cables. This application report describes a circuit which addresses this problem at the output of a low voltage, highly efficient and small step-down converter which is typically used in such environments. The document also details the design and selection of the key components and provides measurement results showing the performance of the circuit.

1 Overview

In this example, the power circuit is implemented based on the TPS62130, a highly efficient synchronous step-down converter. To sense the load current, a current sense amplifier is designed based on the instrumentation amplifier, INA213. The complete circuit is shown in [Figure 1](#).

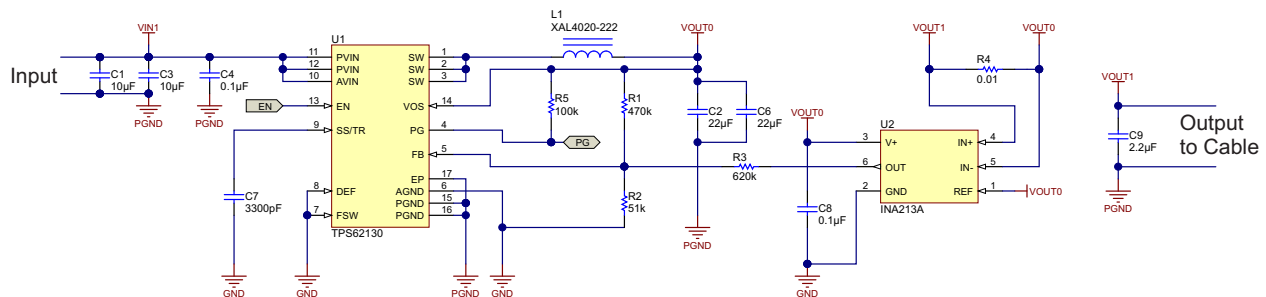


Figure 1. Circuit Schematic

The objective of the circuit is to provide an accurate 5-V supply at the end of the cable for a load which can vary between 0 A and 2 A. The cable connection in this example is 5 meters long (2 x 2.5 m) with a cross section of 0.5 mm². This circuit typically can be used to power a remote USB plug in a car which can be used for USB communication to the media hub and in addition to charge a USB device with 2 A of charge current. An example of an implementation is found in the [TI reference designs library](#).

2 Detailed Description

2.1 Current Feedback System

To measure the output current accurately, a current sense resistor is used. The voltage drop across the current sense resistor is measured by an instrumentation amplifier (INA213). The instrumentation amplifier generates an output voltage proportional to the output current of the DCDC converter (TPS62130). The output voltage of the instrumentation amplifier is connected as an offset voltage into the voltage feedback divider of the TPS62130 and changes the divider in a way that at increasing output current, the output voltage of the TPS62130 is increased. Knowing the voltage drop across the cable for a certain current or knowing the resistance of the cable connecting the load is required to derive the values for the resistors in the feedback network and the current sense resistor.

The minimum value for the resistance of the current sense resistor R_{SHmin} can be calculated using Equation 1.

$$R_{SHmin} = \frac{R_C}{G_{CS} - 1} \quad (1)$$

R_C is the resistance of the cable connected to the output of the TPS62130 and G_{CS} is the gain of the instrumentation amplifier.

After selecting an appropriate value for the current sense resistor, the maximum compensation voltage $\Delta V_{COMPmax}$ the instrumentation amplifier can generate in the feedback divider can be calculated using Equation 2. R_{SH} is the resistance of the selected current sense resistor and I_{OUTmax} is the maximum output current the converter needs to provide.

$$\Delta V_{COMPmax} = R_{SH} \cdot G_{CS} \cdot I_{OUTmax} \quad (2)$$

Equation 3 shows how to calculate the maximum voltage change ΔV_{OUTmax} at the output of the TPS62130. This voltage is adding to the nominal output voltage. The sum of this voltage and the nominal output voltage must not exceed the maximum output voltage rating of the TPS62130.

$$\Delta V_{OUTmax} = (R_C + R_{SH}) \cdot I_{OUTmax} \quad (3)$$

2.2 Voltage Feedback Network

For no output current the resistors in the feedback network can be calculated using the information in the [TPS62130 datasheet](#). To define the order of magnitude of the resistance values, the resistor R_2 needs to be defined. The [TPS62130 datasheet](#) gives guidance for that. With the value of R_2 , knowing the output voltage V_{OUT0} which needs to be regulated at the load and the feedback voltage of the TPS62130 V_{FB} , the value of R_{13} , the resistance of the resistor network with R_1 and R_3 in parallel can be calculated using Equation 4.

$$R_{13} = R_2 \cdot \left(\frac{V_{OUT0}}{V_{FB}} - 1 \right) \quad (4)$$

Using R_{13} , the resistance of R_1 and R_3 in parallel, together with the gain of the instrumentation amplifier G_{CS} , the resistance values of the cable connection R_C and the current sense resistor R_{SH} , R_3 can be calculated using Equation 5.

$$R_3 = R_{13} \cdot \left(\frac{G_{CS} \cdot R_{SH}}{R_C + R_{SH}} \right) \quad (5)$$

Since the value for R_3 and the parallel resistance of R_3 and R_1 is known, R_1 can now be calculated using Equation 6.

$$R_1 = \frac{R_{13} \cdot R_3}{R_3 - R_{13}} \quad (6)$$

3 Example

In the current example, an output voltage V_{OUT0} of 5.0 V should be regulated at a maximum output current I_{OUTmax} of 2.0 A. The resistance of the cable and the connecting headers R_C is calculated to be 0.20 Ω . The current amplifier is based on INA213. It has a fixed gain G_{CS} of 50.

Using Equation 1, the minimum resistance of the current sense resistor R_{SHmin} is calculated to be 4 m Ω . So, using a 10-m Ω current sense resistor for R_{SH} works properly.

With the cable resistance R_C and the maximum output current I_{OUTmax} the maximum voltage change ΔV_{OUTmax} at the output of the TPS62130 is calculated using Equation 3 to be 0.42 V. The maximum output voltage of TPS62130 is 6 V. So the calculated maximum voltage of 5.42 V at the output is well within TPS62130's recommended operating range.

Using the given values for R_{SH} , G_{CS} , and I_{OUTmax} in Equation 2 the maximum output voltage change $\Delta V_{COMPmax}$, the current feedback system can control is calculated to be 1 V.

Selecting 51 k Ω for R_2 , taking the feedback voltage V_{FB} of 800 mV from the [TPS62130 datasheet](#) and using all calculated parameters from above allows calculating R_{13} (268 k Ω , Equation 4), R_3 (620 k Ω , Equation 5), and R_1 (470 k Ω , Equation 6).

The resistors finally selected may not perfectly match the calculation results. To determine the error in the output voltage at different output currents I_{OUT} caused by the nonmatching resistors in the feedback network, Equation 7 and Equation 8 can be used with the selected resistor values.

$$R_{13} = \frac{R_1 \cdot R_3}{R_1 + R_3} \quad (7)$$

$$V_{OUT} = V_{FB} \cdot \left(\frac{R_{13}}{R_2} + 1 \right) + I_{OUT} \cdot \left[R_{SH} \left(\frac{R_{13} \cdot G_{CS}}{R_3} - 1 \right) - R_C \right] \quad (8)$$

Using the 470 k Ω for R_1 , 51 k Ω for R_2 , and 620 k Ω for R_3 in the example results in an output voltage of 4.994 V at 0-A output current and 4.993 V at 2-A output current.

4 Test Results

Unless the test did require a different setup, all the following tests are performed with an 8-V input voltage supply for the circuit. The load is represented by an electronic load, connected with a 5-m cable connection (2 x 2.5 m). In parallel to the load at the end of the cable, a 10- μ F capacitor is used to represent the input capacitor of the load circuit.

4.1 Load Regulation

Figure 2 shows the output voltage at the output of the TPS62130 which is increasing linearly with the load current and the regulated voltage at the load which is staying constant at 5 V. The relative error is shown in Figure 3.

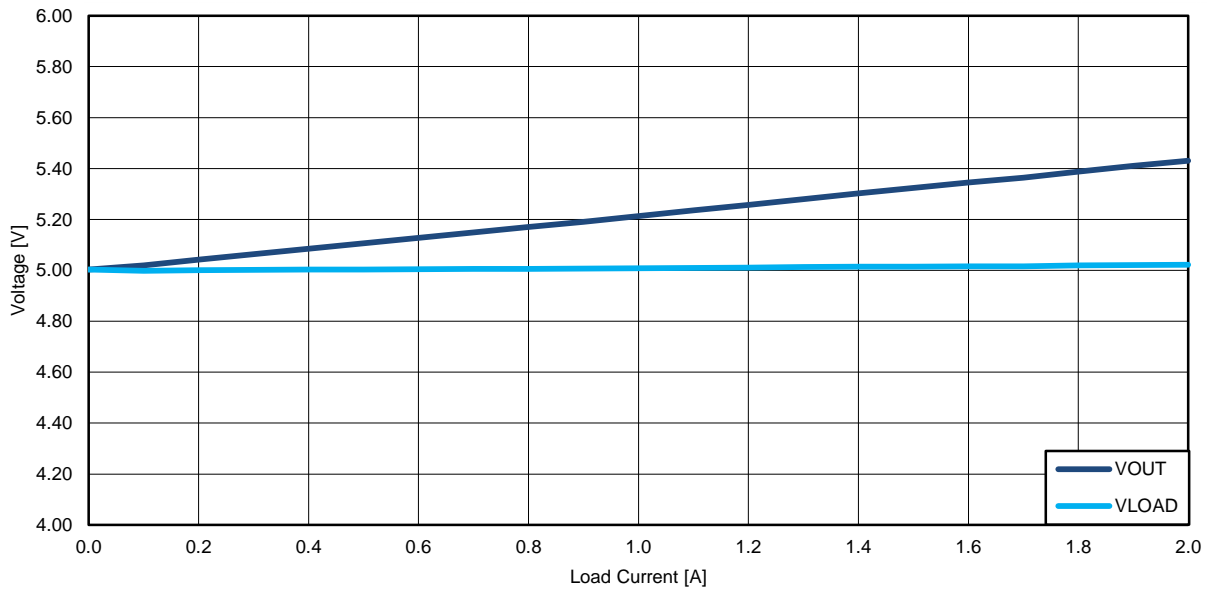


Figure 2. Converter Output Voltage and Regulated Voltage at the Load

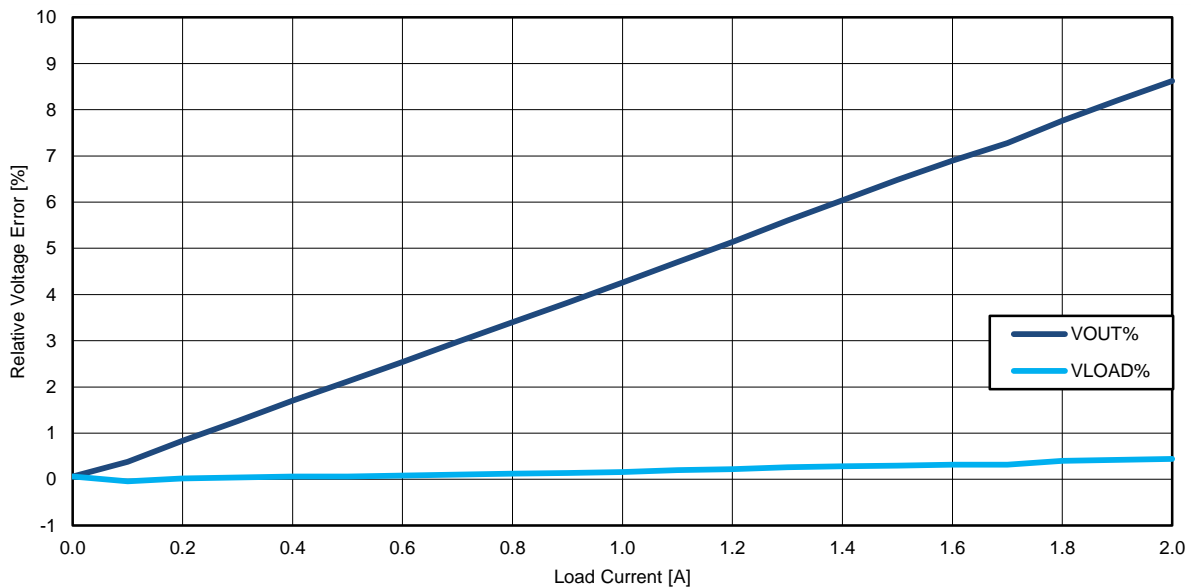


Figure 3. Error of the Converter Output Voltage and Regulated Voltage at the Load

4.2 Load Transient

Figure 4 shows the load transient behavior of the converter. The output voltage of the TPS62130 and the voltage regulated at the load are shown. Since in this circuit there is no direct feedback of the voltage error at the load, the voltage drop during load transients can be significant. In this example, the voltage variation during load transients is up to $\pm 10\%$.

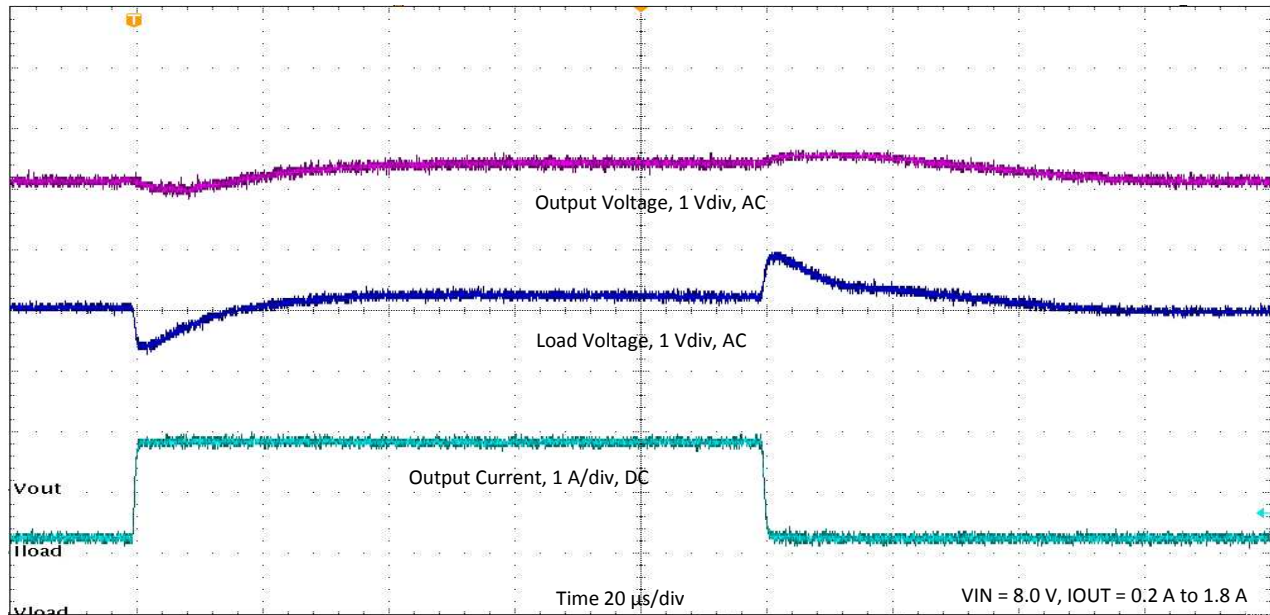


Figure 4. Load Transient

4.3 Line Transient

Figure 5 shows the line transient behavior of the converter. The control topology implemented in the TPS62130 (DCS-Control™), allows maintaining a well-regulated load voltage at the output of the TPS62130 and at the load. The supply voltage change is almost not visible in the curves of the output and load voltage.

If the line transient goes down to voltages lower than the programmed output voltage at the output of the TPS62130, as shown in Figure 6, the output voltage and the load voltage follow the curve of the input voltage with TPS62130 in a 100% duty cycle mode. As soon as the input voltage is again high enough to regulate the output voltage, the control of TPS62130 recovers smoothly.

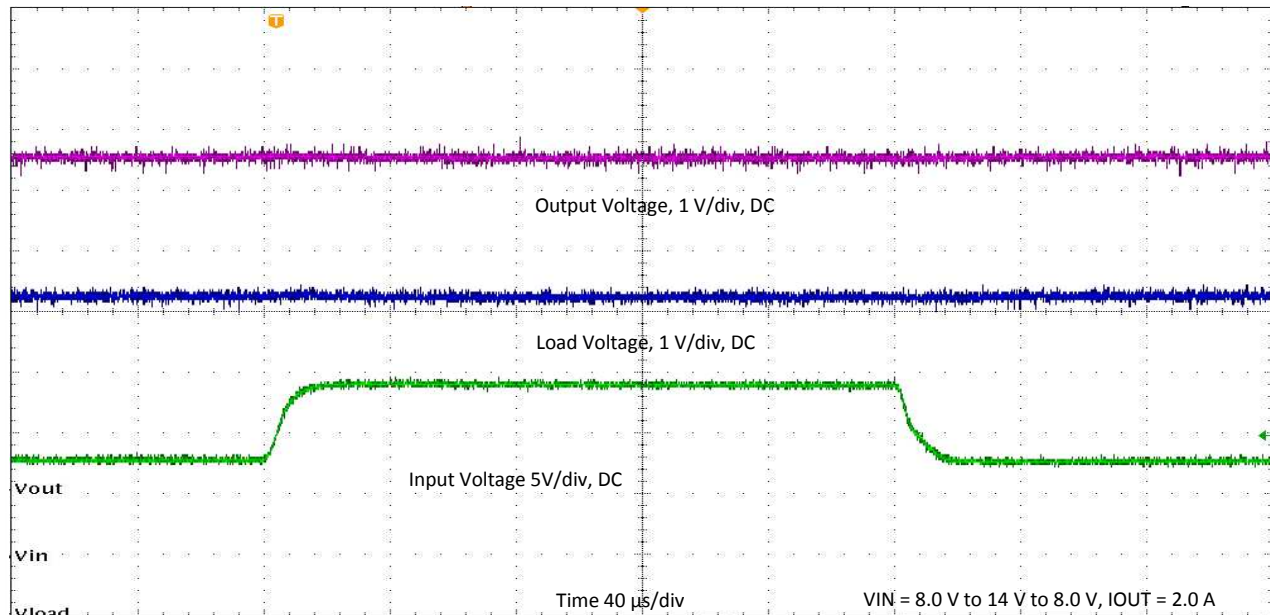


Figure 5. Line Transient

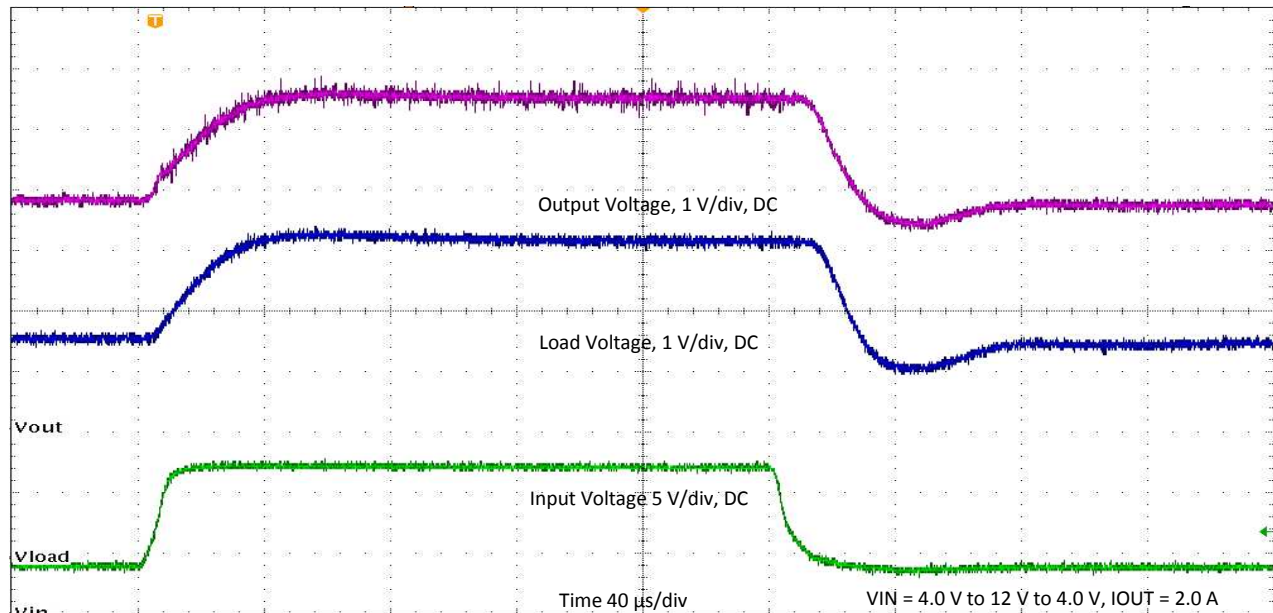


Figure 6. Line Transient into Undervoltage

4.4 Startup

Figure 7 shows the startup behavior of the proposed circuit. The voltage at EN is directly following the input voltage which is just turned on in this measurement. This means the converter starts operating as soon as the input voltage is higher than its undervoltage threshold. The output voltage and the load voltage are ramped up smoothly to the programmed voltage levels. When removing the input voltage, the converter stops operating and actively discharges the output.

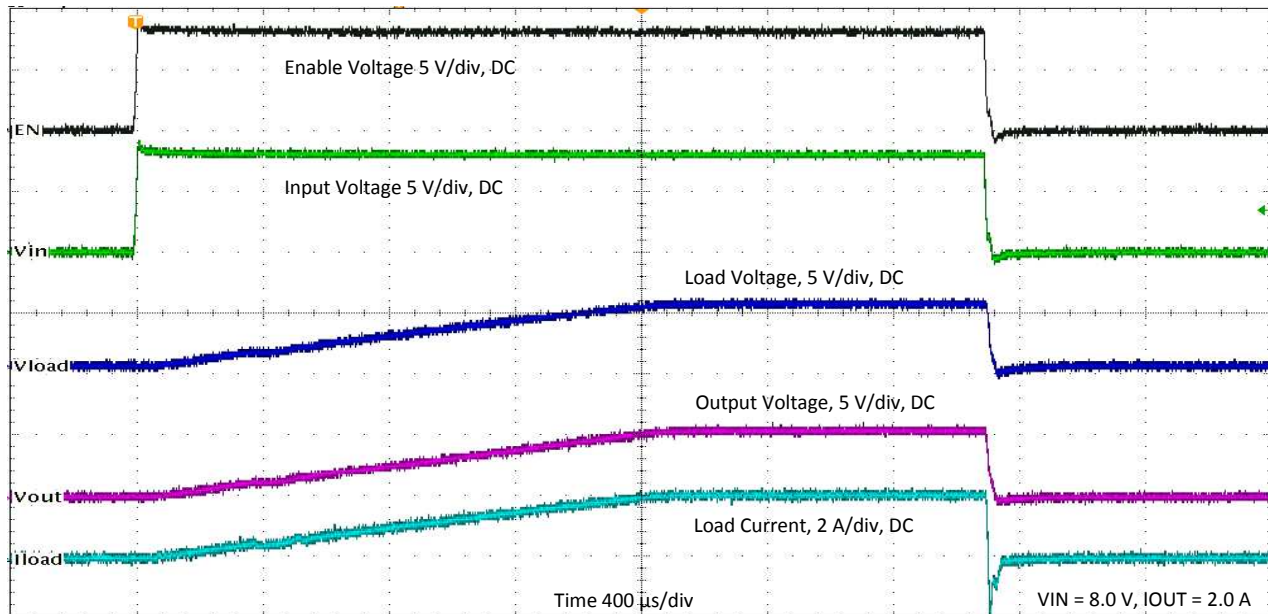


Figure 7. Startup

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com