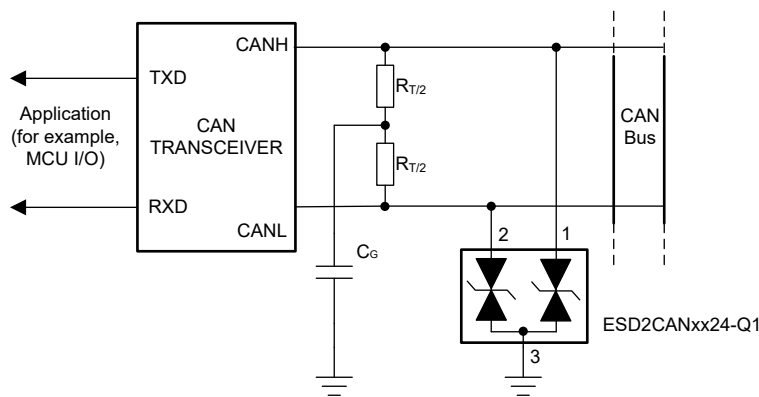


# Protecting Automotive CAN Bus Lines



The Controller Area Network (CAN bus) is a message-based protocol designed to allow the Electronic Control Units (ECUs) to communicate with each other in a reliable priority-based system. CAN is a differential 2-wire interface, also referred to as the Main Bus in an automotive system.

Many CAN transceivers have built-in ESD protection cells, but to keep the size of the chip down, most of the CAN transceivers only protect only up to 8 kV. *CANH* and *CANL* lines in any CAN interface need to be protected against the unpredictable ESD strikes that can go as high as 30 kV. CAN ESD devices can be used to protect the CAN lines and the downstream components from catastrophic failure.



**CAN ESD Application Diagram**

## Design Considerations

- 24-V working voltage ( $V_{RWM}$ ), this voltage is high enough to account for short-to-battery protection for a 12-V battery system.
- Make sure the clamping voltage is lower than the absolute maximum voltage ratings (typically 58 V – 70 V) of the *CANH* and *CANL* pins of the CAN transceiver used.
- Requires a bidirectional diode to account for line faults and miswiring at the battery side.
- Line capacitance must be low enough to provide the signal integrity through the ESD protection diode with minimum signal degradation.

The CAN protocol comes in many different flavors and speeds ranging from 1Mbps for a CAN and up to 10Mbps – 20Mbps for CAN-XL.

The maximum allowable line capacitance of a diode is a function of the signal frequency being protected. When considering a system design, other components like filtering capacitance and input capacitance of the transceivers can add to the total bus capacitance. As a recommended guideline, a diode with < 12 pF to 15 pF is able to support CAN, CANFD, and CANXL protocols communication speed requirements for a majority of designs.

### Recommended Parts

CAN Device	Number of Channels	V <sub>RWM</sub>	IEC61000-4-2 Contact (kV)	Line Capacitor (pF)	Protocols	Package
<a href="#">ESD2CAN24-Q1</a>	2	24 V	±30	3	CAN CANFD CANXL	SOT-23 (2.92 × 2.37) SC-70 (2.0 × 1.25)
<a href="#">ESD2CANFD24-Q1</a>	2	24 V	±25	2.5		SOT-23 (2.92 × 2.37)
<a href="#">ESD2CANXL24-Q1</a>	2	24 V	±20	1.75		SOT-23 (2.92 × 2.37)

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, on-state resistance, and other features.

#### Target Applications and End Equipment

- [Front camera, Rear camera](#)
- [Drive assist ECU](#)
- [Telematics control unit](#)
- [Medium and short range radar](#)
- [Body control module \(BCM\) and Zonal module](#)

#### Learn More

- Texas Instruments, [System-Level ESD Protection Guide Selection Guide](#)
- Texas Instruments, [Protecting Automotive CAN Bus Systems from ESD Overvoltage Events Application Note](#)
- Texas Instruments, [ESD Packaging and Layout Guide Application Note](#)
- Texas Instruments, [ESD fundamentals, part 4: ESD capacitance Technical Article](#)
- Need additional assistance? Ask our engineer a question on TI E2E™ [ESD and TVS Protection Devices: Key Collateral and FAQs](#)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated