

Benefits of a multiphase buck converter

By David Baba

Applications Engineering Manager

Introduction

Single-phase buck controllers work well for low-voltage converter applications with currents of up to approximately 25 A, but power dissipation and efficiency start to become an issue at higher currents. One suitable approach is to use a multiphase buck controller. This article briefly discusses the benefits of using a multiphase buck converter versus a single-phase converter and the value a multiphase buck converter can provide when implemented.

Figure 1 shows a two-phase circuit. From this circuit's waveforms, shown in Figure 2, it is clear that the phases are interleaved. Interleaving reduces ripple currents at the input and output. It also reduces hot spots on a printed circuit board or a particular component. In effect, a two-phase buck converter reduces the RMS-current power dissipation in the FETs and inductors by half. Interleaving also reduces transitional losses.

Output-filter consideration

The output-filter requirements decrease in a multiphase implementation due to the reduced current in the power stage for each phase. For a 40-A, two-phase solution, an average current of only 20 A is delivered to each inductor. Compared to a 40-A single-phase approach, the inductance and inductor size are drastically reduced because of lower average current and lower saturation current.

Output ripple voltage

Ripple-current cancellation in the output-filter stage results in a reduced ripple voltage across the output capacitor compared to a single-phase converter. This is another reason why a multiphase converter is preferred. Equations 1 and 2 calculate the percentage of ripple current canceled in each inductor.

$$m = D \times \text{Phases} \tag{1}$$

and

$$I_{\text{Rip_norm}}(D) = \text{Phases} \times \frac{\left[D - \frac{m \cdot D}{\text{Phases}} \right] \times \left[\frac{1 + m \cdot D}{\text{Phases}} - D \right]}{(1 - D) \times D}, \tag{2}$$

Figure 1. Two-phase buck converter


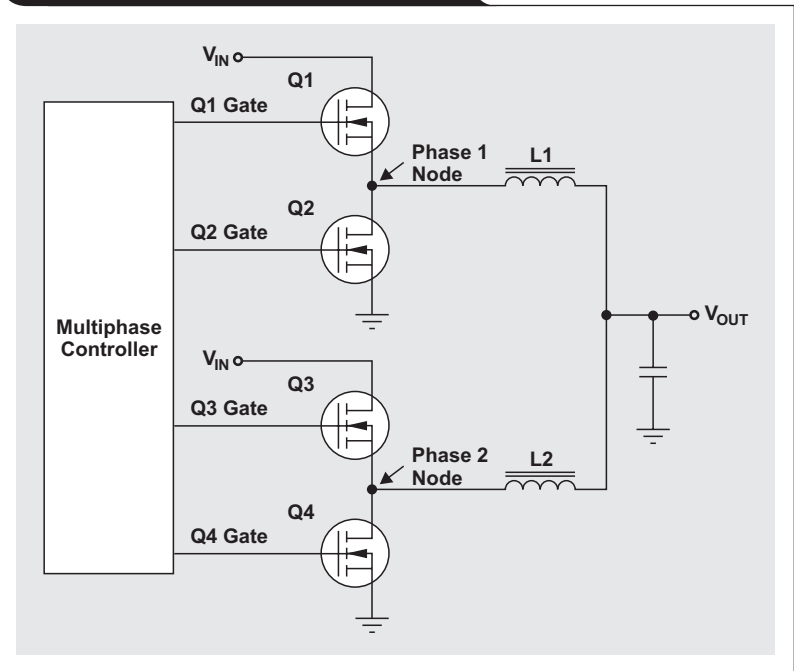


Figure 2. Node waveforms of phases 1 and 2

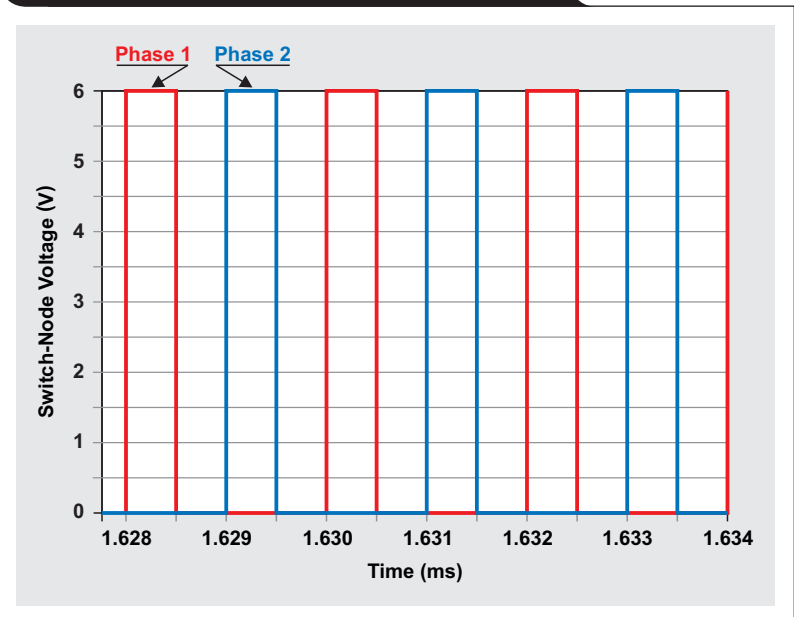


where D is the duty cycle, I_{Rip_norm} is the normalized ripple current as a function of D , and m_p is the integer of m . Figure 3 plots these equations. For example, using two phases at a 20% duty cycle (D) yields a 25% reduction in ripple current. The amount of ripple voltage the capacitor must tolerate is calculated by multiplying the ripple current by the capacitor's equivalent series resistance. Clearly, both maximum current and voltage requirements are reduced.

Figure 4 shows the simulation results for a two-phase buck converter at a duty cycle of 25%. The inductor ripple current is 2.2 A, but the output capacitor sees only 1.5 A due to ripple-current cancellation. With a duty cycle of 50% and two phases, the capacitor sees no ripple current at all.

Load-transient performance

Load-transient performance is improved due to the reduction of energy stored in each output inductor. The reduction in ripple voltage as a result of current cancellation contributes to minimal output-voltage overshoot and undershoot because many cycles will pass before the loop responds. The lower the ripple current is, the less the perturbation will be.

Figure 3. Normalized capacitor ripple current as a function of duty cycle

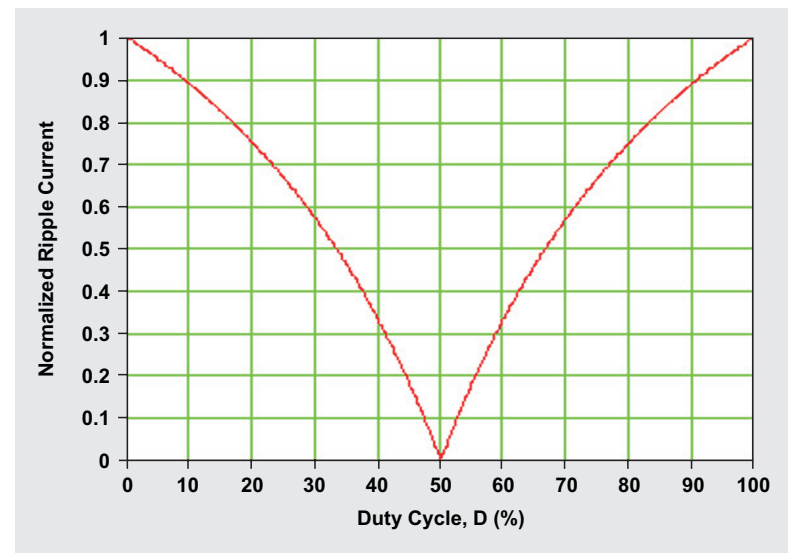

Cancellation of input RMS ripple current

The input capacitors supply all the input current to the buck converter if the input wire to the converter is inductive. These capacitors should be carefully selected to satisfy the RMS-ripple-current requirements to ensure that they

Figure 4. Cancellation of inductor ripple current with $D = 25\%$


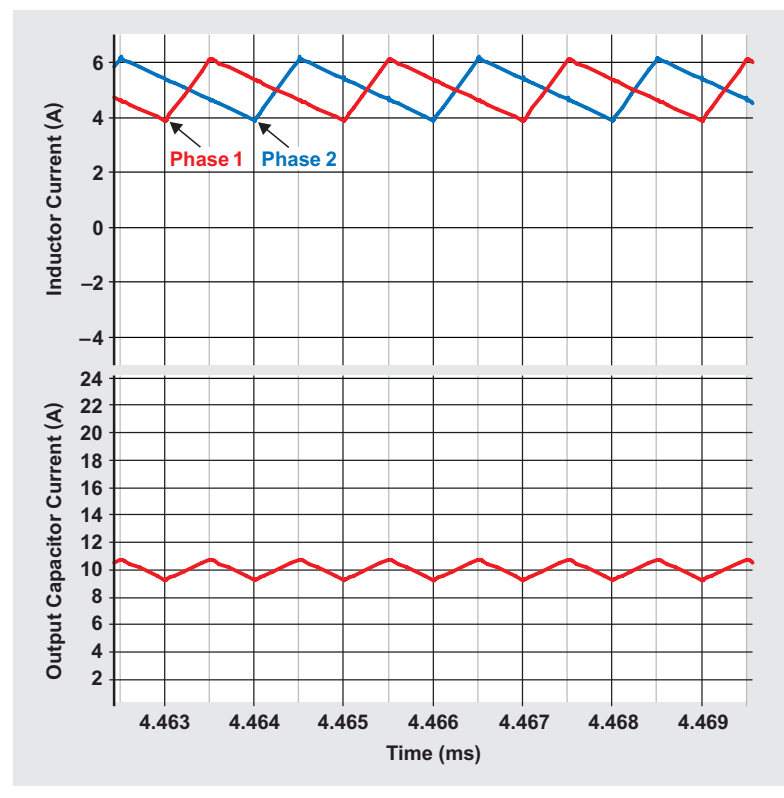


Figure 5. Normalized input RMS ripple current as a function of duty cycle

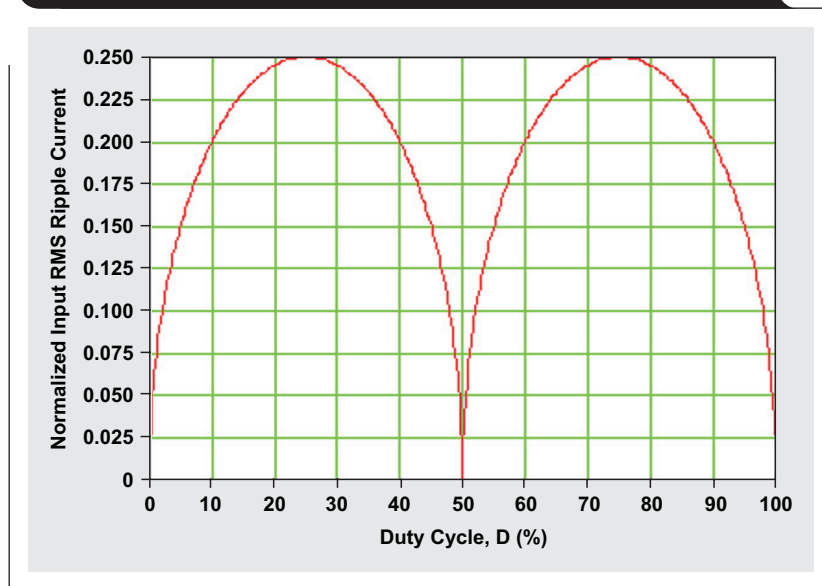

do not overheat. It is well understood that, for a single-phase converter with a duty cycle of 50%, the worst-case input RMS ripple current is typically rated at 50% of the output current. Figure 5 and Equation 3 indicate that, for a two-phase solution, the worst-case RMS ripple current occurs at duty cycles of 25 and 75% and is only 25% of the output current.

$$I_{\text{Input_norm}}(D) = \sqrt{\left[D - \frac{mp(D)}{\text{Phases}} \right] \times \left[\frac{mp(D) + 1}{\text{Phases}} - D \right]} \quad (3)$$

The value of a multiphase solution as compared to a single-phase solution is clear. Less input capacitance can be used to satisfy the RMS-ripple-current demands of the buck stage.

Application example

The LM3754 high-power-density evaluation board delivers 1.2 V at 40 A from a 12-V input supply. The board is 2 × 2 inches, and the area covered by the components is 1.4 × 1.3 inches. The switching frequency of each phase is set to 300 kHz. Table 1 provides a summary of these and other operating conditions. The components are placed on a 4-layer board, with 1 oz. of copper on all layers. Additional pins are included on this board for remote sensing, and a pin is used for margining the output voltage.

Because the LM3754 evaluation board is designed to operate in high-power-density configurations, it utilizes the optimized input capacitors to provide the reduced RMS ripple current that is required. The evaluation board also has a low ripple voltage and good transient performance. The board layout shown in the LM3754 application note¹ should be followed as closely as possible. However, if this

Table 1. Operating conditions of LM3754 evaluation board

Input voltage	10.8 to 13.2 V
Output voltage	1.2 V ± 1%
Output current	40 A (max)
Switching frequency	300 kHz
Module size	2 × 2 inches
Circuit area	1.4 × 1.3 inches
Module height	0.5 inches
Air flow	200 LFM
Number of phases	2

is not possible, close attention should be paid to these considerations. Several more layout considerations will now be described, followed by the test results from a test board using the LM3754. These results are presented in Figures 6–11 on pages 12–13. They are typical of what one can expect to achieve or even improve upon in making the necessary modifications.

Layout considerations

High-current traces require enough copper to minimize voltage drops and temperature rises. The general rule of using a minimum of 7 mils per ampere was applied for the 2 oz. of copper used, and 14 mils per ampere for the inner layers for the 1 oz. of copper used. The input capacitors of each phase were placed as close as possible to the top MOSFET drain and the bottom MOSFET source to ensure minimal ground “bounce.”

Signal components connected to the IC

All small-signal components that connected to the IC were placed as close to it as possible. Decoupling capacitors for V_{REF} and V_{CC} were also placed as close as possible to the IC. The signal ground (SGND) was configured to ensure a low-impedance path from the ground of the signal components to the ground of the IC.

SGND and PGND connections

Good layout techniques include a dedicated ground plane; this board dedicated as much of inner-layer 2 as possible for the ground plane. Vias and signal lines were strategically placed to avoid high-impedance points that could pinch off wide copper areas. The power ground (PGND) and SGND were kept separate, only connected to each other at the ground plane (inner layer 2).

Gate drive

The designer should ensure that a differential pair of traces is connected from the high-gate output to the top MOSFET gate and the return, which is the switch node. The distance between the controller and the MOSFET should be as short as possible. The same procedure should be followed for the LG and GND pins when the traces for the low-side MOSFET are routed.

A differential pair of traces must also be routed from the CSM and CS2 pins to the RC network located across the output inductor. Notice in the layout in Reference 1 that, in order to provide additional noise suppression, the filter capacitor is split into two capacitors—one positioned by the inductor and the other close to the IC. These sense lines should not be run for long lengths in close proximity to the switch node. If possible, they should be shielded by using a ground plane.

Minimizing the switch node

To follow the common rules of keeping the switch-node area as small as possible but large enough to carry high currents, the switch node was built on multiple layers. Because the small evaluation board essentially folds back on itself from input to output, the switch node naturally sits on the outer layer, and the IC sits directly underneath the switch node. Therefore, it is essential to keep the switch node well away from the sense lines and also from the IC. Hence, the switch node was strategically placed facing outwards toward the edge of the board.

Conclusion

There are a number of benefits to using multiphase buck converters, such as higher efficiency from lower transitional losses; lower output ripple voltage; better transient performance; and lower ripple-current-rating requirements for the input capacitor. Some examples of multiphase buck converters that can deliver the full benefits described herein are the LM3754, LM5119, and LM25119 families.

Reference

1. Robert Sheehan and Michael Null, "LM3753/54 evaluation board," National Semiconductor Corp., Application Note 2021, Dec. 15, 2009 [Online]. Available: <http://www.national.com/an/AN/AN-2021.pdf>

Related Web sites

power.ti.com

www.ti.com/product/partnumber

Replace *partnumber* with LM3754, LM5119, or LM25119

Test results

Figure 6. Efficiency plot with 12-V input

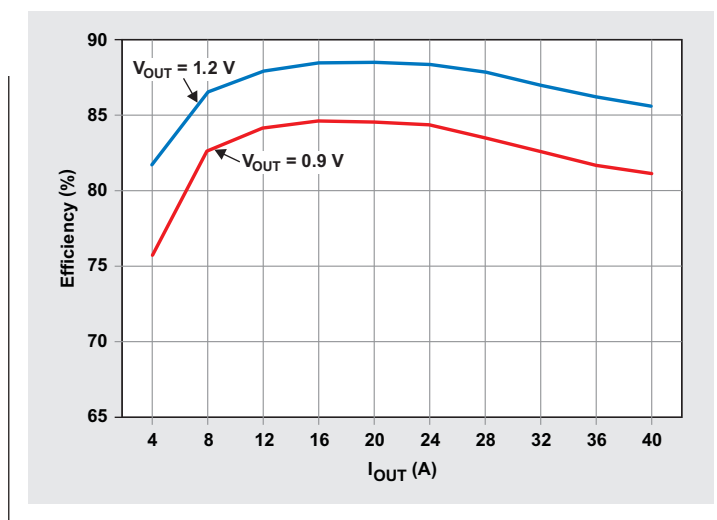


Figure 7. Power loss with 12-V input

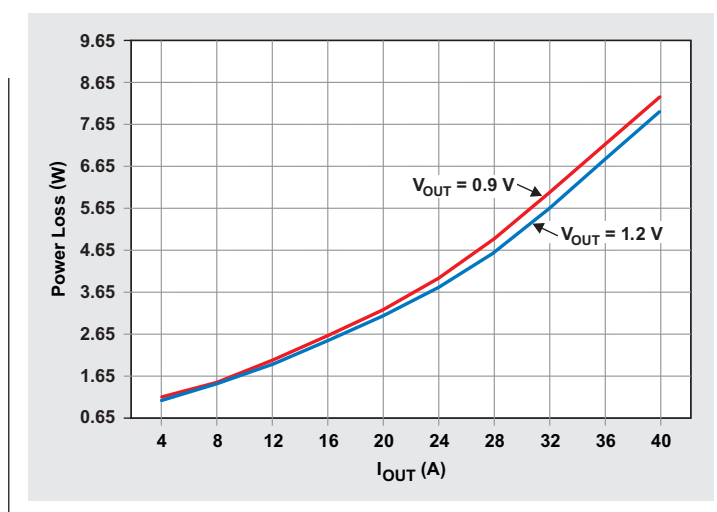


Figure 8. Switch-node voltages

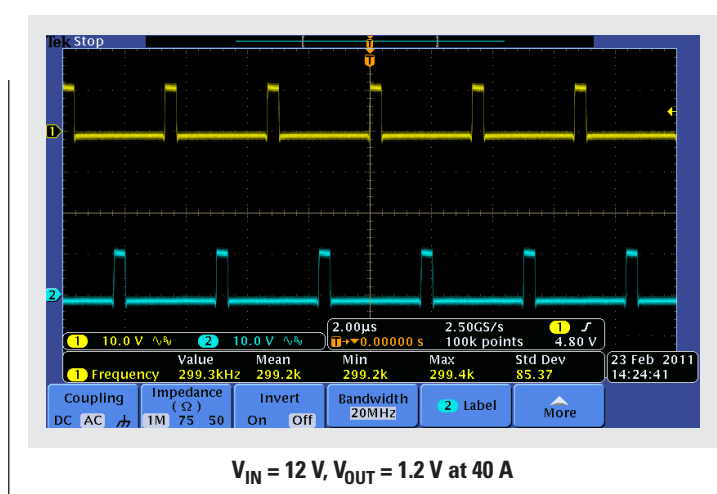


Figure 9. Output voltage ripple

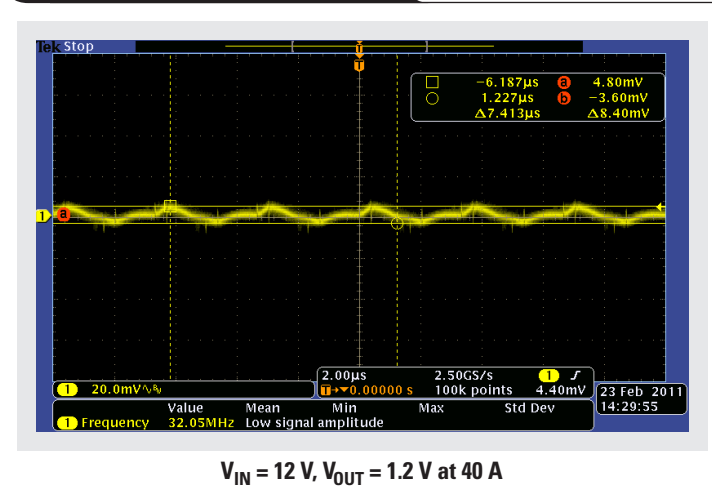


Figure 10. Transient response: 20 µs with 10-A load step (undershoot/overshoot ~ 27 mV)


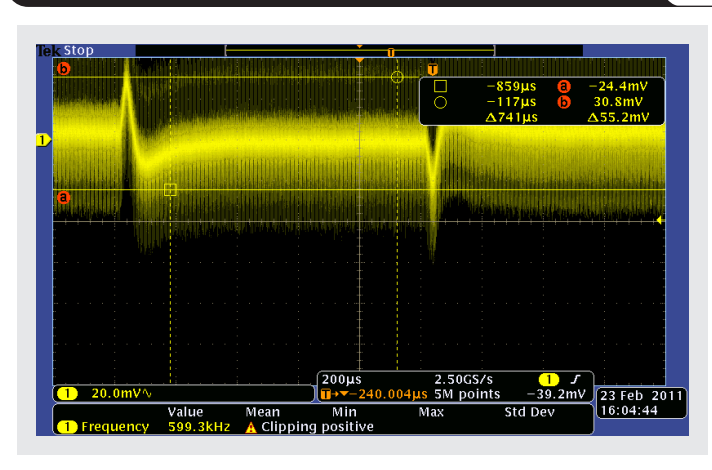


Figure 11. V_{OUT} start-up for 1.2-V output with 40-A load

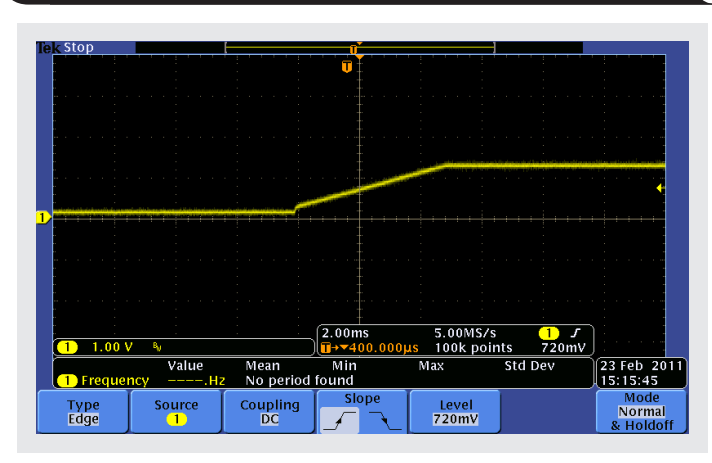

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(972) 644-5580
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Note: Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A011012

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2012, Texas Instruments Incorporated