

AN-1250 Inductive Based Switching Regulator Circuits Provide High Efficiency White LED Drives

ABSTRACT

White LEDs are quickly becoming the light of choice for backlighting of small color displays because of their falling costs, longer life, and smaller size. The problem this presents is that the white LED has a high voltage drop (3.1 V to 4.0 V depending on manufacturer) as compared to the monochrome displays' green LED with a voltage drop of 1.8 V to 2.7 V. Whereas the green LED can be powered directly from the commonly used Li-Ion battery, with a linear regulator, and a ballast resistor, the white LED used for backlight or frontlight purposes will requires the battery voltage be boosted.

Contents

1	Introduction	2
2	The Switching Regulator	2

List of Figures

1	Basic LED Driver for Two to Eight LEDs at up to 30 mA Each	2
2	LED Driver With Improved Compensation for Faster Setup	3
3	High-Efficiency LED Driver With Low Components Count Drives Two to Eight LEDs at up to 20 mA Each	3
4	LM2622 Efficiency (4 LEDs)	4
5	LM2704 Efficiency (4 LEDs)	4

1 Introduction

TI has many solutions for driving LEDs including switched capacitor converters and inductive based switching regulators. This application note will describe some methods of driving white LEDs using inductive based switching regulators and some of the benefits of each. The main areas of concern for most designers of portable equipment are efficiency, size, cost, functionality, and LED current matching. Balancing these competing demands will help designers make the right choice for his or her application.

2 The Switching Regulator

A boost switching regulator set up as a constant current source can drive several white LEDs in series, keeping brightness constant even over a wide variation in supply voltage.

Figure 1, Figure 2 and Figure 3 show some designs using the LM2622 PWM boost regulator and the LM2704 PFM boost regulator.

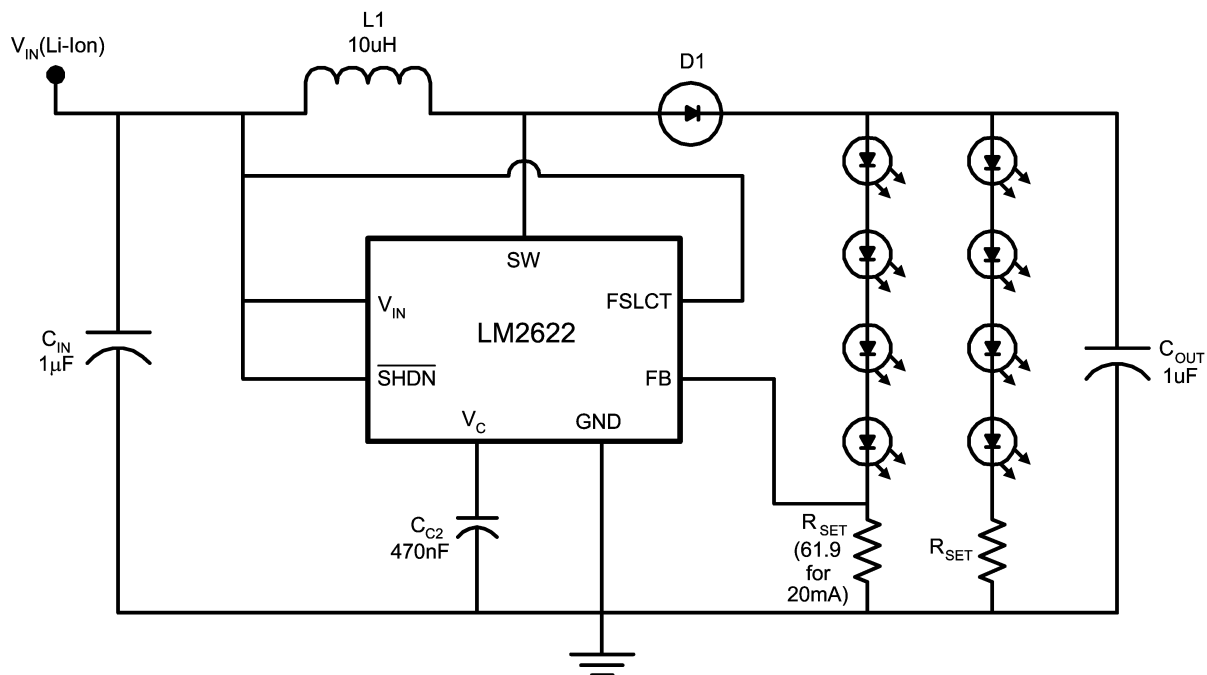


Figure 1. Basic LED Driver for Two to Eight LEDs at up to 30 mA Each

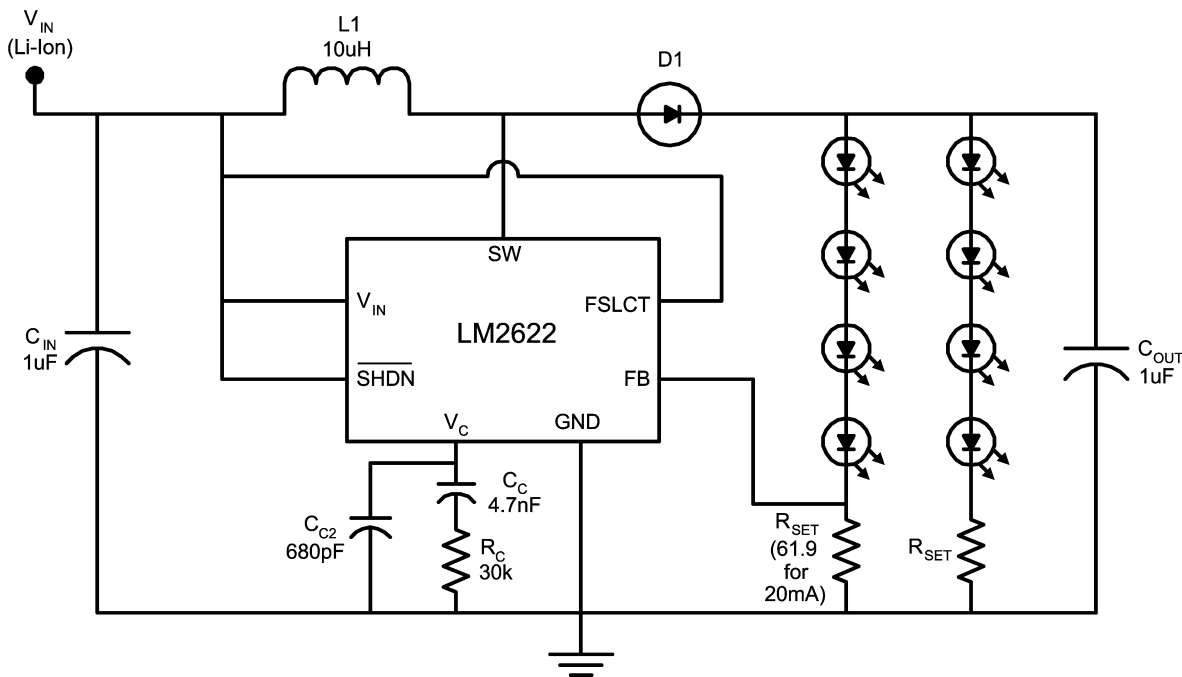


Figure 2. LED Driver With Improved Compensation for Faster Setup

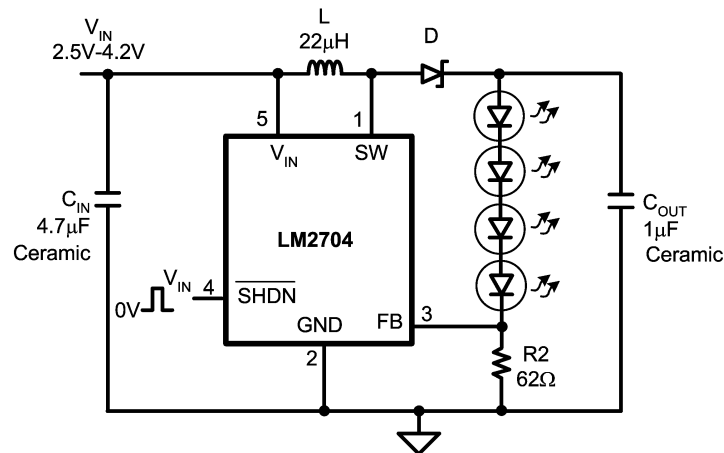


Figure 3. High-Efficiency LED Driver With Low Components Count Drives Two to Eight LEDs at up to 20 mA Each

Figure 1 is capable of driving 2 to 8 white LEDs at up to 30 mA each. When using four or fewer, the second string of LEDs (not connected to the FB pin) is eliminated. The desired LED current is set using the equation:

$$I_D = (1.26V/R_{SET}) \tag{1}$$

When all of the LEDs are in series with each other (using up to four), there is perfect current matching through each.

When a second string of LEDs is added, it too will have perfect current matching through its LEDs, but not with the first string of LEDs. The current matching between the two strings will depend on how well the LED forward voltages match. Probability works to your advantage because the sum of four LEDs VF tend to balance widely varying VF in individual LEDs.

An inductive switching regulator also has a relatively high efficiency of typically 70% to 85% over the Li-Ion input voltage range (see [Figure 5](#) for actual LM2622 measurements). However, higher efficiency comes at the expense of using an inductor for energy storage versus switched capacitor solutions that use only capacitors. The circuit in [Figure 1](#) is best suited for static LED currents so dimming via a pulse width modulated (PWM) (square wave at the shutdown pin) signal is not recommended. This is due to the slow startup time of the circuit, which does not allow a sufficiently fast PWM signal to eliminate visible blinking. [Figure 1](#) is a reduced component count version of [Figure 2](#) at the expense of functionality.

[Figure 2](#) is identical in description to [Figure 1](#), with the only difference being a change in how it is compensated. This requires an extra capacitor and resistor on the VC pin, but provides a faster startup time. The brightness of the LEDs can now be controlled using a PWM signal on the shutdown (SHDN) pin. This signal can be anywhere from 60Hz to 200Hz and the brightness is controlled by the duty cycle of the PWM signal (50% duty cycle equals approximately 50% LED current).

[Figure 3](#) shows the LM2704 pulse frequency modulated (PFM) regulator. The LM2704 circuit has the same benefits of current matching and high efficiency as the LM2622 circuit but with a few advantages. Since it is a PFM architecture, it has a slightly better efficiency than the LM2622. It is also more inherently stable, which means a lower component count since the compensation R's and C's are no longer required. The LM2704 circuit is also physically smaller since it comes in a SOT-23 package versus the MSOP package of the LM2622. The costs of these advantages are a lower current output and a larger input capacitor. The LM2704 is only capable of driving up to 8 LEDs at 20 mA each, but this is plenty for most applications. PFM circuits are also more susceptible to noise and require more energy storage at the input. This requires the use of a large input capacitor relative to the PWM architecture.

In conclusion, the switching regulator approach is desirable for applications that require two to eight LEDs, the highest efficiency, basic brightness functionality, and precise current matching.

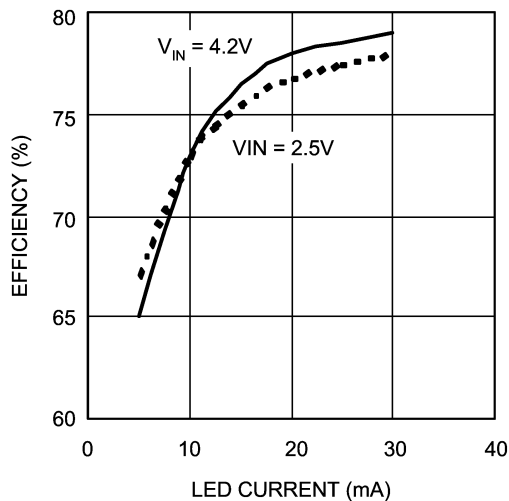


Figure 4. LM2622 Efficiency (4 LEDs)

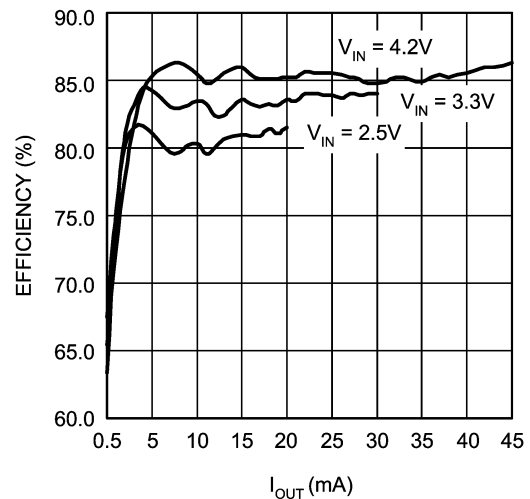


Figure 5. LM2704 Efficiency (4 LEDs)

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com