

Designing an EMC-compliant Interface to Motor Position Encoders – Part 5



Martin Staebler

The first part of this blog series provided an [overview of the various types of motor-position encoders](#) and their interfaces. Parts 2, 3 and 4 explained how to design an interface to absolute encoders with serial interfaces such as [EnDat 2.2](#), [bidirectional serial synchronous \(BiSS\)](#) and [HIPERFACE DSL](#). In this Part 5, I will introduce incremental sine/cosine (sin/cos) encoders with analog output and outline the design of an electromagnetic compatibility EMC-compliant interface.

Sin/cos rotary or linear encoders enable high-resolution position measurement. The high-resolution position is encoded into two 90° phase-shifted sinusoidal differential signals A+, A- and B+, B-, where the number of sinusoidal periods over one mechanical revolution equals the line count of the sin/cos encoder. A further differential analog output is the reference-marker signals R+ and R-, which allows for absolute-angle position detection. [Figure 1](#) shows the output signals A, B and R, where A, B and R represent the differential signals of A+ minus A-, B+ minus B- and R+ minus R-, respectively.

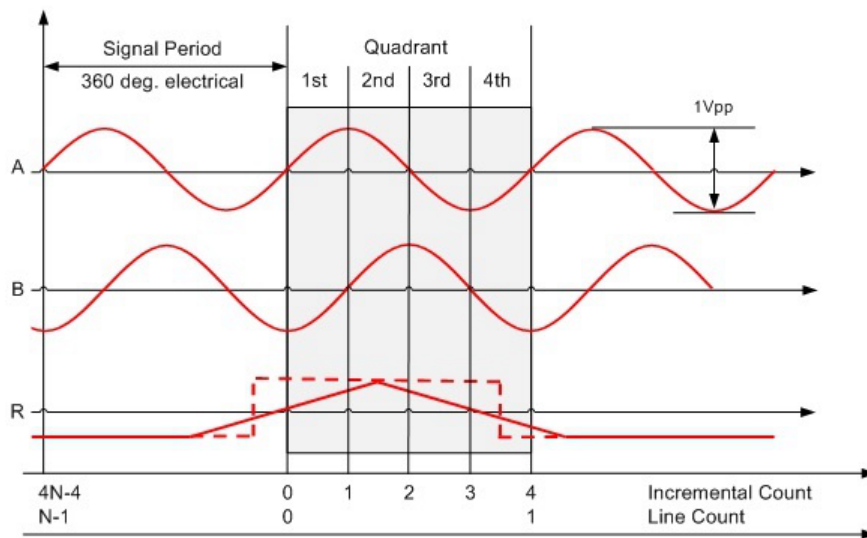


Figure 1. Output Voltage Signals a, B and Marker R of Sin/cos Encoders with N Line Counts per Revolution

Let’s have a closer look at the typical electrical specification of sin/cos encoder’s output signals, as they are an important criterion for the specification of the analog components of the interface design.

The differential output signal amplitude is either 11µA-pp, or more commonly 1V-pp, with a typical 2.5V DC offset.

The frequency of the sin/cos encoder’s differential output signal, A and B, depends on the line count of the encoder as well as the mechanical speed, as outlined in [Figure 2](#):

$$f_{A,B} [Hz] = N \cdot v [rpm] \cdot \frac{1}{60} \quad (1)$$

Figure 2.

where N is the sin/cos encoder's line count and v is the mechanical speed in revolutions per minute. Figure 3 lists typical examples for 1Vpp sin/cos encoders.

Sin/cos encoder model	Signal level A, B	DC offset	Line count N	Limit frequency (-3dB)
1	0.6Vpp to 1.2Vpp, 1Vpp typical	$2.5V \pm 0.5V$	50 ... 5000	$\geq 180\text{kHz}$
2	1Vpp ($\pm 10\%$)	$2.5-V \pm 100\text{mV}$	1,024 or 2,048	400kHz

Figure 3. Encoder Output Signals a, B Examples

Now let's have a look on how you decode the angle position from these output signals, as this is important for the system architecture of the interface design

A typical method to retrieve the sin/cos encoder's angle uses separate hardware blocks for the incremental count (coarse angle) and the interpolated incremental phase (fine angle using the inverse tangent method), as outlined in Figure 4.

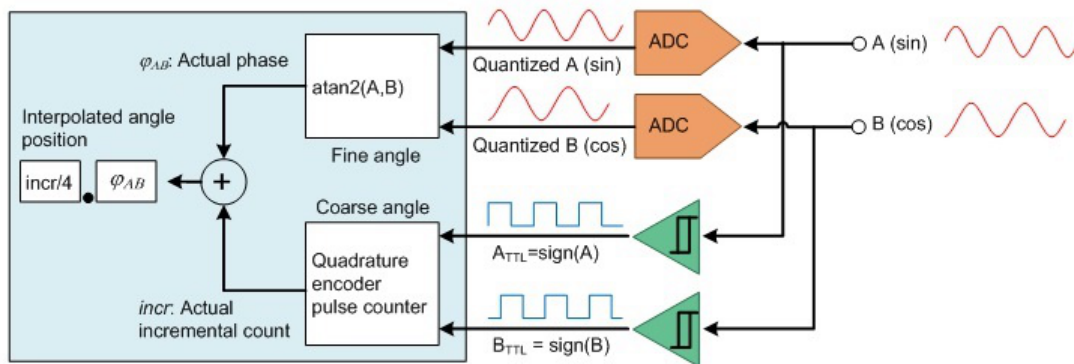


Figure 4.

Two comparators, one for sine and one for cosine, generate digital quadrature-encoded signals A and B, which drive a directional up- and down-counter, often referred to as a quadrature-encoded pulse counter. The analog bandwidth of the dual-sampling analog-to-digital converter (ADC) needs to be at least equal to the maximum sine/cosine frequency.

It is important that the sinusoidal signals, A and B, and the incremental count, incr, sample and latch simultaneously.

Practically, the digitized signals, A_{TTL} and B_{TTL} , have a phase shift compared to the analog signals. This phase shift is typically due to hysteresis and propagation delay of the comparators and nonideal sampling synchronization. This means that upon each transition to the next quadrant, the incremental counter may not be updated immediately because of phase lag. See the first quadrant in Figure 5.

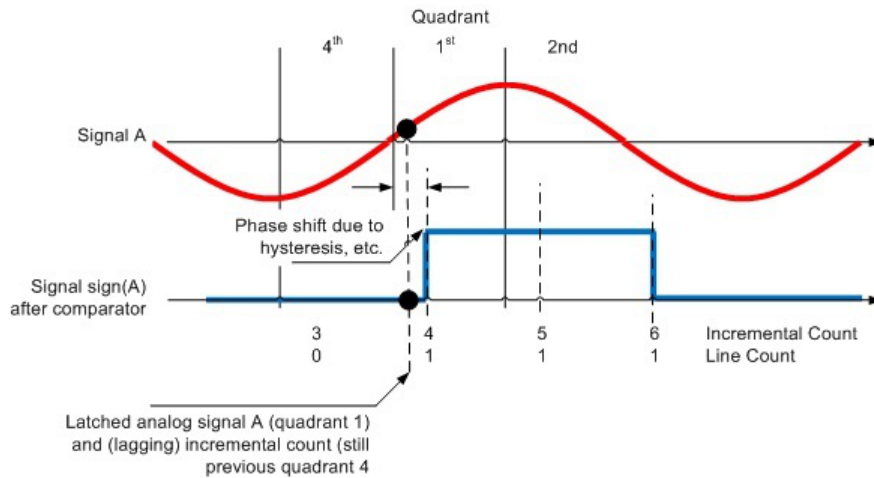


Figure 5. Phase Shift of a_{TTL} Versus Analog Signal a Due to Phase Lag

Due to the redundancy between the two least significant bits LSBs of incremental line count, which represent the four quadrants and analog phase, you can apply a correction method as outlined in Figure 6 as long as the phase shift (see the red and blue signals in Figure 5) remains less than $\pm 90^\circ$.

Since only the phase information is used to identify the quadrant, there are only two exceptions to consider, where the phase doesn't match to the incremental count. These exceptions occur during the transition from quadrant 4 to quadrant 1, or quadrant 1 to quadrant 4, depending on the rotation direction.

Incremental count (<i>incr</i>)	Phase $\phi_{A,B}$	Correction method
$incr \% 4 = 3$	$0 \leq \text{phase} < 90$	$incr = incr + 1$ if $incr > 4 * N - 1$ then $incr = 0$
$incr \% 4 = 0$	$270 \leq \text{phase} < 360$	$incr = incr - 1$ if $incr < 0$ then $incr = 4 * N - 1$

Figure 6. Correction Method

Equation Figure 7 calculates the total high-resolution angle position, F_{TOTAL} :

$$\Phi_{TOTAL} [\text{deg}] = \frac{360^\circ}{N} \cdot \left((incr \gg 2) + \left(\frac{\phi_{A,B}}{360^\circ} \right) \right) + \Phi_0, \quad (2)$$

Figure 7.

where N is the sin/cos encoder's line count (number of signal periods per revolution), *incr* is the actual incremental count, and $\phi_{A,B}$ is the actual phase of the signals A and B calculated using the inverse-tangent method.

The ideal interpolated-angle resolution is a function of the sin/cos encoder's line count, N, and the resolution of the dual ADC. Equation Figure 8 calculates the equivalent interpolated-angle resolution as:

$$\Phi_{RESOLUTION} [\text{bit}] = \log_2(2 \cdot N) + ADC_{RESOLUTION} [\text{bit}] \quad (3)$$

Figure 8.

For a sin/cos encoder with 1,024 line counts, the resolution is 22 bits when using a dual 12-bit dual ADC and 26 bits when using a 16-bit dual ADC. Such high resolution is often not required for position control but for precise speed control, especially at lower mechanical speeds.

A key analog component with an interface to sin/cos position encoders is the dual ADC. It might be external or embedded into the host processor.

Figure 9 shows the system block diagram of the [TI Designs Interface to Sin/Cos Encoders with High-Resolution Position Interpolation reference design](#) (TIDA-00176). The major building blocks are:

- An analog signal chain with two options for flexibility:
 - A 16-bit high-resolution fully differential path with SPI interface to a microcontroller (MCU).
 - A analog path with a single-ended analog output for MCU-embedded ADCs.
 - A high-speed comparator block.
 - Power management.
 - Example firmware on C2000™ Piccolo™ MCUs for digital signal processing, as indicated in the blue box in Figure 2.

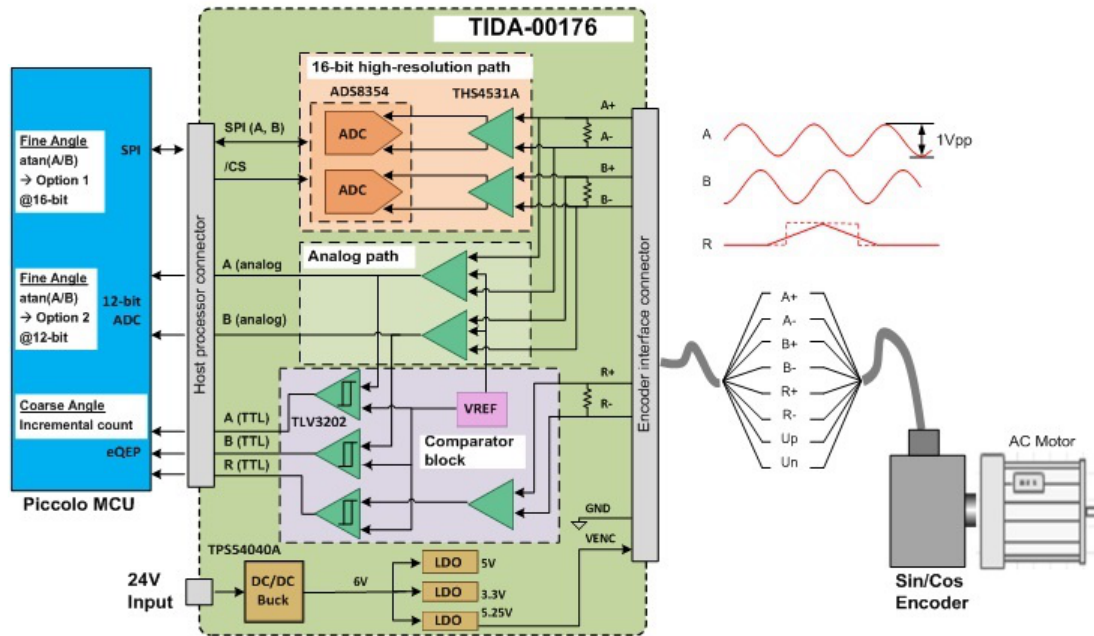


Figure 9. System Block Diagram of TIDA-00176 with Piccolo F28069M MCU LaunchPad™ Development Kit

The first building block is the dual-analog signal path with 120-Ω termination and EMC protection to connect the sin/cos encoder's differential signals: A+, A-, B+, B-, R+ and R-.

The high-performance, fully differential signal path with high common-mode noise rejection leverages the [THS4531](#) fully differential amplifier and the [ADS8354](#) 16-bit dual successive-approximation register (SAR) ADC with SPI interface to the host processor.

The single-ended analog signal path uses the [OPA2365](#) which converts the differential analog inputs into single-ended analog signals A and B from 0 to 3.3V to drive an embedded dual sample and hold (S/H) ADC, like an embedded C2000 Piccolo MCU.

The second building block is the comparator block, which converts the analog signals A, B and R into digital signals with a 3.3V TTL I/O to interface to a quadrature-encoder pulse module like the enhanced quadrature encoder pulse (eQEP) module on the Piccolo MCU. The [TLV3202](#) high-speed, low-propagation delay comparators are configured with hysteresis for better noise immunity.

The third building block is the wide-input-range 24V power supply, leveraging the [TPS54040A](#) high-efficiency DC/DC converter for an intermediate 6V rail and LDOs for point of load. The LDOs provide the necessary voltages for the signal chain as well as the 5.25V supply voltage for the sin/cos encoder.

The schematics and layout have been designed and tested for EMC immunity according to IEC618000-3, which specifies EMC immunity requirements for adjustable-speed electrical power-drive systems.

IEC61800-3 requirements for second environment				TIDA-00176 measurements		
EMC test	Basic standard	Level	Performance (acceptance) criterion	Level	Performance (achieved) criterion	Result
ESD	IEC61000-4-2	±4kV contact discharge (CD)	B	+/-8kV CD	B	Pass (exceed)
Fast transient burst (EFT)	IEC61000-4-4	±2kV/5kHz	B	+/-4kV	B	Pass (exceed)
Surge	IEC61000-4-5	±1kV/2Ω (for shielded cable)	B	+/-1kV	B	Pass

Figure 10. IEC618000-3 EMC Immunity Requirements and TIDA-00176 Test Results

If you're ready to start designing, check out the TI Design [Interface to Sin/Cos Encoders with High-Resolution Position Interpolation reference design](#), which outputs the measured angle from the sin/cos encoder with up to 28-bit resolution through a USB virtual communications port and includes example firmware for the Piccolo MCU. For an example with the Sitara AM437x processor including firmware check out the TI Design [Interface to a Sin/Cos Encoder with Sitara™ AM437x Reference Design](#) folder. A reference solution leveraging the C2000 DesignDRIVE Position Manager technology for on-chip interfacing to SIN/COS encoders is also included as part of the TI Design [TIDM-SERVODRIVE](#).

In the next and final installment of this series, my colleagues and I will take a closer look at a universal multi-standard digital interface to absolute-position feedback encoders.

If you would like to see this series touch on specific topics related to position-encoder interface design, please post a comment below.

Additional Resources

- View these TI Designs reference designs:
 - [Dual Channel Data Acquisition System for Optical Encoders, 12 Bit, 1MSPS \(TIPD117\)](#).
 - [Comparator with Hysteresis Reference Design \(TIPD144\)](#).
 - [Industrial Servo and AC Inverter Drive reference design \(TIDM-SERVODRIVE\)](#).
 - [Universal Digital Interface to Absolute Position Encoders reference design \(TIDA-00179\)](#).
- Order the [C2000 DesignDRIVE development kit for industrial motor control](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated