Test Report: PMP41145

Universal AC Input 65W 20V, 3.25A Flyback With Integrated GaN Reference Design



Description

This reference design is a 65W, 20V fixed output voltage AC-DC power supply design with integrated flyback and Gallium nitride (GaN). This design can deliver 65W full rated power across 90VAC to 264VAC and achieve 93% efficiency at 90VAC. The design can meet efficiency standards and regulations such as DoE Level VII and CoC V5 Tier 2 efficiency standard for average efficiency across 25%, 50%, 75%, 100% and standby power consumption. The design can achieve 2.3W per cubic centimeters and eliminate auxiliary winding as well as associated VCC rectifier circuity. The design can also support a 100W peak power capability for 4ms.



Top view



Bottom View

Features


- Achieve 93% efficiency at 90VAC
- 2.3W per cubic centimeter. Power density based on PCB size
- Meet DoE Level VII and CoC V5 Tier 2 efficiency standards
- No load power consumption 18mW at 115VAC, 28mW at 230VAC
- Provide 100W peak power capability

Applications

- Industrial AC-DC
- USB AC/DC adapter
- USB wall power outlet
- Battery charger



Angle view

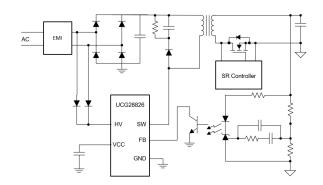

Block Diagram



1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
Input voltage range	90VAC to 264VAC
Output voltage	20VDC
Output current	3.25A
Rated Power	65W
Peak Power	100W, 4ms

1.2 Required Equipment

AC Source: Chroma Model 61601

Digital Power Meter: Yokogawa WT310

Power-Z P240 Bidirectional Multi-protocol Power Supply

DC source: GWinstek, GPS-3303C

• Bidirectional Power Source: IT6010C-80-300

Electronic load: Chroma, 6314A
Oscilloscope: Tektronix, DPO 3054
Infrared Thermal Camera: Fluke, TiS55
Ture-RMS-Multimeter: Fluke, 287C

1.3 Dimensions

PCB board size: 27mm × 48mm × 22mm (open frame)

2 Testing and Results

2.1 Efficiency Graphs

Efficiency is shown in Figure 2-1 through Figure 2-3.

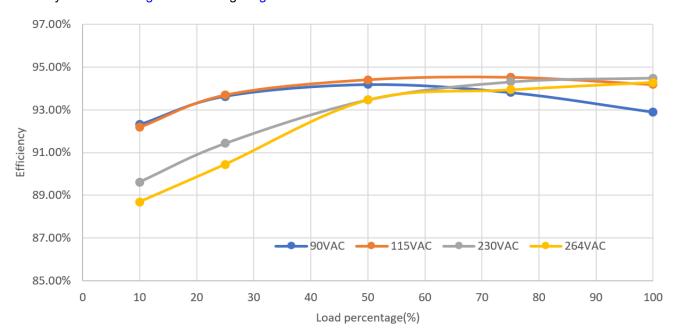


Figure 2-1. Efficiency Versus AC Input and Load

www.ti.com Testing and Results

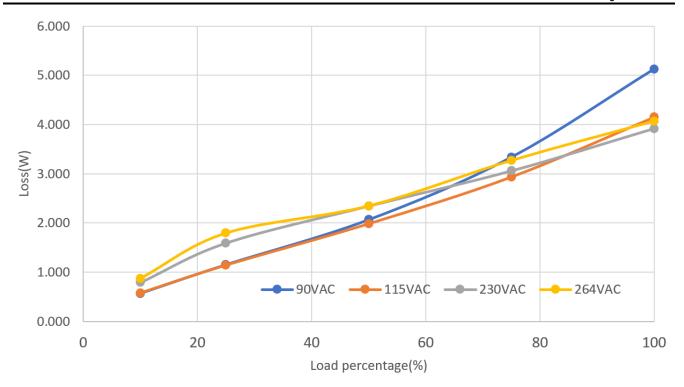


Figure 2-2. Power Loss Versus AC Input and Load

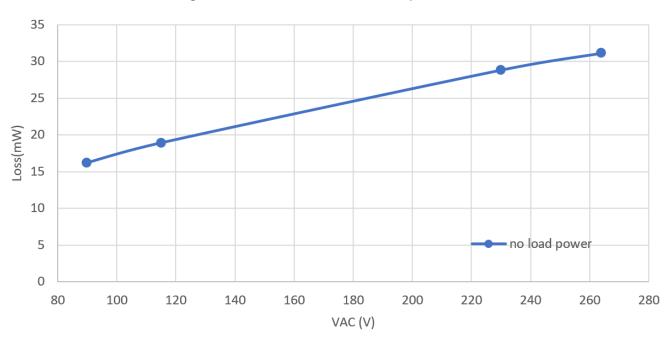


Figure 2-3. No Load Input Power Consumption Versus AC Input Voltage



2.2 Voltage Regulation

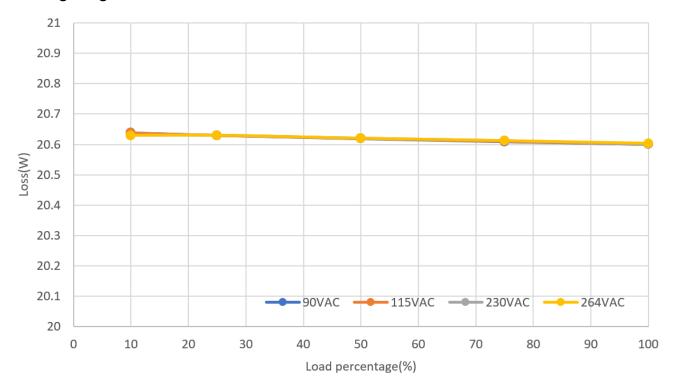


Figure 2-4. Vout Voltage Regulation Versus AC Input and Load

2.3 Efficiency Data

Efficiency data is shown in Table 2-1.

Table 2-1. Efficiency Data

VAC _{IN} (V)	P _{IN} (A)	V _{OUT} (V)	I _{ОИТ} (А)	P _{OUT} (W)	P _{LOSS} (W)	P _{OUT} (%)	Efficiency (%)	Average Efficiency at Four Point (%)
90	72.18	20.61	3.255	67.053	5.127	100	92.9	93.63
90	53.91	20.609	2.454	50.574	3.336	75	93.81	
90	35.53	20.619	1.623	33.465	2.065	50	94.19	
90	18.11	20.63	0.822	16.958	1.152	25	93.64	
90	7.4	20.638	0.331	6.831	0.569	10	92.31	
115	71.2	20.61	3.255	67.053	4.147	100	94.81	94.20
115	53.51	20.61	2.454	50.577	2.933	75	94.52	
115	35.45	20.62	1.623	33.466	1.984	50	94.40	
115	18.1	20.63	0.822	16.958	1.142	25	93.69	
115	7.41	20.638	0.331	6.831	0.579	10	92.19	
230	70.97	20.61	3.255	67.053	3.917	100	94.48	93.41
230	53.64	20.612	2.454	50.582	3.058	75	94.3	
230	35.81	20.62	1.623	33.466	2.344	50	93.46	
230	18.55	20.63	0.822	16.958	1.592	25	91.42	
230	7.62	20.63	0.331	6.829	0.791	10	89.61	



www.ti.com Testing and Results

Table 2-1. Efficiency Data (continued)

VAC _{IN} (V)	P _{IN} (A)	V _{OUT} (V)	l _{оит} (A)	P _{OUT} (W)	P _{LOSS} (W)	Роит (%)	Efficiency (%)	Average Efficiency at Four Point (%)
264	71.13	20.603	3.255	67.063	4.067	100	94.28	93.03
264	53.85	20.612	2.454	50.582	3.268	75	93.93	
264	35.81	20.62	1.623	33.466	2.344	50	93.46	
264	18.75	20.63	0.822	16.958	1.792	25	90.44	
264	7.7	20.63	0.331	6.829	0.871	10	88.68	

Testing and Results Www.ti.com

2.4 Thermal Images

Thermal image is shown in Figure 2-5 through Figure 2-8.

Table 2-2. Thermal Test Result

10.000 = = 10.00000000000000000000000000						
Parts	90VAC	115VAC	230VAC	264VAC		
	Temperature(°C)	Temperature(°C)	Temperature(°C)	Temperature(°C)	Room temperature(°C)	
AC Bridge	105	90	75	73	25	
UCG28826	84	76	79	83	25	
Transformer	75	75	76	77	25	
SR MOSFET	68	66	67	66	25	
RCD Snubber	91	83	80	79	25	



Figure 2-5. Thermal, 90VAC, Full Load



Figure 2-6. Thermal, 115VAC, Full Load





Figure 2-7. Thermal, 230VAC, Full Load

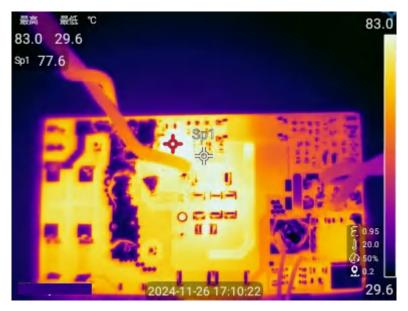


Figure 2-8. Thermal, 264VAC, Full Load



2.5 EMI

EMI is shown in Figure 2-9 through Figure 2-12.

EMI TEST REPORT

Start(MHz) End(MHz) Step(MHz) 1.150 2.000 0.002 1.000 10.000 0.010 0.000 30.000 0.025 IBuV OO EN55032 (QP) IO EN55032 (AV)
00 0 0 0 0 0 0 EN55032 (QP) 60 EN55032 (AV)

Figure 2-9. 115VAC, Full Load, Resistive Load, Unearthed, L phase

8



EMI TEST REPORT

Organiza Place: Detector: Limit: Remark:	tion: PK+AV EN55022	В	Operator: Time: Test-time(m Transducto	2024/12/4/14:23 is): 30 r(PK/AV): PK / AV	Parame EUT: Test equipment:KH3932 SN: 320684 JZ: 2,15,1039
Start(MHz 0.150 2.000 10.000	· 2]		End(MHz) 2.000 10.000 30.000		Step(MHz) 0.002 0.010 0.025
lBuV					scan re
100					
10					
0					
0	-M				
0 *	n / 1 Th	, , ,			EN55022B(QP)
0	M. X	1			EN55022B(AV)
10	/*\	α $\Lambda \Lambda$	who have have	WILL ALM AIMM M	
	M / W	Δ		ASS.	Miller
20 ³	` W \	N, MM	May Lamber	who were	man Jumper
,"		1 1 1	iii i		
,		0.50	1.00	5.00	10.00
.150 MH	lz				30.000 MHz
QP)	freq(MHz)		le∨(dBuV)	Lim(dBuV)	final tes ∆(lev-Lim)
	0.150		60.0	66.0	-6.0
	0.390		46.0	59.1	-13.1


Figure 2-10. 115VAC, Full Load, Resistive Load, Unearthed, N phase



EMI TEST REPORT

-- parameter EUT: Organization: Operator: Test equipment: KH3932 Place: Time: 2024/12/4/14:13 SN: 320684 Detector: PK+AV Test-time(ms): 30 Limit: EN55022B Transductor(PK/AV): PK / AV JZ: 2,15,1044 Remark: ----- freq, step Start(MHz) End(MHz) Step(MHz) 0.150 2.000 0.002 2.000 10.000 0.010 10.000 30.000 0.025 -- scan result dBuV 100 90 80 70 60 EN55022B (QP) 50 EN55022B (AV) 40 30 20 10 0 0.50 1.00 5.00 10.00 0.150 MHz 30.000 MHz ---- final test lev(dBuV) Lim(dBuV) (QP) freq(MHz) ∆(lev-Lim) 50.7 66.0 0.150 -15.3

Figure 2-11. 230VAC, Full Load, Resistive Load, Unearthed, L phase

 



EMI TEST REPORT

Organization: Operator: EUT: Place: Time: Test equipment:KH3932 2024/12/4/14:18 320684 Detector: SN: PK+AV Test-time(ms): 30 Limit: EN55022B Transductor(PK/AV): PK / AV JZ: 2,15,1040 Remark: - freq, step Start(MHz) End(MHz) Step(MHz) 2.000 0.002 0.150 2.000 10.000 0.010 10.000 30.000 0.025 ----- scan result dBuV 100 90 80 70 60 EN55022B(QP) 50 EN55022B (AV) 40 30 20 10 0 0.50 1.00 5.00 10.00 0.150 MHz 30.000 MHz

Figure 2-12. 230VAC, Full Load, Resistive Load, Unearthed, N phase

Waveforms www.ti.com

3 Waveforms

3.1 Start-up and Shut Down Waveform

Start-up behavior is shown in Figure 3-1 through Figure 3-4.

CH1: VAC, CH2:VOUT, CH4: lout

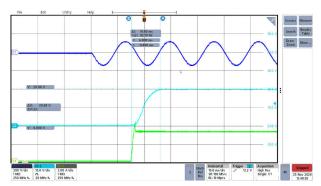


Figure 3-1. 90VAC, Soft Start-Up Time 6ms

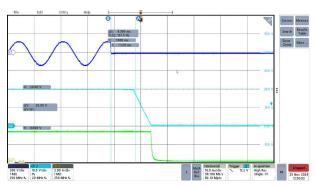


Figure 3-2. 90VAC, Shut Down, Hold Up Time 9.3ms

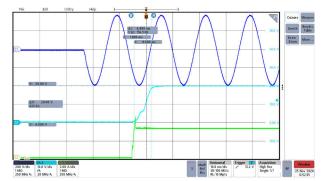


Figure 3-3. 264VAC, Soft Start-Up Time 6ms

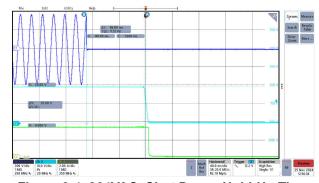


Figure 3-4. 264VAC, Shut Down, Hold-Up Time 87ms

3.2 Switching

Switching behavior is shown in Figure 3-5 through Figure 3-21.

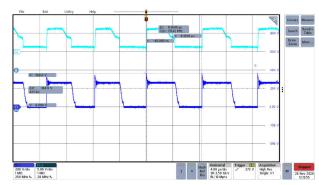


Figure 3-5. 115VAC, Vds_pri, Vsr_gate, Full Load


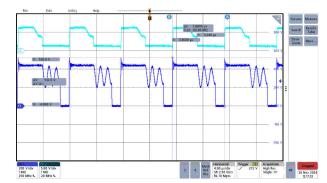


Figure 3-6. 230VAC, Vds_pri, Vsr_gate, Full Load

www.ti.com Waveforms

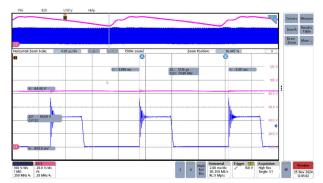


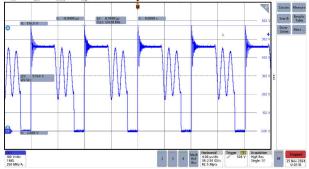


Figure 3-7. 90VAC, Full Load, Vds_pri, Vbus Valley 83V

Figure 3-8. 230VAC, Full Load, 3.25A, fsw = 125kHz

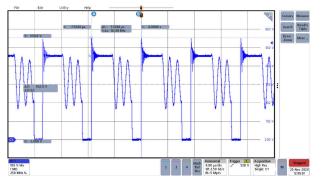


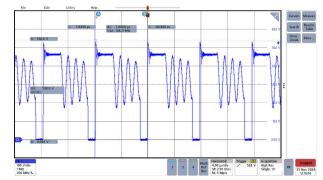


Figure 3-9. 230VAC, 75% Load, 2.45A, fsw = 133kHz Figure 3-10. 230VAC, 50% Load, 1.6A, fsw = 128kHz

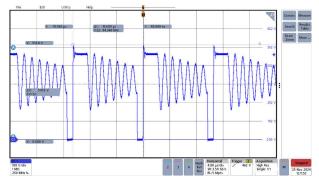


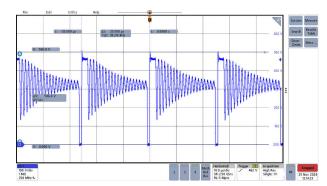


Figure 3-11. 230VAC, 25% Load 0.82A, fsw = 94kHz

Figure 3-12. 230VAC, 10% Load 0.32A, fsw=39kHz

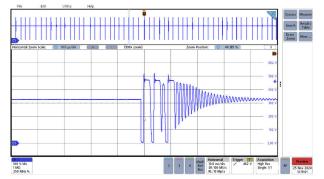

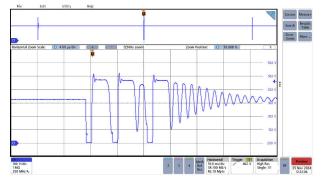


Figure 3-13. 230VAC, 20V, 200mW Load, Vds_pri

Figure 3-14. 230VAC, 20V, Open Load, Vds_pri

Waveforms INSTRUMENTS
www.ti.com

Figure 3-15 through Figure 3-21 are 115VAC input switching waveforms.

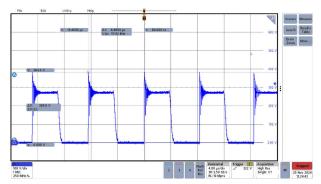


Figure 3-15. 115VAC, 20V, 3.25A Full Load, Vds_pri, fsw = 118kHz

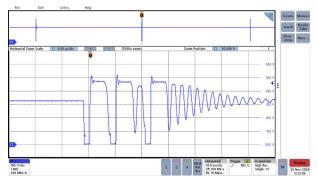


Figure 3-16. 115VAC, 20V, 2.45A 75% Load, Vds_pri, fsw = 127kHz

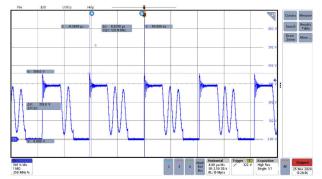


Figure 3-17. 115VAC, 20V, 1.8A 50% Load, Vds_pri, fsw = 120kHz

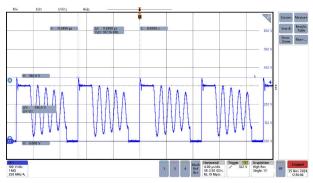


Figure 3-18. 115VAC, 20V, 0.82A 25% Load, Vds_pri, fsw = 107kHz

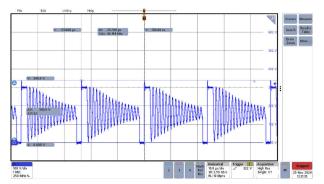


Figure 3-19. 115VAC, 20V, 0.32A 10% Load, Vds_pri, fsw = 42kHz

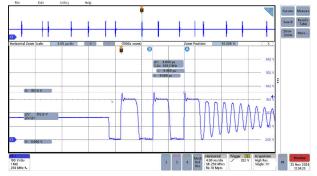


Figure 3-20. 115VAC, 20V, 200mW Load, Vds_pri

www.ti.com Waveforms


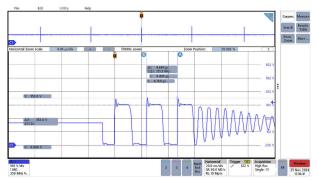


Figure 3-21. 115VAC, 20V, Open Load, Vds_pri, 3 Consecutive Switching Cycles to Achieve First Valley Switching


3.2.1 Voltage Stress

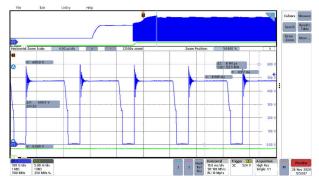

| Second | S

Figure 3-22. 264VAC, Full Load, Vds Peak = 600V

Figure 3-23. 90VAC, Full Load, Vds Peak = 360V

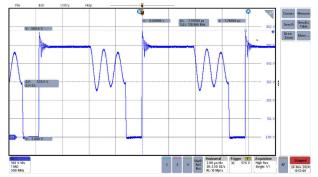

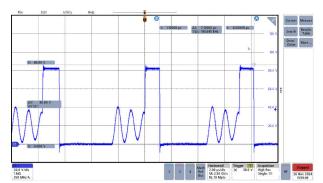



Figure 3-24. 264VAC, Full Load, Steady State Vds Primary 580V

Figure 3-25. 264VAC, Full Load, Vds on Synchronous Rectifier 86.8V

3.3 VCC Self Bias

VCC was regulated across AC input and load condition. Figure 3-26 through Figure 3-31 show VCC waveforms. CH1: Vds, CH2: VCC, CH3: HV Pin, CH4: I_{out}

Waveforms www.ti.com

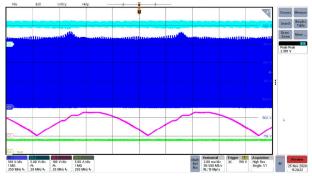

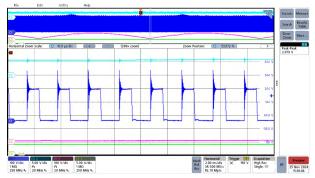


Figure 3-26. VCC Voltage, 90VAC, Full Load

Figure 3-27. VCC Voltage, 90VAC, Full Load, Zoom in at VBUS Valley

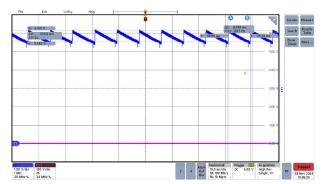


Figure 3-28. VCC Voltage, 115VAC, Open Load, VCC Charging at Around 120Hz Frequency

Figure 3-29 through Figure 3-31 shows VCC at 230VAC input.

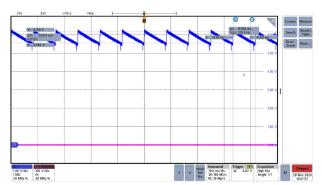


Figure 3-29. VCC Voltage, 230VAC, Open Load, VCC Charging at Around 120Hz Frequency

Figure 3-30. VCC Voltage, 230VAC, Full Load

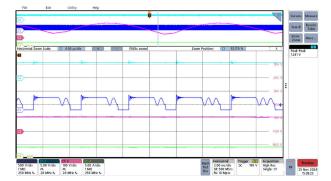


Figure 3-31. VCC Voltage, 230VAC, Full Load, Zoom-In

www.ti.com Waveforms

3.4 Output Voltage Ripple

Output voltage ripple is shown in Figure 3-32 through Figure 3-39.


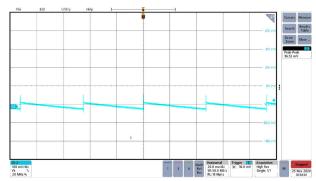


Figure 3-32. Output Voltage Ripple, 115VAC, Open Load

Figure 3-33. Output Voltage Ripple, 115VAC, 10% Load 0.33A

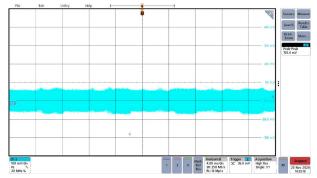


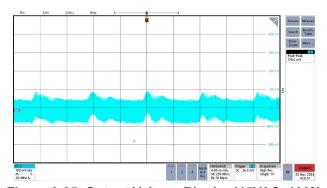


Figure 3-34. Output Voltage Ripple, 115VAC, 50% Load 1.62A

Figure 3-35. Output Voltage Ripple, 115VAC, 100% Load, 3.25A

Figure 3-36 through Figure 3-39 are tested at 230VAC.

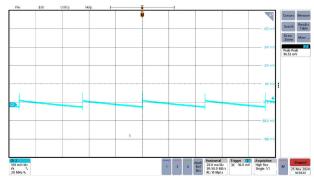

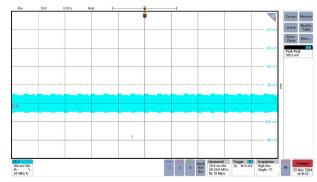


Figure 3-36. Output Voltage Ripple, 230VAC, Open Load

Figure 3-37. Output Voltage Ripple, 230VAC, 10% Load 0.33A

Waveforms www.ti.com

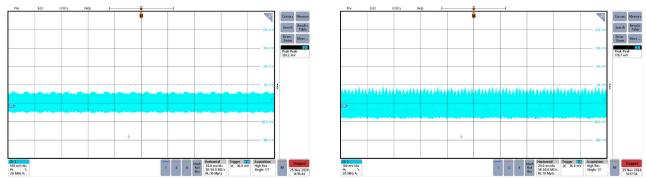


Figure 3-38. Output Voltage Ripple, 230VAC, 50% Load 1.6A

Figure 3-39. Output Voltage Ripple, 230VAC, 100% Load 3.25A

3.5 Load Dynamic Response

The load dynamic test was performed from 0.1A to full load, 3.25A. Output voltage was measured at the PCB end.

CH2: Vout, CH4: Iout

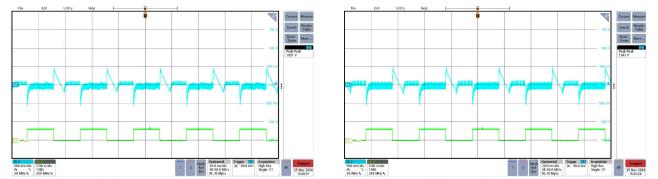



Figure 3-40. Load Transient, 115VAC, 0.1A to 3.25A Figure 3-41. Load Transient, 230VAC, 0.1A to 3.25A Full Load Full Load

Waveforms

3.6 Peak Power

Peak power test was performed by setting the peak power to 1.5 times rated power (100W) for 4ms followed by 36ms 0.9 times rated power (58W).

CH1: Vds_pri, CH2: Vout, C4:Iout

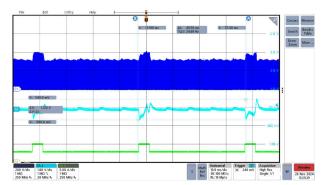

4ms, 58W 36ms, Vout Drop 0.58V

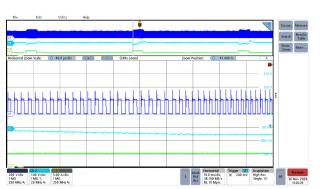


Figure 3-42. Peak Power, 90VAC, 100W Peak Power Figure 3-43. Peak Power, 90VAC, 100W Peak Power 4ms, 58W 36ms, Zoom In, fsw Increase to Provide **Peak Power**

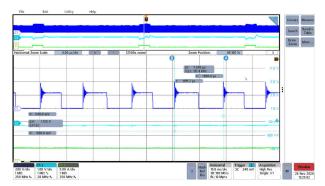


Figure 3-44. Peak Power, 90VAC, 100W Peak Power 4ms, 58W 36ms, Zoom In, CCM Mode to Provide Peak Power With fsw Increased to 137KHz

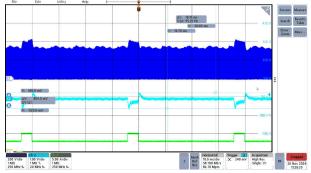


Figure 3-45. Peak Power, 115VAC, 100W Peak Power 4ms, 58W 36ms, Vout Drop 520mV

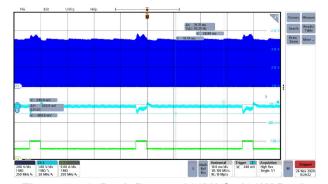


Figure 3-46. Peak Power, 230VAC, 100W Peak Power 4ms, 58W 36ms, Vout Drop 380mV

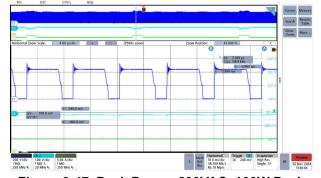


Figure 3-47. Peak Power, 230VAC, 100W Peak Power 4ms, 58W 36ms, Vout Drop 380mV, Zoom In

Waveforms www.ti.com

3.7 Short-Circuit Protection

Short-circuit protection was performed at PCB board end. Auto recovery after short was removed.

CH1: Vds primary, CH2:VCC, CH3: Vout, CH4: Iout

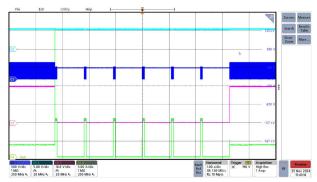


Figure 3-48. Short Circuit at PCB End and Recovery When Short Circuit Removed, 264VAC

3.8 Output Over Voltage Protection

By disconnecting output feedback, Vout ramps up and UCG28826 SW pin senses the output voltage. Once the sensed voltage triggers the OVP threshold, the OVP protection is triggered.

CH2: Vout, CH4: Vds primary switching

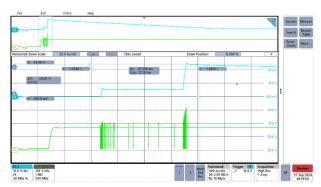


Figure 3-49. 264VAC, OVP, Open Load

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2024, Texas Instruments Incorporated