

**Test Data
For PMP9492
12/21/2014**



Contents


1. Design Specifications	3
2. Circuit Description and PCB details	3
3. PMP9492 Board Photos	4
4. Thermal Data	5
5. Efficiency	6
5.1 Efficiency Chart – Input Voltage Vs Efficiency with all output fully Loaded	6
5.2 Efficiency Chart – 3.3Vout Efficiency Vs Load Current	6
5.3 Efficiency Chart – 2.5V Vout2 and 1.8V Vout3 Efficiency	7
5.3 Efficiency Data	7
6. Waveforms	10
6.1 Load Transient Response	10
6.2 Startup	15
6.3 Output Voltage Ripple and Switch Node Voltage	21
7. Conducted Emissions	25

1. Design Specifications


Vin Minimum	4.5VDC
Vin Maximum	20VDC
Vout1	3.3VDC
Iout 1	1.0A
Vout2	2.5VDC
Iout 2	1.0A
Vout3	1.8VDC
Iout 3	1.0A
Vout4	5
Iout 4	0.1A
Approximate Switching Frequency	2.1MHz for Vout1,2&3 and 1.5MHz for Vout4

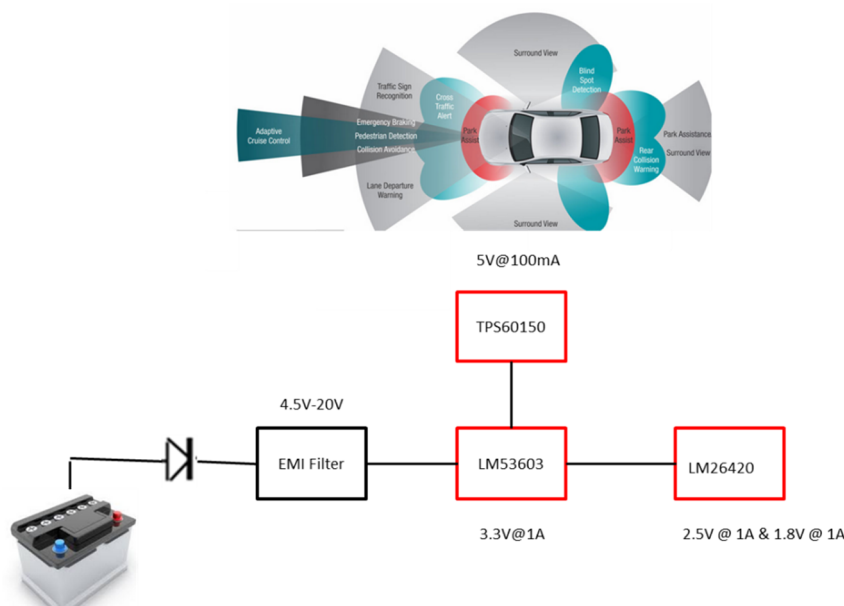2. Circuit Description and PCB details


PMP9492 is a conducted EMI optimized (CISPR 25 Class 5) 9 W Multi output Design for Wide Range Vin automotive ADAS application that supports Cold –Cranking Conditions . The design uses LM53603 regulator IC (Used as Buck), LM26420 (used as dual Buck) and TPS60150 regulator IC (used as Charge pump for 5V output). The design accepts an input voltage of 4.5Vin to 20Vin and provides the outputs of 3.3V@1.0A, 2.5V @ 1.0A , 1.8V @ 1.0A and 5V@ 100mA . It features a small size and is an inexpensive and more efficient solution customized for ADAS and other Automotive related applications. The Board dimension of PMP9492 PCB is 2600mil * 4000mil. Four layer PCB was used for the design.



3. PMP9492 Board Photos

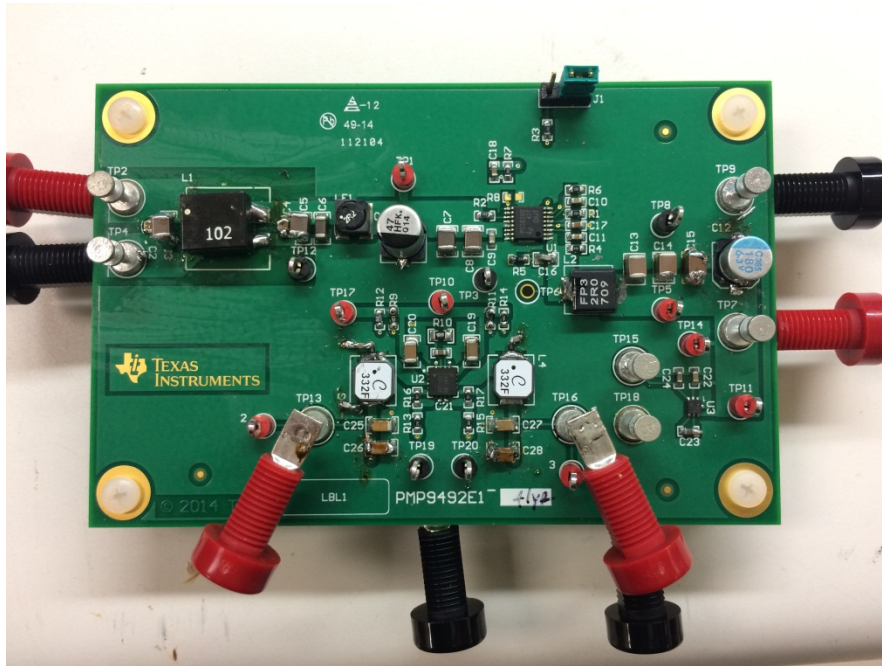


Board Photo (Top)

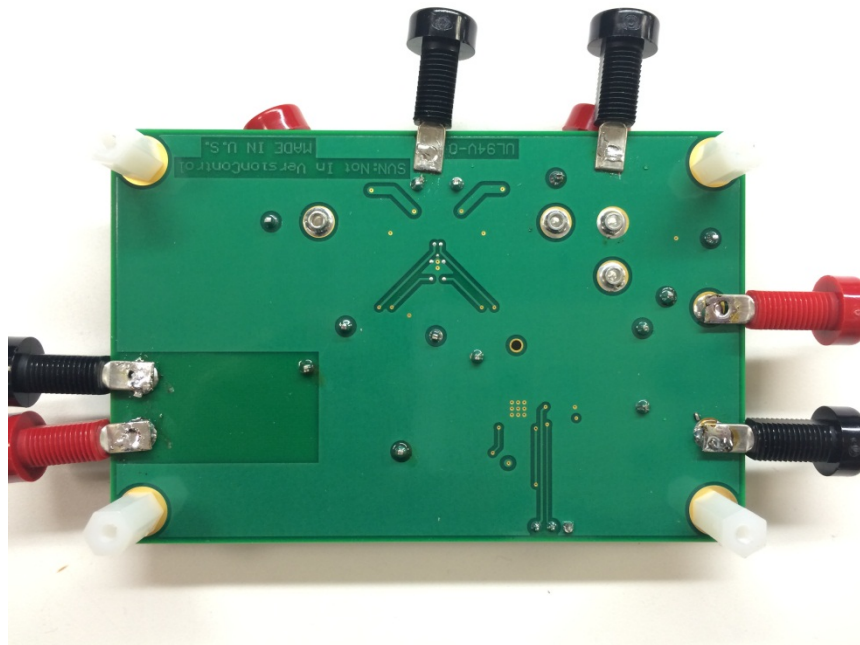

Board Photo (Bottom)

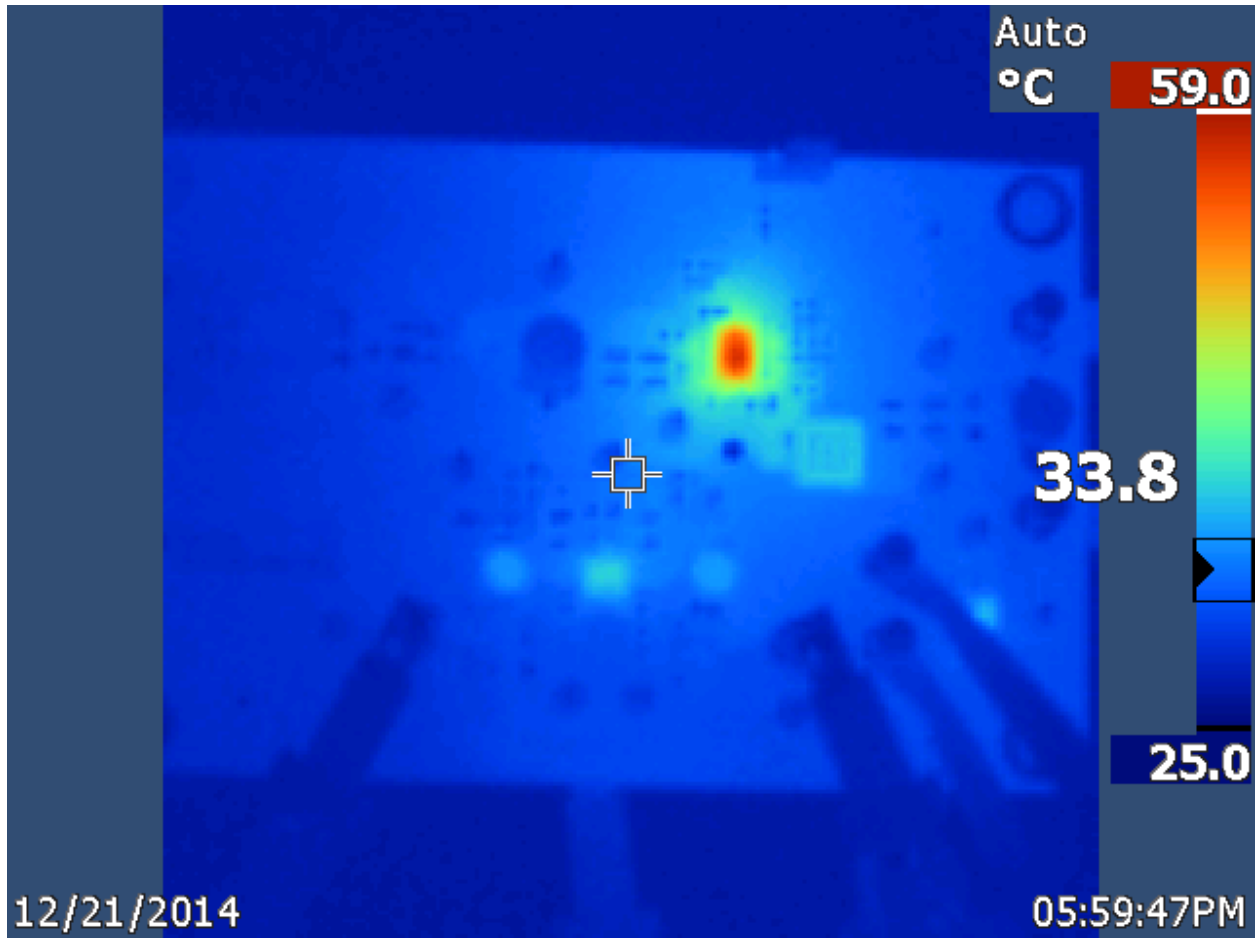
4. Thermal Data

IR thermal image taken at steady state with 12Vin and all the outputs at full load (no airflow)




5. Efficiency

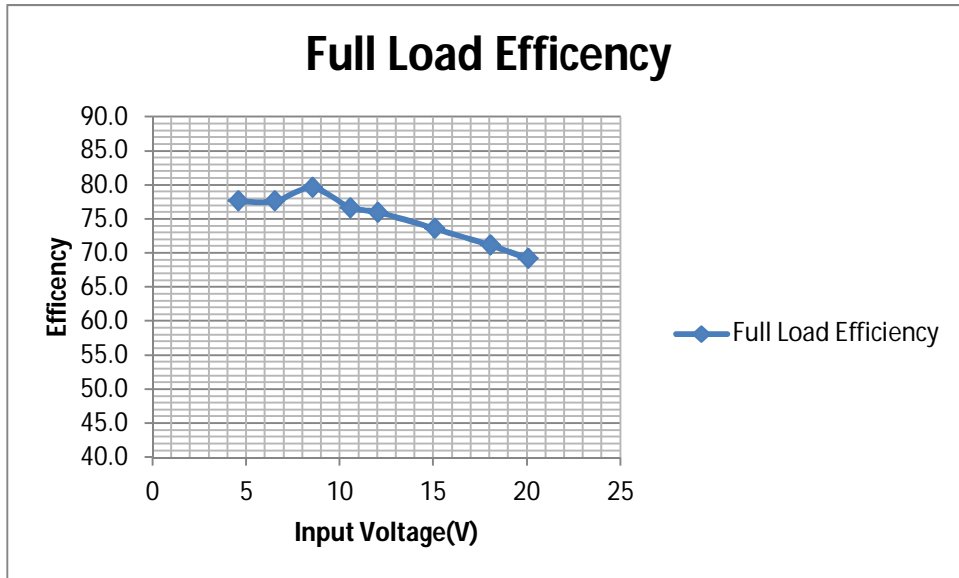
5.1 Efficiency Chart – Input Voltage Vs Efficiency with all output fully Loaded



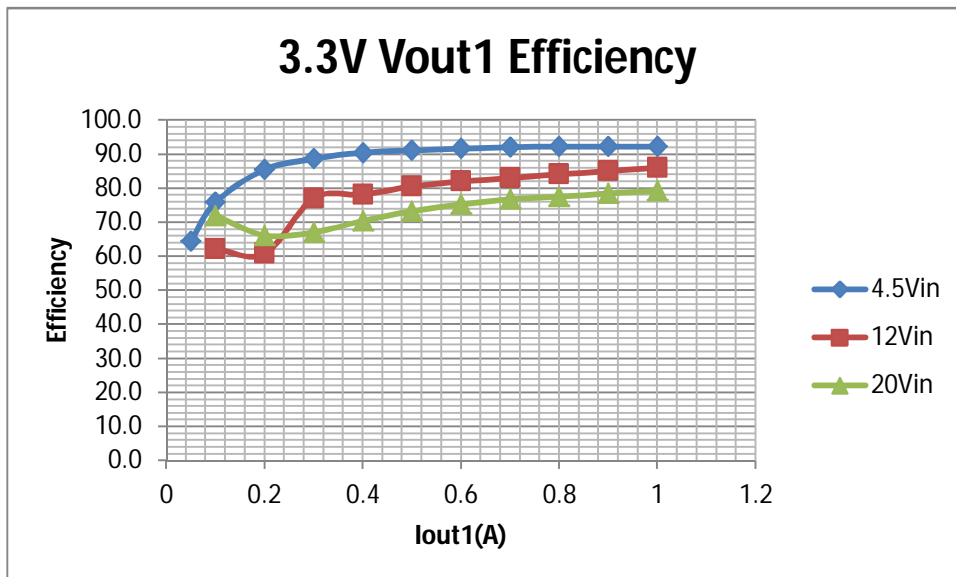5.2 Efficiency Chart – 3.3Vout Efficiency Vs Load Current



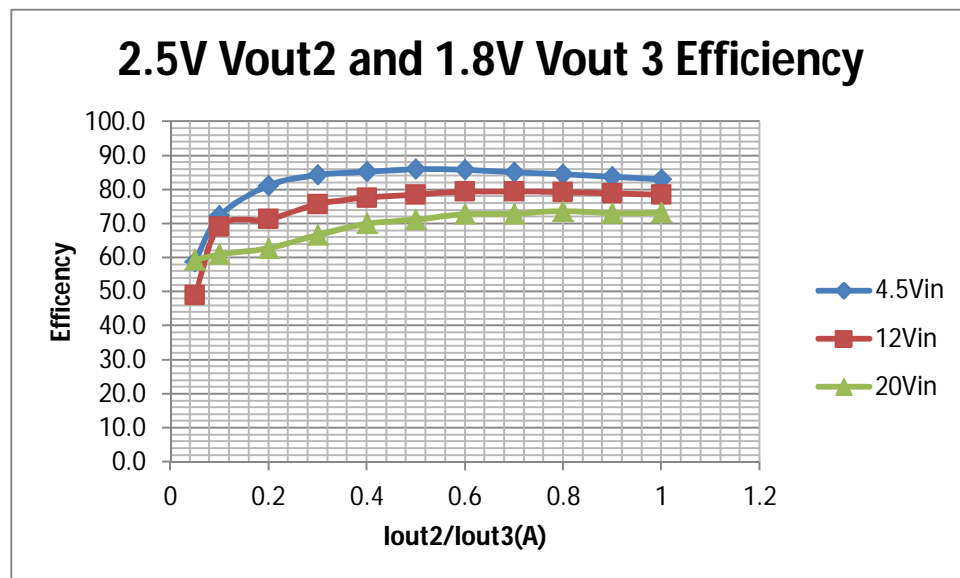5.3 Efficiency Chart – 2.5V Vout2 and 1.8V Vout3 Efficiency



5.3 Efficiency Data

Efficiency of total System Vs Input Voltage

Vin (V)	Iin (A)	Vout 1(V)	Iout 1(A)	Vout 2(V)	Iout 2(A)	Vout 3(V)	Iout 3(A)	Vout 4(V)	Iout 4(A)	Pin (W)	Pout (W)	Efficiency (%)
4.566	2.28	3.31	1	2.47	1	1.8	1	5.02	0.1	10.41048	8.082	77.6
6.507	1.6	3.31	1	2.47	1	1.8	1	5.02	0.1	10.4112	8.082	77.6
8.53	1.19	3.31	1	2.47	1	1.8	1	5.02	0.1	10.1507	8.082	79.6
10.54	1	3.31	1	2.47	1	1.8	1	5.02	0.1	10.54	8.082	76.7
12.04	0.883	3.31	1	2.47	1	1.8	1	5.02	0.1	10.63132	8.082	76.0
15.058	0.729	3.31	1	2.47	1	1.8	1	5.02	0.1	10.97728	8.082	73.6
18.06	0.629	3.31	1	2.47	1	1.8	1	5.02	0.1	11.35974	8.082	71.1
20.06	0.582	3.31	1	2.47	1	1.8	1	5.02	0.1	11.67492	8.082	69.2

Efficiency of 3.3V Vs Load Current


Vin (V)	Iin (A)	Vout 1(V)	Iout 1(A)	Pin (W)	Pout (W)	Efficiency (%)
4.5	0.798	3.31	1	3.591	3.31	92.2
4.51	0.716	3.31	0.9	3.22916	2.979	92.3
4.52	0.635	3.31	0.8	2.8702	2.648	92.3
4.53	0.555	3.31	0.7	2.51415	2.317	92.2
4.55	0.476	3.31	0.6	2.1658	1.986	91.7
4.55	0.399	3.31	0.5	1.81545	1.655	91.2
4.56	0.321	3.31	0.4	1.46376	1.324	90.5
4.57	0.245	3.31	0.3	1.11965	0.993	88.7
4.58	0.169	3.31	0.2	0.77402	0.662	85.5
4.59	0.095	3.31	0.1	0.43605	0.331	75.9
4.59	0.056	3.31	0.05	0.25704	0.1655	64.4
Vin (V)	Iin (A)	Vout 1(V)	Iout 1(A)	Pin (W)	Pout (W)	Efficiency (%)
12.1	0.022	3.31	0.05	0.2662	0.1655	62.2
12.1	0.045	3.31	0.1	0.5445	0.331	60.8
12.09	0.071	3.31	0.2	0.85839	0.662	77.1
12.09	0.105	3.31	0.3	1.26945	0.993	78.2
12.09	0.136	3.31	0.4	1.64424	1.324	80.5
12.08	0.167	3.31	0.5	2.01736	1.655	82.0
12.08	0.198	3.31	0.6	2.39184	1.986	83.0
12.07	0.228	3.31	0.7	2.75196	2.317	84.2
12.07	0.258	3.31	0.8	3.11406	2.648	85.0
12.07	0.287	3.31	0.9	3.46409	2.979	86.0
12.06	0.318	3.31	1	3.83508	3.31	86.3
Vin (V)	Iin (A)	Vout 1(V)	Iout 1(A)	Pin (W)	Pout (W)	Efficiency (%)
19.97	0.209	3.31	1	4.17373	3.31	79.3
19.98	0.19	3.31	0.9	3.7962	2.979	78.5
19.98	0.171	3.31	0.8	3.41658	2.648	77.5
19.98	0.151	3.31	0.7	3.01698	2.317	76.8
19.98	0.132	3.31	0.6	2.63736	1.986	75.3
19.98	0.113	3.31	0.5	2.25774	1.655	73.3
19.99	0.094	3.31	0.4	1.87906	1.324	70.5
19.99	0.074	3.31	0.3	1.47926	0.993	67.1
20	0.05	3.31	0.2	1	0.662	66.2
20	0.023	3.31	0.1	0.46	0.331	72.0
20	0.012	3.31	0.05	0.24	0.1655	69.0

Efficiency Data of 2.5V and 1.8 V

Vin (V)	Iin (A)	Vout 2(V)	Iout 2(A)	Vout 3(V)	Iout 3(A)	Pin (W)	Pout (W)	Efficiency (%)
19.96	0.292	2.47	1	1.8	1	5.82832	4.27	73.3
19.97	0.263	2.47	0.9	1.8	0.9	5.25211	3.843	73.2
19.97	0.232	2.47	0.8	1.8	0.8	4.63304	3.416	73.7
19.98	0.205	2.47	0.7	1.8	0.7	4.0959	2.989	73.0
19.98	0.176	2.47	0.6	1.8	0.6	3.51648	2.562	72.9
19.99	0.15	2.47	0.5	1.8	0.5	2.9985	2.135	71.2
19.99	0.122	2.47	0.4	1.8	0.4	2.43878	1.708	70.0
19.99	0.096	2.47	0.3	1.8	0.3	1.91904	1.281	66.8
19.99	0.068	2.47	0.2	1.8	0.2	1.35932	0.854	62.8
20	0.035	2.47	0.1	1.8	0.1	0.7	0.427	61.0
20	0.018	2.47	0.05	1.8	0.05	0.36	0.2135	59.3
Vin (V)	Iin (A)	Vout 2(V)	Iout 2(A)	Vout 3(V)	Iout 3(A)	Pin (W)	Pout (W)	Efficiency (%)
12.1	0.036	2.47	0.05	1.8	0.05	0.4356	0.2135	49.0
12.1	0.051	2.47	0.1	1.8	0.1	0.6171	0.427	69.2
12.09	0.099	2.47	0.2	1.8	0.2	1.19691	0.854	71.4
12.085	0.14	2.47	0.3	1.8	0.3	1.6919	1.281	75.7
12.08	0.182	2.47	0.4	1.8	0.4	2.19856	1.708	77.7
12.07	0.225	2.47	0.5	1.8	0.5	2.71575	2.135	78.6
12.07	0.267	2.47	0.6	1.8	0.6	3.22269	2.562	79.5
12.064	0.312	2.47	0.7	1.8	0.7	3.763968	2.989	79.4
12.057	0.357	2.47	0.8	1.8	0.8	4.304349	3.416	79.4
12.05	0.404	2.47	0.9	1.8	0.9	4.8682	3.843	78.9
12.04	0.452	2.47	1	1.8	1	5.44208	4.27	78.5
Vin (V)	Iin (A)	Vout 2(V)	Iout 2(A)	Vout 3(V)	Iout 3(A)	Pin (W)	Pout (W)	Efficiency (%)
4.45	1.155	2.47	1	1.8	1	5.13975	4.27	83.1
4.47	1.026	2.47	0.9	1.8	0.9	4.58622	3.843	83.8
4.49	0.9	2.47	0.8	1.8	0.8	4.041	3.416	84.5
4.5	0.78	2.47	0.7	1.8	0.7	3.51	2.989	85.2
4.51	0.662	2.47	0.6	1.8	0.6	2.98562	2.562	85.8
4.53	0.548	2.47	0.5	1.8	0.5	2.48244	2.135	86.0
4.55	0.44	2.47	0.4	1.8	0.4	2.002	1.708	85.3
4.56	0.333	2.47	0.3	1.8	0.3	1.51848	1.281	84.4
4.57	0.23	2.47	0.2	1.8	0.2	1.0511	0.854	81.2
4.58	0.129	2.47	0.1	1.8	0.1	0.59082	0.427	72.3
4.59	0.079	2.47	0.05	1.8	0.05	0.36261	0.2135	58.9

6. Waveforms


6.1 Load Transient Response

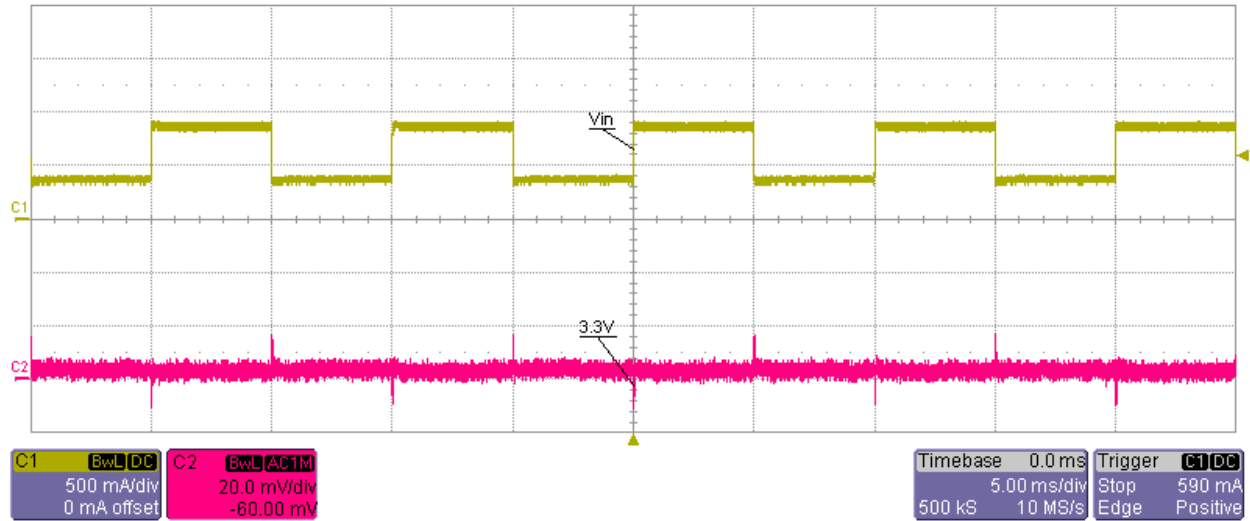

Load Transient Response at 4.5V_{in} and 50%-to-100% Load Step(0.5A-1A) on 3.3V Output Vout1(Full Load were connected to all other outputs)

Ch2 – Vout1 (AC coupled)


Ch1- Iout 1

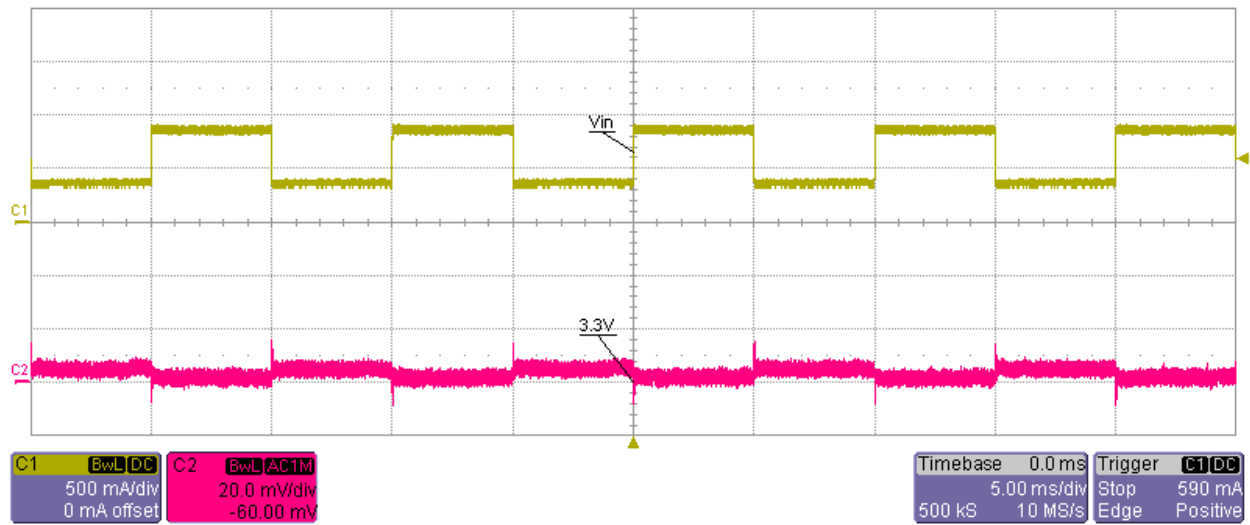

Load Transient Response at 12 Vin and 50%-to-100% Load Step(0.5A-1A) on 3.3V Output Vout1(Full Load were connected to all other outputs)

Ch2 – Vout1 (AC coupled)


Ch1- Iout 1

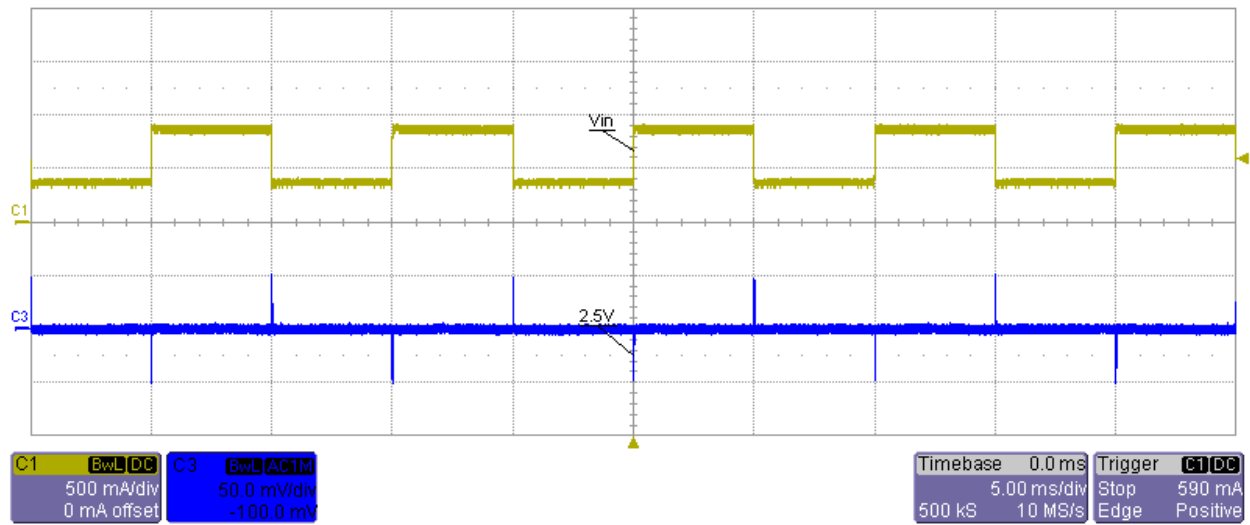

Load Transient Response at 4.5 Vin and 50%-to-100% Load Step(0.5A-1A) on 2.5V Output Vout2(Full Load were connected to all other outputs)

Ch3 – Vout2 (AC coupled)


Ch1- Iout2

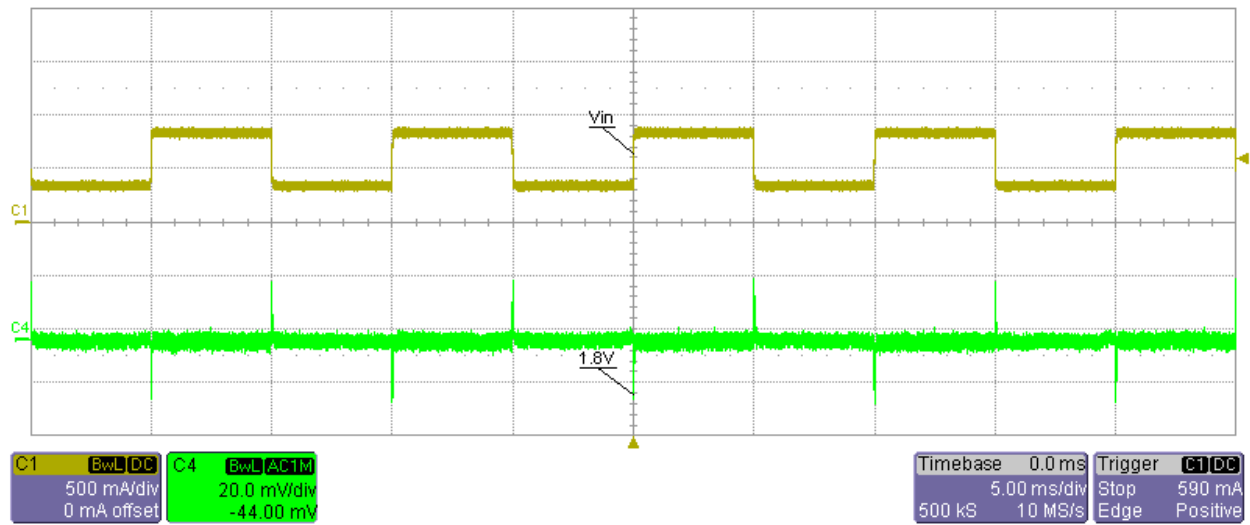

Load Transient Response at 4.5 Vin and 50%-to-100% Load Step(0.5A-1A) on 1.8V Output Vout3(Full Load were connected to all other outputs)

Ch4 – Vout3 (AC coupled)

Ch1- Iout3

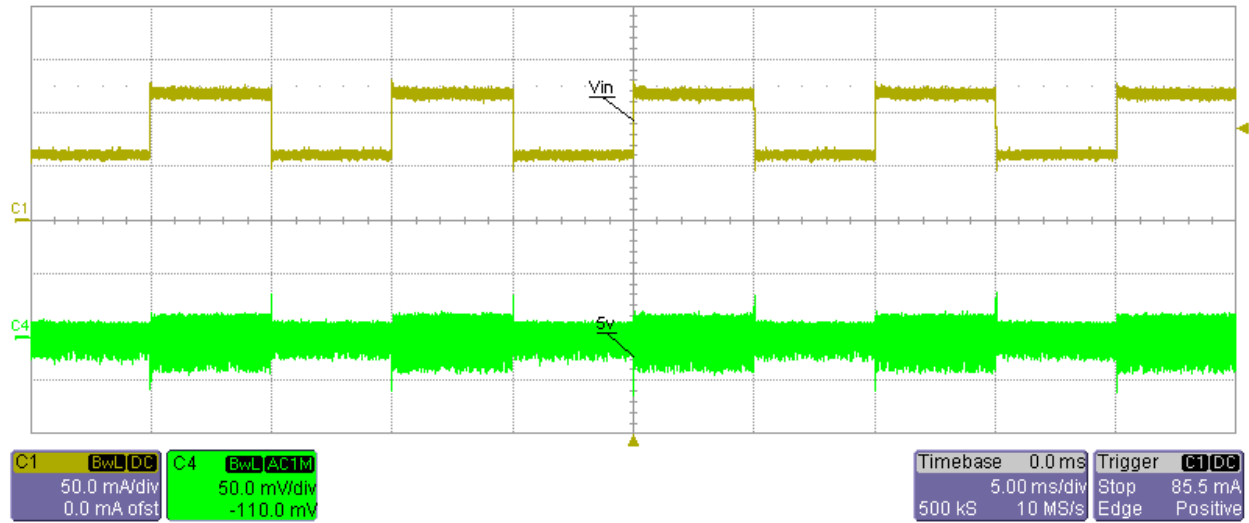


Load Transient Response at 4.5Vin and 50%-to-100% Load Step on 5V Output Vout4 (Full Load were connected to all other outputs)

Ch4 – Vout4 (AC coupled)

Ch4- iout 4

6.2 Startup

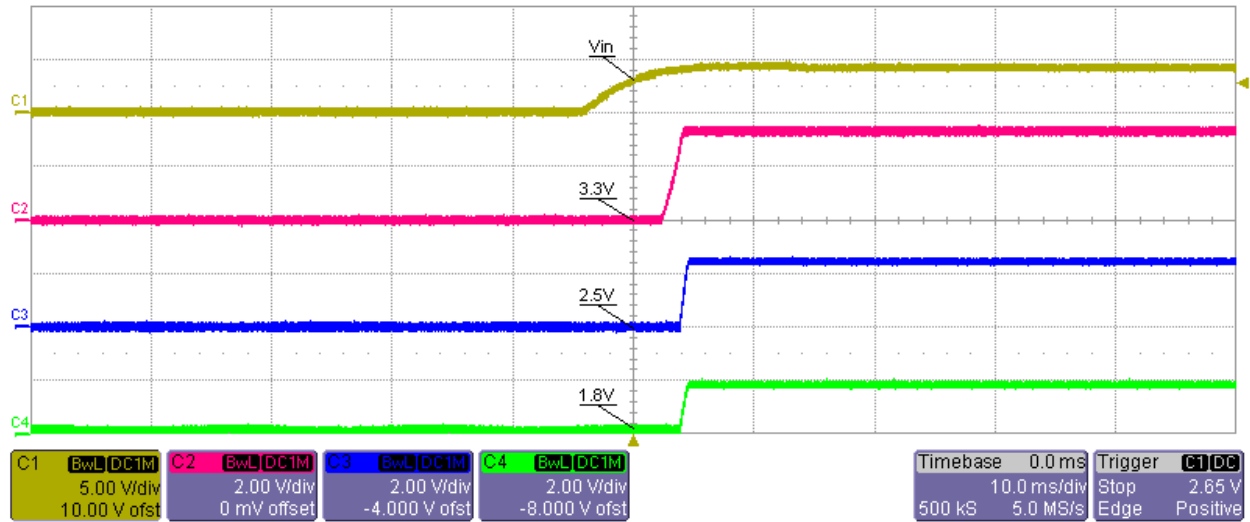


Startup into full Load (all the output was connected to full Load) at 4.5 Vin

Ch1-Vin

Ch2-Vout 1

Ch3-Vout 2

Ch4-Vout3

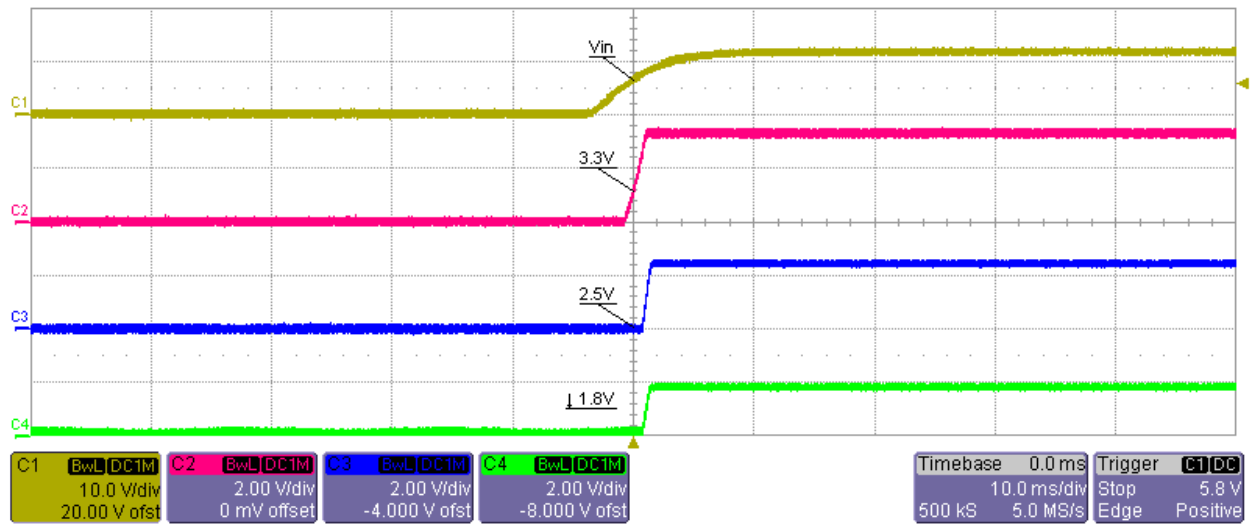


Startup into full Load (all the output was connected to full Load) at 12 Vin

Ch1-Vin

Ch2-Vout 1

Ch3-Vout 2

Ch4-Vout3

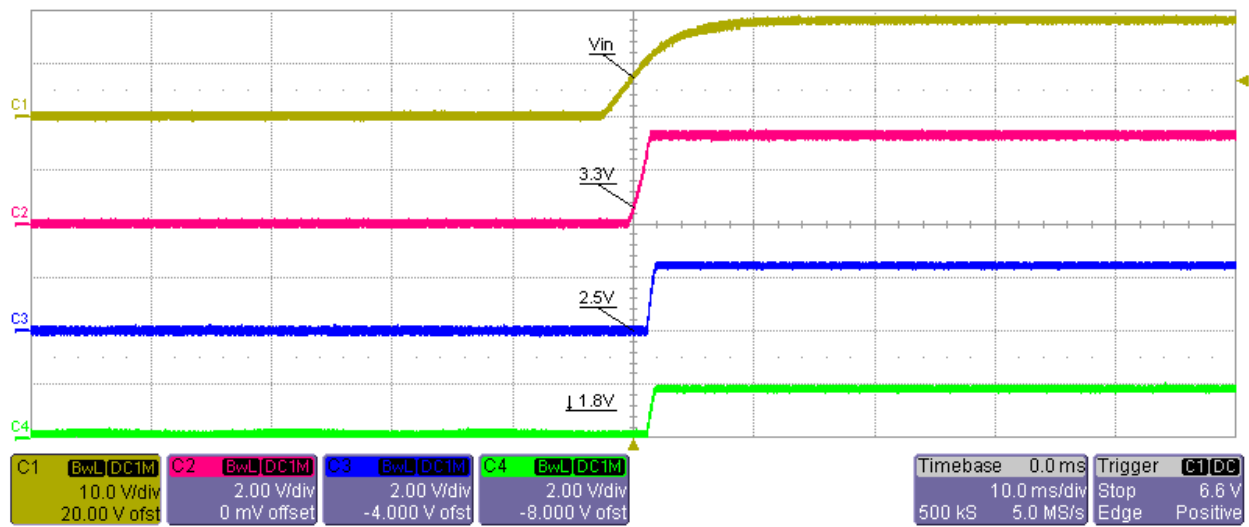


Startup into full Load (all the output was connected to full Load) at 20 Vin

Ch1-Vin

Ch2-Vout 1

Ch3-Vout 2

Ch4-Vout3

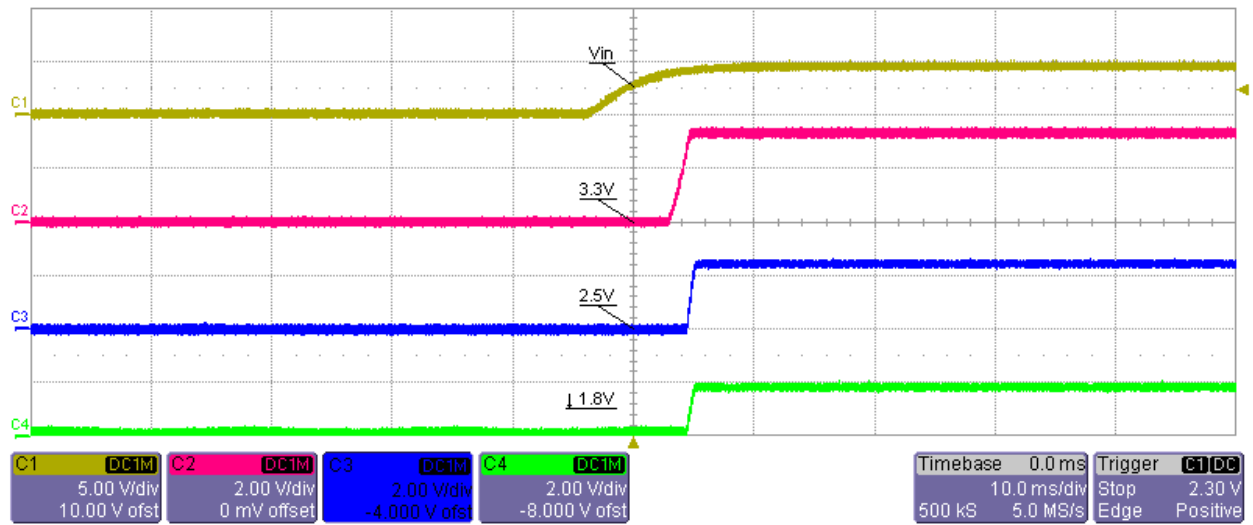


Startup into No Load (all the output was connected to No Load) at 4.5 V_{in}

Ch1- V_{in}

Ch2- $V_{out 1}$

Ch3- $V_{out 2}$

Ch4- V_{out3}

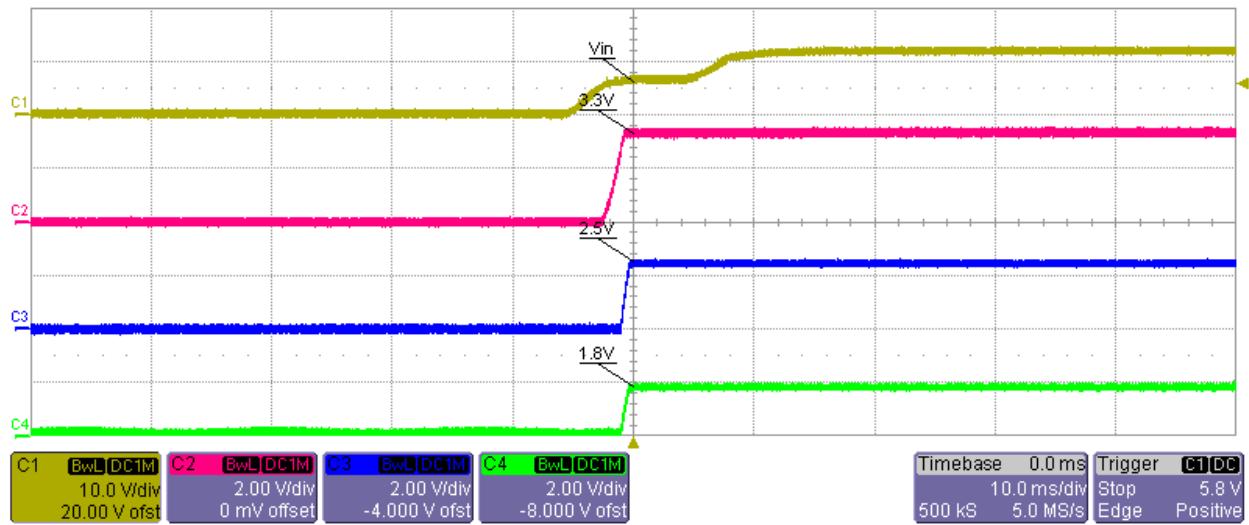


Startup into No Load (all the output was connected to No Load) at 12 Vin

Ch1-Vin

Ch2-Vout 1

Ch3-Vout 2

Ch4-Vout3

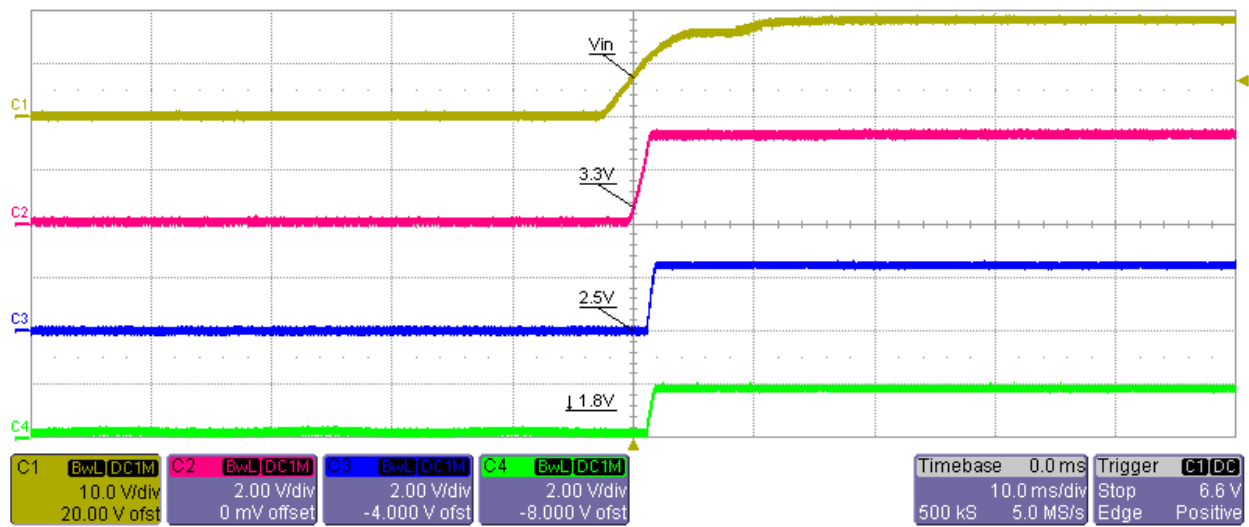

Startup into No Load (all the output was connected to No Load) at 20 Vin


Ch1-Vin

Ch2-Vout 1

Ch3-Vout 2

Ch4-Vout3

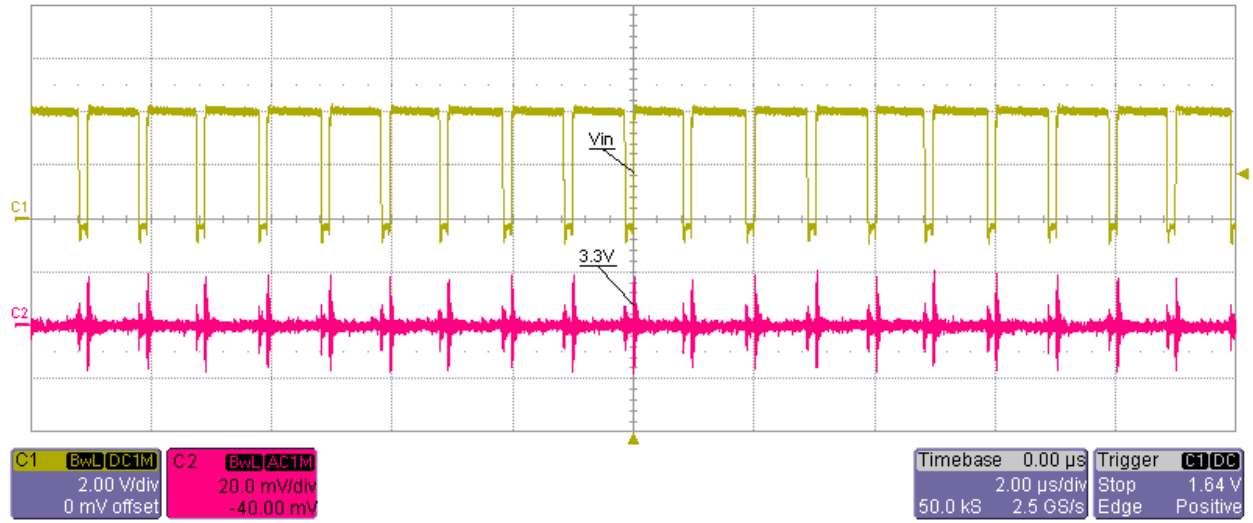
6.3 Output Voltage Ripple and Switch Node Voltage



Switch Node Voltage and Output Voltage Ripple at 4.5 Vin and Full Load on all the outputs

Ch2-Vout1 (AC Coupled)


Ch1-Switching Waveform

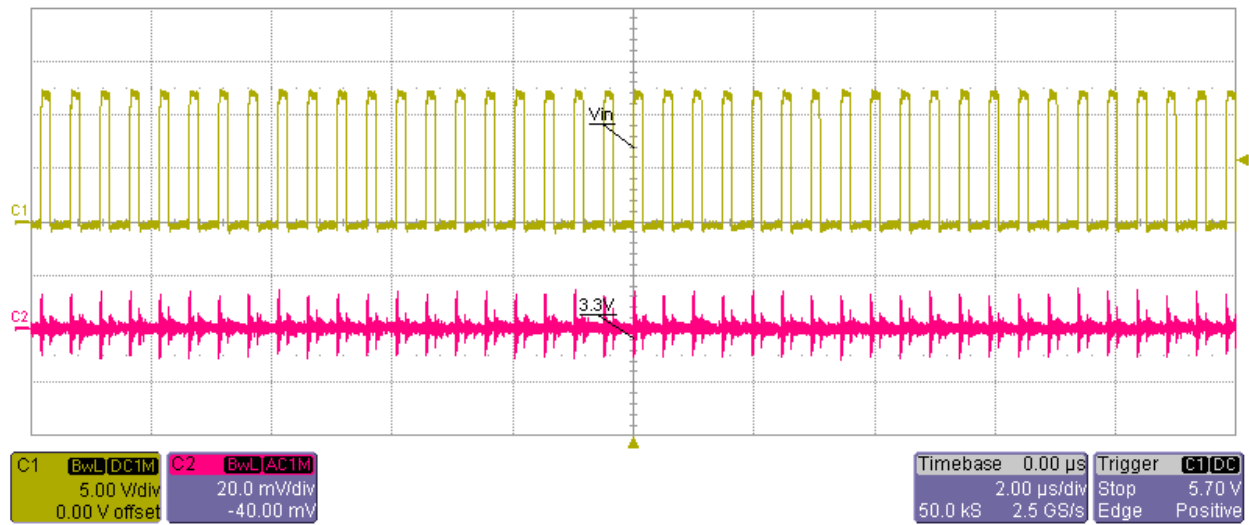

Switch Node Voltage and Output Voltage Ripple at 12 Vin and Full Load on all the outputs

Ch2-Vout1 (AC Coupled)


Ch1-Switching Waveform

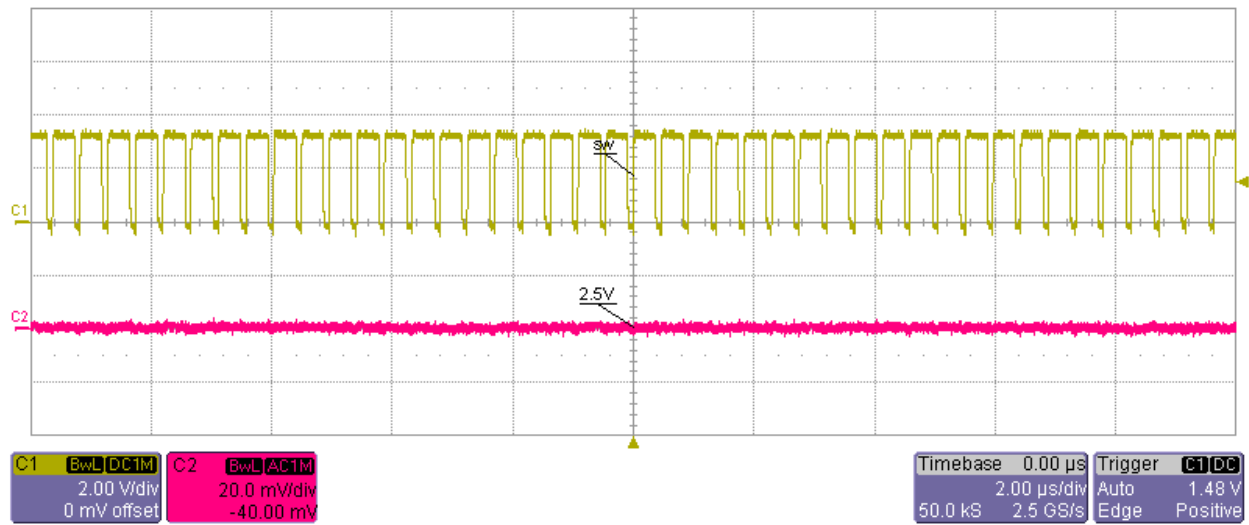

Switch Node Voltage and Output Voltage Ripple at 12 Vin and Full Load on all the outputs (Vripple < 10mVp-p)

Ch2-Vout2 (AC Coupled)

Ch1-Switching Waveform

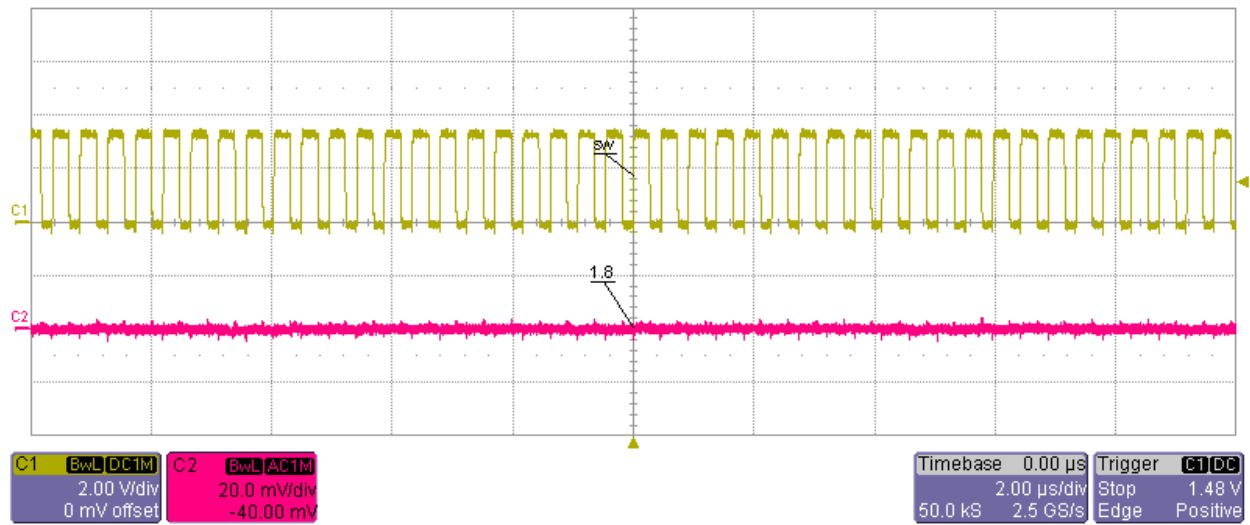


Switch Node Voltage and Output Voltage Ripple at 12 Vin and Full Load on all the outputs (Vripple < 60mVp-p)

Ch2-Vout3 (AC Coupled)


Ch1-Switching Waveform

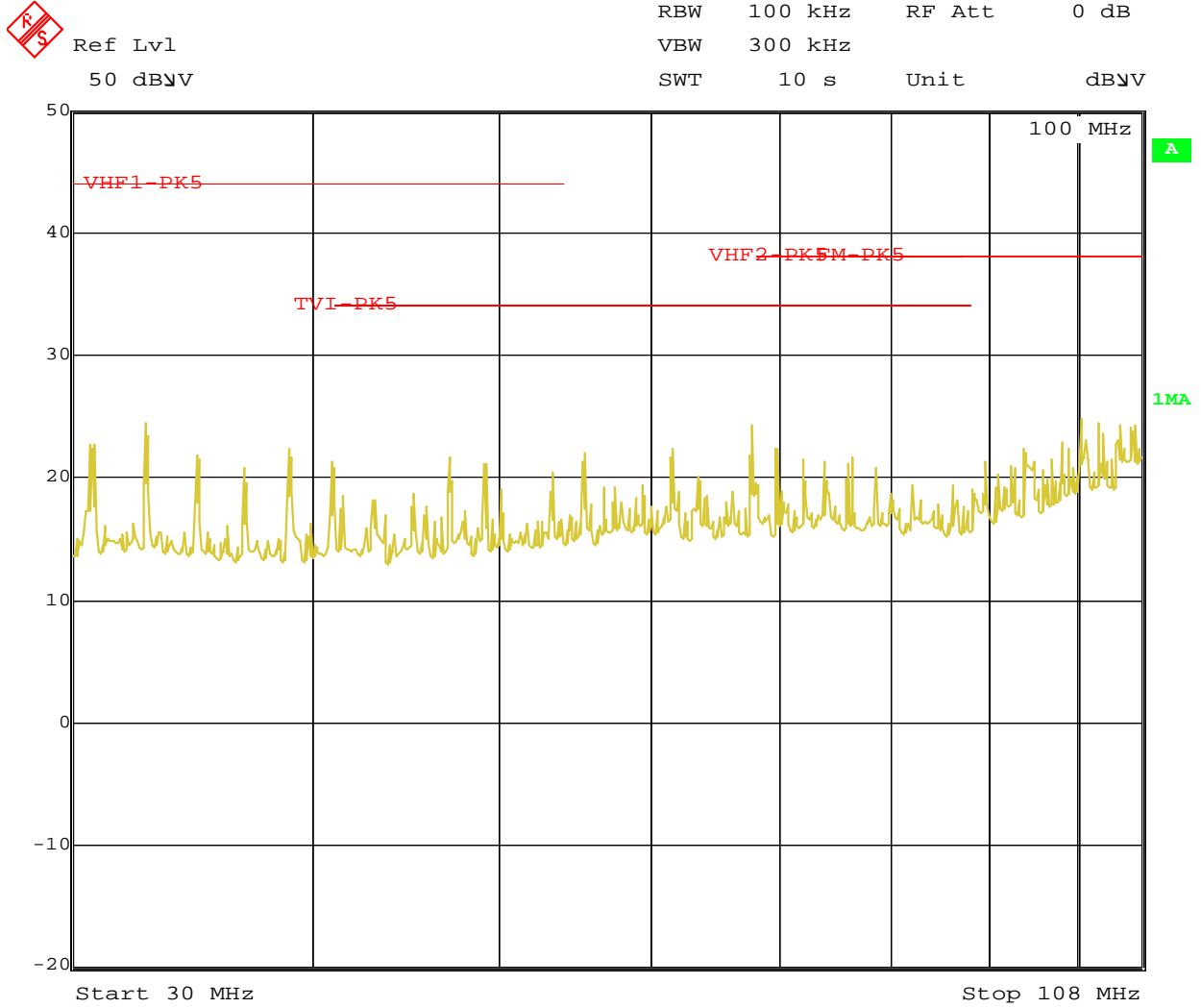Test result – Upto 30MHz Conducted Emission –Peak and Average Detection



Date: 20.DEC.2014 22:24:22

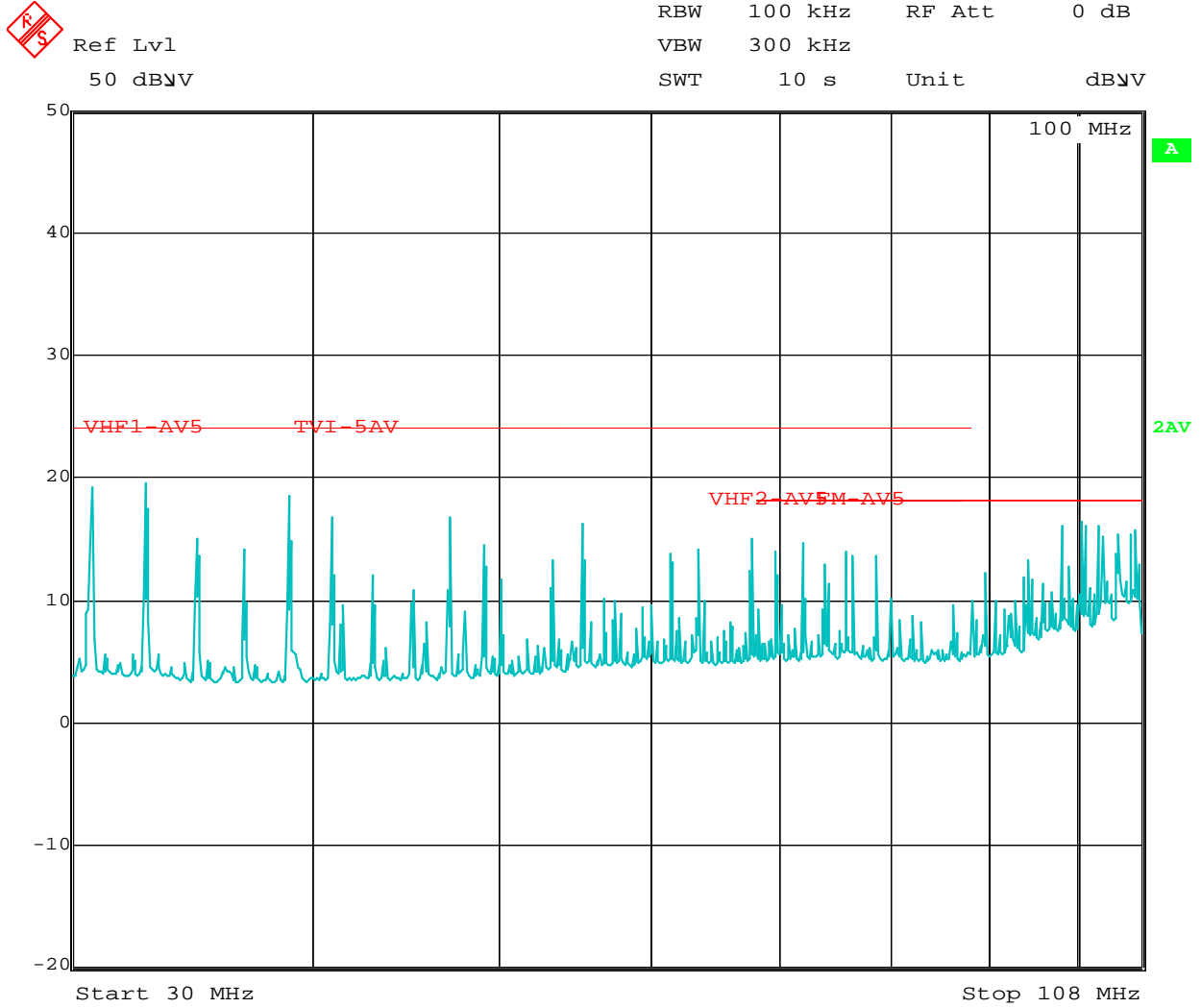Test result –30MHz to 108MHz Conducted Emission –Peak Detection



Date: 20.DEC.2014 22:18:14

Test result -30MHz to 108MHz Conducted Emission -Average Detection

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated