

600W Solar Power Optimizer Reference Design Based on GaN With Wired and Wireless Communication



Description

This reference design is a solar power optimizer, which can support up to 80V input voltage and 80V output voltage, providing upwards of 18A output current and input current. The design uses a configurable four switch buck-boost converter to step up or step down the panel current to the string current. The bypass circuit uses a smart diode controller-based design.

This reference design includes power line communication (PLC) and also features wireless communication. Both the digital control and communication are all implemented in a single C2000™ microcontroller (MCU).

Resources


TIDA-010949	Design Folder
LMG2100R026, TMS320F2800137	Product Folder
TMCS1127, LM74610-Q1	Product Folder
AFE031, CC1352P7	Product Folder
LM5164, INA181	Product Folder

Features


 
- 99.5% peak efficiency and 99.4% CEC weighted efficiency in short mode
- 99.0% peak efficiency and 97.7% CEC weighted efficiency in switching mode at 15A constant output current
- 98.6% peak efficiency and 97.0% CEC weighted efficiency in switching mode at 18A constant output current
- Gallium nitride (GaN) technology with integrated driver-based design
- Power line communication and wireless communication function
- Wide input voltage range: 15V to 80V
- High rated output current: 18A

Applications

- [Solar power optimizer](#)
- [Solar charge controller](#)
- [Rapid shutdown](#)



Ask the TI E2E™ support experts

 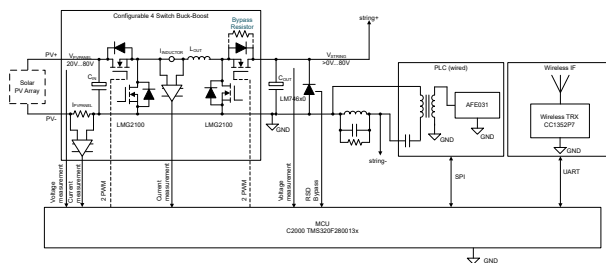

1 System Description

This reference design is developed around TI's half-bridge gallium nitride (GaN) power stage with integrated gate drivers and the TMS320F2800137 C2000 MCU. The design is targeted for single-panel power optimizer designs, capable of operating with 15V to 80V solar panel modules with up to 18A output current.

The design uses the perturb-and-observe algorithm for MPPT and has an operating efficiency of greater than 99%. The high efficiency is attributed to the half-bridge GaN FETs power stage with low $R_{DS(on)}$, low P_{switch} and zero reverse recovery charge in the design. Usage of small sized components is made possible by the high switching frequency (up to 300kHz) of the buck converter.

This design also includes PLC communication based on AFE031 and wireless communication based on CC1352P7 for sending and receiving data such as voltage, current, power, and so forth.

1.1 Key System Specifications

Table 1-1. System Specifications

PARAMETER	SPECIFICATIONS	UNIT
Input panel voltage range	15–80	V
Rated maximum current	18	A
Efficiency	> 99	%
Interleaved buck operating frequency	300	kHz

2 System Overview

2.1 Block Diagram

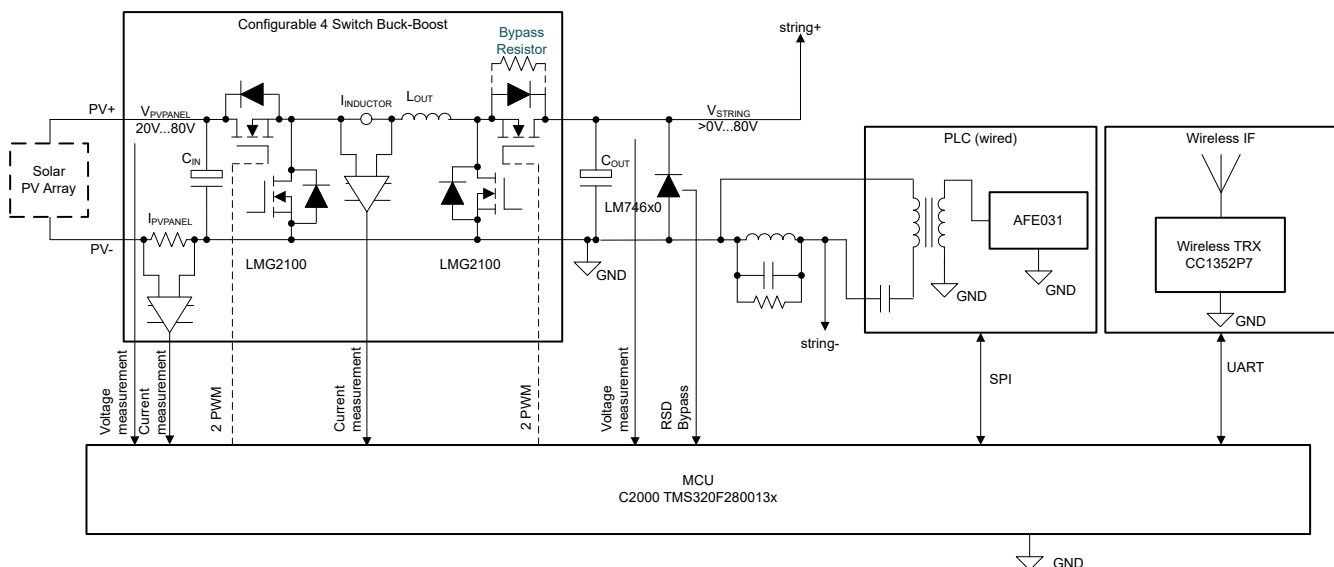


Figure 2-1. TIDA-010949 Block Diagram

2.2 Design Considerations

The TIDA-010949 board consists of a control card (TMS320F2800137) that gathers data from the panel side, string side, and uses this information to do MPPT and close loop control. The MCU then generates PWM signals that directly drive the half-bridge GaN power stage (LMG2100R026). The buck-boost converter modulates the output voltage of the panel to maximize the transmission power.

To power the system, a 100V switching regulator (LM5164) is used to step down the panel voltage to 12V for PLC. The second fly-buck topology (LMR51410) is used to step down from 12V to a non-isolated 5V and two isolated 5V to provide power for the LMG2100 and C2000 control card. Two isolated 5V is to provide driver

voltage for the upper FET of LMG2100 to support 100% duty cycle. From the non-isolated 5V, a low-dropout (LDO) regulator (TPS7A2033) is used to regulate a 3.3V line for the rest of the components.

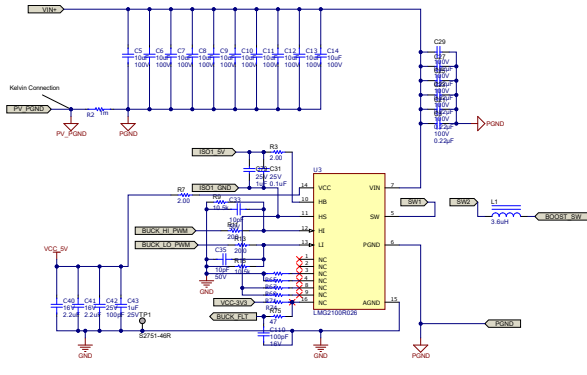


Figure 2-2. DC-DC Converter-Buck Stage

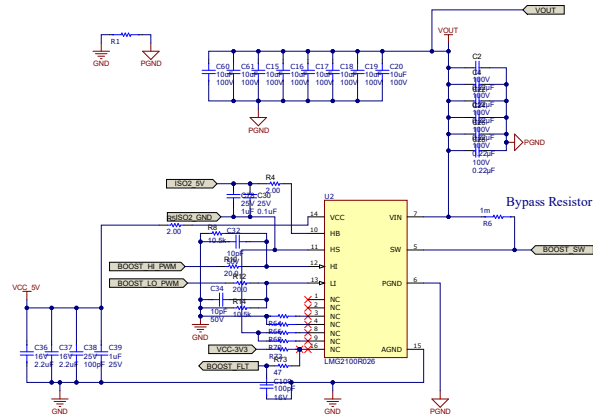


Figure 2-3. DC-DC Converter-Boost Stage

The R6 in the boost stage is a bypass resistor, if the resistor is soldered, then the converter is configured into buck mode. Removing this resistor can configure the converter into 4-switch buck-boost mode. Two LMG2100R026 devices are used in the 4-switch buck-boost power stage. To better utilize the potential of the GaN device, component selection and the layout are important. High-quality input and output MLCCs are needed to better handle the high frequency current during switching. The layout is required to minimized the parasitics in the power loop, thus to reduce the voltage spike and ringing. Short, straight traces produce the lowest impedance path for the signal and minimize the current loop area, thereby reducing loop inductances present. Bypass capacitors filter and condition signals before use and are placed as close to the respective component as possible. Any extraneous trace between the capacitor and component mitigates the effectiveness of the bypass capacitor.

 


Figure 2-4. LMG2100R026 Layout

The AFE031 is used for the power line communication interface. This interface includes a power amplifier, PGAs, and filters for the TX and RX path as well as an internal DAC. The SPI to the MCU is used to configure the filters, PGAs, and the internal DAC. For transmitting data, the PWM mode is used. See also the [AFE031 Powerline Communications Analog Front-End](#) data sheet for a detailed design description for PWM mode. In the RX path, a band-pass filter is implemented using R58, C87, L5, R59, L6, and C91. This filter removes any noise outside the frequency band used for the PLC communication. The output of the band-pass filter is connected to the internal PGAs and RX filters of the AFE031 and is then connected to an ADC of the MCU, which is sampling and decoding the filtered signal.

The coupling circuit connects the AFE031 to the power line and removes the high voltage to protect the low-voltage circuits of the AFE031. The transformer and DC blocking capacitor in series are in parallel with an LRC circuit. The resonance frequency of this LRC circuit needs to be set to the PLC carrier frequency. This makes sure that there is always sufficient impedance to couple the PLC signal onto the power line and the signal is not shorted through the output capacitor of the power optimizer. R23 sets the impedance at the resonance frequency. L4 needs to handle the full DC current without saturation.

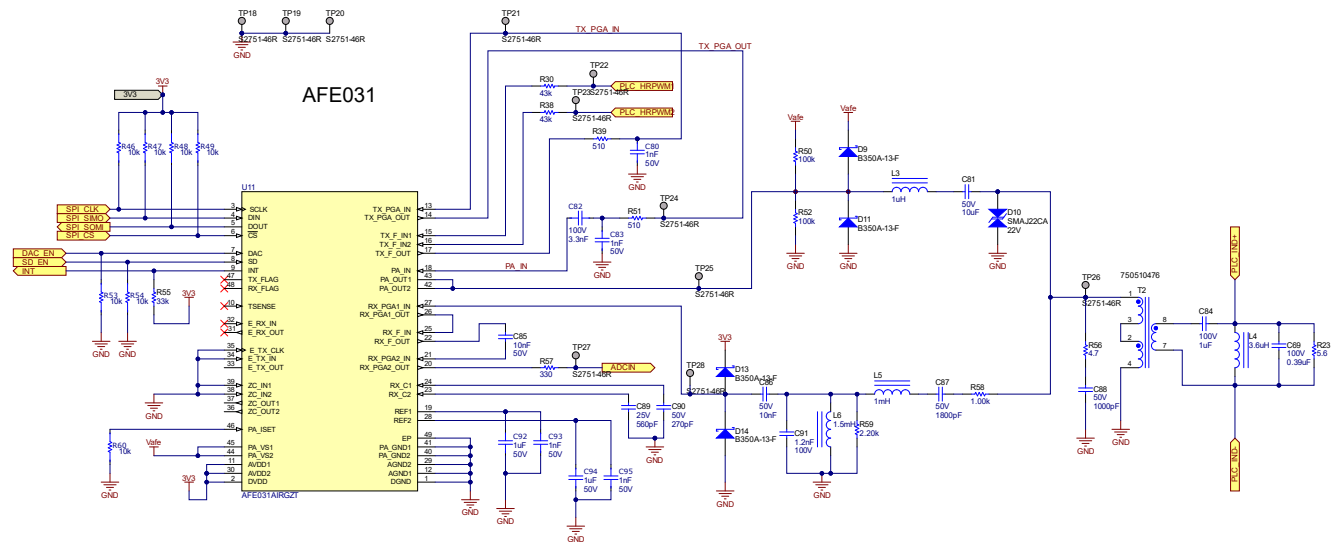


Figure 2-5. PLC Coupling Circuit

The reference design utilizes J4 and J5 connectors for interfacing the MCU with wireless connectivity modules. These modules add a lot of connectivity options like Wi-SUN®, Zigbee®, Bluetooth® Low Energy, and Wi-Fi®.

The C2000 MCU continuously measures parameters like voltages and currents on input and output and periodically sends this data over universal asynchronous receiver-transmitter (UART). This data can be transmitted over a wireless network to a monitoring system. Also the connectors have dedicated pins to enable rapid shutdown over a wireless network feature.

The wireless connectivity example is available for evaluation by request.

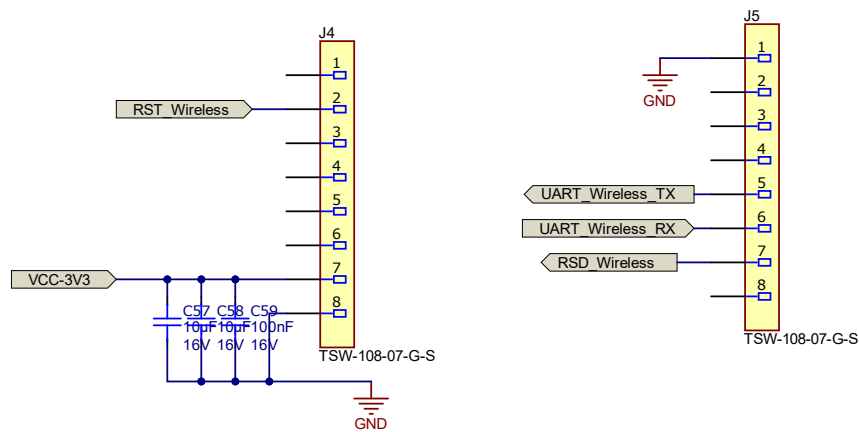


Figure 2-6. Wireless Connectors

2.3 Highlighted Products

2.3.1 TMS320F2800137

The TMS320F280013x (F280013x) is a member of the C2000™ real-time microcontroller family of scalable, ultra-low latency devices designed for efficiency in power electronics.

The real-time control subsystem is based on TI's 32-bit C28x DSP core, which provides 120MHz of signal-processing performance for floating- or fixed-point code running from either on-chip flash or SRAM. The C28x CPU is further boosted by the Trigonometric Math Unit (TMU), speeding up common algorithms key to real-time control systems. The F280013x supports up to 256KB (128KW) of flash memory. Up to 36KB (18KW) of on-chip SRAM is also available to supplement the flash memory.

High-performance analog blocks are integrated into the F280013x real-time microcontroller (MCU) and are closely coupled with the processing and pulse width modulation (PWM) units to provide best-in-class real-time signal chain performance.

Fourteen PWM channels enable control of various power stages from a 3-phase inverter to power-factor correction and other advanced multilevel power topologies.

The voltage and current of the panel and string lines are used to calculate and track the maximum power point (MPP) and the TMS320F2800137 enables quick data acquisition from the various analog signals using the internal analog-to-digital converter (ADC), set to read from the ADC channels once every 40µs. Operating at 120MHz allows for fast conversion and calculation to efficiently perform MPPT and adjust the duty cycle of converter accordingly. The comparator subsystem (CMPSS) is also utilized to fast protect the converter from overvoltage, overcurrent or overtemperature.

An enhanced pulse width modulator (ePWM) is used to generate the PWM for 4 switches. The high-resolution pulse width modulator (HRPWM) can be used to generate a 3-level signal for AFE031, which can be used for PLC transmission function. The internal ADC is used to sample the RX signal at 300kHz to receive the PLC signals. An FSK decoding library (part of the C2000 ware) is used to decode the sampled signal.

Status indicators, controlled by the MCU, are also included in the design to provide feedback to the user.

2.3.2 LMG2100R026

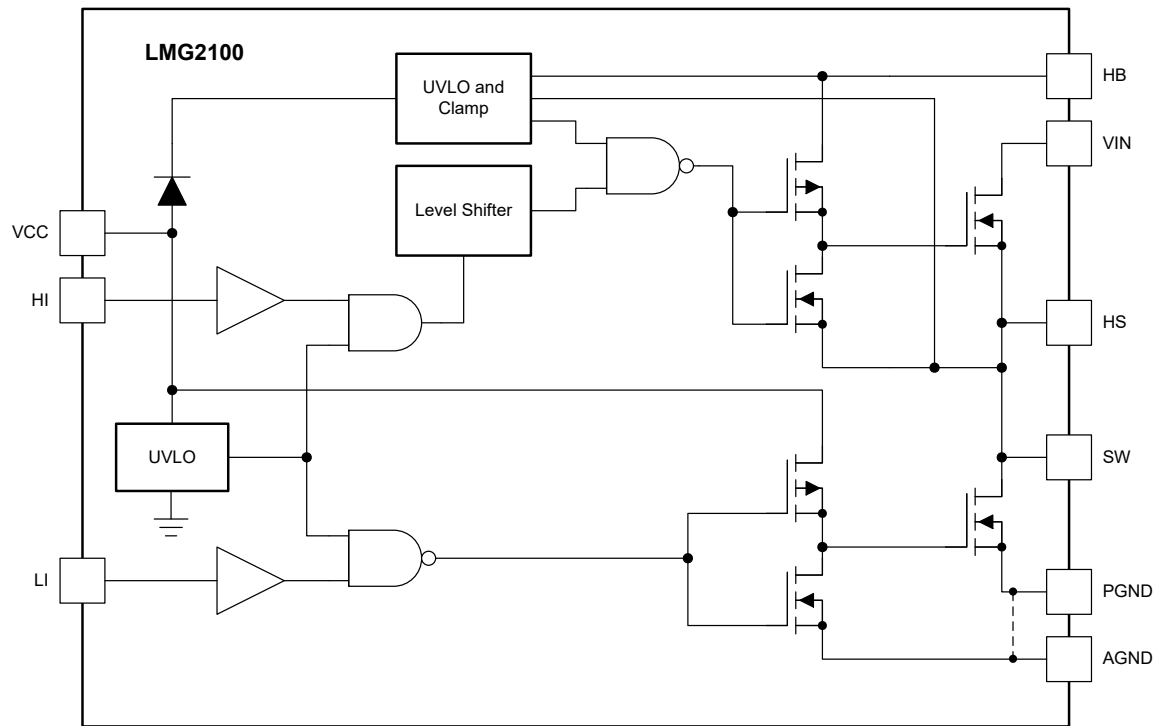


Figure 2-7. LMG2100 Functional Block Diagram

The LMG2100R026 device is an 93V continuous, 100V pulsed, 53A half-bridge power stage, with integrated gate-driver and enhancement-mode Gallium Nitride (GaN) FETs, $2.6\text{m}\Omega$ $R_{DS(on)}$.

- 5V external bias power supply
- Zero reverse recovery
- Very small input capacitance C_{ISS} and output capacitance C_{OSS}
- Internal bootstrap supply voltage clamping to prevent GaN FET overdrive
- Excellent propagation delay (33ns typical) and matching (2ns typical)
- Exposed top QFN package for top-side cooling
- Package optimized for easy PCB layout
- $7.0\text{mm} \times 4.5\text{mm} \times 0.89\text{mm}$ lead-free package

The device extends advantages of discrete GaN FETs by offering a more user-friendly interface. The device has a practical design for applications requiring high-frequency, high-efficiency operation in a small form factor.

The LMG2100R026, half-bridge, GaN power stage with highly integrated high-side and low-side gate drivers, includes built-in UVLO protection circuitry and an overvoltage clamp circuitry. The clamp circuitry limits the bootstrap refresh operation to make sure that the high-side gate driver overdrive does not exceed 5.4V. The device integrates two, $2.6\text{m}\Omega$ GaN FETs in a half-bridge configuration. The device can be used in many isolated and non-isolated topologies allowing very simple integration. The HI and LI pins can be independently controlled to minimize the third quadrant conduction of the low-side FET for hard-switched buck converters. The package is designed to minimize the loop inductance while keeping the PCB design simple. TI recommends a small footprint MLCC to minimize trace length to the pin. Place the bypass and bootstrap capacitors as close as possible to the device to minimize parasitic inductance. The drive strengths for turn-on and turn-off are optimized to make sure high-voltage slew rates without causing much excessive ringing on the gate or power loop.

2.3.3 TMCS1127

The TMCS1127 is a galvanically isolated Hall-effect current sensor with industry-leading isolation and accuracy. An output voltage proportional to the input current is provided with excellent linearity and low drift at all sensitivity options. Precision signal conditioning circuitry with built-in drift compensation is capable of less than 2.75% maximum sensitivity error over temperature and lifetime with no system level calibration, or less than 1.5% maximum sensitivity error including both lifetime and temperature drift with a one-time calibration at room temperature.

AC or DC input current flows through an internal conductor generating a magnetic field measured by integrated, on-chip, Hall-effect sensors. Core-less construction eliminates the need for magnetic concentrators. Differential Hall-effect sensors reject interference from stray external magnetic fields. Low conductor resistance increases measurable current ranges up to $\pm 96\text{A}$ while minimizing power loss and easing thermal dissipation requirements. Insulation capable of withstanding 5kV_{RMS} , coupled with a minimum of 8mm creepage and clearance, provides high levels of reliable lifetime reinforced working voltage. Integrated shielding enables excellent common-mode rejection and transient immunity.

2.3.4 LM5164

The LM5164 synchronous buck converter is designed to regulate over a wide input voltage range, minimizing the need for external surge suppression components. A minimum controllable on-time of 50ns facilitates large step-down conversion ratios, enabling the direct step-down from a 48V nominal input to low-voltage rails for reduced system complexity and design cost. The LM5164 operates during input voltage dips as low as 6V, at nearly 100% duty cycle if needed, making this device an excellent choice for wide input supply range industrial and high cell count battery pack applications.

With integrated high-side and low-side power MOSFETs, the LM5164 delivers up to 1A of output current. A constant on-time (COT) control architecture provides nearly constant switching frequency with excellent load and line transient response. Additional features of the LM5164 include ultra-low I_Q and diode emulation mode operation for high light-load efficiency, remarkable peak and valley overcurrent protection, integrated V_{CC} bias supply and bootstrap diode, precision enable and input UVLO, and thermal shutdown protection with automatic recovery. An open-drain PGOOD indicator provides sequencing, fault reporting, and output voltage monitoring. The LM5164 is available in a thermally-enhanced, 8-pin SO PowerPAD™ integrated circuit package. The 1.27mm pin pitch provides adequate spacing for high-voltage applications.

2.3.5 LM74610-Q1

The LM74610-Q1 is a controller device that can be used with an N-channel MOSFET in a reverse polarity protection circuitry. The device is designed to drive an external MOSFET to emulate an ideal diode rectifier when connected in series with a power source. This scheme is not referenced to ground and thus has Zero I_Q . The LM74610-Q1 controller provides a gate drive for an external N-channel MOSFET and a fast response internal comparator to discharge the MOSFET gate in the event of reverse polarity. This fast pulldown feature limits the amount and duration of reverse current flow if opposite polarity is sensed. The device design also meets CISPR25 Class 5 EMI specifications and automotive ISO7637 transient requirements with a qualified TVS diode.

2.3.6 AFE031

The AFE031 is a low-cost, integrated, power line communications (PLC) analog front-end (AFE) device that is capable of capacitive- or transformer-coupled connections to the power line while under the control of a DSP or microcontroller. This device is an excellent choice for driving low impedance lines that require up to 1.5A into reactive loads. The integrated receiver is able to detect signals down to $20\mu\text{V}_{\text{RMS}}$ and is capable of a wide range of gain options to adapt to varying input signal conditions. This monolithic integrated circuit provides high reliability in demanding power line communications applications.

The AFE031 transmit power amplifier operates from a single supply in the range of 7V to 24V. At maximum output current, a wide output swing provides a 12V_{PP} ($I_{\text{OUT}} = 1.5\text{A}$) capability with a nominal 15V supply. The analog and digital signal processing circuitry operates from a single 3.3V power supply.

2.3.7 CC1352P7

The CC1352P7 device with SimpleLink™ platform is a multiprotocol and multiband Sub-1 GHz and 2.4GHz wireless microcontroller (MCU) supporting Thread, Zigbee®, Bluetooth® Low Energy 5.2, IEEE 802.15.4g, IPv6-enabled smart objects (6LoWPAN), mioty®, Wi-SUN®, proprietary systems, including the TI 15.4-Stack (Sub-1GHz and 2.4GHz), and concurrent multiprotocol through a Dynamic Multiprotocol Manager (DMM) driver. The CC1352P7 is based on an Arm® Cortex®-M4F main processor and optimized for low-power wireless communication and advanced sensing in grid infrastructure, building automation, retail automation, personal electronics, and medical applications.

3 System Design Theory

3.1 MPPT Operation

The power output from a photovoltaic (PV) panel depends on a few parameters, such as the irradiation received by the panel, panel voltage, panel temperature, and so forth. The power output also varies continuously throughout the day because of varying conditions.

Figure 3-1 shows the I-V curve and the P-V curve of a solar panel. The I-V curve represents the relationship between the panel output current and the output voltage. As the I-V curve in Figure 3-1 shows, the panel current is at the maximum when the terminals are shorted and is at the lowest when the terminals are open and unloaded.

 


Figure 3-1. Solar Panel Characteristics I-V and P-V Curves

As Figure 3-1 shows, obtain the maximum power output from the panel represented as P_{MAX} at a point when the product of the panel voltage and the panel current is at the maximum. This point is designated as the maximum power point (MPP).

The graphs in Figure 3-2 and Figure 3-3 show examples of how each of the various parameters affect the output power from the solar panel. The graphs also show the variation in the power output of a solar panel as a function of irradiance. Observe in these graphs how the power output from a solar panel increases with the increase in irradiance and decreases with a decrease in irradiance. Also note that the panel voltage at which the MPP occurs also shifts with the change in irradiance.

 


Figure 3-2. Solar Panel Output Power Variation Under Different Irradiation Conditions—Graph A

 


Figure 3-3. Solar Panel Output Power Variation Under Different Irradiation Conditions—Graph B

Figure 3-4 shows a typical graph representing the variation in the power output of a photovoltaic panel as a function of the temperature. Observe how the panel current (and thereby the panel power) decreases with an increase in temperature. The MPP voltage continues to shift substantially with the change in temperature.

 


Figure 3-4. Solar Panel I-V Curve Variation With Temperature Under Constant Irradiation Conditions

Draw the maximum power from a solar panel by operating the panel close to the MPP point; however, doing so poses two challenges:

1. Providing a way to connect a battery or load with a different operating voltage in comparison to the MPP of the panel
2. Identifying the MPP automatically, as the MPP varies with the environmental conditions and is not a constant

Directly connecting a solar panel with a V_{MPP} close to 17V to a 12V lead acid battery forces the panel to operate at 12V, which reduces the amount of power that can be drawn from the panel. From this situation, one can surmise that a DC/DC converter is able to draw more power from the solar panel because this converter forces the solar panel to operate close to the V_{MPP} and transfer the power to a 12V lead acid battery (impedance matching).

The preceding paragraph explains why the user implements a synchronous buck converter to charge the lead acid battery from the solar panel and address the first challenge.

The second challenge of automatically identifying the MPP of the panel is typically performed by employing MPPT algorithms in the system. The MPPT algorithm tries to operate the photovoltaic panel at the maximum power point and uses a switching power stage to supply the load with the power extracted from the panel.

Perturb and observe is one of the most popular MPPT algorithms used. The fundamental principle behind this algorithm is simple and easy to implement in a microcontroller-based system. The process involves slightly increasing or decreasing (perturbing) the operating voltage of a panel. Perturbing the panel voltage is accomplished by changing the duty cycle of the converter. Assuming that the panel voltage has been slightly increased and that this leads to an increase in the panel power, then another perturbation in the same direction is performed. If the increase in the panel voltage decreases the panel power, then a perturbation in the negative direction is done to slightly lower the panel voltage.

By performing the perturbations and observing the power output, the system begins to operate close to the MPP of the panel with slight oscillations around the MPP. The size of the perturbations determines how close the system is operating to the MPP. Occasionally this algorithm can become stuck in the local maxima instead of the global maxima, but this problem can be solved with minor tweaks to the algorithm.

The P&O algorithm is easy to implement and effective, and was chosen for this design.

3.2 Power Optimizer Function

A string inverter using multi-panels in series is a mainstream type of solar inverter, the lowest cost per watt makes this method attractive. But this method has the risk of catching fire caused by DC arc due to the high voltage and harsh environment, and the fire is difficult to extinguish. PV panels always produce high voltage even when the string inverter has stopped working since the sun is always there. Also, when some panels are

partially shaded, the output current of the shaded panel decreases, thus, the whole string current decreases since panels are in series, causing the string power to drop significantly as shown in Figure 3-5.

For example, like the ideal working condition on the left of Figure 3-5, 10 PV panels are in series, each one with full irradiation can output 600W power, at 40V and 15A. The whole string power is $10 \times 600W = 6000W$.

When the string is partially shaded like on the middle of Figure 3-5, one panel cannot have full irradiation, the output current of this panel drops, the string current is 5A now, the whole string power is only $40V \times 5A \times 10 = 2000W$. As a result, total power drops 66.7% just because one panel is shaded. This reduces the profit of the string inverter a lot, so a power optimizer is needed to help the string inverter solve these conditions.

The right side of Figure 3-5 shows a partially shaded string but power optimizers are installed for each panel. Although the shaded panel can only output 40V, 5A, the DC/DC circuit of optimizer can boost up the current to 15A, other panels are not affected. The string power with optimizer is $40V \times 5A + 40V \times 15A \times 9 = 5600W$. Additional 3600W power is saved to generate more profit.

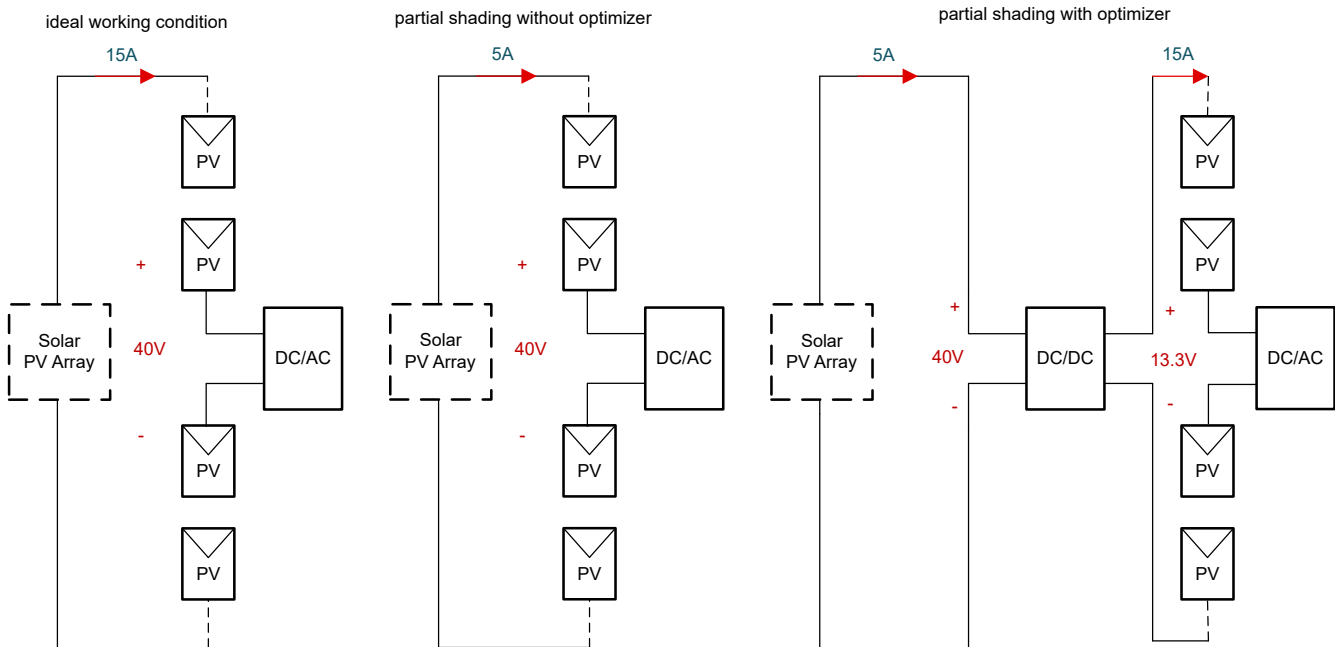


Figure 3-5. PV String Working Conditions With and Without Optimizer

A power optimizer can also better protect the PV string. Since the optimizer is connected independently to each panel, the high voltage of the DC link is on the output side of the optimizer instead of the PV side. The optimizer can easily do the rapid shut down (RSD) function, which is mandatory in many countries.

During fault condition, the PLC receiver of the optimizer gets the RSD signal from host. Then the optimizer cuts the PV panel from the string, and allows the current to go through the bypass circuit. By using the LM74610-Q1 turn on, the bypass circuit does not need the MCU to do anything, thus greatly improving the reliability of the circuit. In arc fault, disconnecting PV panels from the string eliminates high voltage in the string inverter, which significantly reduces the rescue risk.

3.2.1 Power Line Communication (PLC)

The implemented power line communication uses FSK modulation. In this design a SunSpec RSD receiver is implemented, similar to the receiver implementation of TIDA-060001 and BOOSTXL-AFE031-DF1. See also the [SunSpec® Rapid Shutdown Transmit and Receive](#) design guide and [BOOSTXL-AFE031-DF1](#) user's guide. A bidirectional frequency shift keying (FSK) based PLC can be implemented in this reference design.

3.3 Four-Switch Buck-Boost Converter

Table 3-1. Specifications for Four-Switch Buck-Boost Converter

PARAMETER	SPECIFICATIONS	UNIT
Maximum input voltage	80	V
Maximum output voltage	80	V
Maximum current	18	A

This reference design implements a 4-switch buck-boost topology to step up or step down the panel current to string current, so this reference design can be used in many applications that need to operate module-level optimization.

This topology can also be configured to a buck topology by using a bypass resistor to bypass the upper switch of the boost side. This bypass resistor simplifies the design and implementation of both topologies.

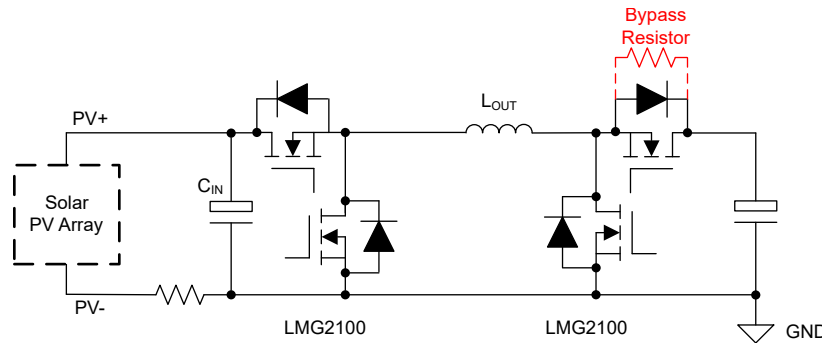


Figure 3-6. Configurable Four-Switch Buck-Boost Topology

A stack-carrier modulation is used to generate the PWMs for the 4-switch buck-boost topology, as shown in [Figure 3-6](#).

The carrier of the buck stage and boost stage is stacked. The buck carrier amplitude is between 0 to 1.05, the boost carrier amplitude is between 0.95 to 2, so, naturally, these two carriers have an overlapping when the modulator is between 0.95 to 1.05. Thus, this modulation scheme can seamlessly change from buck mode to buck-boost mode and boost mode, as shown in [Figure 3-7](#).

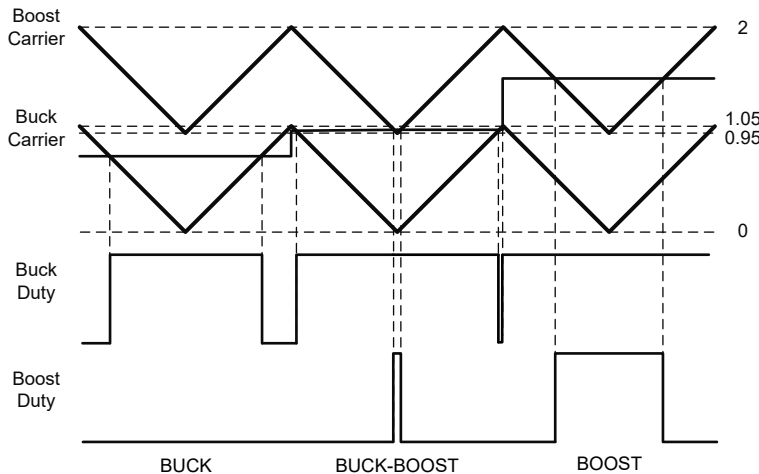


Figure 3-7. Four Switch Buck-Boost Topology Modulation Scheme

Adjusting the carrier starting point in C2000 causes a loss of PWM resolution, if using the theoretical implementation, then the PWM resolution can lose almost 50%, this reduces the performance of the converter. So in software, this is realized by adjusting the modulator of the boost stage and buck stage, as shown in [Figure 3-8](#), the carrier of boost and buck is still between 0–1, while the modulator is between 0–2. By simply multiplying

the modulator of buck by 0.95, which is equivalent to multiplying the carrier of buck by 1.05. The boost stage is similar; first, subtract the modulator of boost by 0.95, and then, multiply the result by 0.95 to get the final modulator of the boost stage. In Equation 1 and Equation 2, M_{buck} is the modulator of the buck stage, M_{boost} is the modulator of the boost stage:

$$M_{\text{buck}} = M_{\text{loop}} \times 0.95 \tag{1}$$

$$M_{\text{boost}} = (M_{\text{loop}} - 0.95) \times 0.95 \tag{2}$$

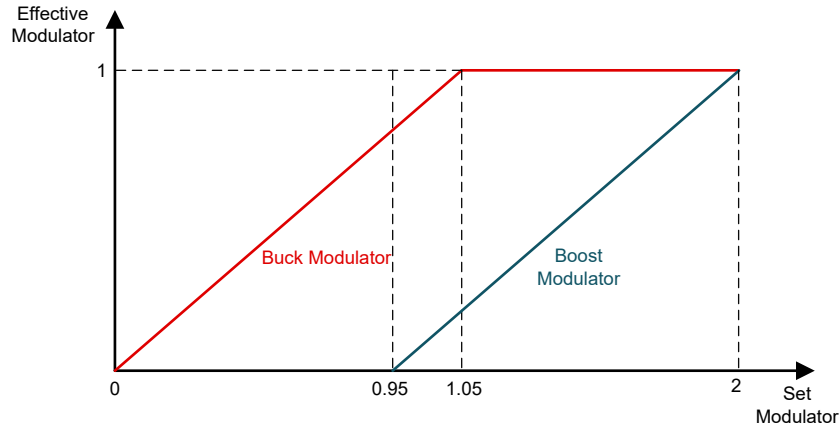


Figure 3-8. Four Switch Buck-Boost Topology Modulation Scheme Implemented in C2000™

To make this four-switch buck-boost power stage more compact and efficient, the LMG2100R026 half-bridge power stage is selected for this reference design for the high maximum V_{DS} of 93V continuous, 100V pulsed rating, and low Q_g and $R_{\text{DS(on)}}$ of 12nC and 2.6m Ω , respectively, at a gate voltage of 5V. Also, the 7.0mm \times 4.5mm \times 0.89mm lead-free package saves a lot of PCB area, and this package is optimized for a smaller high-frequency current loop to provide the very small ringing during the switching period. This is a desirable design for a compact, high power density, and high-efficiency power optimizer of the medium power rating.

3.4 Output Inductance

Continuous conduction mode (CCM) is desired to maintain a high efficiency while delivering the constant current required for the string inverter. When the input voltage range, output voltage, and load current are defined, this leaves the inductor value as the design parameter to maintain CCM.

Put simply, define the desired ripple current (ΔI) for the converter. Normally ΔI is 0.2–0.4 times the output current (I_O). A value of 0.4 is selected as the coefficient of ripple current.

Considering 18A maximum output current, and ignoring the voltage drop on the FETs and resistance of the inductor gives:

$$L \times \frac{\Delta I}{T_{\text{off}}} = V_o \tag{3}$$

The output voltage at an 18A, 600W condition is about 33.3V, the input voltage can be considered 43V at the maximum power point of the PV panel, then, the output inductance can be derived, 3.48 μ H. At half load, considering output voltage at an 18A, 300W condition is about 16.7V, the input voltage is also 43V since the MPP voltage at half irradiation is similar with the MPP voltage at full irradiation, the output inductance is about 4.7 μ H.

In the case of the same size, an inductor with smaller inductance can have a larger saturation current. Finally, a 3.6 μ H inductor is chosen to make the design compact.

3.5 Input Capacitance

Select input capacitors carefully to both reduce the size and satisfy the big ripple current capability (see the [How to select input capacitors for a buck converter](#) analog applications journal).

To get a satisfied MPPT effect, such as 99.5% of maximum power tracking, the input ripple voltage value needs to be small, for many panels, when the V_{panel} is within 97.5%–102.5% of the V_{mpp} , the output power of the panel is above 99.5% of maximum power. For most panels, the MPP voltage is higher than 30V. So, 0.75V is taken as the maximum input ripple voltage (ΔV_{in}).

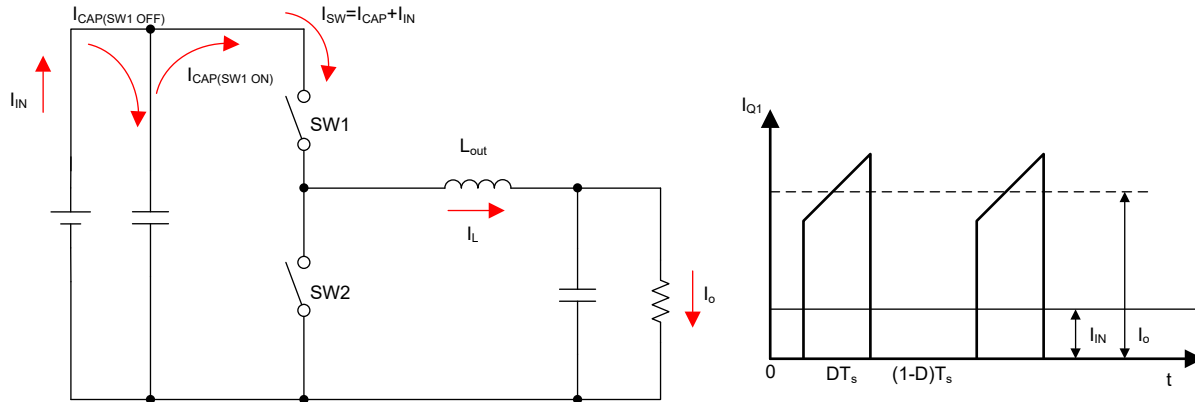


Figure 3-9. Input Current Waveform

The AC current flowing through the input capacitors results in input voltage ripple. Even the majority of the ripple current goes through MLCC, thanks to the low equivalent series resistance (ESR), ripple voltage results from this can be ignored. The rest of the ripple current goes through the electrolytic capacitor if the system has one, although the electrolytic capacitor has a much bigger ESR, the AC current is small, the overall impact for input voltage ripple is minor.

Use [Equation 4](#) to estimate the required effective capacitance that meets the ripple voltage requirement. At 50% duty cycle, the input capacitance C_{in} is biggest.

$$C_{\text{IN}} \geq \frac{D \times (1 - D) \times I_o}{\Delta V_{\text{in}} \times f_{\text{sw}}} \quad (4)$$

Where I_o is 18A and f_{sw} is 300kHz, C_{in} needs to be bigger than 20 μF . Considering the DC bias effect of the MLCC as the voltage increases, the actual value taken needs to be larger depending on the practical situation.

Additionally, the input capacitors also need to meet the thermal stress caused by the ripple current, the bigger the footprint, the lower the temperature rise. Use [Equation 5](#) to calculate the root mean square (RMS) current of the input ripple current.

$$I_{\text{in_rms}} = I_o \times \sqrt{D \times (1 - D) + \frac{1}{12} \times \left(\frac{V_o}{L \times f_{\text{sw}} \times I_o} \right)^2 \times (1 - D)^2 \times D} \quad (5)$$

Duty cycle has a significant impact on the input RMS ripple current. [Figure 3-10](#) is a plot of Input RMS current to Load Current Ratio versus Duty Cycle, from which the largest ripple current RMS can be observed. The largest ripple current occurs when the duty cycle is 0.5. The maximum value of $I_{\text{in_rms}}$ is 9.5A. To reduce the temperature rise of the MLCC, the 1210 footprint is chosen. Meanwhile, it is better to parallel multiple capacitors with small capacity than just use one with a bigger capacity.

 


Figure 3-10. Input RMS, Load Current Ratio vs Duty Cycle

Place additional small MLCCs with low equivalent series inductance (ESL) and low ESR as close as possible to the input side of the FETs, especially using GaN devices with high di/dt and dv/dt slope. These MLCCs can greatly alleviate overshoot of the switching node waveform without sacrificing efficiency.

Bulk capacitors like aluminum electrolytic capacitors can also be added to satisfy the transient response if the response speed of the system is important. Because of the high ESR of electrolytic capacitors, the ripple current can be approximated by dividing the input ripple voltage by the ESR. Also, the waveform is triangular, so the RMS value can be estimated with Equation 6.

$$I_{\text{bulk_rms}} = \frac{1}{2\sqrt{3}} \times \frac{\Delta V_{\text{in}}}{\text{ESR}} \tag{6}$$

Take care when selecting a bulk capacitor due to the low tolerance for RMS current.

3.6 Current Sensor

Table 3-2. Current Sensor Design Criteria

PARAMETER	SPECIFICATION
Maximum common-mode voltage	80V
Maximum input current	18A
Maximum output voltage	3.3V

This reference design requires accurate measurement of the panel and battery currents to calculate and track the maximum power point. The design supports panels of up to 80V, so a maximum common-mode voltage of at least 80V is required.

The TMCS1127 Hall-effect sensor is selected for this reference design due to excellent performance for common-mode noise and low sensitivity error. Equation 7 and Equation 8 are used to calculate the resolution of the current sensor and power dissipation of the sensor for the parameters given in Table 3-2, and an example follows. TMCS1127B2A is selected due to the capability of sensing up to ±31A.

3.6.1 Current Measurement Resolution

The sensitivity of TMCS1127B2A is 50mV/A. The current resolution of the amplifier into a 12-bit ADC is given by:

$$I_{RES} = (V_{OUT} / (ADCMAX \times \text{Sensitivity})) = (3.3V / (4095 \times 50mV/A)) \quad (7)$$

$I_{RES} = 16.1mA$ per bit, that is, 1A equals 62.05bit in MCU

3.6.2 Current Sensor Power Dissipation

Equation 8 is the maximum power dissipation calculation:

$$P_{DISS} = I_{MAX2} \times R_{IN} = (18A)^2 \times 0.7m\Omega \quad (8)$$

$$P_{DISS} = 0.23W$$

3.7 Switching Regulator

This reference design requires 12V for AFE031, 5V for the C2000 control card and GaN device (the LMG2100R026), subsequently stepped down from 5V to 3.3V for the sampling device and other components, to operate. To generate the 12V line from the power lines (panel), a wide VIN buck, switching regulator LM5164 is needed to support a maximum voltage of 80V.

A fly-buck topology based on LMR51410XF, a fixed switching frequency regulator is used to generate two isolated 5V for the upper FET of LMG2100 to support a 100% duty cycle.

3.8 Bypass Circuit

The bypass circuit plays an important role when the optimizer main circuit or the panel malfunctioning. Traditional solar power optimizers use a Schottky diode or a P-N junction diode for the bypass circuit. When the string current is high, the power dissipation of the diode can cause severe thermal issues due to the high forward voltage drop. To reduce the power dissipation of the bypass circuit, another design is using an active MOSFET controlled by the MCU, but the normal operation of the MOSFET relies on the MCU.

In this design, a high reliable and low-power dissipation method is used. The design does not rely on the signal of the MCU for turning on or off, thus the design can bypass the string current with low-power dissipation even when the MCU is not functioning. LM74610-Q1 is used in this design for stand-alone MOSFET control that can work autonomously without any external intervention. The [How to use an ideal diode controller as a scalable input bypass switch in solar applications](#) analog design journal article explains the detailed design and working principle for this method. By adding a depletion MOSFET Q_D in the sense path, the reverse voltage range of the ideal diode controller (42V rated) can be easily extended. String current flows through the power MOSFET Q_1 which lowers the power dissipation of the bypass circuit.

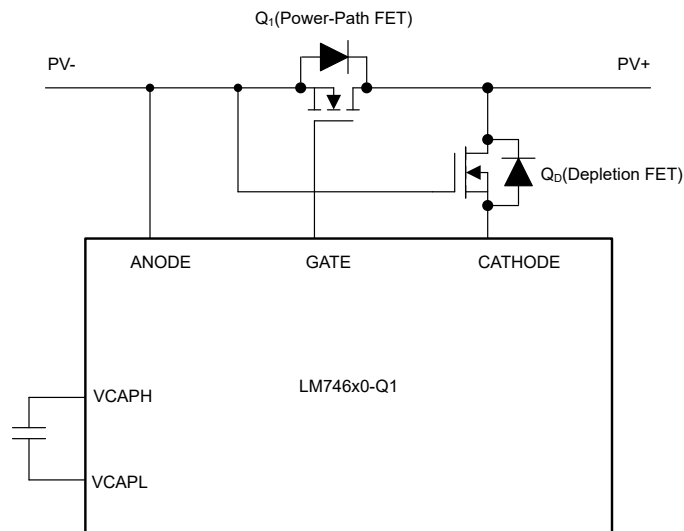


Figure 3-11. Bypass Circuit Based on LM74610-Q1

4 Hardware, Software, Testing Requirements, and Test Results

4.1 Hardware Requirements

The hardware of this reference design is composed of the following:

- TIDA-010949
- TMDSCNCD2800137 control card
- USB Type-C® cable
- USB isolator
- Laptop

The following equipment was used to power and evaluate the board:

- DC power source: ITECH IT6010C-80
- DC load: Chroma 63203A
- Power analyzer: YOKOGAWA WT500

4.2 Software Requirements

To test the board, see the digital power SDK, TIDA-010949 software, and the software user guide.

Figure 4-1 shows the software flow chart.

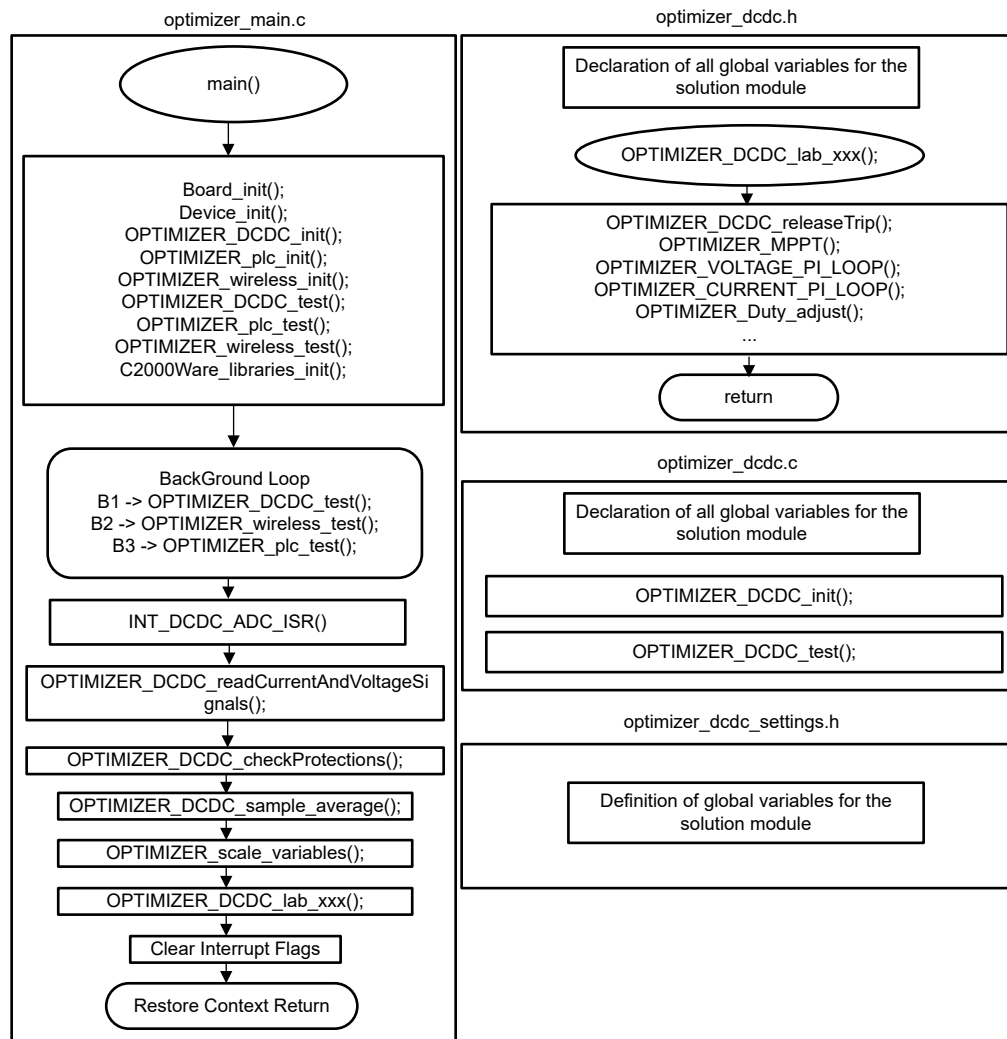


Figure 4-1. Software Flow Chart

4.3 Test Setup

Connect the input to the DC power source and output to the DC load to test the power stage.

If four-switch buck-boost topology is tested instead of buck topology, remove the bypass resistor, see [Figure 4-2](#).

 


Figure 4-2. Test Connection

4.4 Test Results

In these test results, the extra power consumed by the control card (the power consumption of C2000 is retained) is subtracted to better reflect the losses and efficiency of a real system.

4.4.1 Short Mode Test Result

In short mode, the DC source is directly connected to the load through the on-resistance of power switch and passive components on the board. The buck stage duty cycle is 100%, the boost stage duty cycle is 0%. [Figure 4-3](#) shows the block diagram of this mode.

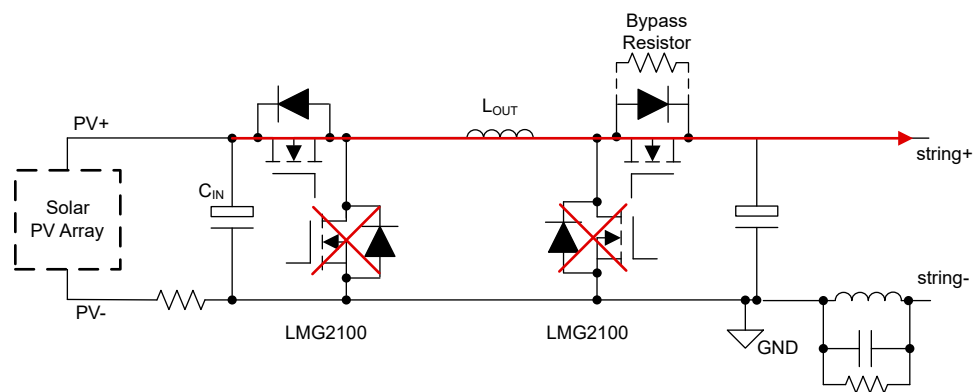


Figure 4-3. Short Mode Block Diagram

Table 4-1, Table 4-2, and Figure 4-4 show the efficiency for different input voltage and power rating. A value of 33V is chosen because most of the MPPT voltage of the 400W panels is at about this range. A value of 43V is chosen because this is a representative voltage for the MPPT voltage of 500W and 600W of the panels.

- Peak efficiency for 33Vin is 99.5% from 120W to 240W and full load efficiency at 400W is 99.3%
- Peak efficiency for 43Vin is 99.6% at 250W, full load efficiency at 600W is 99.3%

Table 4-1. TIDA-010949 Short Mode Efficiency, 33Vin

OUTPUT POWER	20W	40W	80W	120W	180w	240w	300w	400w
V _{in} =33V	97.8%	98.9%	99.3%	99.5%	99.5%	99.5%	99.4%	99.3%

Table 4-2. TIDA-010949 Short Mode Efficiency, 43V_{IN}

OUTPUT POWER	25W	50W	100W	150W	200W	250W	320W	450W	500W	600W
V _{in} =43V	97.6%	98.8%	99.3%	99.5%	99.5%	99.6%	99.5%	99.5%	99.5%	99.3%

 


Figure 4-4. Short Mode Efficiency

4.4.2 Switching Mode Test Result

In switching mode, the power switch starts to switch to operate the active MPPT algorithm. Table 4-3 through Table 4-5 and Figure 4-5 show the test results for different power ratings and currents.

For 400W panels, set a constant output current at 9A, peak efficiency is achieved at 98.7% for power higher than 300W. At 300W output power, the converter works in buck-boost mode. At 400W output power, the converter works in boost mode, see Table 4-3. At other power points, the converter works in buck mode.

For 500W panels, set a constant output current at 12A, peak efficiency is achieved at 98.8% at 500W full load condition. At 500W output power, the converter works in buck-boost mode, see Table 4-4. At other power points, the converter works in buck mode.

For 600W panels, at 15A constant output current condition, peak efficiency is achieved at 99.0% at 600W full load, see Table 4-5. At 18A constant output current condition, peak efficiency is also achieved at 98.6% at full load. At all power points, the converter works in buck mode.

Table 4-3. TIDA-010949 Switching Mode Efficiency, 400W

OUTPUT POWER	20W	40W	80W	120W	200W	300W	400W
$V_{in} = 33V$, $I_{out} = 9A$	89.9%	94.2%	96.6%	97.5%	98.5%	98.7%	98.7%

Table 4-4. TIDA-010949 Switching Mode Efficiency, 500W

OUTPUT POWER	25W	50W	100W	150W	250W	375W	500W
$V_{in} = 43V$, $I_{out} = 12A$	83.9%	92.3%	95.8%	96.8%	97.8%	98.7%	98.8%

Table 4-5. TIDA-010949 Switching Mode Efficiency, 600W

OUTPUT POWER	30W	60W	120W	180W	300W	450W	600W
$V_{in} = 43V$, $I_{out} = 15A$	83.8%	91.6%	95.2%	96.4%	97.6%	98.5%	99.0%
$V_{in} = 43V$, $I_{out} = 18A$	80.6%	89.2%	93.7%	95.7%	97.0%	97.9%	98.6%

 


Figure 4-5. Switching Mode Efficiency

Figure 4-6 shows the switching node waveform in buck stage. Overshoot is very small and there is no obvious ringing.

 


Figure 4-6. No Load Switching Node Waveform, Buck Stage

 


Figure 4-7. Switching Node Waveform Rising Edge With Full Load, Buck Stage

 


Figure 4-8. Switching Node Waveform Falling Edge With Full Load, Buck Stage

Figure 4-9 shows the switching node waveform in boost stage. The waveform is also clean.

 


Figure 4-9. Switching Node Waveform With Full Load, Boost Stage

4.4.3 Bypass Circuit Test Results

Figure 4-10 and Figure 4-11 show the test result of the bypass circuit based on LM746x0-Q1. Channel 2 is the voltage drop of the bypass circuit. Channel 3 is the gate drive voltage of LM74610-Q1. Channel 4 is the bypass current.

The waveform illustrates that this design can effectively bypass the string current with very low voltage drop and provides around a 98.5% duty cycle. This design reduces the power dissipation and improves the system reliability.

 


Figure 4-10. Bypass Circuit Test Results—Graph A

 


Figure 4-11. Bypass Circuit Test Results—Graph B

4.4.4 PLC Test Results

Testing the PLC hardware implementation includes validating the coupling circuit and the band-pass filter in the receive path.

To check the coupling circuit, the impedance was measured using a frequency response analyzer (Venable Instruments Model 3120). Importantly, the coupling network needs to present a high impedance at the PLC carrier frequencies and maintains lower impedances outside the communication band. Figure 4-12 shows the measured impedance. Yellow markers highlight the impedance at the mark and space frequencies of the RSD PLC protocol.

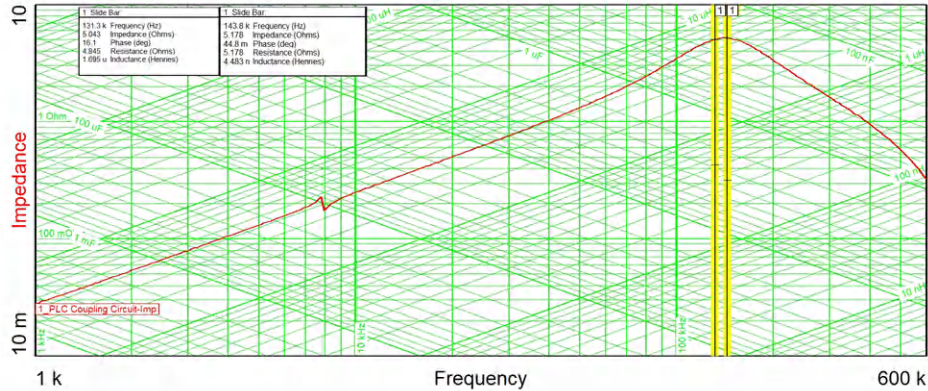


Figure 4-12. Impedance Coupling Circuit

An additional band-pass filter is implemented in the receive path. In this path it is important that the pass band is set to the carrier frequencies of the PLC communication. Figure 4-13 shows the measured transfer curve of the bandpass filter. The pass band is located between 70kHz and 150kHz. The same frequency response analyzer was used for this measurement.

 


Figure 4-13. Transfer Curve Band-Pass Filter Receive Path

This design verified the PLC coupling circuit and AFE031 with rapid shutdown function in combination with the TIDA-060001 reference design. See also [SunSpec Rapid Shutdown Transmit and Receive Reference Design](#).

5 Design and Documentation Support

5.1 Design Files

To download the design files, see the design files at [TIDA-010949](#).

5.1.1 Schematics

To download the schematics, see the design files at [TIDA-010949](#).

5.1.2 BOM

To download the bill of materials (BOM), see the design files at [TIDA-010949](#).

5.2 Tools and Software

Tools

[TMDSCNCD2800137](#) TMS320F2800137 evaluation module C2000™ MCU controlCARD™

Software

[Code Composer Studio™](#) Integrated development environment (IDE)
[C2000WARE-DIGITALPOWER-SDK](#) DigitalPower software development kit (SDK) for C2000™ MCUs

5.3 Documentation Support

1. Texas Instruments, [Understanding Buck Power Stages in Switchmode Power Supplies Application Note](#)
2. Texas Instruments, [400-W GaN-Based MPPT Charge Controller and Power Optimizer Reference Design Guide](#)

5.4 Support Resources

[TI E2E™ support forums](#) are an engineer's go-to source for fast, verified answers and design help — straight from the experts. Search existing answers or ask your own question to get the quick design help you need.

Linked content is provided "AS IS" by the respective contributors. They do not constitute TI specifications and do not necessarily reflect TI's views; see TI's [Terms of Use](#).

5.5 Trademarks

C2000™, E2E™, SimpleLink™, and TI E2E™ are trademarks of Texas Instruments.

Wi-SUN® is a registered trademark of Wi-SUN Alliance.

Zigbee® is a registered trademark of ZigBee Alliance.

Bluetooth® is a registered trademark of Bluetooth SIG, Inc.

Wi-Fi® is a registered trademark of Wi-Fi Alliance.

mioty® is a registered trademark of Fraunhofer-Gesellschaft zur Förderung der angewandten Forschung e.V.

Arm® and Cortex® are registered trademarks of Arm Limited.

SunSpec® is a registered trademark of SunSpec Alliance, Inc.

USB Type-C® is a registered trademark of USB Implementers Forum.

All trademarks are the property of their respective owners.

6 About the Author

BOWEN LING is a system engineer at Texas Instruments, where he is working in the area of Solar Energy within the Energy Infrastructure team.

ANDREAS LECHNER is a Systems Engineer for Energy Infrastructure working in Texas Instruments. Andreas supports customers within the Energy Infrastructure sector worldwide. Andreas earned his master's degree from the University of Applied Sciences in Landshut, Germany.

VSEVOLOD ELANTSEV is a Systems Engineer for Energy Infrastructure at Texas Instruments Germany. Vsevolod focuses on power conversion systems. Vsevolod graduated from the South Russian State Technical University, Novocherkassk, Russia, in 2011.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated