

Power Supply Design Seminar

(Demo Hall Presentation)

Designing Low-EMI Power Converters for Industrial & Automotive Systems

TI Literature Number: **SLUP362**

© 2016, 2017 Texas Instruments Incorporated

Power Seminar topics and online power training modules are available at: ti.com/psds



Designing Low-EMI Power Converters for Industrial & Automotive Systems

Perry Tsao, David Baba & JP Fung
SVA Systems/Apps Managers

Agenda

- Key features of Wide Input Voltage (Wide VIN) Automotive and Industrial DC/DC Converters
- Techniques for reducing emissions in Switching Power Supplies
- EMI Mitigation by proper PCB Layout
- Spread Spectrum
- Slew Rate Control
- Input EMI filter design
- WEBENCH EMI tool

Wide Vin DC-DC Leadership



Synchronous Switchers

- Synchronous regulators - up to 40V operation
- 2.2MHz switching frequency options
- Very Low (μA) no-load quiescent current
- LM536xx 0.65A to 3.5A 2.1MHz
- Coming Soon: LMR23610/25/30 1A, 2.5A, 3A




Specialty Buck Regulators

- Synchronous regulators, up to 100V operation
- Fly-Buck support: smallest multi-output bias supplies
- LM5160A and LM5161 65V and 100V Sync Buck / Fly-Buck
- Coming soon: LM5165/6 Ultra-low Sync Buck
 - 65V, 150mA/500mA versions w/ $10\mu\text{A}$ standby I_q



Wide Vin Buck Regulator Power Modules

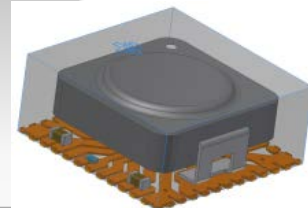- Integrated inductor modules with input range to 60V
- Proven EMI performance
- LMZ34202 and LMZ36002 4.5V to 42V or 60V at 2A



Wide Vin DC-DC Leadership




Buck-Boost, Boost Controllers

- Synch & non-synch buck-boost controllers up to 75Vin & 200W
- Stackable, multi-phase synchronous boost controllers
- LM5175-Q1 USB PD (Type C) reference designs in progress
- Coming soon: LM5170 - the first 48<->12 bidirectional controller




Buck Controllers

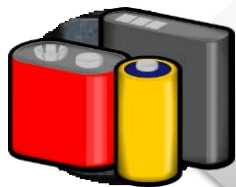- The only 100V buck controller in the TI portfolio
- Emulated Current Mode simplifies high step-down & high current
- LM5140/1 Dual/single 2.2MHz buck controllers - 3.8-65Vin, 2.2MHz, 30 μ A Iq, phase interleaved, EMI reduction




Smart Diode Controllers

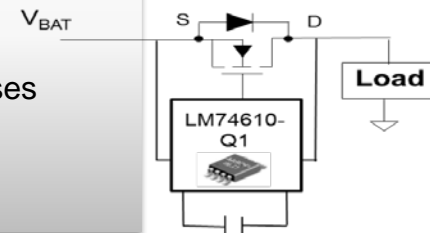- Replaces reverse voltage protection diode with NFET to reduce losses
- Ideal diode for wired OR' applications with multiple power sources
- No ground connection required – zero quiescent current
- LM74610 / LM74670



EMI in Switch Mode Power Supplies

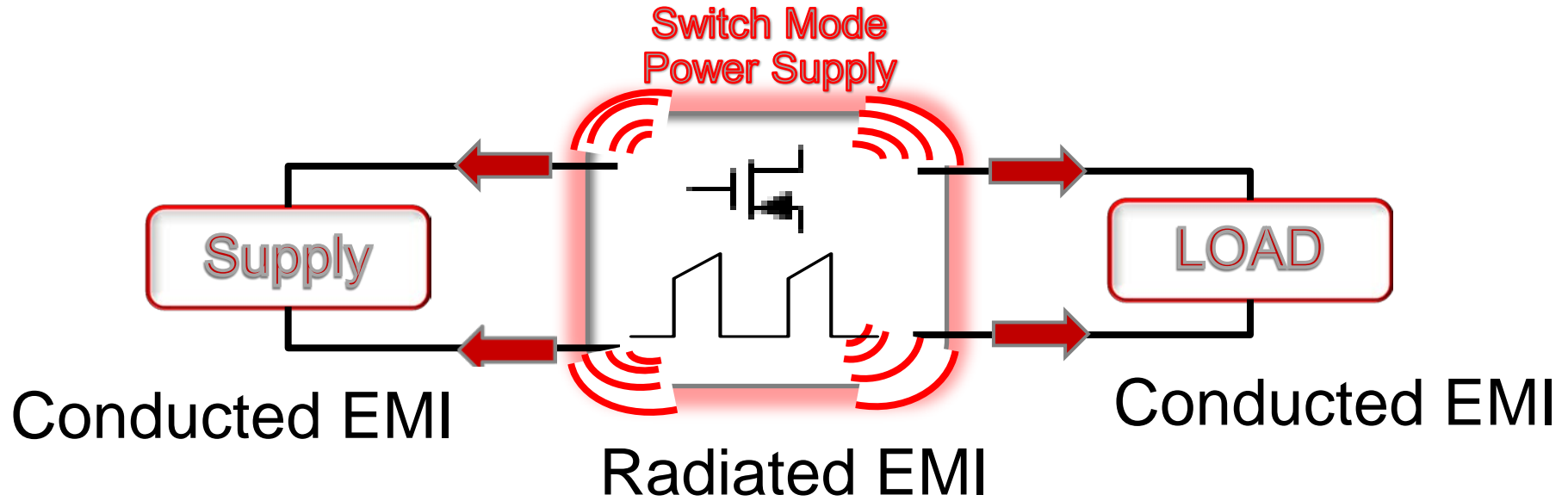

GOAL:



**EMI Noise
Generation**



**EMC Noise
Compatibility**



Engineering Approach To Mitigate EMI

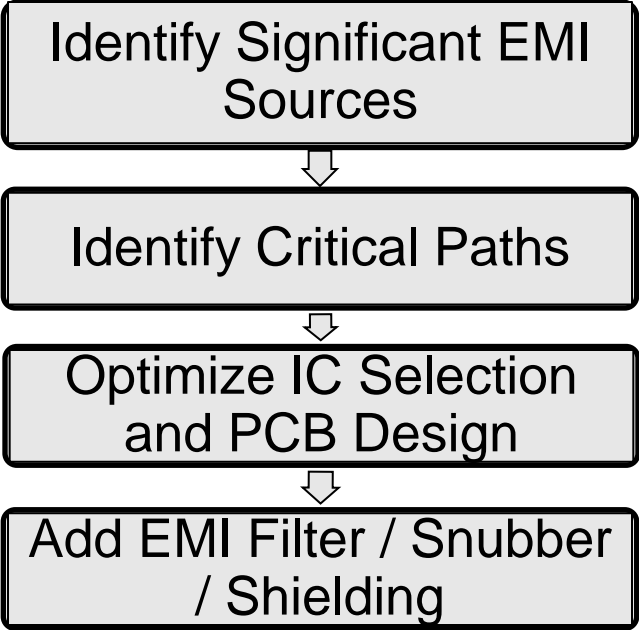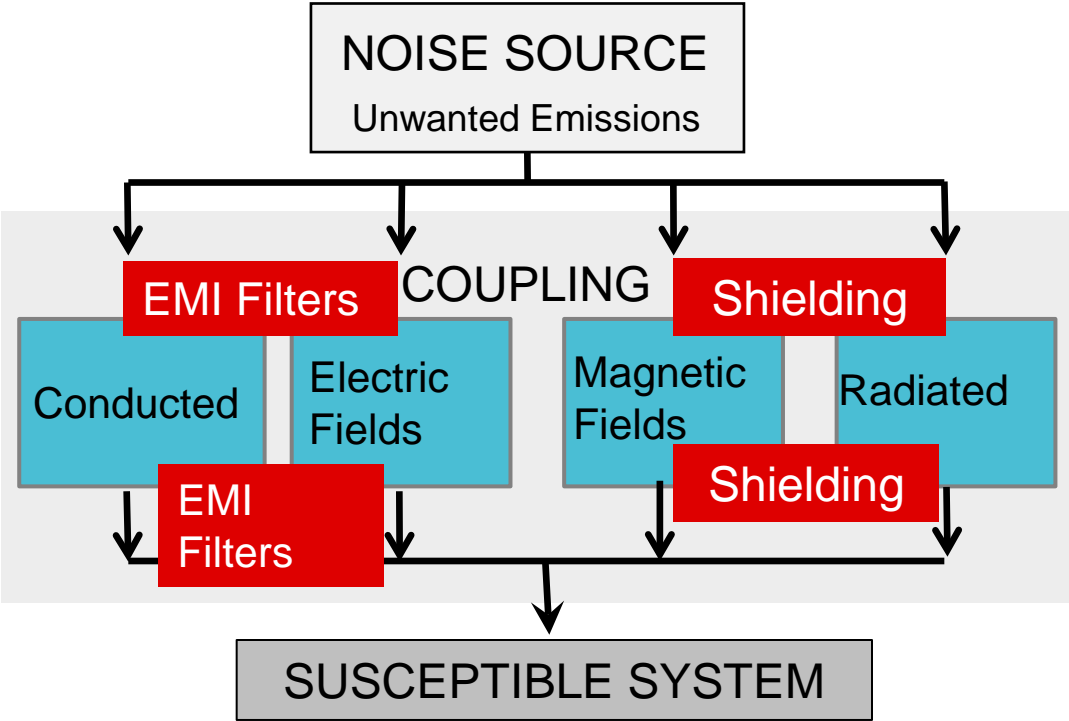


Steps To Mitigate EMI In PCB Design

Identify the high di/dt nodes and paths




Reduce high di/dt loop area
(inductance)



Protect sensitive circuits from
noise

What Can We Do In PCB Layout?

Buck Converter

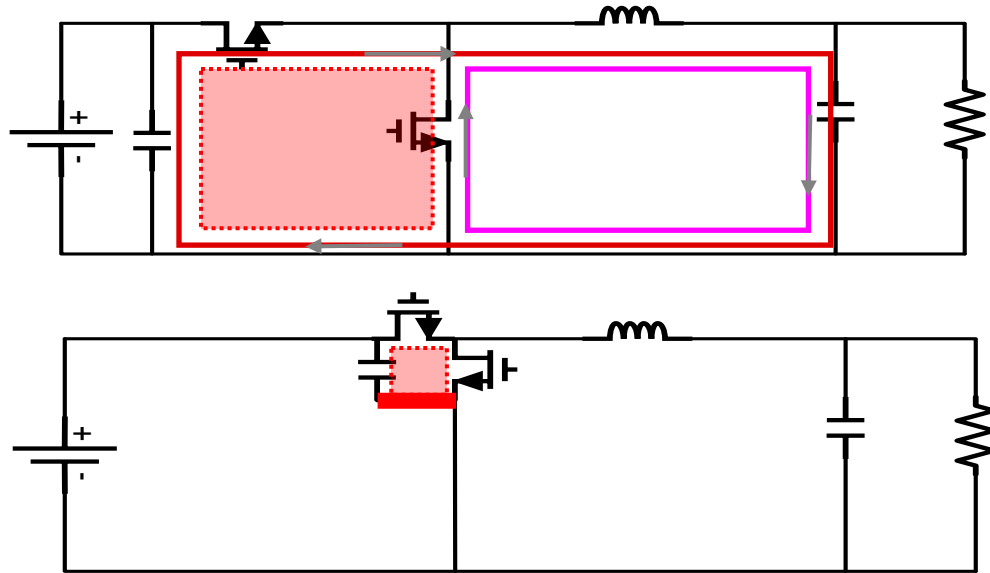

- Minimize critical path area
- Separate noisy ground path from quiet ground



Critical Path Area Comparison

Critical Path Area Reduction


Grounding

High di/dt Caps

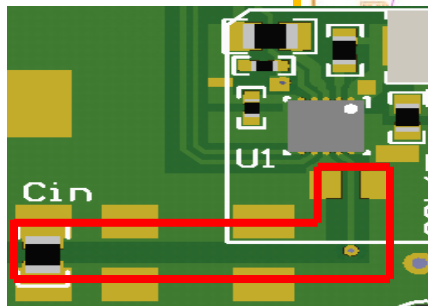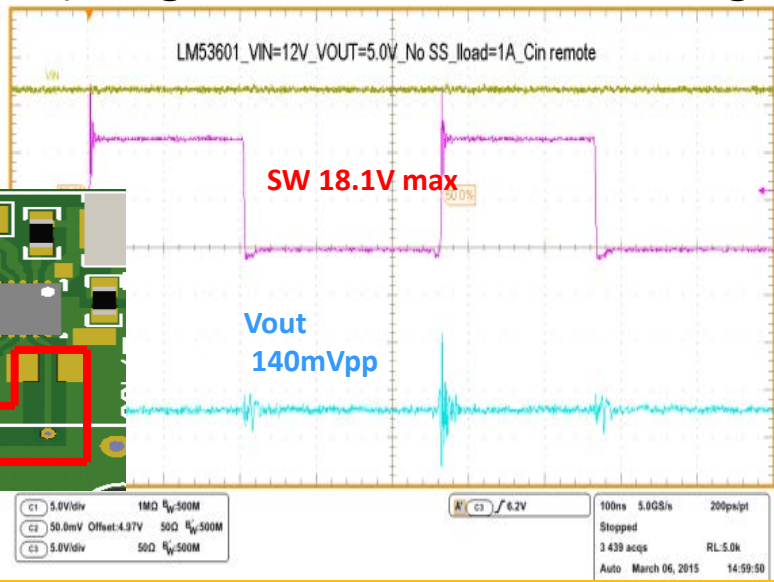- Buck Regulator comparison with Cin location (single Cin, ~3 times larger area)



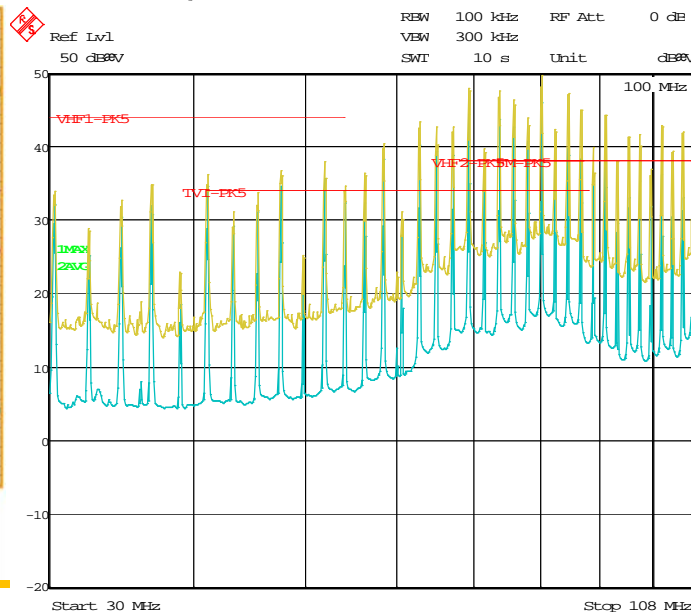Yellow trace is Peak measurement and Blue trace is Average.





Critical Path Area Comparison

Critical Path Area Reduction

Grounding

High di/dt Caps

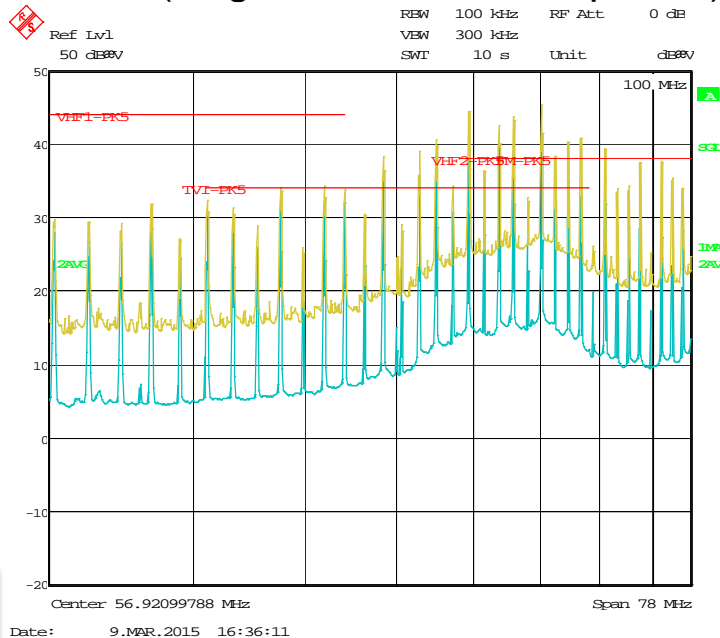
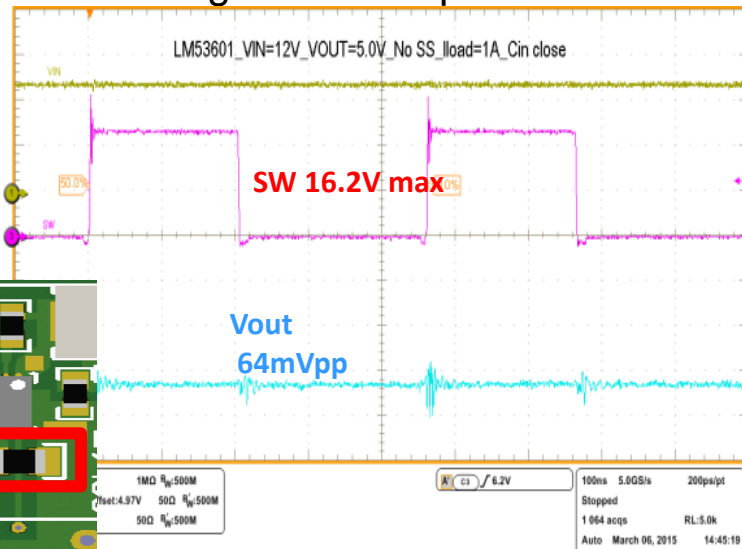
- Buck Regulator Comparison with Cin location (single Cin, smaller loop area)





Comparison	SW max (V)	Vout p2p (mV)	EMI peak (dBμV)
Smaller Area	16.2	64	45
Larger Area	18.1	140	50

PINOUT Designed With Performance In Mind

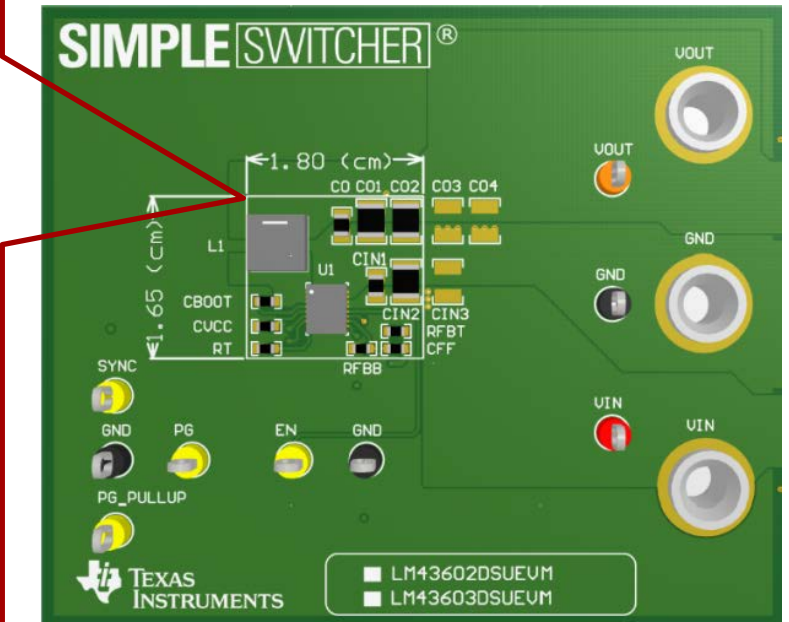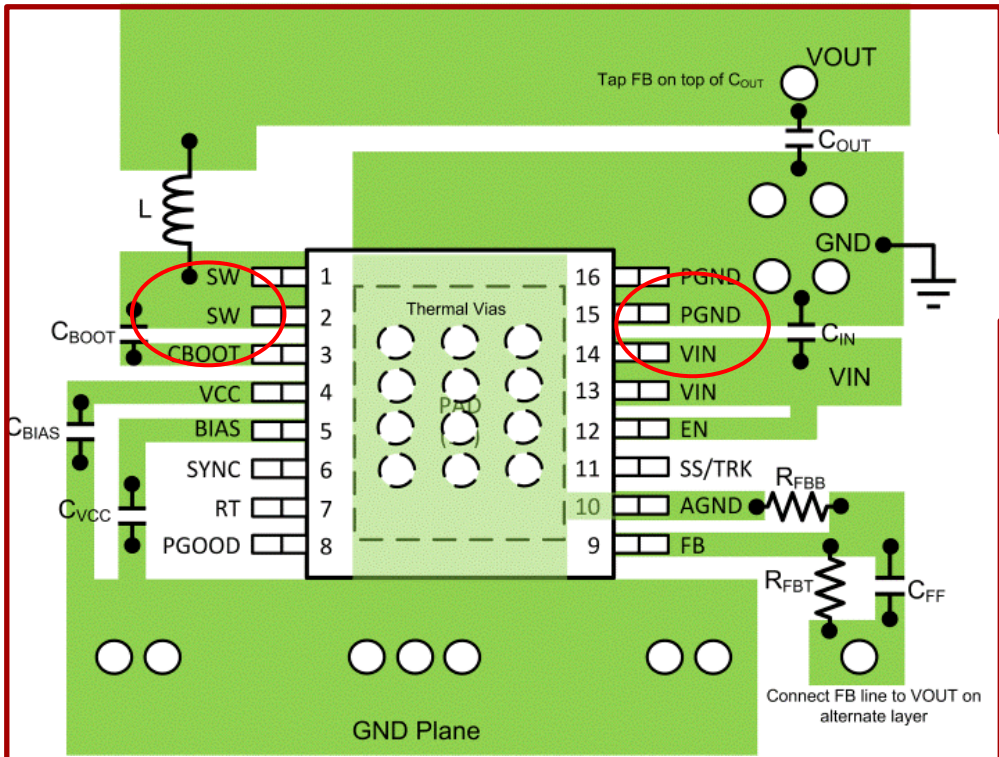Compact, Low EMI, Good Thermal Performance for Industrial applications




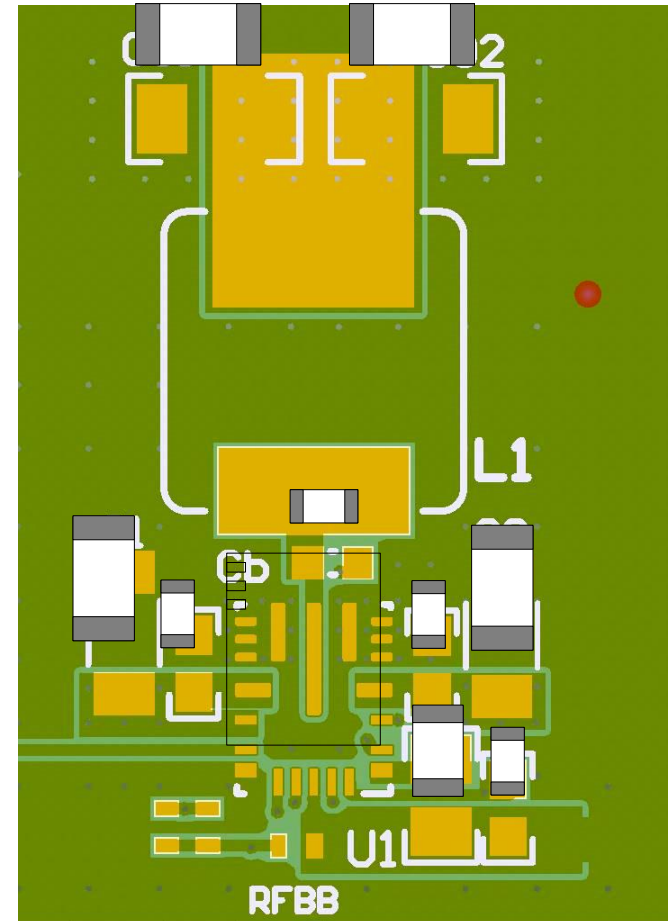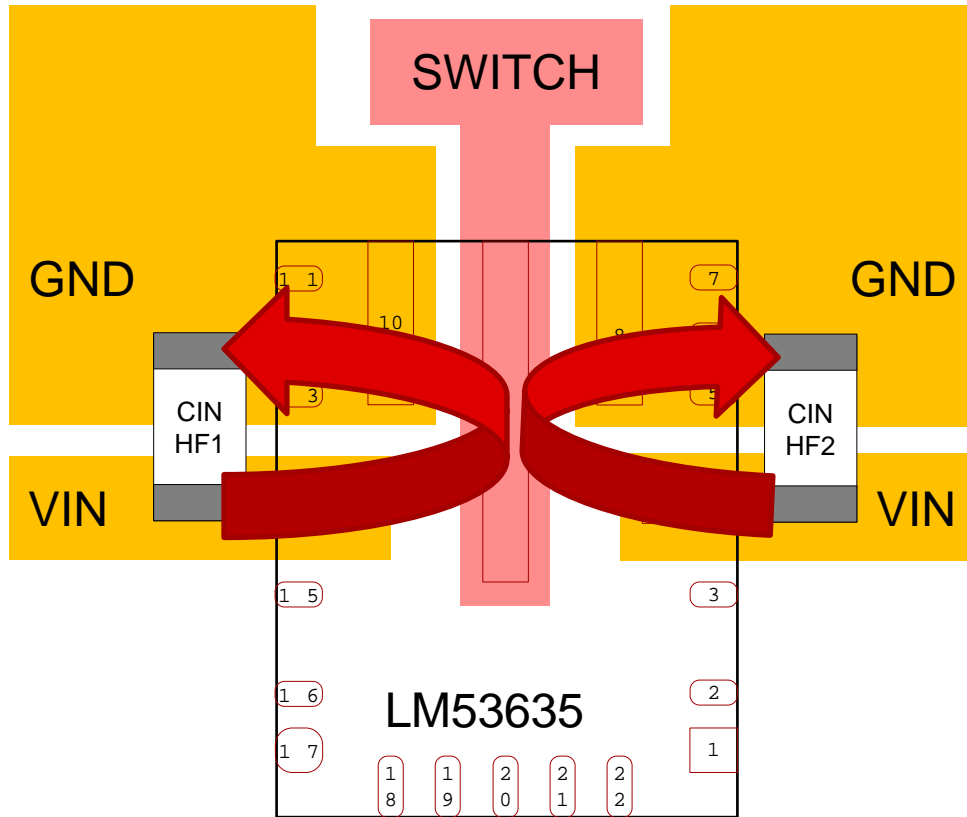Parallel input cap placement for Automotive Applications



PCB Layout Tips...for High Current Buck Converter Applications

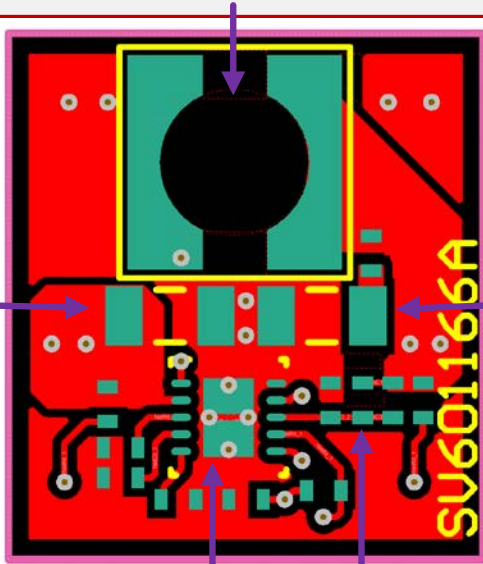Remove copper between inductor pads to reduce parasitic capacitance




Keep Input Cap close to LM5165

Output Cap

μ Power Converter IC

Position Feedback Resistors close to FB & GND pins

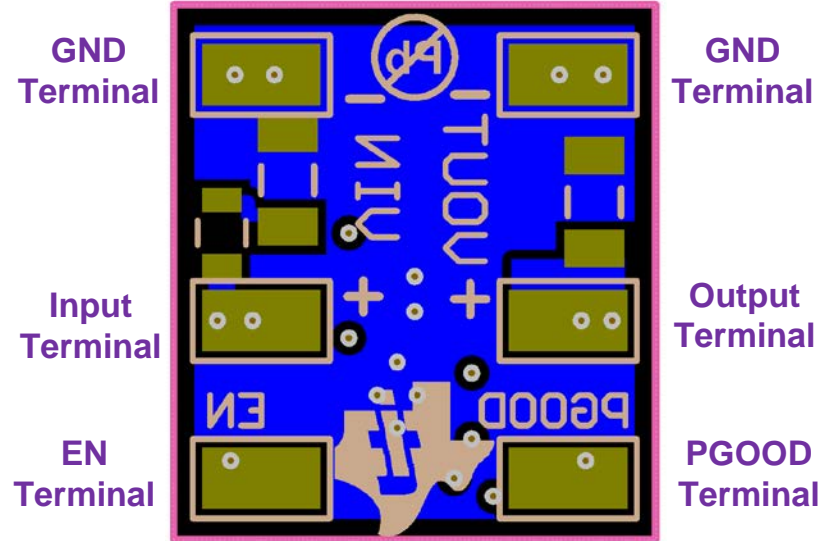Full layer ground plane under converter top side layout provides H-field cancellation




EMI Mitigation by PCB Layout


Critical Path Loop Reduction

Grounding

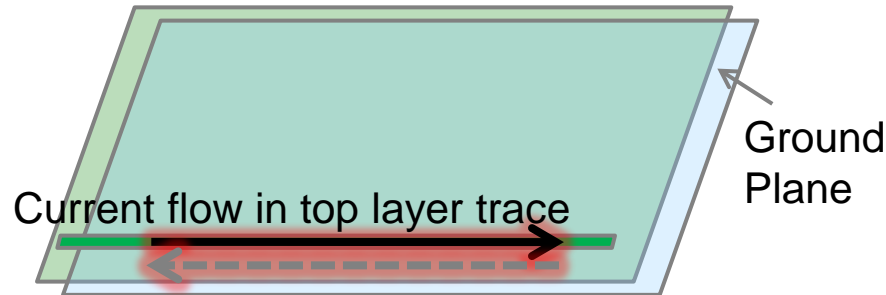- Ground Plane
 - Return Current Takes The Least IMPEDANCE Path
 - Unbroken Ground Plane Provides Shortest Return Path – Image current return path



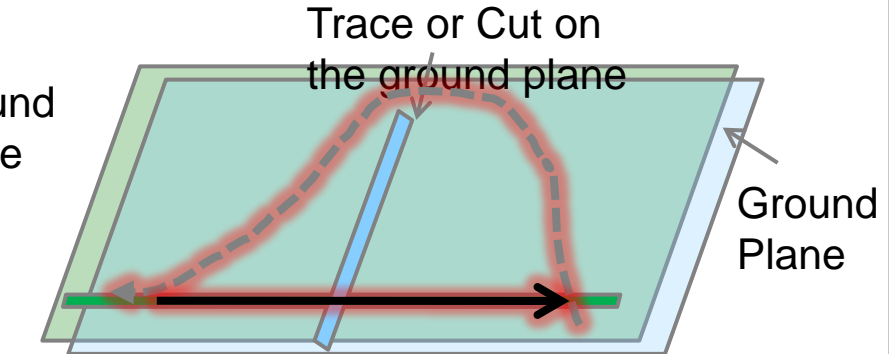
Return current path in unbroken ground plane directly under path
Area minimized, B field minimized



Return current path enclose much larger area if the direct path is blocked

What makes a low EMI Buck

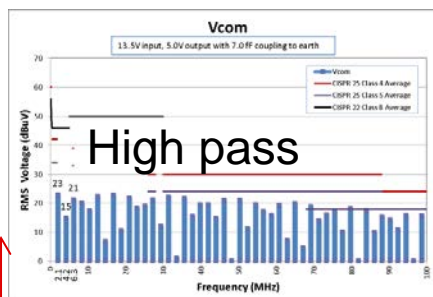SW node capacitive coupling to the environment





Return path of coupling is over Input wires
-> Now it's source of the Common Mode Noise

$$C = 7fF$$

SW dV/dt
Near E-Field coupling



DC Source

Input cable

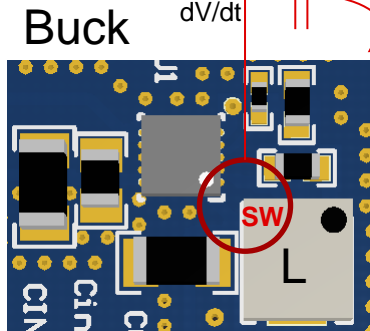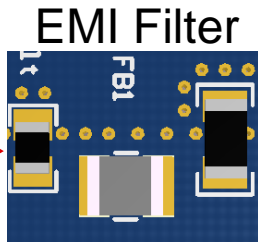

Output cable

Load

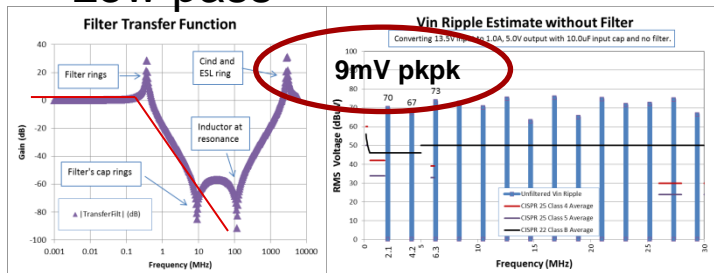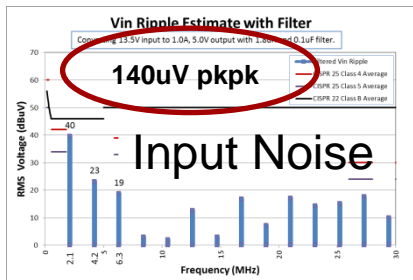


Output Noise

Examples:
1mV pkpk on PCB trace


140uV pkpk with unshielded Cable similar to CISPR

-12dB/Oct -40dB/Dec

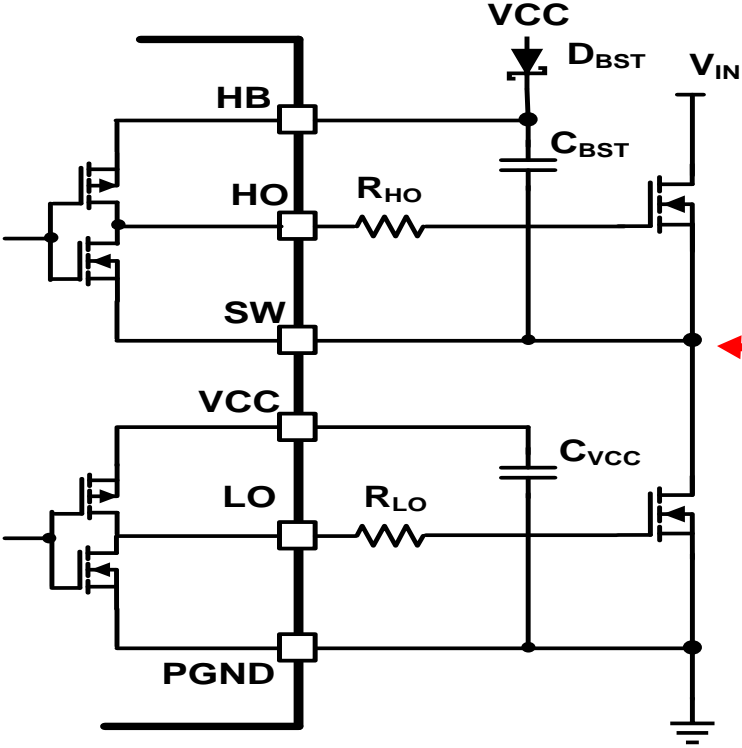Buck Switch Node Voltage Ringing Due to Circuit Parasitics




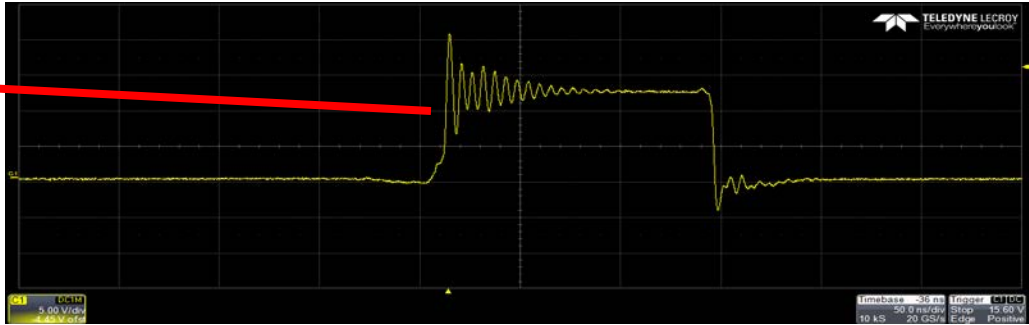Switch node ringing generates EMI in the FM Band > 30 MHz




FET Package and PBC Parasitics

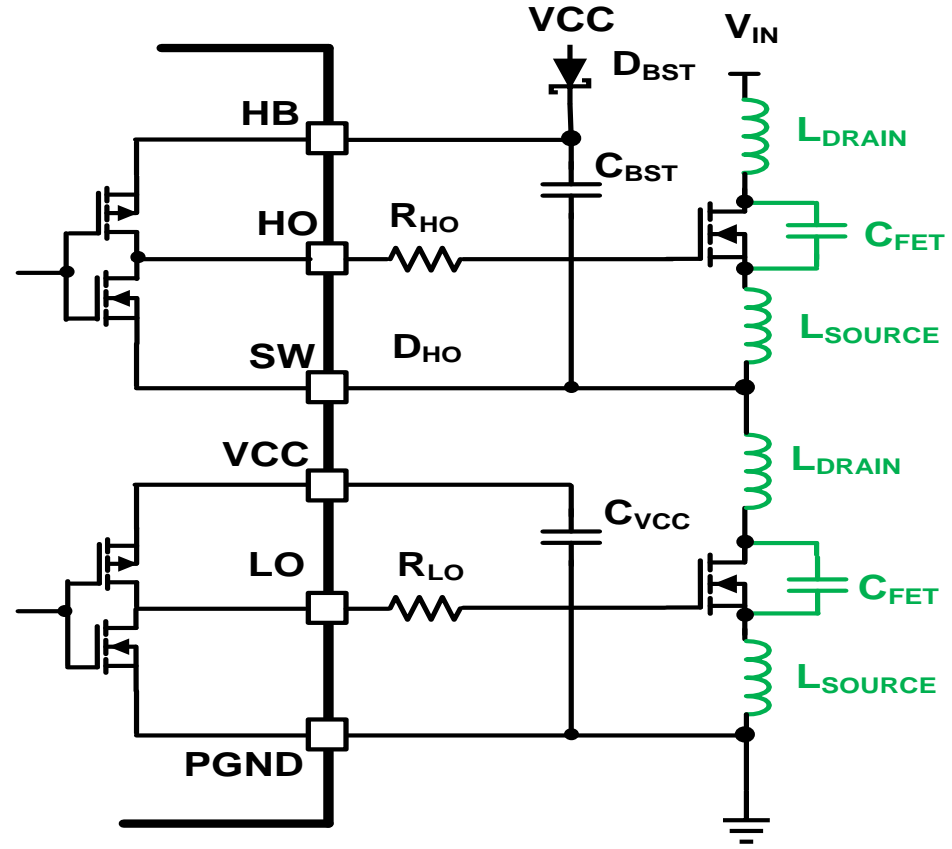
- MOSFET package inductance, and capacitance
- PCB inductance and capacitance



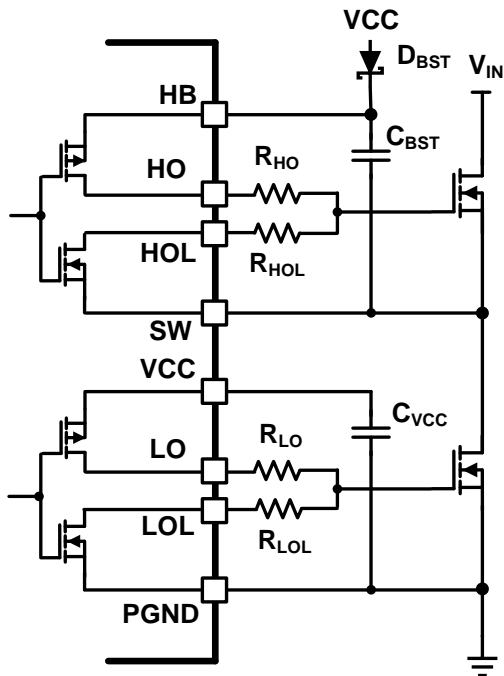Buck Switch Node Waveform with Slew Rate Control No Snubber



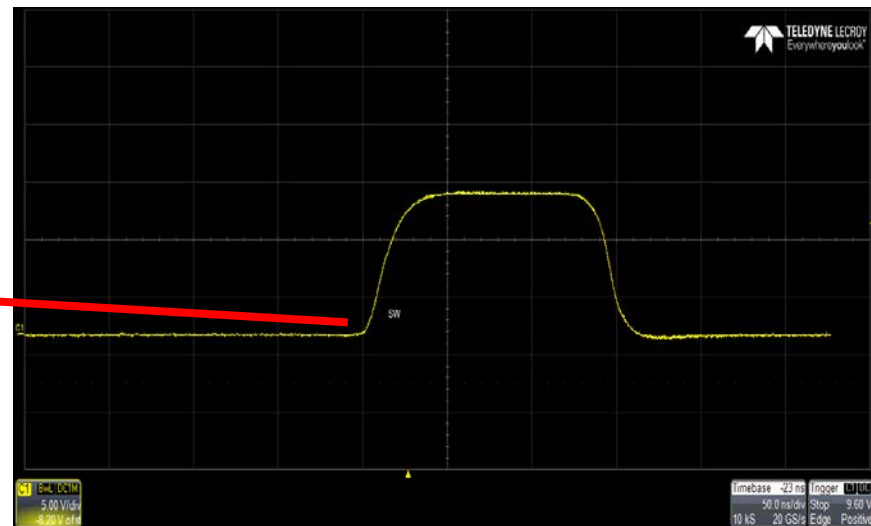
Using slew rate control the switch node ringing is eliminated




$R_{HOH}=10$ ohms
 $R_{HOL}=0$ ohms
 $L_{LOH}=10$ ohms
 $R_{LOL}=10$ ohms

Benefits of LM5140 Gate Driver Slew Rate Control

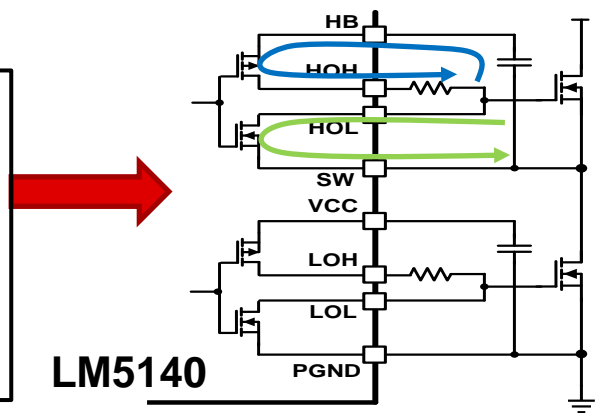
- High and Low Side FET Drivers have separate source and sink pins allowing the turn-on and turn-off times to be independently controlled via series resistors
- Optimizing gate drive slew rate reduces EMI with ~1% reduction in efficiency (as measured on LM5140 EVM)



No Slew Rate Control

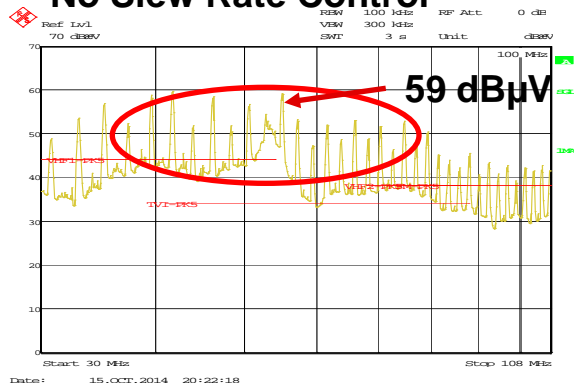


With Slew Rate Control

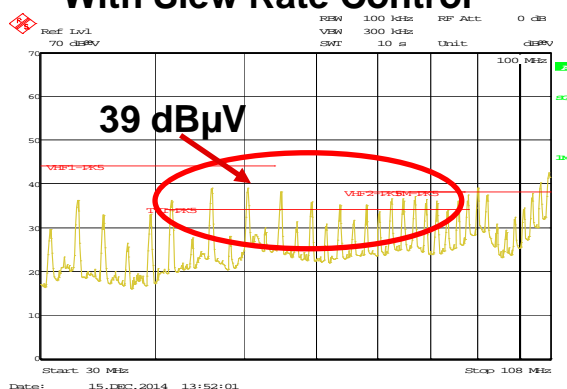

Measured on
LM5140 Standard EVM:
2.2MHz, 3.3V/5.0Vout

Spread spectrum/Dithering – What is it?

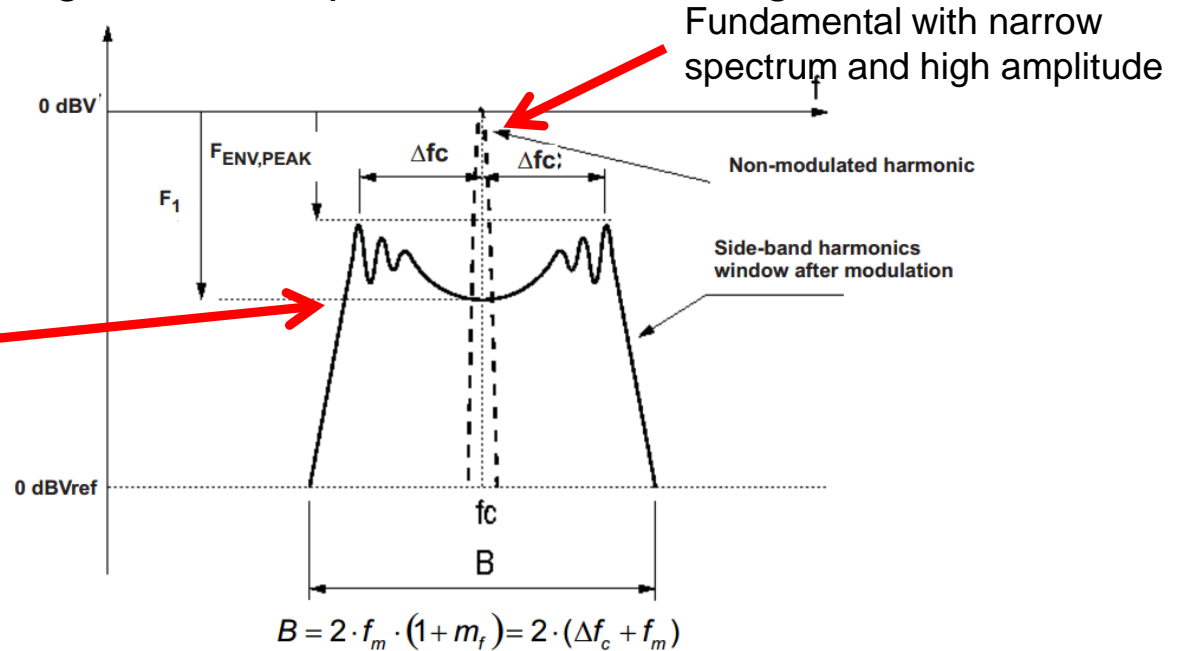
- Spread spectrum is a means of reducing EMI interference by dithering the switching regulator frequency, in the case of LM53600/53601, by +/-4%. This has the effect of widebanding the noise spectrum and reducing the fundamental energy, as shown




Spread spectrum reduces the fundamental signal energy and the overall peak value while widening the spectrum

Combining Slew Rate Control and Spread Spectrum

- Wide Input voltage range: 3.8V to 65V (Abs Max 70V)
- Fixed output 3.3V, 5V, or adjustable from 1.5V-15V
- Fixed 2.2MHz, or 440 kHz oscillator; frequency can be shifted from the fundamental via RT pin resistor setting
 - RT adjustment range 300kHz-500kHz, or 1.8MHz-2.53MHz
- EMC features:
 - Spread Spectrum selectable
 - Gate drive slew rate control
 - Synchronizable to external clock
 - FPWM mode disables skip mode at light load assuring operation at fixed frequency

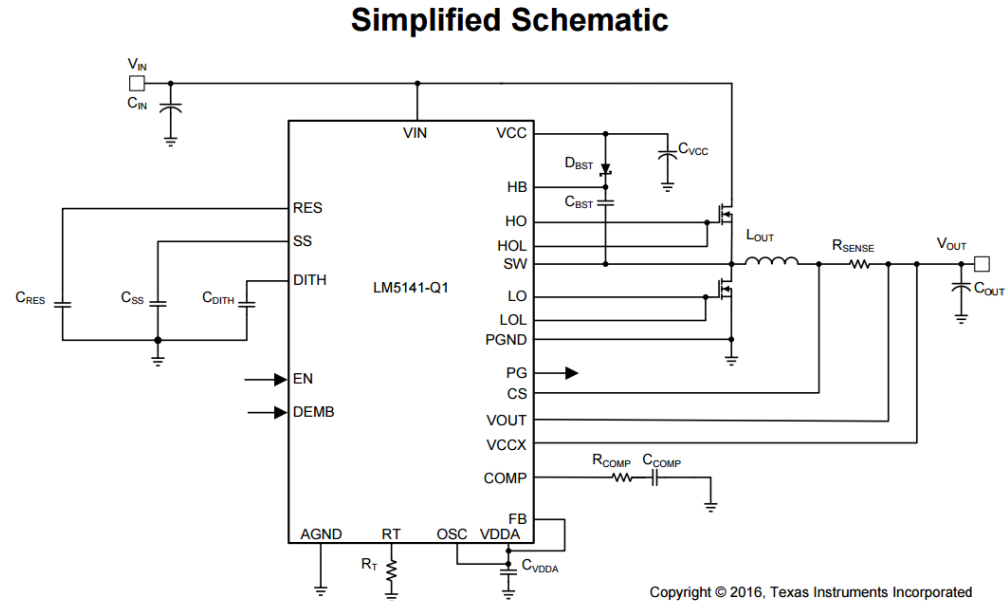

Differential Mode Conducted EMI

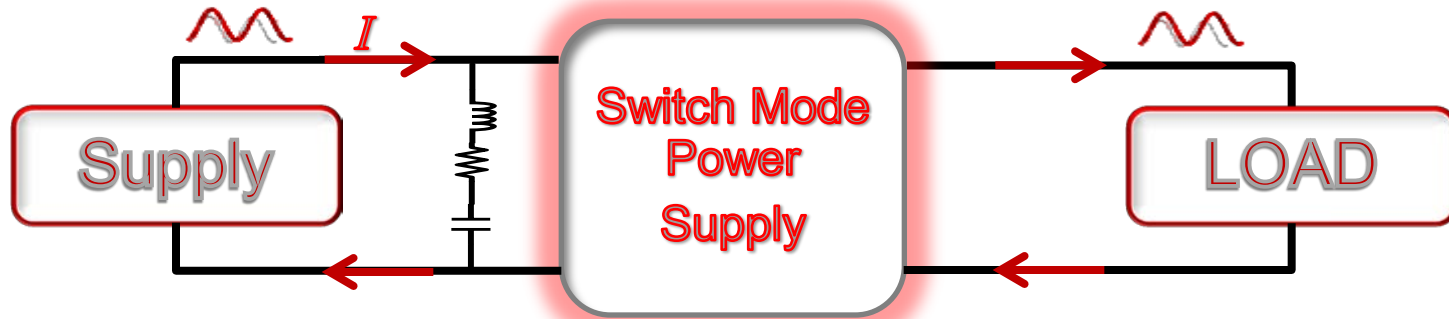

- Differential Mode Conducted EMI
 - In DC-DC converter topology differential mode noise usually dominates common mode
 - Involves the Normal Operation of the Circuit
 - Only Related to CURRENT, not voltage
 - For example, with the same power level Buck converter, lower input voltage means higher input current, thus worse conducted EMI
- Why we care?
 - Excessive Input and/or Output Voltage Ripple can compromise operation of Supply and/or Load

Input Filter Design for Conducted EMI

There are two basic requirements for the conducted EMI filter:


- Meet noise attenuation requirement (i.e. CISPR 25)
- Not interfere with the normal operation of the SMPS converter

Conducted EMI plot LM53603 without Input Filter

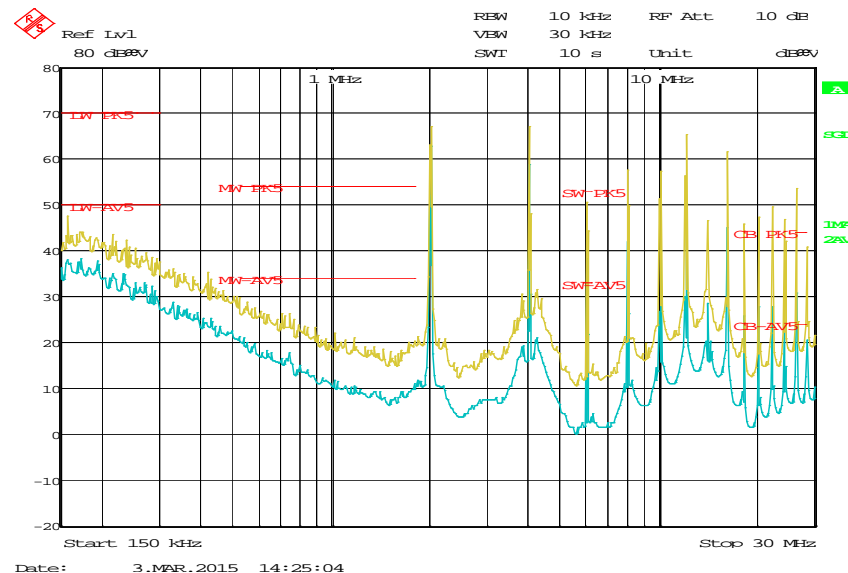Example of a Buck regulator

- No input filter
- Fails CISPR 25 regulation limits

But how do we estimate how much filter attenuation to add?



Necessary Input Filter Attenuation

Methods of estimating the filter attenuation prior to making a certified measurement with a LISN (Line Impedance Stabilization Network) and Spectrum Analyzer

- **Method 1 – estimation using oscilloscope measurement**

- Measure the input ripple voltage using a wide bandwidth scope and calculate the attenuation.

$$|Att|_{dB} = 20 \times \log\left(\frac{V_{inRipple\ pk-pk}}{1\mu V}\right) - V_{MAX}$$


- V_{MAX} is the allowed dB μ V noise level for the particular EMI standard.

- **Method 2 – Estimation using the first harmonic of input current**


- Assume the input current is a square wave (small ripple approximation)

$$|Att|_{dB} = 20 \log\left(\frac{\frac{I}{\pi^2 f_s C_{IN}} \sin(\pi D)}{1\mu V}\right) - V_{max}$$

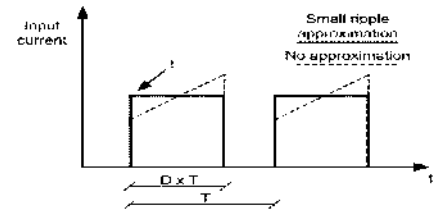- V_{MAX} is the allowed dB μ V noise level for the particular EMI standard.
- C_{IN} is the existing input capacitor of the Buck converter.
- D is the duty cycle , I is the output current, F_s is the switching frequency



Typical Conducted EMI Filter

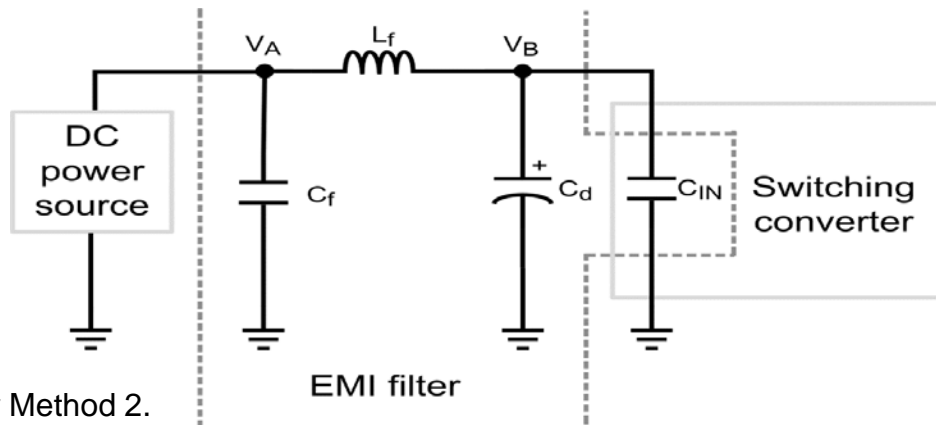

Follow the design steps described in AN-2162.

- Calculate the required attenuation using Method 1 or Method 2.
- Capacitor **CIN** represents the existing capacitor at the input of the switching converter.
- Inductor **Lf** is usually between 1 μ H and 10 μ H, but can be smaller to reduce losses if this is a high current design.
- Calculate capacitor **Cf**. Use the larger of the two values (Cfa and Cfb) below:

$$C_{fa} = \frac{C_{IN}}{C_{IN}L_f(2\pi f_s/10)^2 - 1}$$

$$C_{fb} = \frac{1}{L_f} \left(\frac{10^{|\text{Att}|_{dB}/40}}{2\pi f_s} \right)^2$$

- Capacitor **Cd** and its ESR provides damping so that the Lf Cf filter does not affect the stability of the switching converter.

$$C_d \geq 4 \times C_{IN} \quad \text{ESR}_d \approx \sqrt{L_f / C_{IN}}$$


Conducted EMI Before and After Filter – LM53603 – 150kHz to 30MHz

Input 13V, Output 5V@3A, resistor load, CISPR 25 CE setup


Red Line: Class 5 Limits (Peak/Average Detection)

Yellow: Peak detection result, Blue: Average detection result

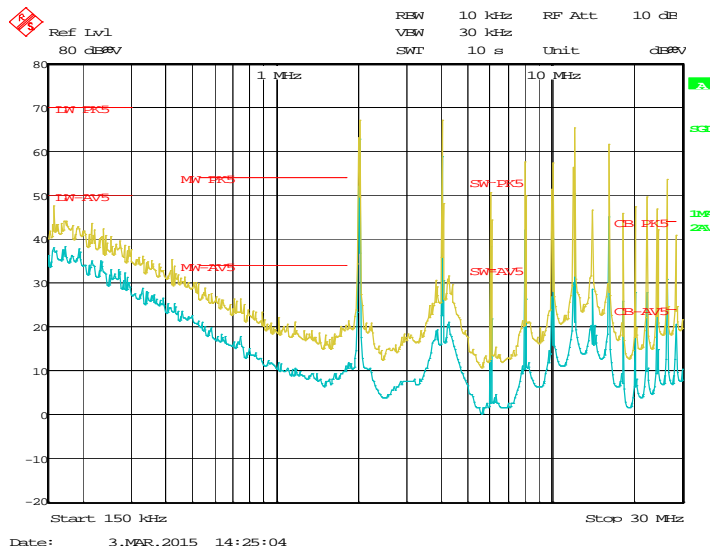Using guidelines on the previous slides the filter was implemented and Conducted EMI retaken




No Input Filter

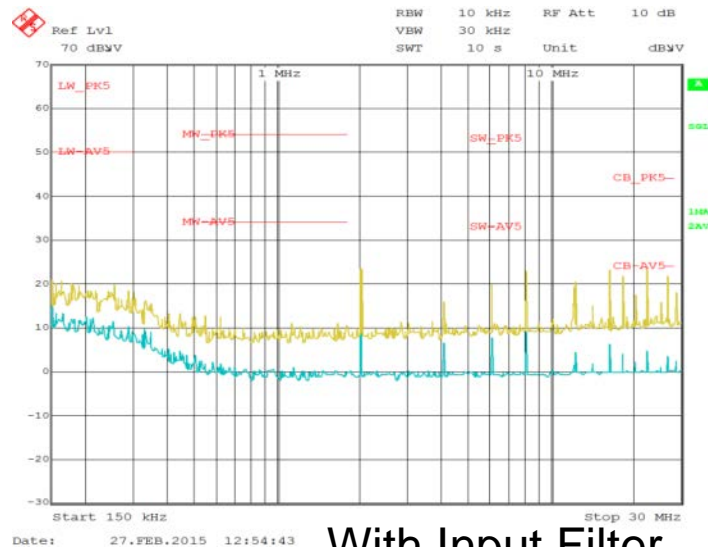

With Input Filter


COT Converter with EMI Input Filter

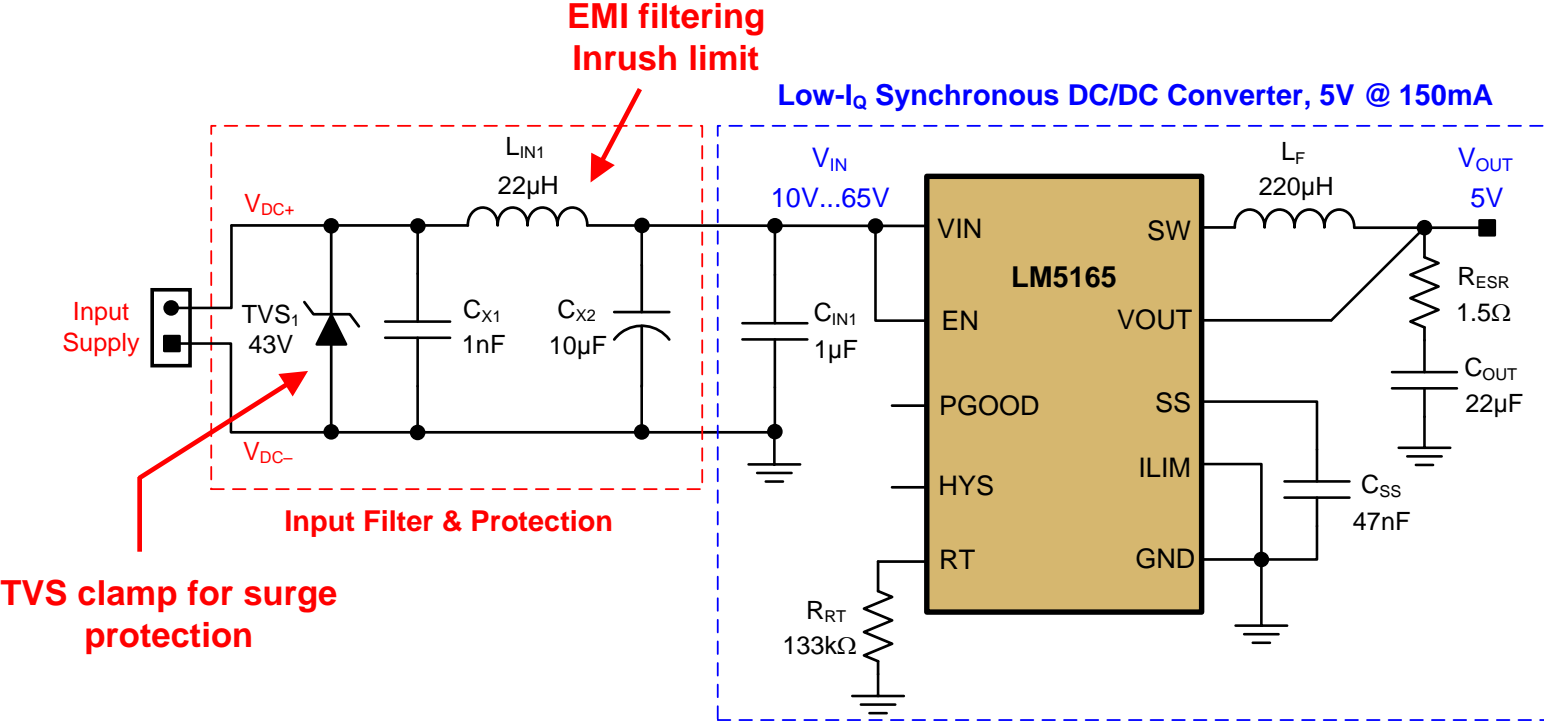Low- I_Q Synchronous DC/DC Converter, 5V @ 150mA




Conducted EMI Plots: CISPR 22 Class B (150kHz → 30MHz)

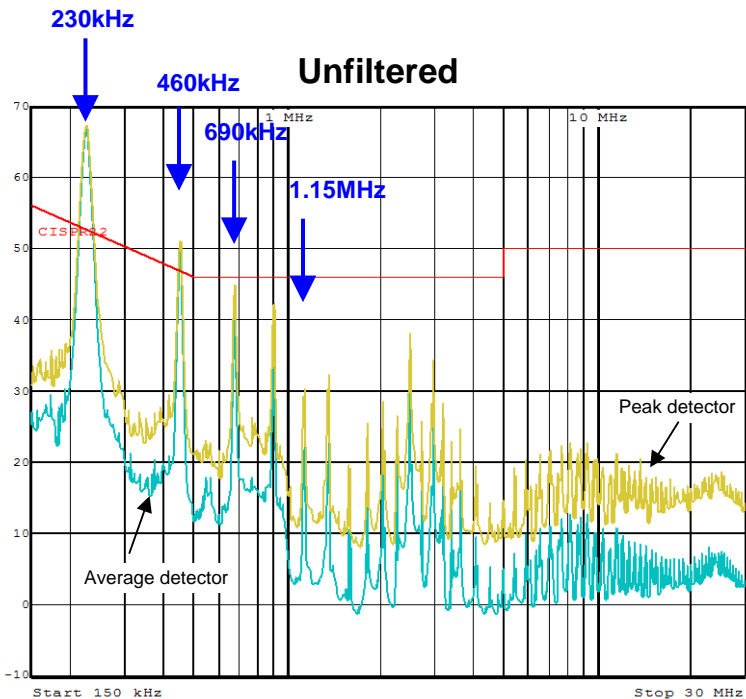Input 13.5V, Output 5V @ 100mA, COT mode, Resistive load, CISPR 22 CE setup




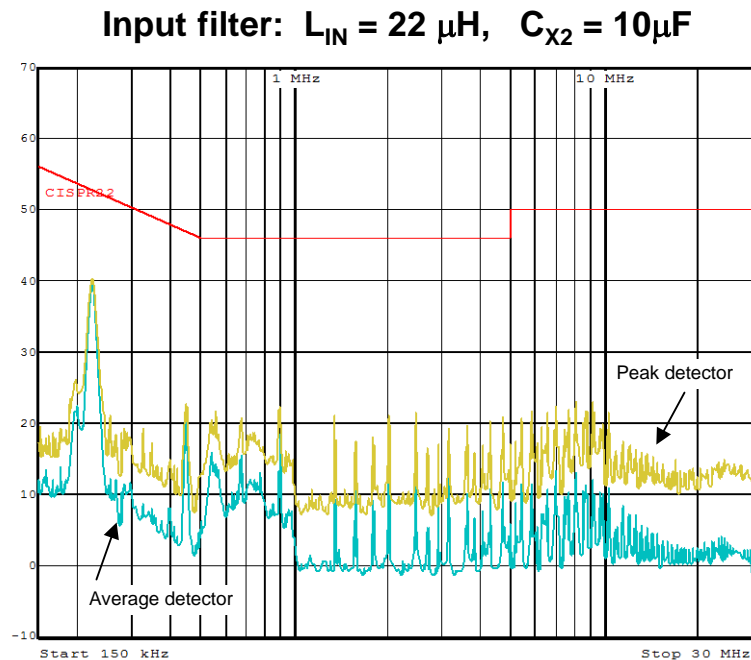Red Lines Class B Limits
(Peak & Average detection)



Yellow
Blue Peak detection result
Average detection result

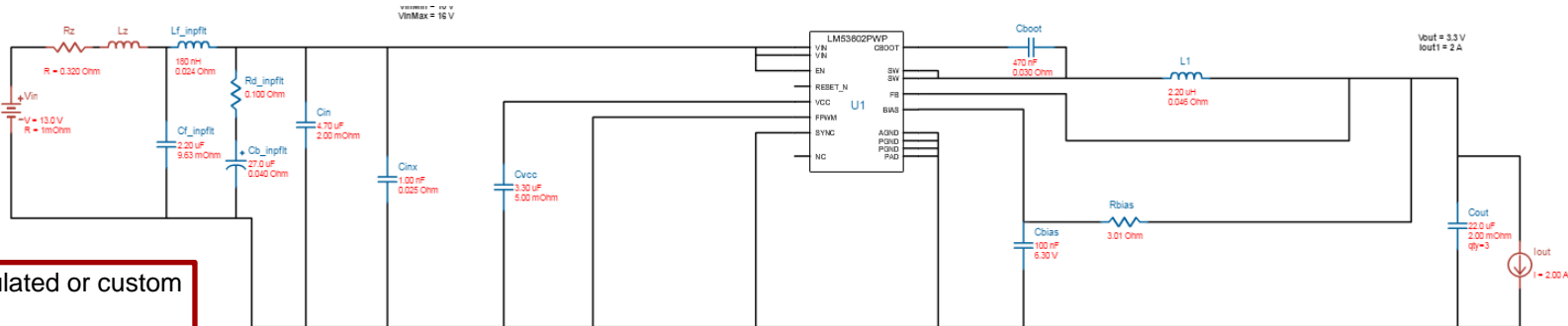Conducted EMI Filter Design Tool- Webench



Auto calculated or custom Input filter

Noise Specification

Noise Standard: CISPR 25
Noise Class: CLASS 5

Source Resistance: 1m Ohm
Load Impedance: 320.34m Ohm

Support & More

Edit filter components manually


Parameter Name	Calculated
Lf_inpfilt (H)	180n
Cf_inpfilt (F)	2.200u
Cb_inpfilt (F)	27u
Rd_inpfilt (Ohm)	100m

Apply modifications to design


History for Design #449: LMS302PWP_CSDOT_1.0.0V_10.0K_30-4.00V_2.0A

ID	Standard	Class	Noise Before (dBuV)	Noise After (dBuV)	Mode	Load
✓ D0	CISPR 25	CLASS 5	82.170	45.870	Auto	Load

EMI limits

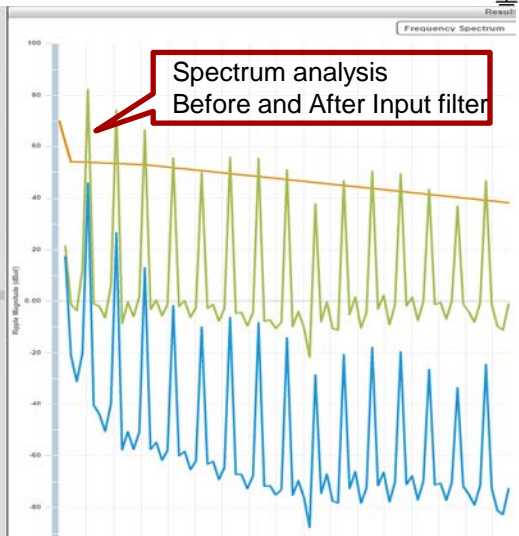

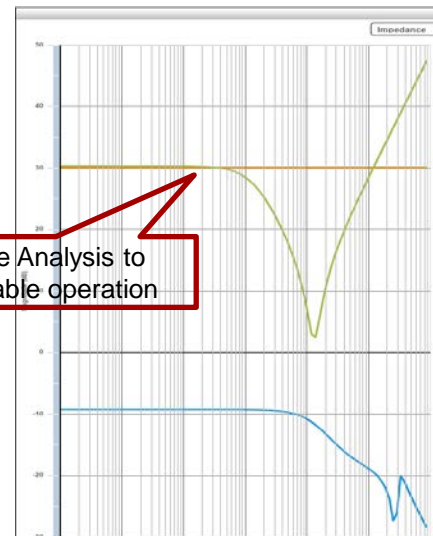Impedance Analysis to Ensure stable operation



TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(512) 434-1560
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	Toll-Free Number

Note: Toll-free numbers do not support mobile and IP phones.

Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010

International	+86-21-23073444
Fax	+8621-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

B021014

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com