

Low-Power Sensor Measurements: 3.3V, 1kSPS, 12-Bit, Single-Ended, Single-Supply Circuit



Reed Kaczmarek


Input	ADC Input	Digital Output ADS7042
VinMin = 0V	AIN_P = 0V, AIN_M = 0V	000 _H or 0 ₁₀
VinMax = 3.3V	AIN_P = 3.3V, AIN_M = 0V	FFF _H or 4096 ₁₀

Power Supplies

AVDD	Vee	Vdd
3.3V	0V	4.5V

Design Description

This design shows an ultra-low power amplifier being used to drive a SAR ADC that consumes only nanoWatts of power during operation. This design is intended for collecting sensor data by providing overall system-level power consumption on the order of single-digit microWatts. [PIR sensors](#), [gas sensors](#), and [glucose monitors](#) are a few examples of possible implementations of this SAR ADC design. The values in the *component selection* section can be adjusted to allow for different data throughput rates and different bandwidth amplifiers. [Low-Power Sensor Measurements: 3.3V, 1ksps, 12-bit Single-Ended, Dual Supply](#) shows a more sophisticated version of this circuit where the negative supply is connected to a small negative voltage (−0.3V). The single-supply version has degraded performance when the amplifier output is near zero volts. However, in most cases the single-supply configuration is preferred for its simplicity.

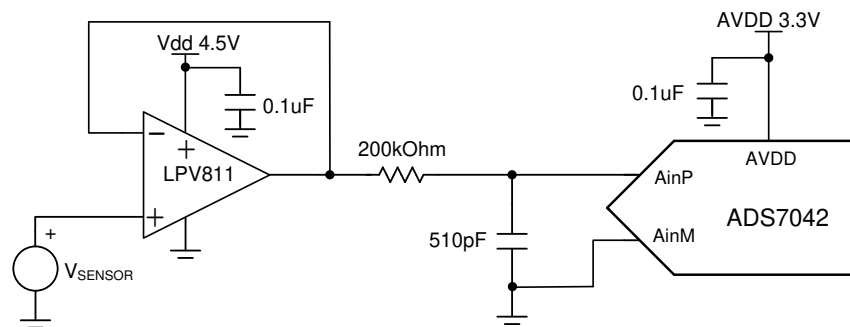

Specifications

Specification	Calculated	Simulated	Measured
Transient ADC Input Settling (1ksps)	< 0.5×LSB = 402μV	41.6μV	N/A
AVDD Supply Current (1ksps)	230nA	N/A	214.8nA
AVDD Supply Power (1ksps)	759nW	N/A	709nW
VDD OPAMP Supply Current	450nA	N/A	431.6nA
VDD OPAMP Supply Power	2.025μW	N/A	1.942μW
AVDD + VDD System Power (1ksps)	2.784μW	N/A	2.651μW

Design Notes

1. Determine the linear range of the op amp based on common mode, output swing, and linear open loop gain specification. This is covered in the *component selection* section.
2. Select COG capacitors to minimize distortion.
3. Use 0.1% 20ppm/°C film resistors or better to minimize distortion.
4. The [TI Precision Labs – ADCs](#) training video series covers methods for selecting the charge bucket circuit Rfilt and Cfilt. These component values are dependent on the amplifier bandwidth, data converter sampling rate, and data converter design. The values shown here give good settling and AC performance for the amplifier and data converter in this example. If you modify this design you need to select a different RC filter. Refer to the [Introduction to SAR ADC Front-End Component Selection](#) training video for an explanation of how to select the RC filter for best settling and AC performance.

Component Selection

1. Select a low-power operational amp:
 - Supply current < 0.5μA
 - Gain bandwidth product > 5kHz (5 times the sampling rate)
 - Unity gain stable
 - For this cookbook, the LPV811 was selected. It has a 450-nA supply current, 8-kHz gain bandwidth product, and is unity gain stable.
2. Find op amp maximum and minimum output for linear operation

$$V_{ee} + 0V < V_{out} < V_{dd} - 0.9V \quad \text{from LPV811 } V_{cm} \text{ specification}$$

$$V_{ee} + 10mV < V_{out} < V_{dd} - 10mV \quad \text{from LPV811 } V_{out} \text{ swing specification}$$

$$V_{ee} + 0.3V < V_{out} < V_{dd} - 0.3V \quad \text{from LPV811 } A_{ol} \text{ linear region specification}$$

$$0.3V < V_{in} < 3.4V \quad \text{Combined worst case}$$

Note

The linear range of the LPV811 is 300mV above ground. This means to design a system to establish a full linear range from 0V to 3.3V (full-scale range (FSR) of ADS7042), then a negative supply is required. This design shows that full-measured SNR and THD specifications of the ADS7042 are met without using a negative supply voltage. This testing was only at room temperature and for a more robust system; [Low-Power Sensor Measurements: 3.3V, 1kSPS, 12-bit Single-Ended, Dual Supply](#) shows this design using a negative supply instead of ground.

3. Typical power calculations (at 1kSPS) with expected values:

$$P_{AVDD} = I_{AVDD_Avg} \times AVDD = 230nA \times 3.3V = 759nW$$

$$P_{LPV811} = I_{LPV811} \times (V_{dd} - V_{ee}) = 450nA \times (4.5V - 0V) = 2.025\mu W$$

$$P_{total} = P_{AVDD} + P_{LPV811} = 759nW + 2.025\mu W = 2.794\mu W$$

4. Typical power calculations (at 1kSPS) with measured values:

$$P_{AVDD} = I_{AVDD_Avg} \times AVDD = 214nA \times 3.3V = 709nW$$


$$P_{LPV811} = I_{LPV811} \times (V_{dd} - V_{ee}) = 431.6nA \times (4.5V - 0V) = 1.942\mu W$$

$$P_{total} = P_{AVDD} + P_{LPV811} = 709nW + 1.942\mu W = 2.651\mu W$$

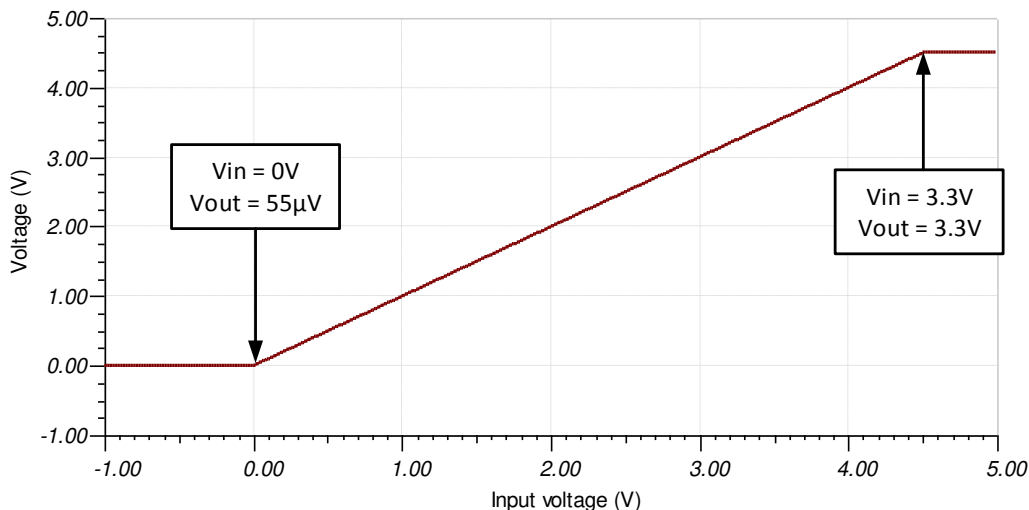5. Find Rfilt and Cfilt to allow for settling at 1kSPS. [Refine the Rfilt and Cfilt Values](#) (a *Precision Labs* video) showing the algorithm for selecting Rfilt and Cfilt. The final value of 200kΩ and 510pF proved to settle to well below ½ of a least significant bit (LSB).

DC Transfer Characteristics


The following graph shows a linear output response for inputs from 0 to 3.3V. The FSR of the ADC falls within the linear range of the op amp.



AC Transfer Characteristics


The bandwidth simulation includes the effects of the amplifier output impedance and the RC charge bucket circuit (R_{filt} and C_{filt}). The bandwidth of the RC circuit is shown in the following equation to be 1.56kHz. The simulated bandwidth of 2kHz includes effects from the output impedance interacting with the impedance of the load. See [TI Video Library - Op Amps: Bandwidth 1](#) for more details on this subject.
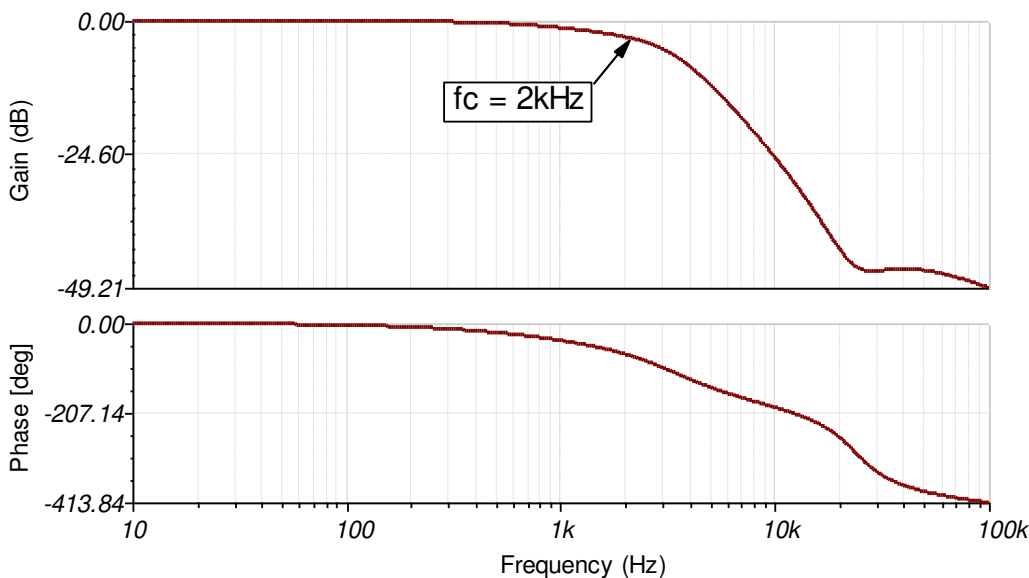
$$f_c = \frac{1}{2 \cdot \pi \cdot R_{filt} \cdot C_{filt}} = \frac{1}{2 \cdot \pi \cdot (200k\Omega) \cdot (510pF)} = 1.56kHz$$



Transient ADC Input Settling Simulation

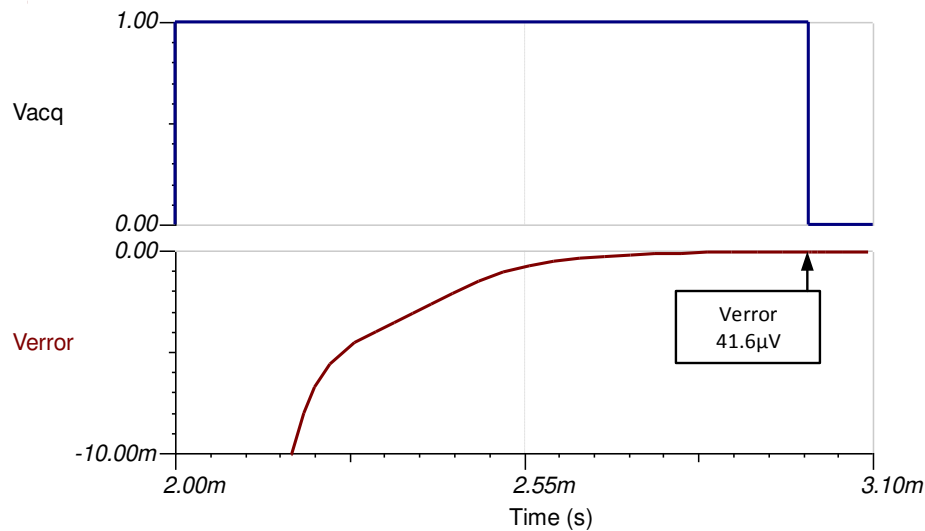The following simulation shows settling to a 3-V DC input signal. This type of simulation shows that the sample and hold kickback circuit is properly selected to within 1/2 of a LSB (402µV). Refer to [Introduction to SAR ADC Front-End Component Selection](#) for detailed theory on this subject.




Noise Simulation

This section details a simplified noise calculation for a rough estimate. We neglect resistor noise in this calculation as it is attenuated for frequencies greater than 10kHz.

$$f_c = \frac{1}{2 \cdot \pi \cdot R_{\text{filt}} \cdot C_{\text{filt}}} = \frac{1}{2 \cdot \pi \cdot (200\text{k}\Omega) \cdot (510\text{pF})} = 1560.3\text{Hz}$$


$$E_n = e_{n811} \times \sqrt{2 \times K_n \times f_c} = (340\text{nV}/\sqrt{\text{Hz}}) \times \sqrt{1.57 \times (1560\text{Hz})} = 16.8\mu\text{V}$$

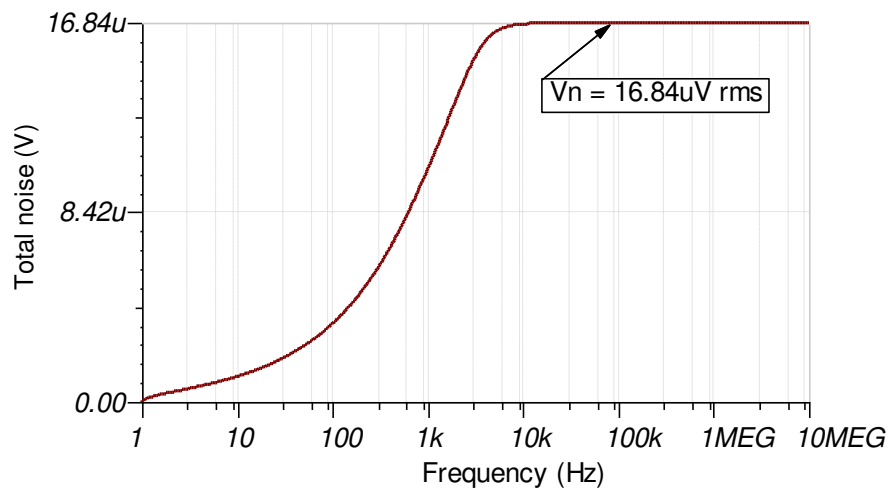Note that calculated and simulated match well. Refer to [Calculating the Total Noise for ADC Systems](#) for detailed theory on this subject.



Measure FET

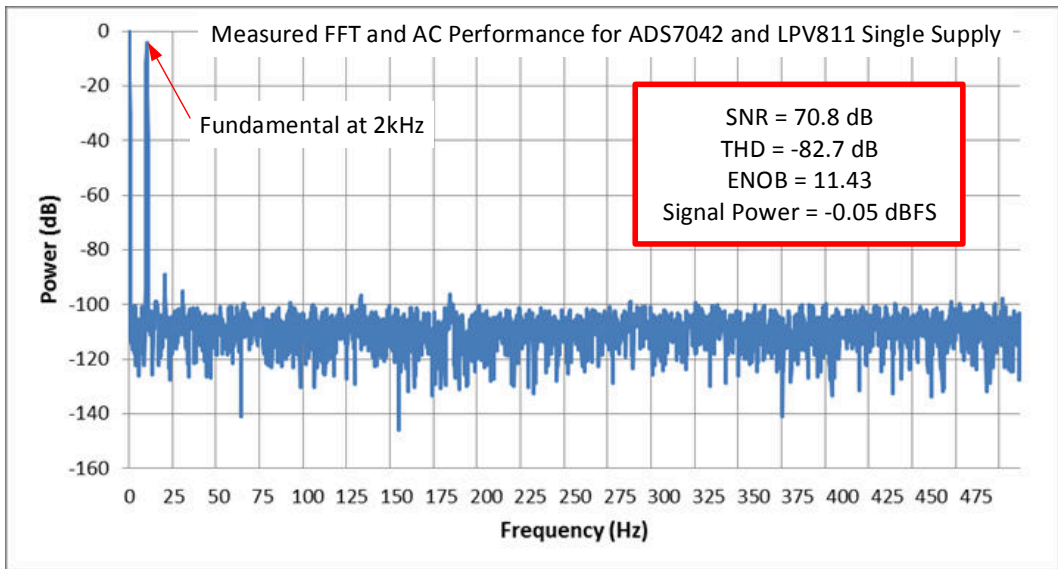This performance was measured on a modified version of the ADS7042EVM-PDK. The AC performance indicates SNR = 70.8dB, THD = -82.7dB, and ENOB (effective number of bits) = 11.43, which matches well with the specified performance of the ADC of SNR = 70dB.



Design Featured Devices

Device	Key Features	Link	Similar Devices
ADS7042 ⁽¹⁾	12-bit resolution, SPI, 1-Msps sample rate, single-ended input, AVDD, Vref input range 1.6V to 3.6V.	12-Bit 1MSPS Ultra-Low-Power Ultra-Small-Size SAR ADC With SPI	ADCS
LPV811 ⁽²⁾	8kHz bandwidth, Rail-to-Rail output, 450nA supply current, unity gain stable	Single Channel 450nA Precision Nanopower Operational Amplifier	Op amp

- (1) The ADS7042 uses the AVDD as the reference input. A high-PSRR LDO, such as the TPS7A47, can be used as the power supply.
- (2) The LPV811 is also commonly used in low speed applications for sensors. Furthermore, the rail-to-rail output allows for linear swing across all of the ADC input range.

Link to Key Files

Texas Instruments, [LPV811 TINA files](#), software download

Revision History

Changes from Revision A (March 2019) to Revision B (September 2024)	Page
• Updated the numbering format for tables, figures, and cross-references throughout the document.....	1

Changes from Revision * (February 2018) to Revision A (March 2019)	Page
• Changed <i>AC Transfer Characteristic</i> section to improve bandwidth confusion and to be more in line with Low-power sensor measurements: 3.3-V, 1-ksps, 12-bit single-ended, dual-supply circuit.....	1
• Changed the title to Data Converters. Added link to circuit cookbook landing page.....	1

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated