


# Realizing Remote Temperature Sensing and Protection Using TI High-Side Switch Controllers



Swarna Sagar, Rakesh Panguloori

## System Introduction


With increasing demand for vehicle electrification to meet stringent emission targets, automotive manufacturers are using dual 48V/12V battery systems which can allow engineers to move all power-hungry loads such as air conditioning compressors, electrical power steering, and so on to the 48V battery side while the 12V battery continues to power remaining loads such as lighting, infotainment, and so on. [Figure 1](#) is a typical block diagram for 48V/12V battery system in which High side switch controllers drive external MOSFETs, functioning as battery disconnect and circuit breaker switches. These system designs include DC/DC converter, battery management systems, power distribution box, and so on in dual battery systems.

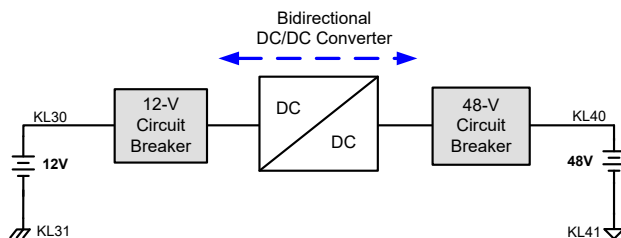

**Figure 1. Block Diagram of a Bidirectional 48V to 12V System in Electric Vehicles**

In such high power designs, while driving external power MOSFETs, one of the key considerations from power design engineers is to make sure robust thermal protection to prevent overheating and thermal runaway. So, accurate temperature sensing and overtemperature protection is crucial. This application brief covers the design considerations of realizing remote temperature sensing and protection using TI's smart high side switch controller.

TPS4811x-Q1 and TPS1211x-Q1 are TI's smart high side switch controller with protection and diagnostics. These features an integrated remote temperature sensing, protection and dedicated fault output. The remote temperature measurement is done by using external transistor in diode configuration as shown in [Figure 2](#).

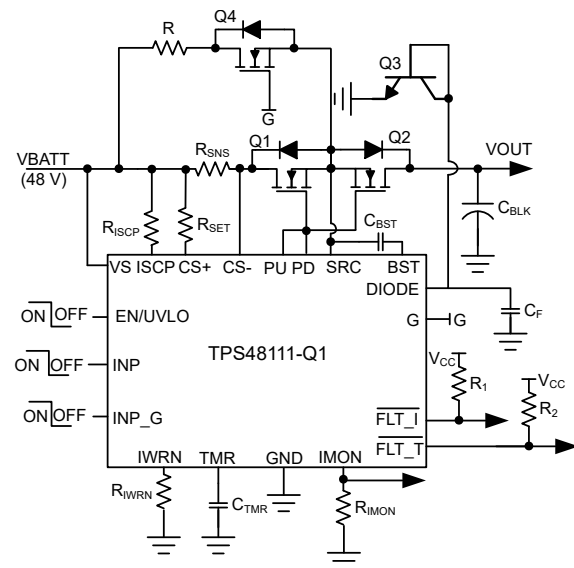

**Figure 2. Circuit Breaker for DC-DC Converter**

## Diode Based Remote Temperature Sensing

A common practice is to use an external NPN Bipolar Junction Transistor (BJT) as a remote temperature sensing element. The NPN transistor is connected in diode mode such that case temperature of device or PCB can be estimated by base emitter forward voltage. The standard Ebers-Moll model gives simplified equation for the collector current as [Equation 1](#).

$$I_C = I_S \times e^{\left(\frac{V_{BE}}{\eta \times V_T}\right)} \quad (1)$$

$$V_T = \frac{kT}{q} \quad (2)$$

where

- $I_C$  is the collector current
- $I_S$  is the reverse saturation current
- $V_{BE}$  is the base emitter forward voltage drop
- $V_T$  is the thermal voltage
- $T$  is the temperature of the transistor in Kelvin degrees

- $\eta$  is the ideality factor( $\eta$ -factor), varies from manufacturer to manufacturer
- $k$  is the Boltzmann constant ( $1.38 \times 10^{-23}$  J/Kelvin)
- $q$  is the charge of an electron ( $1.602 \times 10^{-19}$  C)
- $k/q$  is constant( $8.61423 \times 10^{-5}$ )

Solving for temperature results in [Equation 3](#)

$$T = \frac{q \times V_{BE}}{\eta \times k \times \ln\left(\frac{I_2}{I_1}\right)} \quad (3)$$

Because  $\eta$ -factor,  $k$ , and  $I_S$  are constants, the straightforward way to measure temperature is to force collector current, measure voltage and then calculate temperature accordingly. However, the reverse saturation current has process dependencies and varies widely, which significantly impacts the temperature measurement accuracy. To overcome these drawbacks, the two current delta method approach has gained popularity. This method employs two currents such that temperature is determined by the difference of two diode voltage ( $V_{BE}$ ) measurements, as shown in [Equation 6](#).

$$\Delta V_{BE} = V_{BE2} - V_{BE1} \quad (4)$$


$$\Delta V_{BE} = \frac{\eta k T}{q} \ln\left(\frac{I_2}{I_S}\right) - \frac{\eta k T}{q} \ln\left(\frac{I_1}{I_S}\right) = \frac{\eta k T}{q} \ln\left(\frac{I_2}{I_1}\right) \quad (5)$$

$$T = \frac{q \times \Delta V_{BE}}{\eta \times k \times \ln\left(\frac{I_2}{I_1}\right)} \quad (6)$$

By maintaining precise current ratio of ( $I_2/I_1$ ), this approach cancels out the process variation effects of reverse saturation current ( $I_S$ ) making the temperature measurement dependence only on the  $\eta$ -factor, which is relatively stable compared to  $I_S$  and can be obtained from the transistor manufacturer.

### Overtemperature Protection using TI High Side Switch Controllers

The TPS4811x-Q1/ TPS1211x-Q1 controller forces two currents  $10\mu A(I_1)$  to  $160\mu A(I_2)$  in to external transistor and measures change in  $V_{BE}$  voltage ( $\Delta V_{BE}$ ) to detect over temperature and trigger thermal shutdown to turn-off the external MOSFET under any fault conditions. The device has also features a dedicated fault( $\overline{FLT\_T}$ ) pin which asserts low when overtemperature fault is detected. The simplified block diagram of DIODE based remote temperature sensing scheme in TPS4811x-Q1 is shown in [Figure 3](#).

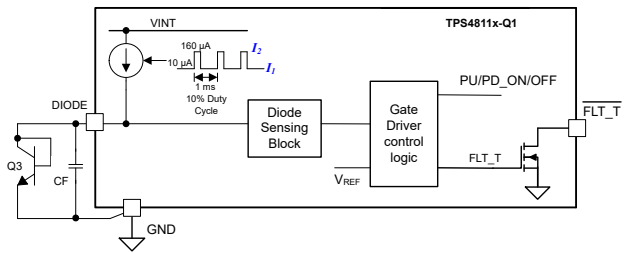


**Figure 3. DIODE Based Remote Temperature Sensing in TPS4811x-Q1**


As the PCB temperature increases,  $\Delta V_{BE}$  increases accordingly and at  $150^\circ C$ ,  $\Delta V_{BE}$  approaches  $101.5mV$  which is set as internal threshold for TPS4811x-Q1 to trigger overtemperature protection. [Figure 4](#) shows timing diagram of overtemperature protection scheme.

- In TPS48110-Q1, once the sensed temperature reaches approximately  $150^\circ C$ , the device pulls PD(Gate driver Pull-Down) to SRC(Source of MOSFET), turning off the external MOSFET and also asserts  $\overline{FLT\_T}$  low. After the temperature reduces to  $135^\circ C$ , an internally fixed auto-retry cycle of  $512ms$  commences. The device turns on the external MOSFET and  $\overline{FLT\_T}$  also de-asserts after the retry duration of  $512ms$  is lapsed.
- In TPS48111-Q1,once the sensed temperature crosses  $150^\circ C$ , the device turns off the external FET and device remains in latched state. The latch gets reset by toggling  $V_{EN/UVLO}$  below  $V_{(ENF)}$  or by power cycling  $V_S$  below  $V_{(VS\_PORF)}$ .


[Figure 5](#) and [Figure 6](#) shows diode pin voltage profile at room temperature and at the instant of overtemperature shutdown.

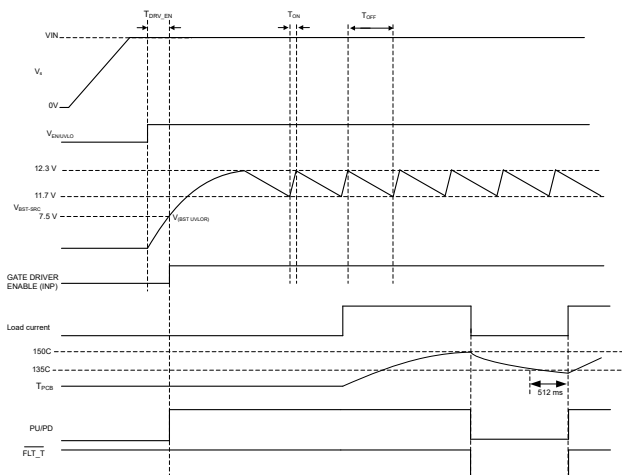

**Figure 4. Timing Diagram of Overtemperature Protection Scheme**

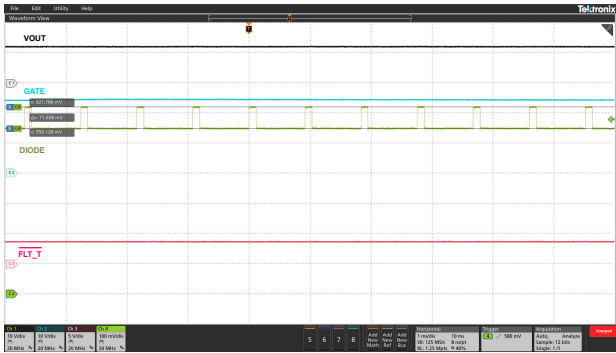

**Figure 5. Diode Pin Voltage Profile at 25°C**

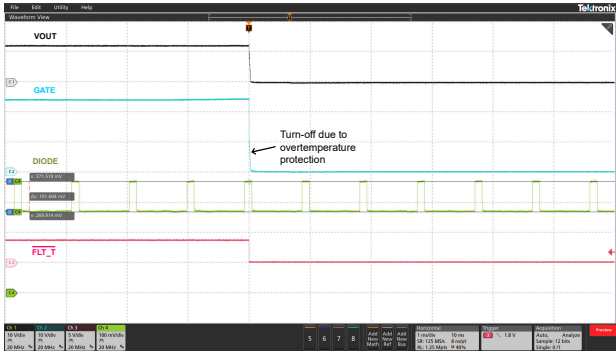

**Figure 6. Diode Pin Voltage Profile at 150°C**

### Design and Layout Guidelines

Accurate overtemperature protection depends on proper NPN selection and good layout. A simple set of design and layout rules can prevent a lot of problems during system operation and help to achieve overtemperature protection within  $150 \pm 10^\circ\text{C}$ .


- The overtemperature protection threshold depends on the ideality factor ( $\eta$ ) which can vary widely from one transistor type to another. TI recommends BJT MMBT3904 to use as a remote temperature sense element (Q3). Any 3904 manufacturer with ideality factor close to 1.004 is preferred as mentioned in [Table 1](#).

**Table 1. Details of Ideality Factor from Suitable Vendors**

3904 Manufacturer	Typical Ideality Factor ( $\eta$ -factor)
Diodes Inc.	1.0044
Philips	1.0049
ST Micro	1.0045
On Semi	1.0045
Infineon	1.0044

- Place a small filter capacitor (CF) of 1000pF near controller between DIODE and GND pins to reduce/mitigate the effects of noise.

- Place transistor (Q3) adjacent to pass MOSFET or in between the MOSFETs in parallel configuration.
- Route a differential pair connection from the transistor (Q3) to the controller with minimum spacing as shown in [Figure 7](#). Connect return path directly to the GND pin and eliminate shared ground path.
- High PCB trace resistance from Q3 to the controller can cause temperature offset. So, use thicker traces to minimize the parasitic resistance.
- Keep the trace length short as much as possible as longer trace run offers more opportunity to pick up noise due to trace inductance.
- Avoid routing near noise generators such as fast clock, switching nodes, large current traces, and so on.

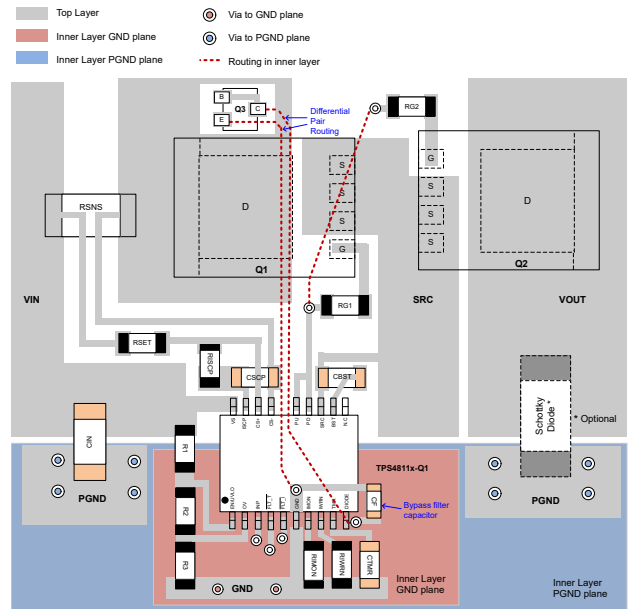

**Figure 7. Layout and Placement Recommendation for the Temperature Sense Diode (Q3)**

### Conclusion

The TPS4811x-Q1 features an integrated remote temperature sensing and overtemperature protection to prevent overheating and thermal runaway in high power system designs. Proper selection of NPN transistor and layout techniques such as differential pair routing discussed in this application brief are essential to make sure overtemperature protection at the correct threshold point.

### References

- Texas Instruments, [Optimizing Remote Temperature Sensor Design](#), application report.
- Texas Instruments, [TPS4811-Q1 100V Automotive Smart High-Side Driver With Protection and Diagnostics](#), data sheet.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated