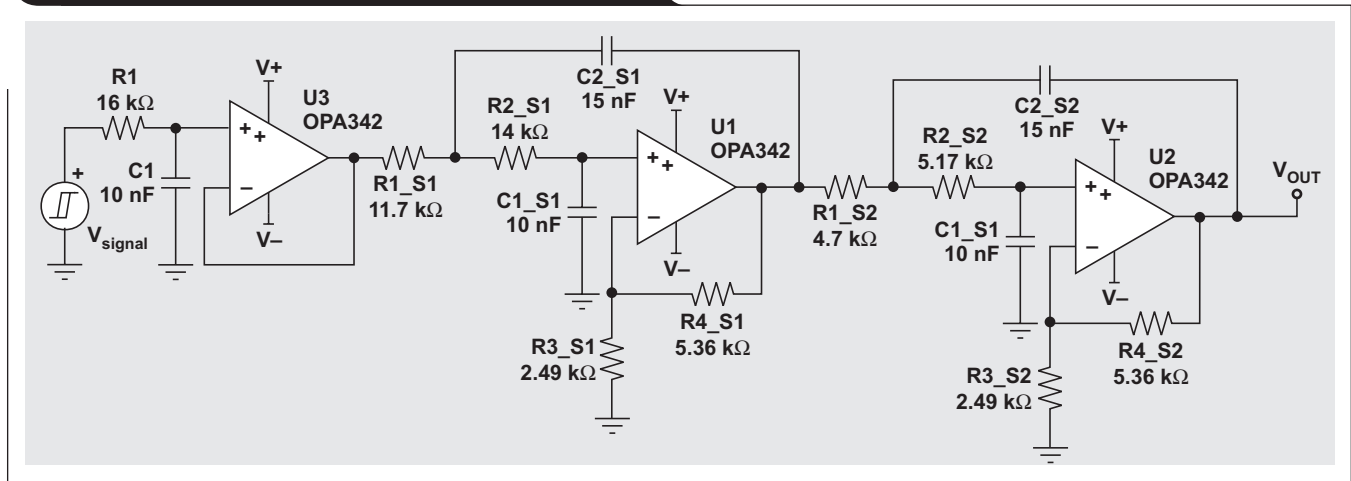


How to compare your circuit requirements to active-filter approximations

By Bonnie C. Baker

WEBENCH® Senior Applications Engineer

Figure 1. Example of a low-pass Butterworth filter



Introduction

Numerous filter approximations, such as Butterworth, Bessel, and Chebyshev, are available in popular filter software applications; however, it can be time consuming to select the right option for your system. So how do you focus in on what type of filter you need in your circuit? This article defines the differences between Bessel, Butterworth, Chebyshev, Linear Phase, and traditional Gaussian low-pass filters. A typical Butterworth low-pass filter is shown in Figure 1.


Generic low-pass filter frequency and time response

Figure 2 illustrates the frequency response of a generic low-pass filter. In this diagram, the x-axis shows the frequency in hertz (Hz) and the y-axis shows the circuit gain in volts/volts (V/V) or decibels (dB).

The low-pass filter has two frequency areas of operation: the passband region and the transition region. In the passband region, the input signal passes through with minimum modifications. The level of modification depends on the filter approximation type. For example, the amount of modification for the Butterworth filter is minimal because the transfer function is often described as maximally flat. In contrast, the Chebyshev filter will have ripple in the passband region.

In the transition region, the filter attenuates the input signal with increasing frequency. This attenuation rate is generally dependent on the filter order or number of poles. A first-order filter (single pole) performs with a

Figure 2. Generic frequency response of a low-pass filter

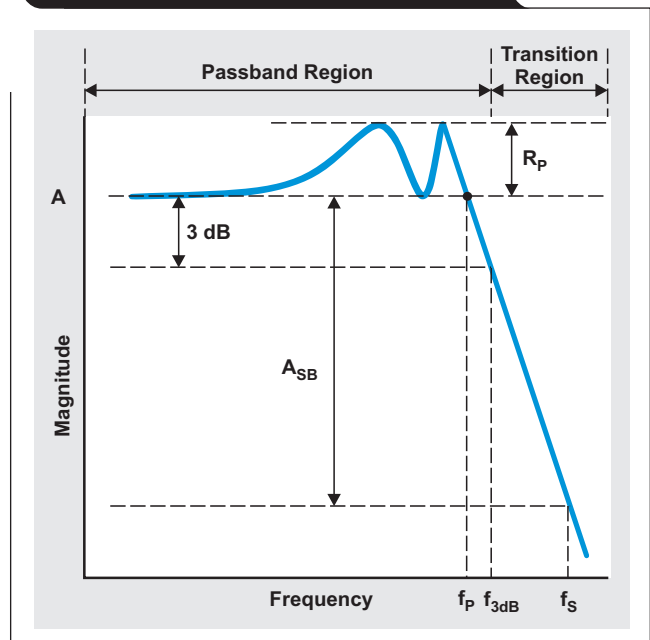


20-dB/decade attenuation after the 3-dB frequency. A fifth-order filter (five poles) generally produces a 20×5 -dB/decade attenuation, or 100 dB/decade. Again, this attenuation rate has minimal variations between the approximation types.

In Figure 2, the DC gain of the filter is defined with the A parameter. Some filters exhibit a ripple on the DC gain curve as the frequency increases. This ripple magnitude is defined as R_p .

The corner frequency of the low-pass filter is at the 3-dB point below the DC gain level. Beyond the corner frequency, A_{SB} in combination with A and f_s , define the rate of attenuation.

Figure 3 shows the generic time response of a low-pass filter. In order to generate this filter response, a step response is applied to the input of the filter. In this diagram, the units for the x-axis is time, and the y-axis represents the responses amplitude in volts. There are five parameters that define the step-response curve: propagation delay, slew rate, overshoot, settling time, and settling-time error.

Figure 3. Generic time response of a low-pass filter

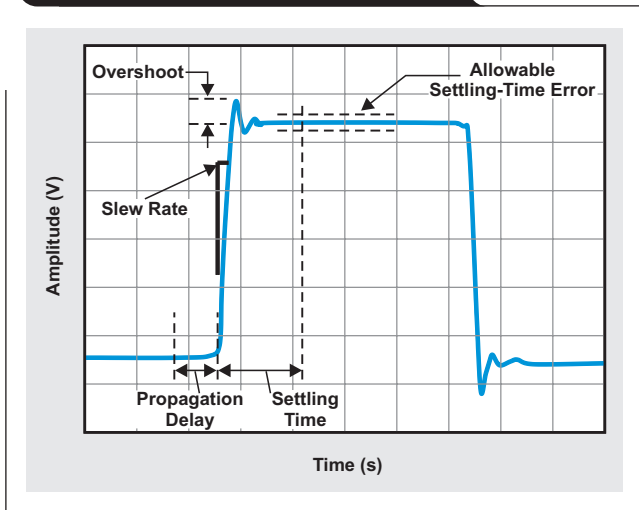

The propagation delay of a filter’s response is a result of the magnitude of the frequency domain phase. By definition, the propagation delay is the time delay between the filter’s input step and the resulting change at the output.

Following the propagation delay period, the output of the filter attempts to match the input signal. During this time, the output rises and the measurement of the slew occurrence is from 10 to 90% of the entire span. This catch-up activity causes a signal overshoot. The overshoot is typically measured as a percentage.

The amplifier filter continues to attempt to match the input signal. During this time, there is a settling activity. The settling time combines the slew time and the time it takes for the filter circuit to settle to a final value. The definition of this final value is the settling-time error band. For 12-bit systems, this error band is usually equal to a half of the least significant bit (LSB), or 0.01%. For a 16-bit system, this error band is usually equal to 0.001%.


Bessel low-pass active filter

W. E. Thomson applied the Bessel function, which Friedrich Bessel developed in the mid-1800s, to filter a design in 1949. Figure 4 shows the frequency, phase and time response of a fifth-order, low-pass Bessel filter.

The frequency behavior has a maximally flat group/phase delay. This type of phase delay retains the wave shape in the passband region and exhibits very little ringing or overshoot in the transition region. This benefits the time-domain step response because there is very little overshoot or ringing compared to the Butterworth and Chebyshev filters. The rate of attenuation in the transition band is the slowest of the filters examined, so if a “brick-wall” filter is expected, the Bessel filter is not a good choice.

Where does this filter come in handy? It is found in audio cross-overs because of the minimal overshoot responses in the time domain.

Figure 4. Fifth-order, low-pass Bessel filter

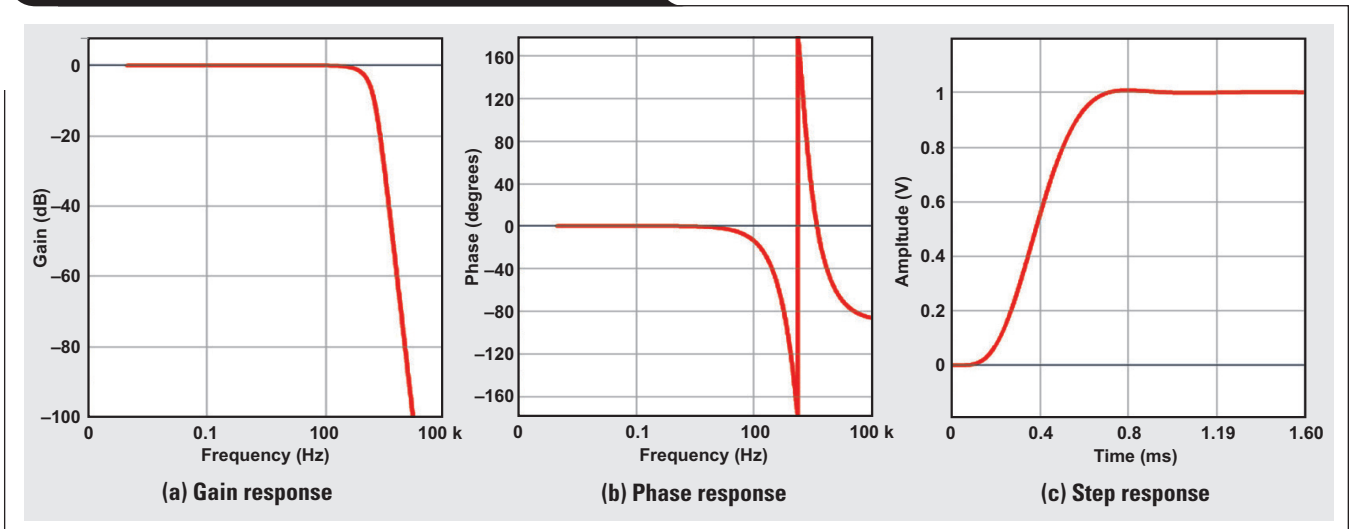

Butterworth low-pass active filter

Stephen Butterworth described the Butterworth filter in his 1930 paper titled, “On the Theory of Filter Amplifiers.” As Figure 5 shows, the frequency behavior of the Butterworth filter has a maximally flat magnitude response in the passband.

The rate of attenuation in the transition band is an improvement over the Bessel filter. However, the step-response overshoot and ringing of the Bessel filter can be lower.

The uses of this middle-of-the-road filter are extensive. This filter is found across the entire range of applications. The maximally-flat characteristic in the passband region is beneficial.

Chebyshev low-pass active filter

In the frequency domain, there is a magnitude of ripple in the passband. The ripple magnitude in the gain response shown in Figure 6a is 3 dB. The rate of attenuation in the transition band is steeper than the Butterworth and Bessel filters, but there is a price to pay for this faster frequency fall-off. As Figure 6 shows, the step response has a fair degree of overshoot and ringing.

The attenuation rate can be faster in the transition region by increasing the magnitude of the ripple in the passband. However, be aware that this action will increase the ringing with the step response.

The Chebyshev filter would be used in systems where the higher-frequency noise requires more aggressive attenuation.

Figure 5. Fifth-order, low-pass Butterworth filter


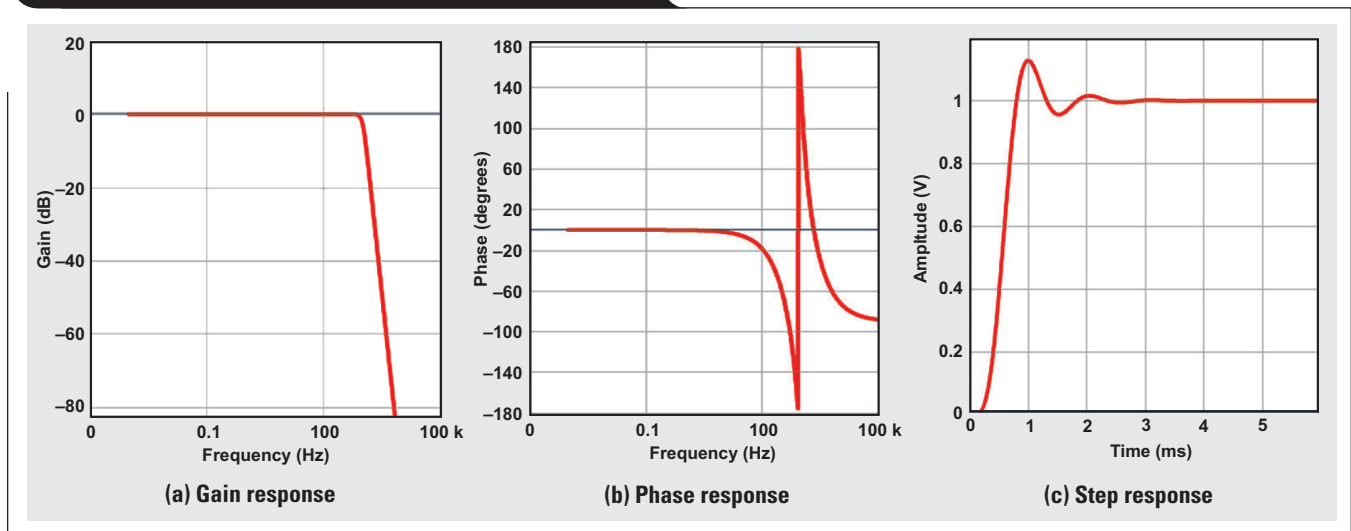


Figure 6. Fifth-order, low-pass Chebyshev 3-dB ripple filter

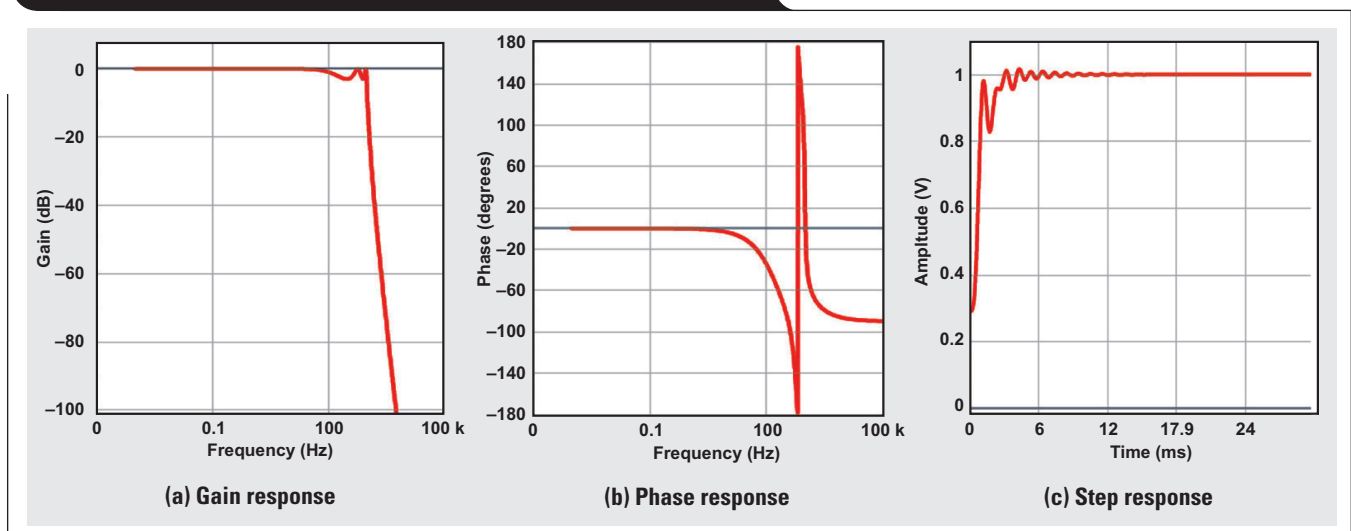

Linear-phase low-pass active filter

As the name of this filter indicates, the linear-phase filter has a linear-phase response in the passband (Figure 7). This is similar to the Bessel filter, but the linear range in this filter exceeds the wide range of the Bessel.

Because of ripples in the phase response, this filter also has faster attenuation after the 3-dB frequency. As the phase ripple increases, the constant delay region extends further into the transition region. The step response shows slightly more overshoot than the Bessel, but not as much as the Butterworth and Chebyshev.

Traditional Gaussian low-pass active filter

The traditional Gaussian 6-dB filter (Figure 8) is a compromise between a Chebyshev and a Bessel filter. The traditional Gaussian filter is similar to a Bessel filter, in that it has nearly linear phase shift and smooth, monotonic roll-off into the transition region.

The Gaussian 6-dB step response has less overshoot and is between the Bessel and Butterworth filter.

Figure 7. Fifth-order, low-pass linear-phase, 0.5-degree filter

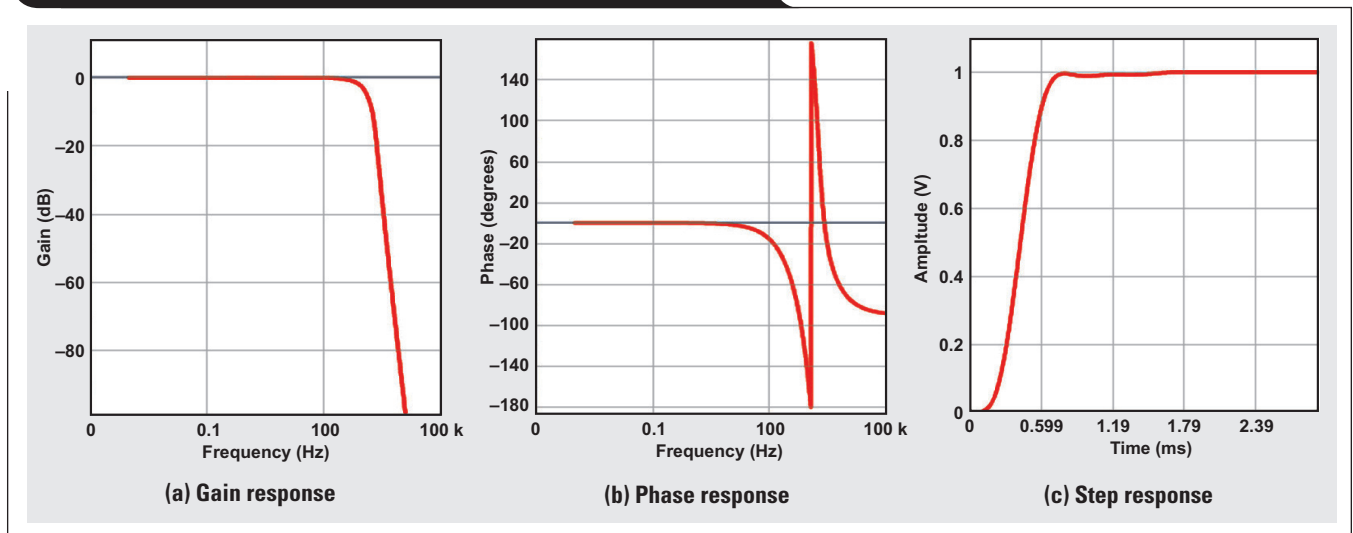


Figure 8. Fifth-order, low-pass traditional Gaussian 6-dB filter

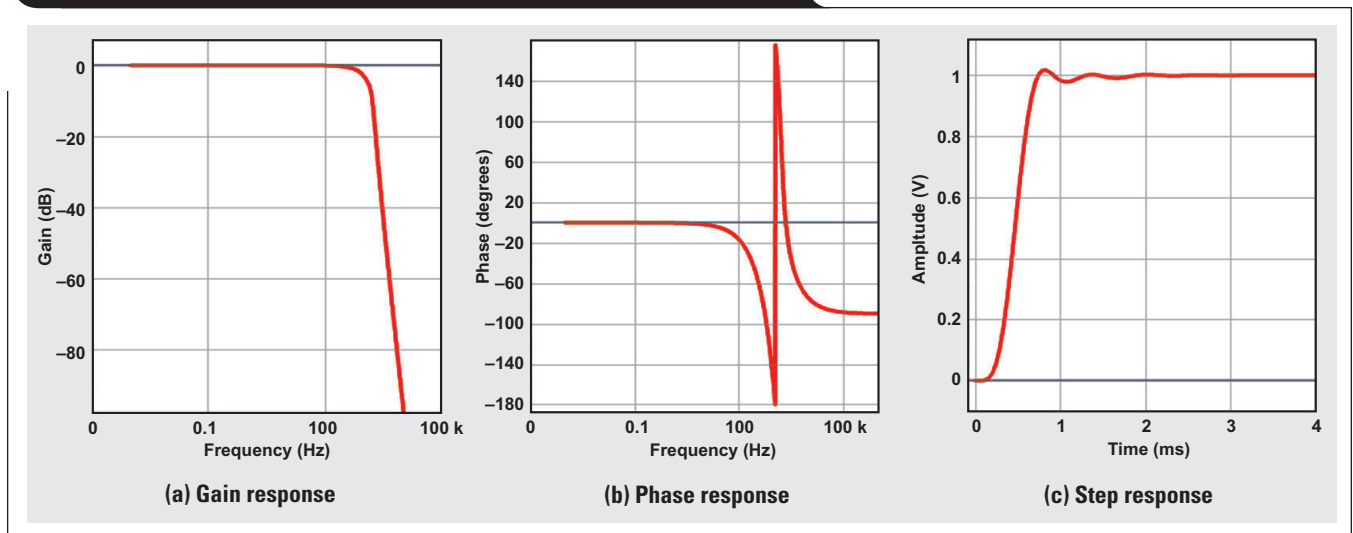


Table 1. Comparison between active fifth-order, low-pass filters

Filter Approximation	Passband Region	Transition Region	Step Response
Bessel	Flat magnitude response in pass-band	Slower than the Butterworth or Chebyshev filters	Very little overshoot or ringing as compared to the Butterworth and Chebyshev filters
Butterworth	Maximally flat magnitude response in pass-band	Steeper than Bessel, not as good as Chebyshev filter	Some overshoot and ringing, but less than the Chebyshev filter
Chebyshev	Ripple in the pass-band	Steeper than Butterworth and Bessel filters	Fair degree of overshoot and ringing
Linear Phase	Linear phase response, which exceeds the bandwidth of the Bessel	Faster attenuation than Bessel due to ripples in phase response	Slightly more overshoot than Bessel, but not as much as the Butterworth
Traditional Gaussian	As with the Bessel, has a linear phase response	Smooth roll-off	Overshoot less than the Butterworth, with some ringing

Conclusion

This article addressed the difference between Bessel, Butterworth, Chebyshev, linear phase, and traditional Gaussian low-pass filters. As shown in Table 1, these filters present variations in passband flatness, phase response, and step-response ringing and overshoot.

At this point, the decision now lies with you and your circuit requirements. If a well-behaved step response with minimal ringing is required, consider the linear phase filter. In contrast, if a filter to attenuate quickly in the transition region is required, the Chebyshev may be the best alternative.

The TI Filter Designer tool is a quick and easy way to compare these filters with your parameters. In this software, you can select a filter and then run simulations to take a closer look.

Related Web sites

WEBENCH® Filter Designer tool

Product information:

OPA342

Visit www.ti.com/aaaj to see all AAJ articles.

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(512) 434-1560
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone		
European Free Call	00800-ASK-TEXAS (00800 275 83927)	
International	+49 (0) 8161 80 2121	
Russian Support	+7 (4) 95 98 10 701	

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	<u>Toll-Free Number</u>
Note: Toll-free numbers may not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
International	+86-21-23073444
Fax	+86-21-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

E2E is a trademark and WEBENCH is a registered trademark of Texas Instruments. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com