

Integrated digital output drivers simplify sensor designs



Max Robertson
Applications Manager
Interface, TRX
Texas Instruments

Highly integrated digital output drivers expand digital sensor functionality and improve robustness while reducing design complexity.

Improvements in automation technology are enabling factories to become increasingly flexible, efficient and intelligent. To realize these improvements, though, requires the ability to continuously monitor various operating conditions, environmental factors and process variables at all stages of production. Increased monitoring drives the need for smaller, more robust and more cost-effective sensors of all types. This white paper focuses on digital output sensors, which are commonly used in factory automation and process automation applications when analog reporting is not needed.

Digital output sensors

Digital output sensors translate a real-world variable like pressure, temperature or target proximity into a binary state based on a transducer threshold level. The sensor expresses this binary state electrically as a high voltage, low voltage or high impedance, and sends an output to either a programmable logic controller (PLC) or a binary actuator so that

an action can occur based on a change in the sensor's value. Sensors commonly use three types of digital outputs: p-channel n-channel p-channel (PNP), n-channel p-channel n-channel (NPN) and push-pull. These three output types are illustrated in **Figure 1**; a PNP output is shown at left, an NPN output is shown in the center, and a push-pull output is shown at right.

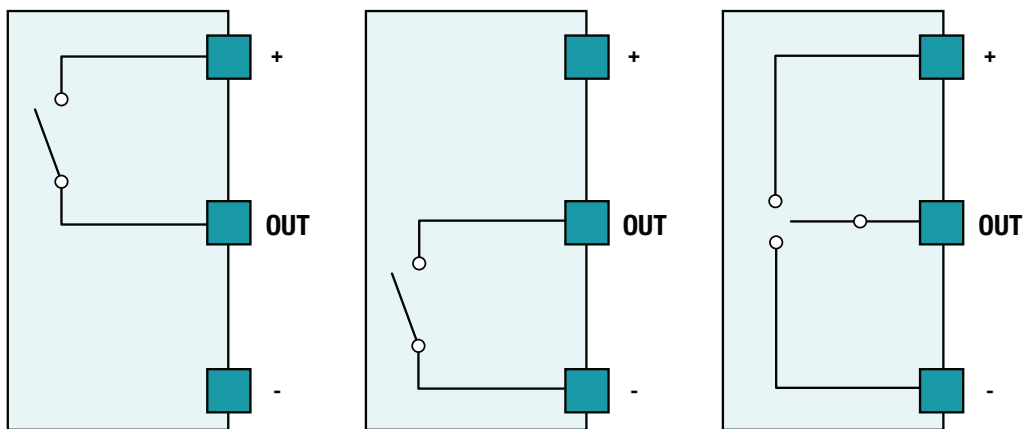


Figure 1. PNP (left), NPN (center) and push-pull (right) output types.

Discrete implementations

Given the seeming simplicity of a binary output, many designers opt to pursue a discrete

implementation based on individual transistors.

Figure 2 shows example implementations for PNP (top), NPN (center) and push-pull (bottom) outputs.

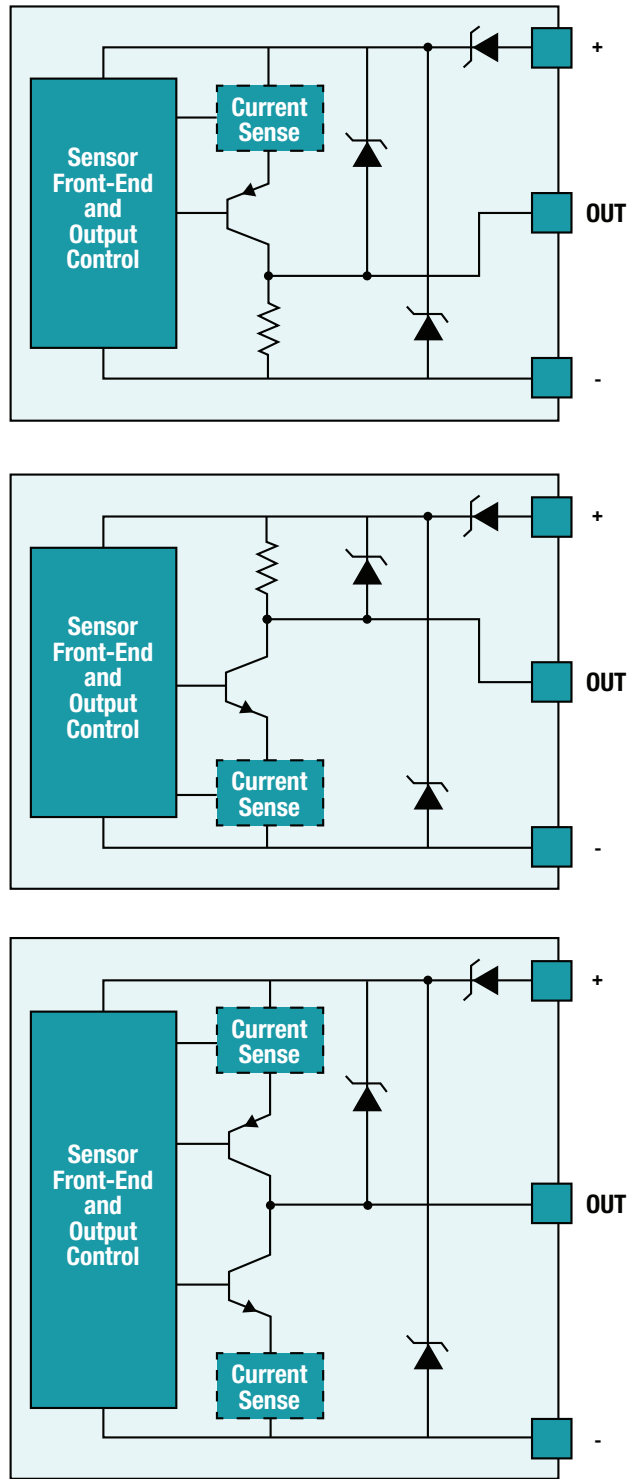


Figure 2. PNP (top), NPN (center) and push-pull (bottom) output implementations.

Although a single transistor is sufficient for basic output-switching functionality, you'll need several other components in order for the sensor to meet common system requirements:

- As sensors are installed in the field, there is a chance for miswirings to occur such that the positive and negative power supplies are reversed or connected to the sensor output. To prevent such conditions from damaging the sensor, you must use a reverse-polarity blocking diode.
- During operation, sensor outputs and power rails may be subject to transient stresses such as electrostatic discharges or voltage surges coupling onto the wiring. Transient voltage suppression (TVS) diodes are frequently used to protect against these stresses. Care must be taken in component selection, though, since the TVS must be able to clamp the voltage within the supported voltage range of the sensor even during high-current surge events.
- Overcurrent protection is necessary in order to prevent excess power dissipation in the transistor, since thermal damage could occur if not controlled. This protection requires a current-sensing circuit placed in series with the transistor, which unfortunately can result in a drop in voltage at the sensor output. In some cases, this extra voltage drop prevents the sensor from meeting the input-voltage specifications of the digital input to which it connects. You will also need some additional logic (not shown in **Figure 2**) to control the output transistor accordingly so that it is disabled (high impedance) when an overcurrent condition persists.
- External pull-up and pull-down resistors on the sensor output lines keep the output voltage fully high or low, even when connected to a high-impedance digital input.

- Many sensors require a lower-voltage power rail (for example, 5 V or 3.3 V) in addition to a high-voltage DC field supply. This lower-voltage rail may power certain sensor elements, microcontrollers or other logic circuits, which then necessitates the inclusion of an additional voltage regulator such as a linear regulator or switched-mode DC/DC converter.
- For sensors designed to operate from lower-voltage rails, you may need additional driver circuitry in order to translate low-voltage sensor outputs to a high-enough signal to fully enable the PNP output transistor.

A further drawback of a discrete implementation is that it is relatively inflexible. The sensor isn't reconfigurable between PNP, NPN and push-pull modes, and any output current limits (if implemented) would be fixed values. This means that designers may need to keep an inventory of several different sensor devices to interface with different input types.

Integrated implementations

Semiconductor vendors have responded to the market need for smaller, more robust and more flexible sensors by developing highly integrated solutions that implement all of the functionality shown in **Figure 2** in a single integrated circuit. **Figure 3** shows an example of such a device, TI's [TIOS101](#).

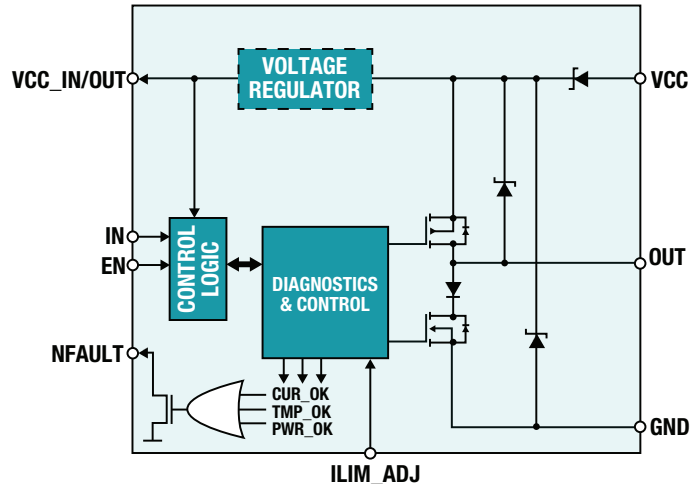


Figure 3. TIOS101 block diagram.

This integrated approach has several key advantages. One major advantage is that you can implement a high degree of transient protection. In the case of the TIOS101, it's possible to achieve system-level immunity to electrostatic discharge (ESD) (per International Electrotechnical Commission [IEC] 61000-4-2) up to ± 16 kV, electrical fast transient (per IEC 61000-4-4) up to ± 4 kV and surge (per IEC 61000-4-5 with 500- Ω source impedance) up to ± 1.2 kV with no external components. If you need additional protection, the device's tolerance to ± 65 -V transients enables the use of small, cost-effective TVS diodes.

In addition to improved transient immunity, integrated devices are also capable of tolerating DC stresses. Integrated reverse-polarity blocking diodes prevent damage in the event of any miswiring. Implementing output overcurrent protection and overtemperature shutdown can prevent fault conditions, such as short circuits on the output line and the resulting high power dissipation, from damaging the sensor. In the case of the TIOS101 device, you can configure the output overcurrent threshold over a wide range by varying a single external resistance, and thus use the same design for a variety of applications.

When the output current exceeds the configured threshold for a certain amount of time, the output driver automatically shuts itself off, indicates a fault condition via a single logic output pin and waits a fixed amount of time before reactivating. This feature eliminates the need for external logic such as timers to help manage fault states. The TIOS101 output driver's ability to source or sink large currents for short periods before activating overcurrent protection enables the sensor to interface directly with loads that require significant demagnetization (in the case of inductive loads) or discharge (in the case of capacitive loads).

Devices like the TIOS101 also help sensor designers support multiple different output types with a common hardware implementation. Sensors are reconfigurable as NPN, PNP or push-pull through the control of just two logic lines. A single design for all three output types simplifies development, product qualification and inventory management on the back end.

Finally, with an integrated device, it is possible to include other functions outside of simple output switching. For example, the [TIOL101-5](#) integrates a linear voltage regulator in addition to a digital output driver, thus reducing the number of components needed for sensors implementing low-voltage, low-current power rails.

Even with all of these advantages, integrated digital output drivers still maintain a small footprint on a printed circuit board. The TIOS101 device is just 2.5 mm wide and 3 mm long. These dimensions, coupled with flowthrough signal routing, enable sensors with extremely small form factors.

Conclusion

Advancing the trend of more efficient and intelligent industrial production requires digital output sensors that are small, robust and flexible. Although fully discrete output driver implementations are pervasive, a new class of highly integrated devices can improve performance and expand functionality while decreasing component count and solution size.

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

The platform bar is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated