

LM2577,LM4040

Negative Buck Switching Regulator (using LM258x)



Literature Number: SNVA536

Negative Buck Switching Regulator

High efficiency step-down switching regulators for positive voltages are very common, especially since National introduced the SIMPLE SWITCHER™ product line of IC switchers. But occasionally negative step-down switching regulators are needed in some systems.


The circuit shown here accepts a negative input voltage and efficiently converts it to a smaller negative voltage, at load currents up to approximately 2.8 Amps. (negative voltage in, negative voltage out, common ground)

Circuit description

The LM2577-ADJ step-up switching regulator IC is used in a non standard configuration to provide a negative buck regulator function. The 3 Amp IC switch current rating allows the regulator circuit to provide a guaranteed 2.8 Amps of load current when the circuit is operating in the continuous mode.

Since the 1.24V feedback sense voltage for the LM2577-ADJ is referenced to the IC's ground pin, (which is $-V_{IN}$ in this circuit) some feedback level shifting is needed. A PNP transistor is used to sense the output voltage and level shift the output voltage (which is referenced to the positive rail) down to the LM2577 feedback pin (which is referenced to the negative rail). With the values shown, the 5V output causes approximately 300 μ A of emitter current to flow through the PNP, down through the 4.12k resistor, developing the needed feedback sense voltage of 1.24V to force the output to be -5V.

D1 provides output voltage temperature compensation by cancelling out the effects of the temperature drift of the PNP emitter-base voltage. D2 & D3 provide some pre-regulation for the biasing current needed for D1, thus improving both line regulation and 120 Hz ripple rejection by a factor of 2. Additional performance improvement is possible by replacing the two series connected diodes with a 1.2V reference diode such as the LM385-1.2 or the LM4040-2.5. To simplify the circuit, or if the input voltage is relatively constant and has very little 120 Hz ripple on it, D2 and D3 could be eliminated and the 1k & 3.9k resistors could be

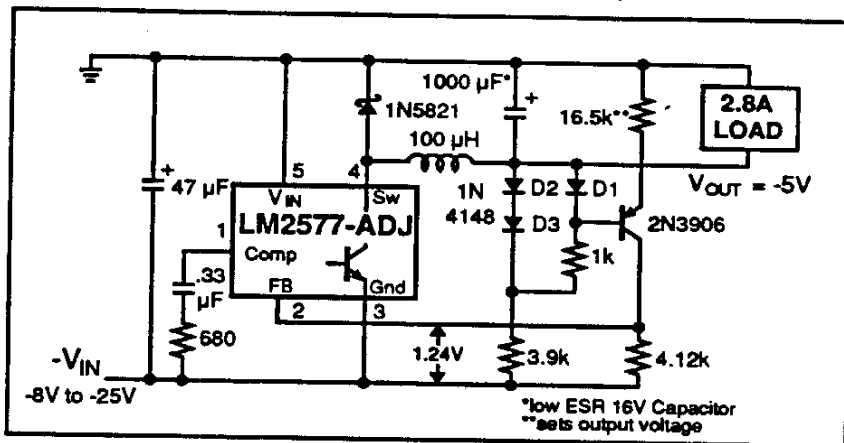


Typical Specs for the above circuit are:

Line Regulation (V_{IN} from -10V to -20V)	35 mV (Output decreases with increasing input voltage)
Load Regulation ($V_{IN} = 15V$, I_{LOAD} from 0.5A to 3A)	45 mV (Output increases with increasing load)
Ripple Rejection ($V_{IN} = 15V$, 120 Hz, 0.5A Load)	46 dB
Efficiency (depending on input voltage and output load current)	75% to 86%
52 kHz Output Ripple Voltage (Output capacitor ESR = 20 m Ω)	20 mV p-p

placed with a 27k resistor. Also, eliminating D1 will provide a negative temperature coefficient of the output voltage.

Loop stability is determined by the compensation components (the R & C on pin 1) and also the Equivalent Series Resistance (ESR) of the output capacitor. Different types of output capacitors may need different values of compensation (R & C). Perhaps the easiest method to check compensation is to pulse load the output and look at how the output voltage responds. The capacitor used in this circuit had a very low ESR (20 m Ω) because it was a high frequency "switching type" capacitor. Input voltage may also affect overall stability, so if a different range of input voltages are to be used, the RC components may need some tweaking.

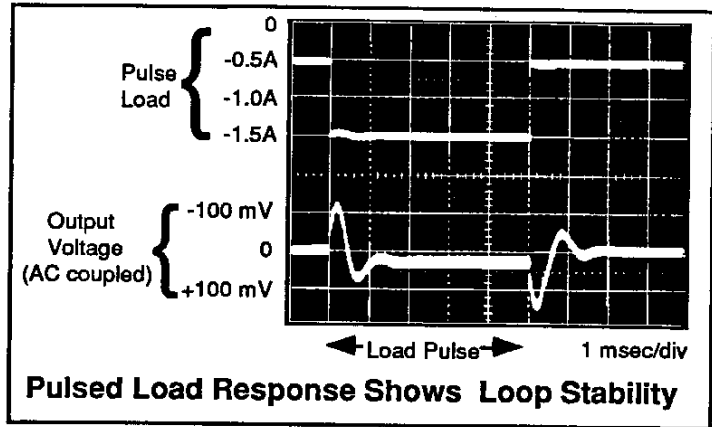Other output voltages are also obtainable by varying the 16.5 k Ω resistor. For a stable output voltage, use 1% resistors. Different voltages may need different values of compensation R & C.



The inductor used must be rated for 52 kHz operation and of course its current rating must be approximately 10% greater than the maximum load current. The inductance value is not critical, and its value can range from 80 μ H to 220 μ H without any problem. For higher ambient temperatures and at the higher load currents, a small heat sink may be needed on the LM2577-ADJ to keep it at a safe temperature.

Always breadboard your circuit first, (and don't use one of the wireless breadboards because they have too much inductance and stray capacitance for a good switcher circuit), and follow good switcher layout techniques. Keep leads short, especially the schottky catch diode and input and output capacitors. Locate the input capacitor near the input and ground pins of the IC. Use a scope probe with a low inductance ground connection when looking at the switching spikes on the output voltage, otherwise you may be seeing transients that are larger than they actually are.

One additional item. Because of the level shifting circuitry, the minimum input voltage is approximately -8V, and if this voltage is ramped down slowly, (such as when the voltage adjust pot on a power supply is turned) the regulated output voltage will overshoot by approximately 2V before snapping into regulation. Because of the soft start feature built into the LM2577, this 2V overshoot doesn't occur when the input ramps down quickly.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated