

In Automotive Lighting, It's Time to Say Goodbye to Discrete Solutions



Allie Zhang

Auto manufacturers are using light-emitting diodes (LEDs) beyond the traditional front, rear, day-running, stop and turn lights to make their vehicles stand out in the market. LEDs are now appearing in side markers, license plates, brand logos, welcome lights, and ambient lights.

To drive these LEDs, you must consider:

- The accuracy of the current so that the homogeneity of the LEDs are much better.
- The changing brightness of the LEDs, thus requiring some kind of dimming.
- The diagnosis and protection of the LED open/short circuit, as well as thermal protection, since safety is always a key concern in automobiles.
- How to improve energy efficiency.

LEDs have traditionally been driven by discrete solutions. Figure 1 shows three typical options: an operational amplifier (op amp) (option 1), a bipolar configuration with the power directly connected to the car battery (option 2) or some type of shunt regulation (option 3).

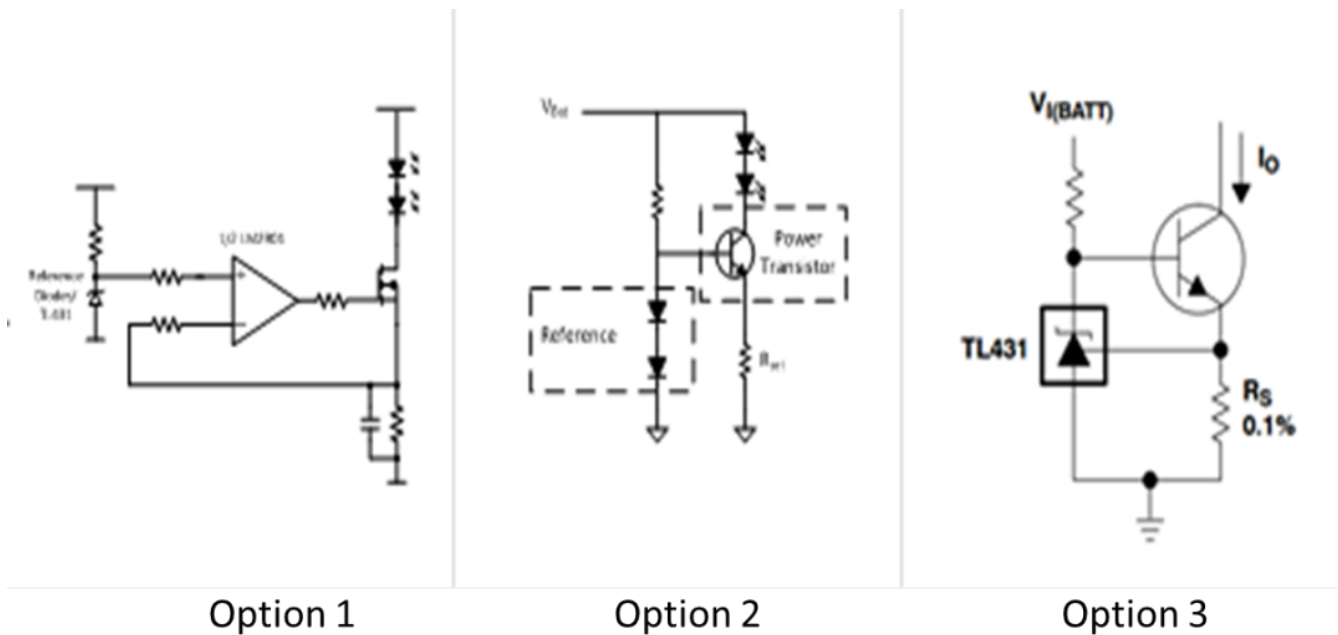


Figure 1. Typical Discrete Solutions to Drive LED

Let's take a look at option 1 first, an op amp driven from the low side. An op amp enables you to achieve relatively high accuracy (<10%) and dimmable LEDs are also possible. With this solution, however, it's difficult to achieve the diagnostics for LED open and short circuits. And the dropout voltage is as high as 1V, which is not very energy-efficient.

Option 2 is also popular and consists of diodes and a N-type P-type N type (NPN) transistor. This solution is simple and cost-effective, but the accuracy is only about 20%, which is far from enough. The dropout voltage could be as high as 1.2V, making this solution's efficiency even lower compared to option 1. Again, no

diagnostics are available for LED open and short circuits, and no pulse-width modulation (PWM) dimming is available. This solution is really too old for today's designs.

Option 3 is popular in applications that require very high output accuracy (<5%). The dropout voltage is extremely high (up to 3V). No diagnostics or PWM dimming are available for this solution; thus, adoption of this option is narrow and the trade-offs are huge.

Every solution has its advantages and disadvantages, but compared to discrete solutions, a low-cost monolithic solution lowers system-level component counts and significantly improves current accuracy and reliability. The TPS9261x-Q1 family shown in [Figure 2](#) is designed just for this purpose.

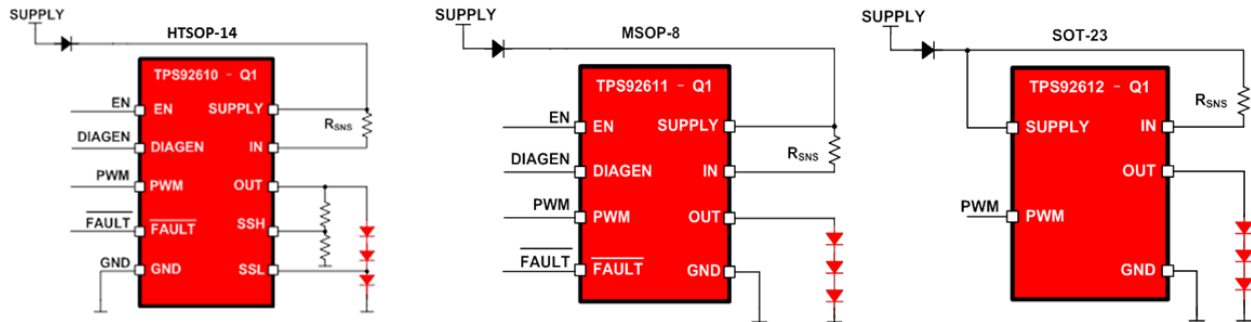


Figure 2. TPS9261x-Q1 Simplified Circuit

The TPS92610-Q1 device is a single-channel high-side LED driver operating from an automotive car battery. It is a simple and elegant solution to deliver constant current for a single LED string with full LED diagnostics. The accuracy is as high as 7%, which is adequate for most applications.

The TPS9261x-Q1 has different package options, from small outline transistor (SOT)-23, MSOP-8 up to thermally enhanced thin shrink small-outline package (HTSSOP)-14 to support different output power levels. With this family of single-channel automotive LED drivers, you can now say goodbye to discrete solutions.

Additional Resources:

- Read this blog post [“Drive LEDs in virtual reality applications”](#)
- Learn more about TI's large [LED driver portfolio](#).
- Check out the the body electronics and lighting portfolio [here](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated