




In [part 1 of this series](#), I discussed the concepts of low-side or high-side monitoring and current flow directionality. In this second installment, I will discuss “how” the current information is used.

What do I mean when I say “how”? A current-sense amplifier measures the current value, and in some cases can also calculate the power. In some cases, the amplifier can compare the current value to a threshold, but it cannot make a decision about what the value means and what the system should do about it.

The output of a current-sense amplifier typically has one of three uses in the signal-conditioning chain, listed below.

1. The output can act as feedback to control a specific action of the next portion of the circuit.
2. It can go into a system microcontroller (MCU) that will make systemwide decisions based on the current level.
3. It can act as an interrupt to notify a controller that a specific threshold has been exceeded, without the controller caring about the actual value.


The first use of a current-sense amplifier output is leveraging the current level as feedback into other portions of the circuit, as shown in [Figure 1](#). In this case, an analog output device such as the [INA210](#) or [INA282](#) will most likely offer the best type of solution. The voltage output feeds into the input pin of the device that needs the feedback. An example of this is regulating a light-emitting diode (LED) with a constant current regulator. The current fed into the LED is measured with a current-sense amplifier, and that output goes into the feedback pin of the regulator, such as the [TPS54218](#), a 2.95-V-to-6-V-input, 2-A synchronous step-down SWIFT™ converter.

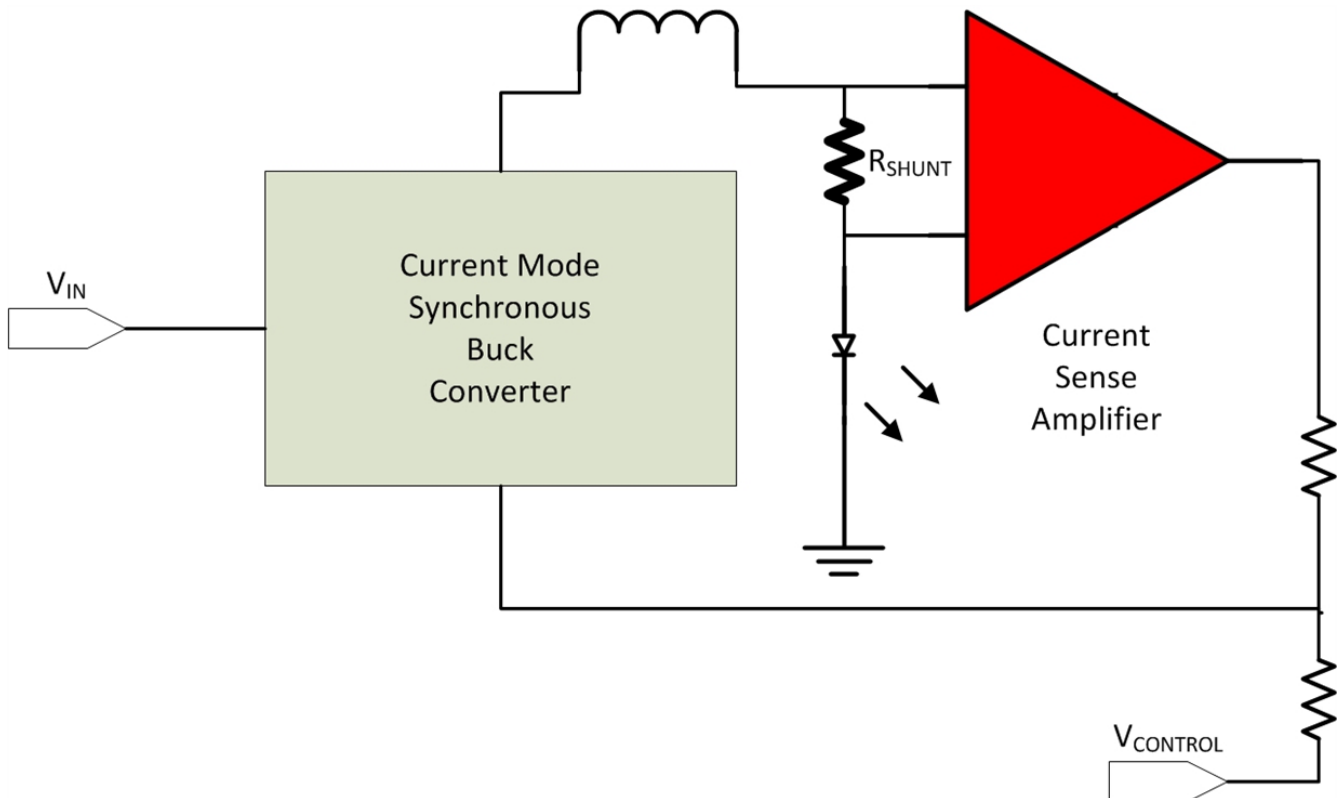

**Figure 1. Current-level Output Gives Feedback to Control an Action in Other Parts of the Circuit**


The second and most common use case is to provide the current level information to a controller that will then control other aspects of the system based on the level, as shown in [Figure 2](#). For example, the current system's current level may be used to adjust fan speed to match the required cooling to the heat being created. The current level can also adjust the clock speed, at which a high-performance integrated circuit (IC) is operating to balance the performance versus the heat.

While the analog output devices referenced above may offer all of the performance needed for this use case, there needs to be an analog-to-digital converter (ADC) for the controller to use the data. Many MCUs offer integrated ADCs that can do this job. However, using a digital-output device such as the [INA226](#) or [INA230](#) may allow the use of a lower cost MCU or free up the integrated ADC to perform other functions. In addition, many of these newer digital-output devices offer an alert functionality that can allow the MCU to ignore the current measurement system until a certain threshold is reached. Once the alert triggers the MCU, it then starts monitoring the current to determine the next steps.

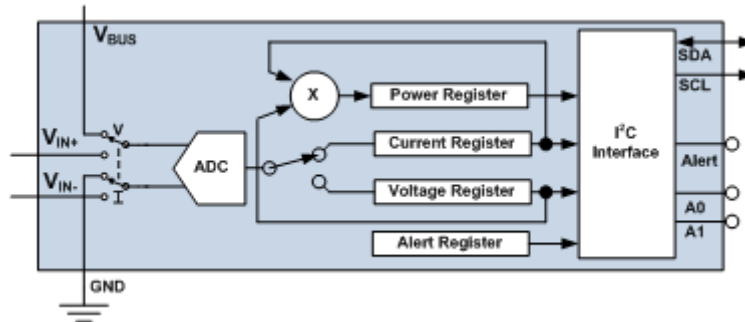

**Figure 2. Current Level Feeds into an MCU, Which Controls Other Aspects of the System**

This brings us to the third common use case: simple alerts that trigger when an overcurrent threshold is exceeded, as shown in [Figure 3](#). (Think eFUSE technology.) A device like the [INA300](#) is a simple-to-implement, small-footprint, low-cost, overcurrent comparator that supports this type of alert-only use case.

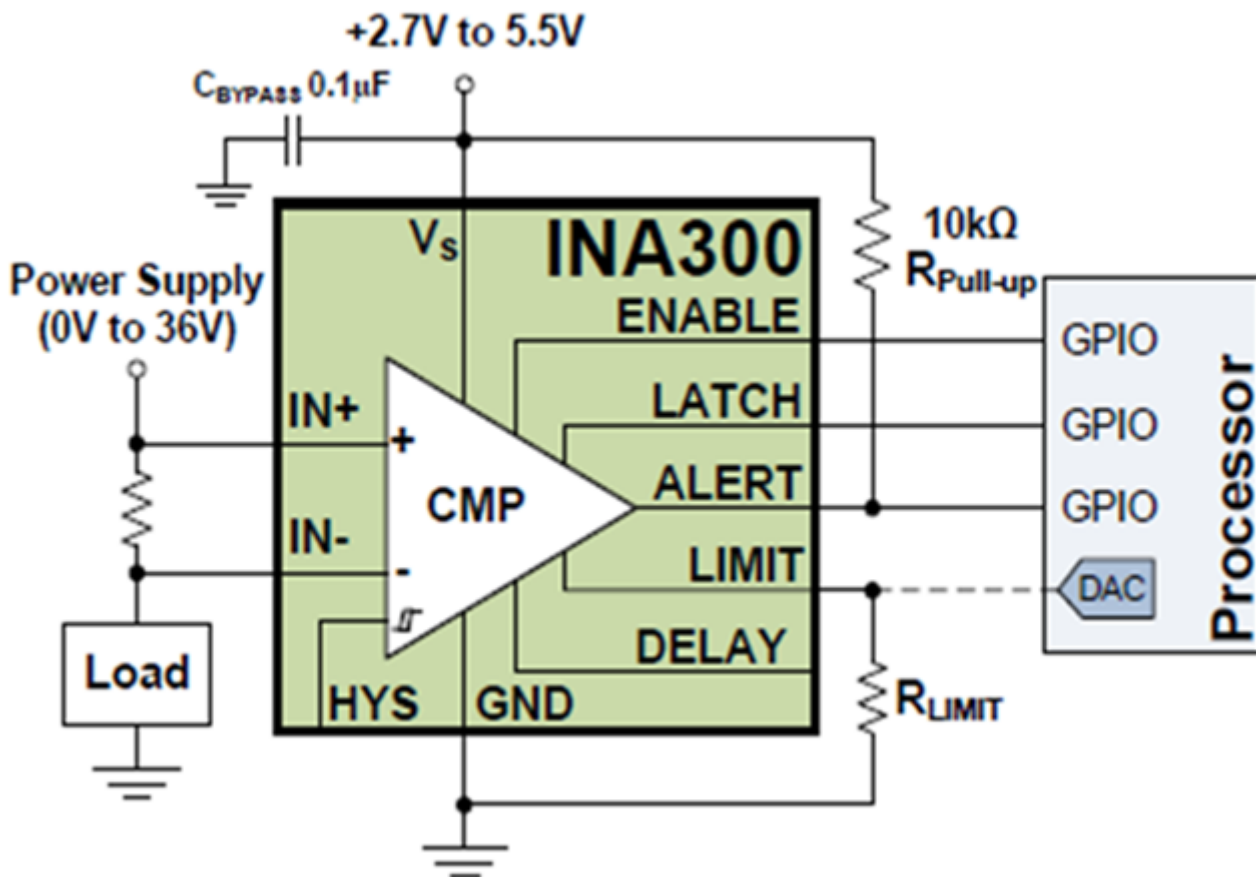

**Figure 3. Current Level Serves as an Interrupt, Notifying a Controller That a Specific Threshold Has Been Exceeded**

I hope you now understand the three main ways that current information is used in current-sense amplifiers. In the next installment, I'll discuss how the current range affects device-selection criteria and basics on calculating the value of the shunt resistor needed.

#### Additional Resources

- Learn more about [TI's broad current-sense amplifier portfolio](#).
- Watch this [video](#) about how the INA300 is optimizing overcurrent detection.
- Check out these related TI Designs reference designs:
  - [High-Voltage 12V-400V DC Current-Sense Reference Design](#).
  - [Current-Shunt Monitor with Transient Robustness Reference Design](#).
  - [EMC-Compliant High-Side Current-Sensing Reference Design with Overvoltage Protection](#).

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated