




Precision Low-Level Measurement Design

1

REAL WORLD SIGNAL PROCESSING™






Overview

- Hardware
 - Tradeoffs
 - Demonstrations
- Software
 - Firmware design considerations
 - Signal processing in software

2

REAL WORLD SIGNAL PROCESSING™

 TEXAS INSTRUMENTS

This seminar will discuss design tradeoffs and techniques for analog-to-digital data acquisition circuits for low-level, high-precision signal measurement.

Everything begins in the hardware design. We will discuss several common design tradeoffs for these kinds of systems, and offer advice on making the right choice in your own designs. This seminar will not consist in talk only: we will also back up our assertions with demonstrations of real hardware. We will compare different designs, and, in some cases, show designs that don't work, so that you'll know what not to do.

Modern digital data acquisition systems invariably use some kind of microprocessor. This means that you have to write firmware. Most people know (or think they know) how to write good firmware for SAR-based conversion systems, but delta-sigma-based systems often require a different way of thinking. If you know the basics of interfacing to a delta-sigma converter, you can avoid a great many problems in your final system.

Even if you're only designing the hardware, and leaving the firmware to the CS guys, you should still pay attention to the software section: your programmer has to live with your hardware, and if you make his job easier, you'll make your own job easier in the process.



Measuring Noise

- RMS noise
 - Usually calculated from standard deviation of a series of samples
 - Used to calculate ENOB
 - Does not depend on noise type
- Peak-to-peak noise
 - Gives “display resolution”
 - Estimates typically assume that the noise is Gaussian

3

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

In the demonstrations that follow, we will evaluate the noise performance of several classes of data acquisition circuitry. Although it is not the only figure of merit for a measurement system, noise performance, as we will see, has a great deal to do with its performance.


Noise is the uncertainty of a measurement. In the days of 8 and 12-bit converter ICs, not as much attention was paid to this important aspect of electronic measurement, because it isn't at all difficult to make an 8 or 12 bit converter noise-free.

Ironically, it is low-noise delta-sigma converters that have brought this topic to the attention of many designers. Many engineers, used to getting steady values from their low-resolution converters, are dismayed when they find the output value of a 24-bit device fluctuating madly in its least significant bits. It's not hard for an engineer, long used to working with low-resolution devices, to feel a bit cheated when he finds out that a 24-bit device isn't really 24 bits when noise is taken into account! Unfortunately, the laws of physics make 24 bit noise-free resolution an extraordinarily difficult thing to obtain. Because of this, we need a way to measure and evaluate noise.

In many AC measurement applications, such as audio and radio circuits, noise measurement techniques are well known, and typically done by analyzing the measured signal in the frequency domain. An FFT taken of a high-speed converter's output provides a useful estimate of its noisiness. The figure measured here is called *signal-to-noise ratio*.

In low-frequency measurement applications, however, the FFT isn't nearly as useful, since we are measuring signals near DC. What is wanted instead is a measure of how certain we are of the value reported by the converter. We measure this by making many successive conversions with a single DC input applied to the converter and calculating statistical functions over the data.

The two most common measurements of certainty for an ADC are *RMS noise* and *peak-to-peak noise*. RMS noise is the better figure-of-merit for an ADC, since it does not depend on the kind of noise. Peak-to-peak noise calculations are not as mathematically rigorous, and often assume that the noise is Gaussian in distribution, but they are essential for applications where the “flicker” or constancy of a displayed value must be known, such as weigh scales and thermometers.



Measuring Noise

Calculating RMS noise

Variance of a set of N samples:

$$s^2 = \frac{\sum_{i=0}^N (x_i - \bar{x})^2}{N}$$


Standard deviation:

$$s = \sqrt{s^2}$$

Effective number of bits (if samples are ADC codes):

$$\text{ENOB} = M - \log_2 s$$

4

REAL WORLD SIGNAL PROCESSING™


The equations in the slide are used to calculate RMS noise from a set of samples taken from the ADC being evaluated. The samples are assumed to be conversions made of the same DC input value.


The first step is to calculate the mean, or average, value of the sample set. This is shown above as \bar{x} with a bar above it.

Next, the set's variance is calculated. Variance is a measure of the average deviation of each sample from the average of all the samples. This is calculated by averaging the squares of the differences of each sample from the average. In the equation shown, N is the number of samples, and x_{i-1} is the i th sample in the set.

Standard deviation is variance expressed in a "standard" form, i.e., in the same units as the samples. This is simply the square root of the variance. (Note that standard deviation is a root-mean-square of the deviations from the average.)

We can convert the standard deviation into several forms. The standard deviation itself is the RMS noise of the sample set in the same units as the sample set. If the samples are voltages, the standard deviation gives the RMS noise in volts, and if the samples are ADC codes, the standard deviation is the RMS noise in ADC codes (often called *counts*).

A increasingly common measure is *effective number of bits*, or *ENOB*. This is the number of bit positions in each ADC code which are numerically unaffected by RMS noise. As shown above, it is the ADC's word-length M minus the base 2 log of the standard deviation.



Measuring Noise


Peak-to-peak noise

For Gaussian noise, > 99% of samples occur in the interval:

$$(\bar{X} - 3.3\sigma_X, \bar{X} + 3.3\sigma_X)$$

Then our rule of thumb is:
 Peak-to-peak noise = 6.6 * RMS noise

6

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

It is extremely useful to have some kind of certainty of how constant the numbers emitted by your system will actually be. A user of a weigh-scale expects that if he places a rock on the platform, the display will not return fluctuating values, since the mass of the rock does not fluctuate over time (at least, not much).

Unfortunately, high-resolution converters typically have noise imposed on their output signals. It follows that if you calculate mass based on all 24 bits of a 24-bit converter's output, the mass you calculate will appear random. Your users may not appreciate this, and may question (perhaps unfairly!) your product's accuracy.

RMS noise tells you how random your samples are, but it does not tell you how "clean" your display will be. A 24-bit converter with an ENOB of 18 bits will typically show fluctuations all the way up to the 15th least-significant bit. The number of bits which typically do not change are called "noise-free". It is from this number of bits that you may need to calculate your instrument's output.

(Note: Many people estimate noise-free bits by watching the converter's binary output and counting the number of bits that appear to be changing, but this can be very misleading. Suppose you have a 24-bit twos-complement converter that randomly returns one of two values: -1 and 0. This is a very quiet converter by anyone's reckoning, but if you watch the binary output, you will see that *all* of the bits fluctuate! Similar arguments apply to any kind of binary converter around major carry transitions. You cannot measure noise-free resolution merely by watching which bits are changing – you must analyze the sample set.)

All kinds of noise are not the same. One way to describe a random set of numbers is through its *distribution*. The distribution describes how the various numbers are distributed around a certain value, generally the mean of the set. Put another way, a distribution tells you how likely it is that a random value will take on a given value. In measurement applications, it turns out that the Gaussian distribution (the well-known “bell curve”) is a reasonable approximation in a surprising number of cases. A great many electrical engineering formulae dealing with noisy signals therefore are constructed on the assumption that the noise follows the Gaussian distribution.

This is important because it affects our view of peak-to-peak noise. Suppose that we *know* that our noise is Gaussian. We could then conclude the following:


- The majority of the readings occur very close to the average of the sample set.
- 2/3 of the readings we take will be no further away from the average than the standard deviation.
- A minority of the readings will occur some ways off from the average.
- Greater than 99% of the readings will be no further away from the average than 3.3 times the standard deviation of the sample set.
- Less than 1% of the readings will be further away from the average than 3.3 times the standard deviation of the sample set.

Since very few of the readings will assume highly deviant values – we define “highly deviant” as any value that is further from the average than 3.3 times the standard deviation – we ignore them: we literally pretend that they will never occur, and we can then define the peak-to-peak range of a noisy sample set having a Gaussian distribution. Peak-to-peak noise is then very simply RMS noise times 6.6.

It may seem that we have taken a lot of trouble to get such a simple formula, but it is vitally important that you understand the sweeping assumptions behind it. Unless you know that your noise is Gaussian, or extremely close, the formula is a rule-of-thumb only, and you cannot know what your noise looks like unless you actually measure its distribution.

This is important enough to repeat: *the formula above is a rule of thumb*. You should *always* verify peak-to-peak noise in a real design.

The discussion above should also show you why converter manufacturers very seldom publish peak-to-peak noise in their datasheets: it's simply too hard to guarantee, because it's impossible to know what the distribution of your noise in your application will be. RMS noise measurements have fewer uncertainties.



Resolution

- Often expressed in counts or decimal digits
- Internal resolution is calculated from RMS noise
- Display resolution is calculated from peak-to-peak noise

8

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS


We are now ready to discuss the topic of resolution. Resolution is a way of describing the smallest interval your system can reliably measure. A system with 60,000 counts of resolution can accurately tell you what a measurement is out of 60,000 possibilities.

Two kinds of resolution, called internal resolution and display resolution, are typically referred to. *Internal resolution* is calculated from the RMS noise of your measurement. *Display resolution* is the number of digits you can display with a reasonable confidence that they will not fluctuate; this is calculated from peak-to-peak noise.

The resolution your designs achieve is not directly related to the resolution of your ADC. It is possible to build systems having 65,000 counts of resolution from 12-bit converters, which have, at best, only 4,096 counts of resolution. It is also usually the case that systems built using a 24-bit converter, which can output any of over 16 million different codes, will typically not have anything like 16 million counts of resolution.

Clearly, the word-length of your converter doesn't necessarily indicate much about how your system will perform. In any measurement system, there is a seemingly endless parade of "gotchas" and details which conspire against your goals for precision, and the length of this ugly list only increases as your requirements become more stringent. A good IC can help fight off some of these nasties, but it can never deal with all of them.

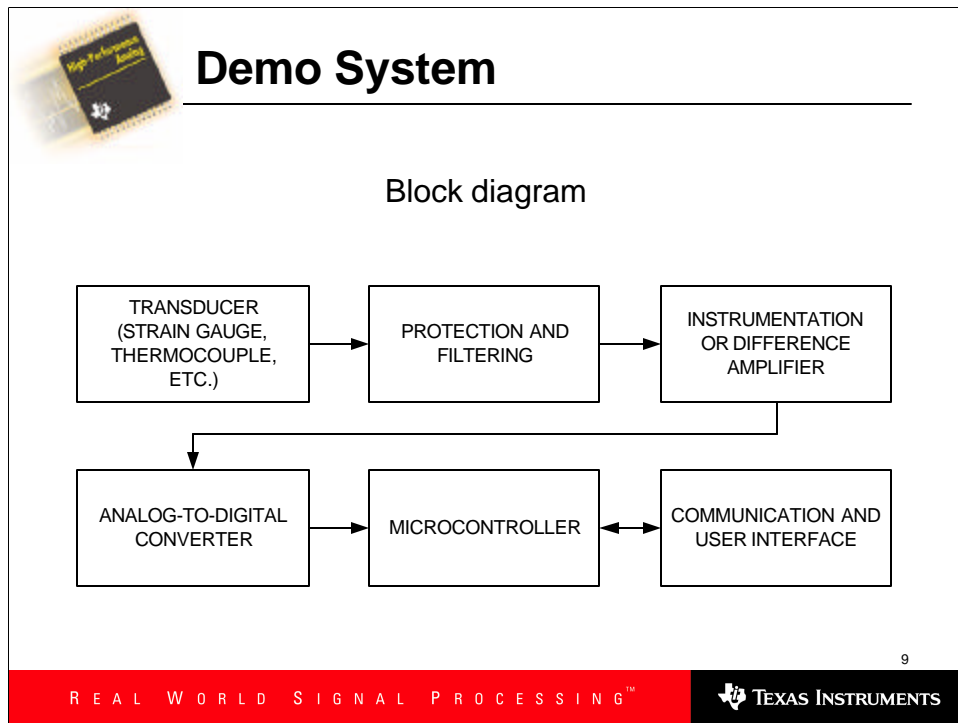
The display and internal resolutions of your design represent the cold, hard truth about how well your system performs. It's probably no good bragging that you used a 24-bit converter if your system only has 1,000 counts of resolution (then again, perhaps your measurement is extremely difficult to make!).




The demonstrations in this portion of the seminar will compare the merits of various data acquisition circuits. All of the circuits we will demonstrate are of the same basic type, having the block diagram shown in the slide.

Each system has:

- An input stage, consisting of protection circuitry and amplification. In some circuits, the amplification is incorporated into the A/D converter.
- An A/D converter. We will show a SAR converter, but most of the systems demonstrated here will use delta-sigma converters.
- A microcontroller, whose task is to collect data from the converter, possibly process the data collected, convert it to a useful form, and make it available to the user. In our test system, the data will be shown both using LabView and through a user-interface board. LabView will be used to display and sometimes analyze the data taken; the user-interface board is representative of hardware used in a real data-collection instrument, and we will discuss it in the section on Software.

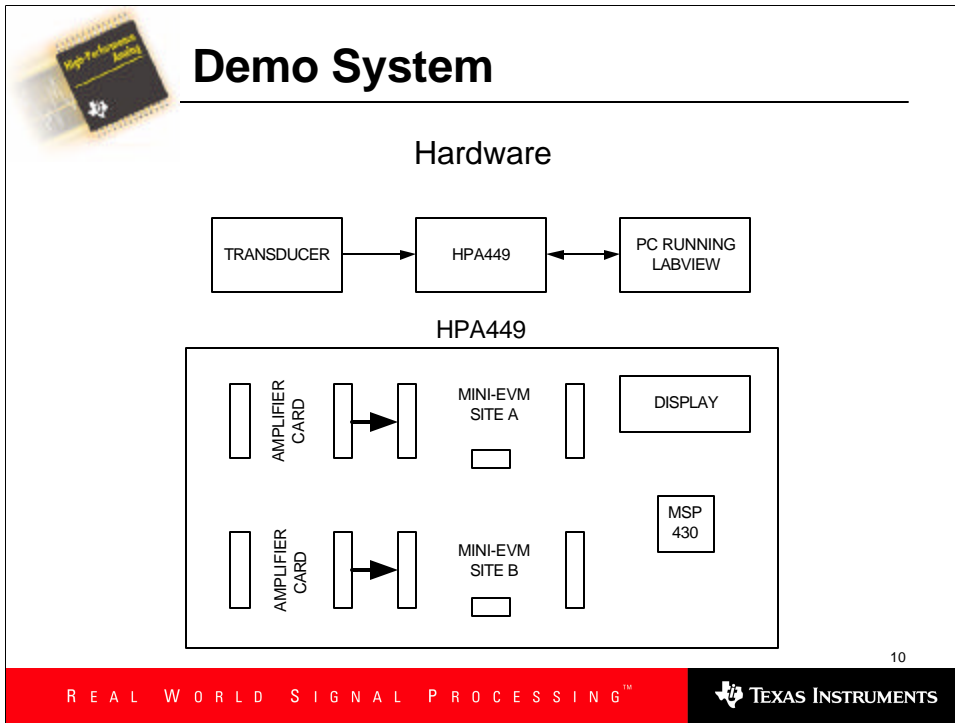

We will use the same microcontroller and user interface portions of the circuit for all of the demonstrations. Because of this, we have designed the system to be modular. All of the circuits are in a standard form-factor, and can be connected to a *motherboard*. For this seminar, we will use the HPA449 motherboard from SoftBaugh. This motherboard uses the Texas Instruments MSP430F449 microcontroller. The capabilities of this microcontroller are quite representative of the processing capabilities found in many data acquisition systems.

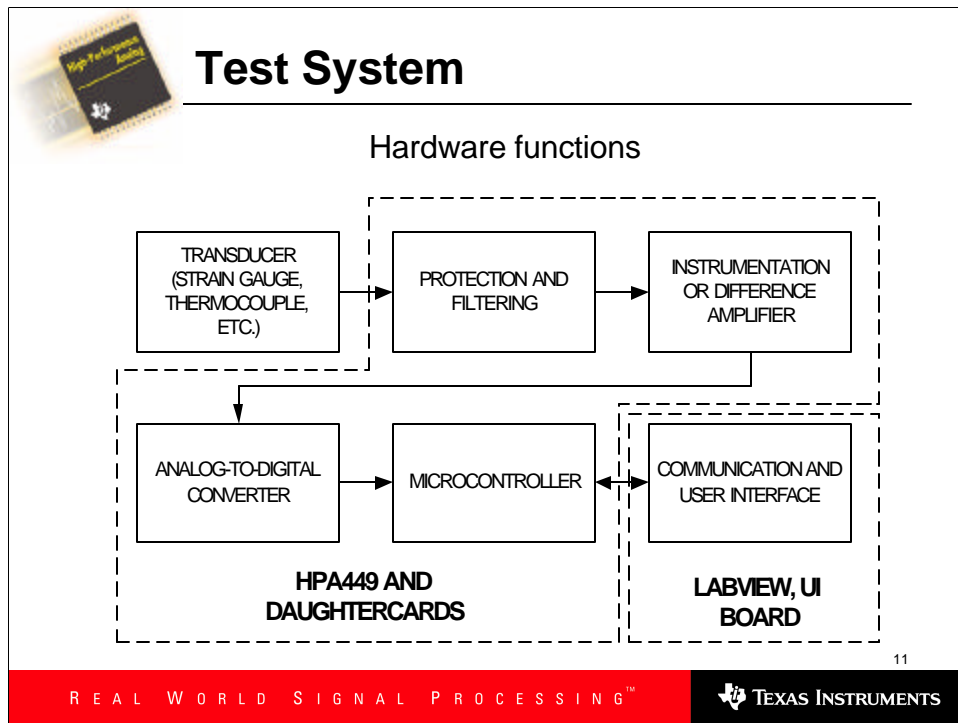

This diagram shows how the HPA449 will be used in the demonstrations.

The HPA449 can host amplifier cards and mixed-signal cards. Mixed-signal cards have connections for both analog and serial digital signals (all of the converters we will look at have serial interfaces), and contain the analog-to-digital converter. When an external amplifier is needed, this will be hosted on an amplifier card.

Collected data is displayed and/or analyzed in LabView, and optionally on the user-interface board (UI Board). The system can be controlled through either interface.

We will generally use a differential-output transducer, such as a strain gauge, for the measurement device.



Comparison of Approaches

- First system: the traditional approach
 - SAR + difference amplifier
- Second system: low-cost delta-sigma
 - Direct connect 16-bit delta sigma converter with medium gain PGA
- Third system: cost + performance balance
 - Direct connect 24-bit delta sigma converter with high gain PGA

12

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

We will now demonstrate some typical circuits. In particular, we will contrast the “traditional” approach using a SAR with two different delta-sigma based setups.

The first system will show a traditional circuit using a 16-bit SAR converter, the ADS8325, with a front-end difference amplifier based on the auto-zeroed OPA335.

The second system will show an extremely low-cost delta-sigma converter, the ADS1110, used without a front-end amplifier.

The third system will demonstrate a 24-bit delta-sigma converter, the ADS1241, which is designed for bridge sensing.

Demonstration

**The traditional approach:
ADS8325 with differential amplifier**

The diagram illustrates a circuit where a strain gauge is connected to an OPA335 differential amplifier. The amplifier is configured with a gain of 256. The output of the amplifier is connected to the ADS8325 SAR ADC. The ADS8325 is connected to an MSP430 microcontroller (ON HPA449) via SPI. The negative input of the ADS8325 is grounded. The positive input of the ADS8325 is connected to the output of the OPA335. The OPA335 is a differential amplifier with a gain of 256. The strain gauge is connected to the OPA335. The positive input of the OPA335 is connected to one terminal of the strain gauge, and the negative input is connected to the other terminal. The positive input of the OPA335 is also connected to a +VE supply. The negative input of the OPA335 is connected to ground.

13


REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

In our first demonstration, we show an ADS8325 SAR ADC reading a strain-gauge through an input amplifier. An input amplifier is required because the ADS8325's input is not truly differential: the negative input terminal is not allowed to exceed the voltage of the positive input terminal, and has a limited input range. In our setup, the input is grounded.


Even if an input amplifier were not required – i.e., if the ADS8325 had a truly differential input – it would still be beneficial because of the ADS8325's limited dynamic range. The ADS8325, like most SAR converters, cannot read very small signals directly with good accuracy. The input amplifier scales the millivolt-scale output of the transducer to near the ADS8325's full range.

Before the advent of industrial delta-sigma converters, small-signal measurements were nearly always made with a circuit like this. The alternative was to build a custom ADC circuit, which can still be an expensive and time-consuming proposition for this kind of application.



Demonstration

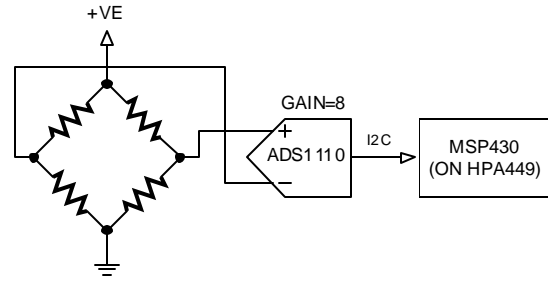Lowest cost: ADS1110 with direct connection



14

REAL WORLD SIGNAL PROCESSING™


TEXAS INSTRUMENTS

The ADS1110 is a very low cost 16-bit delta-sigma converter. It has a fully differential input, a built-in low-drift reference, a self-calibration facility, and a built-in programmable gain amplifier which can amplify the signal up to eight times. Since the input is fully differential, we can connect the sensor directly, without an amplifier.

The ADS1110's reference is fixed at 2.048 volts, and since it is a differential-input device, the voltages it reads can range up to $\pm 2.048\text{V}$ differentially. (Note that you can *not* apply negative voltages on either input. Doing so usually damages the device.) If the PGA is turned up to 8, the input range becomes $\pm 0.256\text{V}$.


$\pm 256\text{mV}$ is still much greater than the output of the transducer, but we can still get fairly good performance from this circuit. The real advantage of this configuration is its extremely low cost: other than the ADS1110, which is itself extremely inexpensive, only a few protection components are required in the converter section.

This circuit is the lowest-cost configuration we will demonstrate. Cheaper circuits exist, but they do not offer anything like this level of precision, and are arguably not worth the trouble needed to design them.



Demonstration

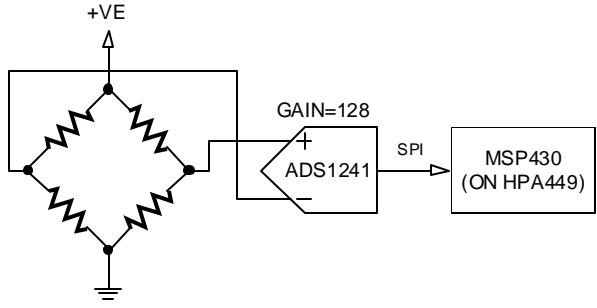High resolution:
ADS1241 with direct connection



15

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

The ADS1241 is a 24-bit delta-sigma converter with several features designed for bridge-sensor measurement. This demonstration shows that it can achieve even higher resolution than the ADS1110 with only a modest increase in cost. This circuit is still cheaper than the ADS8325-based design.

The ADS1110 has a PGA with gain of up to 8; the ADS1241's PGA has a gain of up to 128. This means that its range can be very much closer to the actual output range of the transducer. The ADS1241 can also filter out 50 and 60 Hz signals appearing on its input – a very important feature for many industrial applications. Despite this, the ADS1241 is still a relatively low-cost device.

The ADS1241 is not the highest-performance bridge-measurement ADC on the market, but for what it offers, it comes at a very modest price. Devices like the ADS1241 offer a good balance between high performance and low cost.



Comparison

Approach	Technology	Device	Performance	Cost
Traditional	SAR + amplifier	ADS8325 + OPA335	Decent	Highest
Low cost	Delta-sigma	ADS1110	Decent	Lowest
Integrated	Delta-sigma	ADS1241	High	Fairly low

16

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

The ADS8325-based demonstration represents the “traditional” approach, using a SAR. Although its performance is not bad, there’s not much room for improvement with this approach, and the cost is high.

The ADS1110 shows what even a very low-cost delta-sigma device can do. Its performance isn’t much worse than the SAR, but the circuitry is incredibly simple.

The ADS1241 is an example of a device designed for the job. Its performance is much better than the other two approaches, and its cost still comes in at under that of the ADS8325-based circuit.



External vs. Internal Amplification

- External amplifiers
 - Usually required when the ADC has no on-board amplifier
 - Can be expensive
- Internal amplifiers
 - Available on many delta-sigma ADCs and some SARs

17


REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

We will now compare two amplification approaches: external and internal.

Many designers are in the habit of placing an amplifier in front of ADCs, whether or not the ADC has on-board gain. This is not always the best approach. Many high-resolution delta-sigma ADCs can actually perform better without an external amplifier. Eliminating it not only can improve performance, but save on board space, parts count, and cost.

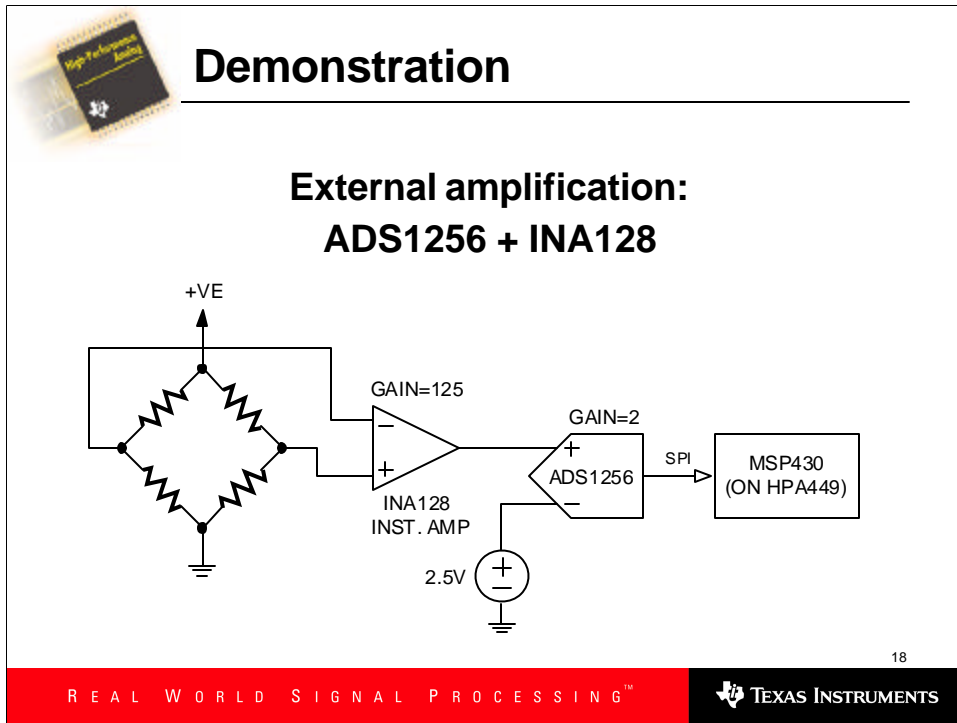The next two demonstrations will also demonstrate one of TI's highest-performance delta-sigma converters, the ADS1256. This device (and its companion, the single-channel ADS1255) offers both extremely low noise at low data rates and good performance at higher data rates.




The ADS1256 is a 24-bit delta-sigma converter. It is among the lowest-noise devices available today, and has a large number of features that make it an excellent choice for high precision transducer measurements. Like nearly all delta-sigma devices designed for small-signal measurement, it has an onboard PGA. The PGA in the ADS1256 has a gain of up to 64.

In this demonstration and the next, we will compare the performance of the ADS1256's PGA with that of a high-quality instrumentation amplifier IC, the INA128.

The circuit demonstrated here shows the INA128 set for a gain of 125, and the ADS1256 set for a gain of 2. The combined gain of 250 gives the circuit a measuring range of +/- 20mV.


The ADS1256 is set for a gain of 2 because its gain-of-1 input range is +/- 5V differentially. Applying this kind of input would require a differential-output amplifier. Instead, we set the ADS1256's negative input to 2.5V (the same as the reference), and make the positive input swing from 0V-5V. The ADS1256 reads this as +/- 2.5V. Gaining this up by two results in a +/- 5V signal, which is the ADS1256's full range with a 2.5V reference.

At a gain of two, the ADS1256 has almost exactly the same noise performance as it does at a gain of one, so the comparison is still valid.



Demonstration

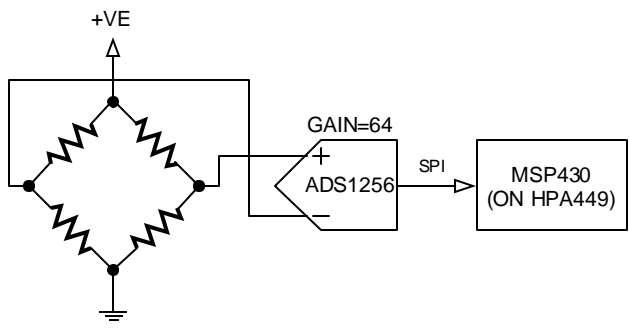Internal amplification: ADS1256 at gain of 64




19

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

We now connect the ADS1256 directly to the transducer. The ADS1256's on-board PGA can only gain up to 64, so our input range is now $\pm 78.1\text{mV}$. This increased input range means that we have lost two bits, or 12dB, of dynamic range, since we can no longer use the ADC's full measurement range.

Fortunately, it's not all bad news. We can now use the converter's self-calibration facility instead of its system calibration facility (we will see later why this is important). The circuit is also less complex, and cheaper, than the previous circuit. Finally, the noise performance is still comparable to the previous circuit, even with the loss in dynamic range.



External vs. Internal Amplification

Approach	Gain	Cost / complexity	Calibration
Internal	Lower	Low	Simple
External	High	Higher	More difficult

20

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

Which approach should you use?

If component count is important, and the ADC's built-in amplification offers performance that's good enough, then use it. Remember that gain alone isn't everything. External amplifiers have problems of their own, and these problems may cost you in noise performance and calibration requirements.

External amplification is a good approach for many applications. Specially-designed instrumentation amplifiers can outperform on-board PGAs in some applications, especially when very high gain is required. However, you will usually have to consider the complexity of calibration, which sometimes requires additional hardware.

Finally, don't forget that you can use a "two-stage" approach: nothing prevents you from using the ADC at a high gain together with an external amplifier. You may be able to get the best performance from this configuration in high-gain applications.

In summary, don't add an external amplifier unless you really need to. Modern delta-sigma ADCs often do very well without one.



RFI Immunity

- RFI can cause measurement errors
- Easy to test for
- Often costs only NRE (layout changes) to improve immunity
- In some locales, it's the law!

21


REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS


There's no question that there is more radio-frequency energy around us today. Radio-frequency interference, or RFI, can do all sorts of unexpected things to an electronic circuit. With more and more wireless and RF systems in use, this isn't something you can afford to ignore – literally, because in many countries, the law of the land now requires that your systems operate properly even when bombarded by RFI.

In small-signal measurement, RFI contributes to noise, of course, but perhaps more seriously, it can cause offset shifts. When picked up in the system's cabling and by the amplifiers, this RFI can cause your measurement to be noisy at best, and completely wrong at worst.

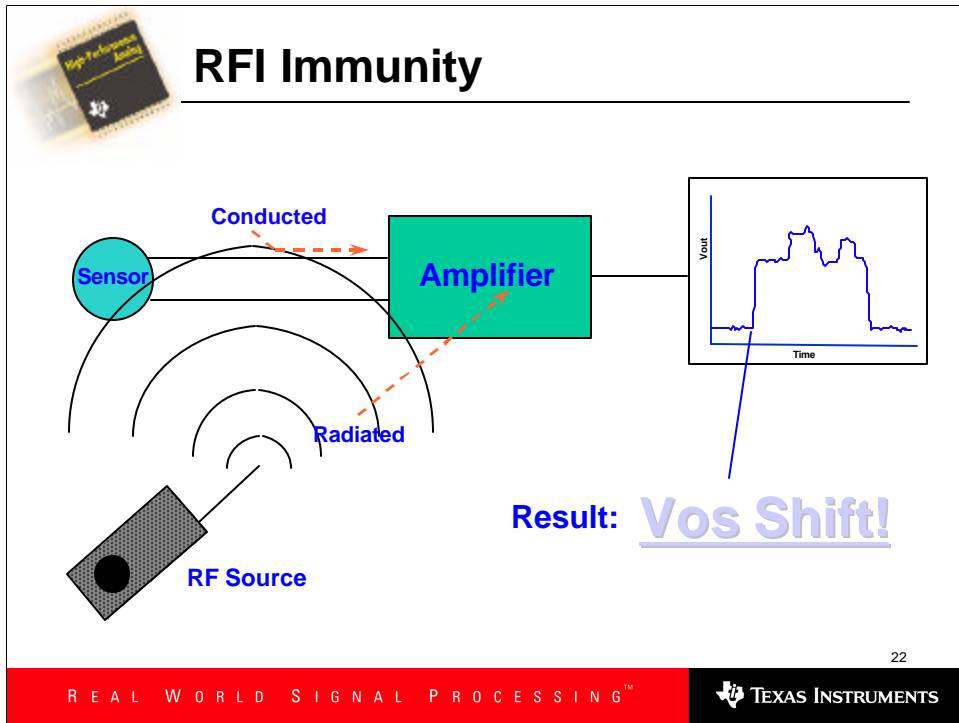Fortunately, RFI immunity is not costly to implement. Very often, it's a mere matter of changing the layout to follow a few rules – rules you should be following anyway in precision measurement applications. The next two demonstrations show how dramatically a simple layout change can affect RFI performance.




Here we show a typical situation. The source, shown here (not coincidentally) as a handheld radio, is shown radiating energy into a system. The system, consisting of a sensor, connecting wires, and an amplifier, picks up the radiated energy in two ways: by conduction, caused by inductive pickup on the connecting wires, and by direct radiation, picked up by the amplifier circuit itself. The result is often a voltage offset shift.

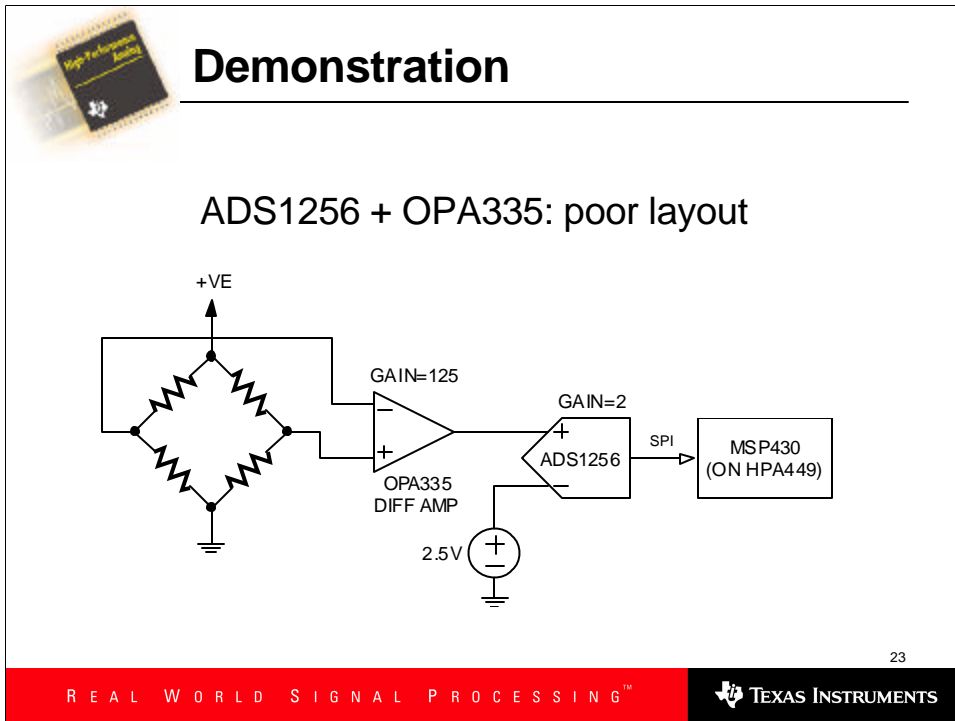

The first system shows how poor layout can cause a circuit to act, unintentionally, more like a radio receiver instead of a measuring device. The “RF generator” is a simple US Family Radio Service walkie-talkie, which operates in the 400MHz range, a very common source of troublesome frequencies.

Note what happens to the measurement when we turn the radio on.

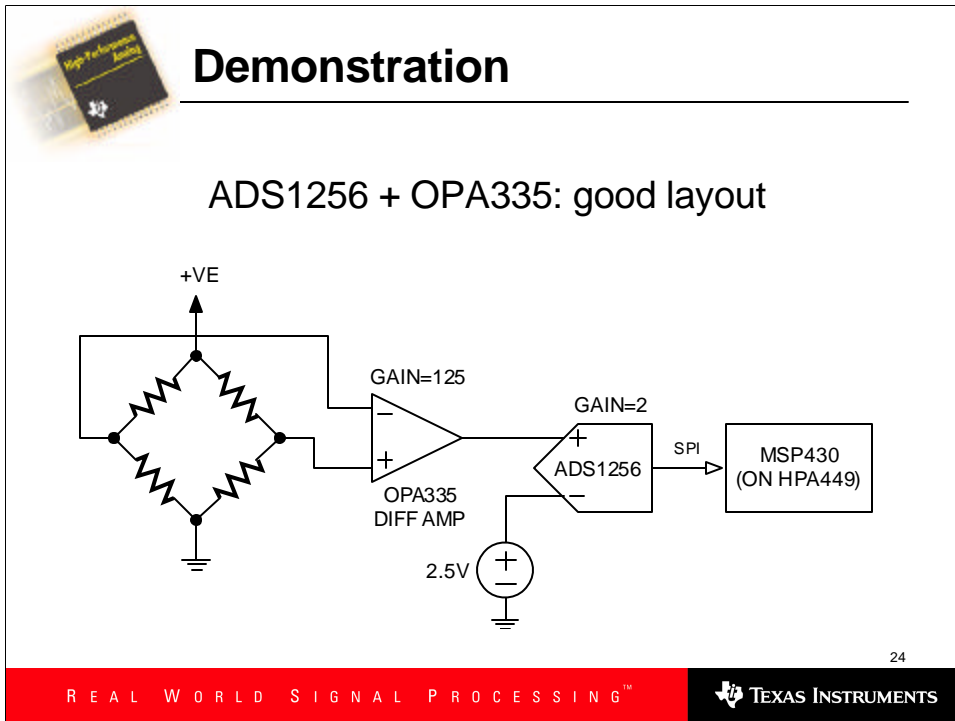The layout used here is not entirely far-fetched. We at Texas Instruments have seen even worse examples in products currently on the market. One high-end weigh-scale we tested measured over 60g, when empty, when this model of radio was turned on three feet away!



The second system uses the exact same circuit – the layouts were generated from the same schematic. Part cost is the same, but this circuit measures the same thing whether or not we turn our “RF generator” on, unlike the previous one.

Remember this simple demonstration, and note that you can easily perform the same test on your own circuits. We highly recommend that you do so!



Temperature Compensation

- Many sensors must be temperature compensated
- Nearly all components act like thermometers!
- Use temperature sensors and firmware to compensate
 - Examples: thermistors, on-board temp diodes, IC temp sensor devices

25

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

Unless you are measuring temperature, you will likely want to perform some kind of temperature compensation in your circuit.


Most sensors, whether intentionally or not, act as thermometers. A strain-gauge drifts with temperature due to a number of effects: the resistance strips have a temperature characteristic, and self-heating caused by excitation can cause the strips to expand, which in turn causes a strain on the gauge, which affects the measurement.

Another source of temperature drift is, of course, the components in your circuit. Resistors, capacitors, and especially anything made of silicon – all are really thermometers, whether you like it or not.

Fortunately, compensating for temperature is not expensive, especially if you are using a microcontroller which can calculate the necessary corrections mathematically. Also, most good IC designers are well aware of temperature effects on circuits – a remarkable amount of their time is spent compensating for them.

To compensate for temperature, you have to know what the temperature is. In temperature compensation, it is usually not necessary to have an extremely accurate measurement of temperature. In some circuits, all that is needed is information about whether the temperature has recently changed by an appreciable amount.


Many kinds of temperature sensors are available. If you have extra channels on your ADC, a simple thermistor can be used to measure the ambient temperature. Some ADCs have temperature-measurement diodes built in to them, as do some microcontrollers – the MSP430F449 used in our demonstrations has one. You can also purchase temperature-measurement ICs, which are precalibrated and ready to use. The TMP100 is an example, and we have included one on our amplifier card.

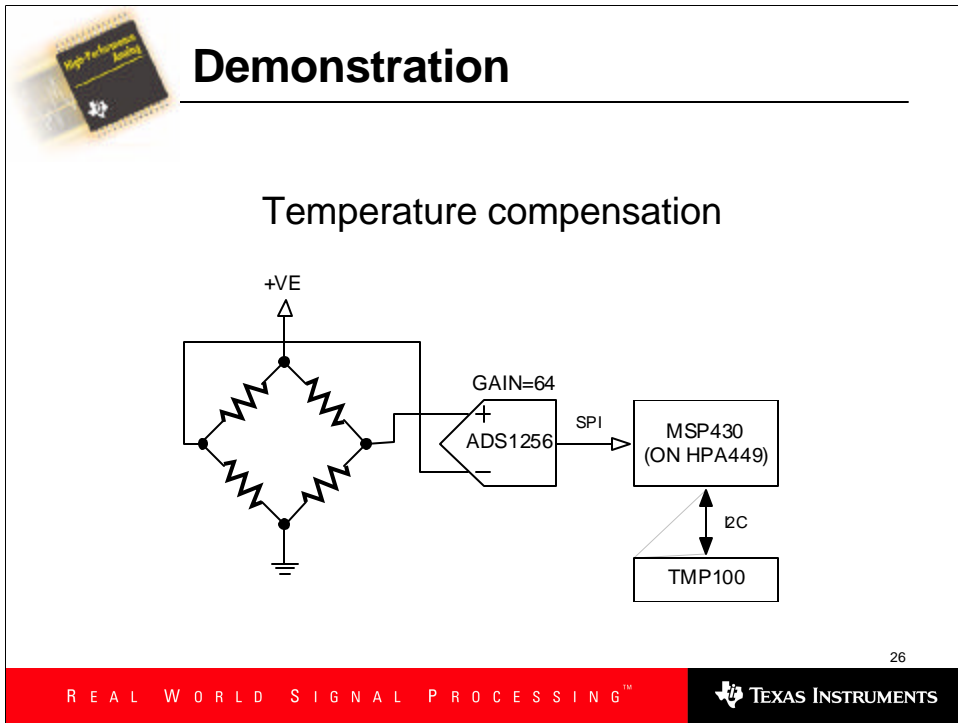

In this demonstration, we use a heat gun to show how temperature can affect a strain-gauge measurement.

The amplifier card has a TMP100 on it. We use this to read the ambient temperature, and this figure is used to compensate the reading from the strain gauge.

The drift of the ADS1256 itself is very low, but the drift of the reference used with it here unfortunately is not. Fortunately, the temperature compensation process also corrects for this.




Ratiometric Measurement

$$\text{code} = \frac{V_{\text{in}}}{V_{\text{ref}}} 2^N = \frac{V_{\text{in}}}{V_E} 2^N$$


$$V_{\text{in}} = \frac{F_{\text{strain}}}{k V_E F_{\text{max}}}$$
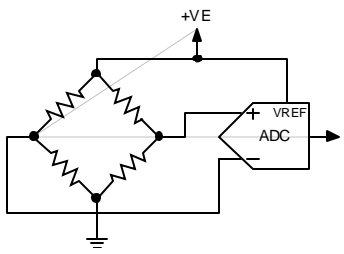
$$\text{code} = \frac{F_{\text{strain}} V_E}{k V_E F_{\text{max}}} 2^N$$



$$\text{code} = \frac{F_{\text{strain}}}{k F_{\text{max}}} 2^N$$

27

REAL WORLD SIGNAL PROCESSING™


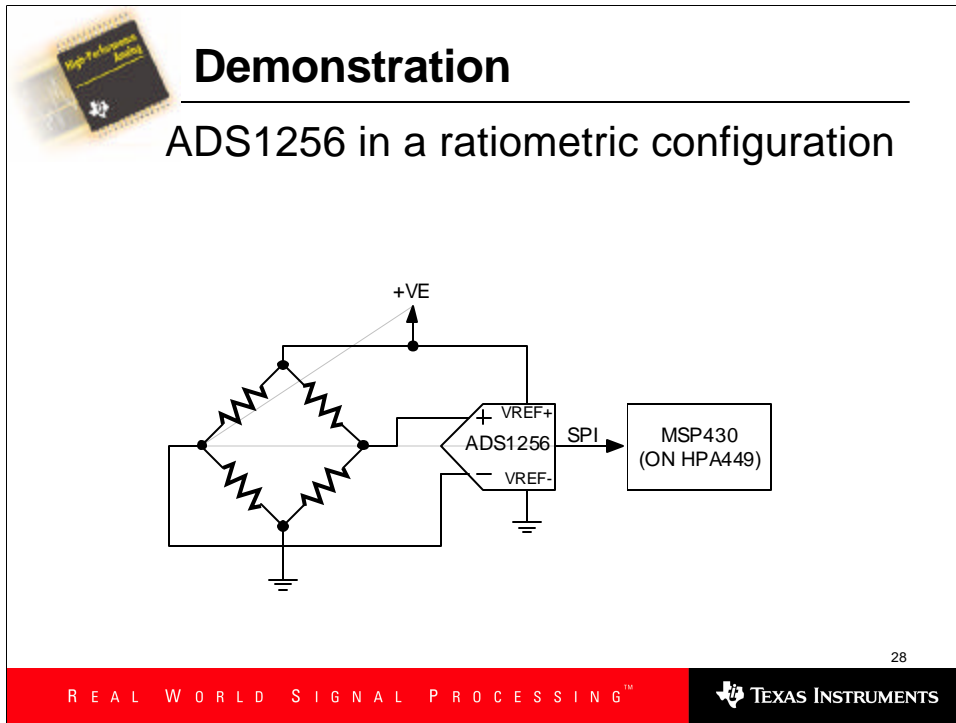
In the previous section, we discussed voltage references; now we will show how you can sometimes get along without one.

In a *ratiometric* configuration, the voltage reference and the bridge excitation are the same, as shown in the schematic. Since the same voltage is used for both excitation and the reference, the reference voltage cancels out, and only the resistances in the bridge contribute to the measurement.

The equations in the slide show the mathematics for a strain gauge. The basic ideal transfer function for an ADC is shown at the top. Since this is a ratiometric configuration, $V_{\text{ref}} = V_E$.

The next equation relates a strain gauge's output to its input. F_{strain} is the strain force, F_{max} is the strain gauge's maximum force, k is the strain gauge's rated output ratio in V/V, and V_E is the excitation voltage.

In the next equation, the strain gauge formula is substituted for V_{in} in the code formula. The boxed equation is the overall system function; note that V_E , the excitation voltage, has cancelled out. In the new code formula, V_{ref} no longer appears; the measurement depends (ideally!) only on k , F_{max} , and F_{strain} .




This demonstration shows a ratiometric system using the ADS1256.

Ratiometric configurations frequently give higher performance than those using fixed reference voltages, and have a lower cost. There are a few things to watch out for:

- If the power supply is used as the reference, and is very noisy, this noise can couple into the ADC and affect the measurement. The reference should always be filtered, even in ratiometric applications.
- Some ADCs have limited reference voltage ranges which also limit the excitation voltage on the strain gauge. In this case, it may be necessary to resistively divide down the reference, or better yet, use a resistor between the excitation voltage and the bridge.

The connection shown is not the only way to perform ratiometric measurements. In some systems, a fixed reference voltage is used with the ADC, and a second channel measures the excitation voltage. This excitation voltage measurement is used in the calculation of the circuit's output.



Firmware Design

- I/O: the main task
- Output is easy
- Input is hard

29

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

In a data-acquisition system, the main task of the firmware is input and output. This statement may seem obvious, but it has important implications for the design of data-acquisition firmware.

Many people focus on the signal-processing functions of firmware. These are certainly important, but they do not affect the overall design of the firmware nearly as much as the input and output structure does.

A computer, as typically programmed, is a naturally proactive device. The vast majority of programming languages and computer designs see the computer as a tool for executing algorithms. Almost all programming languages are essentially ways to give the computer a list of things to do. This makes the output functions easy: in most programming languages, when you want to output data, you simply do so. In this sense, output is not much different from mathematical processing.

Unfortunately, input often is not well provided for, and this is partly because input is hard. When you are generating data, you have complete control; you can ensure that you generate the right data. When you must process incoming data, however, there is much more room for error. You must be prepared to accept and deal properly with anything that can enter your system, and you must do it when the input arrives. This is a fundamentally more difficult problem than generating output.



Data Input Strategies

- Polling
- Interrupts
- Blocking


30

REAL WORLD SIGNAL PROCESSING™

 TEXAS INSTRUMENTS

In this seminar, we are focusing on analog-to-digital conversion. This requires data collection, which is an input process. Let's look at the major ways to do input.

There are three major strategies for dealing with input in a computer program: polling, interrupts, and blocking. Almost all programs which collect data do so using one of these three methods.



Data Input Strategies

A polled system

```

    graph TD
      START([START]) --> CHECK[CHECK FOR DATA]
      CHECK --> PRESENT{DATA PRESENT?}
      PRESENT --> DELAY[DELAY]
      DELAY --> CHECK
      PRESENT --> RETRIEVE[RETRIEVE DATA]
      RETRIEVE --> PROCESS[PROCESS DATA]
      PROCESS --> DELAY
  
```

31

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS


In *polling*, a program repeatedly queries, or *polls*, an input source to see whether data is available. If data is available, it collects the data; otherwise, it goes back to polling. The flowchart in the slide illustrates this.

Polling is a popular strategy because it's easy, and very natural for a computer. A polling program never relinquishes control to the hardware or to different code; it's easy to visualize what the program is doing at any given time.

Unfortunately, polling has many disadvantages:

- Polling isn't very accurate. Events usually occur when you're not checking for them (the proverb "a watched pot never boils" is perhaps appropriate here). In many situations, it's possible to miss events altogether. Polled systems aren't always as easy as they seem.
- Polling wastes CPU time. To avoid missing events, you have to poll very frequently. The more frequently you poll, the less often you'll find data available. If, on average, you get one "yes" answer to a query for every 99 "no" answers, the other 99 times are essentially a waste, especially given the more efficient ways to do things. In battery-powered applications, this wasted CPU time translates into shorter battery life.
- Some systems can't be polled at all, but people try to do it anyway. This leads to much trouble and strife.

Polling is an obvious solution, but very frequently ends up being the most complex of the three strategies.



Data Input Strategies

An interrupt-triggered system

```

    graph TD
      A([INTERRUPT]) --> B[RETRIEVE DATA]
      B --> C[PROCESS DATA]
      C --> D([END INTERRUPT])
  
```

32

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

In an *interrupt-triggered* system, the computer waits for an *interrupt*, which is a signal that alerts the computer that some event has occurred. Almost all microcontrollers can be interrupted using input pins provided for the purpose; indeed, there have been very few microprocessors ever designed without the ability to be interrupted. (An interesting exception is the very first single-chip microprocessor to reach production, the famous 4004 from Intel Corporation. It had no provision for interrupts. Texas Instruments' TMS1000, designed earlier but produced later, also had no interrupt capability.)


Interrupts relieve microprocessors from the need to poll, as shown in the flowchart in the slide. When an interrupt occurs, the microprocessor drops what it's doing and jumps to an *interrupt service routine*. An ISR is code that runs in response to a particular interrupt. In this case, we show an ISR which simply retrieves data, does something with it, and exits the interrupt, at which time the microprocessor resumes what it was doing before the interrupt occurred.

In contrast to polling, we now need not hang about in a loop checking for something to happen. This can potentially save a great deal of CPU time. Even better, the CPU can potentially do other things while it's waiting for the event to occur.

Interrupts do have some disadvantages:


- Interrupts take additional work to set up. Few programming languages make provision for interrupts; C is an example, and so C compilers which support ISRs must usually add special keywords and procedures for declaring ISRs. This can seem an awful lot of trouble. Furthermore, hardware must usually be initialized to begin the interrupt process.
- Interrupt service routines can be difficult to debug. Some debuggers allow tracing and stepping through interrupt service routines, but this is usually difficult since the debugging facility may itself use interrupts. Partly because of this, many programmers associate interrupts with low-level, "close to the metal" programming, and try to avoid them or wrap them in layers of abstraction.
- Using interrupts typically makes your code non-portable, or at least harder to port. This is because programming languages almost never offer direct support for interrupts. Indeed, it would be very difficult for them to do so, since interrupt support and structure varies widely from system to system.
- Interrupts usually require special provision to be made for them in the hardware. Sometimes the circuitry needed for interrupts isn't provided, either as the result of oversight or for lack of resources. For example, the designers of isolated data-acquisition front-ends often try to bring as few signals across the isolation barrier as they can, since isolation channels are usually very expensive.

While interrupts can be tricky and tedious to set up and get working properly, the result is often a much more reliable system. The effort expended on building a system to use interrupts is frequently rewarded later on with fewer problems in debugging and operation.



Data Input Strategies

A blocking system

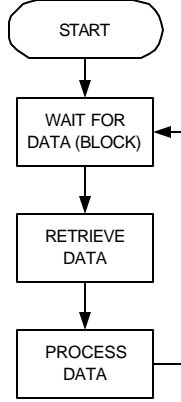

```
graph TD; START([START]) --> WAIT[WAIT FOR DATA (BLOCK)]; WAIT --> RETRIEVE[RETRIEVE DATA]; RETRIEVE --> PROCESS[PROCESS DATA]; PROCESS --> WAIT;
```

33

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

In *blocking*, a program executes an operation or calls a function which does not return until something happens. Blocking is a common feature of programs running on operating systems, which handle the details of waiting for events; in many systems, blocking is the only convenient way of waiting for input.

Blocking is not usually supported directly by hardware systems, so a very small embedded system is unlikely to use it. However, if you are using a real-time OS or microkernel in your system, you will very likely use blocking in some way.

One form of blocking is commonly supported by microcontrollers. You can put many modern microcontrollers into a “sleep” state, in which the microprocessor does not execute instructions, but does respond to interrupts. When an interrupt occurs, the microprocessor wakes and executes the ISR. It may then resume normal operation or go back to sleep, depending on the system and its configuration.

If you are using an operating system to perform blocking I/O, note that the operating system itself is likely written using one of the other two strategies. For example, calling a “receive” function may cause the operating system to wait for an interrupt or poll for some condition. However, from the programmer’s perspective, the operation is still blocking, no matter what the underlying mechanism used in the OS is.



Interfacing to the ADC

- SAR interfacing
- Delta-sigma interfacing
 - Continuous conversion
 - Triggered conversion
 - Using synchronization
- Channel scanning
 - Scanning with SARs
 - Scanning with delta-sigma converters

34

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS


We now turn to interfacing strategies for various types of ADCs.

It might seem that the process of retrieving data from an ADC ought to be the same no matter what the type of converter – after all, what should the architecture have to do with the interface to the device? While to an extent this is true in principle, in practice, various ADC architectures do require slightly different interface methods.

Some of the differences in ADC interfacing arise from the usual application for each architecture. SAR ADC ICs were originally used for signal measurement under microprocessor control. They were designed with microprocessors in mind. At first, SAR ADCs had parallel busses; later, serial-interface versions were introduced. In both cases, the devices were designed for easy interface to microprocessors.

By contrast, delta-sigma ADCs came later and were first used for voice-band audio applications. The devices were therefore designed with interfaces that could be easily connected in digital telephone applications. Audio signals are continuous, and so the digital interface was designed to act as an unbroken stream of digital data. The first delta-sigma converters, therefore, sent out their data immediately as it was converted, had no convert-start pin, and converted over and over, without pause. All delta-sigma audio ADCs work in a similar fashion.

The very nature of delta-sigma converters makes them well suited for continuous conversion, which gives maximum throughput. As delta-sigmas began to be marketed as SAR alternatives, however, many users of SARs found the continuous-conversion interface confusing. Although most delta-sigma devices are still continuously converting, a few have been introduced which convert only on command, much as SARs do.



Interfacing to the ADC

Reading a SAR converter

```
graph TD; A([BEGIN CONVERSION]) --> B[ASSERT START CONVERT LINE]; B --> C[DELAY FOR CONVERSION]; C --> D[SHIFT OUT DATA]; D --> E([RETURN DATA]);
```

35

REAL WORLD SIGNAL PROCESSING™


TEXAS INSTRUMENTS

The slide shows an example flowchart for reading a SAR ADC.

Note that the process of reading a SAR ADC includes telling it to convert. The vast majority of SARs convert only on request. The flowchart shown has a block labelled “ASSERT START CONVERT LINE”. The intent here is for the program to toggle a line connected to the SAR’s convert-start pin. Doing this causes the SAR to convert the data. If this is not done, the SAR will not perform a conversion.

Following the assertion of the convert-start line is a delay. This must be long enough for the SAR to complete the operation of conversion.

Finally, data is shifted or otherwise read from the device. The data is from the conversion begun with the assertion of the convert-start line.



Interfacing to the ADC

Reading a continuous delta-sigma converter

```
graph TD; A([RECEIVE DATA-READY]) --> B[SHIFT OUT DATA]; B --> C([RETURN DATA]);
```

36

REAL WORLD SIGNAL PROCESSING™ TEXAS INSTRUMENTS

The corresponding flowchart for a continuously converting delta-sigma device is deceptively simple. In the flowchart, we show an interrupt service routine which responds to the converter's data-ready line. The data-ready line signals that new data is available. When our program receives the signal, it shifts data out of the device. The routine is then done.

The converter itself, however, is not done at all. Even while we are shifting out data – before, actually – it is hard at work on the new conversion. A continuously converting delta-sigma does not wait for data to be shifted out before beginning a new conversion; it is *always* converting, unless explicitly told to stop.

In practice, then, the interface to a typical delta-sigma ADC – most of them are, in fact, continuous-conversion devices – is quite different from the interface to a typical SAR. Note that, in the previous flowchart, we told the converter to begin converting; with a continuous delta-sigma ADC, the converter converts all the time, without being told. We therefore must respond to it, instead of it responding to us, as is the case in a SAR system.

Many people new to delta-sigma ADCs make the mistake of trying to use them like SARs. A common error is to poll the data-ready line, or even to use a timer to estimate the intervals at which data will become available. In most cases, the former is unnecessary, and in almost no case is the latter necessary. A much simpler solution is to connect the data-ready line to an interrupt input and let the chip wake the microprocessor. No polling or time-estimation is then necessary.



Calibration

- *Every* measurement system must be calibrated
- Calibration can be done in software or hardware
- Software is preferable

37

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

Q: When is a measurement system not a measurement system?

A: When it isn't calibrated.

When a measurement system is not calibrated, it isn't a measurement system at all, but a rather poor random-number generator. The data generated by an uncalibrated measurement system is almost completely meaningless. Calibration isn't simply a "nice feature to have": it's a core part of what a measurement system does. Without it, your measurement system design is quite useless.

Here is part of a dictionary definition of calibration:

"... The determination of the true value of the spaces in any graduated instrument."

This is an excellent starting point for our purposes. An ADC is a graduated instrument: it has gradations, which most people call "codes", and it is certainly an instrument, usually measuring voltage. Although an ADC doesn't look much like a ruler, it is much more like a ruler than many people realize. When we calibrate an ADC, we are actually trying to find out what the true value of each gradation is, just as the dictionary tells us. Although we can never find out the exact values (in fact, Heisenberg tells us that there *are* no exact values!), we can come quite close, and so in calibrating, we will make this our objective.

To calibrate an ADC-based measurement system, we must do the following:

1. Measure a known quantity with the ADC.
2. Record the value reported by the ADC.
3. Use this value to adjust, or correct, subsequent values reported by the ADC.

The process of measurement is, of necessity, done by the ADC itself; the correction may be done in hardware or software.

Measurement systems not employing an ADC are typically calibrated in hardware. Probably the simplest hardware calibration tool is the lowly trimmer potentiometer. Where an ADC is employed, however, there is likely to be a microcontroller, and we may well be able to correct the values delivered by the ADC, using the microprocessor. If it allows sufficient accuracy, this is to be preferred, as fewer manufacturing steps need to be taken. Best of all, in the field, the device need not be opened and trimmed for calibration.



Calibration

- Linear errors
 - Easy to correct using addition and multiplication
 - Many ADCs can do this for you
- Non-linear errors
 - More difficult to correct and calibrate for
 - Best done in software

38

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS


While calibration is technically the act of discovering what the gradations of the ADC really mean, the word is frequently used to refer to the process of correcting the incorrect values delivered by an ADC. The goal of this process is to adjust the values delivered, and to do this, the adjustment must be known.

For each code reported by an ADC, there is an associated error by which it deviates from the actual value. One way to correct a “bad” ADC would be to measure every possible measurable value, note the deviation from the correct value, and use this in subsequent corrections. With a 24-bit ADC, however, this is impractical for most systems, as 2^{24} , or over a million, correction values must be captured and recorded. The primary difficulty here is not storing the corrections, but finding out what they are; it is extraordinarily difficult to generate and measure that many values in a reasonable amount of time – less than, say, a few months.


Fortunately, we can make many generalizations about the kinds of errors encountered in a measurement system. Broadly speaking, all errors are either *linear* or *non-linear*. Linear errors can be corrected by simple addition or multiplication; non-linear errors can not. Obviously, the linear errors are far easier to deal with. Luckily for us, they also form the bulk of the inaccuracies in a typical measurement system; once we have corrected the linear errors, our system will (usually) be very accurate.

The need to compensate for linear errors is almost universal, and so many ADCs have facilities for correcting linear errors on board, particularly delta-sigma ADCs. Most self-calibrating ADCs can even run the calibration procedure automatically. Furthermore, code adjustment is often done internally in such devices, so that no dynamic range is lost.

Non-linear errors are more difficult. Some non-linear errors follow a polynomial or exponential function, and can be corrected on that basis; others follow complex functions which may not be knowable at design time. These must be corrected empirically. Strategies exist for dealing with these, but are beyond the scope of this presentation.



Calibration

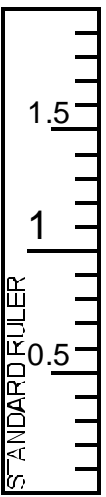


39

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS


Shown in the slide is a ruler. This ruler has two units, and is marked in tenths. We will use this ruler to illustrate various kinds of errors that we can correct in calibration.

Let us suppose, for the purposes of this discussion, that this ruler is our standard. For example, anything the same length as this ruler is, by definition, two units long. Since this ruler is a standard, we can use it to calibrate other rulers.



Calibration

Offset error

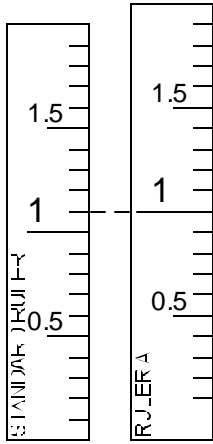


40

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS


Here we are calibrating a ruler of unknown quality, labeled in the slide as Ruler A. When we compare it to the Standard Ruler, we find that all the marks are too far upwards by $1/10$ of a unit, but are otherwise exact.

This ruler has an *offset error*. Having calibrated it against the Standard Ruler, we now know that any reading we take with it should have 0.1 subtracted from it, and it will then be correct.



Calibration

Gain error

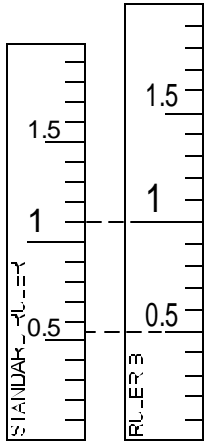

41

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

In this slide, we show Ruler B being calibrated. This ruler is too long: the marks are evenly spaced, but are too wide compared to the Standard Ruler. When we measure the 1 unit mark on Ruler B against the Standard Ruler, we find that it is positioned at 1.1 units.

Ruler B has a *gain error*. Any reading taken from Ruler B should be divided by 1.1, and it will then be correct.

Calibration

Offset calibration for a weigh scale

No weight (0kg)

Before offset calibration

After offset calibration

42

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

This slide and the next illustrate calibration for a weigh scale.

In this slide, the scale is offset calibrated. Prior to calibration, the scale displays a negative offset. After calibration, with no weight applied, the scale reads zero, as it should.

(Note that in the case of an analog scale, calibration can be performed merely by rotating the movement of the gauge.)

Calibration

Offset calibration for a weigh scale

5kg ← Known weight

4.8 kg

Before gain calibration

5kg ← Known weight

5kg

After offset calibration


43

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS


In this slide, the scale is shown being calibrated for gain. A known weight is obtained and placed on the scale. The scale is then adjusted until its reading is equal to the mass of the known weight.

This scale reads too low when the 5kg known weight is placed on it. Following calibration, the scale reads 5kg with a 5kg known weight on it, as it should.



Calibration

Offset calibrating an ADC

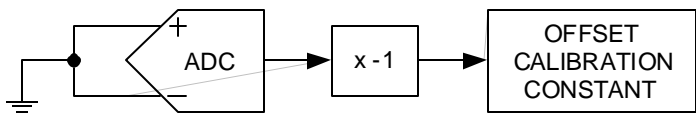

44

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

Calibrating linear errors out of an analog-to-digital converter is, in principle, exactly like calibrating a ruler or a weigh scale for linear errors.

Shown in the slide is a setup for calibrating an ADC for offset. The procedure is as follows:


1. Connect 0V to the ADC's input. In the slide, our ADC has a differential input, so we ground both inputs. The reference input is not shown here, and in theory, it should not affect the measurement.
2. A reading is taken from the ADC.
3. The reading taken is negated.
4. The result is stored and used in subsequent measurements as the offset correction constant.

The offset correction constant obtained in the foregoing procedure is subtracted from each reading taken. The readings are thus corrected for offset.

Note that we have not changed the operation of the ADC – it is still “incorrect”. Instead, we determine the offset error of the ADC, and correct for it after the fact.


It is also possible to correct ADC offsets by applying a correction voltage in hardware. This may help increase dynamic range, but is more complex. In practice, the dynamic range lost from software offset correction is usually negligible and may well be close to the ADC's noise floor.

Note that self-calibrating ADCs can perform this procedure automatically, using either an internal short or a measurement made of an external voltage.



Calibration

Gain calibrating an ADC

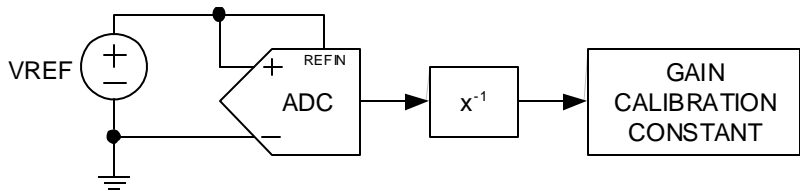

45

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

This slide shows the basic setup for gain calibration of an ADC. The procedure is as follows:

- Full-scale voltage is connected to the ADC. In this example, this happens to be equal to the reference voltage. (Note that not all ADCs behave this way.)
- A reading is taken from the ADC.
- The reading is divided from 1.
- The result is stored and used in subsequent measurements as the gain calibration constant.

Each measurement taken from the ADC is multiplied by the gain calibration constant. Again, we have not changed the behavior of the ADC; we simply correct the codes coming out of it.

As with offset calibration, it is possible to perform gain calibration in hardware. In practice, this is even more difficult than in software, and has many disadvantages. For example, most converters exhibit gain drift, i.e., their gain varies with temperature. Compensating for this requires different calibration constants to be used in various temperature ranges. If calibration is done in hardware, doing this automatically requires a programmable gain circuit. In software, it is only necessary to load in a different calibration constant when the temperature changes.

Note that self-calibrating ADCs can perform this procedure automatically, using either an internal connection to the reference or a measurement made of an external voltage.



Converting codes to units

Example: Weigh scale (mass measurement)

$$m_{\text{meas}} = (x_{\text{adc}} + x_{\text{zero}}) \frac{m_{\text{cal}}}{x_{\text{cal}}}$$

m_{meas} : measured mass

x_{adc} : code from ADC

x_{zero} : code recorded with zero mass

m_{cal} : mass of calibration weight

x_{cal} : code recorded for calibration weight

46

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

Once we have calibrated the measurement system, we are prepared to convert the codes output by the ADC into the real units delivered by the measurement system. The slide shows one possible formula to use for this purpose for a weigh scale, but most any measurement system will have a similar formula.

The formula combines four values to obtain the measured mass m_{meas} :

- x_{adc} is the code obtained from the ADC back-end. Note that some signal processing may have been performed on this value.
- x_{zero} is the code recorded with nothing on the scale. This is the offset calibration constant for the system.
- m_{cal} is the mass of the standard weight used for calibration. Generally this is entered by the user during calibration, or it may be hard-coded into the system, which will then require that the hard-coded mass is used for calibration.
- x_{cal} is the code recorded during calibration with the standard weight on the scale. This code, together with m_{cal} , sets the scale factor which converts the code into the units of m_{cal} .

Note that we cannot use this formula, or indeed generate any real-valued units at all, until we have obtained values for x_{cal} and x_{zero} . In general, this must be done empirically.



Signal Processing

- Averaging
 - Very simple to implement
 - Offers some improvement
- Complex digital filtering
 - More complex to implement
 - Can offer more dramatic improvement

47

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

While a good ADC is essential for making accurate measurements, further processing in software can bring improvements to almost any system.

The most common processing, and the simplest to implement, is signal averaging. Averaging attempts to remove uncorrelated noise from a signal being measured. Since much of the noise on a signal is uncorrelated to the data being collected, averaging can reduce it greatly.

Averaging is a case of digital filtering, and it is certainly possible, and sometimes beneficial, to implement digital filtering on a signal. A complex digital filter is especially useful for rumble filtering, which we will discuss further on.



Basic Averaging

$$x_{\text{ave}} = \frac{1}{N} \sum_{i=0}^N x_i$$

$$S_{\text{ave}} = \frac{S_{\text{sig}}}{\sqrt{N}}$$

48

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

The two primary kinds of signal averaging are *coherent* and *incoherent* averaging. The terms apply primarily to non-DC signal situations. When we are measuring a signal that is essentially DC, the averaging is always coherent; since our primary focus here is on near-DC signals, we will not discuss these terms further.


(A thorough discussion of digital signal averaging can be found in *Understanding Digital Signal Processing* by Richard G. Lyons [1997], ISBN 0-201-63467-8, chapter 9. This book is highly recommended for anyone performing any level of digital signal processing. Several figures from this book appear in this presentation.)

The process of averaging is well known: the numbers to be averaged are summed, and divided by the number of them, as shown in the top equation.

When averaging is coherent – i.e., the signal remains constant, while the noise changes – the noise, being uncorrelated, averages out. The more averaging performed, the more the noise cancels. If the signal is DC, and the noise component is random, then with each successive sample averaged, the signal-to-noise ratio will improve.

In fact, it can be shown that the improvement is proportional to the square root of the number of samples in the average. The second equation illustrates this: the standard deviation of the average of a number of noisy samples of the same signal is the standard deviation of the original signal divided by the square root of N. Therefore, there is a diminishing return associated with averaging.

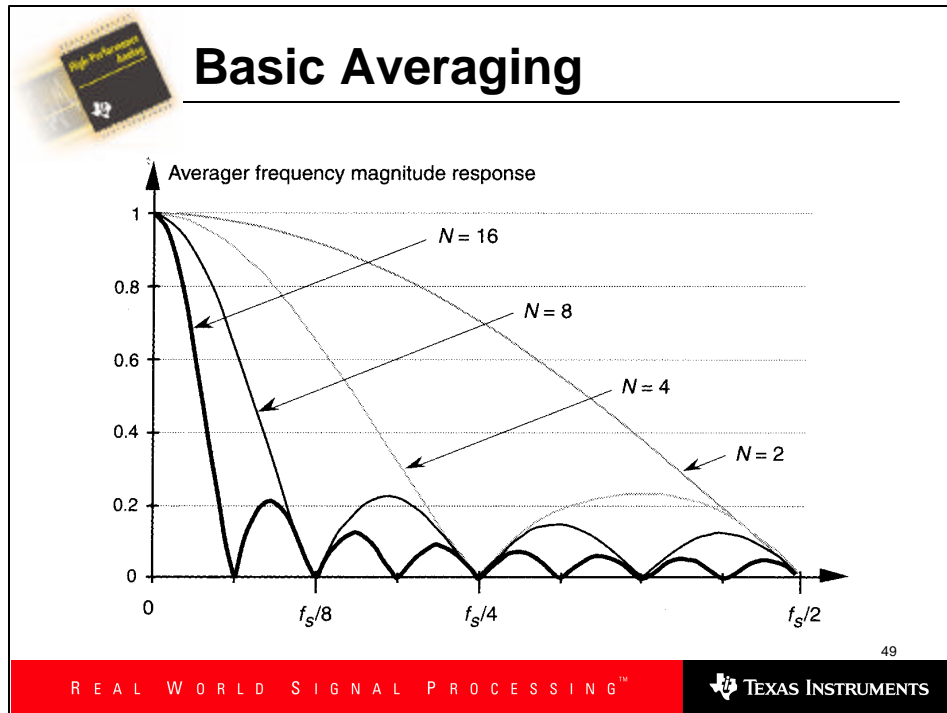
The second equation assumes that each averaged signal is the same. In reality, this is not the case, as no real signal is exactly at DC. Any quantity we measure will exhibit some level of slow drift, and this will appear in averages over time. This limits the effectiveness of large numbers of averages.



Simple averaging is, in fact, a special case of FIR filtering. The slide shows several frequency responses of various N-point averaging functions. The response of these functions is the well-known sinc^N function ($\sin^N(x)/x^N$). Almost all delta-sigma converters use averaging filters in their first stage decimation filters. Many industrial delta-sigma converters do not have a second-stage decimator, and their overall frequency response is the sinc^N decimated (aliased).

Note that averaging filters have notches at regular intervals. These notches can be put to good use in filtering out strong signals such as power-line interference.

 
(Illustration from Lyons [1997], page 341.)



The difference equation in the slide performs two-point *exponential averaging*. The response of an exponential filter can easily be varied from weak filtering with a quick step response (fast settling time) to strong filtering with a slow step response by varying the alpha coefficient.

This is a useful feature for many measurement systems. For example, in weigh scales, it is desirable to obtain a reading right away when a weight is placed on the scale. As more samples are taken, however, the weight can be determined more precisely by further averages. The exponential averager can be set to a high alpha when the scale is first loaded, and over time the alpha can be decreased to obtain more precise results.

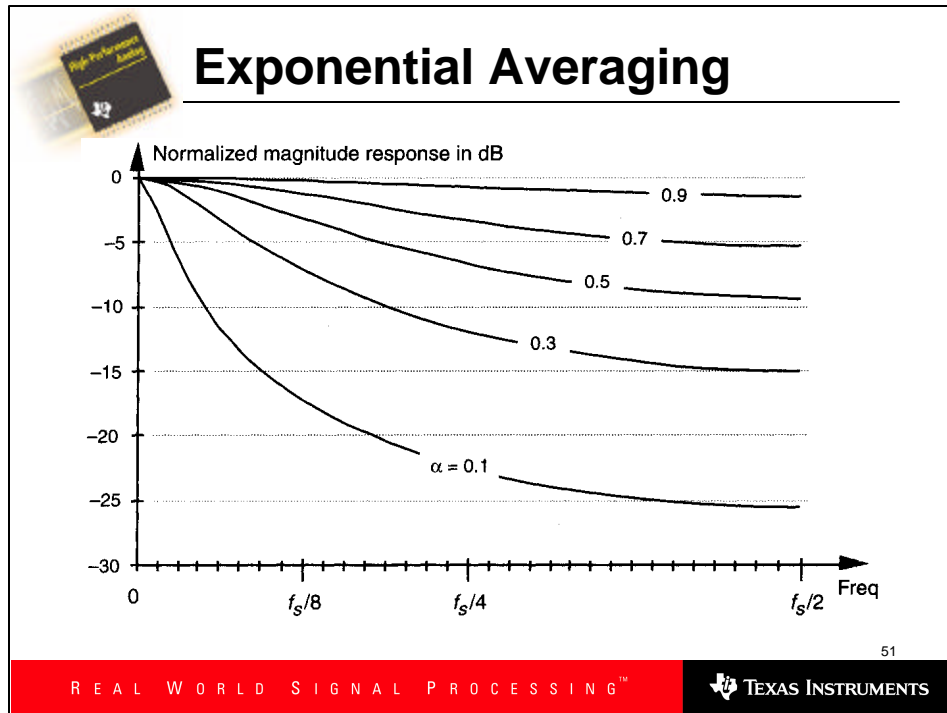(Illustration from Lyons [1997], page 344.)



Exponential averaging is a special case of IIR filtering. Changing the alpha coefficient changes the frequency response of the filter. The slide shows the response of an exponential averager for several values of alpha.

(Illustration from Lyons [1997], page 347.)



Signal Processing

Rumble filtering

- Useful in instruments measuring force or vibration
 - Weigh scales
 - Strain gauges
 - Vibration meters
- Methods
 - Low-pass filtering
 - Notch / inverse comb (sinc^N)

52

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

Rumble filtering (not to be confused with the switchable high-pass filtering often used in mixing consoles) is designed to eliminate extraneous data from vibration and force measurements.

A typical weigh scale, for example, does not directly measure mass, but force, usually through strain. Vibrations (rumbling) occurring in the vicinity of a very precise weigh scale, such as people walking by, heavy traffic, and even air currents, can easily appear in the data. Such vibrations occur at fairly low frequencies, but are certainly not DC. They can therefore be filtered.

Averaging filters, which have notches, are particularly useful for rumble filtering. Rumbles are often clustered near particular frequencies, and can therefore be removed very effectively with the notches in an averaging (sinc^N) filter.

Many delta-sigma converters have sinc^N filters. In a typical delta-sigma decimation filter, the notches are positioned at multiples of the output data rate, which provides optimal aliasing performance. By adjusting the data rate, or decimation ratio, these notches can be positioned precisely, which can greatly reduce rumble.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265