

## Bill of Materials

TI DESIGNS TIDA-00443 REVB 230V, 900W, Power Factor Regulator Converter (PFC) for Inverter Fed Drives – Appliances

Qty	Reference	Part Description	Manufacturer	Manufacturer Part Number	Note
1	PCB	Printed Circuit Board	Any	TIDA-00443	Fitted
1	BR1	Diode, Bridge Rectifier, GPP 15A 800V GBJ	Micro Commercial Co	GBJ1508-BP	Fitted
2	C1, C2	CAP, Film, 0.68 μF, 630 V, +/- 20%, TH	EPCOS Inc	B32923C3684M	Fitted
1	С3	CAP, Film, 1.5 μF, 630 V, +/- 20%, 0.017 ohm, TH	EPCOS Inc	B32923C3155M	Fitted
3	C4, C5, C18	CAP, ALUMINIUM, RADIAL, 220 uF, 450 V, 20%, TH	RUBYCON	450QXW220MEFC18X50	Fitted
4	C6, C7, C8, C9	CAP CER 1000PF 300VAC 20% RADIAL DISC 7mm Dia	TDK	CS65ZU2GA102MYNKA	Fitted
1	C10	CAP, CERM, 2700 pF, 100 V, +/- 5%, X7R, 0603	AVX	06031C272JAT2A	Fitted
1	C11	CAP, CERM, 820 pF, 50 V, +/- 10%, X7R, 0603	Kemet	C0603C821K5RACTU	Fitted
3	C12, C17, C23	CAP, CERM, 1 μF, 25 V, +/- 10%, X7R, 0603	TDK	C1608X7R1E105K080AB	Fitted
1	C13	CAP, CERM, 0.39 μF, 16 V, +/- 10%, X7R, 0603	Kemet	C0603C394K4RACTU	Fitted
1	C14	CAP, CERM, 4.7 μF, 16 V, +/- 10%, X5R, 0603	MuRata	GRM188R61C475KAAJ	Fitted
1	C15	CAP, CERM, 1000 pF, 100 V, +/- 10%, X7R, 0603	AVX	06031C102KAT2A	Fitted
1	C16	CAP, CERM, 0.1 μF, 50 V, +/- 10%, X7R, 0603	AVX	06035C104KAT2A	Fitted
1	C19	CAP, AL, 10uF, 35V, +/-20%, 0.95 ohm, TH	Nichicon	UPW1V100MDD6	Fitted
1	C20	CAP, CERM, 10 μF, 25 V, +/- 10%, X5R, 0805	TDK	C2012X5R1E106K125AB	Fitted
1	C21	CAP, CERM, 330 pF, 1000 V, +/- 5%, U2J, 1206	MuRata	GRM31A7U3A331JW31D	Not-Fitted
1	C24	CAP, CERM, 0.47 μF, 16 V, +/- 10%, X7R, 0603	Kemet	C0603C474K4RACTU	Fitted
1	C25	CAP CER 10UF 50V 20% X5R 1206	Taiyo Yuden	UMK316BBJ106ML-T	Fitted
1	C26	CAP, CERM, 100 pF, 1000 V, +/- 5%, U2J, 1206	MuRata	GRM31A7U3A101JW31D	Not-Fitted
1	D1	Diode, Schottky, 600 V, 4 A, TH	Cree	C3D04060A	Fitted
1	D2	Diode, Switching-Bridge, 600 V, 3 A, TH	Vishay-Semiconductor	1N5406	Fitted
1	D3	Diode, Switching, 100 V, 0.2 A, SOD-323	Micro Commercial Components	MMDL914-TP	Fitted
3	D4, D8, D10	Diode, Schottky, 30V, 0.2A, SOD-323	Fairchild	BAT54HT1G	Fitted
1	D5	Diode, Ultrafast, 100V, 0.15A, SOD-123	Diodes Inc.	1N4148W-7-F	Fitted
2	D6, D7	Diode, P-N, 1000 V, 1 A, 3.9x1.7x1.8mm	Comchip Technology	CGRM4007-G	Fitted
1	D9	Diode, Zener, 12V, 300mW, SOD-323	NXP Semiconductor	BZX384-C12,115	Fitted
1	F1	FUSE CLIP, CARTRIDGE, 250V, 10A, PCB	LITTELFUSE	01110501Z	Fitted
4	FID1, FID2, FID3, FID4	Fiducial mark. There is nothing to buy or mount.	N/A	N/A	Fitted
4	H1, H2, H3, H4	Bumpon, Hemisphere, 0.44 X 0.20, Clear	3M	SJ-5303 (CLEAR)	Fitted
4	H7, H8, H9, H10	Machine Screw, Round, #4-40 x 1/4, Nylon, Philips panhead	B&F Fastener Supply	NY PMS 440 0025 PH	Fitted
3	HS1, HS2, HS3	HEATSINK ALUM Black Anodized, Board Mount	Assmann	V6560Y	Fitted
1	J1	TERMINAL BLOCK 5.08MM VERT 3POS, TH	On-Shore Technology	ED120/3DS	Fitted
1	J2	TERM BLOCK HDR 5POS R/A 5.08MM	PHOENIX CONTACT	1786433	Fitted
1	J3	Header, 100mil, 4x1, Tin, TH	Sullins Connector Solutions	PEC04SAAN	Fitted
1	K1	Relay, SPST-NO (1 Form A), 10A, 12 VDC, TH	Omron Electronic Components	G5LE-1A4 DC12	Fitted
1	L1	INDUCTOR, 360 uH, 8.3 A, 10%, TH	Wurth Electronik	750342810	Fitted
2	L2, L3	INDUCTOR, CHOKE, COMMON MODE, 5 mH, 8.9 A, 22 mOHM, TH	Bourns Inc	8113-RC	Fitted
1	Q1	MOSFET, N-CH, 600 V, 20.2 A, TO-220	Infineon Technologies	IPP60R190P6	Fitted
	· · · · · · · · · · · · · · · · · · ·	• • • • • • • • • • • • • • • • • • • •	<u> </u>		

Qty	Reference	Part Description	Manufacturer	Manufacturer Part Number	Note
1	Q2	Transistor, PNP, 40V, 0.2A, SOT-23	Fairchild Semiconductor	MMBT3906	Fitted
2	Q3, Q5	MOSFET, N-CH, 60V, 0.17A, SOT-23	Diodes Inc.	2N7002-7-F	Fitted
1	Q4	Transistor, NPN, 45 V, 0.1 A, SOT-23	ON Semiconductor	BC847CLT1G	Fitted
3	R1, R15, R23	RES, 10.0 k, 1%, 0.1 W, 0603, RES, 10.0k ohm, 1%, 0.1W, 0603, RES, 10.0 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060310K0FKEA	Fitted
1	R2	RES, 3.9, 5%, 0.25 W, 1206	Vishay-Dale	CRCW12063R90JNEA	Fitted
1	R3	RES, 1.05, 1%, 0.25 W, 1206	Vishay-Dale	CRCW12061R05FKEA	Fitted
1	R4	RES, 0.02, 1%, 3 W, 2512	Bourns	CRA2512-FZ-R020ELF	Fitted
1	R5	RES, 0.2, 1%, 2 W, 2512	Bourns	CRM2512-JW-201ELF	Fitted
4	R6, R7, R20, R21	RES, 332 k, 1%, 0.25 W, 1206	Vishay-Dale	CRCW1206332KFKEA	Fitted
4	R8, R22, R25, R26	RES, 340 k, 1%, 0.25 W, 1206	Vishay-Dale	CRCW1206340KFKEA	Fitted
1	R9	RES, 13.0 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060313K0FKEA	Fitted
1	R10	RES, 23.7 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060323K7FKEA	Fitted
1	R11	RES, 221 ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW0603221RFKEA	Fitted
1	R12	RES, 21.5 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060321K5FKEA	Fitted
1	R13	RES, 100, 1%, 0.25 W, 1206	vishay-Dale	CRCW1206100RFKEA	Fitted
1	R14	RES, 13.7 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060313K7FKEA	Fitted
1	R16	RES, 6.8 k, 5%, 0.1 W, 0603	Vishay-Dale	CRCW06036K80JNEA	Fitted
1	R17	RES, 100 k, 1%, 0.1 W, 0603	, Vishay-Dale	CRCW0603100KFKEA	Fitted
1	R18	RES, 15.4, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060315R4FKEA	Fitted
1	R19	RES, 2.21 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW06032K21FKEA	Fitted
1	R24	RES, 2.10, 1%, 0.25 W, 1206	Vishay-Dale	CRCW12062R10FKEA	Not-Fitted
1	R27	RES, 221 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW0603221KFKEA	Fitted
1	R28	RES, 100, 1%, 1 W, 2512	Vishay-Dale	CRM2512-FX-43R2ELF	Not-Fitted
8	R29, R30, R32, R33, R34, R35, R36, R37	RES, 221 k, 1%, 0.25 W, 1206	Vishay-Dale	CRCW1206221KFKEA	Fitted
1	R31	RES, 47.5 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060347K5FKEA	Fitted
1	R38	RES, 21.0 k, 1%, 0.25 W, 1206	Vishay-Dale	CRCW120621K0FKEA	Fitted
1	R39	RES, 1.00 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW06031K00FKEA	Fitted
1	R40	RES, 0, 5%, 0.125 W, 0805	vishay-Dale	CRCW08050000Z0EA	Fitted
1	RCL1	RES 10 OHM 7W 5% AXIAL	Vishay-Dale	AC07000002009JAC00	Fitted
1	RV1	Varistor 275V RMS 10MM Radial, TH	EPCOS Inc	\$10K275E2	Fitted
7	TP1, TP2, TP3, TP5, TP7, TP8, TP9	Test Point, Miniature, Red, TH	Keystone	5000	Fitted
2	TP6, TP10	Test Point, Miniature, Black, TH	Keystone	5001	Fitted
1	U1	8-PIN Continous Conduction Mode (CCM) PFC Controller	Texas Instruments	UCC28180D	Fitted
1	U2	IC, 4A Single Channel High-Speed Low-Side Gate Drivers	Texas Instruments	UCC27517ADBV	Fitted
3	MK1-MK3	Mounting Kit TO-220	Aavid Thermalloy	4880G	Fitted

## IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design. TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have *not* been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.