

Test Report: PMP23033

# 40-W, 5-V, Single-Switch Forward Converter With Magnetic Feedback Reference Design



## Description



This reference design generates an isolated 5 V at 40 W from a 60-V to 120-V DC input voltage. The design uses a magnetic feedback circuit to replace the function of an optocoupler.

## Features

- Use of 100-krad ICs and magnetics
- Magnetic feedback used to replace optocoupler
- Operation with external supply or self-bias
- Remote sensing
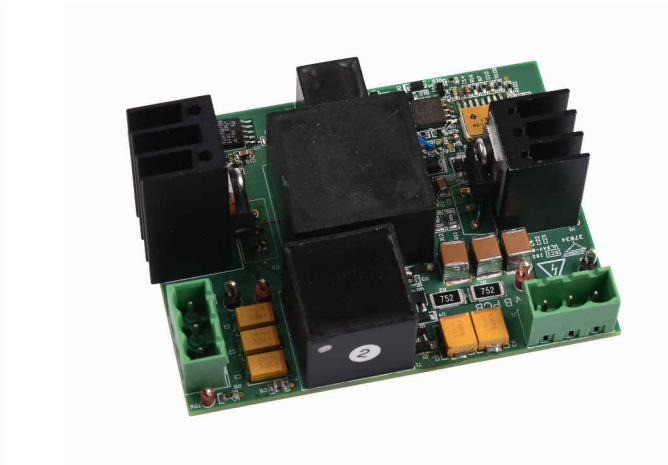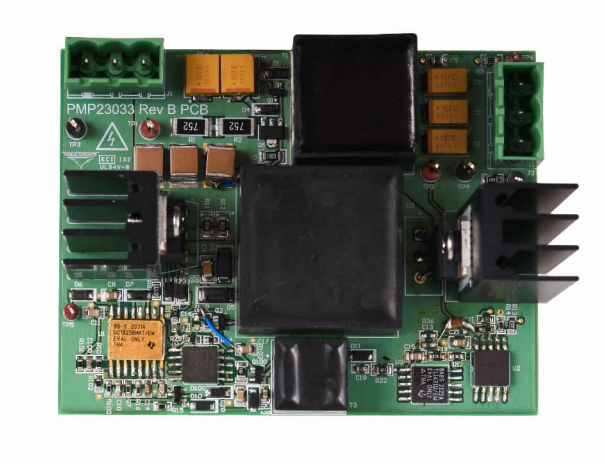
## Applications

- Satellite buses and payloads
- [Communications payload](#)
- [Optical imaging payload](#)
- [Radar imaging payload](#)
- Space launch vehicles



## 1 Test Prerequisites

### 1.1 Voltage and Current Specifications

**Table 1-1. Voltage and Current Specifications**

| Parameter | Specifications |
|-----------|----------------|
| $V_{IN}$  | 60–120 VDC     |
| $V_{OUT}$ | 5 VDC          |
| $I_{OUT}$ | 8 A            |

### 1.2 Dimensions

The board dimensions are 85 mm × 65 mm × 25.4 mm.

## 2 Testing and Results

### 2.1 Efficiency Graphs

Figure 2-1 shows the efficiency graph.

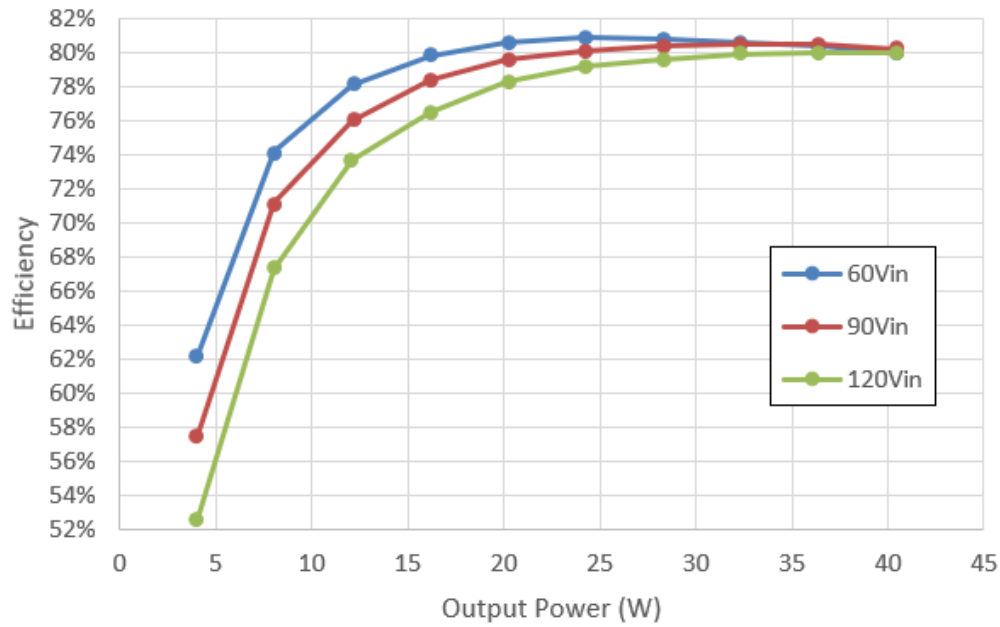


Figure 2-1. Efficiency

Figure 2-2 shows the power loss graph.

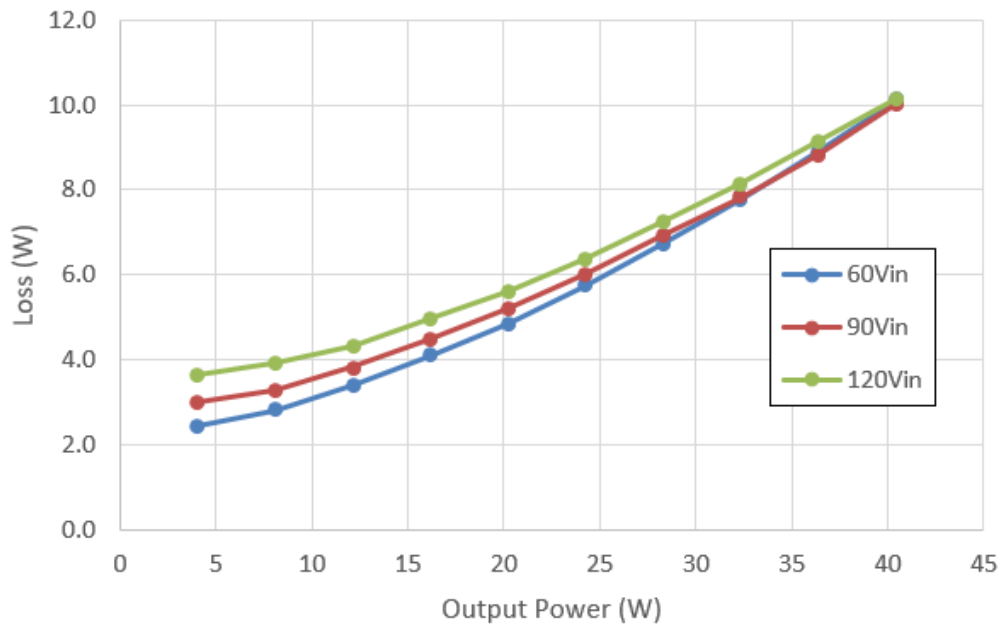


Figure 2-2. Power Loss

## 2.2 Efficiency Data - Minimum Load of 100 mA

Efficiency data is shown in the following tables.

| $I_{OUT}$ (A) | $V_{OUT}$ (V) | $V_{IN}$ (V) | $I_{IN}$ (A) | $P_{OUT}$ (W) | $P_{IN}$ (W) | $P_{loss}$ (W) | Efficiency (%) |
|---------------|---------------|--------------|--------------|---------------|--------------|----------------|----------------|
| 0.100         | 5.05          | 60.2         | 0.027        | 0.51          | 1.63         | 1.12           | 31.0%          |
| 0.800         | 5.05          | 60.2         | 0.108        | 4.04          | 6.50         | 2.46           | 62.2%          |
| 1.60          | 5.05          | 60.2         | 0.181        | 8.08          | 10.90        | 2.82           | 74.2%          |
| 2.40          | 5.05          | 60.2         | 0.258        | 12.12         | 15.52        | 3.40           | 78.1%          |
| 3.20          | 5.05          | 60.2         | 0.337        | 16.17         | 20.27        | 4.10           | 79.8%          |
| 4.00          | 5.05          | 60.1         | 0.417        | 20.20         | 25.07        | 4.87           | 80.6%          |
| 4.80          | 5.05          | 60.1         | 0.499        | 24.24         | 29.99        | 5.75           | 80.8%          |
| 5.60          | 5.05          | 60.1         | 0.583        | 28.29         | 35.03        | 6.74           | 80.8%          |
| 6.40          | 5.05          | 60.1         | 0.668        | 32.33         | 40.11        | 7.79           | 80.6%          |
| 7.20          | 5.05          | 60.0         | 0.754        | 36.36         | 45.26        | 8.90           | 80.3%          |
| 8.00          | 5.05          | 60.0         | 0.842        | 40.40         | 50.52        | 10.12          | 80.0%          |

| $I_{OUT}$ (A) | $V_{OUT}$ (A) | $V_{IN}$ (V) | $I_{IN}$ (A) | $P_{OUT}$ (W) | $P_{IN}$ (W) | $P_{loss}$ (W) | Efficiency (%) |
|---------------|---------------|--------------|--------------|---------------|--------------|----------------|----------------|
| 0.100         | 5.05          | 90.2         | 0.025        | 0.51          | 2.25         | 1.75           | 22.4%          |
| 0.800         | 5.05          | 90.2         | 0.078        | 4.04          | 7.03         | 2.99           | 57.5%          |
| 1.60          | 5.05          | 90.2         | 0.126        | 8.08          | 11.36        | 3.28           | 71.2%          |
| 2.40          | 5.05          | 90.1         | 0.177        | 12.12         | 15.95        | 3.83           | 76.0%          |
| 3.20          | 5.05          | 90.1         | 0.229        | 16.17         | 20.64        | 4.47           | 78.3%          |
| 4.00          | 5.05          | 90.1         | 0.282        | 20.20         | 25.41        | 5.20           | 79.5%          |
| 4.80          | 5.05          | 90.1         | 0.336        | 24.24         | 30.27        | 6.02           | 80.1%          |
| 5.60          | 5.05          | 90.1         | 0.391        | 28.29         | 35.22        | 6.93           | 80.3%          |
| 6.40          | 5.05          | 90.1         | 0.446        | 32.33         | 40.16        | 7.84           | 80.5%          |
| 7.20          | 5.05          | 90.0         | 0.502        | 36.37         | 45.20        | 8.83           | 80.5%          |
| 8.00          | 5.05          | 90.0         | 0.560        | 40.40         | 50.41        | 10.01          | 80.1%          |

| $I_{OUT}$ (A) | $V_{OUT}$ (V) | $V_{IN}$ (V) | $I_{IN}$ (A) | $P_{OUT}$ (W) | $P_{IN}$ (W) | $P_{loss}$ (W) | Efficiency (%) |
|---------------|---------------|--------------|--------------|---------------|--------------|----------------|----------------|
| 0.100         | 5.05          | 120.2        | 0.021        | 0.51          | 2.52         | 2.02           | 20.0%          |
| 0.800         | 5.05          | 120.1        | 0.064        | 4.04          | 7.69         | 3.65           | 52.6%          |
| 1.60          | 5.05          | 120.1        | 0.100        | 8.08          | 12.01        | 3.93           | 67.3%          |
| 2.40          | 5.05          | 120.1        | 0.137        | 12.12         | 16.46        | 4.34           | 73.7%          |
| 3.20          | 5.05          | 120.1        | 0.176        | 16.17         | 21.14        | 4.97           | 76.5%          |
| 4.00          | 5.05          | 120.1        | 0.215        | 20.20         | 25.82        | 5.62           | 78.3%          |
| 4.80          | 5.05          | 120.1        | 0.255        | 24.24         | 30.62        | 6.38           | 79.2%          |
| 5.60          | 5.05          | 120.1        | 0.296        | 28.28         | 35.54        | 7.26           | 79.6%          |
| 6.40          | 5.05          | 120.1        | 0.337        | 32.32         | 40.46        | 8.14           | 79.9%          |
| 7.20          | 5.05          | 120.0        | 0.379        | 36.36         | 45.50        | 9.14           | 79.9%          |
| 8.00          | 5.05          | 120.0        | 0.421        | 40.40         | 50.53        | 10.13          | 80.0%          |

## 2.3 Thermal Images

All thermal images were captured with the DUT at 25°C ambient, after a 30 minute warm up. The output was loaded with 40 W.



Figure 2-3. 60-VDC Input

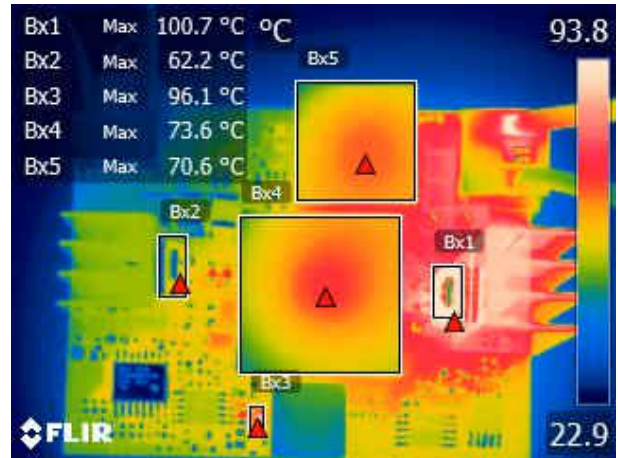


Figure 2-4. 90-VDC Input

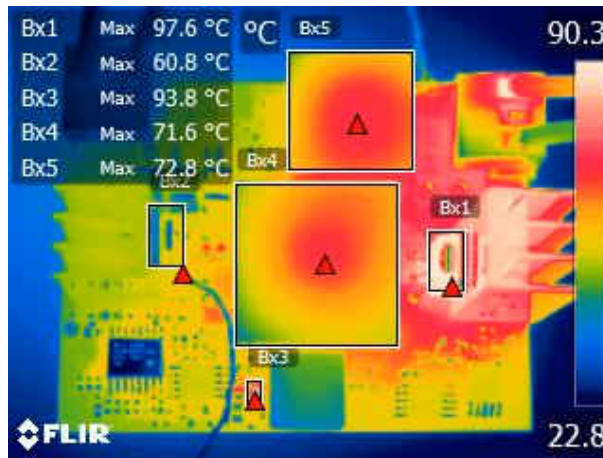


Figure 2-5. 120-VDC Input

## 2.4 Loop Response

Loop response at various input and load levels is shown in the following images.


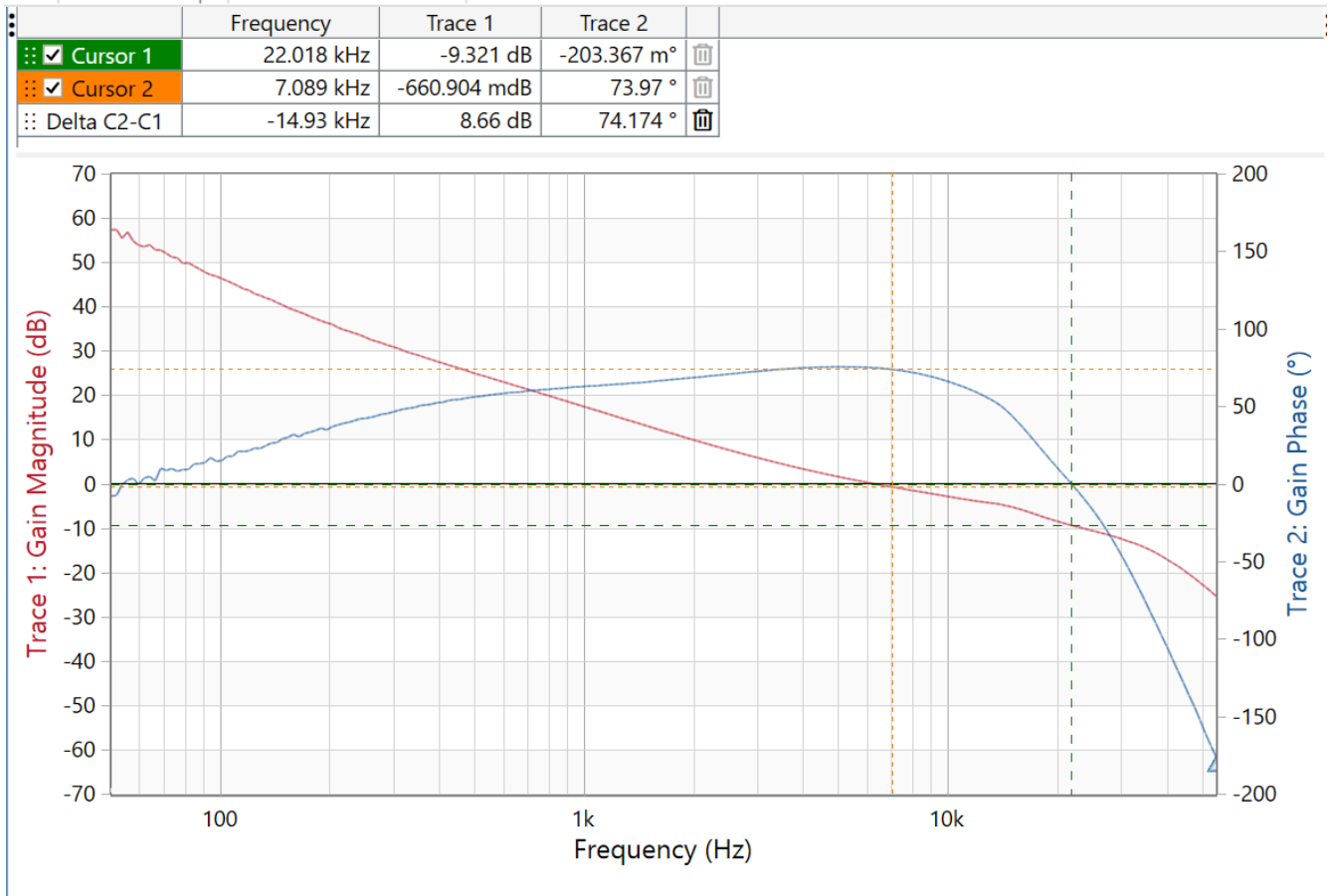


Figure 2-6. 60-VDC Input, 8-A Load

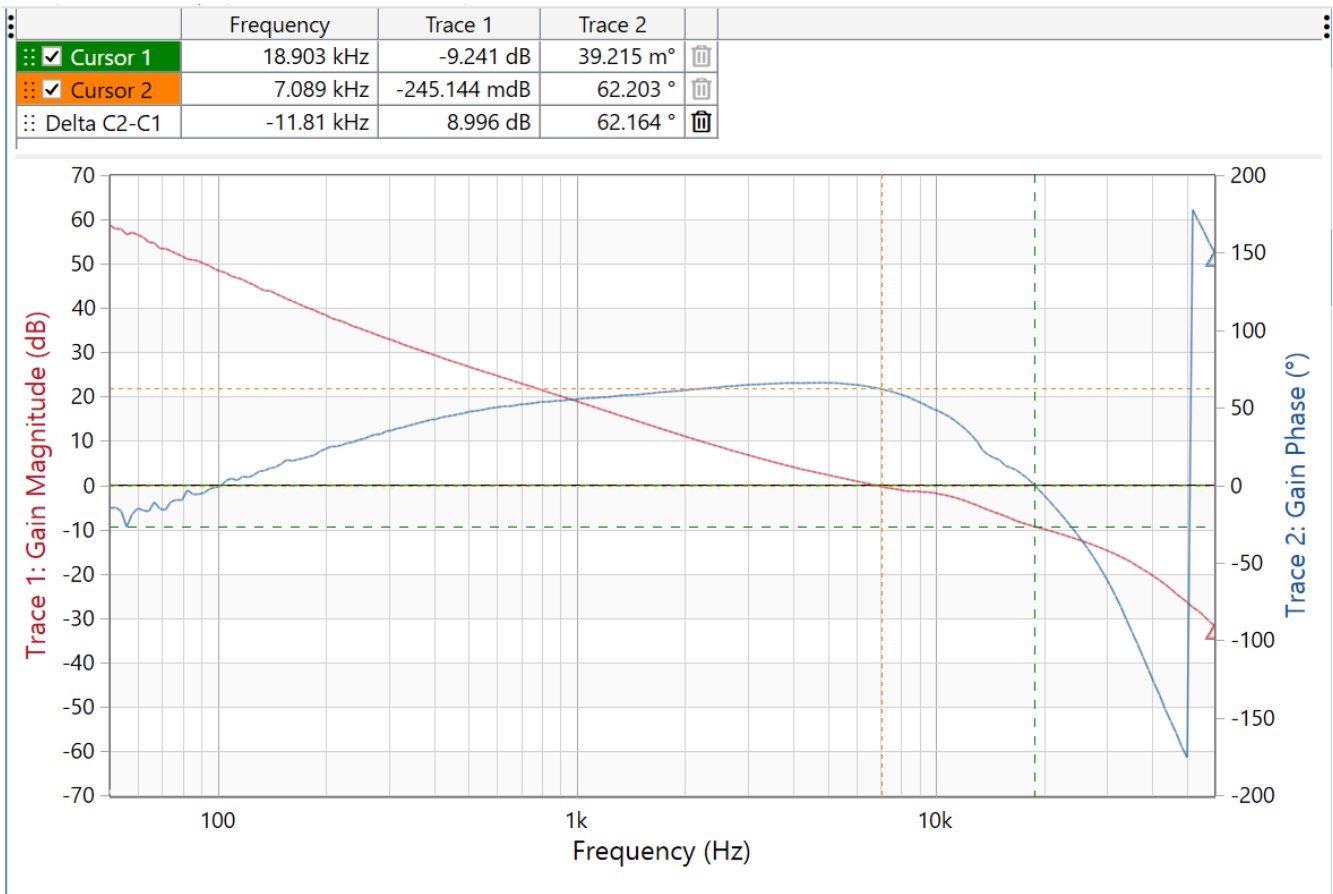

**Figure 2-7. 60-VDC Input, 2-A Load**

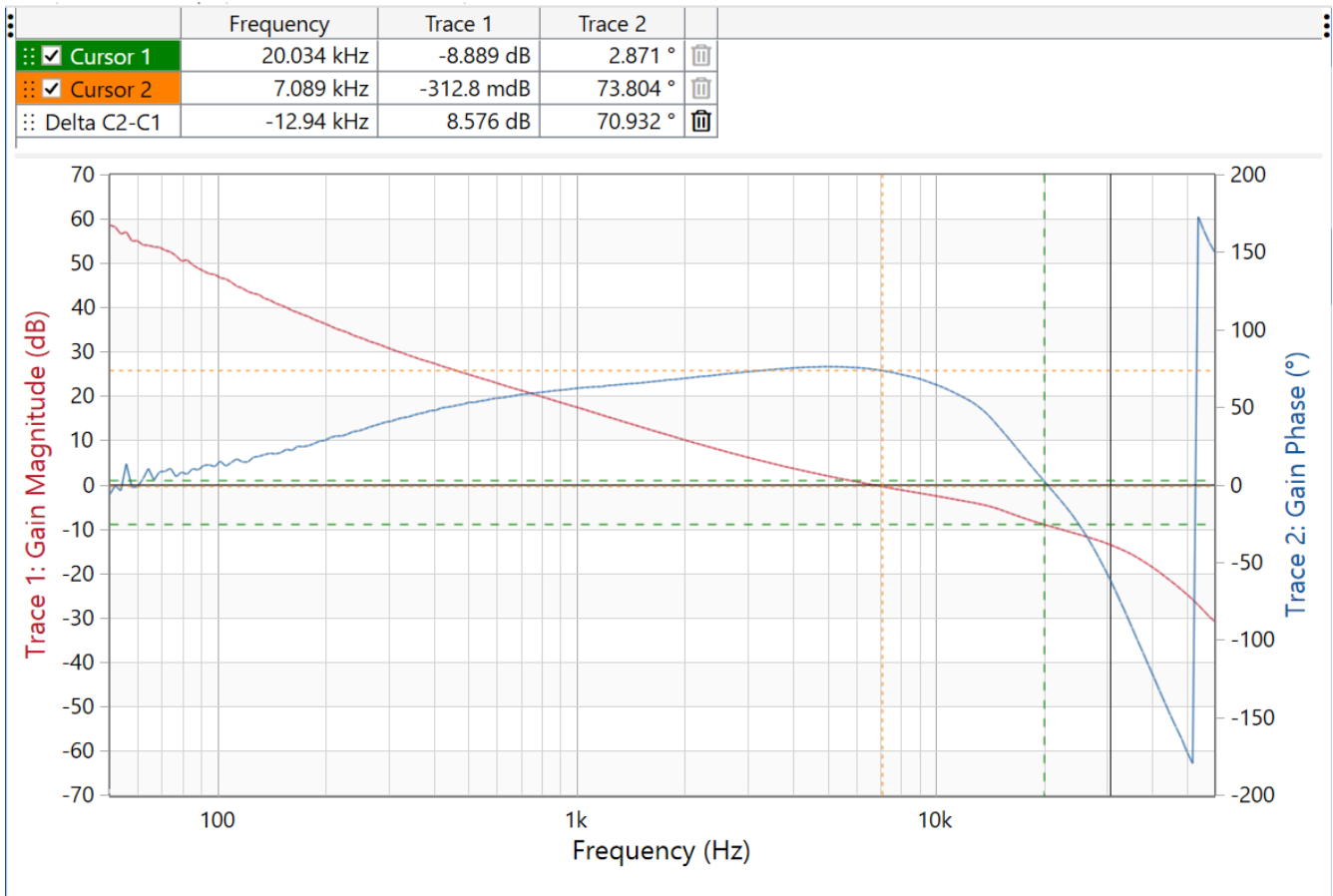


Figure 2-8. 120-VDC Input, 8-A Load




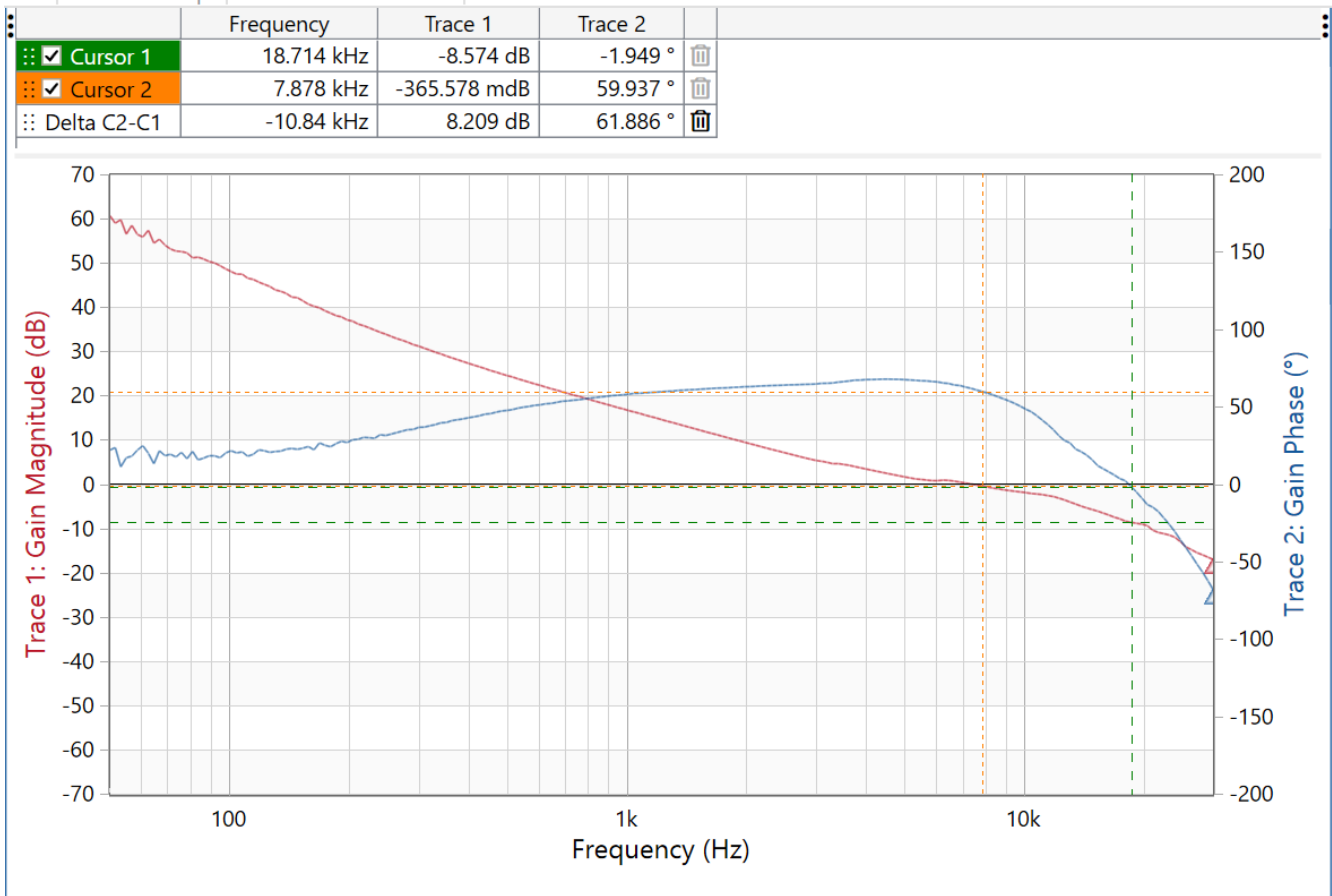


Figure 2-9. 120-VDC Input, 2-A Load

### 3 Waveforms

#### 3.1 Switching

Switching behavior is shown in the following figures.

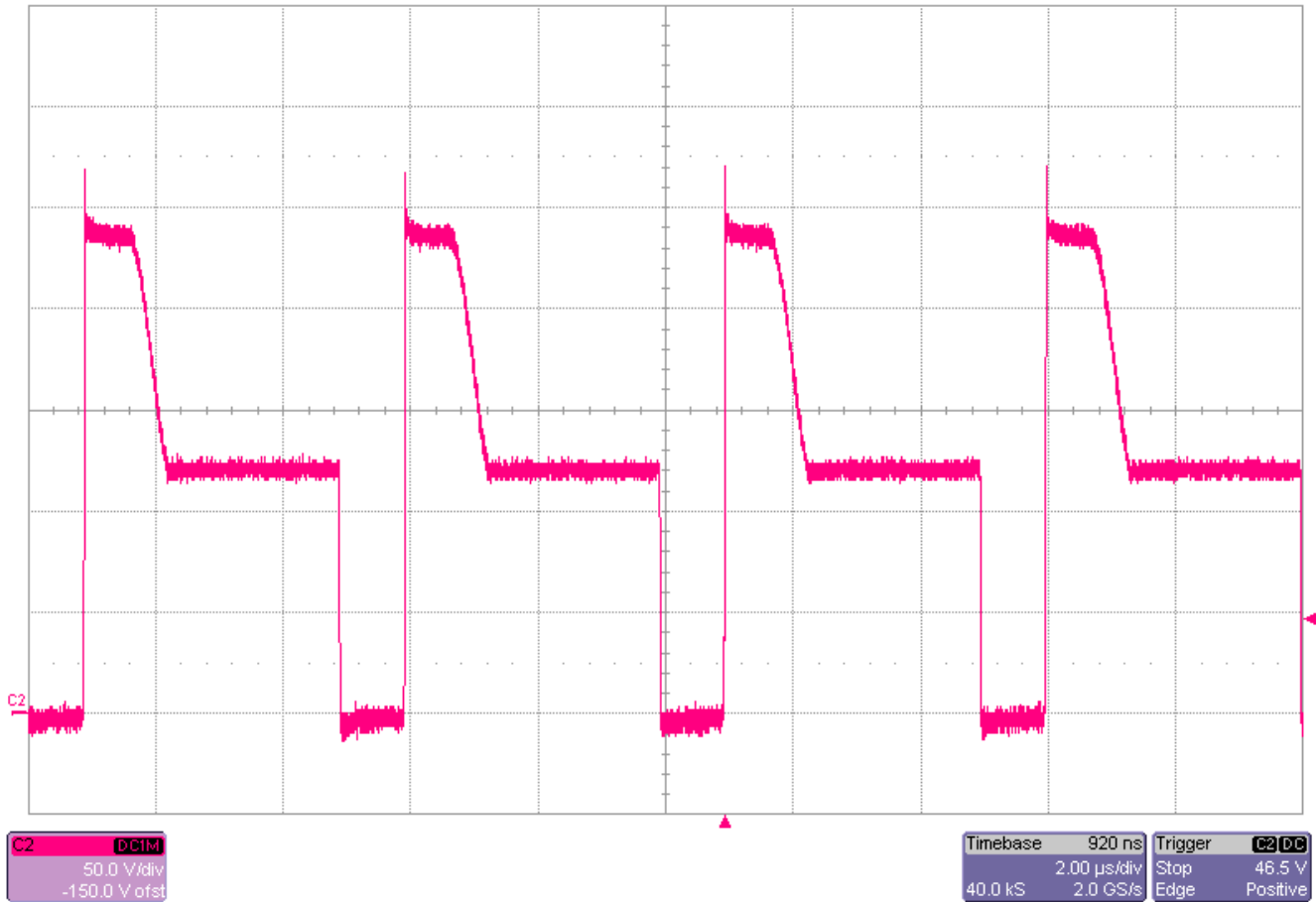

**Figure 3-1. Vds of Primary FET (Q3),  
120-VDC Input, 40-W Output**

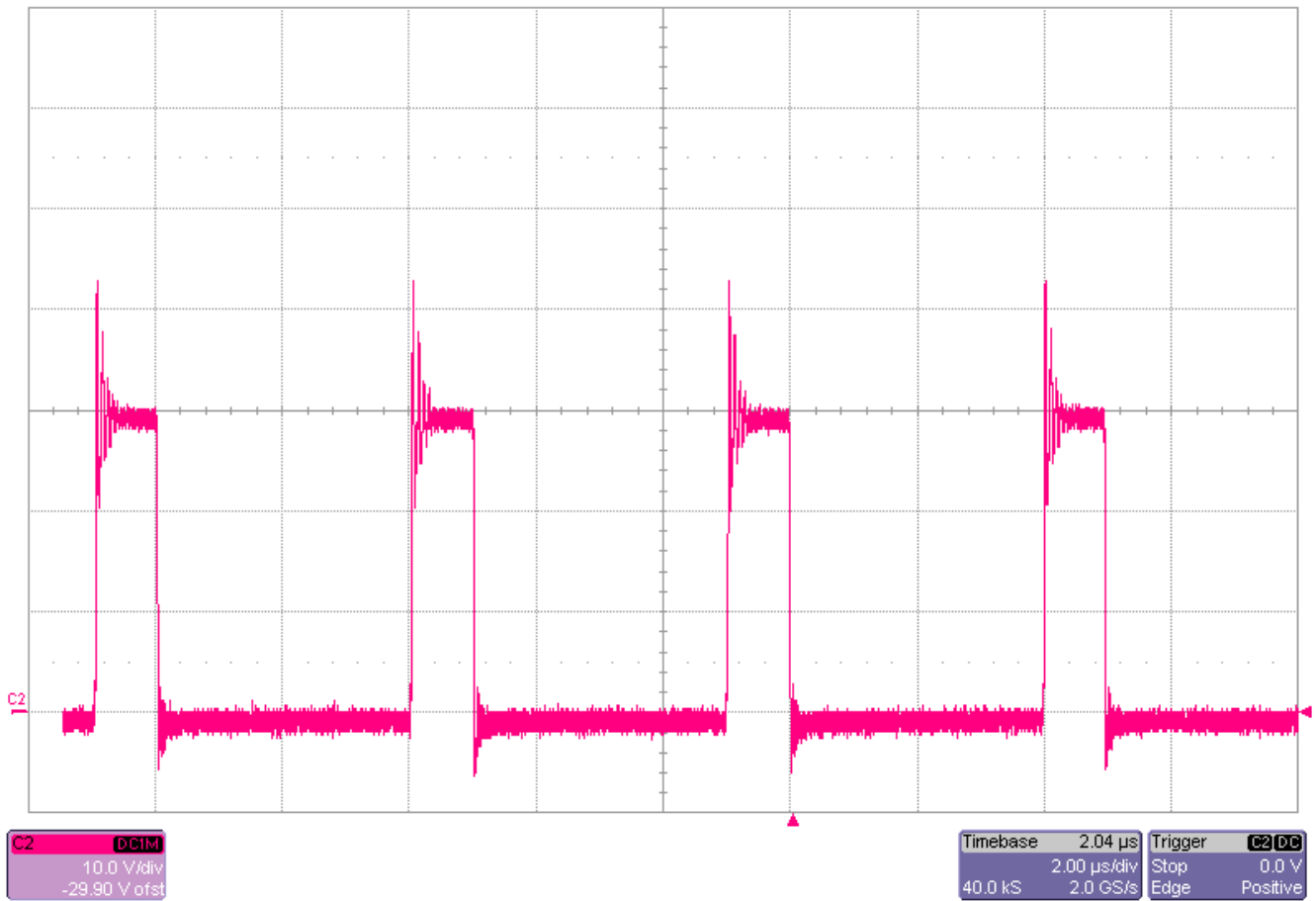


Figure 3-2. Voltage on Cathodes of Output Diodes (D3), 120-VDC Input, 40-W Output

### 3.2 Output Voltage Ripple

Output voltage ripple is shown in the following figures.

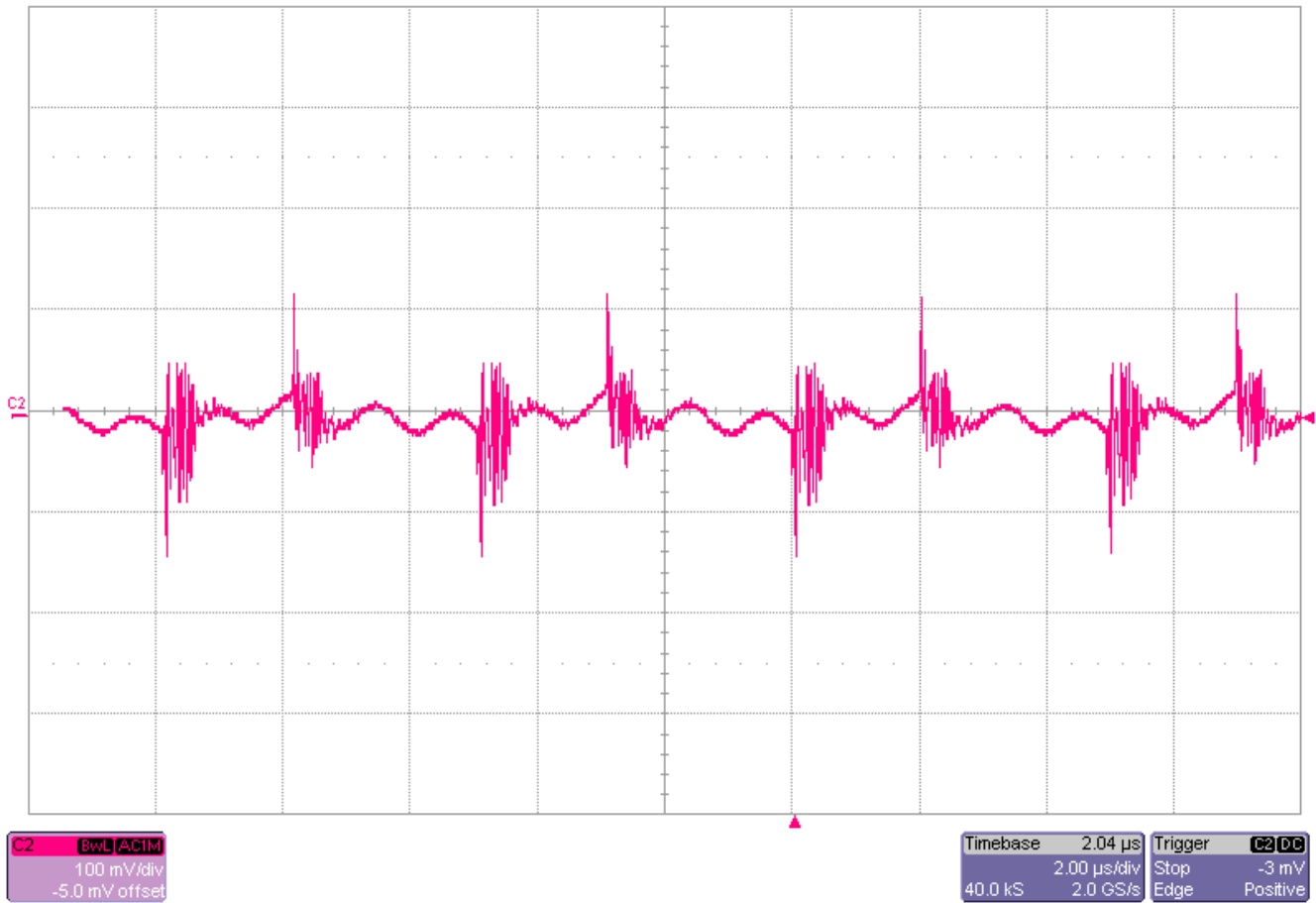


Figure 3-3. 60-VDC Input

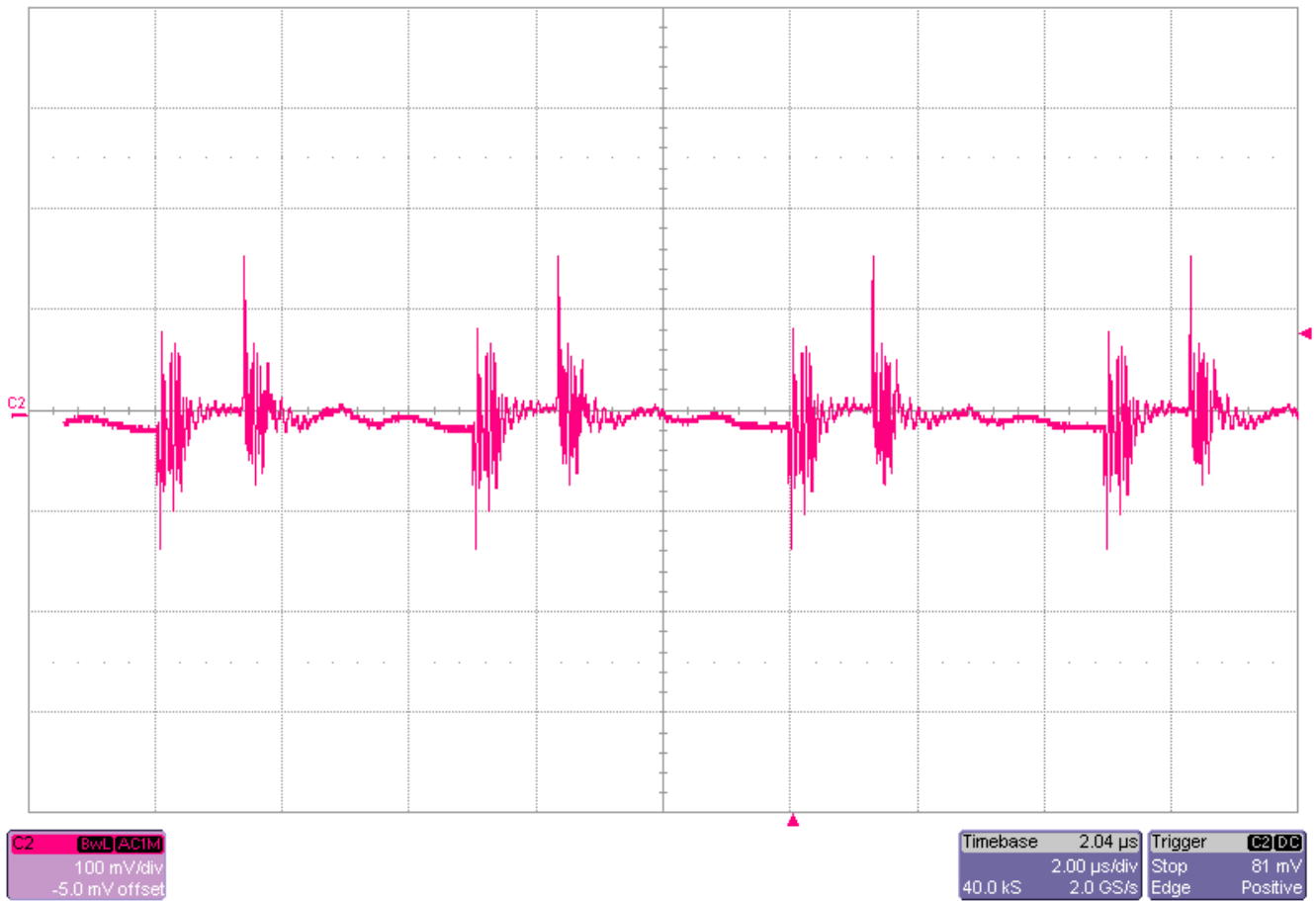


Figure 3-4. 90-VDC Input

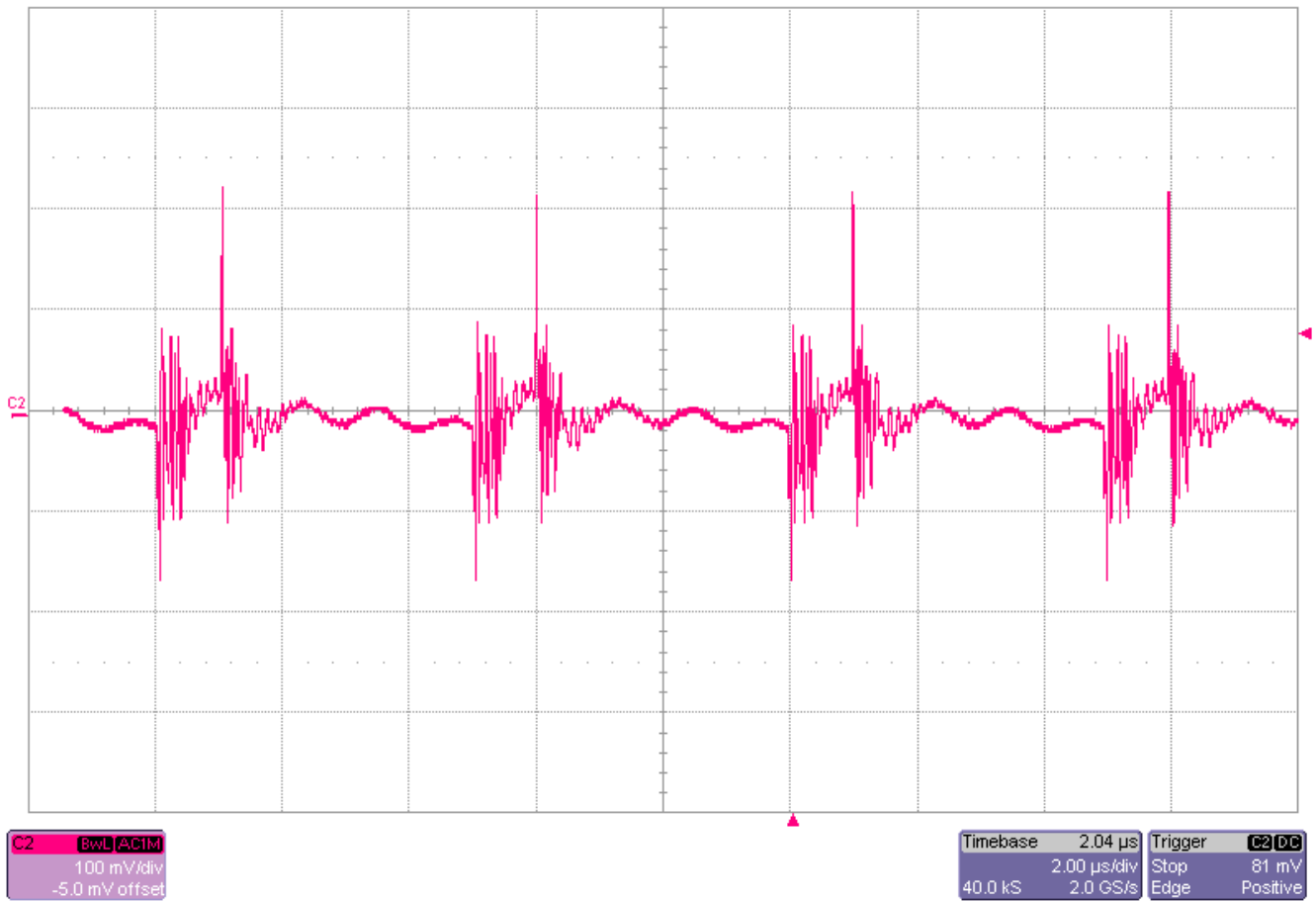


Figure 3-5. 120-VDC Input

### 3.3 Load Transients

Load transient response is shown in the following figures.

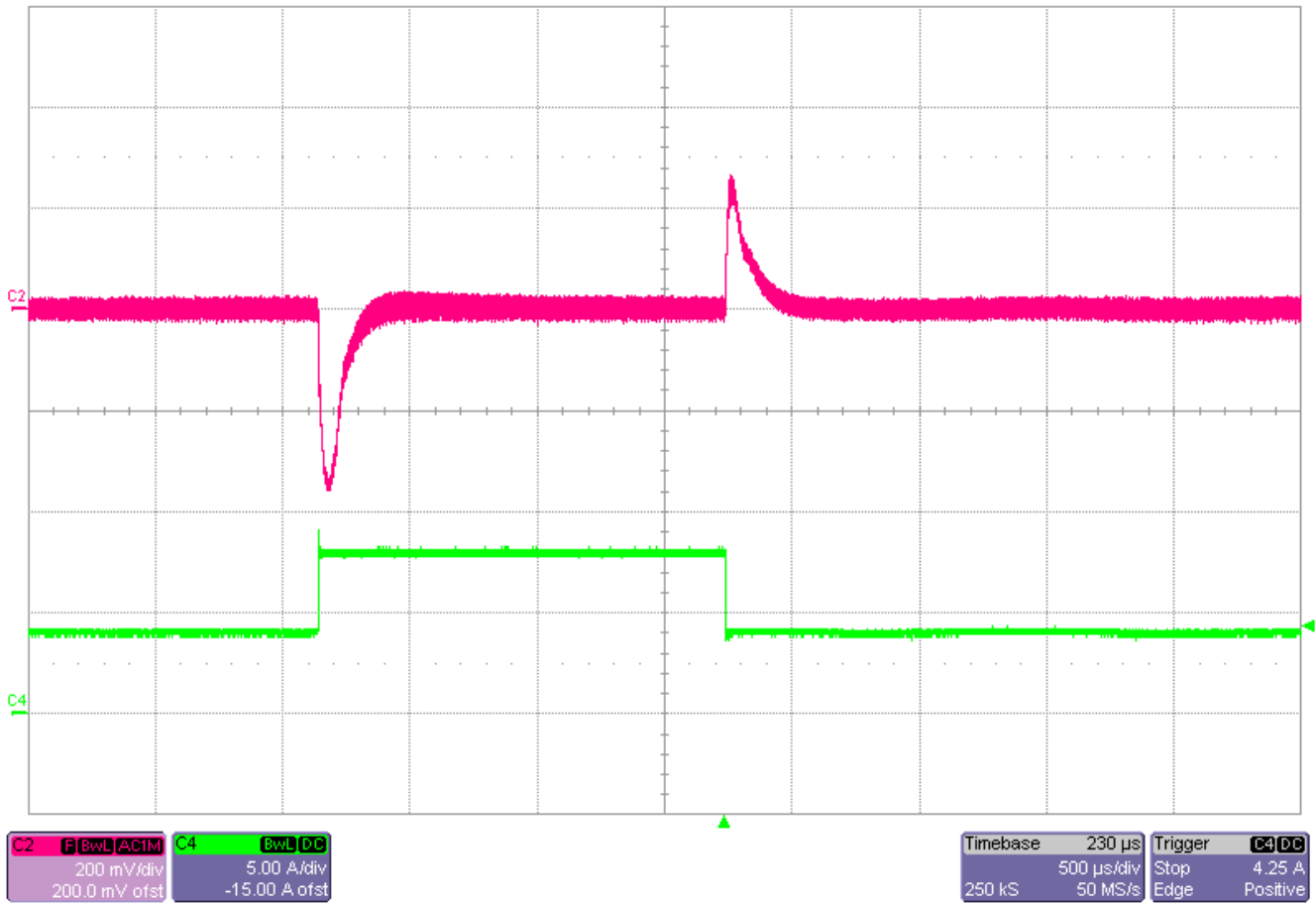


Figure 3-6. 4-A to 8-A Step, 60-VDC Input

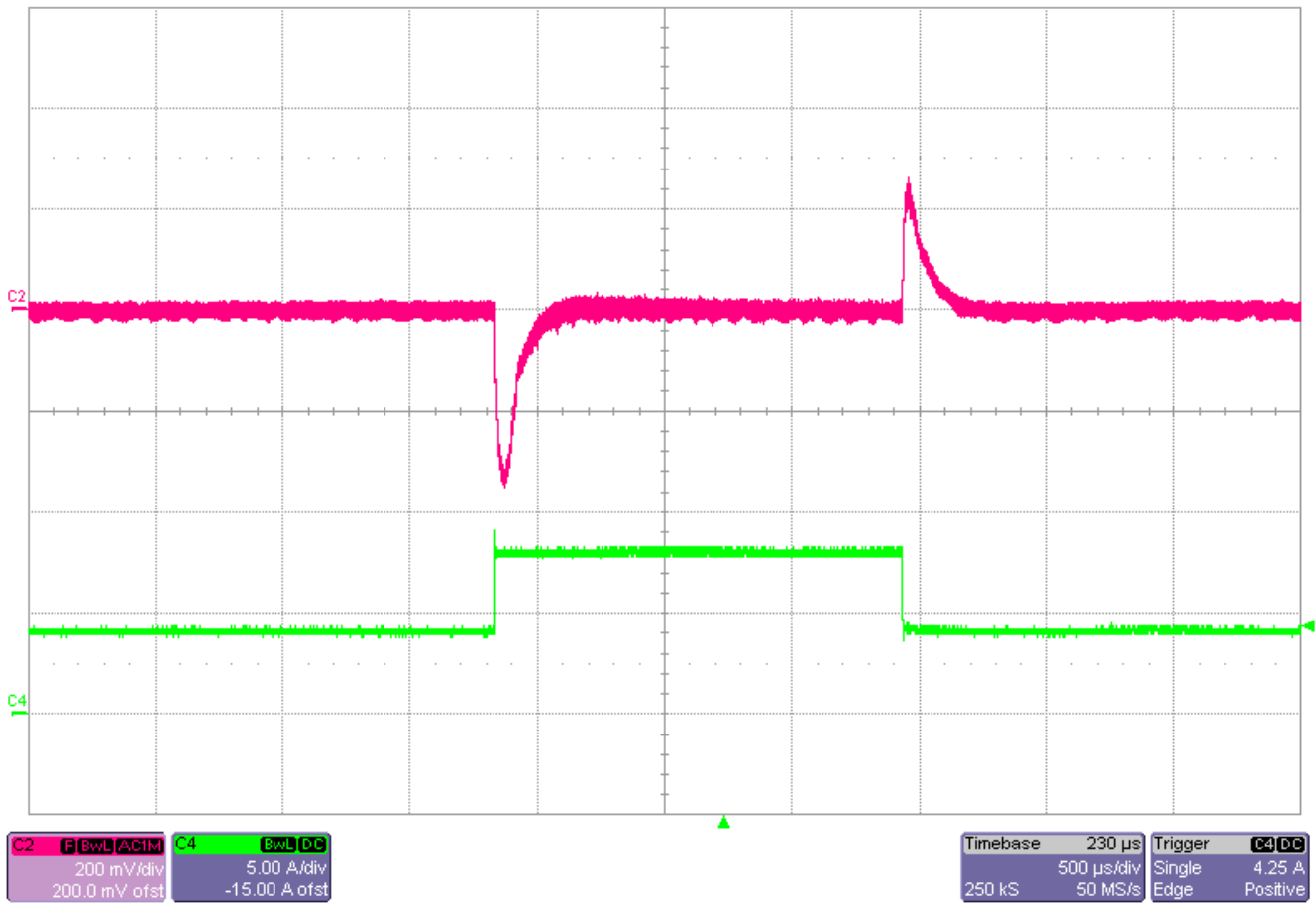


Figure 3-7. 4-A to 8-A Step, 90-VDC Input



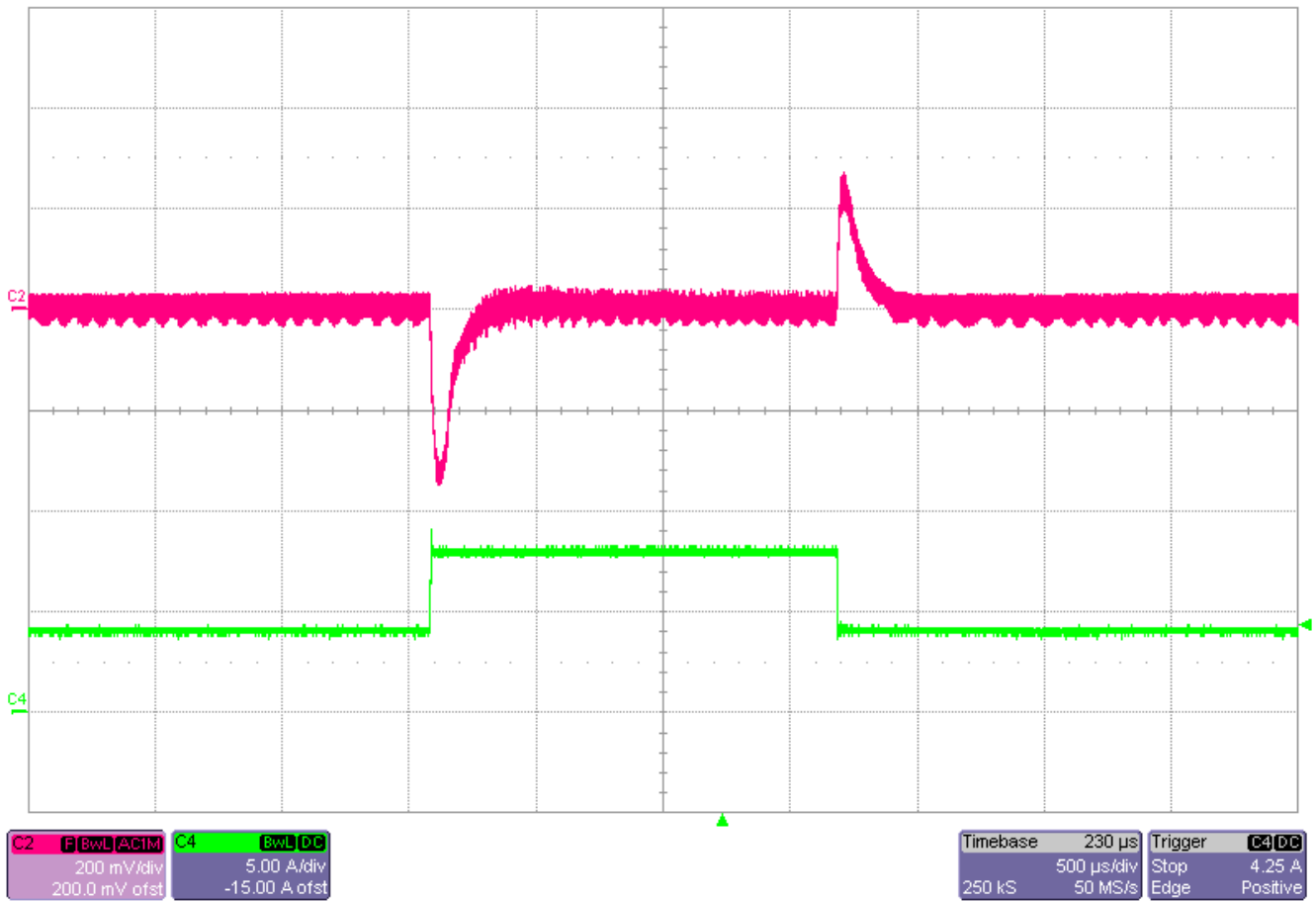


Figure 3-8. 4-A to 8-A Step, 120-VDC Input

### 3.4 Output Voltage at Start-up

Output voltage start-up behavior is shown in the following figure.

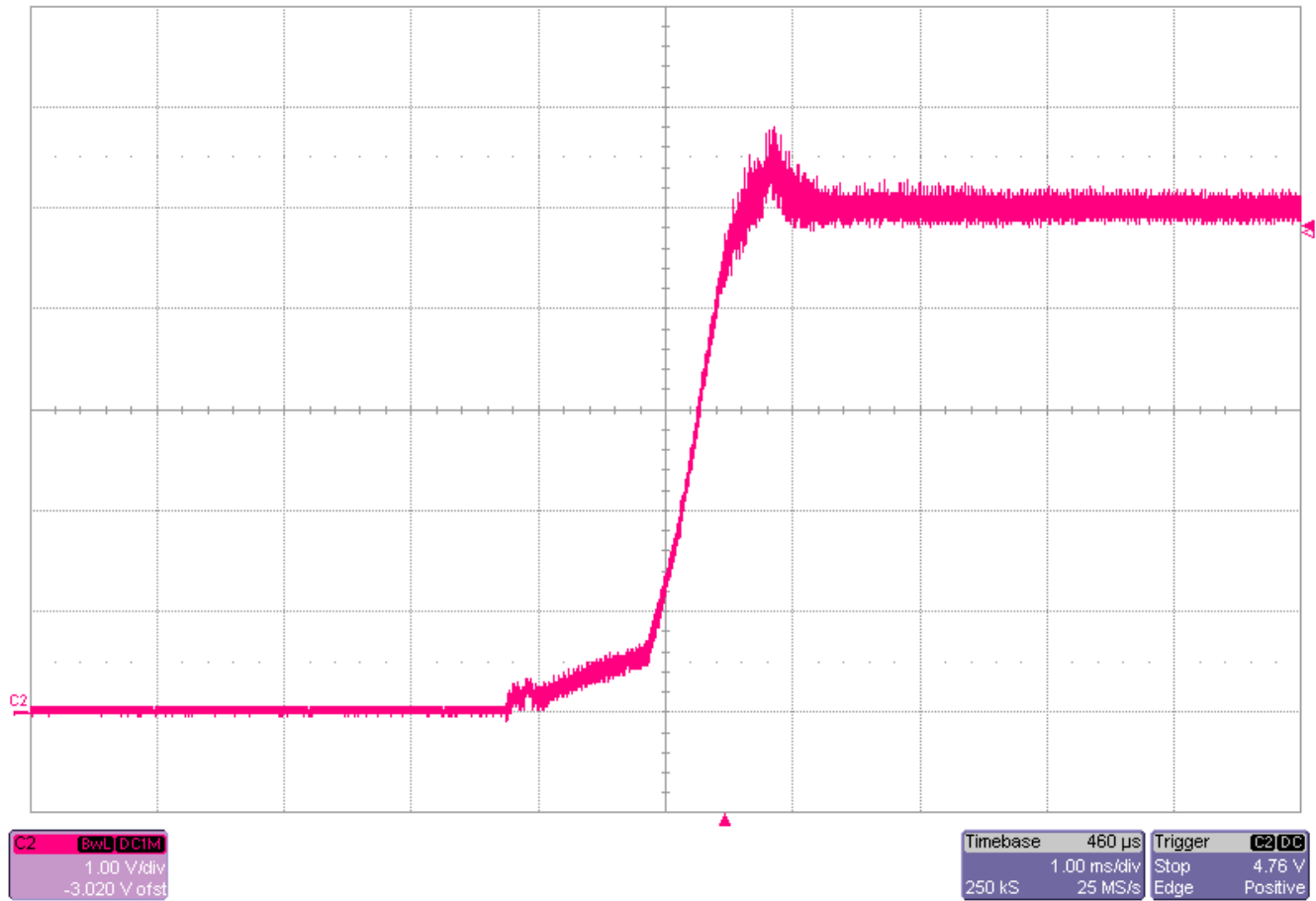


Figure 3-9. 120-V Input, 40-W Load

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated