

PMP40040 Test Results

1 General

1.1 Purpose

This test report is to provide the detailed data for evaluating and verifying the PMP40040 which employs one Buck Converter ---- LMR23625 and a USB Charging Port Controller ---- TPS254900-Q1.

1.2 Reference Documentation

Schematic: PMP40040_Sch.pdf

Gerber: PMP40040_GerberNCdrills.zip

Layer Plot: PMP40040_PCBlayers.pdf

Assembly Drawing: PMP40040_Assy.pdf

CAD File: PMP40040_CAD.zip

BOM: PMP40040_BOM.pdf

1.3 Test Equipment

Multi-meter (current): Fluke 287C

Multi-meter (voltage): Fluke 287C

DC Source: Chroma 62012P-600-8

E-Load: Chroma 63105A module


Oscilloscope: Tektronix DPO3054

Electrical Thermography: Fluke Ti9

2 Performance Data and Waveform


2.1 Efficiency

Vin (V)	Iin (A)	VBUS (V)	Io (A)	Efficiency
9.003	0.026	5.039	0.016	35.09%
8.991	0.325	5.238	0.499	89.45%
8.979	0.672	5.441	0.998	89.99%
8.964	1.059	5.637	1.499	89.01%
8.947	1.499	5.819	1.998	86.69%
8.943	1.594	5.856	2.096	86.08%
12.002	0.021	5.036	0.009	17.38%
11.993	0.251	5.236	0.499	86.78%
11.983	0.514	5.438	0.998	88.11%
11.972	0.808	5.633	1.499	87.29%
11.960	1.134	5.820	1.998	85.75%
11.954	1.204	5.857	2.099	85.41%
14.502	0.020	5.035	0.009	15.10%
14.495	0.213	5.236	0.499	84.61%
14.486	0.432	5.438	0.998	86.73%
14.477	0.676	5.633	1.499	86.28%
14.467	0.947	5.820	1.998	84.89%
14.464	1.005	5.857	2.099	84.57%

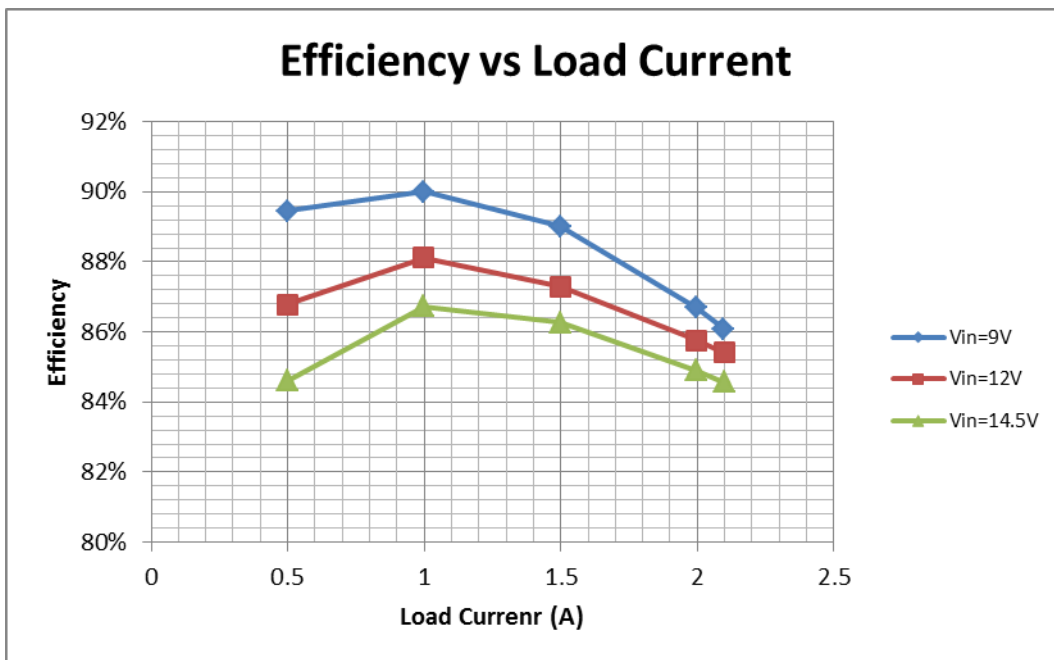

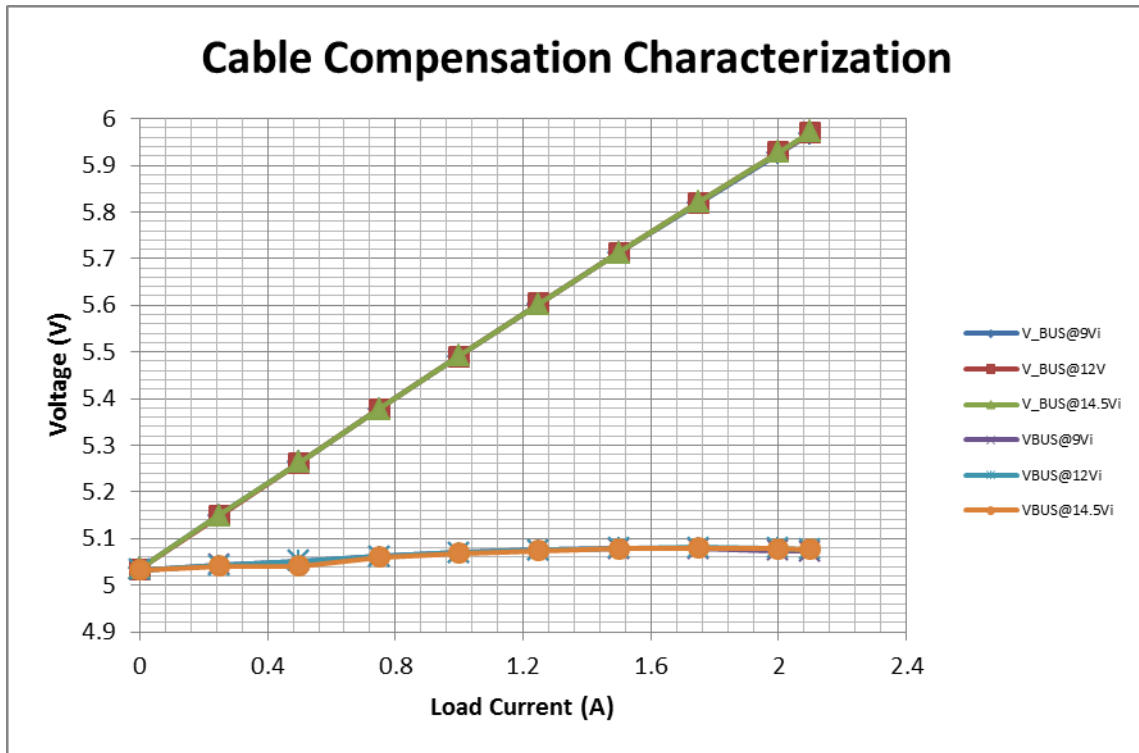
2.2 Cable Compensation

Test the output voltage (V_{BUS}) of DCDC converter with the increase of load current. The resistance of attached cable is about 370mOhm.




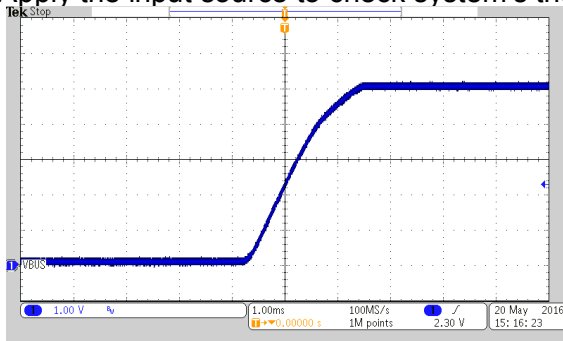2.3 Start Up


Apply the input source to check system's the soft start.




Vin=9V and No Load
CH1: VBUS 1V/Div

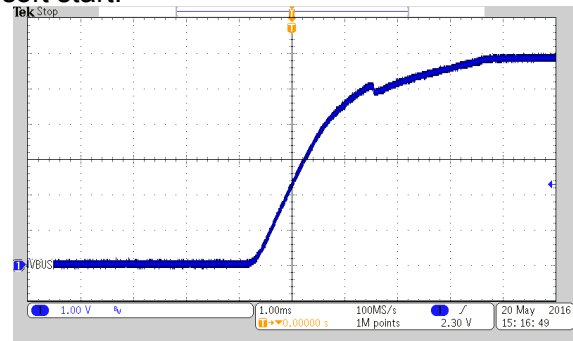


Vin=9V and Full Load
CH1: VBUS 1V/Div

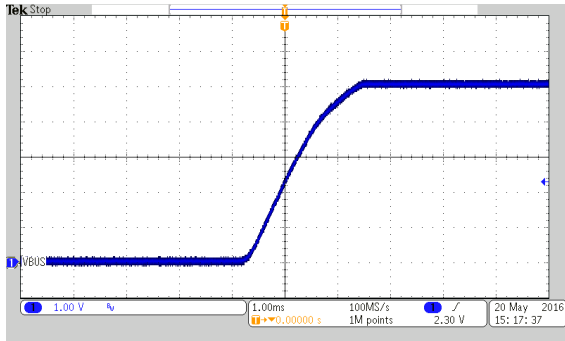


Vin=12V and No Load
CH1: VBUS 1V/Div

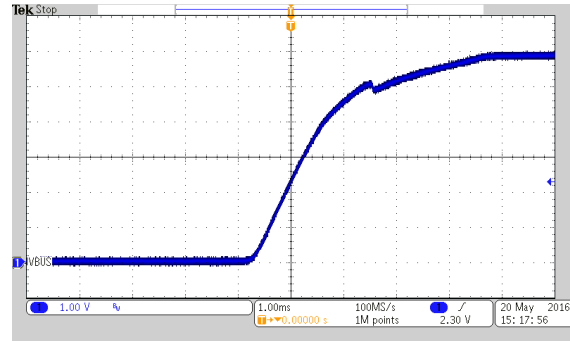

Vin=12V and Full Load
CH1: VBUS 1V/Div

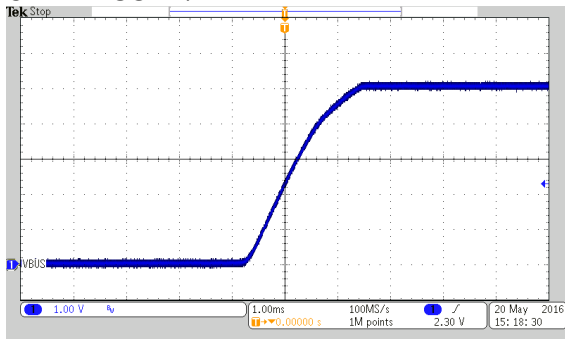


Vin=14.5V and No Load
CH1: VBUS 1V/Div

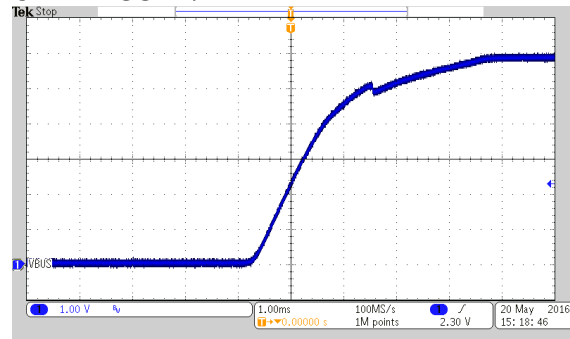


Vin=14.5V and Full Load
CH1: VBUS 1V/Div

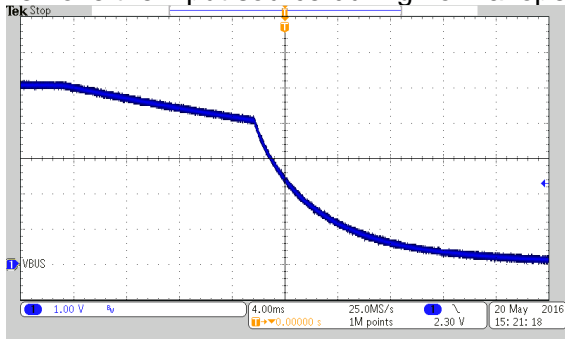2.4 Shut Down


Remove the input source during normal operation.




Vin=9V and No Load
CH1: VBUS 1V/Div

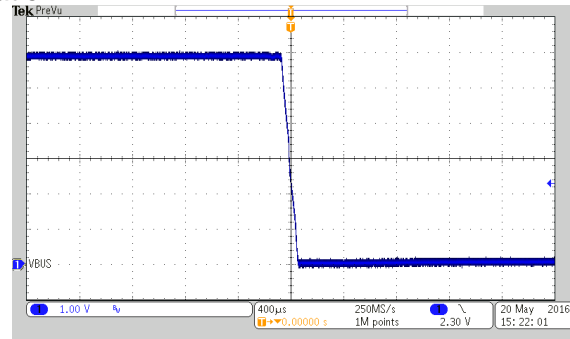


Vin=9V and Full Load
CH1: VBUS 1V/Div

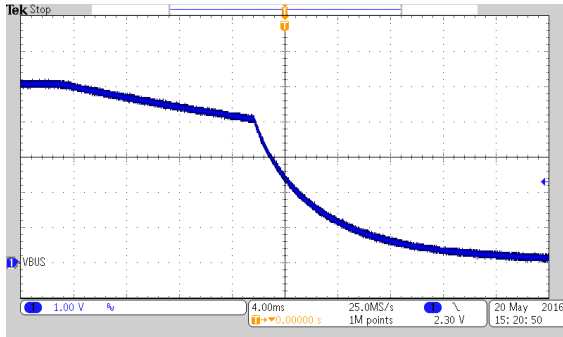


Vin=12V and No Load
CH1: VBUS 1V/Div

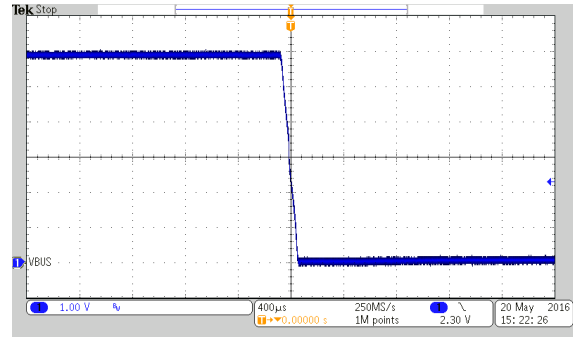

Vin=12V and Full Load
CH1: VBUS 1V/Div

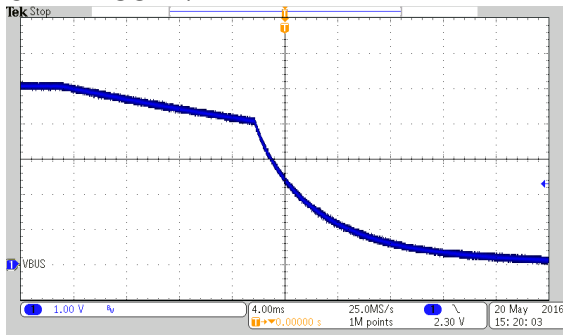


Vin=14.5V and No Load
CH1: VBUS 1V/Div

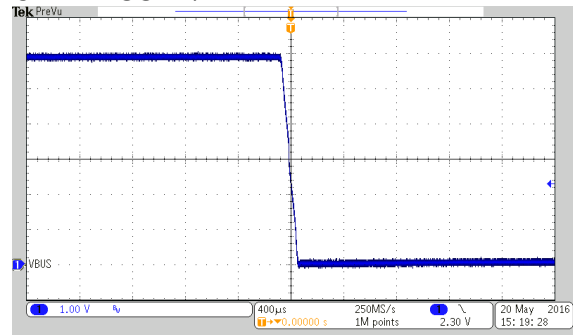


Vin=14.5V and Full Load
CH1: VBUS 1V/Div

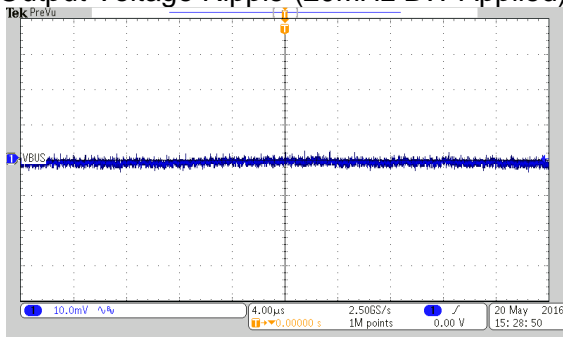
2.5 Output Voltage Ripple (20MHz BW Applied)



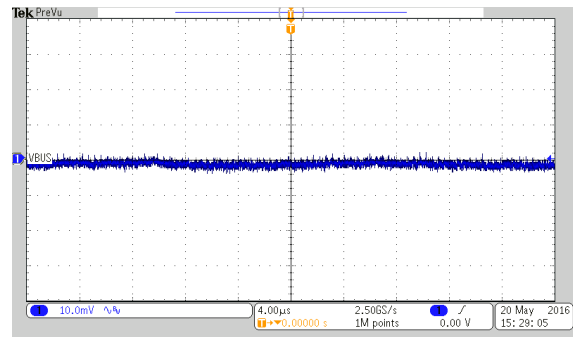
Vin=9V and No Load
CH1: VBUS (AC Coupled) 10mV/Div



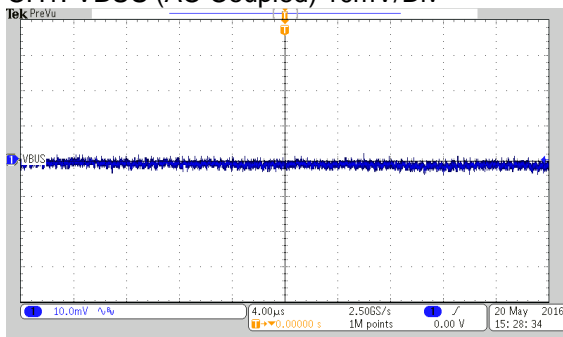
Vin=9V and Full Load
CH1: VBUS (AC Coupled) 10mV/Div




Vin=12V and No Load

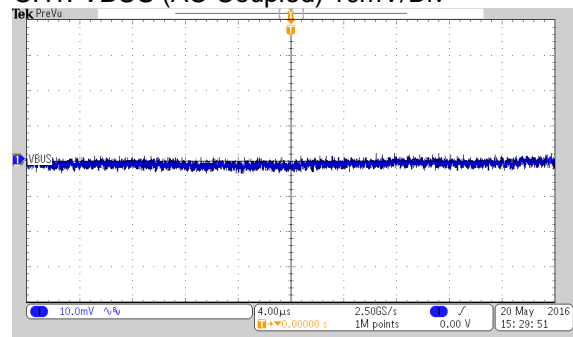

Vin=12V and Full Load

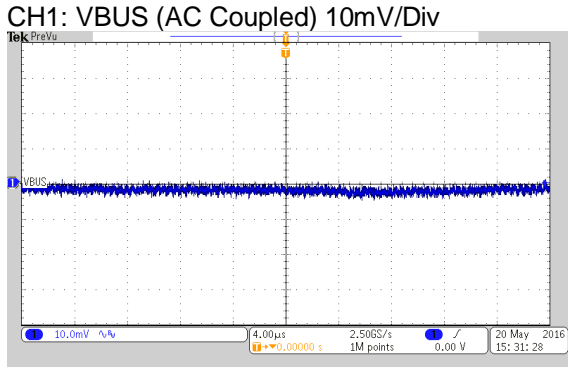


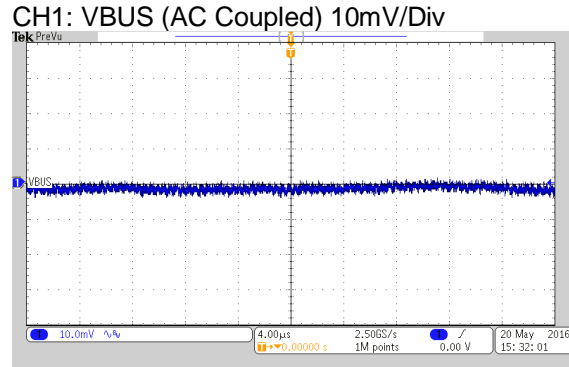Vin=14.5V and No Load
CH1: VBUS (AC Coupled) 10mV/Div




Vin=14.5V and Full Load
CH1: VBUS (AC Coupled) 10mV/Div


2.6 Dynamic Performance

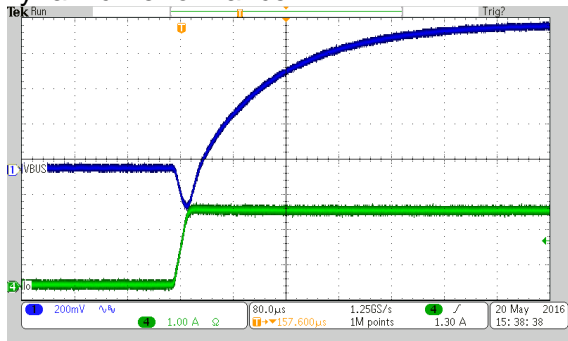

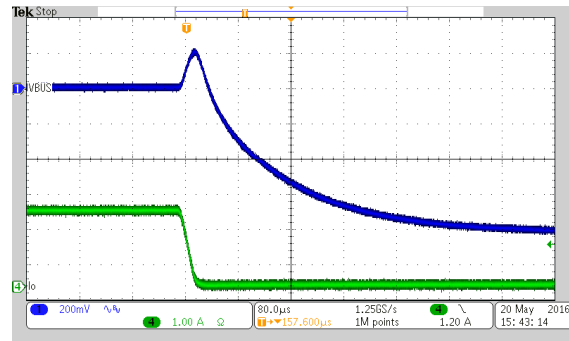
Vin=9V and Load switching from 0A to 2.1A
CH1: VBUS (AC Coupled) 0.2V/Div
CH4: Load Current 1A/Div



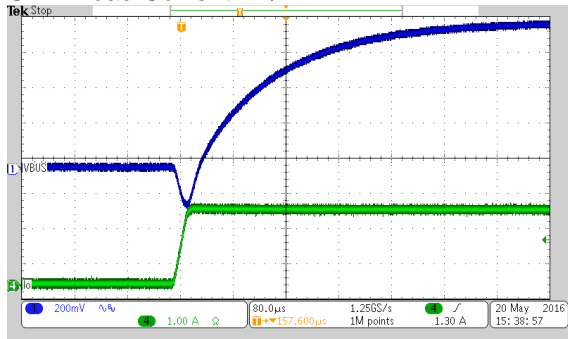
Vin=9V and Load switching from 2.1A to 0A
CH1: VBUS (AC Coupled) 0.2V/Div
CH4: Load Current 1A/Div



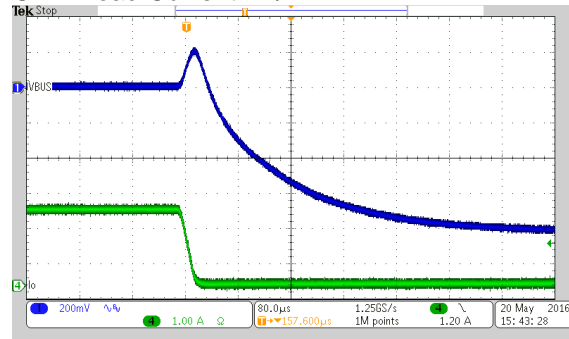
Vin=12V and Load switching from 0A to 2.1A
CH1: VBUS (AC Coupled) 0.2V/Div
CH4: Load Current 1A/Div



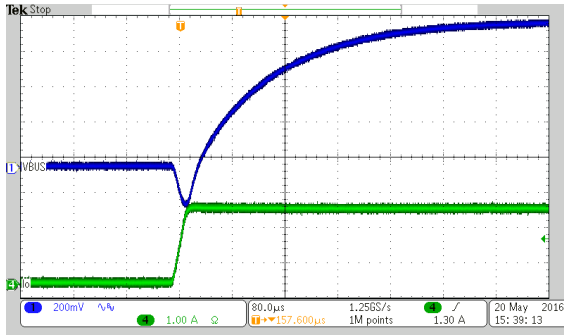Vin=12V and Load switching from 2.1A to 0A
CH1: VBUS (AC Coupled) 0.2V/Div
CH4: Load Current 1A/Div



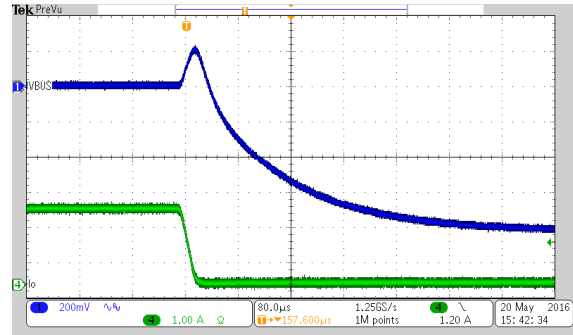
Vin=14.5V and Load switching from 0A to 2.1A
 CH1: VBUS (AC Coupled) 0.2V/Div
 CH4: Load Current 1A/Div



Vin=14.5V and Load switching from 2.1A to 0A
 CH1: VBUS (AC Coupled) 0.2V/Div
 CH4: Load Current 1A/Div

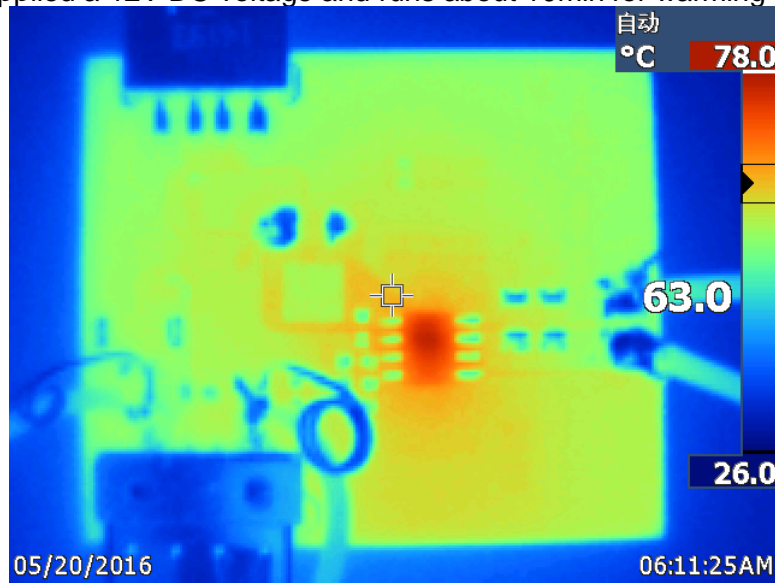2.7 Thermal Performance

The board is applied a 12V DC voltage and runs about 10min for warming up.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated