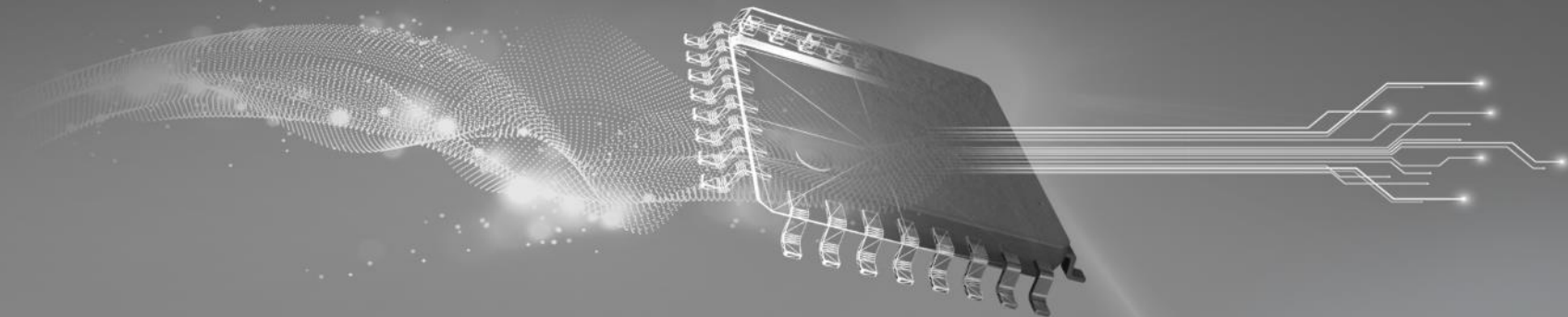


TI TECH DAYS




Gallium nitride: Understanding TI's portfolio and how to use it to enhance industrial designs

Fei Yang


High Voltage Power - GaN Applications Engineer

GaN vs. other power devices


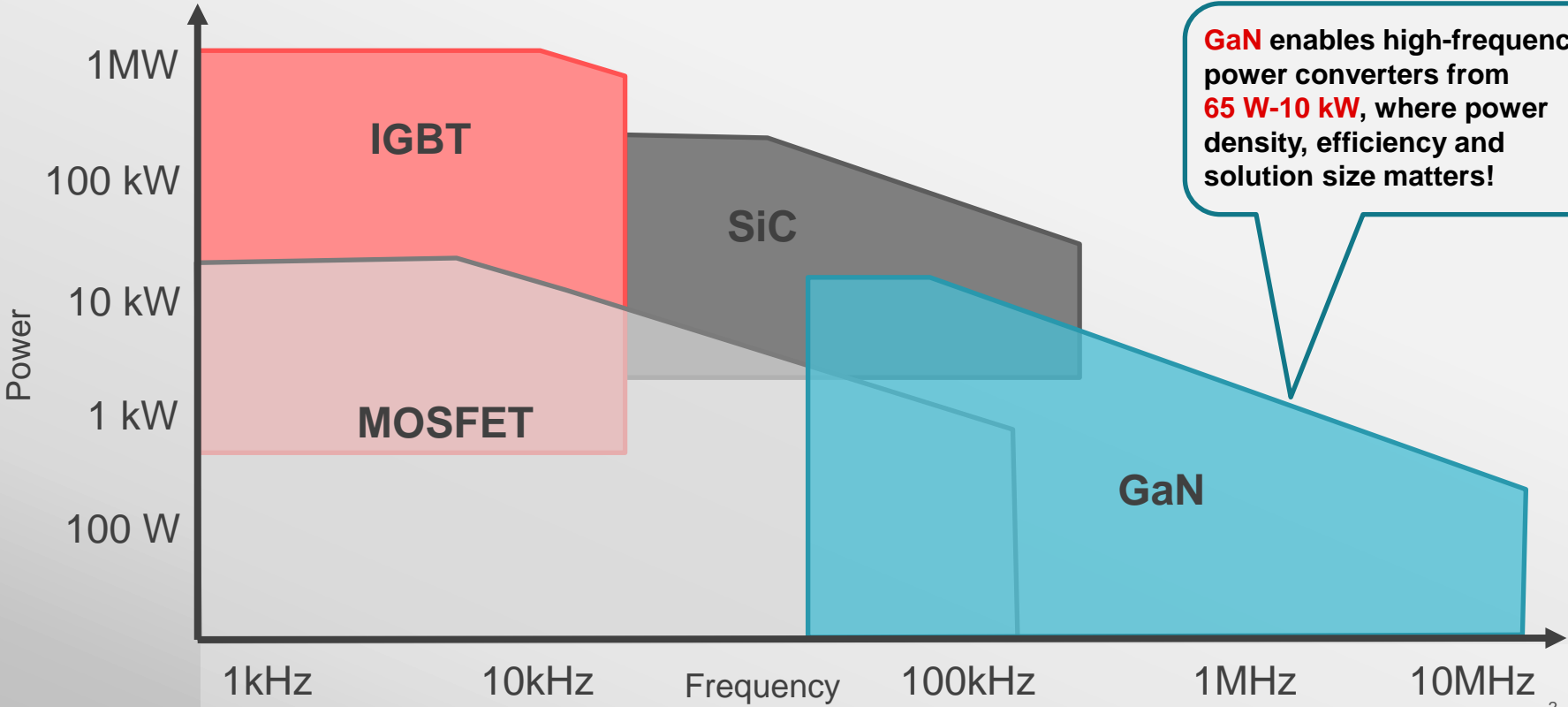


GaN enables high-frequency power converters from 65 W-10 kW, where power density, efficiency and solution size matters!

GaN comparison to Si and SiC

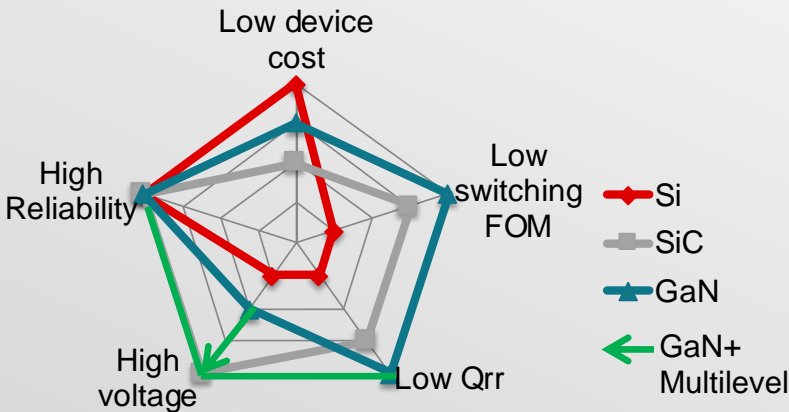

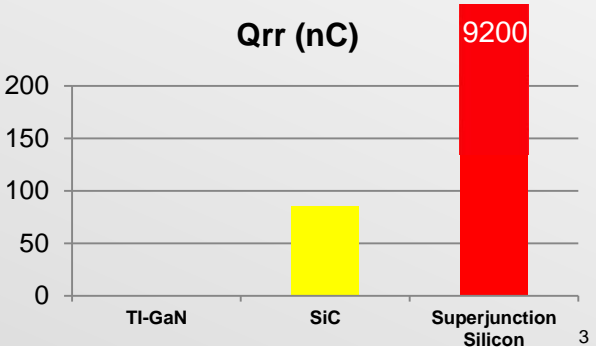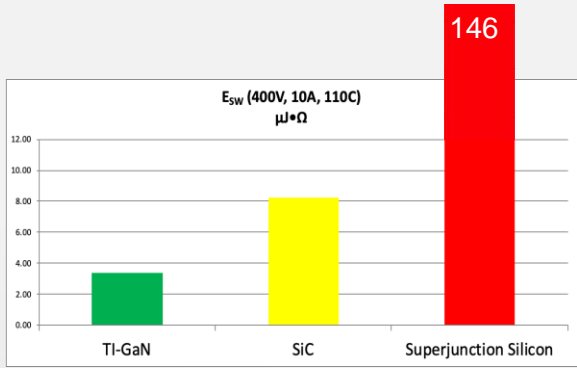GaN offers the best overall cost and performance



GaN applications: from watts to kW

GaN applications

65 W-4 kW

AC/DC PSU

- Server, telecom and 5G PSU
- Industrial power AC/DC
- USB Type-C®, DTV, gaming



<2k W

Robotics

- Robots and cobots
- Industrial transport
- Factory automation



>5 kW

Grid

- Energy storage
- Solar energy and UPS
- Grid test and measurement



3.3-22 kW

Automotive

- Onboard charger
- HV isolated DC/DC converter



Why TI GaN

>2X higher density vs. Superjunction

[LMG3410R150](#), [LMG3410R070](#),
[LMG3410R050](#), [LMG3422R030](#)

- 99%-efficient PFC
- MHz HV DC/DC
- TI analog and digital controllers

No cooling fans and 85% smaller heatsinks

[LMG3410R050](#), [LMG3422R030](#)

- 99%-efficient inverters
- No cooling fan
- Integration of drive and motor

3X higher density vs IGBT and 1.25X vs. SiC

[LMG3410R050](#), [LMG3422R030](#)

- Multi-level topologies
- 3-Phase grid and >900 V DC Bus
- Scalable


50% lower cost than SiC

[LMG352xR030-Q1](#)

- Up to 2.2 MHz switching frequency
- Support for 400/800 V battery
- AECQ-100 Grade 1

Using GaN in: AC/DC PSU designs

2 kW silicon PFC


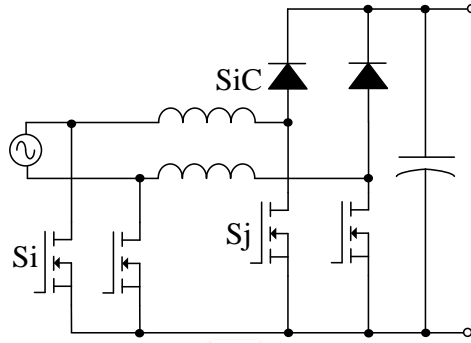


2.8x higher density


2 kW GaN PFC



40% reduction in component count

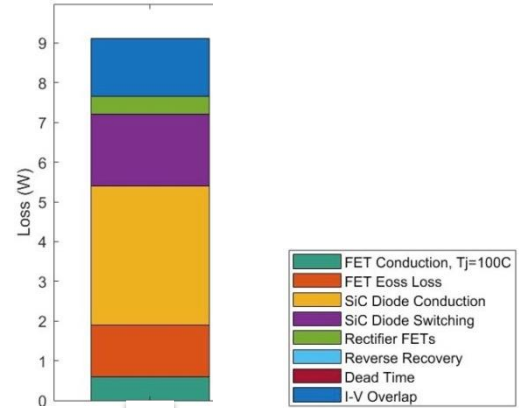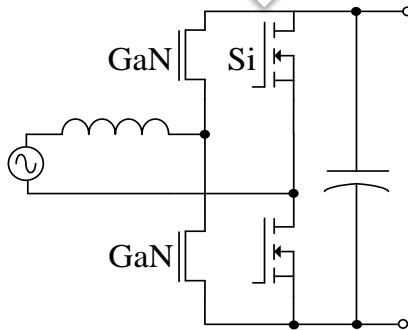


50% lower losses

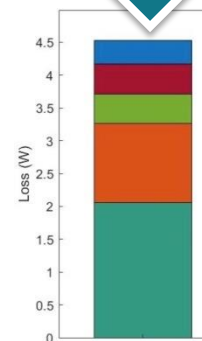

Reducing power magnetics size with GaN

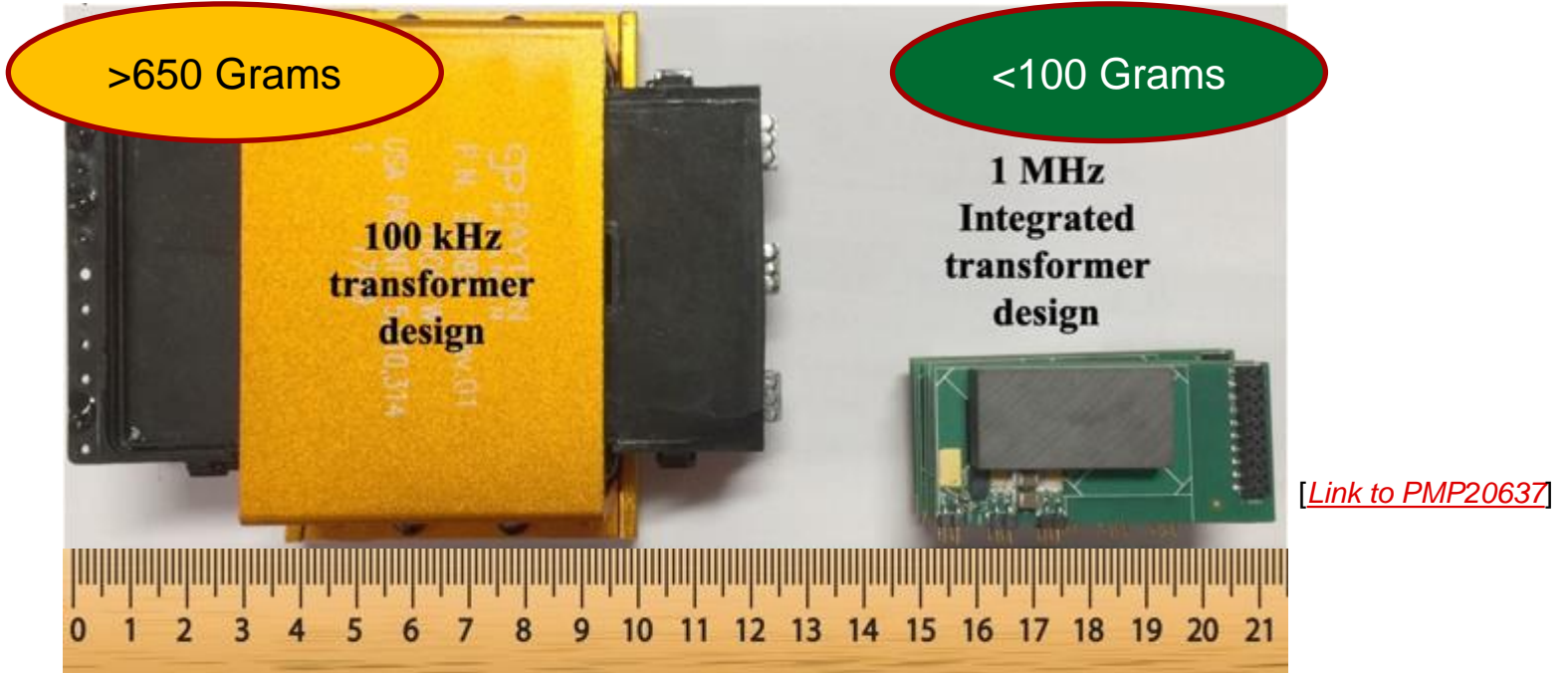Compared with 100 kHz LLC design, the 1 kW transformer is
6X smaller



Using GaN in: servo drive designs

Silicon servo drive
@ 1.5 kW



Cooling Area: Fan + 145 x 82 x 42 mm



Integrated GaN drive
@ 1.2 kW



Cooling Area: No fan: 80 x 46 x 20 mm

- 75% reduction factory floor cabinets
- 90% less power and communication cabling
- 85% smaller heatsink and **NO FAN**


• **in 6 axis robotic system*

Using GaN in: three-phase grid applications

900 V - 5 kW Bi-directional AC/DC converter with TI GaN



- 3X power density improvement over IGBT
- 1.25X power density improvement over SiC – at a lower solution cost

Typical operating conditions	IGBT	SiC	TI GaN
Frequency (kHz)	20	100	140
Open frame power density (W/in ³)	73	170	211
Efficiency (%)	98.3	98.9	99.2

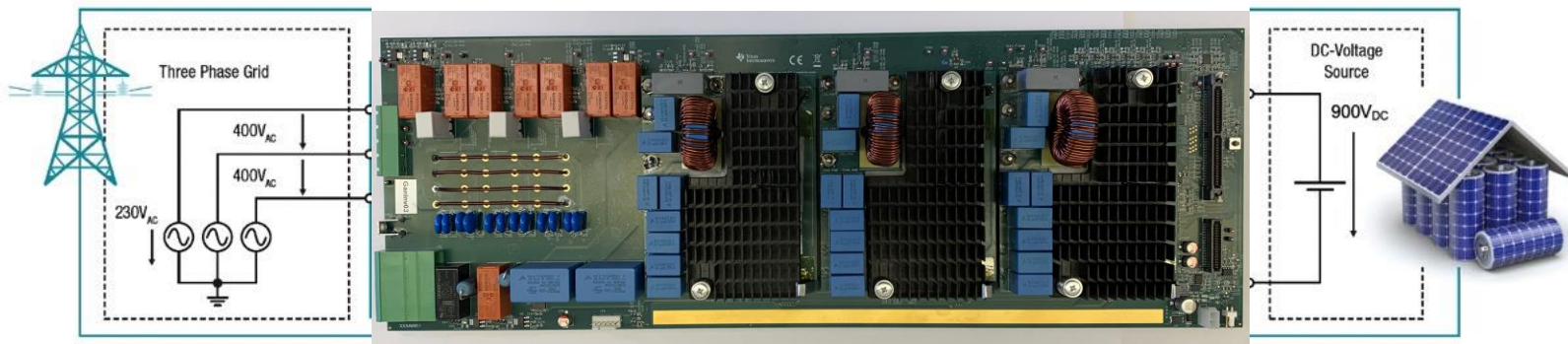

470 mm x 162 mm x 51 mm

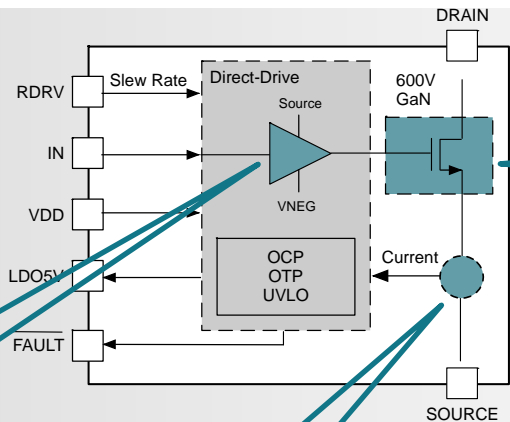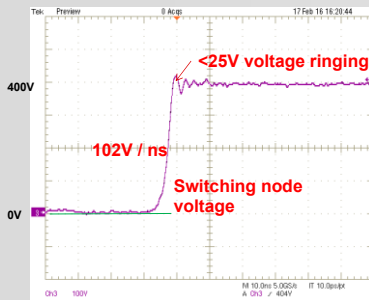Driver and protection integration: why is it important?




600-V GaN FETs


150 m Ω
70 m Ω
50 m Ω
30 m Ω

Integrated driver cuts losses by 50% compared to discrete GaN
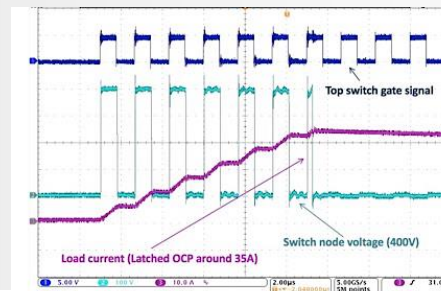
<math><100\text{ ns}</math> short-circuit protection with zero external components




Integration simplifies BOM and cost

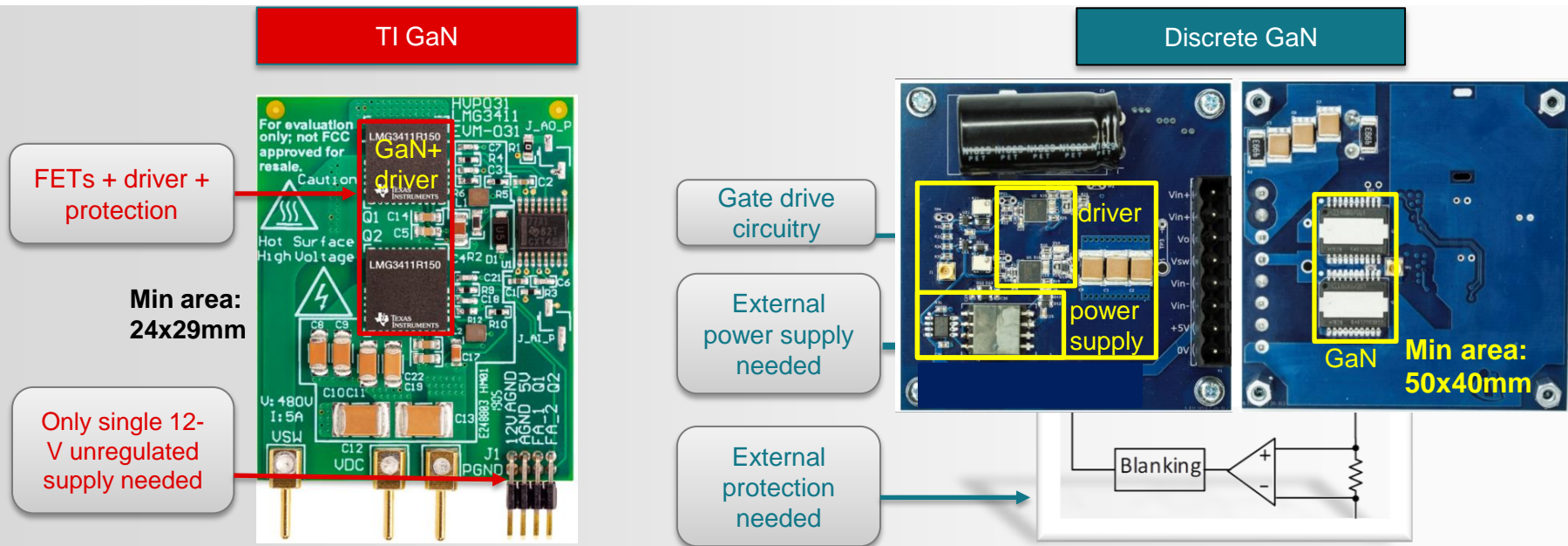


TI GaN: lifetime reliability

Multi-kW lifetime testing

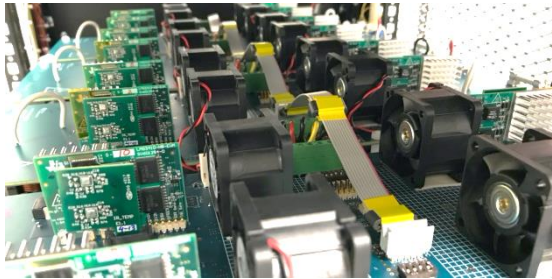- >40 million hours and >5 GWhr of energy converted
- <1 FIT over 10-year life
- ZERO field returns



Self-protected in extreme conditions

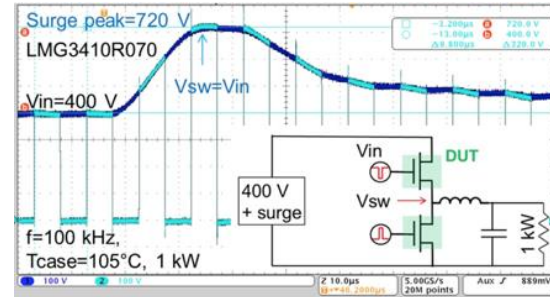

- Designed to withstand 720-V surge and lightning
- <100 ns short-circuit protection
- Thermal protection to 150°C
- Digital fault reporting for system diagnostics

LMG341x portfolio: GaN FET + integrated driver

Power delivery

Motor Drives, FAC, BA

OBCs and energy storage



ACF



PFC



LLC



Inverter



Bi-directional AC/DC, Multi-level

65 W – 100 W

400 W – 3 kW

5 kW – 11.6 kW

150mΩ

LMG341xR150

70 mΩ

LMG341xR070

50 mΩ

LMG341xR050
LMG342xR050

30 mΩ

LMG342xR030



- 600-V GaN FETs
- Fully integrated protection with fault alert and integrated gate driver
- 100% TI-owned manufacturing, supply and cost

LMG342x: next-generation 600-V GaN FETs with integrated driver + protection

Features

- **50mΩ, and 30mΩ** $R_{DS(on)}$ Drain to Source
- **Integrated GaN gate driver:**
 - TI direct-driver technology switches the GaN directly
 - Internal buck-boost generates negative drive voltage
 - **>200 V/ns CMTI** and **2.2 MHz** switching frequency
 - Only single **7.5-19 V** unregulated supply needed
 - 5V LDO to power external isolator
- **Ideal diode mode** Reduces third quadrant losses by 66%
- **External resistor sets drive strength (RDRV pin):**
 - **30 V/ns to 150 V/ns** adjustability
 - No compromise in gate-drive inductance
- **Fault monitoring and protection:**
 - Cycle-by-Cycle over-current protection (<100 nS)
 - Latched short circuit protection (<100 ns)
 - Over-temperature protection
 - UVLO protection
- **Reporting:**
 - Variable duty cycle PWM **temperature reporting**
 - Fault indication

Functional block diagram and package

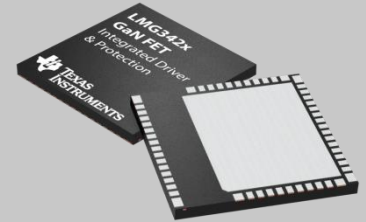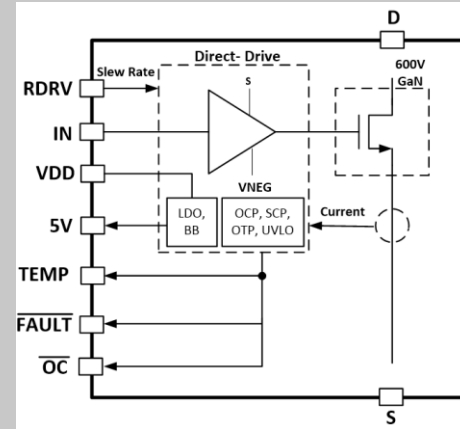

12x12mm QFN

(Thermal pad connected to source)

- **50mΩ:** [LMG342xR050](#)
- **30mΩ:** [LMG342xR030](#)



**Samples and EVM
available now**

Additional resources

Technical content

Direct-drive configuration for GaN devices



[\[Link\]](#)

GaN drives energy efficiency to the next level



[\[Link\]](#)

Half the space, double the power: How gallium nitride is revolutionizing robotics, renewable energy, telecom and more

[\[Link\]](#)



Training videos




[\[Link\]](#)



[\[Link\]](#)



[\[Link\]](#)

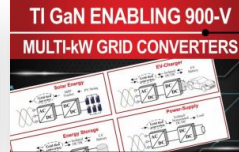


[\[Link\]](#)



[\[Link\]](#)

Motor Drive Training

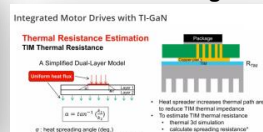

[\[Link\]](#)

Design tools

GaN reference designs

[99% efficient 3-phase inverter](#)

[1MHz 1.6kW CrM Totem Pole PFC](#)

[Bidirectional 3.3kW CCM Totem Pole PFC](#)



GaN plug-in daughter cards

[LMG3411R150 Daughter Card](#)

[LMG3411R070 Daughter Card](#)

[LMG3411R050 Daughter Card](#)

[GaN Buck-Boost Motherboard](#)



ti.com/gan



©2020 Texas Instruments Incorporated. All rights reserved.

The material is provided strictly "as-is" for informational purposes only and without any warranty.
Use of this material is subject to TI's **Terms of Use**, viewable at [TI.com](https://www.ti.com)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2020, Texas Instruments Incorporated