



Texas Instruments

PMP4344 Test Procedure

China Power Reference Design

REV A


11/07/2012



# **1 GENERAL**
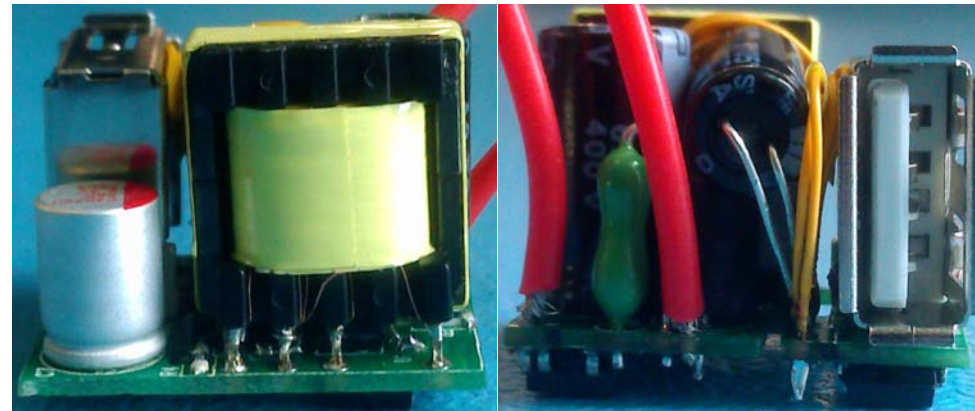
## **1.1 PURPOSE**

To provide detailed data for evaluating and verifying the PMP4344, which uses TI new Primary Side Controller UCC28710 for USB charger with 22mmx21mmx20mm. The below photo shows this demo board.



## **1.2 REFERENCE DOCUMENTATION**

Schematic PMP4344\_SCH.PDF

Assembly PMP4344\_PCB.PDF

BOM

Promotion tools

## **1.3 TEST EQUIPMENTS**

Power-meter: YOKOGAWA WT210

Multi-meter(current): Fluke 8845A

Multi-meter(voltage): Fluke 187

AC Source: Chroma 61530


LED load: Chroma 63110A module

Testing demoboard

## 2 INPUT CHARACTERISTICS


Otherwise Specified, the test is under the condition With 1m USB cable

### 2.1 STANDBY POWER

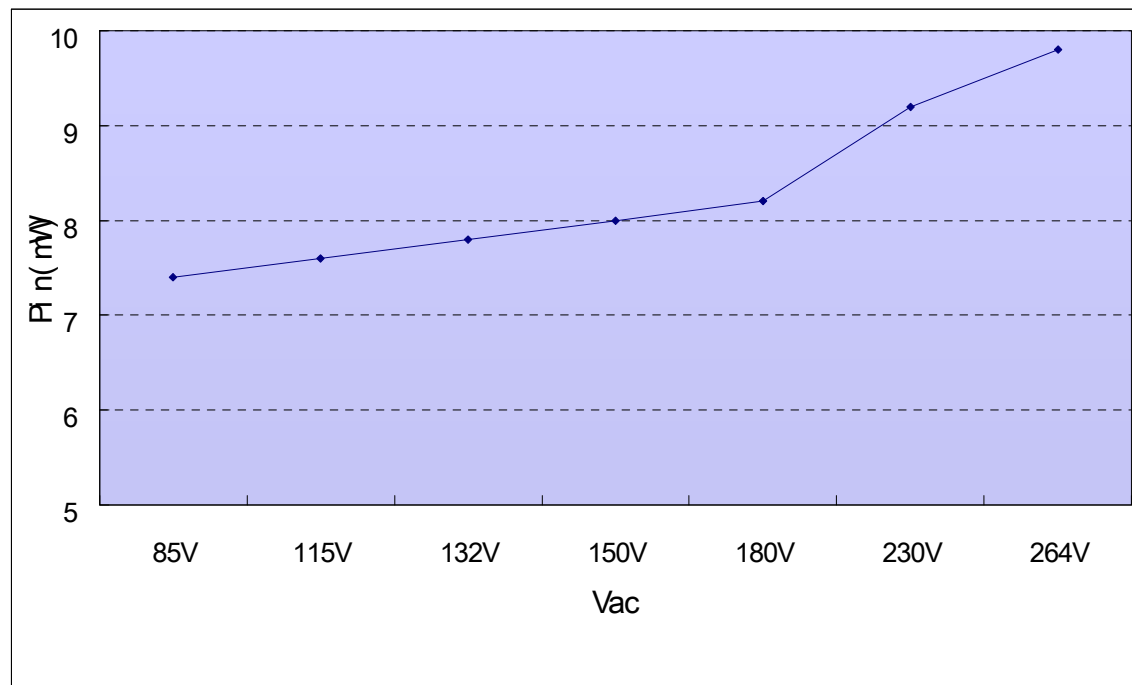


## 2.2 LOAD AND INPUT VOLTAGE VS EFFICIENCY

Notes: efficiency test is based USB port

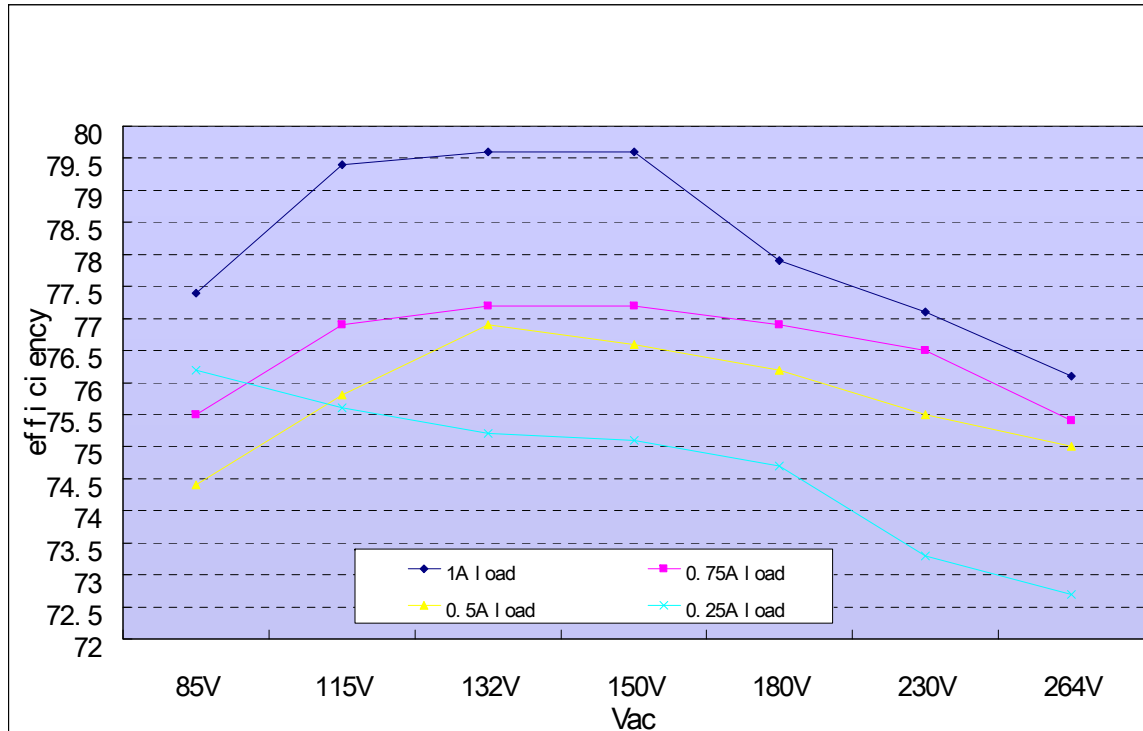


## 2.3 AVERAGE EFFICIENCY AT 0.25A, 0.5A, 0.75A AND 1A

Notes: efficiency test is based USB port

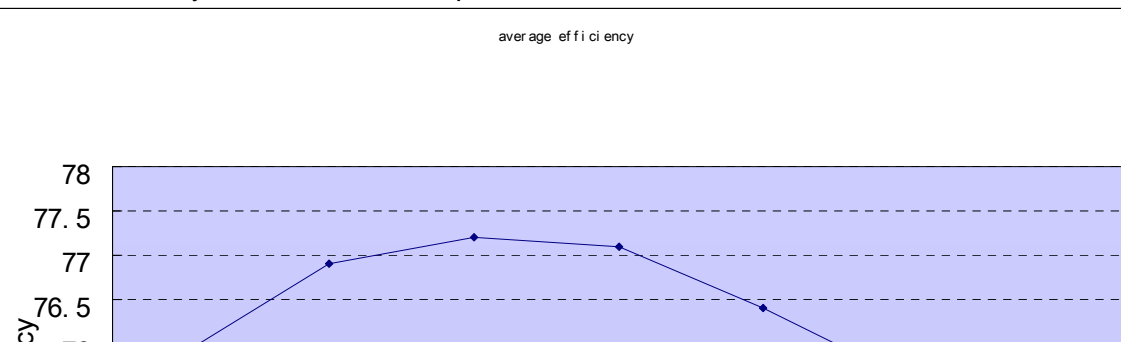

## 2.4 EFFICIENCY VS LOAD

Notes: efficiency test is based USB port

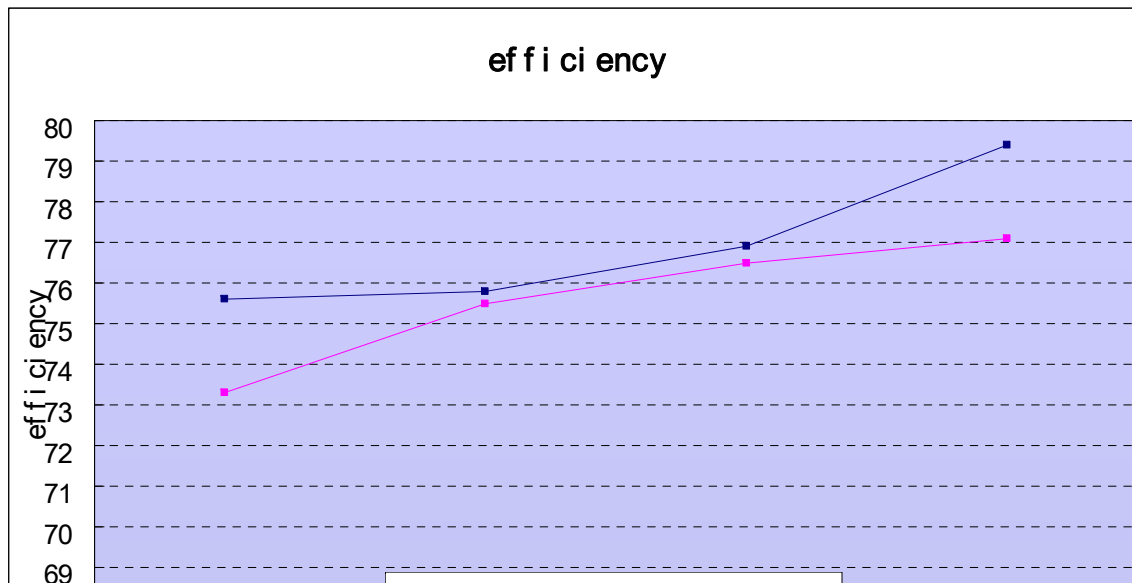


**2.5 INPUT CURRENT**

Vin(Vac)	Freq(Hz)	Iin(Arms)	Pass/Fail
85	60	<b>0.138</b>	

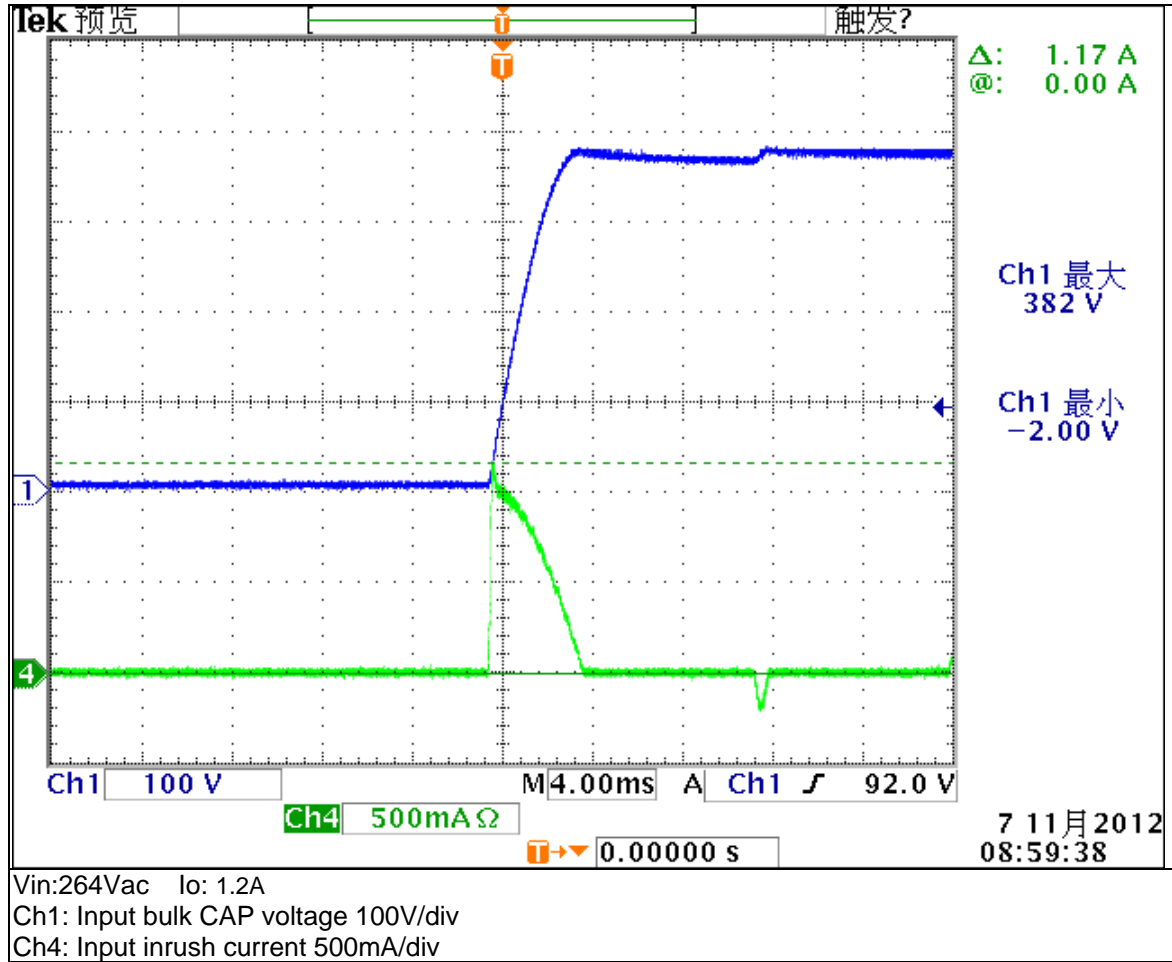**2.6 INPUT INRUSH CURRENT**

Max inrush current: 1.17A @264Vac and 1.2A load




### 3 OUTPUT CHARACTERISTICS

#### 3.1 STARTUP TIME




Input voltage	Output current	Startup time	Pass/Fail
115Vac	1A	<b>79.6mS</b>	
230Vac	1A	<b>65.6mS</b>	

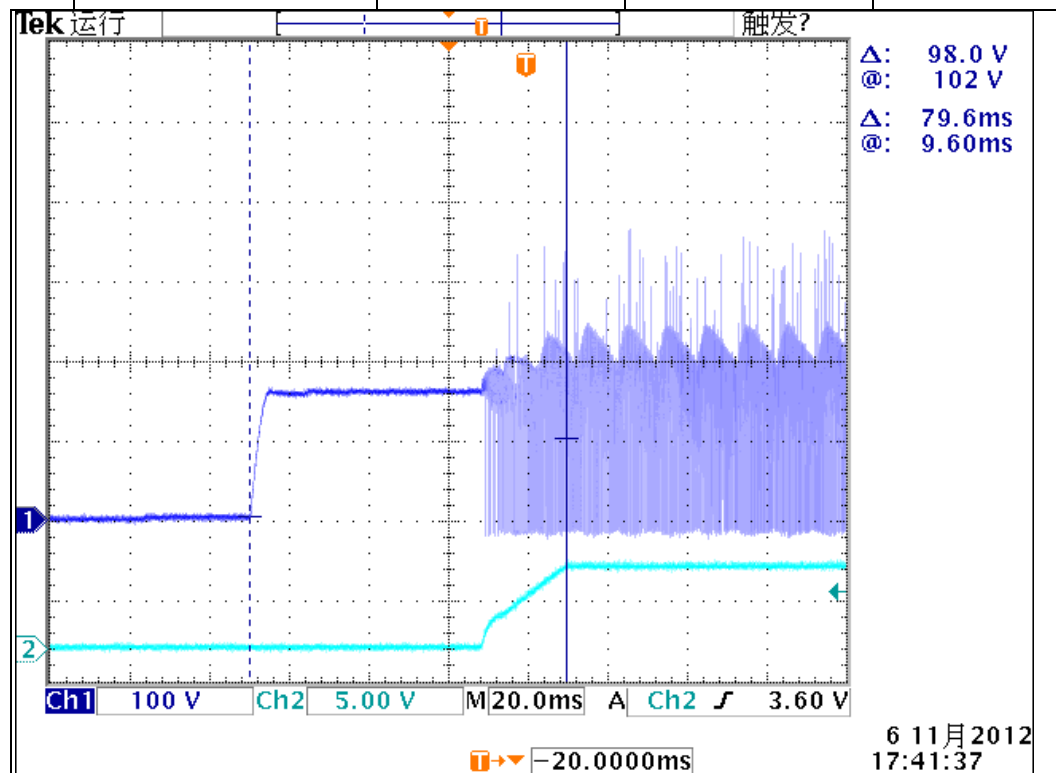


Vin:115Vac Io: 1A  
 Ch1: MOSFET's drain voltage, 100V/div  
 Ch2: output voltage, 5V/div


6 11月 2012  
 17:41:37

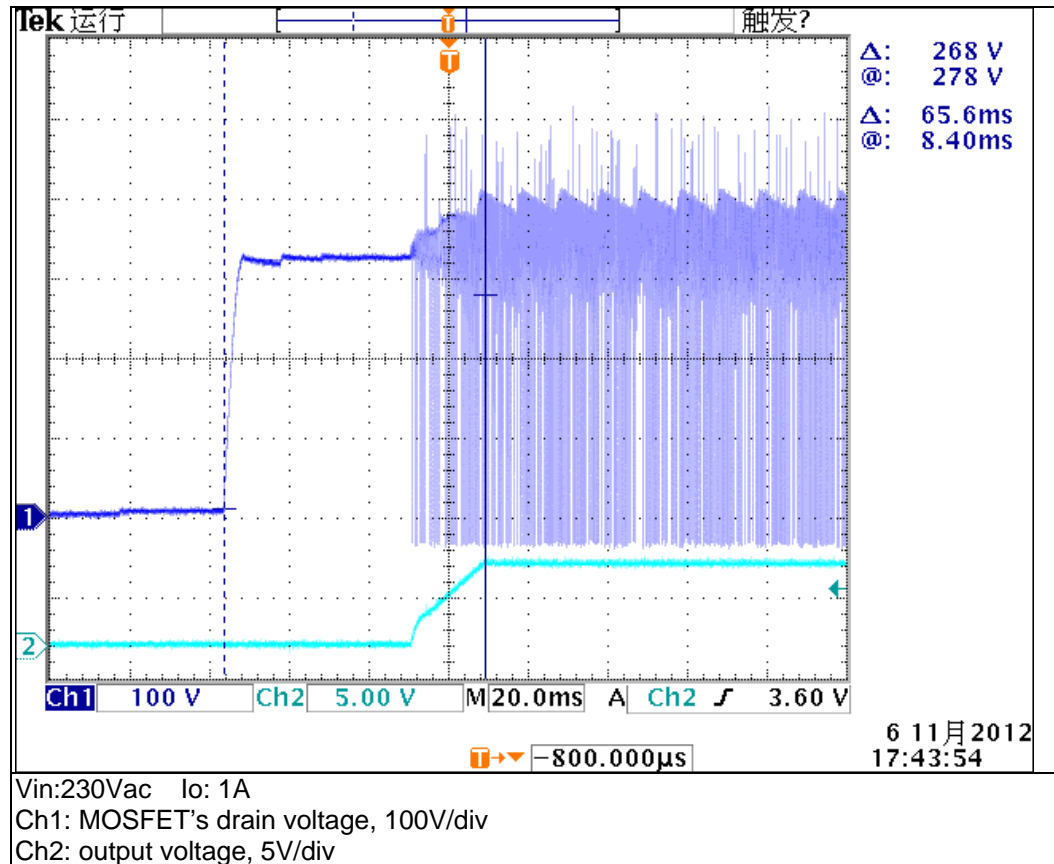

### 3.2 OUTPUT VOLTAGE RISE TIME


Input voltage	Output current	Startup time	Pass/Fail
115Vac	1A	<b>21.6mS</b>	
230Vac	1A	<b>18.8mS</b>	

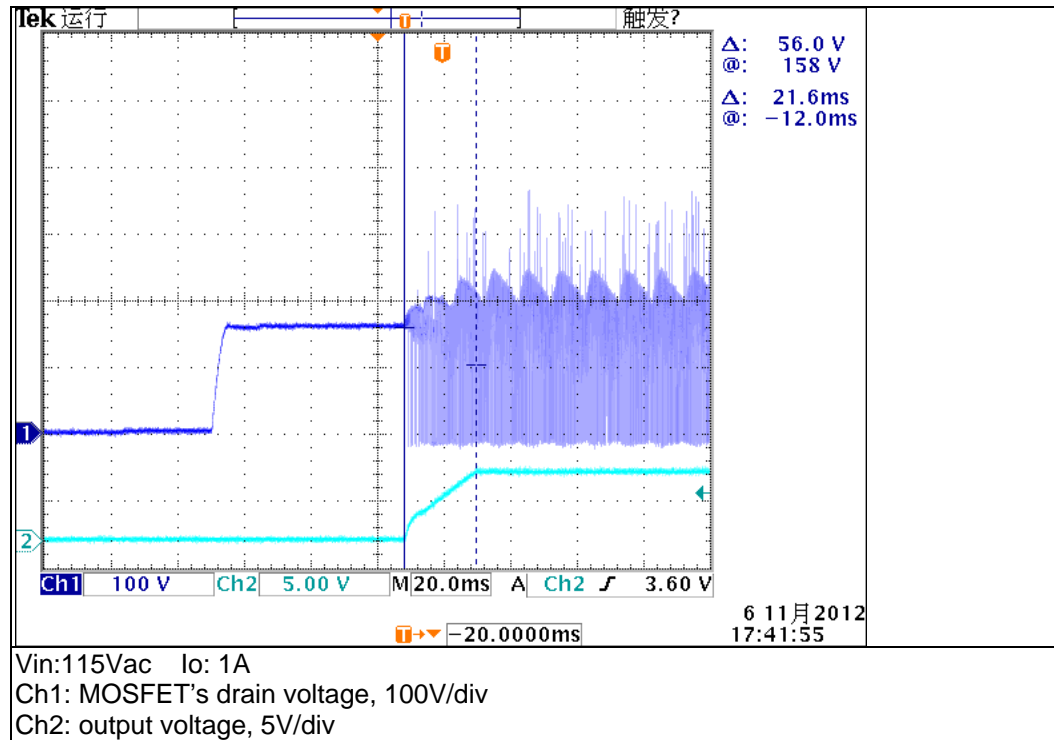

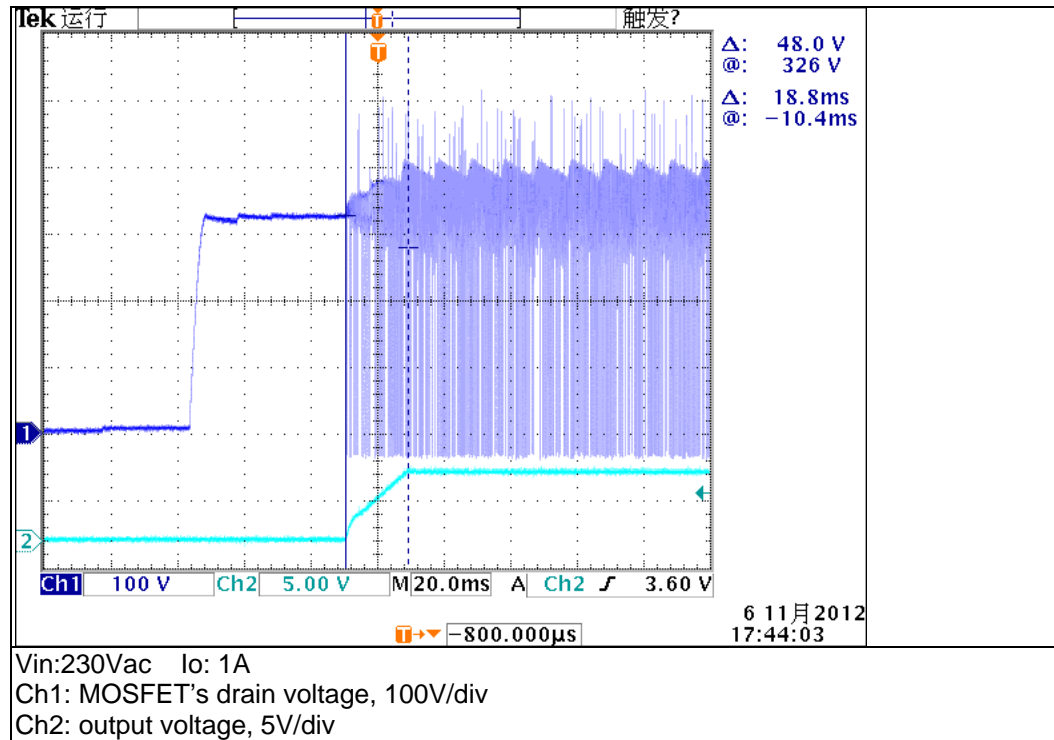


### 3.3 OUTPUT VOLTAGE OVERSHOOT

Input voltage	Output current	overshoot voltage	Pass/Fail
115Vac	0A	<1%	
230Vac	0A	<1%	

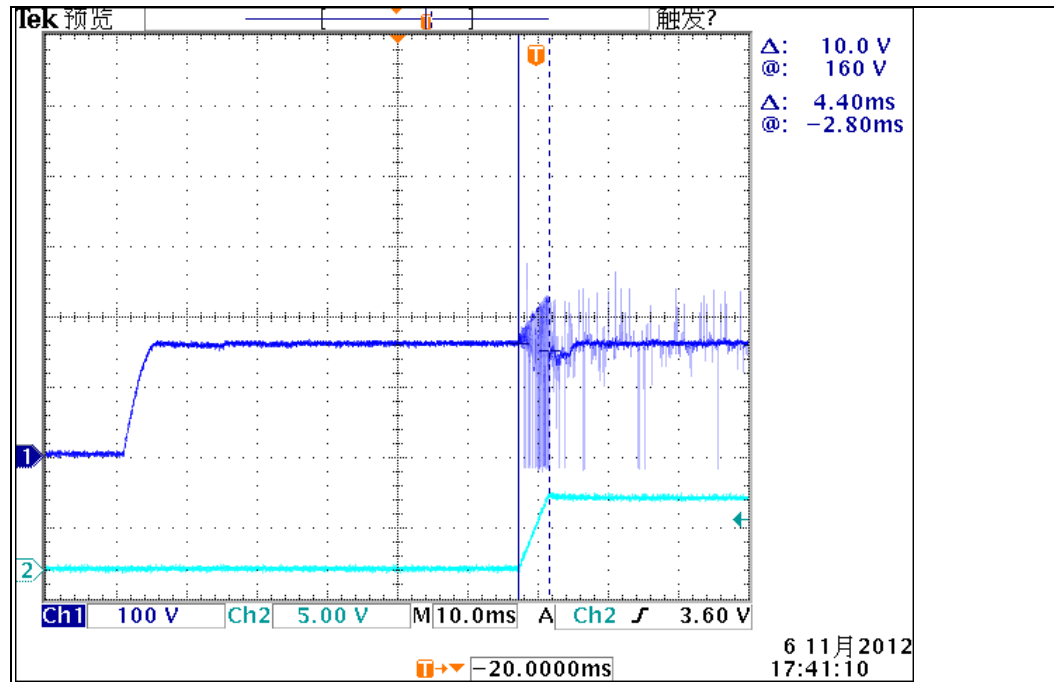


Vin:115Vac Io: 0A  
Ch2: voltage, 2V/div

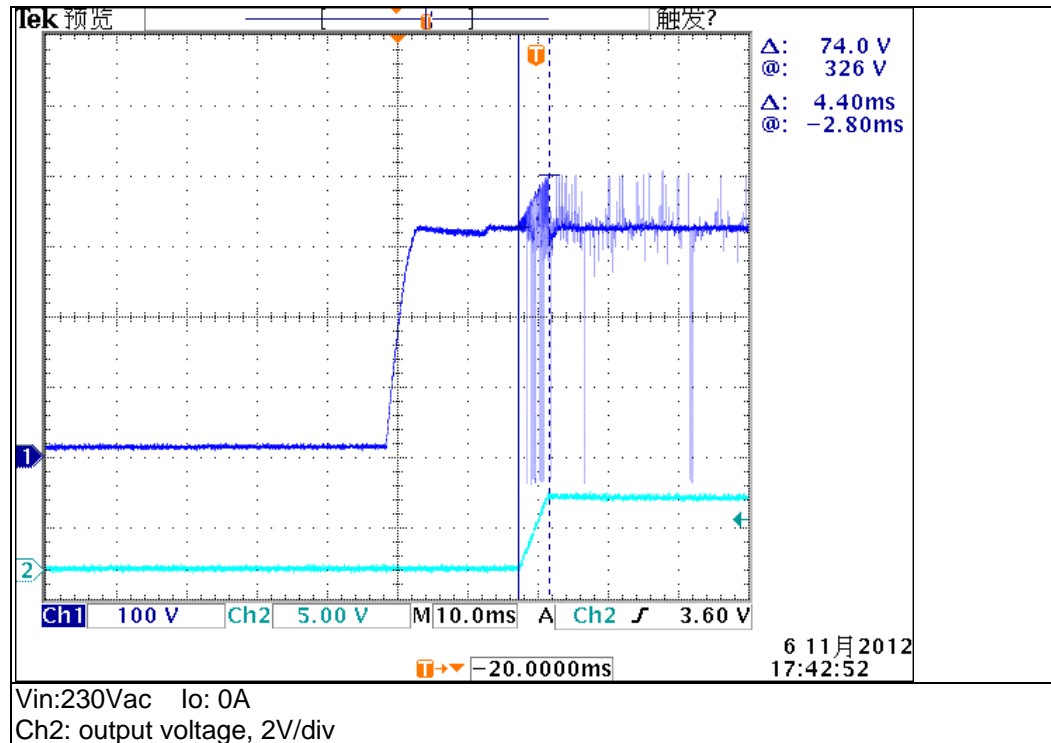


### 3.4 RIPPLE VOLTAGE


Input voltage	Output current	Ripple voltage	Pass/Fail
115Vac	0.25A	<b>39mV</b>	
115Vac	0.5A	<b>58mV</b>	
115Vac	0.75A	<b>52mV</b>	
115Vac	1A	<b>48mV</b>	


230Vac	0.25A	38mV	
230Vac	0.5A	59mV	
230Vac	0.75A	49mV	
230Vac	1A	50mV	

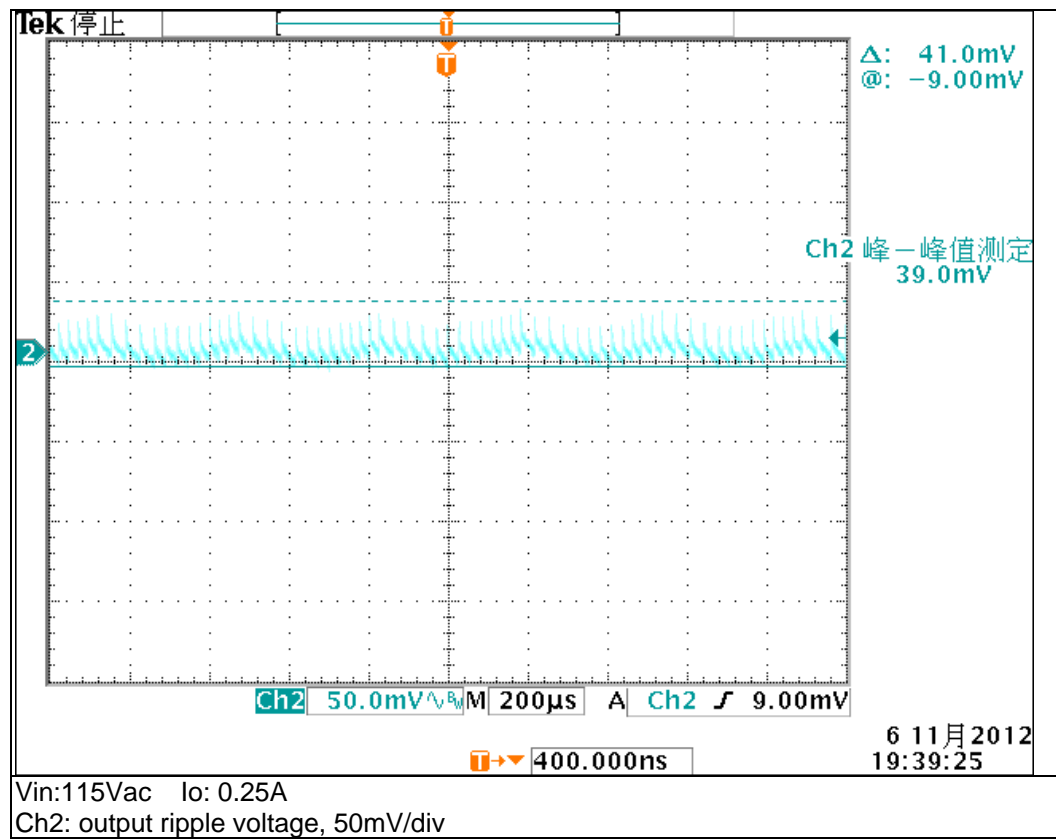


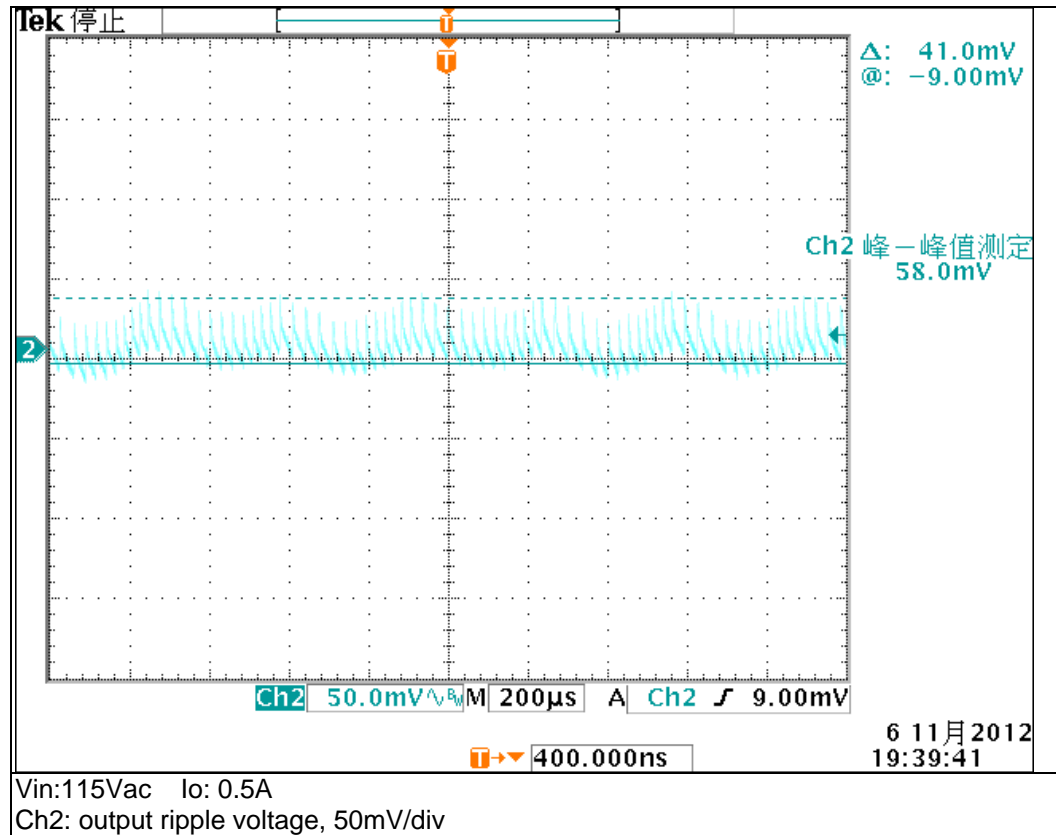





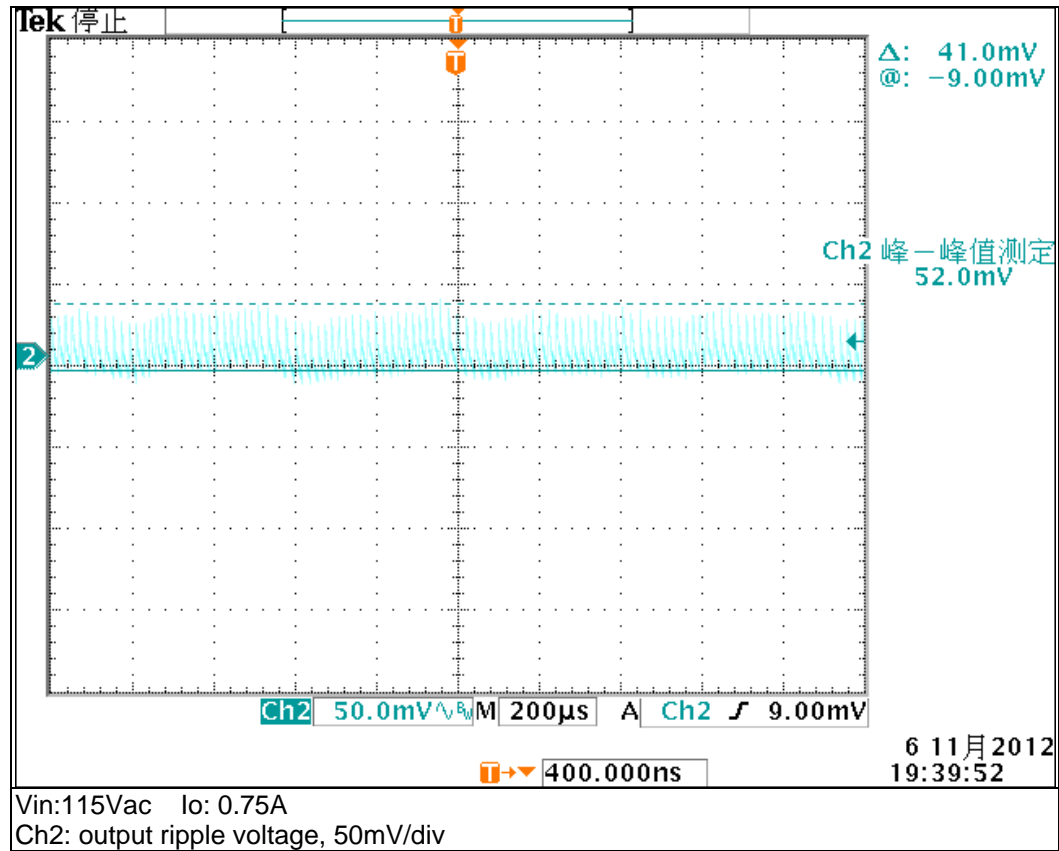


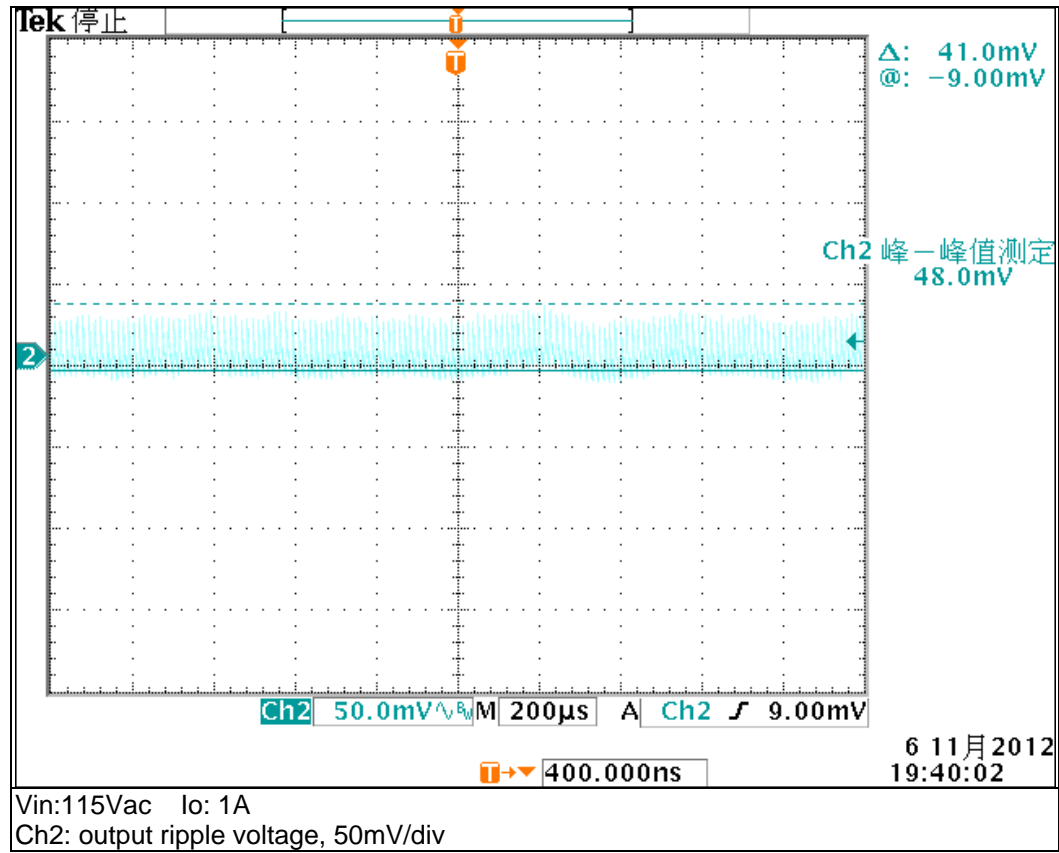

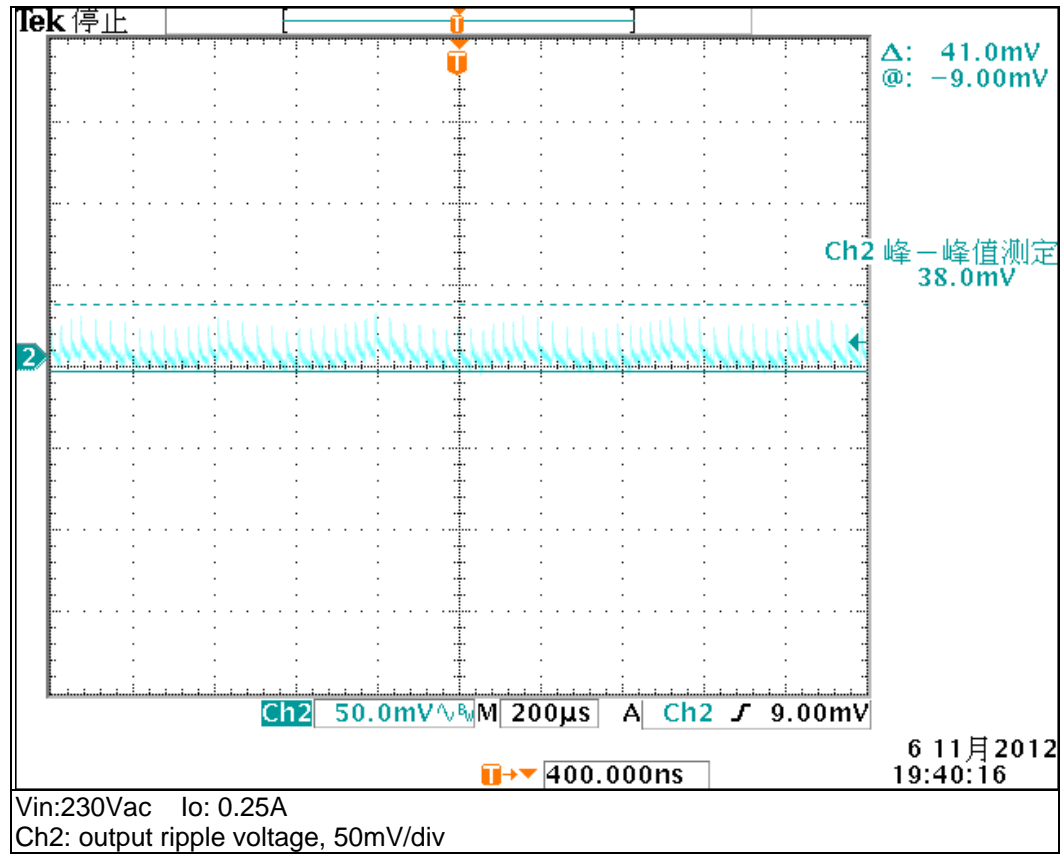

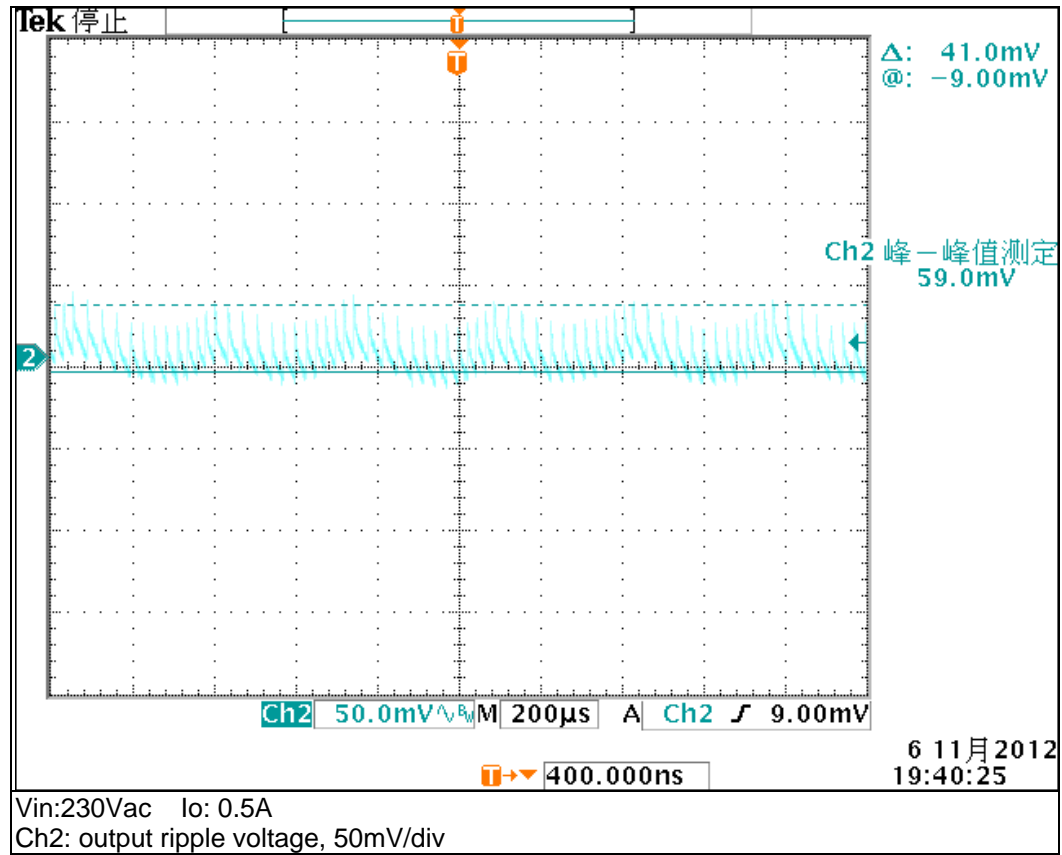


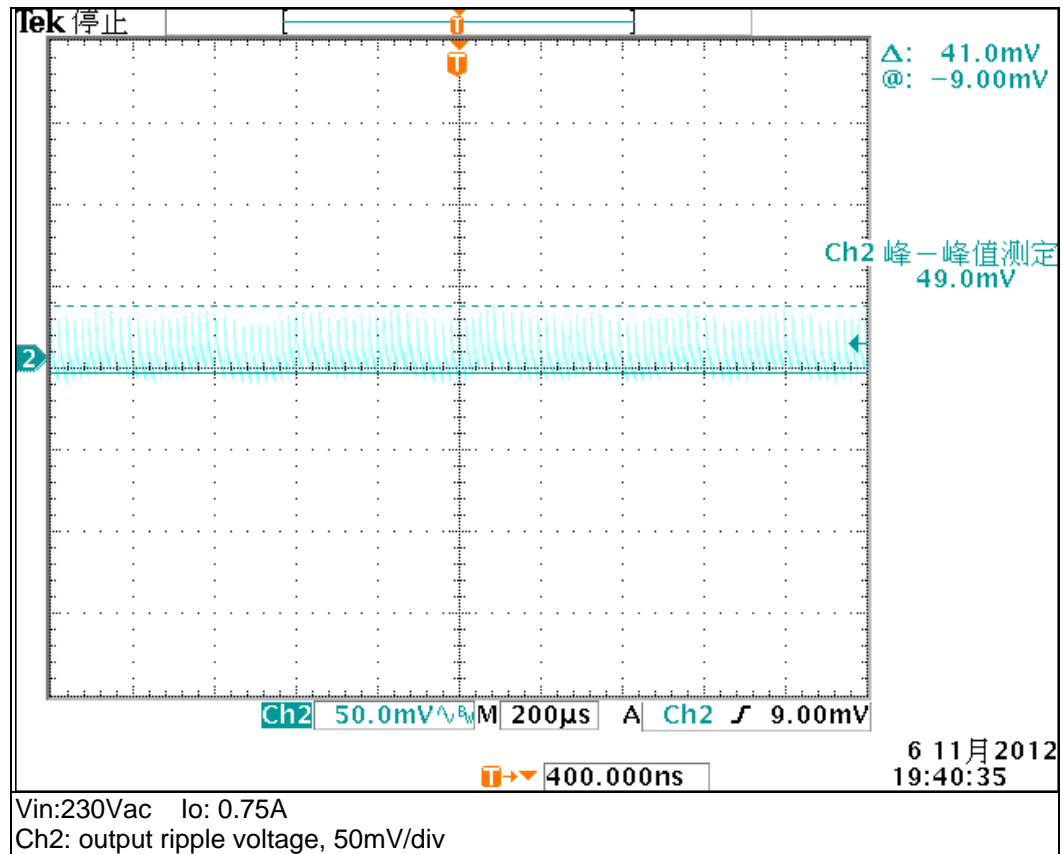


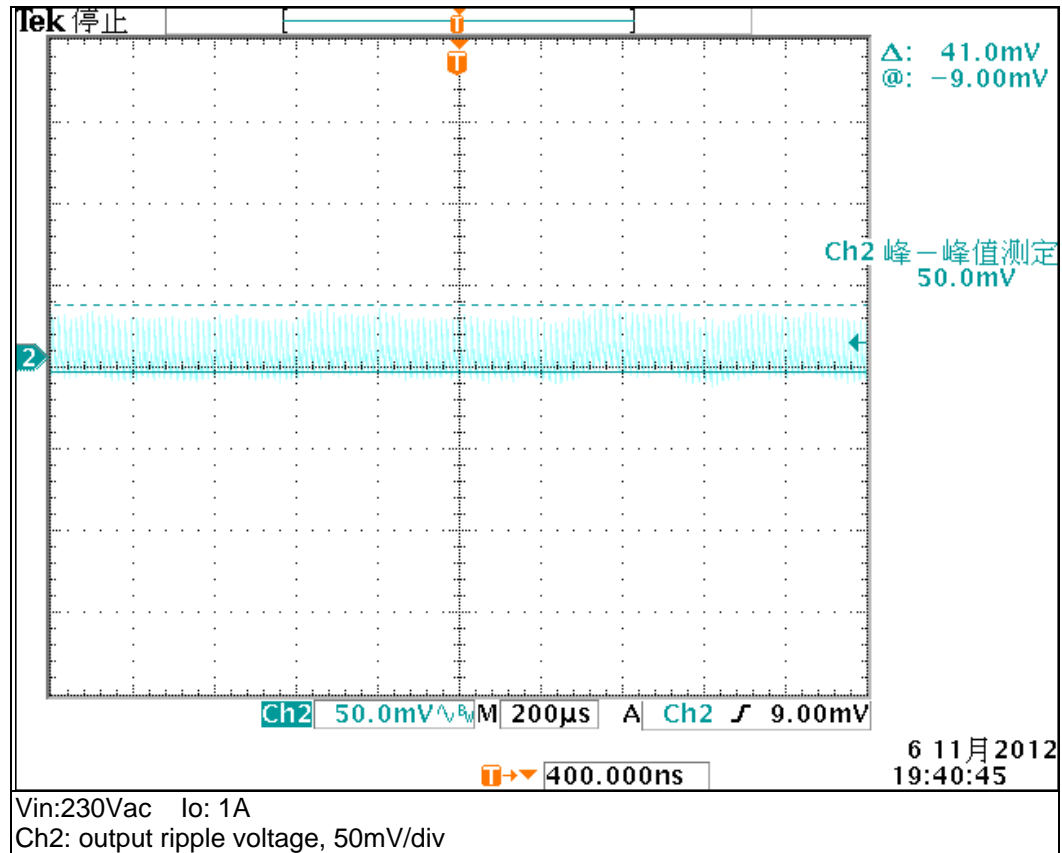

### 3.5 DYNAMIC RESPONSE

Input voltage	Output current	Max voltage	Min voltage
115Vac	0-0.5A	5.12V	4V
230Vac	0-0.5A	5.12V	4V

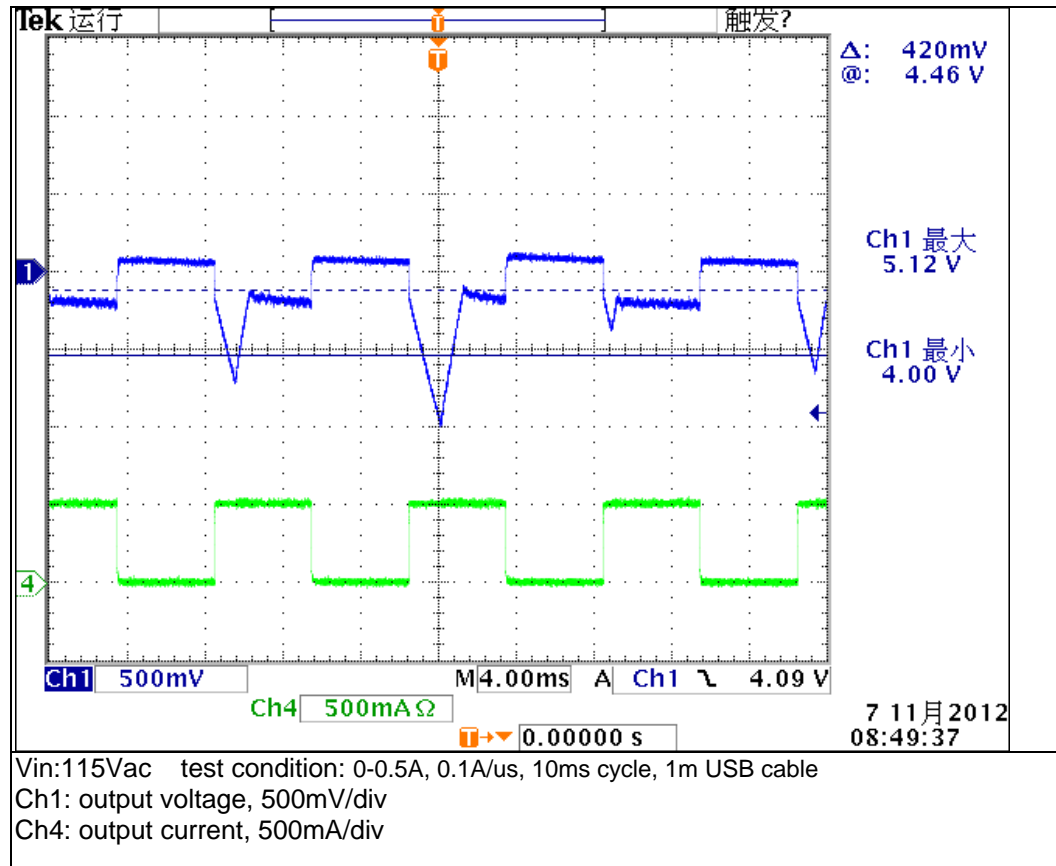

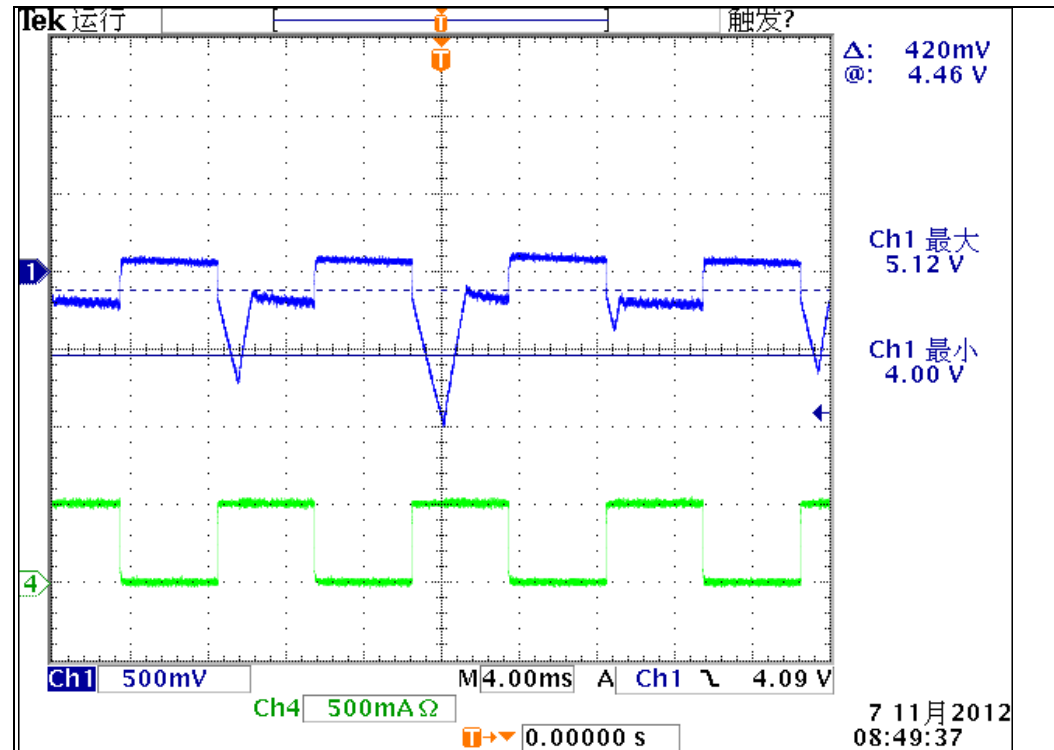

Vin: 115Vac test condition: 0-0.5A, 0.1A/us, 10ms cycle, 1m USB cable


Ch1: output voltage, 500mV/div

Ch4: output current, 500mA/div

### 3.6 OUTPUT VOLTAGE PROTECTION


CONDITIONS	Protection voltage ( V )	Pass/Fail
Vin (Vac)		
115&230	5.75	



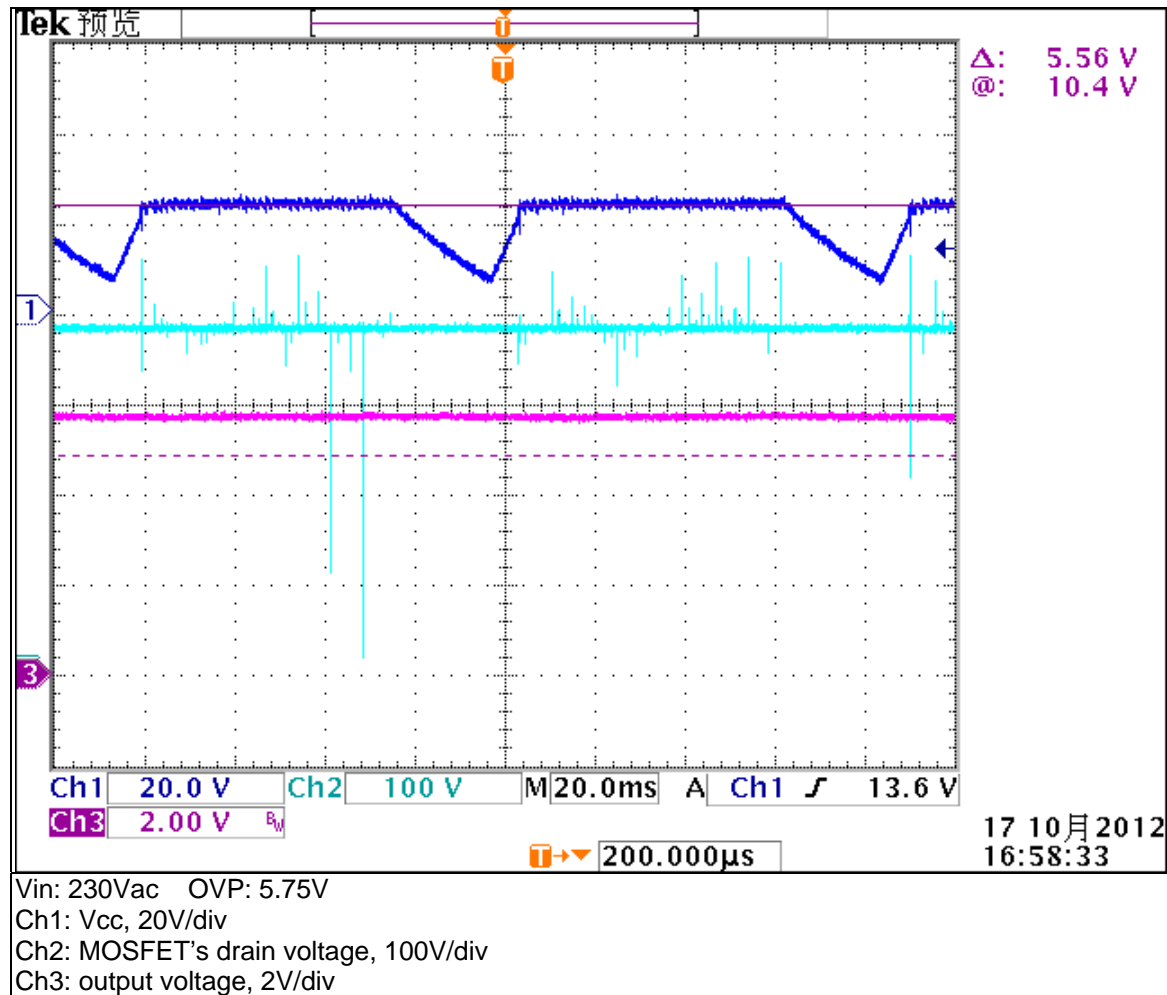


### 3.7 OUTPUT SHORT PROTECTION

Input voltage	Output short protection
115&230Vac	<b>Hiccup up mode</b>

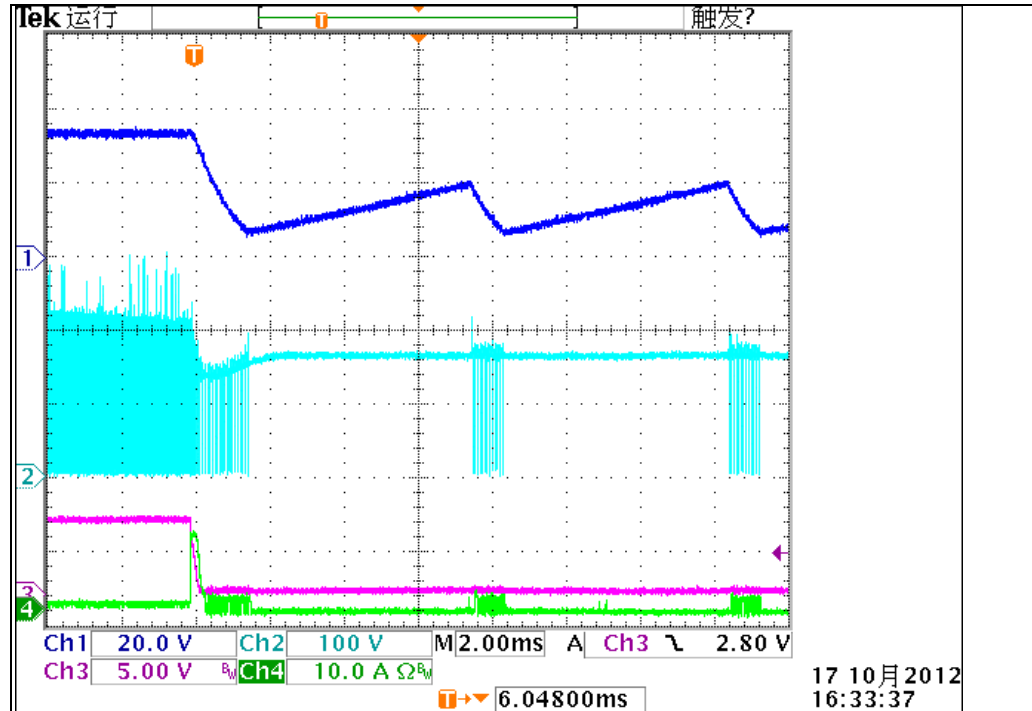


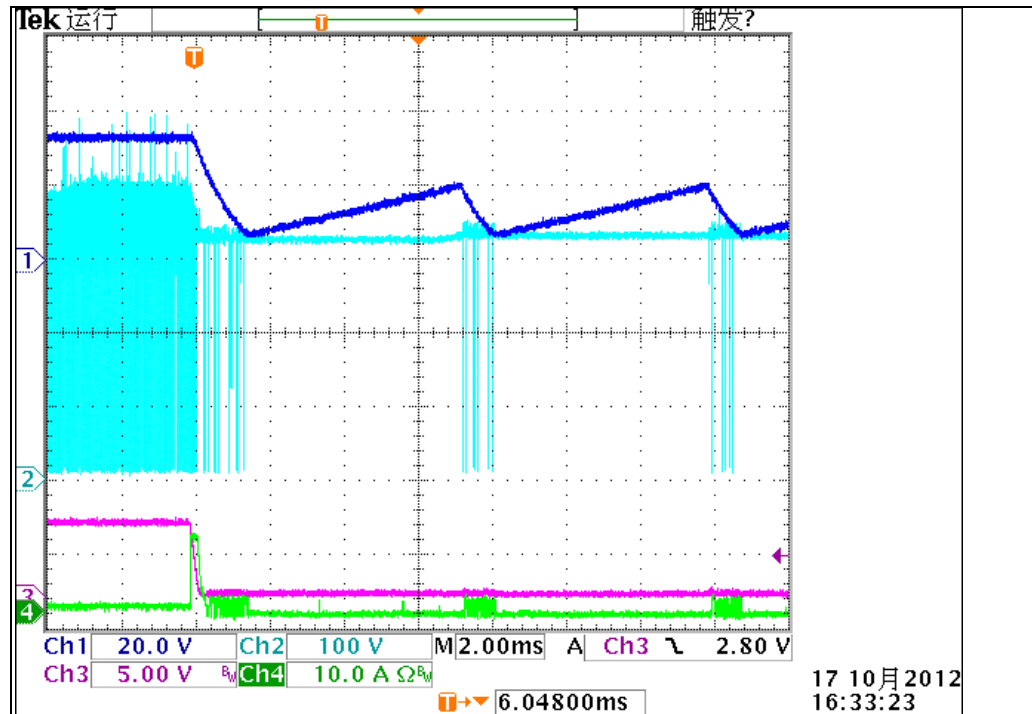Vin:115Vac  
Ch1: Vcc, 20V/div  
Ch2: MOSFET's drain voltage, 100V/div  
Ch3: output voltage, 5V/div  
Ch4: output current, 10A/div




Vin:115Vac  
 Ch1: Vcc, 20V/div  
 Ch2: MOSFET's drain voltage, 100V/div  
 Ch3: output voltage, 5V/div  
 Ch4: output current, 10A/div

#### 4 IV CURVE

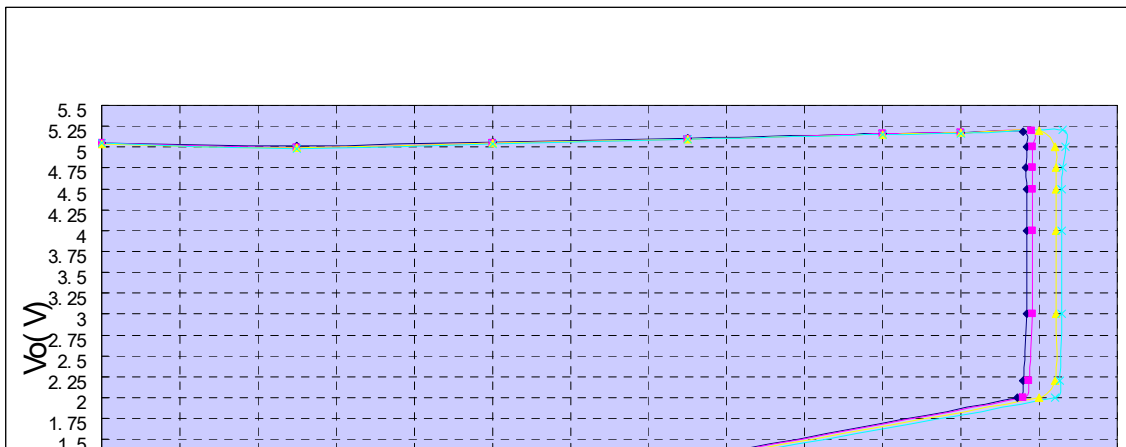





## **5 THERMAL IMAGE**

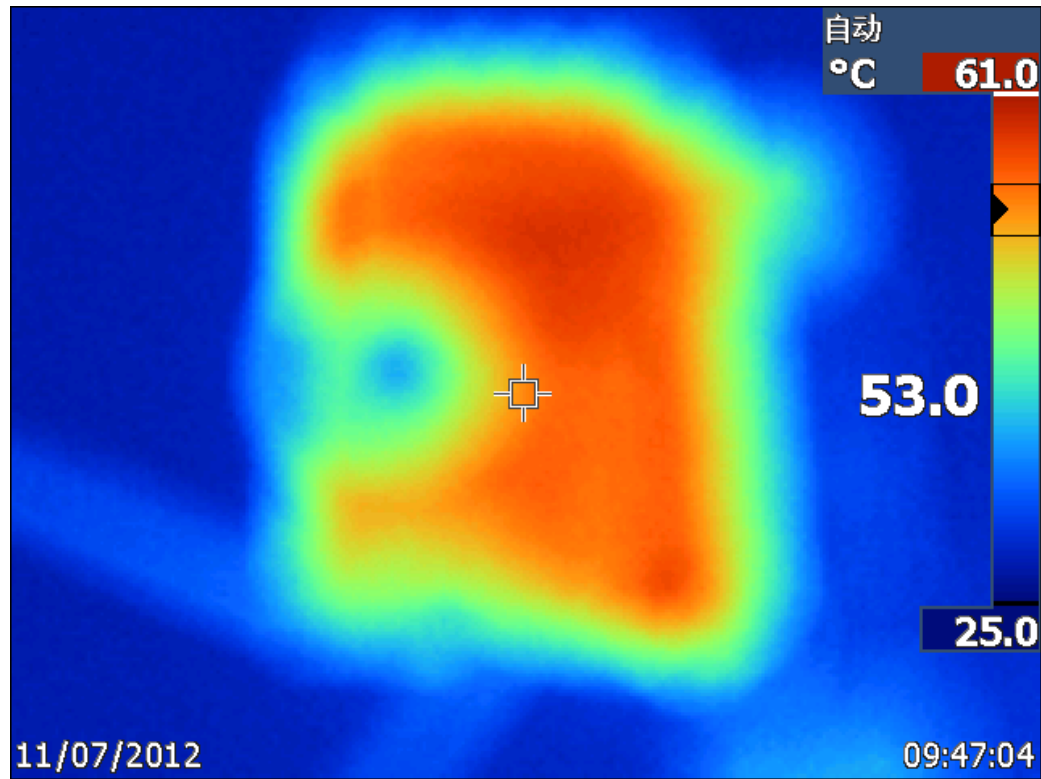

Component side, 115Vac and 1A load

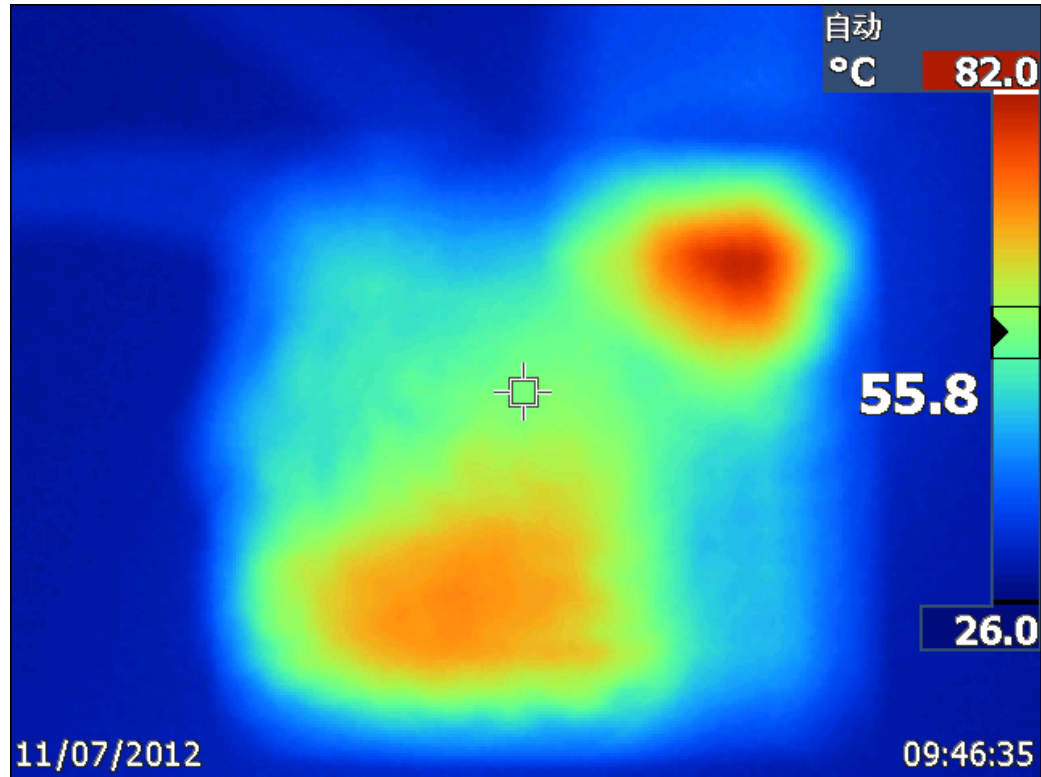


Soldering side, 115Vac and 1A load

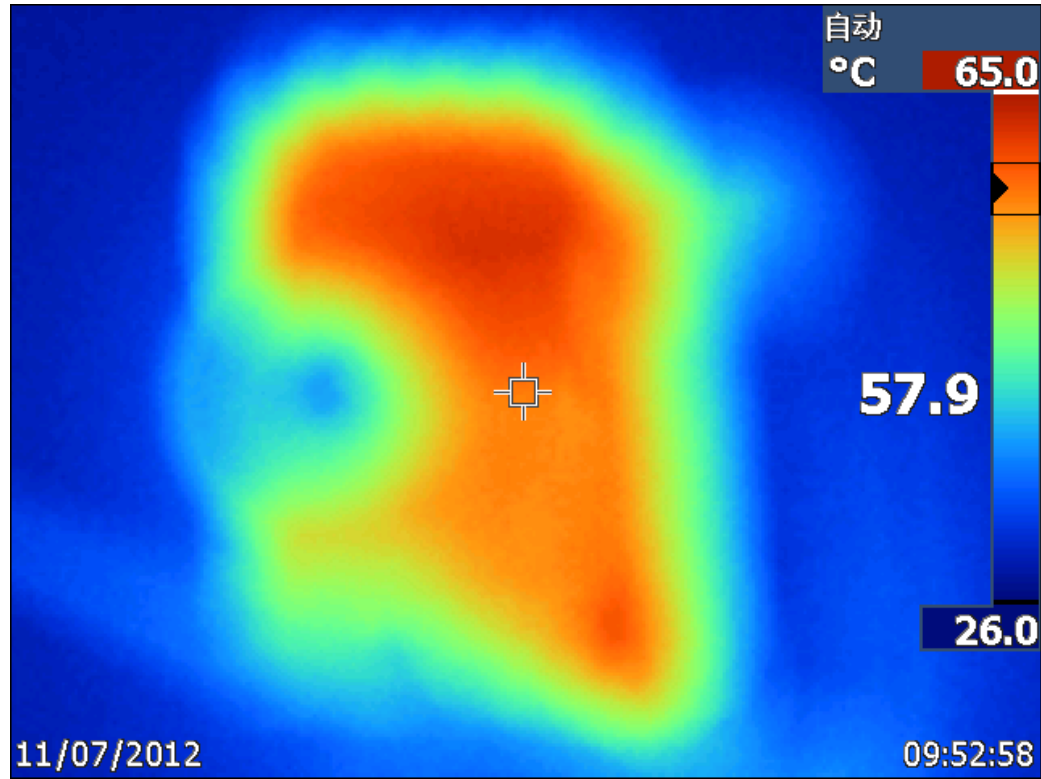


Component side, 230Vac and 1A load



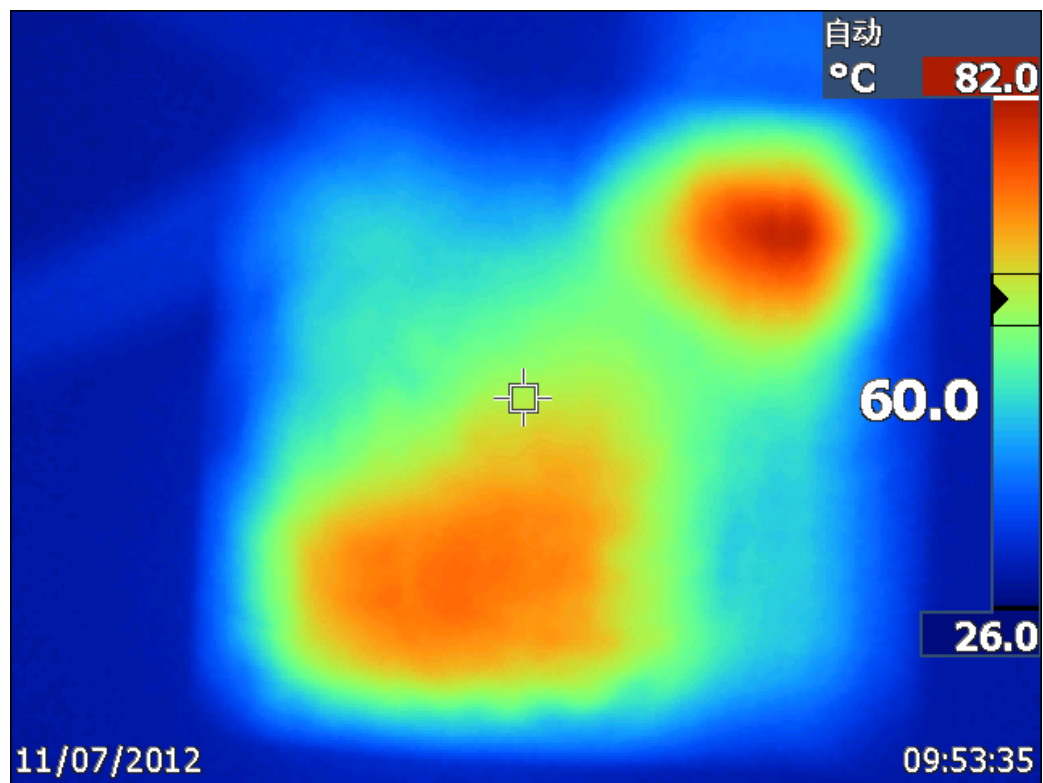



Soldering side, 230Vac and 1A load

## 6 EMI Test

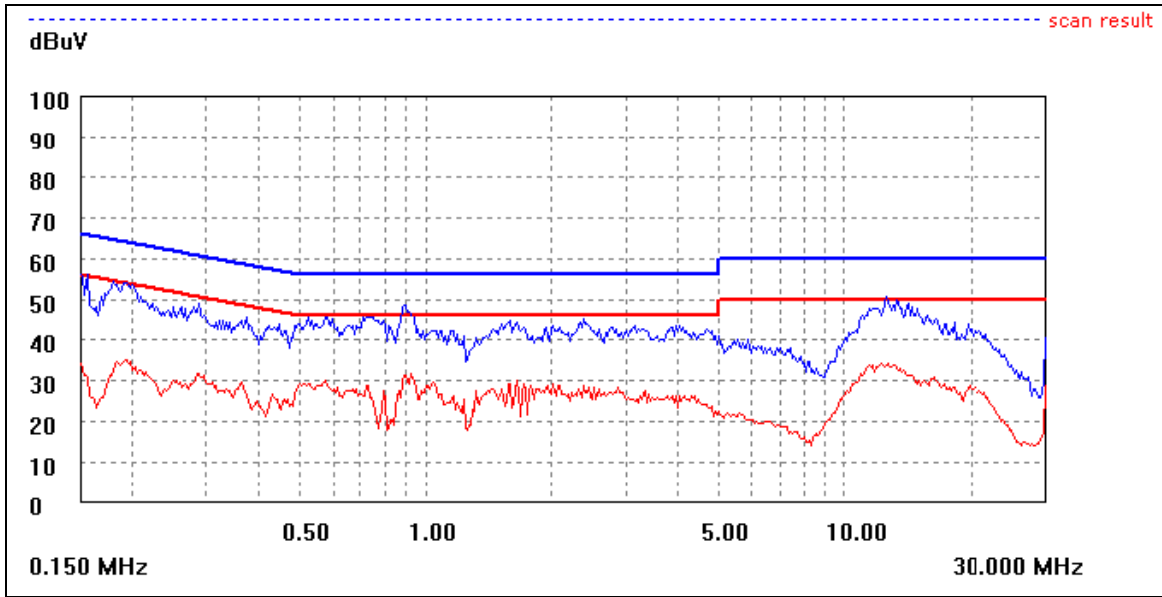


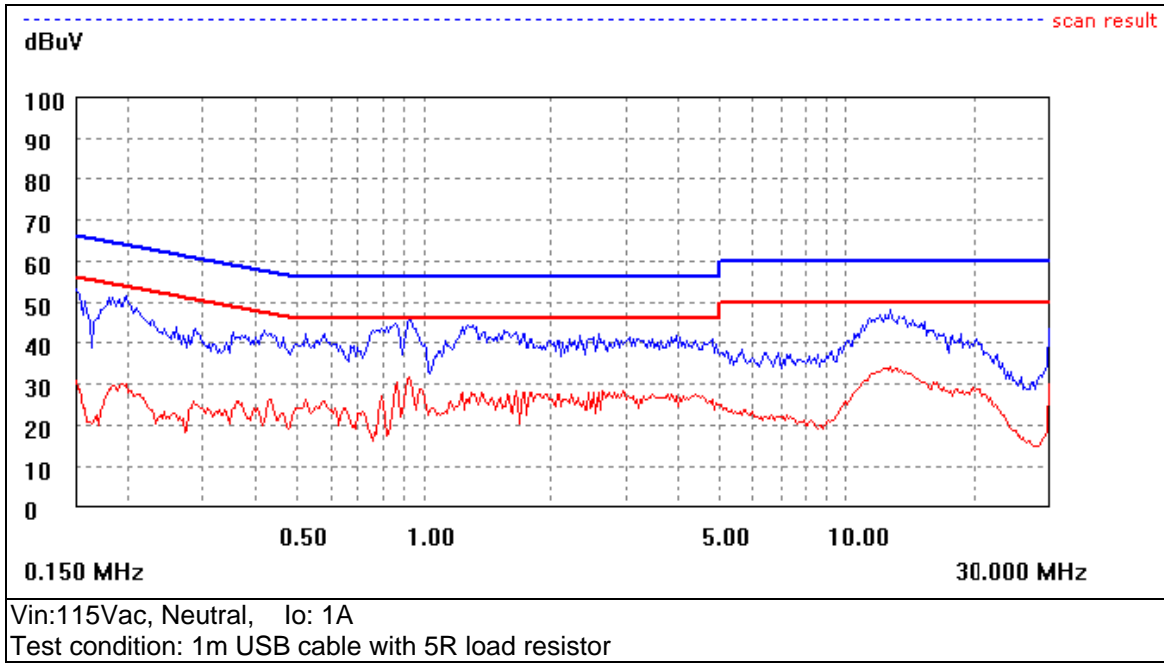Vin: 115Vac, Line, Io: 1A  
Test condition: 1m USB cable with 5R load resistor



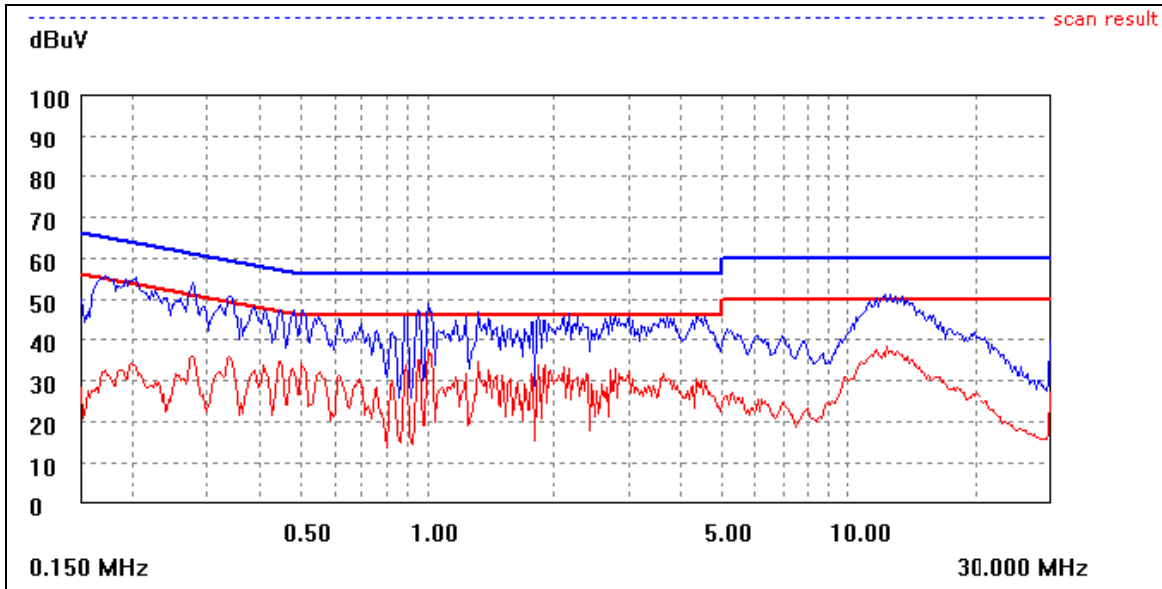

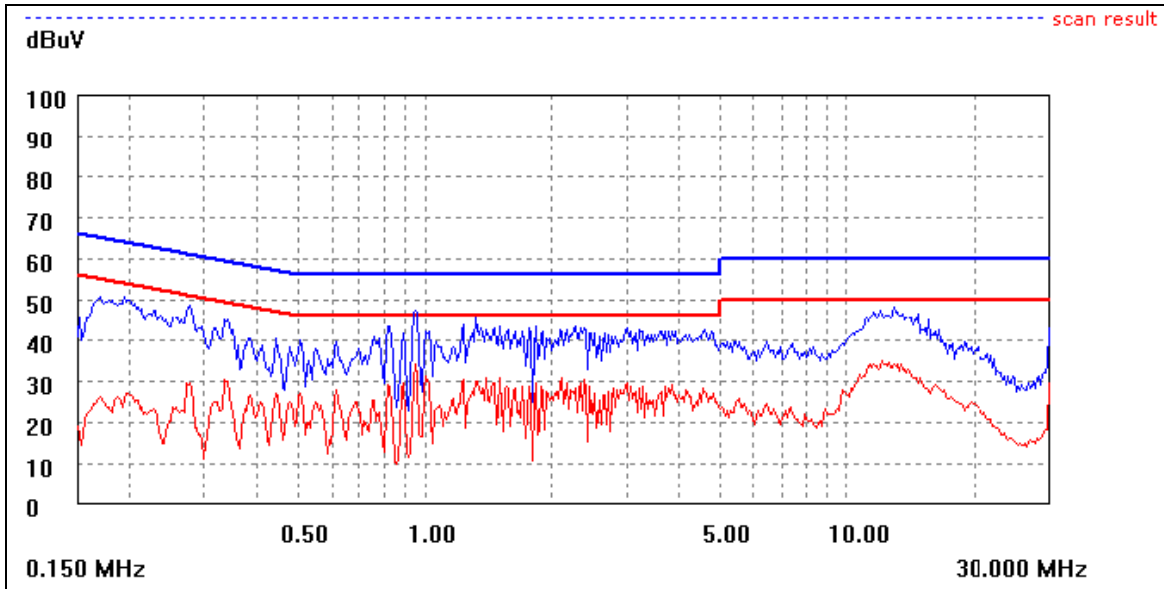Vin: 230Vac, Line, Io: 1A  
Test condition: 1m USB cable with 5R load resistor



Vin:230Vac, Neutral, Io: 1A  
Test condition: 1m USB cable with 5R load resistor

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated