
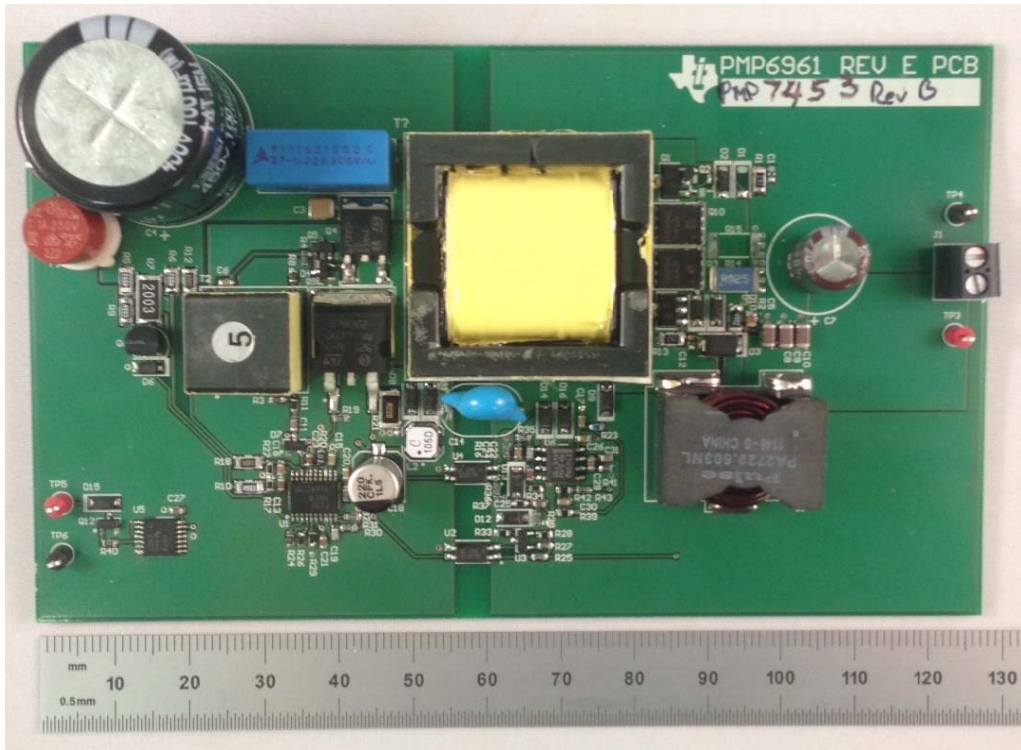

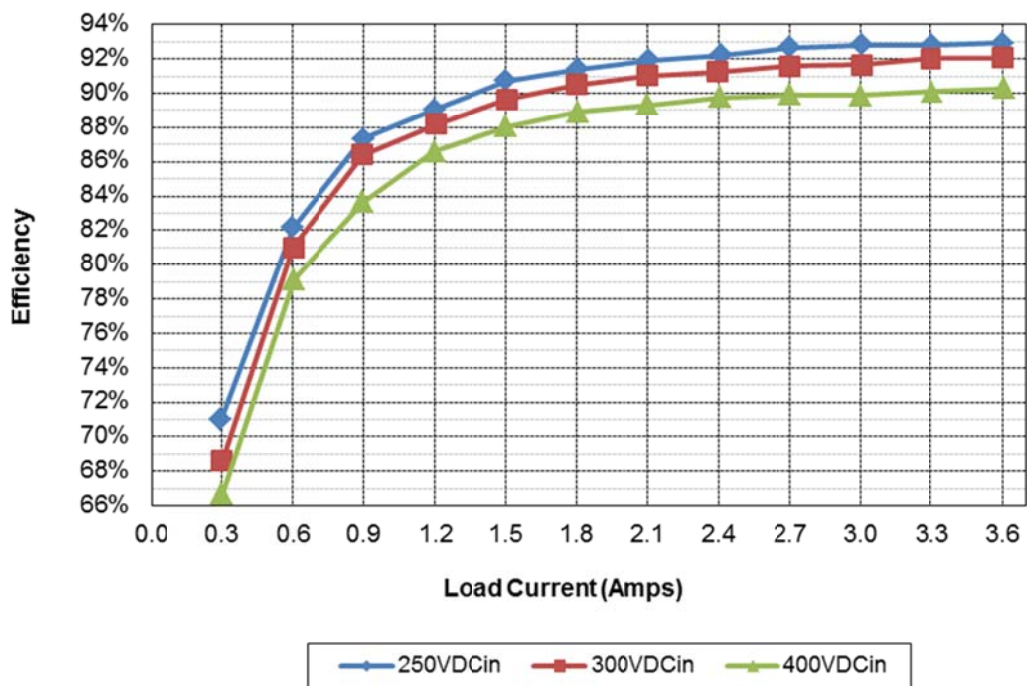
## 1 Photo

The photograph below shows the PMP7453 Rev B demo board. This circuit was build using a PMP6961 Rev E PCB.



## 2 Efficiency



<b>250VDCin</b>							
lout	Vout	Vin	lin	Pin	Pout	Losses	Efficiency
0.000	27.48	250.0	0.014	3.50	0.00	3.50	0.0%
0.297	27.48	250.0	0.046	11.50	8.16	3.34	71.0%
0.598	27.48	250.0	0.080	20.00	16.43	3.57	82.2%
0.898	27.47	250.0	0.113	28.25	24.67	3.58	87.3%
1.199	27.47	249.9	0.148	36.99	32.94	4.05	89.1%
1.502	27.47	249.9	0.182	45.48	41.26	4.22	90.7%
1.804	27.47	249.9	0.217	54.23	49.56	4.67	91.4%
2.107	27.47	249.9	0.252	62.97	57.88	5.10	91.9%
2.408	27.47	249.9	0.287	71.72	66.15	5.57	92.2%
2.705	27.47	249.8	0.321	80.19	74.31	5.88	92.7%
3.006	27.46	249.8	0.356	88.93	82.54	6.38	92.8%
3.302	27.45	249.8	0.391	97.67	90.64	7.03	92.8%
3.602	27.45	249.8	0.426	106.41	98.87	7.54	92.9%


<b>300VDCin</b>							
lout	Vout	Vin	lin	Pin	Pout	Losses	Efficiency
0.000	27.47	300.3	0.014	4.20	0.00	4.20	0.0%
0.300	27.47	300.3	0.040	12.01	8.24	3.77	68.6%
0.602	27.47	300.2	0.068	20.41	16.54	3.88	81.0%
0.897	27.47	300.2	0.095	28.52	24.64	3.88	86.4%
1.205	27.46	300.2	0.125	37.53	33.09	4.44	88.2%
1.509	27.46	300.2	0.154	46.23	41.44	4.79	89.6%
1.801	27.46	300.2	0.182	54.64	49.46	5.18	90.5%
2.100	27.46	300.2	0.211	63.34	57.67	5.68	91.0%
2.393	27.46	300.1	0.240	72.02	65.71	6.31	91.2%
2.702	27.46	300.1	0.270	81.03	74.20	6.83	91.6%
3.006	27.45	300.1	0.300	90.03	82.51	7.52	91.7%
3.300	27.45	300.1	0.328	98.43	90.59	7.85	92.0%
3.603	27.45	300.1	0.358	107.44	98.90	8.53	92.1%

<b>400VDCin</b>							
lout	Vout	Vin	lin	Pin	Pout	Losses	Efficiency
0.000	28.47	387.5	0.012	4.65	0.00	4.65	0.0%
0.301	27.46	387.5	0.032	12.40	8.27	4.13	66.7%
0.603	27.46	387.4	0.054	20.92	16.56	4.36	79.2%
0.897	27.46	387.4	0.076	29.44	24.63	4.81	83.7%
1.197	27.46	387.4	0.098	37.97	32.87	5.10	86.6%
1.503	27.46	387.4	0.121	46.88	41.27	5.60	88.0%
1.806	27.46	387.4	0.144	55.79	49.59	6.19	88.9%
2.104	27.46	387.4	0.167	64.70	57.78	6.92	89.3%
2.406	27.46	387.4	0.190	73.61	66.07	7.54	89.8%
2.703	27.45	387.4	0.213	82.52	74.20	8.32	89.9%
2.999	27.45	387.3	0.237	91.60	82.32	9.27	89.9%
3.305	27.45	387.3	0.260	100.70	90.72	9.98	90.1%
3.605	27.45	387.3	0.283	109.61	98.96	10.65	90.3%


## 3 Thermal Images

The ambient temperature was 25C with 200LFM of forced air flow. The output was loaded with 3.6A.

### 3.1 400VDC Input

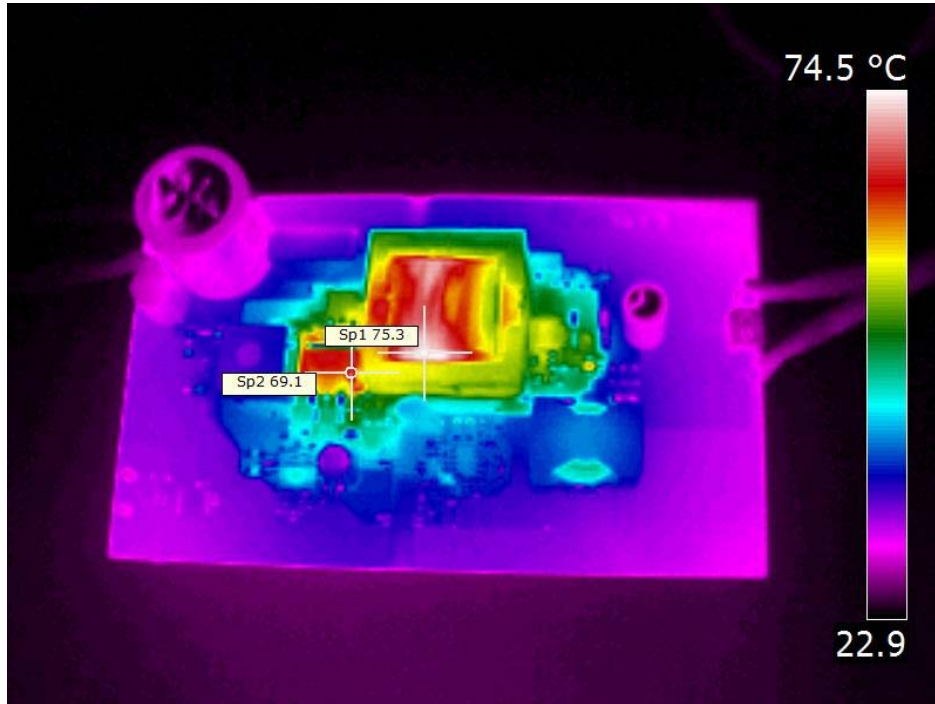


### 3.2 250VDC Input

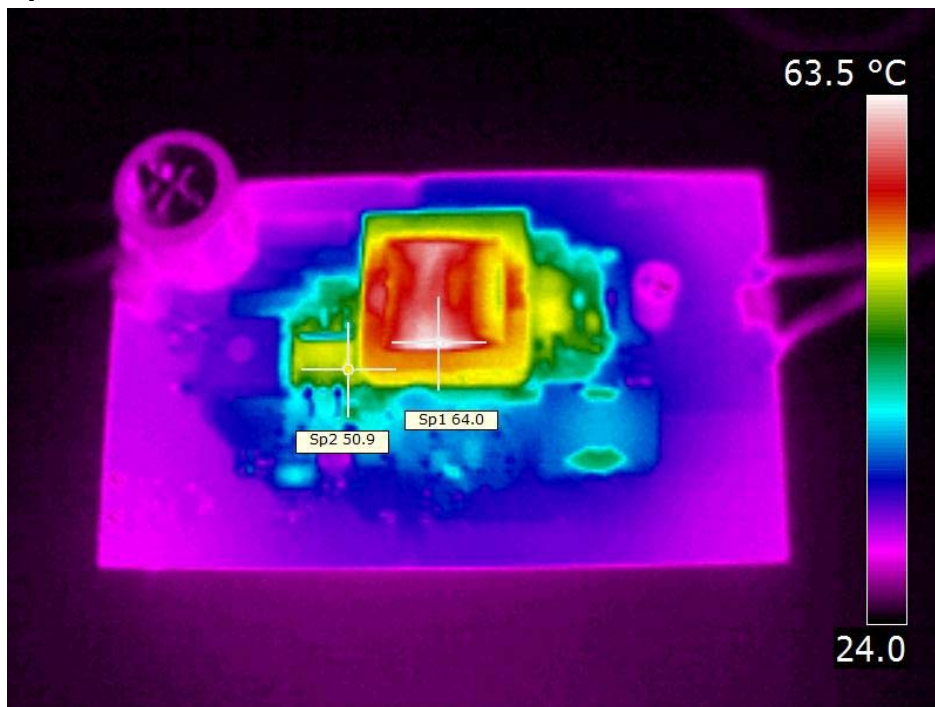


## 4 Startup


### 4.1 400VDC Input Startup, No Load

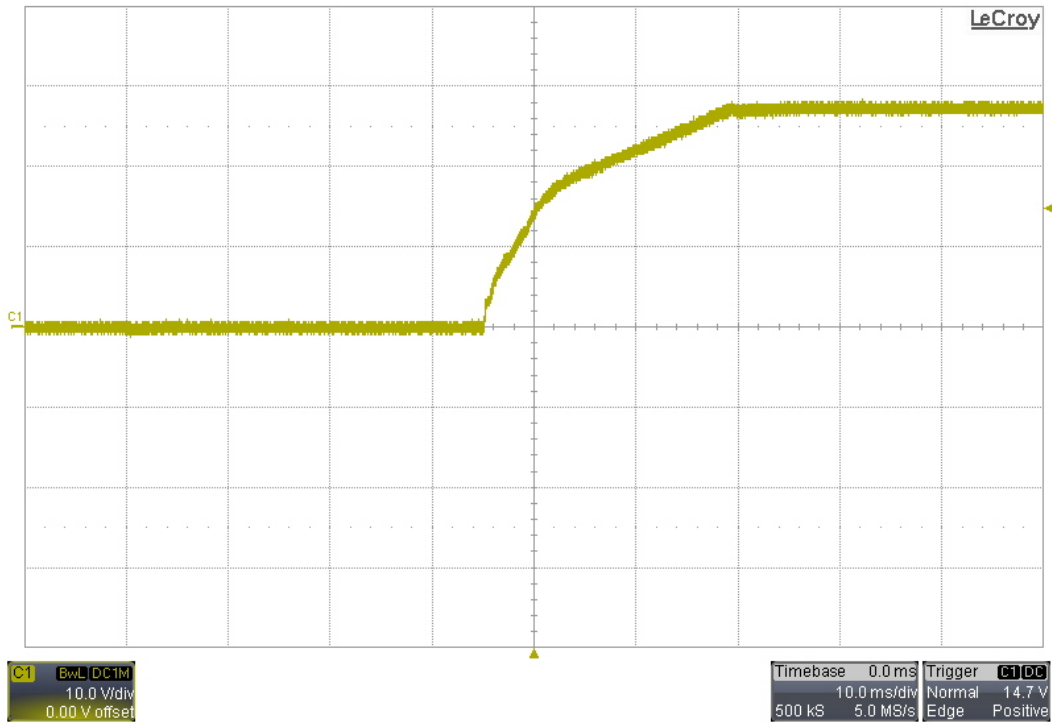


### 4.2 400VDC Input Startup, 8Ω Load

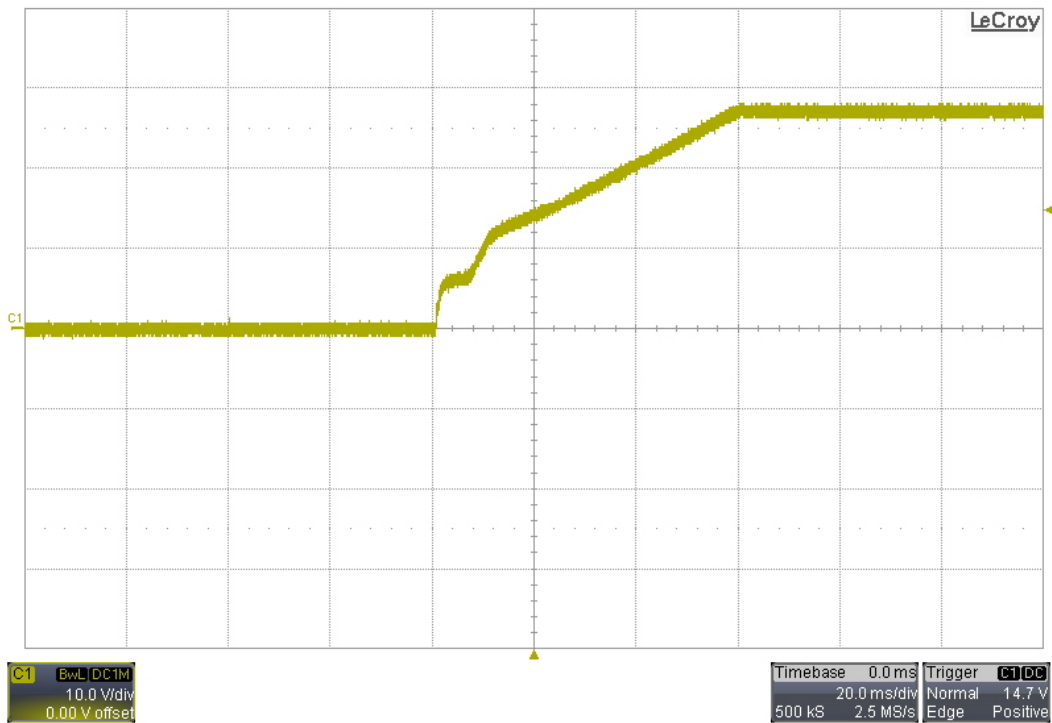

## 4.3 250VDC Input Startup, No Load

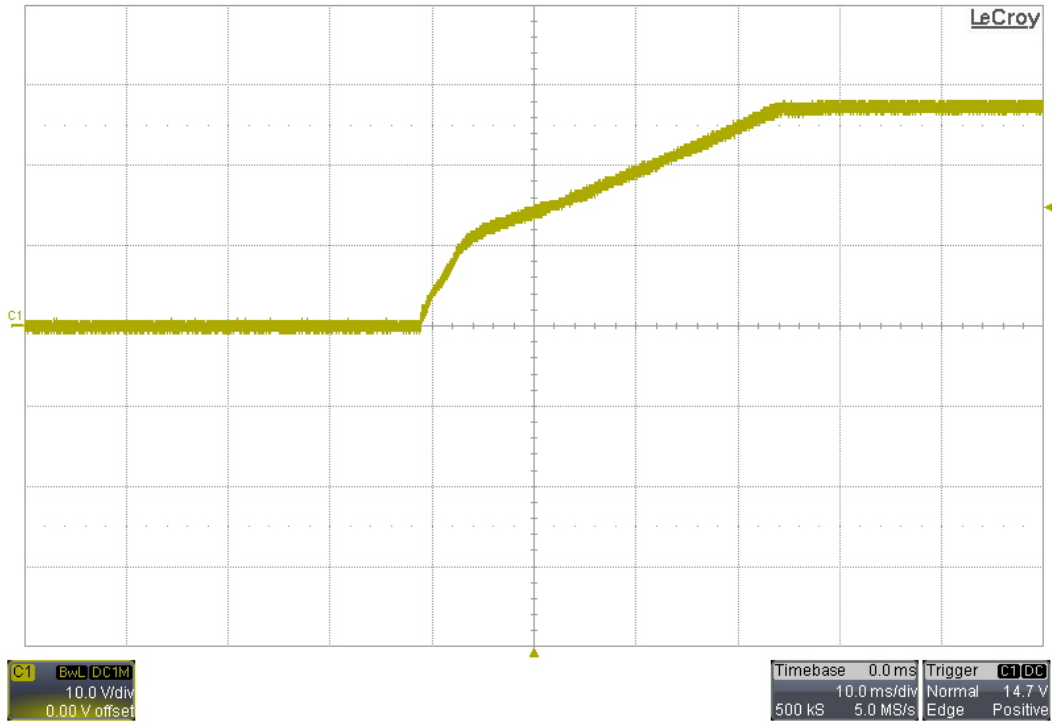


## 4.4 250VDC Input Startup, 8Ω Load

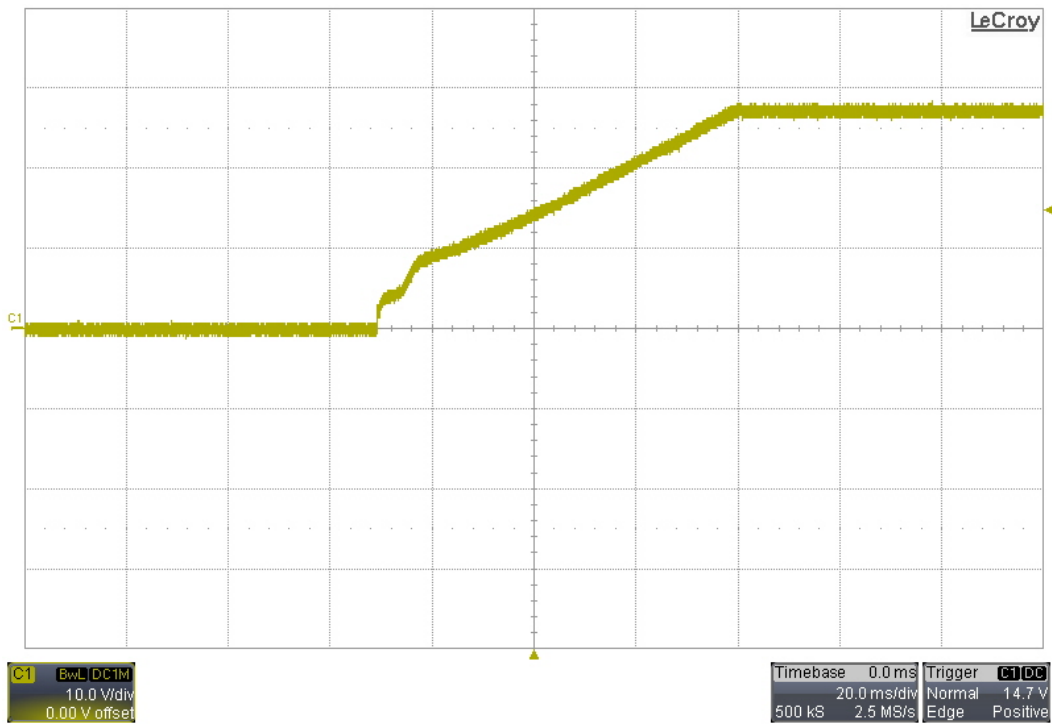




## 5 Output Ripple Voltage
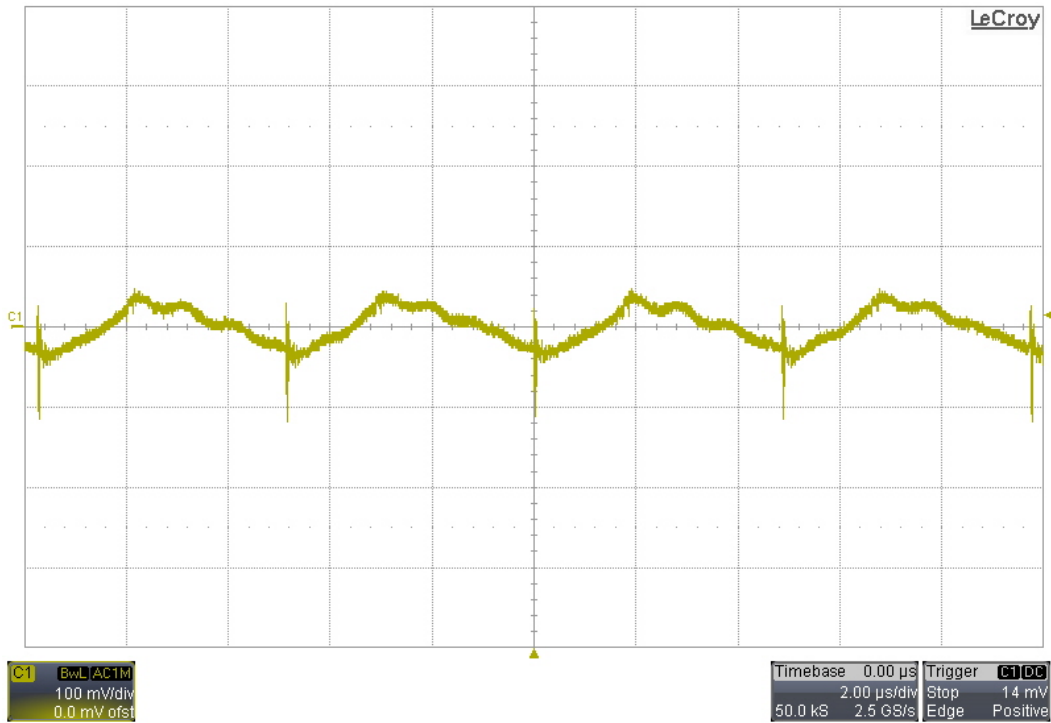
### 5.1 400VDC Input, 3.6A Ripple Voltage



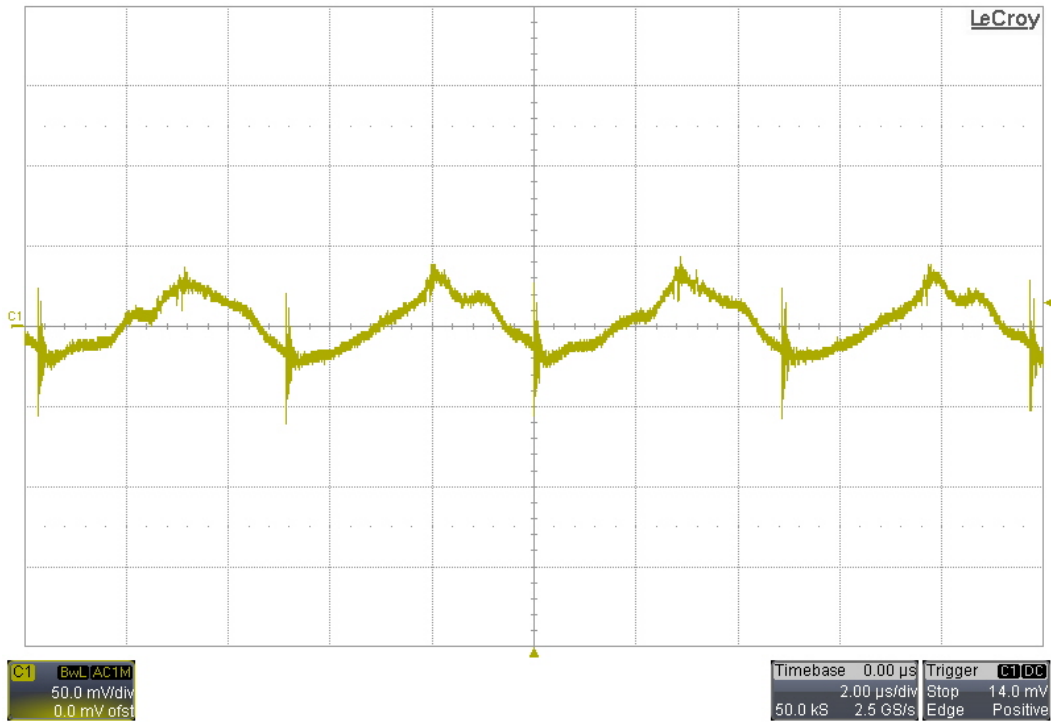
### 5.2 250VDC Input, 3.6A Ripple Voltage


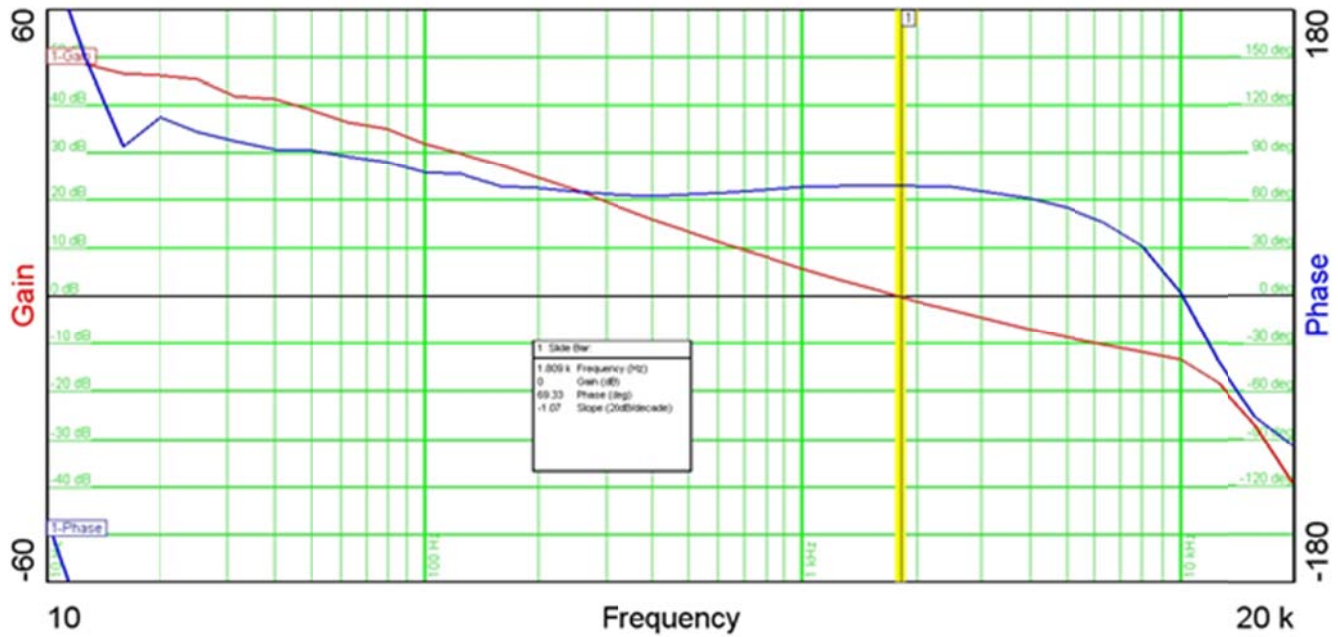
## 6 Voltage Loop Response


The frequency response of the voltage feedback loop is shown in the image below. The input was 350VDC and the output was loaded with 3.6A.




## 7 Load Transients

The response to a load step from 0A to 3.6A is shown in the images below. Channel 1: Vout (ac coupled); Channel 4: Iout


### 7.1 400VDC Input

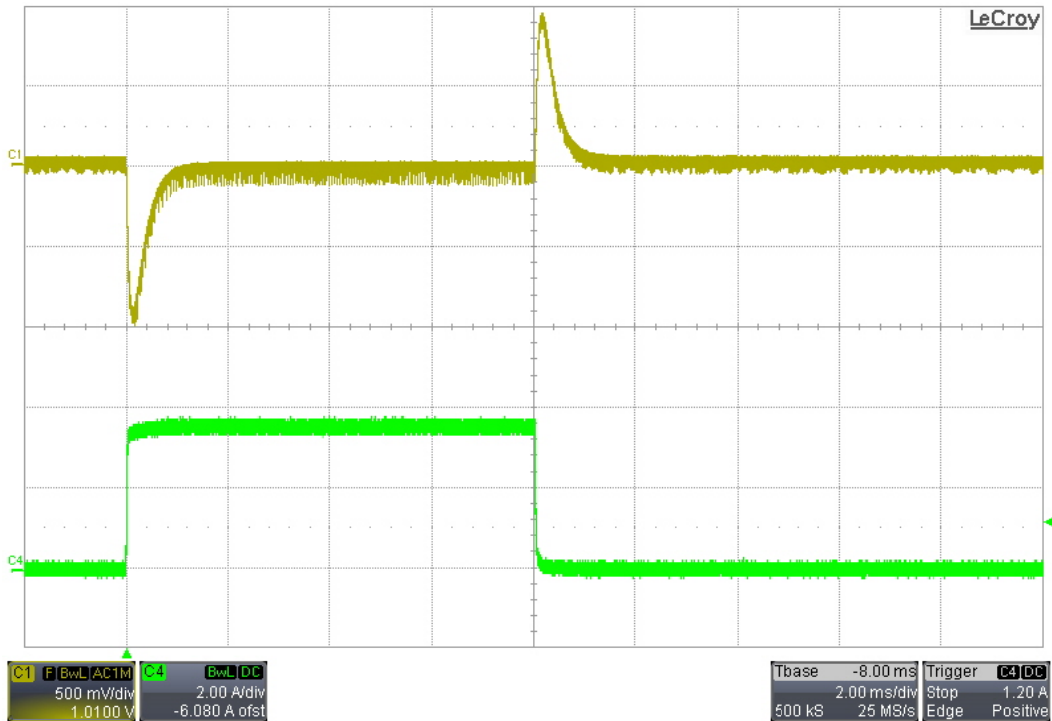

## 7.2 250VDC Input

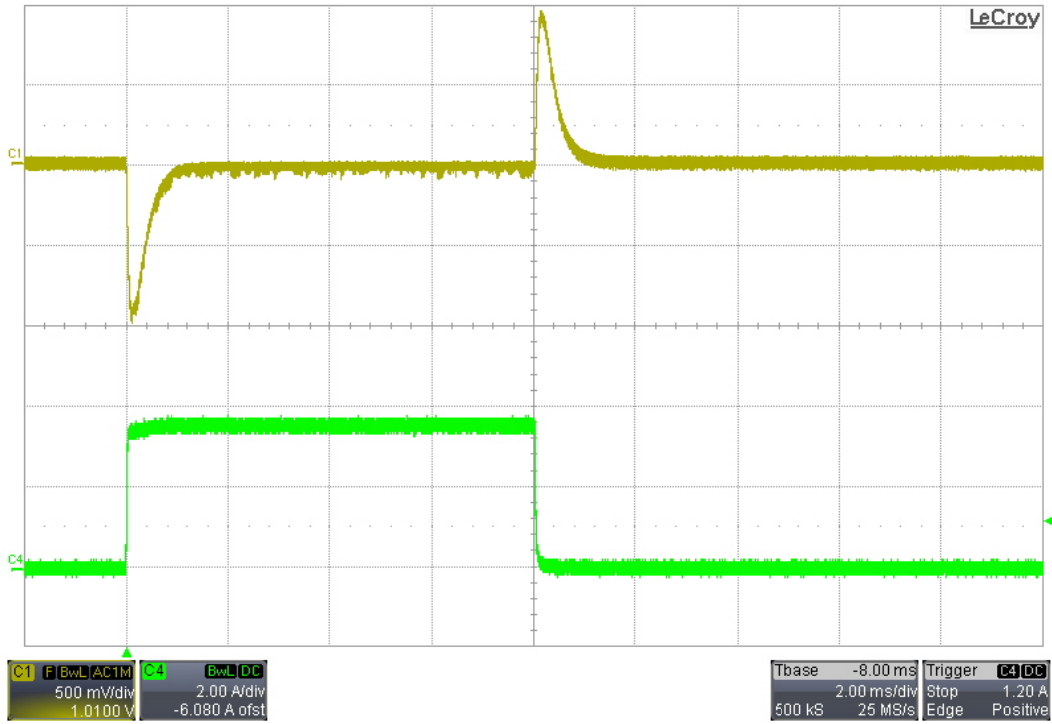


## 8 Overload V-I Characteristics

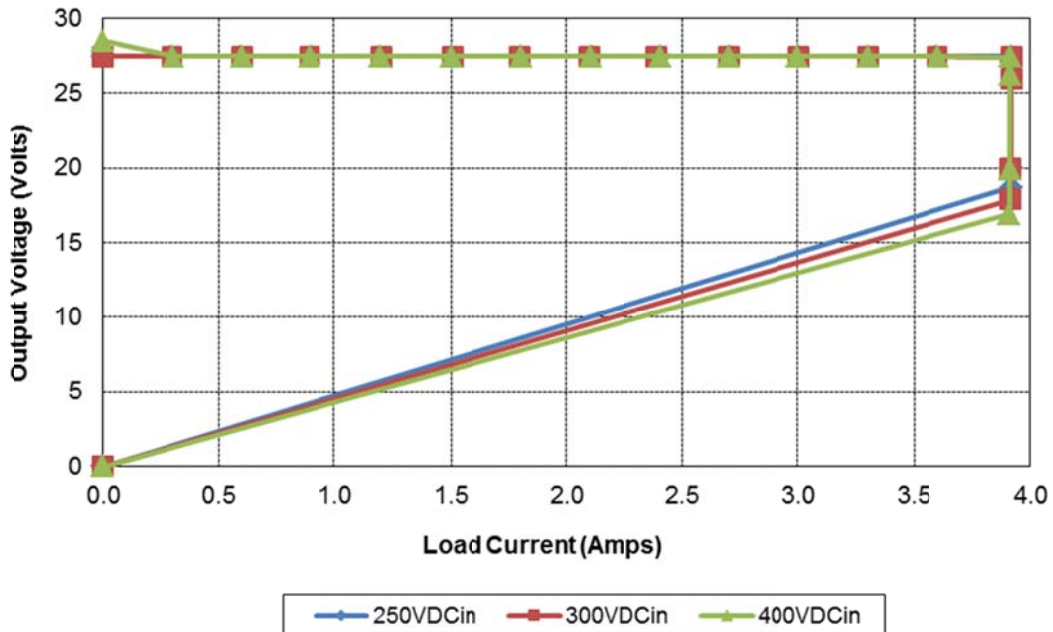




## 9 Primary Drain Waveforms
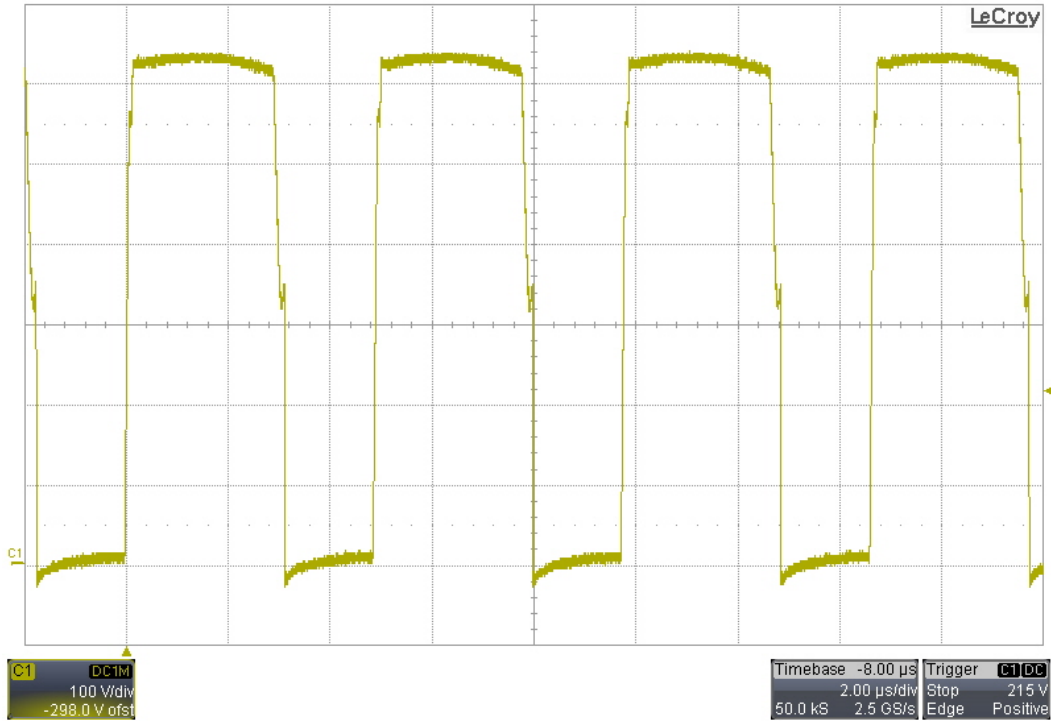
### 9.1 Primary FET (Q9) Vds – 400VDC Input, 3.6A Load



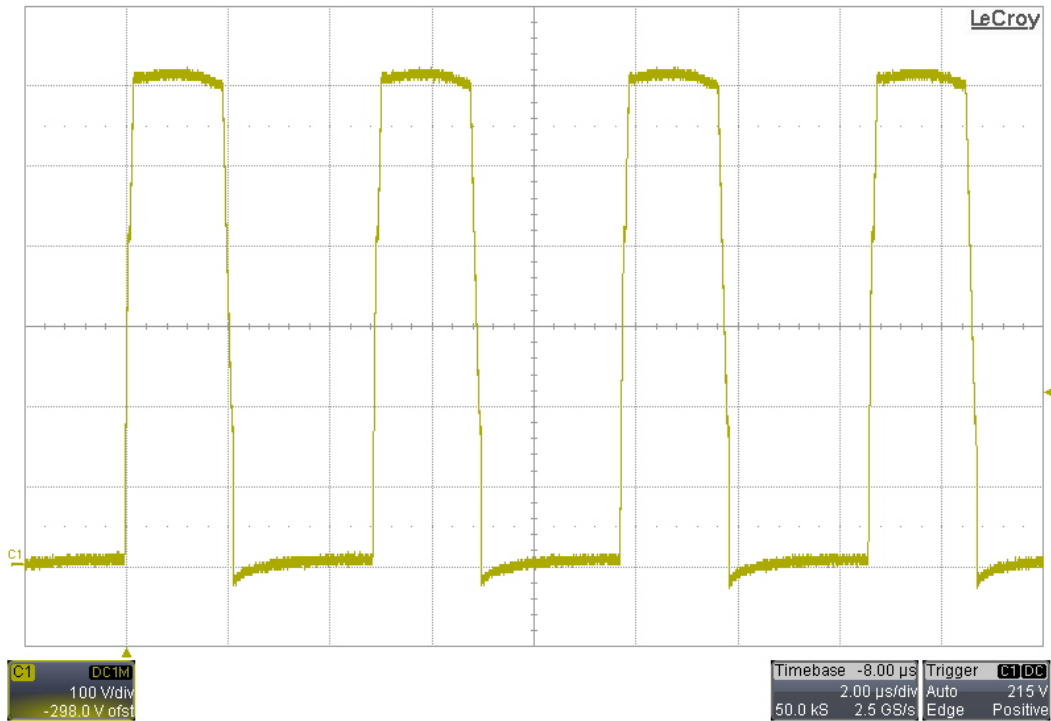
### 9.2 Primary FET (Q9) Vds – 250VDC Input, 3.6A Load




## 10 Synchronous FET Drain Waveforms

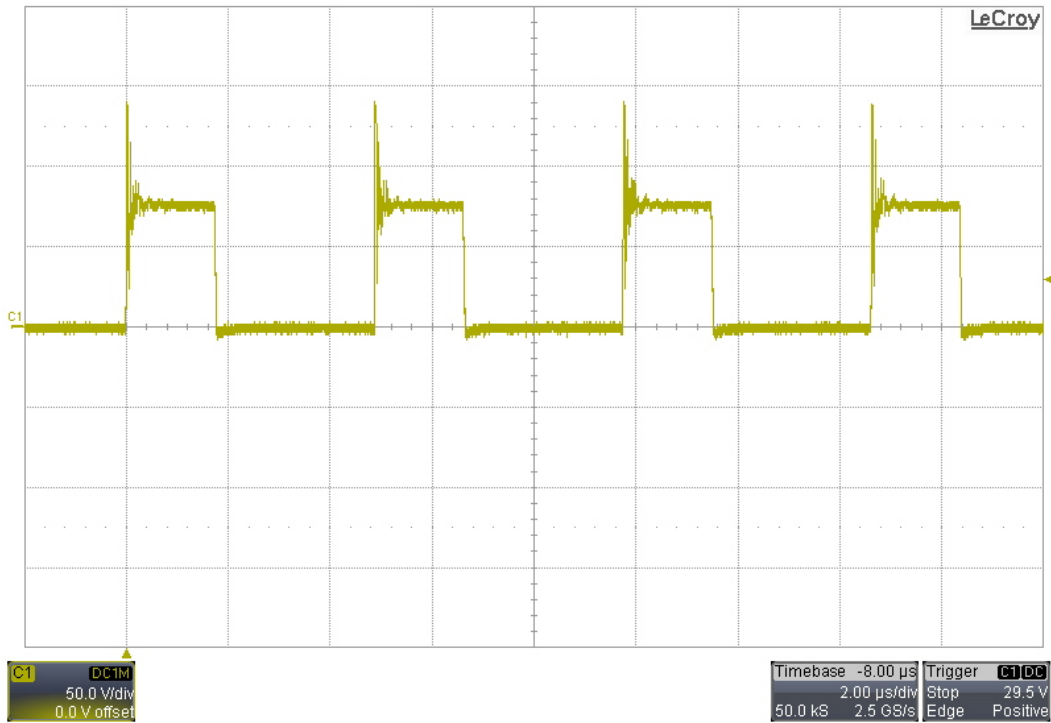
### 10.1 Q3 Synchronous FET Vds – 400VDC Input, 3.6A Load



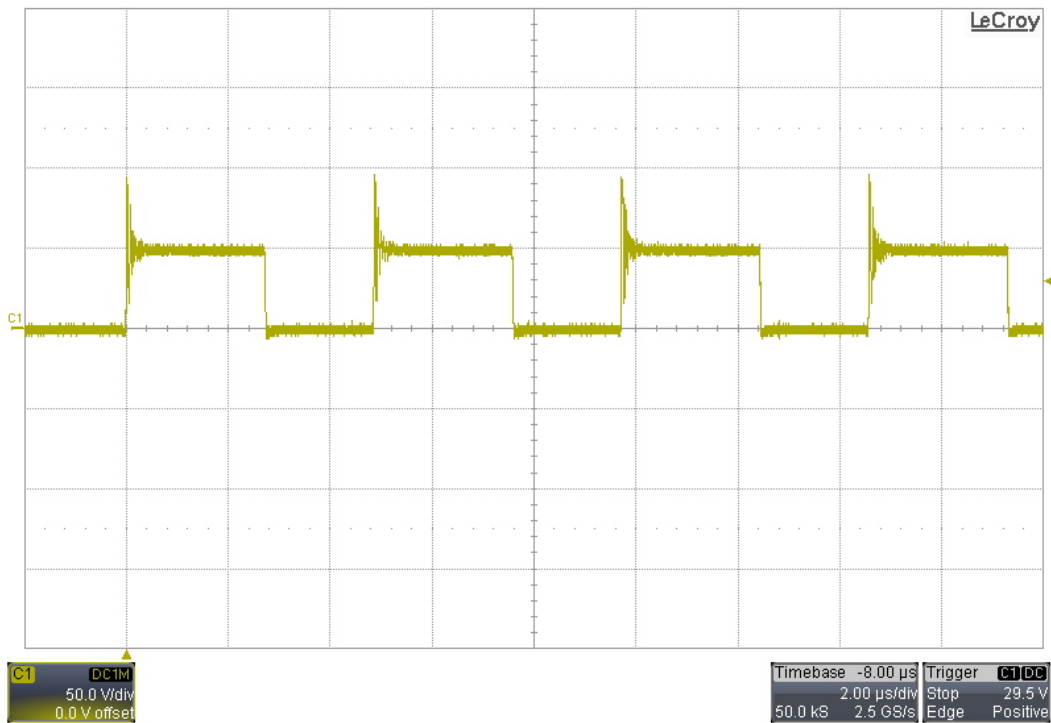
### 10.2 Q3 Synchronous FET Vds – 250VDC Input, 3.6A Load


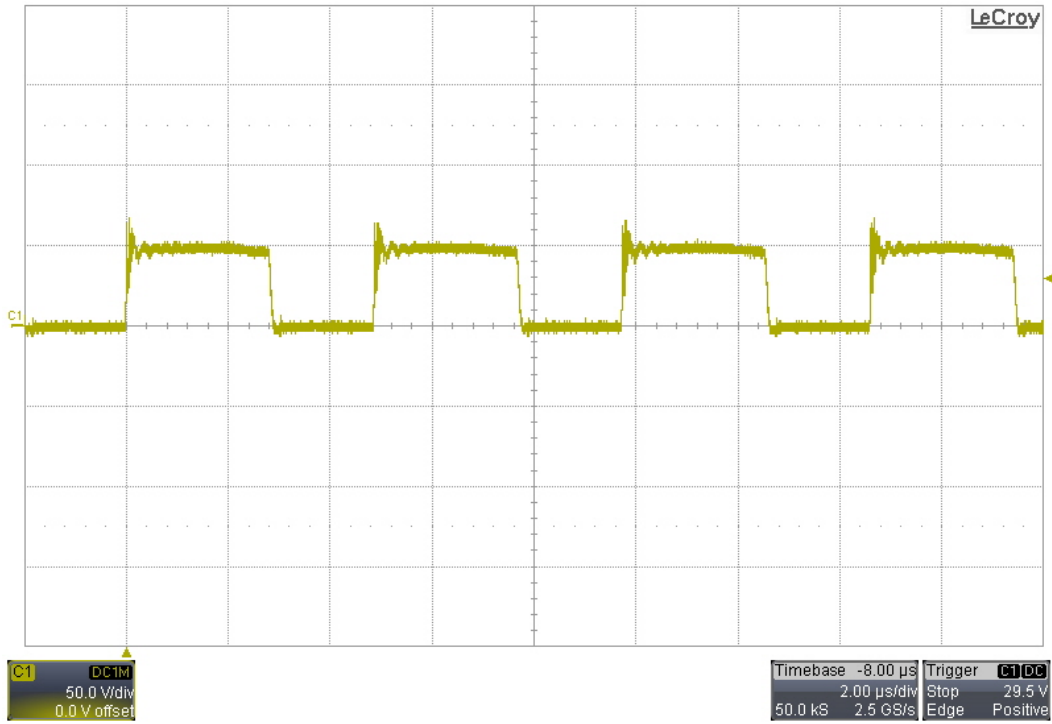
## 10.3 Q10 Synchronous FET Vds – 400VDC Input, 3.6A Load



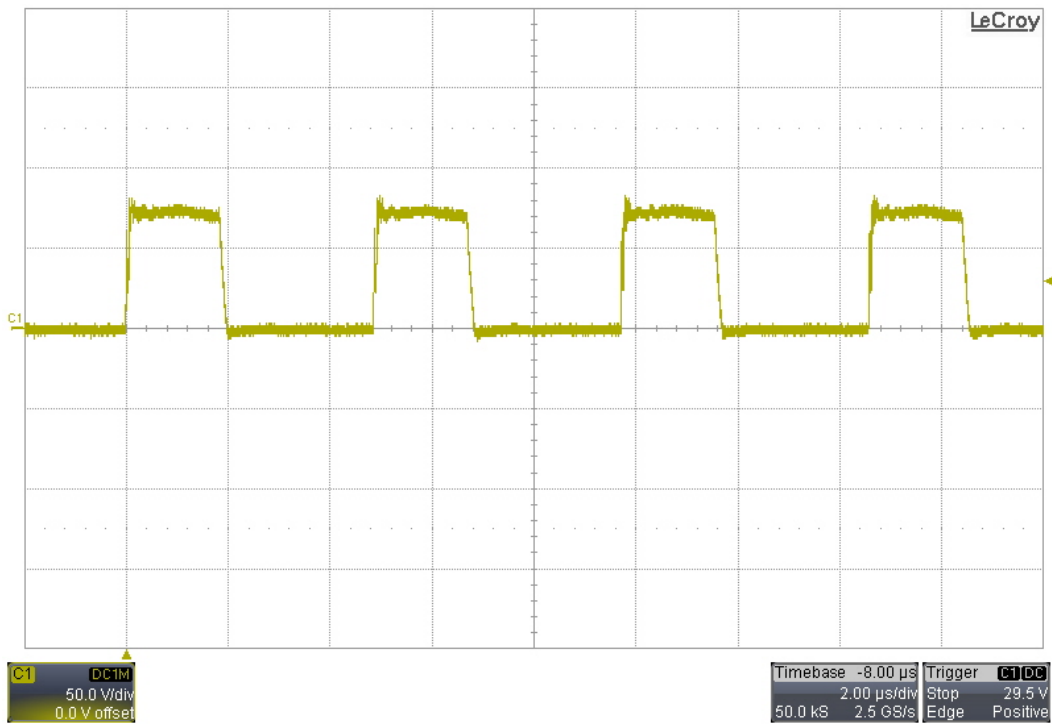
## 10.4 Q10 Synchronous FET Vds – 250VDC Input, 3.6A Load


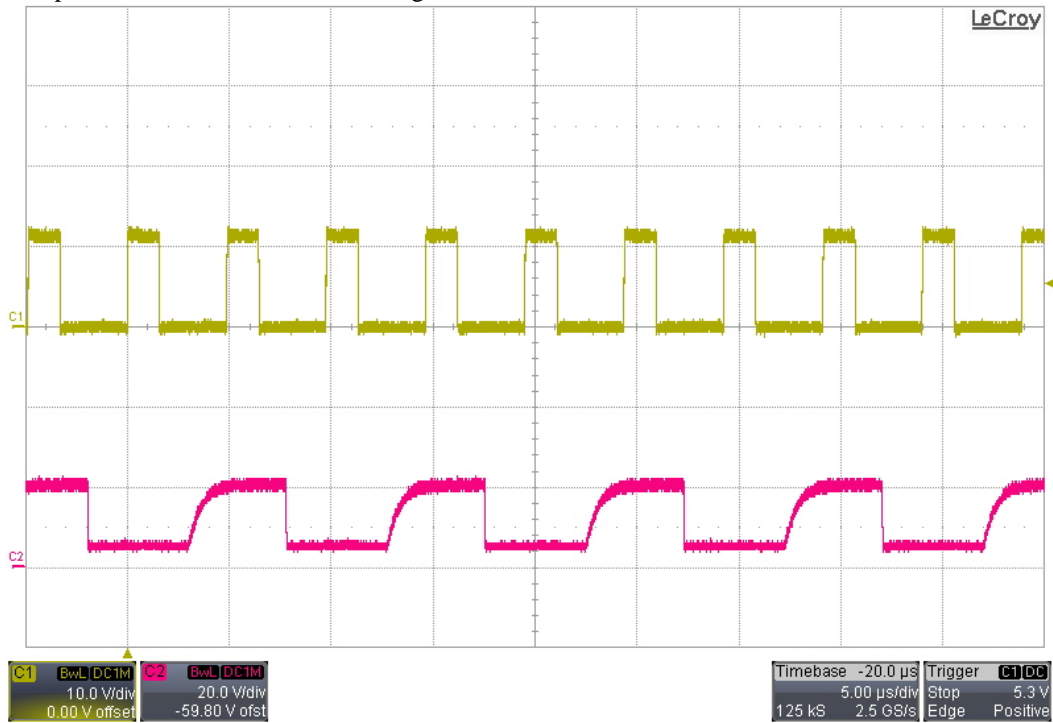
## 11 Synchronization Output

Channel 1 shows the voltage on the gate of the primary FET (Q9). Channel 2 shows the sync output (TP5). The sync output signal was pulled up to an external 20V source through a 30k resistor.



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated