

PMP40041 Test Results

1. Efficiency

Vin=5.5V

	Vin(V)	Iin(A)	Vo1(V)	Io1(A)	Vo2(V)	Io2(A)	Vo3(V)	Io3(A)	Effi.(%)
Half Load	5.466	1.130	1.008	2.5	1.005	1.5	1.005	1.0	81.5
Full Load	5.423	2.689	1.012	5.0	1.010	3.0	1.010	2.0	69.3

Vin=12V

	Vin(V)	Iin(A)	Vo1(V)	Io1(A)	Vo2(V)	Io2(A)	Vo3(V)	Io3(A)	Effi.(%)
Half Load	11.98	0.617	1.07	2.5	1.001	1.5	1.004	1	70.1
Full Load	11.96	1.243	1.001	5	1.005	3	1.001	2	67.4

2. Line and Load Regulation

Vin	4.5V		5.5V		6V	
Load	Io1=0A Io2=Io3=0A	Io1=0A Io2=3A Io3=2A	Io1=0A Io2=Io3=0A	Io1=0A Io2=3A Io3=2A	Io1=0A Io2=Io3=0A	Io1=0A Io2=3A Io3=2A
Vout1	1.008V	1.011V	1.008V	1.008V	1.008V	1.007V

Vin	4.5V		5.5V		6V	
Load	Io2=0A Io1=Io3=0A	Io2=0A Io1=5A Io3=2A	Io2=0A Io1=Io3=0A	Io2=0A Io1=5A Io3=2A	Io2=0A Io1=Io3=0A	Io2=0A Io1=5A Io3=2A
Vout2	1.809V	1.822V	1.809V	1.813V	1.808V	1.811V

Vin	4.5V		5.5V		6V	
Load	Io3=0A Io1=Io2=0A	Io3=0A Io1=5A Io2=3A	Io3=0A Io1=Io2=0A	Io3=0A Io1=5A Io2=3A	Io3=0A Io1=Io2=0A	Io3=0A Io1=5A Io2=3A
Vout3	3.343V	3.374V	3.344V	3.362V	3.343V	3.345V


Vin	7.8V		12V		14V	
Load	Io1=0A Io2=Io3=0A	Io1=0A Io2=3A Io3=2A	Io1=0A Io2=Io3=0A	Io1=0A Io2=3A Io3=2A	Io1=0A Io2=Io3=0A	Io1=0A Io2=3A Io3=2A


Vout1	1.014V	1.012V	1.013V	1.011V	1.012V	1.011V
-------	--------	--------	--------	--------	--------	--------


Vin	7.8V		12V		14V	
Load	Io2=0A Io1=Io3=0A	Io2=0A Io1=5A Io3=2A	Io2=0A Io1=Io3=0A	Io2=0A Io1=5A Io3=2A	Io2=0A Io1=Io3=0A	Io2=0A Io1=5A Io3=2A
Vout2	1.805V	1.804V	1.804V	1.803V	1.805V	1.805V

Vin	7.8V		12V		14V	
Load	Io3=0A Io1=Io2=0A	Io3=0A Io1=5A Io2=3A	Io3=0A Io1=Io2=0A	Io3=0A Io1=5A Io2=3A	Io3=0A Io1=Io2=0A	Io3=0A Io1=5A Io2=3A
Vout3	3.322V	3.322V	3.323V	3.324V	3.322V	3.315V


3. Ripple and noise

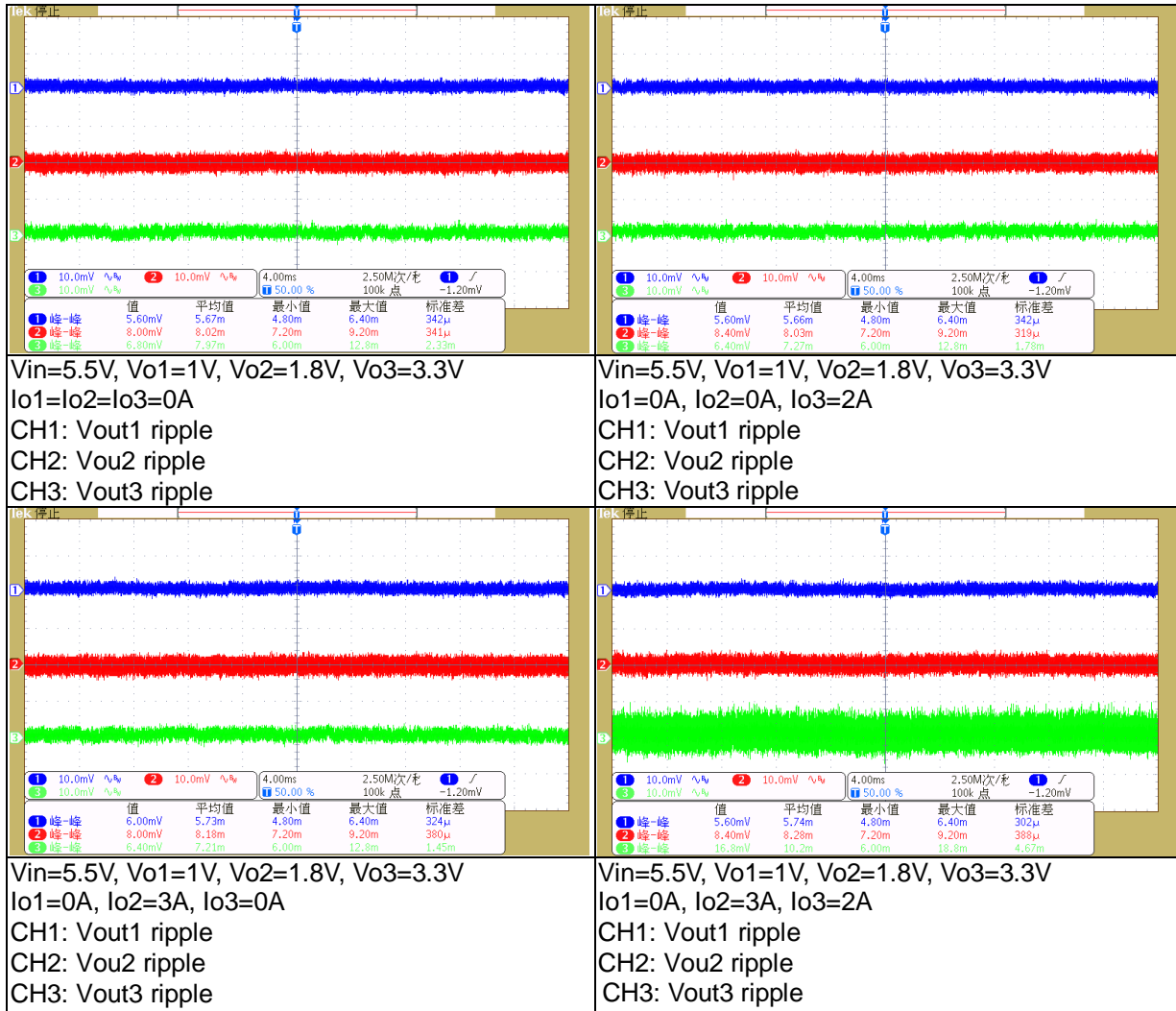

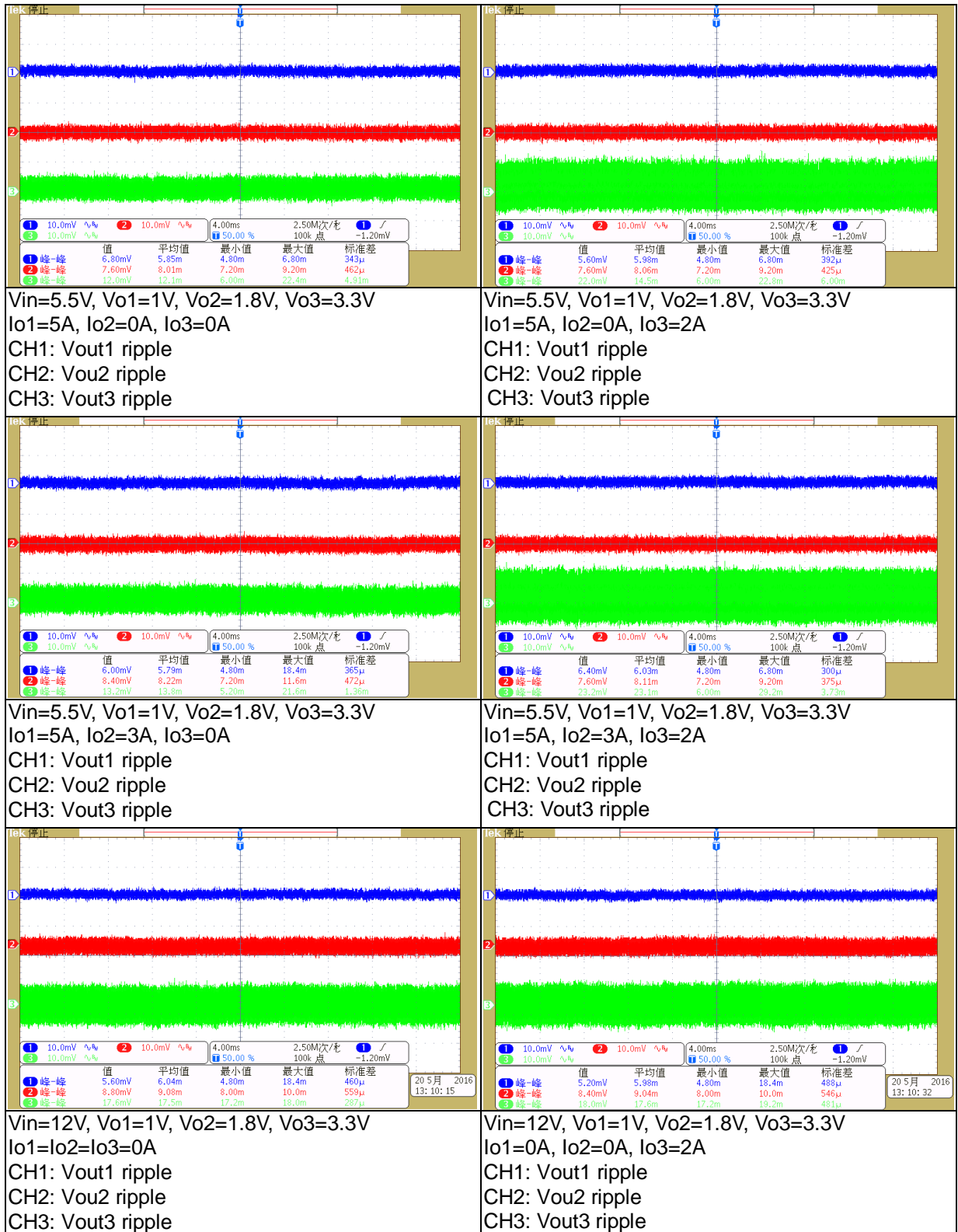


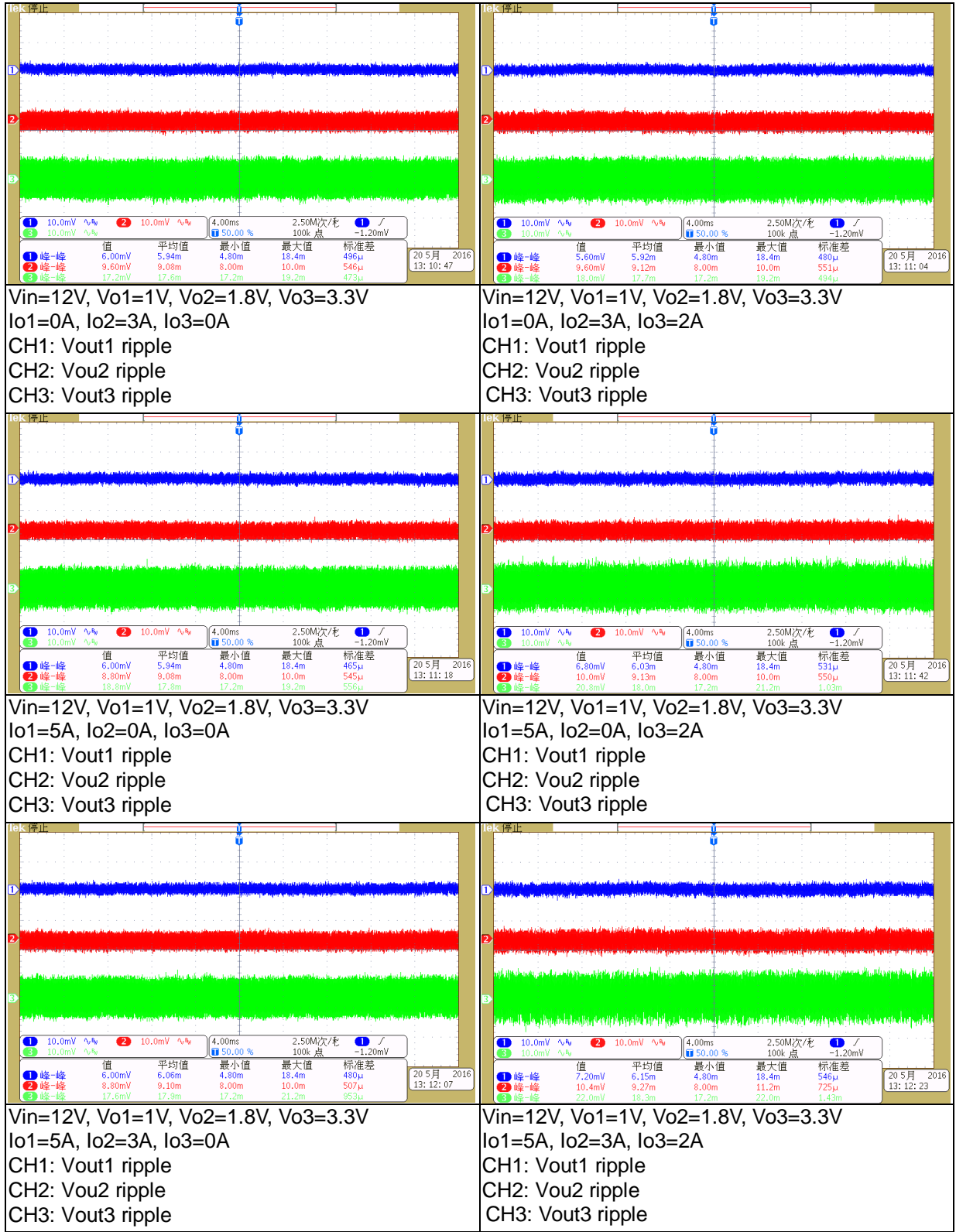


4. Start up

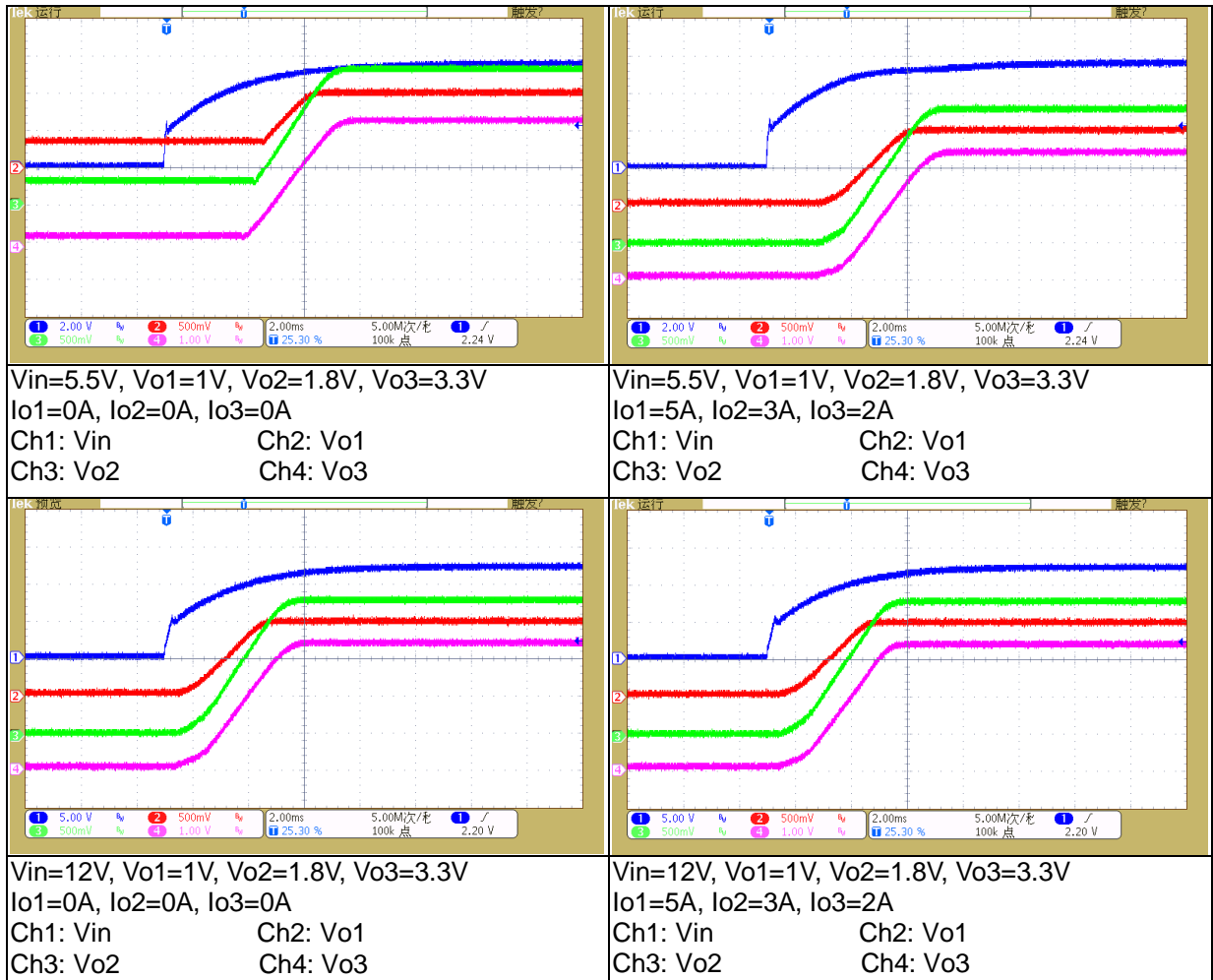



5. Shut down

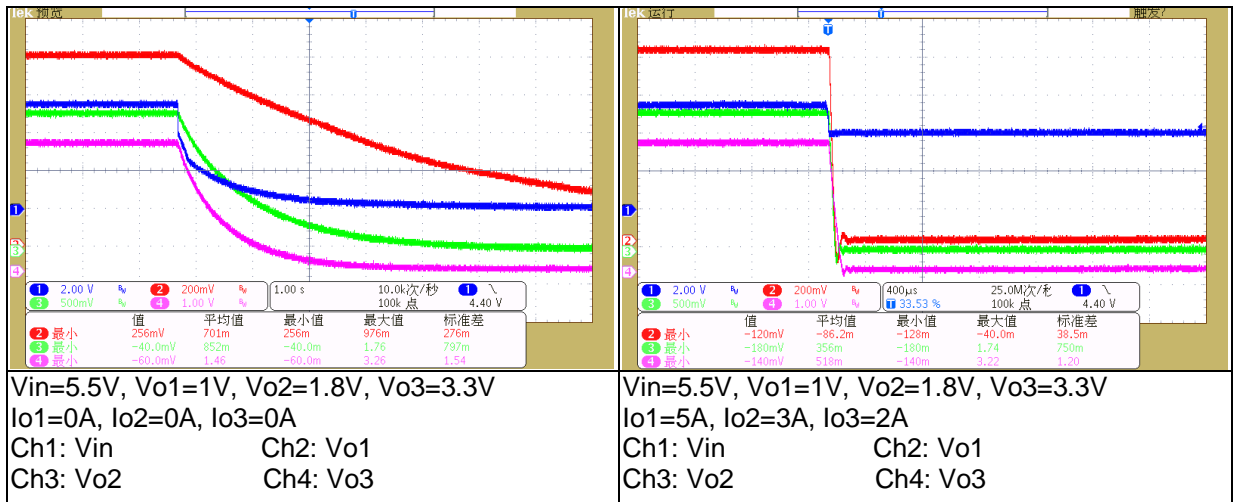

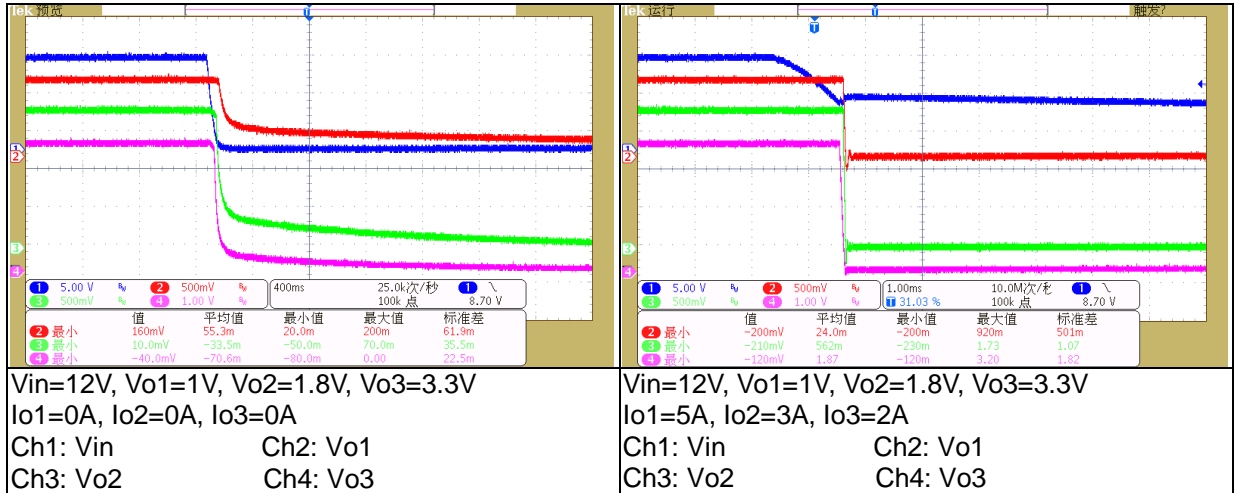



6. OCP

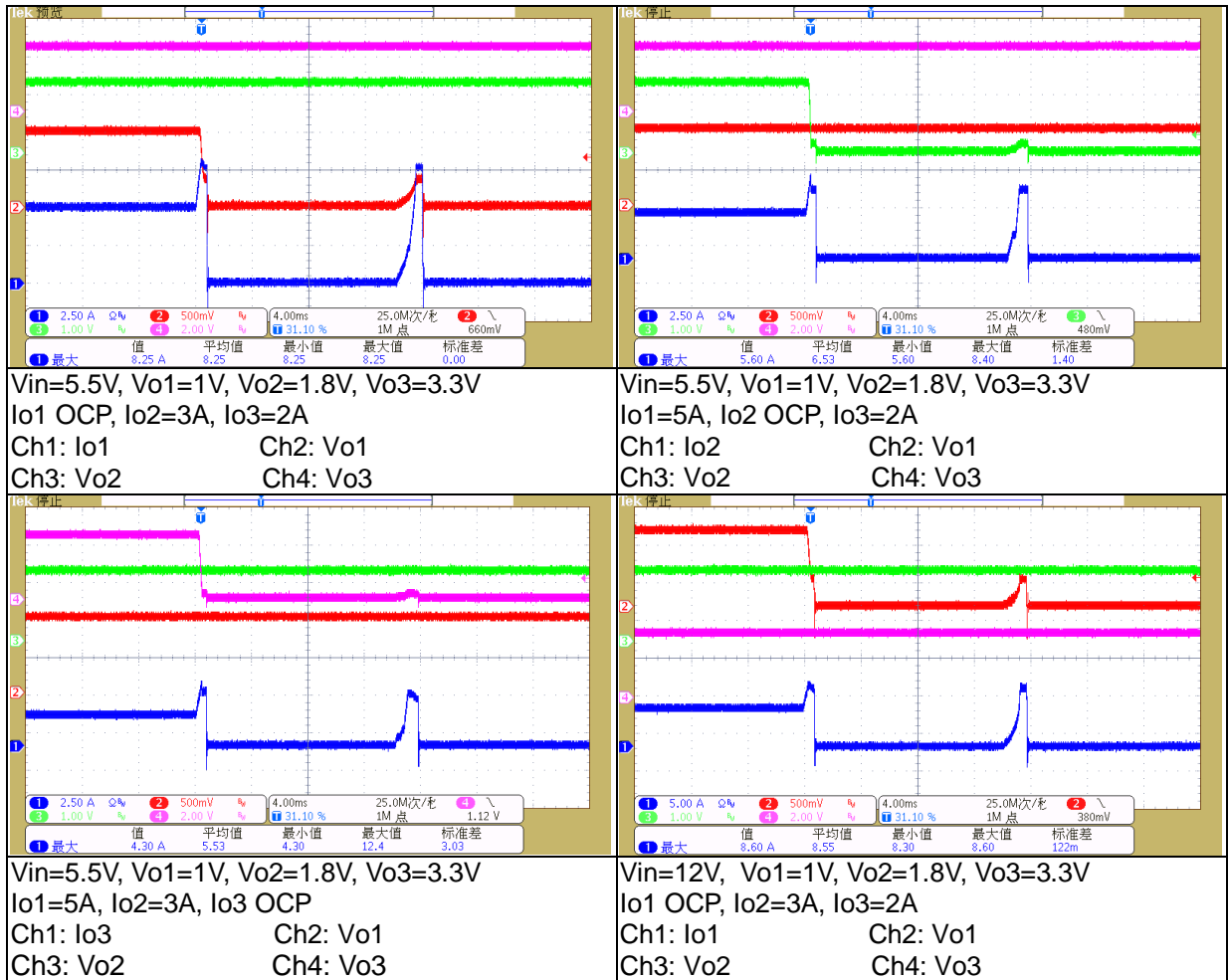

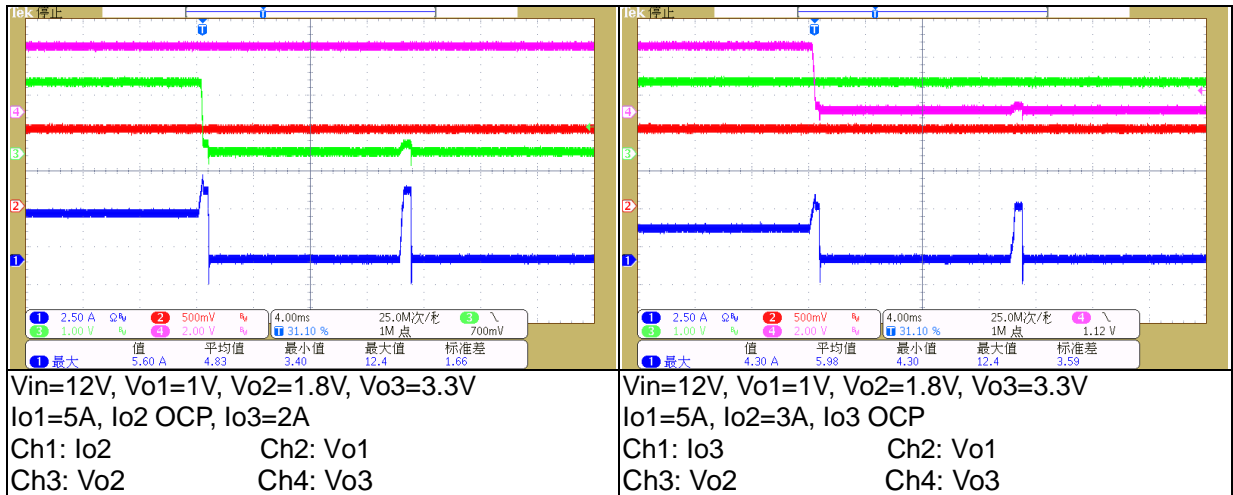


7. Load Transient

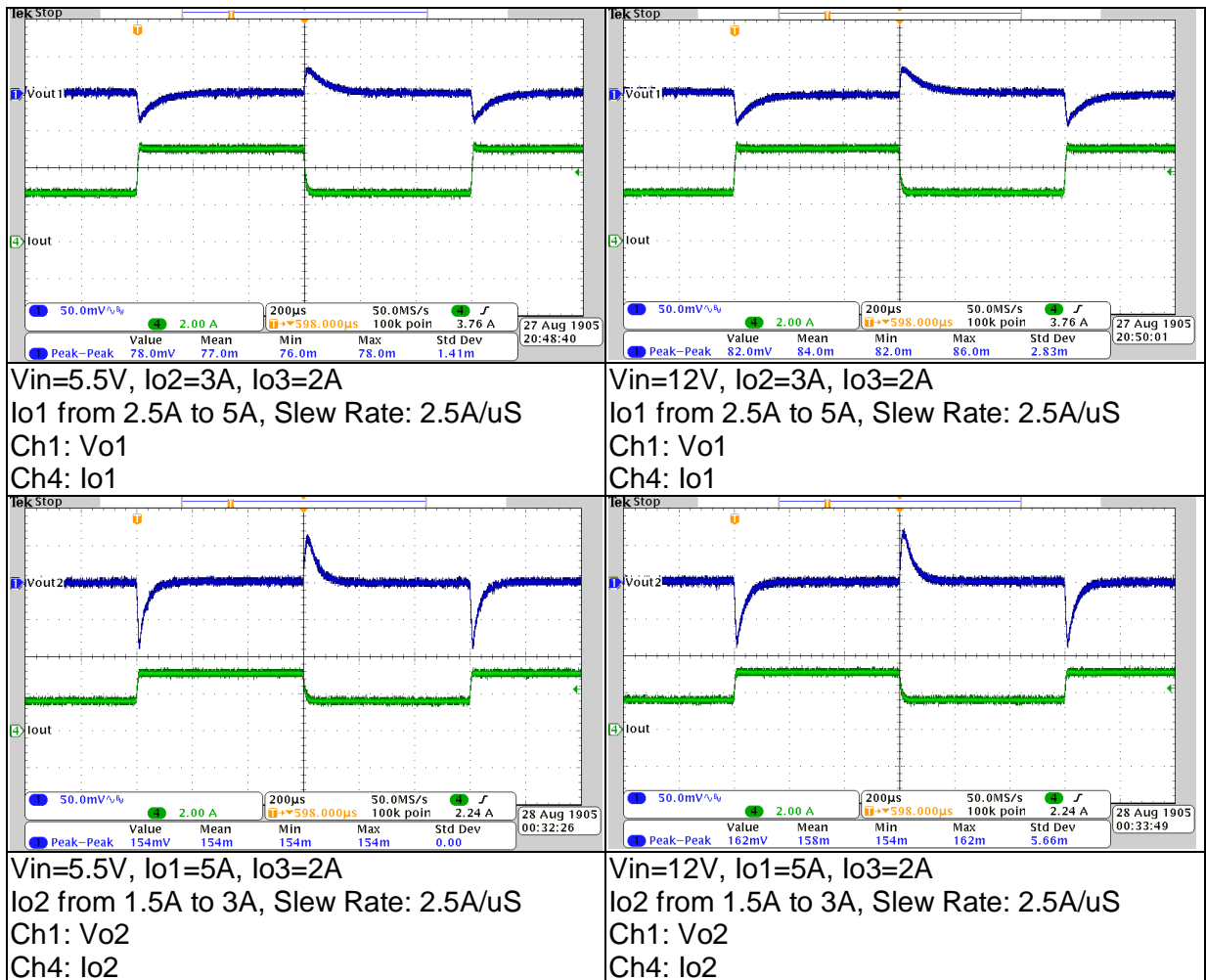


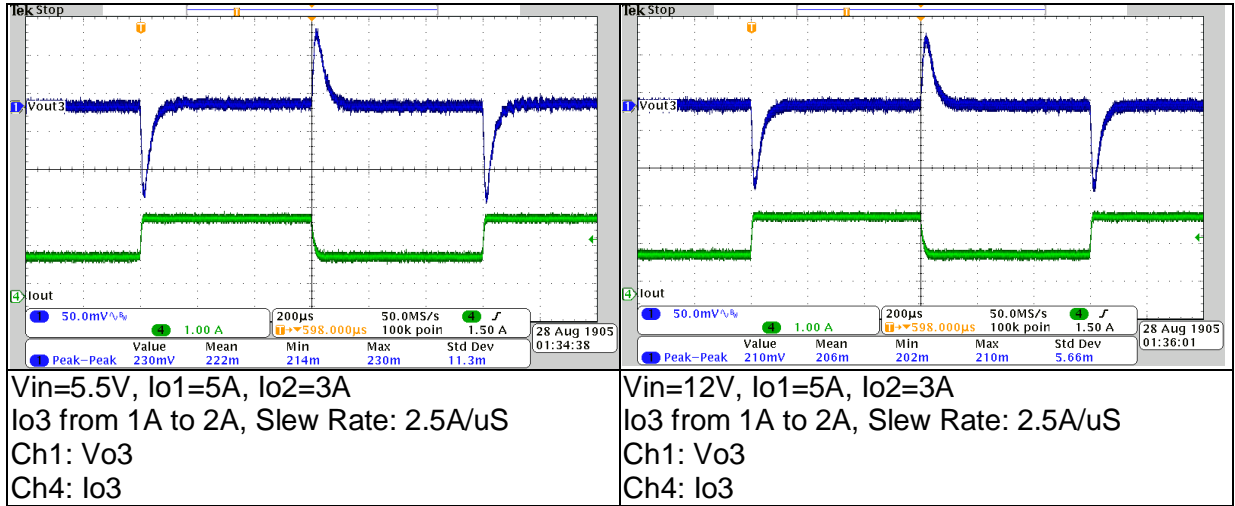


8. Bode Plot

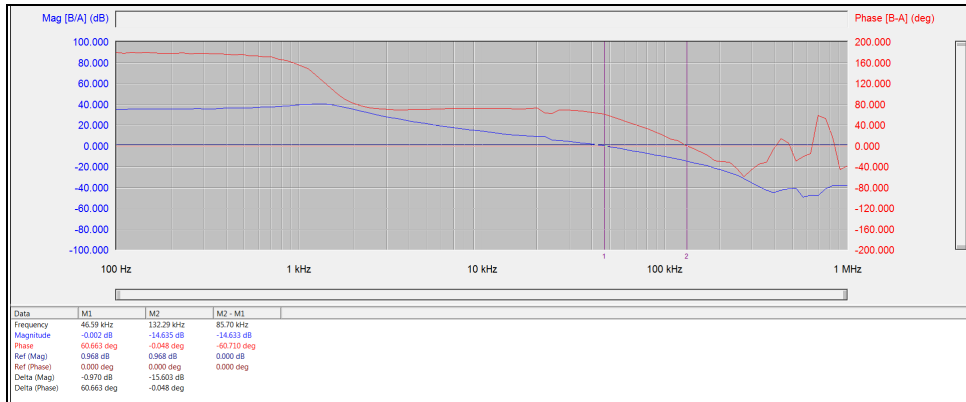

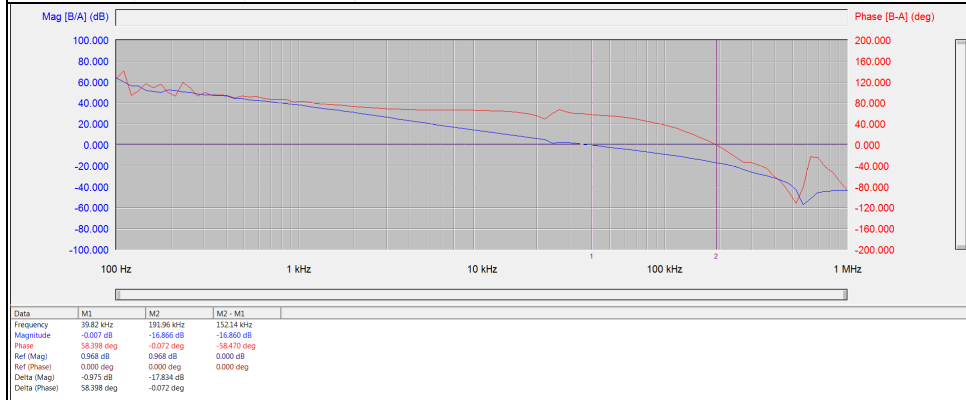
VOUT1 bode plot
 $V_{in}=5.5V$, $I_{o1}=5A$, $I_{o2}=3A$, $I_{o3}=2A$



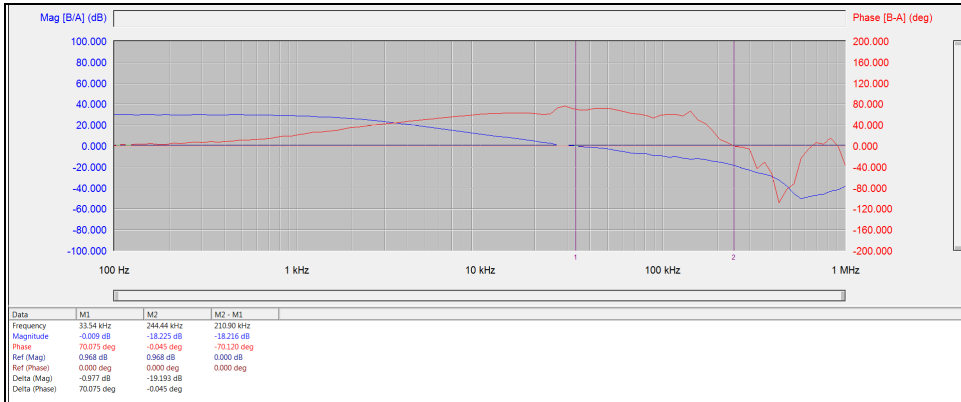
VOUT2 bode plot
 $V_{in}=5.5V$, $I_{o1}=5A$, $I_{o2}=3A$, $I_{o3}=2A$



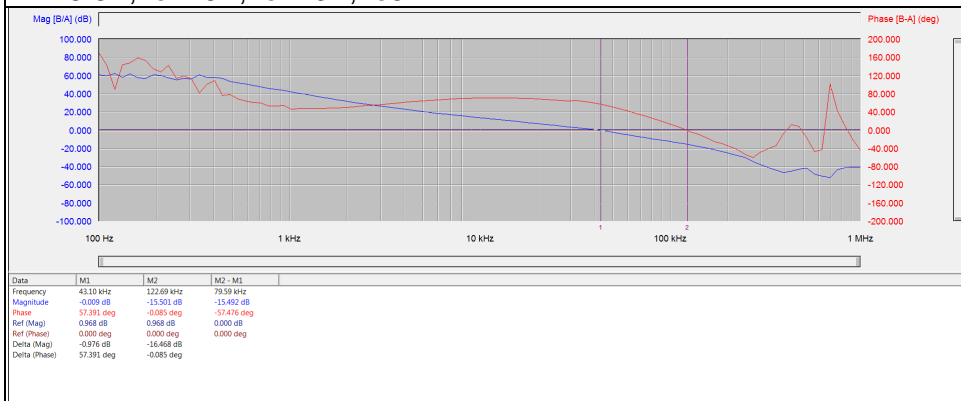
VOUT3 bode plot
 Vin=5.5V, Io1=5A, Io2=3A, Io3=2A



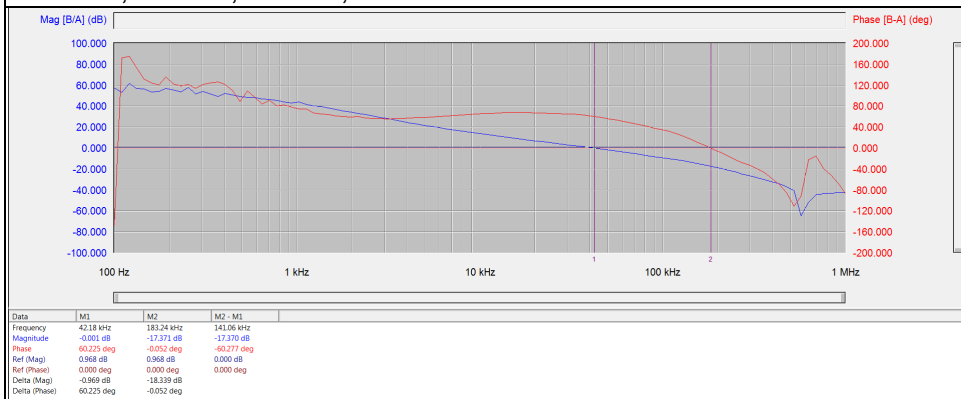VOUT1 bode plot
 Vin=12V, Io1=5A, Io2=3A, Io3=2A



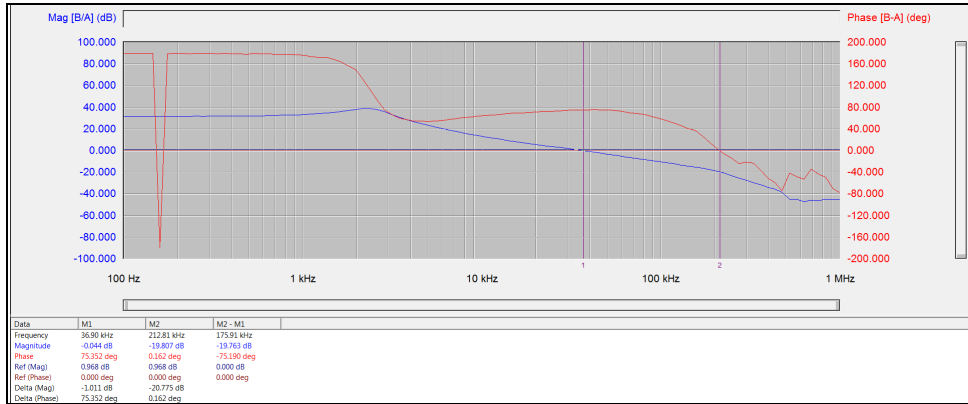VOUT2 bode plot
 Vin=12V, Io1=5A, Io2=3A, Io3=2A



VOUT3 bode plot

Vin=12V, Io1=5A, Io2=3A, Io3=2A

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated